

Implementing a Variable-Length Cat5e Cable Equalizer

Xavier Ramus
Abhijeet Godbole

*High-Speed Products
Power Design Group*

ABSTRACT

Unshielded twisted pair (UTP) cables have long been used to transmit data over long distances, starting with telephone line networks. As a result of the relatively low cost, these cables have also been adopted for various uses including video distribution. All UTP cables attenuate the signal over frequency with maximum attenuation at maximum signal frequency. This attenuation will also increase as the cable length increases. This application note focuses on a continuously-adaptable equalization technique of Category-5 enhanced (Cat5e) cable for applications intended to be used with various length of Cat5e cable. As an example, a voltage-controlled amplifier (VCA) implementation is developed for standard video distribution for distances up to 500 feet (152.4 m).

Contents

1	Introduction	1
2	Cat5e Cable Attenuation Characteristics	2
3	Equalizer Circuit Description	3
4	Physical Implementation	6
5	Results and Discussion	8
6	Conclusion	11

List of Figures

1	Typical Attenuation Characteristics of Cat5e Cable	2
2	VCA822 Internal Schematic	3
3	Equalizer Circuit Using the VCA822.....	4
4	Analysis Schematic	5
5	Frequency Response of the Circuit for Various Gain Voltage Combinations	6
6	Evaluation Board Layout (Top View): (a) Top Layer, (b) Mid Layer 1; (c) Mid Layer 2; (d) Bottom Layer.....	7
7	Schematic	8
8	Equalized AC Responses for Different Lengths of Cat5e Cable	9
9	Differential Gain (a) and Differential Phase (b) Measurements for 500ft Cat5e Cable.....	10

1 Introduction

Cat5e cable consists of four twisted pairs of wire that allows a red (R), green (G), and blue (B) signal on each of three lines, freeing the fourth line to transmit audio, timing, or control signals.

In theory, equalization techniques can be used at either the transmit (Tx) or receive (Rx) amplifier. In practice, however, equalization is generally used on the Rx side in order to limit noise and maximize signal-to-noise ratio (SNR). This practice imposes a flatness requirement on the Tx side. For more information on the Tx side and its interaction with the Rx side, refer to the Texas Instruments application report, *Wireline Data Transmission and Reception* (literature number [SBOA123](#)).

Focusing only on the Rx side for the balance of this report, we will start by looking at the Cat5e transmission media characteristics; then we will consider the proposed implementation based on the [VCA822](#); and finally, we implement and evaluate the circuit.

All trademarks are the property of their respective owners.

2 Cat5e Cable Attenuation Characteristics

[Table 1](#) shows the typical electrical characteristics of Cat5e cable.

Table 1. Electrical Characteristics for Cat5e UTP Cable

Property	Nominal Value	Tolerance	Units
Characteristic impedance at 100MHz	100	± 15	Ω
Nominal characteristic impedance at 100MHz	100	± 5	Ω
DC-loop resistance	≤ 0.188		Ω/m
Capacitance at 800Hz	52		pF/m
Inductance	525		nH/m

The characteristic impedance for a lossless transmission line is given by [Equation 1](#):

$$Z_0 = \sqrt{\frac{L}{C}} \quad (1)$$

Applying [Equation 1](#) to the typical cable inductance and capacitance (from [Table 1](#)), we find that it is equal to 100.5Ω .

For the Sewell Cat5e cable used for this project, the frequency responses for various cable lengths are shown in [Figure 1](#).

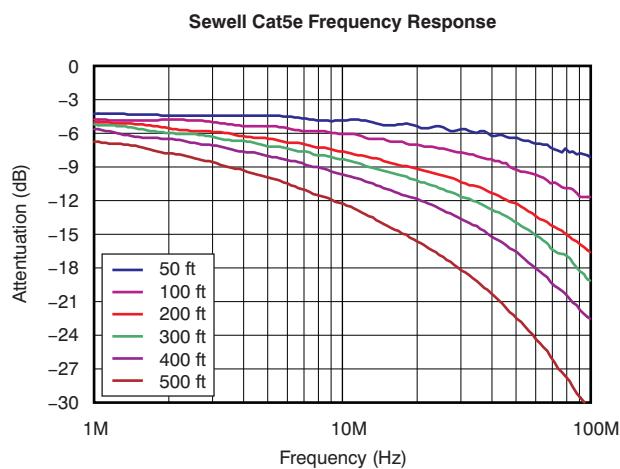


Figure 1. Typical Attenuation Characteristics of Cat5e Cable

Using TI application report [SBOA124](#), *A Numerical Solution to an Analog Problem*, as a starting point, we can determine the pole location associated with the longest cable length. This network determines the maximum attenuation for which the circuit can compensate. It is understood that this calculated network may need some adjustment to actual component values and test environments.

3 Equalizer Circuit Description

A differential cable equalizer can be easily implemented using a voltage-controlled amplifier (VCA). Texas Instruments offer a selection of high-speed VCAs (as shown in [Table 2](#)) that could be used in this application.

Table 2. VCA82x Device Comparison

Device	Bandwidth ($G = 2V/V$)	Comments
VCA820	168MHz	Linear in dB Gain control
VCA821	710MHz	Linear in dB Gain control
VCA822	168MHz	Linear in V/V Gain control
VCA824	710MHz	Linear in V/V Gain control

The VCA selected for this investigation is the VCA822, a wideband, variable gain amplifier. For the VCA822, the maximum gain is set by using independent feedback and gain resistors, and the gain control voltage attenuates the signal from the maximum gain. The gain-adjust range for the VCA822 is 40dB. [Figure 2](#) illustrates the internal schematic of the VCA822.

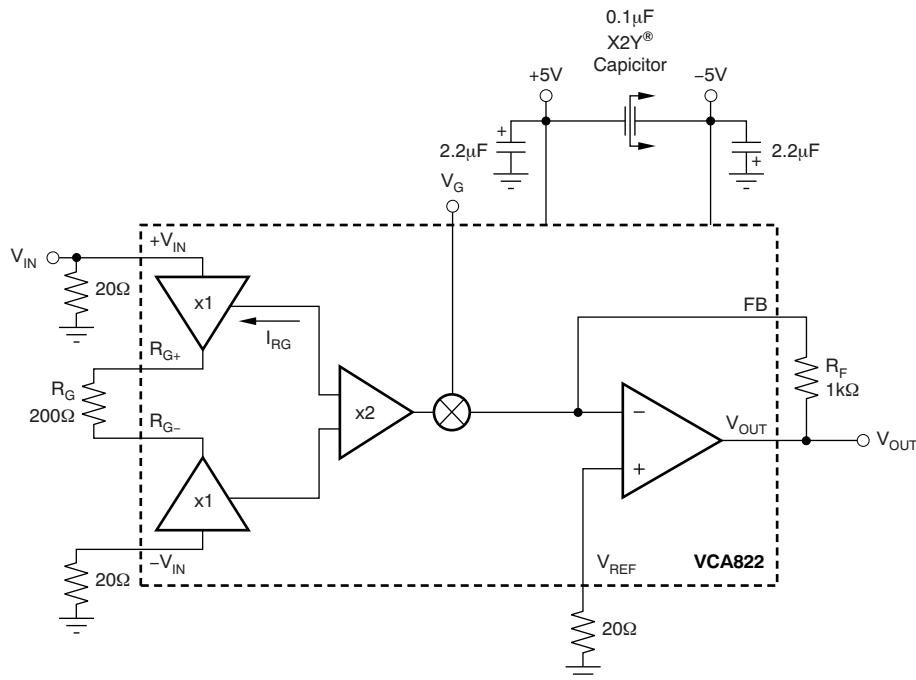


Figure 2. VCA822 Internal Schematic

The VCA822 input stage places the transconductance element between two input buffers, using the output currents as the forward signal. As the differential input voltage increases, a signal current is generated through the gain element. This current is then mirrored and gained by a factor of two before reaching the multiplier. The other input of the multiplier is the voltage gain control pin, V_G . Depending on the voltage present on V_G , up to two times the gain current is provided to the transimpedance output stage. The transimpedance output stage is a current-feedback amplifier that provides the high output current and high slew rate capability.

The proposed schematic for the Cat5e cable equalizer is shown in [Figure 3](#).

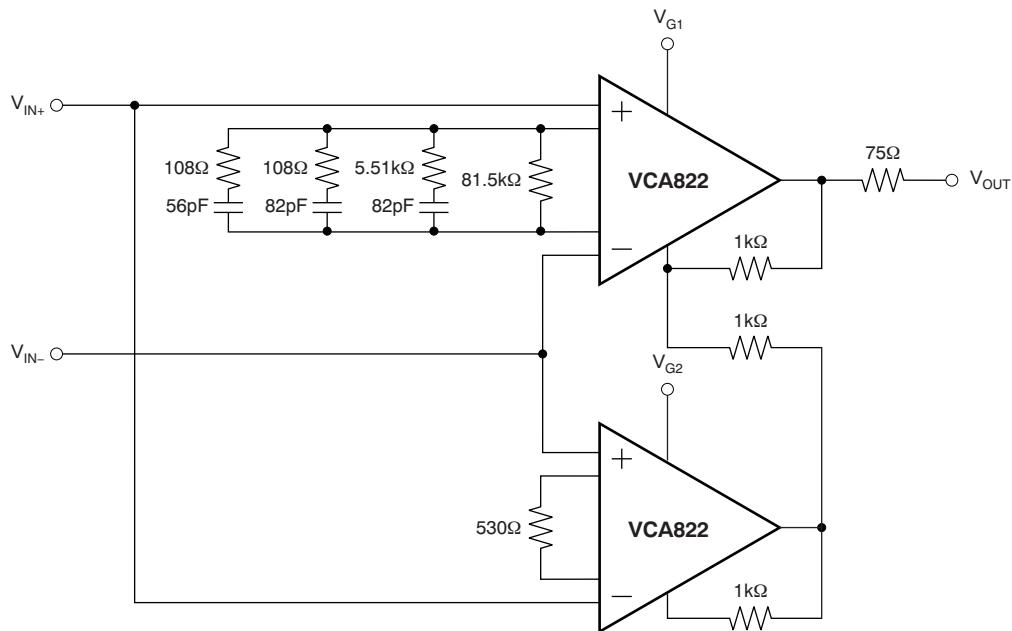


Figure 3. Equalizer Circuit Using the VCA822

This circuit uses two VCA822s and takes advantage of the high impedance nature of both devices. Notice that the top VCA is connected in a noninverting configuration while the bottom VCA is connected in an inverting configuration. The signal passing through the inverting amplifier is inverted again before finding its way to the output. Remember that the output stage of the VCA822 is an operational amplifier; therefore, if a gain resistor is used in conjunction with a feedback resistor, the resulting signal is inverted in relation to the output. In the example shown in [Figure 3](#), both feedback and gain resistors have the same value; thus, the bottom VCA822 has its gain inverted by this configuration to the output of the top VCA device.

Additionally, the bottom VCA is amplified by a fixed gain over frequency while the top VCA has an equalization circuit to set the gain. Note that the resistor setting the dc gain for the equalization VCA is very large compared to the feedback resistor, resulting in a small gain at dc. To understand the behavior of this circuit, we will analyze it in two steps by successively eliminating one amplifier from the equation by adjusting the gain control voltage.

Because the VCA822 has a 40dB gain adjust range, it can attenuate the maximum gain by 40dB. Keep in mind that by setting the gain of the first VCA in the equalization circuit, you eliminate (in effect) the signal that passes through the noninverting amplifier. Referring to [Figure 4](#), then, the gain for each case is shown in the subsequent section.

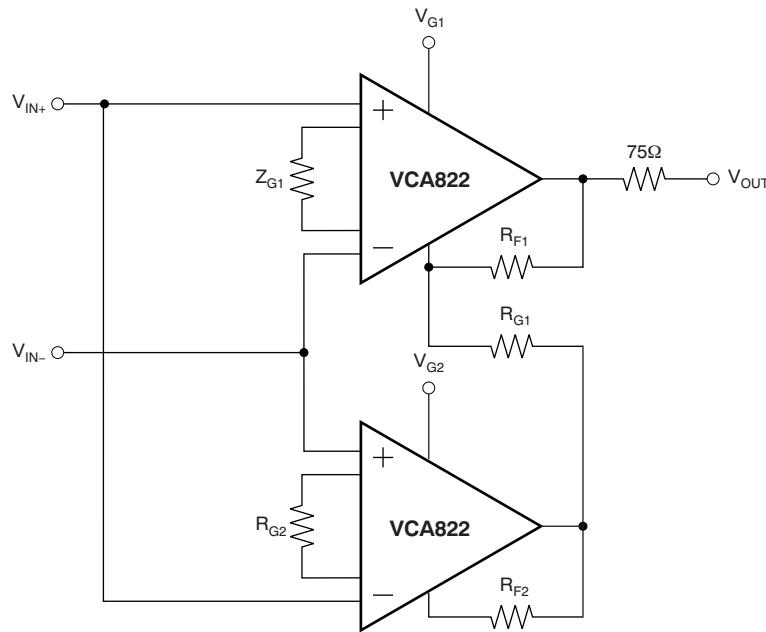


Figure 4. Analysis Schematic

3.1 Gain-Setting Examples

Case #1

$V_{G1} = -1V$ (input signal fully attenuated); $V_{G2} = 1V$ (input signal at maximum gain)

$$\frac{V_{OUT}}{V_{IN+} - V_{IN-}} = \frac{R_{F1}}{R_{G1}} \cdot \frac{R_{F2}}{R_{G2}} \cdot (V_{G2} + 1) \quad (2)$$

Case #2

$V_{G1} = 1V$ (input signal at max gain); $V_{G2} = -1V$ (input signal fully attenuated)

$$\frac{V_{OUT}}{V_{IN+} - V_{IN-}} = \frac{R_{F1}}{Z_{G1}} \cdot (V_{G1} + 1) \quad (3)$$

It is now possible to see that by simply combining [Equation 2](#) and [Equation 3](#) by superposition, the gain equation for this circuit appears as [Equation 4](#).

$$\frac{V_{OUT}}{V_{IN+} - V_{IN-}} = \frac{R_{F1}}{R_{G1}} \cdot \frac{R_{F2}}{R_{G2}} \cdot (V_{G2} + 1) + \frac{R_{F1}}{Z_{G1}} \cdot (V_{G1} + 1) \quad (4)$$

From the circuit in [Figure 3](#), we can see that the poles have been located at 350kHz, 1.8MHz, and 26.3MHz. To summarize, at frequencies less than 350kHz, the gain equation ([Equation 4](#)) is dominated by the bottom VCA, while it is dominated by the top VCA (the equalizer circuit) at frequencies above 350kHz. The gain control voltage (V_{G1} and V_{G2} , respectively) allow the designer to have full control on the total contribution of each amplifier. This characteristic enables this circuit to adjust the required equalization for various Cat5e cable lengths.

The frequency responses of Case #1 and Case #2 of this analysis, as well as a similar case where both VCAs are fully contributing to the output, are shown in [Figure 5](#).

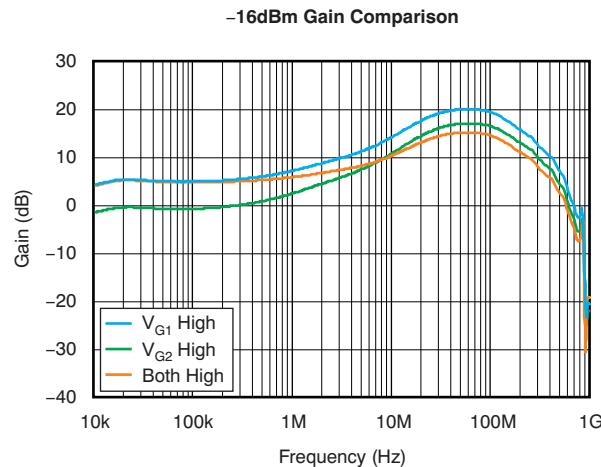


Figure 5. Frequency Response of the Circuit for Various Gain Voltage Combinations

4 Physical Implementation

The circuit shown in [Figure 3](#) was implemented using two VCA822ID amplifiers. The layout for this design is illustrated in [Figure 6](#).

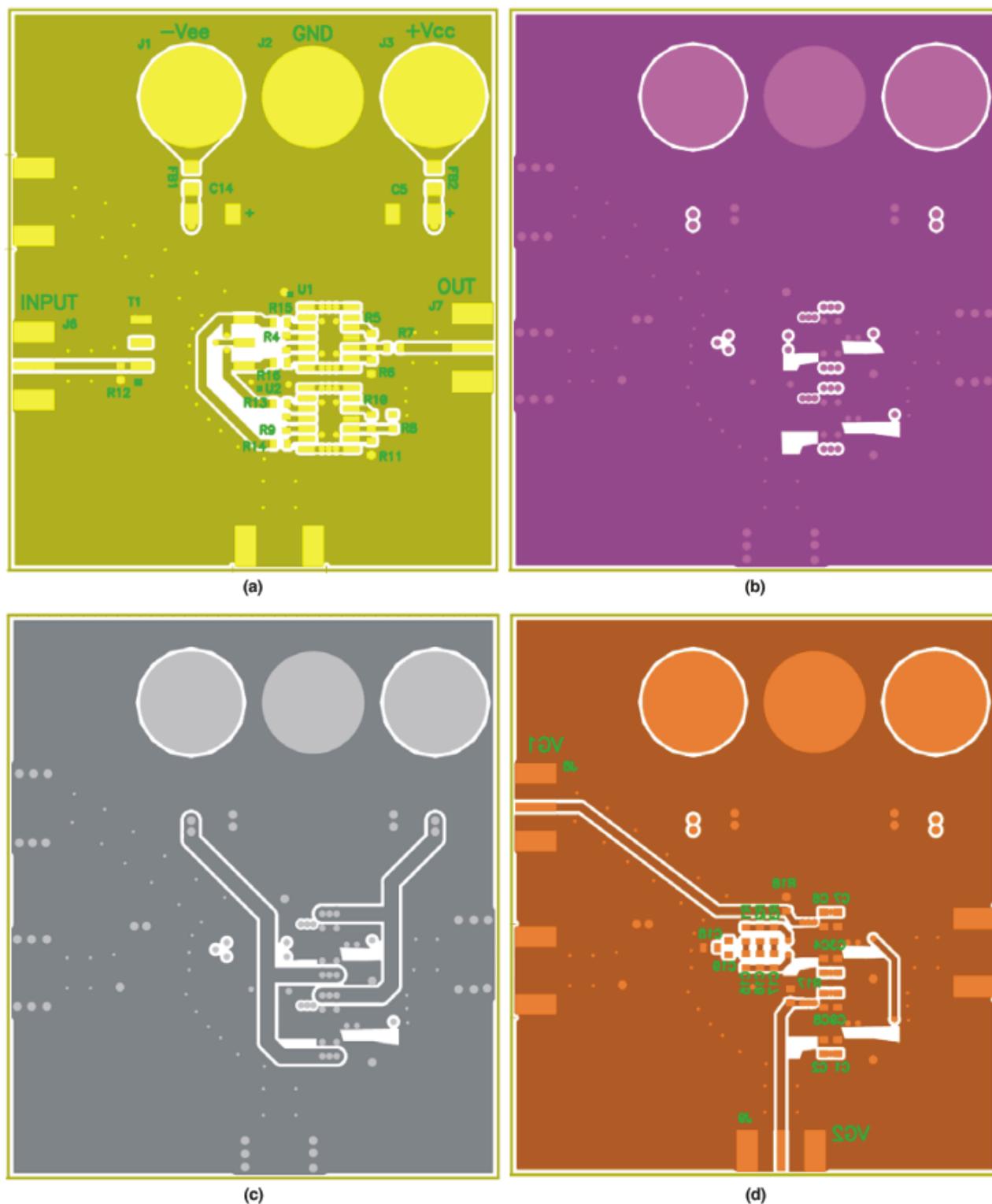


Figure 6. Evaluation Board Layout (Top View): (a) Top Layer, (b) Mid Layer 1; (c) Mid Layer 2; (d) Bottom Layer

This layout is implemented with a four-layer printed circuit board (PCB). Components are placed on both top and bottom layers, with the ground and power supply on the mid layers. Ground filling is also used on the top and bottom layers.

The schematic associated with this layout is given in [Figure 7](#). We can see that four $0.1\mu F$ bypass capacitors are used for each VCA because of the number of supply pins for the SO-14 package. Several placeholder capacitors are also set for each of the gain control voltage pins, V_{G1} and V_{G2} . The input is connected through a transformer to emulate a fully differential signal driving the high-impedance input stage of the VCA822. The equalization circuit described earlier can be seen on the bottom layer.

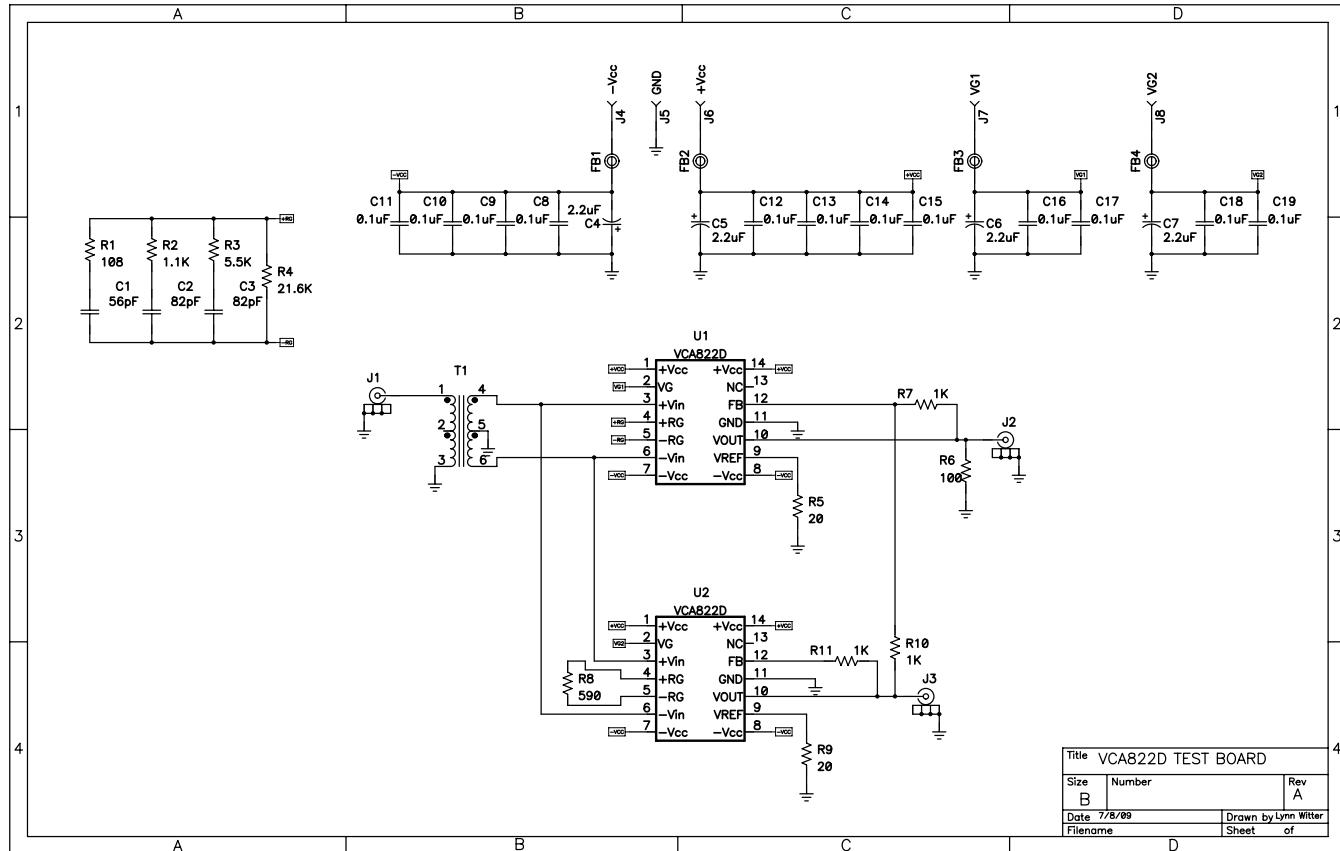


Figure 7. Schematic

5 Results and Discussion

5.1 Frequency Domain Analysis

The primary objective of the equalizer circuit is to shape the frequency response in order to compensate for the Cat5e cable loss. Different cable lengths cause different levels of attenuation, with the longest cable length showing the worst attenuation.

This circuit was tested for six different cable lengths varying from 50ft to 500ft. The gain control voltage of the amplifiers was adjusted for each cable length, such that the amplifier output remains constant at $1V_{PP}$ over the desired frequency band (0Hz to 20MHz). [Table 3](#) shows the various gain voltage combinations for different lengths of cable. [Figure 8](#) shows the equalized response with different cables inserted in the signal path. [Figure 8](#) also shows that independent of the cable length, good flatness to greater than 20MHz is achieved by this circuit. Further improvement may be achieved by using the higher bandwidth [VCA821](#) or [VCA824](#) devices.

From [Table 3](#), it is clear that for shorter cable lengths, it is not required to boost a high-frequency signal, whereas for longer cables, high frequencies require maximum compensation. As a result, the gain control voltage for the equalization VCA (U1 in [Figure 7](#)) is negative for shorter cable lengths. For the VCA822, the closer the gain control voltage is to $-1V$, the more this VCA is attenuating. The equalization VCA is, in this manner, removed from the loop. The longer the cable length, the more that U1 contributes to the output signal.

Table 3. Gain Control Voltage Settings for Different Lengths of Cat5e Cable

Cable Length (feet)	V_{G1}	V_{G2}
50	-0.5V	0.50V
100	-0.3V	0.55V
200	0.10V	0.65V
300	0.20V	0.70V
400	0.40V	0.80V
500	0.75V	0.85V

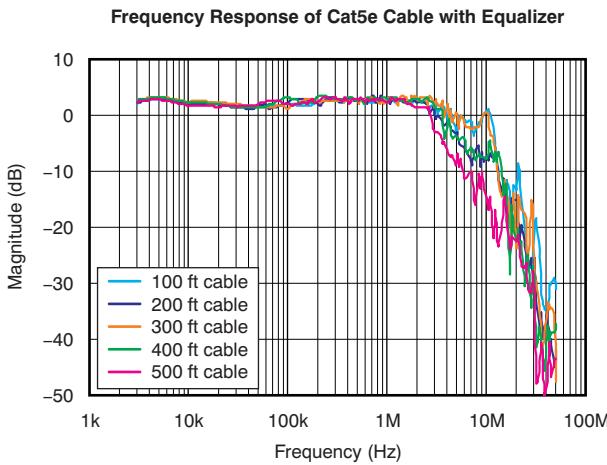


Figure 8. Equalized AC Responses for Different Lengths of Cat5e Cable

5.2 Differential Gain-Differential Phase Measurement (dGdP)

One of the most critical factors within a composite video system is how well an amplifier reproduces the composite video signal. Differential gain is the error in the amplitude of the color signal as a result of a change in luminance (or brightness) level. Differential phase is the error in the phase of the color signal because of a change in luminance level. This characteristic is usually specified as the parameter **dGdP** in amplifier data sheets.

Typically, amplifiers that have a dGdP error of less than 1% are considered to be good, because the human eye cannot discern the differences of color saturation if the differential gain error is 1% or lower.

In this test, we used the VM700T, a video test measurement instrument, to measure the dGdP of the equalizer circuit. A five-step modulated signal (NTSC format) from a video signal generator was used as the tested video signal. The dGdP error increased with the Cat5e cable length. The worst-case differential gain and differential phase error was 0.5% and 0.19% max, respectively, for a 500ft cable. [Figure 9](#) shows the dGdP responses for a 500ft cable.

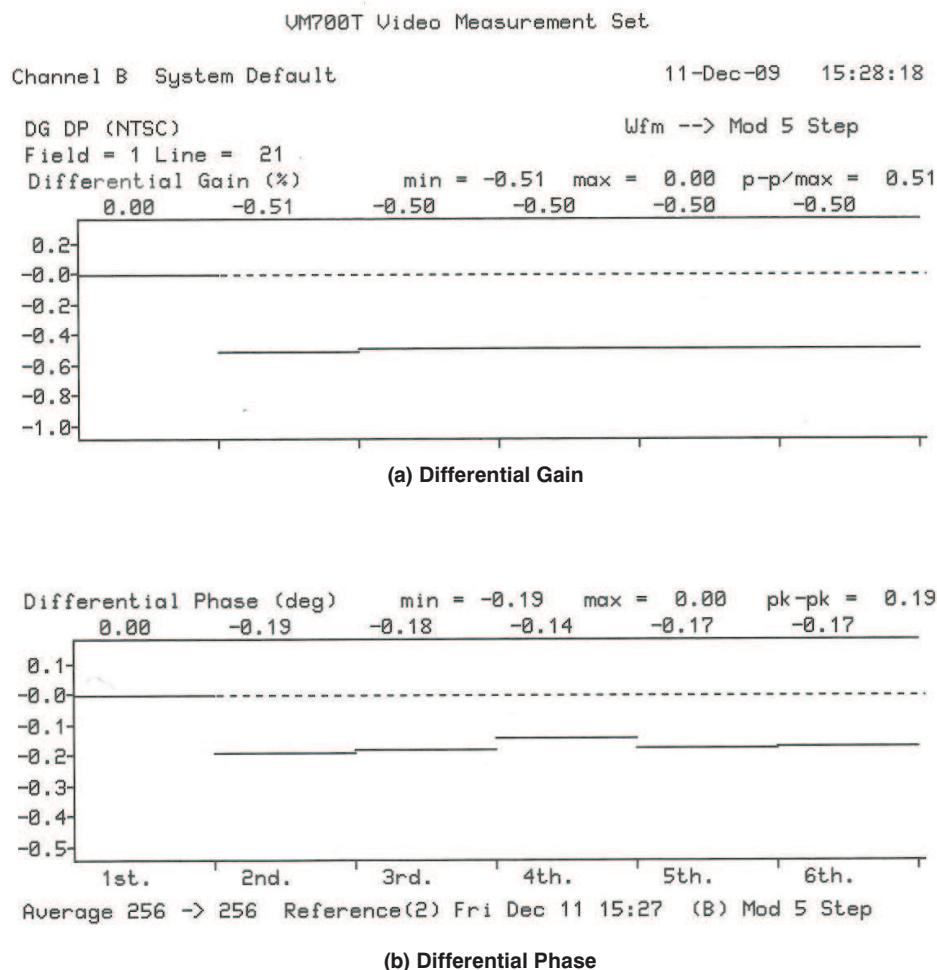


Figure 9. Differential Gain (a) and Differential Phase (b) Measurements for 500ft Cat5e Cable

6 Conclusion

Cat5e UTP cables are extensively used for communication wiring because of the low cost and performance characteristics. In this report, we implemented an adjustable equalizer for various Cat5e cable lengths that compensated the cable loss at high frequencies. An application for composite video signal using the VCA822, a wideband, variable gain amplifier, was implemented that clearly demonstrated how this equalizer circuit allows optimization for various cable lengths by adjusting the gain control voltage of both VCA components. This equalizer circuit was also tested for differential gain and phase performance, and found to be within the acceptable human tolerance limit.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Communications and Telecom	www.ti.com/communications
DSP	dsp.ti.com	Computers and Peripherals	www.ti.com/computers
Clocks and Timers	www.ti.com/clocks	Consumer Electronics	www.ti.com/consumer-apps
Interface	interface.ti.com	Energy	www.ti.com/energy
Logic	logic.ti.com	Industrial	www.ti.com/industrial
Power Mgmt	power.ti.com	Medical	www.ti.com/medical
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Space, Avionics & Defense	www.ti.com/space-avionics-defense
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless-apps