
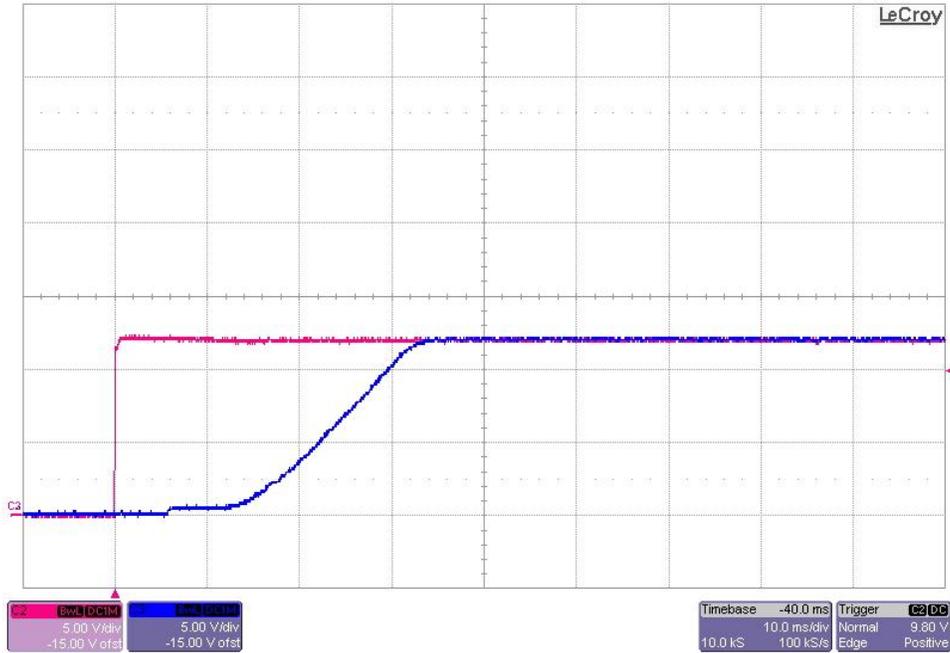


1 Startup

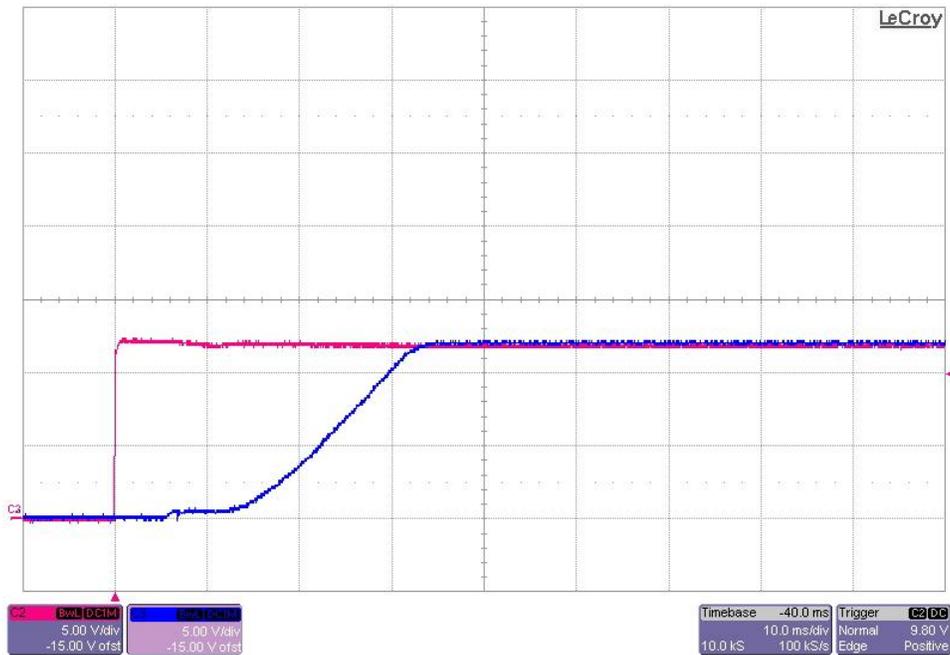
The photo below shows the 12V output voltage startup waveforms after the application of 12Vdc in. The output was loaded with a 0A resistive load. (Vin is 5V/DIV, Vout is 5V/DIV, 10mS/DIV)




The photo below shows the 12V output voltage startup waveforms after the application of 12Vdc in. The output was loaded with a 1A resistive load. (Vin is 5V/DIV, Vout is 5V/DIV, 10mS/DIV)



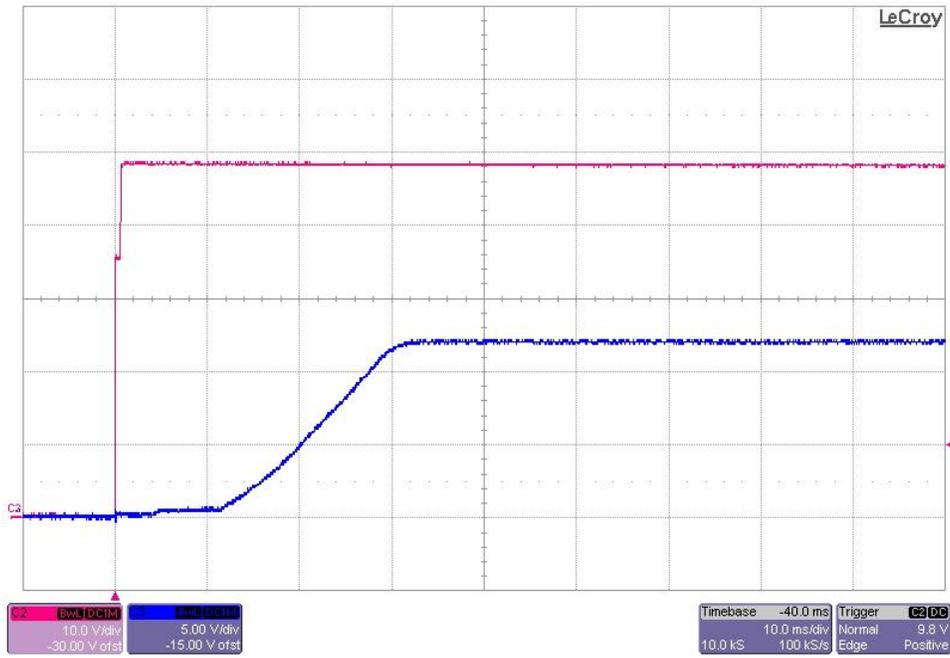The photo below shows the 12V output voltage startup waveforms after the application of 48Vdc in. The output was loaded with a 0A resistive load. (Vin is 10V/DIV, Vout is 5V/DIV, 10mS/DIV)




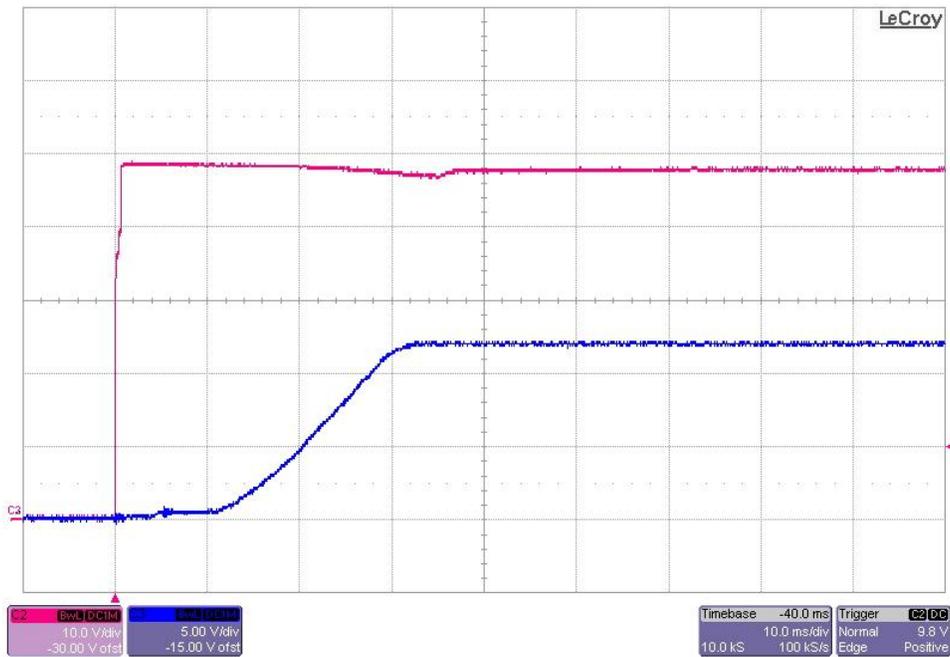The photo below shows the 12V output voltage startup waveforms after the application of 48Vdc in. The output was loaded with a 1A resistive load. (Vin is 10V/DIV, Vout is 5V/DIV, 10mS/DIV)




2 Output Ripple Voltage

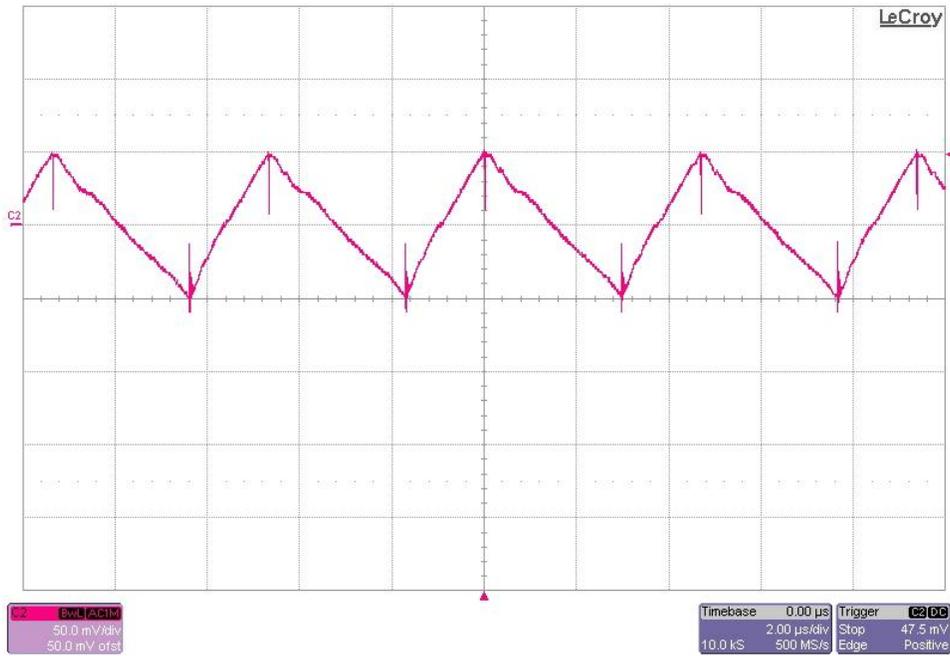
The 12V output ripple voltage is shown in the figure below. The image was taken with the output loaded to 1A and the input voltage set to 8Vdc. (50mV/DIV, 2uS/DIV)



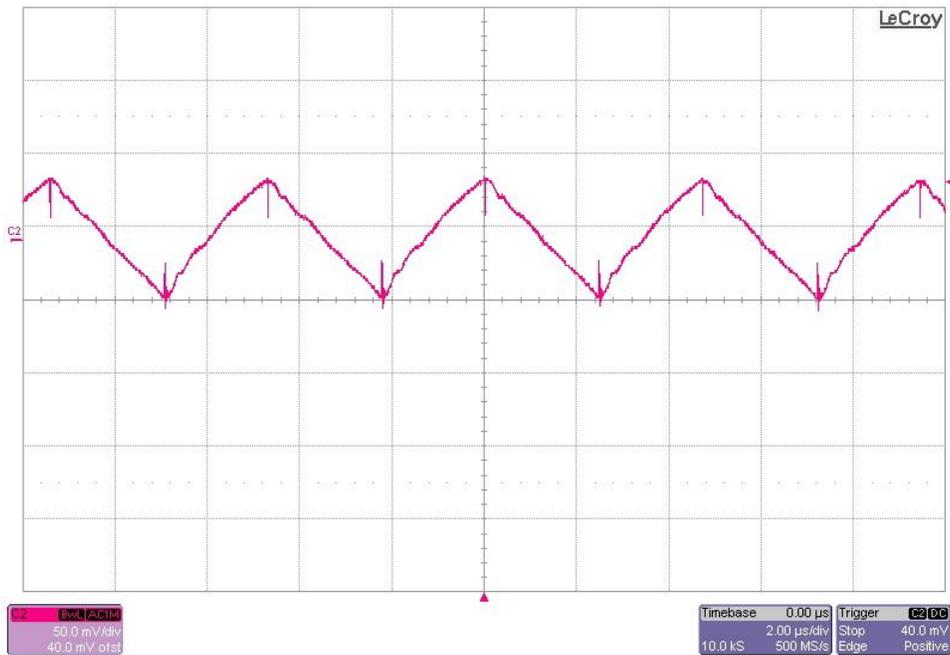The 12V output ripple voltage is shown in the figure below. The image was taken with the output loaded to 1A and the input voltage set to 12Vdc. (50mV/DIV, 2uS/DIV)





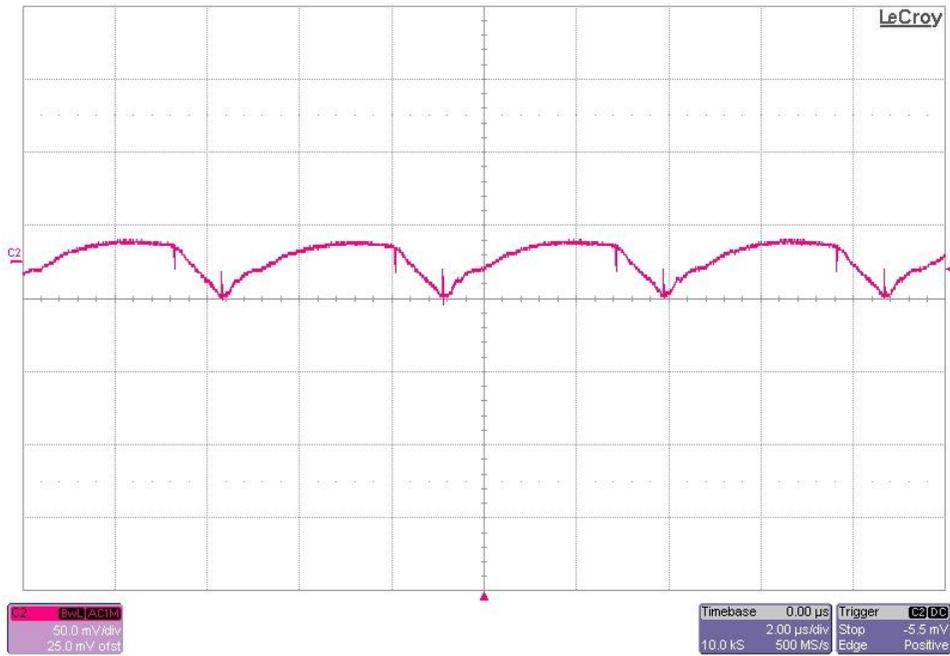The 12V output ripple voltage is shown in the figure below. The image was taken with the output loaded to 1A and the input voltage set to 48Vdc. (50mV/DIV, 2uS/DIV)




3 Efficiency

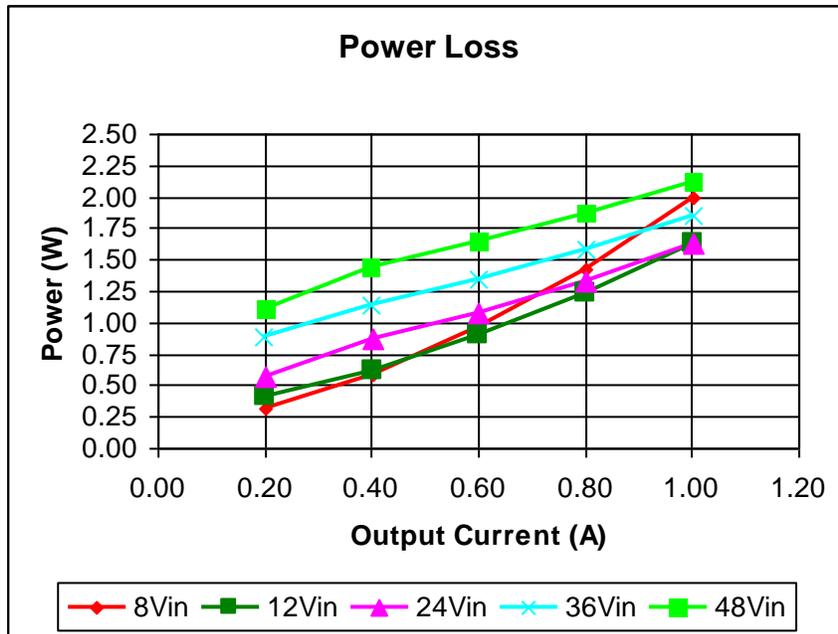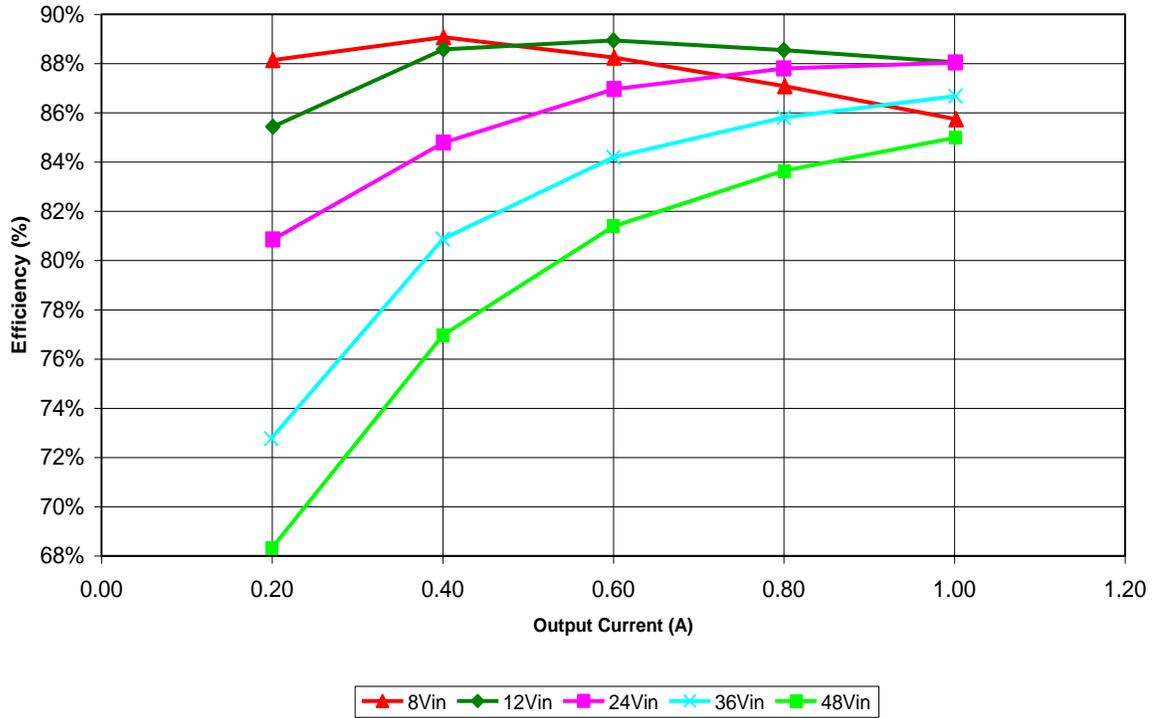The converter efficiency is shown in the figure below.




4 Load Transients

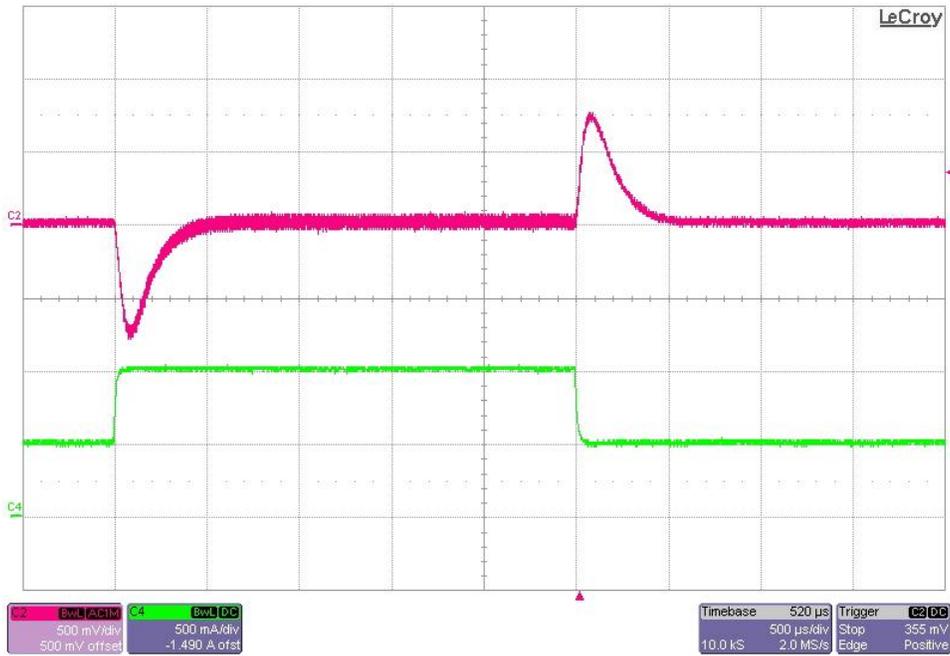
The photo below shows the 12V output voltage (top, ac coupled) when the load current is stepped between 0.5A to 1A. $V_{in} = 8V_{dc}$ (500mV/DIV, 500mA/DIV, 500uS/DIV)



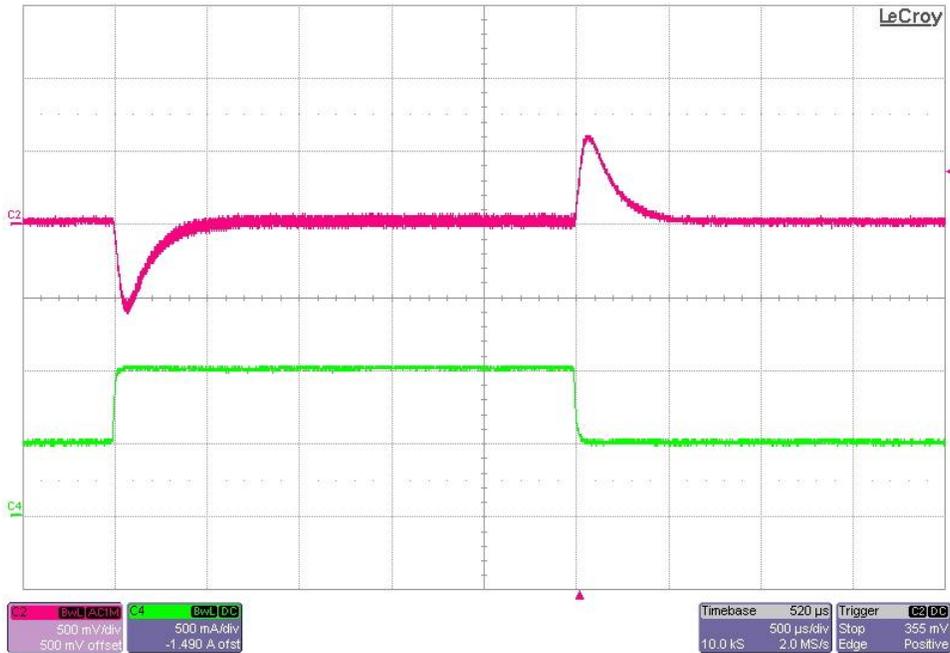The photo below shows the 12V output voltage (top, ac coupled) when the load current is stepped between 0.5A to 1A. $V_{in} = 12V_{dc}$ (500mV/DIV, 500mA/DIV, 500uS/DIV)




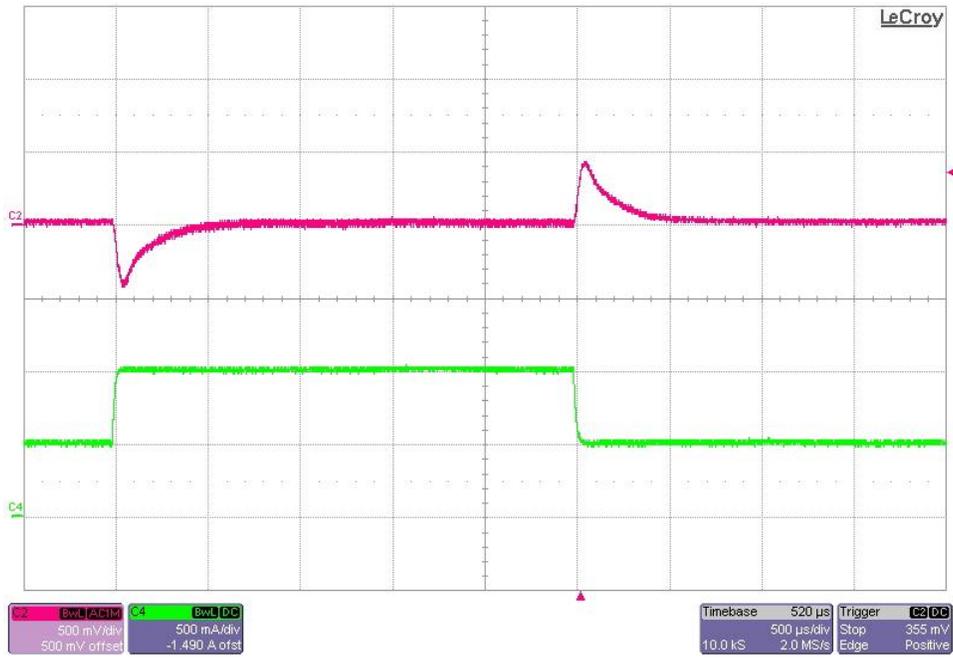The photo below shows the 12V output voltage (top, ac coupled) when the load current is stepped between 0.5A to 1A. $V_{in} = 48V_{dc}$ (500mV/DIV, 500mA/DIV, 500uS/DIV)




5 Switching Waveforms

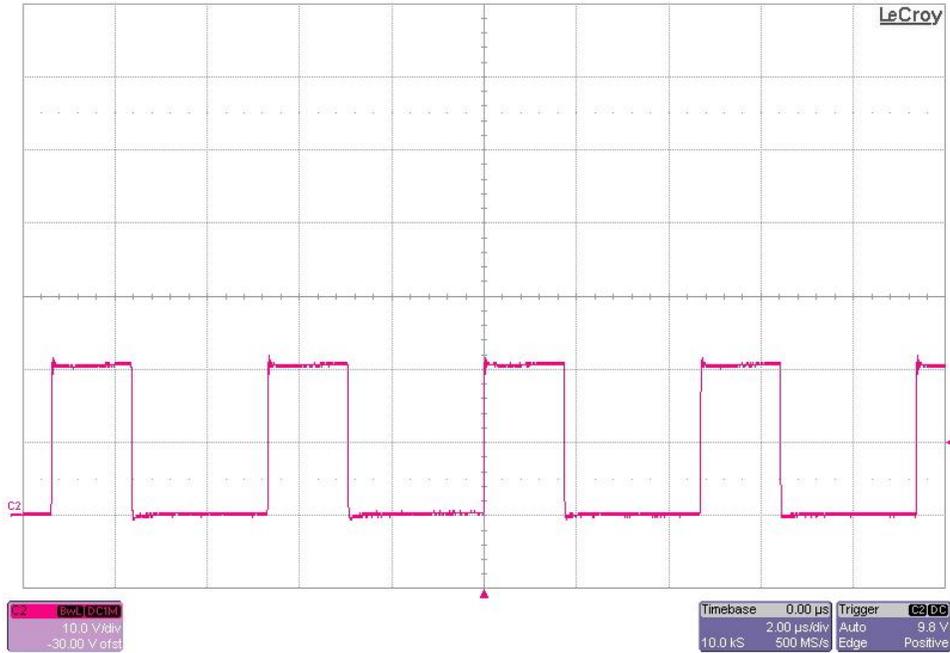
The photo below is the N-ch FET drain waveform. The input voltage is 8V and the output is loaded to 1A.
(10V/DIV, 2uS/DIV)



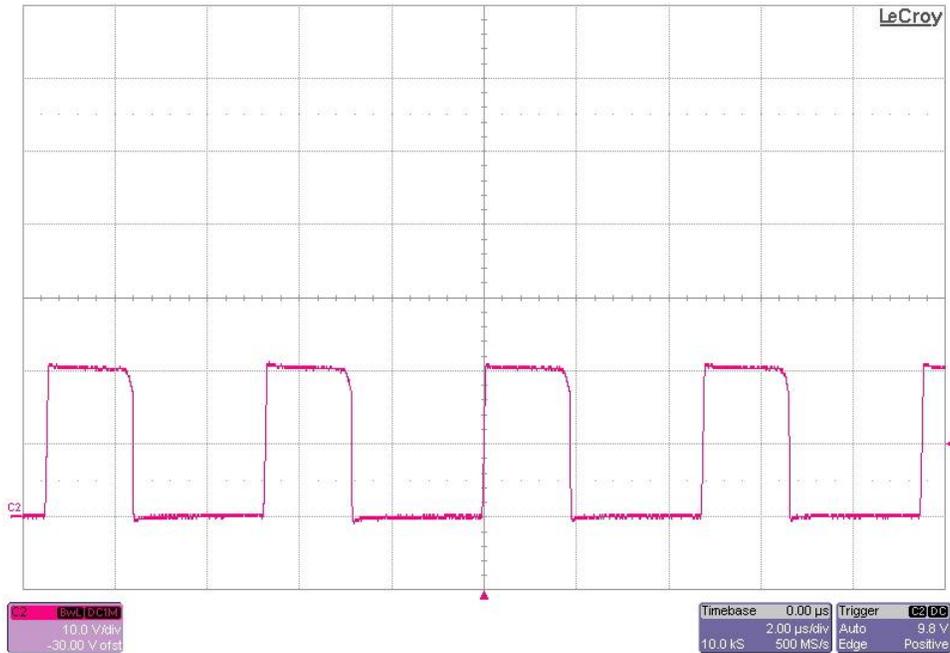
The photo below is the N-ch FET drain waveform. The input voltage is 8V and the output is loaded to 0.075A (the converter is entering discontinuous operation). (10V/DIV, 2uS/DIV)



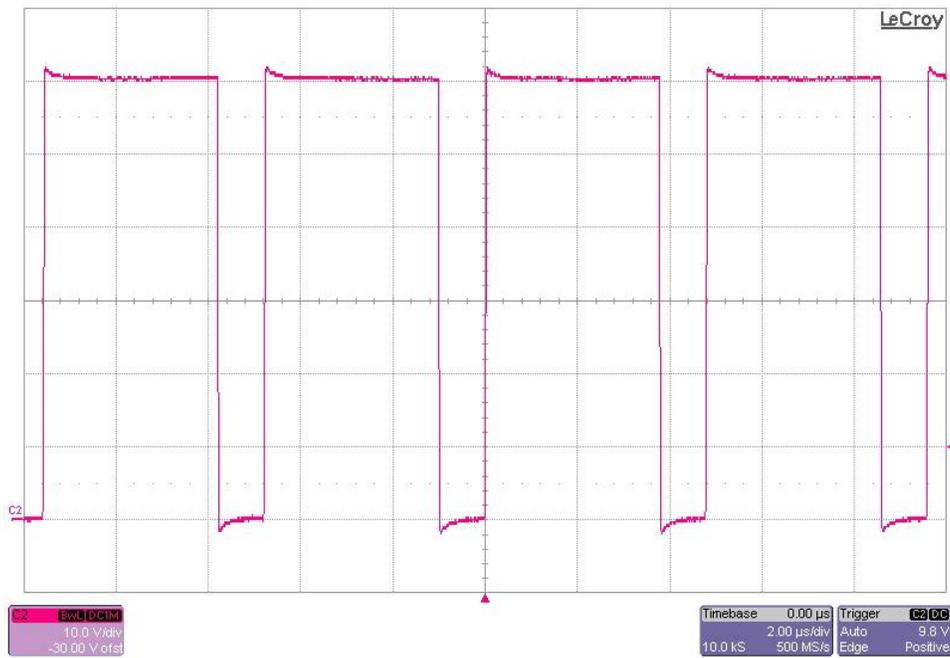The photo below is the N-ch FET drain waveform. The input voltage is 48V and the output is loaded to 1A. (10V/DIV, 2uS/DIV)



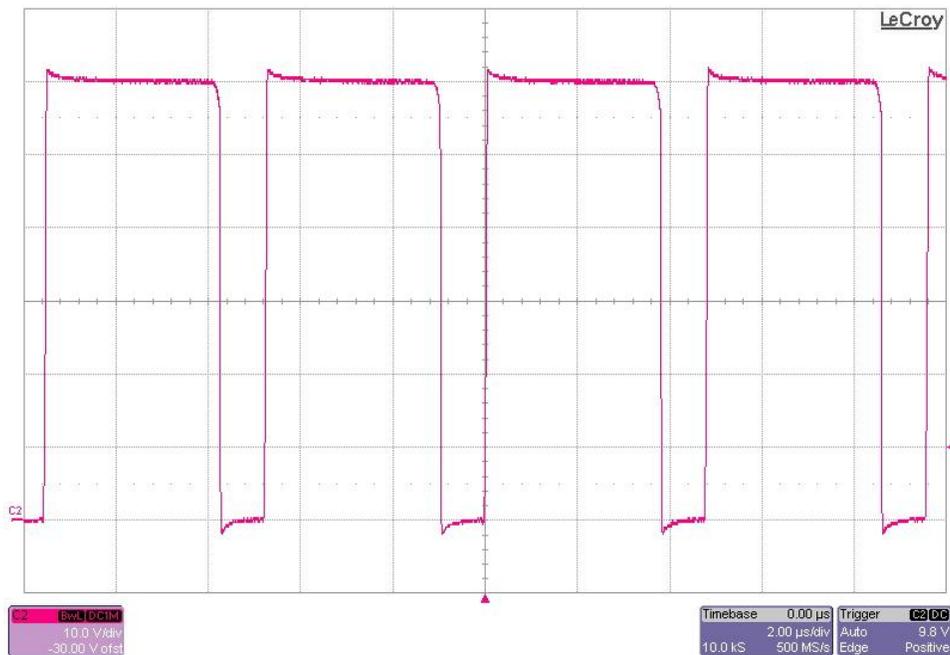
The photo below is the N-ch FET drain waveform. The input voltage is 48V and the output is loaded to 0.345A (the converter is entering discontinuous operation). (10V/DIV, 2uS/DIV)



6 Loop Gain


The plot below shows the loop gain with the input voltage at 12V and Iout at 1A and 0.2A.

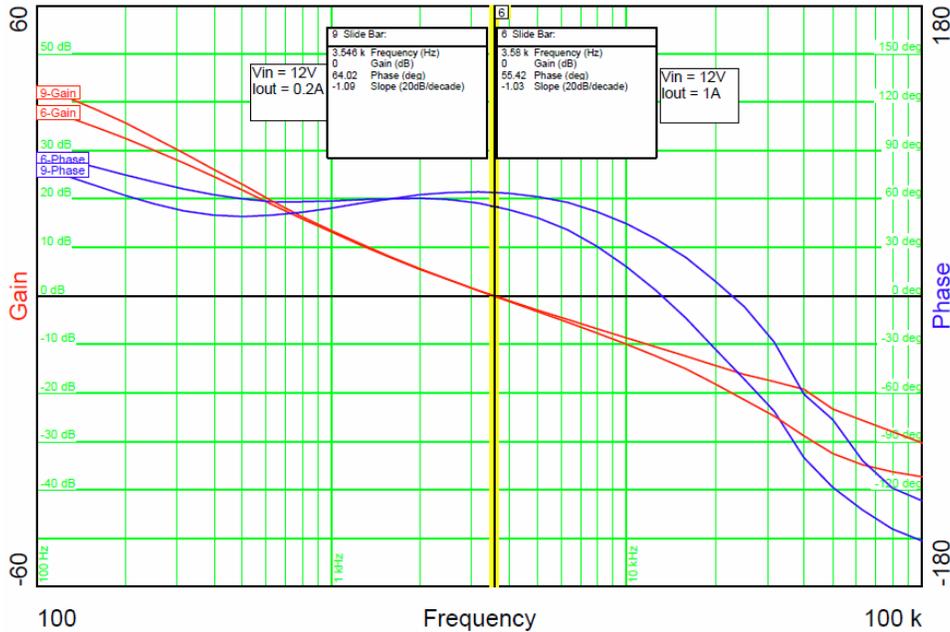Loop Gain (Iout = 1A) BW: 3.58KHz PM: 55 degrees
 Loop Gain (Iout = 0.2A) BW: 3.55KHz PM: 64 degrees




The plot below shows the loop gain with the input voltage at 1A and Vin at 8V and 48V.

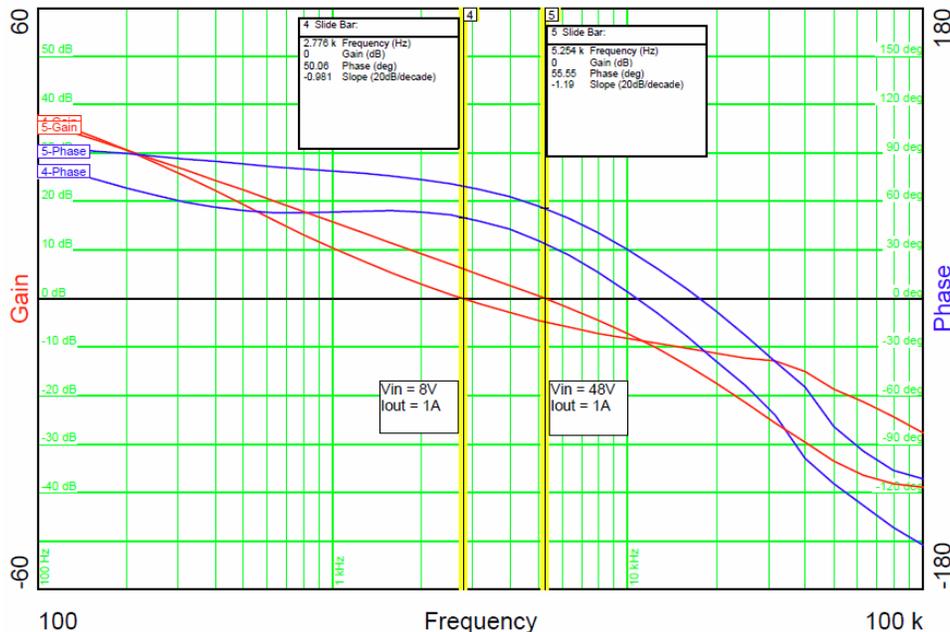Loop Gain (Vin = 8V) BW: 2.78KHz PM: 50 degrees
 Loop Gain (Vin = 48V) BW: 5.25KHz PM: 56 degrees



7 Photo

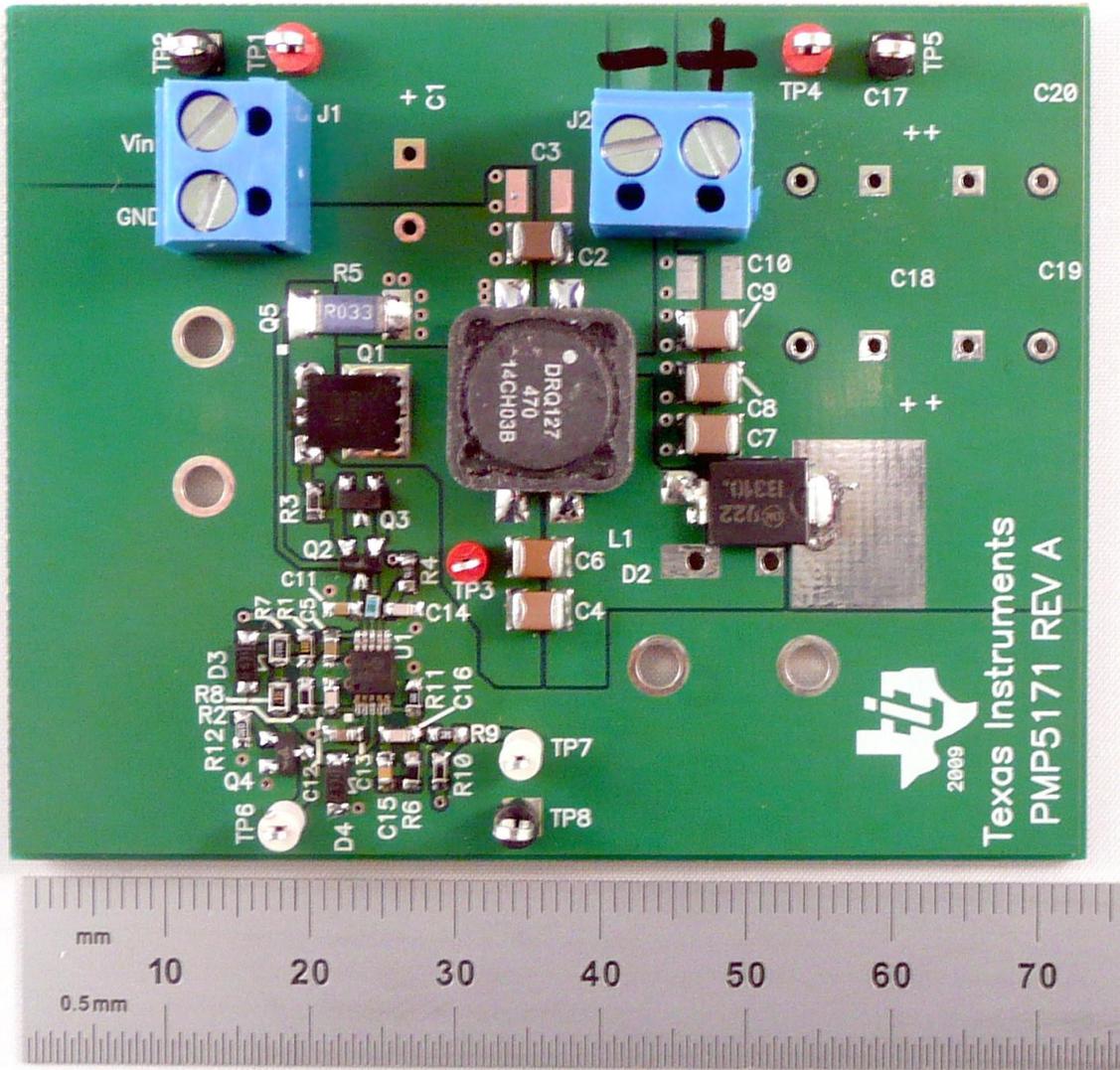The photo below shows the PMP8313 REVB prototype circuit (Built on PMP5171 REVA PWB).



8 Thermal Image

A thermal image is shown below when operating at 12Vin and 1A output, no air flow.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated