

Using the TPS56300 to Power DSPs

Bang S. Lee

Mixed Signal Products

ABSTRACT

The synchronous buck converter controllers (TPS56100, TPS56300, TPS56xx, and TPS5602) made by Texas Instruments are specifically designed to provide excellent transient response and high efficiency to the microprocessor power applications such as the TMS320C6000 and TMS320C5000 families from TI, as well as similar digital loads. In addition, hysteresis control method is used such that power supply designers do not have to worry about the stability and compensation issues.

1 Introduction

The TI TPS56300 features programmable dual channels (a synchronous buck controller and a LDO controller) with fast feedback control. The ripple regulator (synchronous buck converter) efficiently powers the TI DSP core voltage. The LDO controller drives an external N-channel power MOSFET. When the input supply voltage exceeds the required DSP I/O voltage, the MOSFET is controlled as a linear regulator. When the input supply voltage equals the required DSP I/O voltage (or, less than I/O voltage), the MOSFET is fully enhanced and used as a power distribution switch. The TPS56300 also includes inhibit, slow start, and under-voltage lockout features to aide in controlling power sequencing.

Many protection features are incorporated to ensure better system integrity. An open-drain output power good status circuit monitors both output voltages, and is pulled low if output falls below the threshold. An over current shutdown circuit protects the high-side power MOSFET against short-to-ground faults at load or the phase node, while overvoltage protection turns off the output drivers and LDO controller if output exceeds its threshold. Under voltage protection turns off the high-side and low-side MOSFET drivers and the LDO controller if output is 25% below V_{ref} . Lossless current-sensing is done by detecting the drain-source voltage drop across the high-side power MOSFET while it is conducting.

1.1 TPS56300 Operating Conditions

Table 1. Summary of the TI Synchronous Buck Converter Controller and EVM Characteristics

	V_I RANGE (POWER STAGE)	V_{CC} RANGE (CONTROLLER)	V_O RANGE (POWER STAGE)	I_O, MAX^\dagger (POWER STAGE)	DRIVER CURRENT (CONTROLLER)	OTHERS
TPS56100	4.5 ~ 6 V	4.5 ~ 6 V	1.3 to 2.6 V	7 A	2 A	1 channel
TPS56300	2.8 ~ 5.5 V	2.8 ~ 5.5 V	1.3 to 3.3 V	4 A for RR 6 A for LDO	2 A	2 channels
TPS56xx	4.5 ~ 6 V	12 V	1.5V, 1.8 V, 2.5 V, or 3.3 V	8 A	2 A	1 channel
TPS5602	4.5 ~ 25 V	4.5 ~ 25 V	Adjustable	4 A/channel	1.2 A at $V_O = 3$ V	2 channels

[†] The current capability can be extended if the switching devices are added in parallel; see Table 2 in TI TPS56100/56300 data sheets.

1.2 Key Features

- Programmable Dual Output Controller
 - Switching Regulator Controls DSP Core Voltage
 - LDO Controller Regulates DSP I/O Voltage
- Programmable Slow-Start
- Simultaneous Power-Up of Both Outputs
- Power Good Output
- Efficiencies Greater Than 90% on Switching Regulator
- $\pm 1.5\%$ Reference Voltage Tolerance
- Overvoltage, Undervoltage, and Adjustable Overcurrent Protection
- Fully Compliant With TI DSP Power Requirements
- Evaluation Module TPS56300EVM–139 Available

2 Application Circuit

Figure 1 shows a typical circuit design using the TPS56300, which features a dual-channel output, a ripple regulator (1.8-V output) and an LDO (3.3-V output). During input voltage ranging from 2.8 to LDO_OUT (LDO output voltage), the LDO's power MOSFET looks like a small resistor (11 m Ω) and can be used as a power distribution switch. Over the input voltage range higher than the LDO_OUT, the LDO regulates the output at 3.3 V. The ripple regulator of TPS56300 regulates the DSP core voltage over the input range (2.8 V ~ 5.5 V). The two output voltages are independent and are easily set by voltage identification network (VID) pins. Tri-level VID pins set both regulated voltages to any of nine preset voltage pairs from 1.3 V to 3.3 V. Other voltages are possible by implementing an external voltage divider.

 


Figure 1. Typical Circuit Design Using the TPS56300

 


Figure 2. Efficiencies of Ripple Regulator (3.4-V Input)

Table 2 shows the setting values of TPS56300 to generate the output voltages 1.5 V, 1.8 V, 2.5 V, and 3.3 V for TI DSP power requirements. Figure 2 shows the efficiency of the ripple regulator.

Table 2. Summary of Setting Values for TPS56300 1.5/1.8/2.5/3.3-V Outputs

VID TERMINALS (0 = GND, 1 = FLOATING, 2 = V(BIAS))		VO1	VO2
VID1	VID0	(RR_OUT, Vdc)	(LDO_OUT, Vdc)
2	1	1.5	3.3
1	0	1.8	3.3
1	2	2.50	3.3

Most LDOs Power MOSFET manufacturers specify the maximum power dissipation allowable without damaging the device. The safe operating area for the LDO regulator using IRF7811 as the power MOSFET is shown in Figure 3. The LDO regulator must operate within this area. The LDO regulator power dissipation is calculated using equation 1.

$$P_D = (V_I - V_O) \times I_O \tag{1}$$

 


Figure 3. Safe Operating Area of the LDO (3.3-V Output, 3.4-V Input)

NOTE: TI DSPs do not require specific power sequencing between the core supply and the I/O supply. However, systems should be designed to ensure that neither supply is powered up for extended periods of time if the other supply is below the proper operating voltage. Excessive exposure to these conditions can adversely affect the long term reliability of the device. System level concerns, such as bus contention, may require supply sequencing to be implemented. In this case, the core supply should be powered up at the same time as, or prior to (and powered down after), the I/O buffers.

3 Power Supply Solutions

The power solution for 1.8-V core and 3.3-V I/O voltage using TPS56300 is shown in Figure 4. Both supplies (LDO and ripple regulator) will ramp up together to promote better system reliability during power up.

 


Figure 4. TI DSP Power Supply Solution Using the TPS56300

The Schottky diode (D1) provides a measure of protection during the power-down sequence and during other periods when the DV_{DD} supply is below the CV_{DD} supply by limiting the CV_{DD}-DV_{DD} voltage to the forward drop of D1.

The two power supplies should be placed close to the DSP to minimize the trace resistance and inductance, and to minimize the ground loop current between the two output grounds. This ground loop current can generate radiated EMI noise that can adversely affect any circuitry within the loop. The ground connection must be made directly on the DSP to help minimize the problem.

4 Evaluation Module

An EVM (evaluation module)—SLVP139—is available to provide a convenient method for evaluating the performance of the TPS56300. A completed and tested power supply is included in the EVM.

5 References

For detailed information:

1. Data sheet and EVM Board; <http://www-s.ti.com/sc/psheets/slvs261a/slvs261a.pdf>
2. EVM board order; http://www.ti.com/sc/docs/tools/analog/tps56300evm_139.html
3. SVS application note; http://www.ti.com/sc/docs/apps/analog/supervisory_circuits.html
4. Application note; http://www.ti.com/sc/docs/apps/analog/power_management.html

For general information:

5. TI Power Management Products;
<http://www.ti.com/sc/docs/products/msp/pwrmgmt/index.html>

IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, license, warranty or endorsement thereof.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations and notices. Representation or reproduction of this information with alteration voids all warranties provided for an associated TI product or service, is an unfair and deceptive business practice, and TI is not responsible nor liable for any such use.

Resale of TI's products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service, is an unfair and deceptive business practice, and TI is not responsible nor liable for any such use.

Also see: [Standard Terms and Conditions of Sale for Semiconductor Products](http://www.ti.com/sc/docs/stdterms.htm). www.ti.com/sc/docs/stdterms.htm

Mailing Address:

Texas Instruments
Post Office Box 655303
Dallas, Texas 75265