

# Analog Dimming with the TPS61181

Oliver Ou / Clancy Soehren

Battery Power Applications

## ABSTRACT

The TPS61181 LED driver supports PWM dimming; however, it also has the ability to support analog dimming with some simple modifications. Analog dimming causes less EMI noise and achieves better efficiency than PWM dimming. Analog dimming can be achieved by using an analog voltage to control the current sourced by the ISET pin. This application note explores this alternative dimming method for the TPS61181.

## Contents

1	Introduction .....	1
2	Theory .....	1
3	Design Example .....	3
4	Conclusion .....	6
5	References .....	6

## List of Figures

1	TPS61181 Analog Dimming Configuration .....	2
2	RC Filter to get the Average Value of PWM Signal .....	2
3	Theoretical Led Current and External Voltage .....	4
4	Actual LED Current vs External Voltage .....	5
5	$K_m$ vs LED Current .....	5

## 1 Introduction


The TPS61181 is an ideal LED driver for medium sized LCD panel backlighting. For the cost advantage and ease of use, this chip is well suited for use in small-sized handheld equipment. Popular applications include the displays for MP3 players, GPS, etc. This device supports six current sinks of 25mA each and, although designed to operate with PWM dimming, can be modified to operate with analog dimming.

The benefits of analog dimming over PWM dimming include lower EMI and slightly higher efficiency. When PWM dimming, EMI noise is generated from pulsing the maximum current through the LEDs at the applied duty cycle. When analog dimming, a DC current directly proportional to brightness and LED forward voltage flows through the LEDs. At lower DC currents, the LED forward voltages drop, resulting in slightly lower output power for the same brightness level. The only drawback to analog dimming is a slight shift in hue at very low dimming levels. Either an external analog voltage ( $V_x$ ) or a PWM signal can drive the analog dimming. In order to use this type of dimming a few extra circuit components are required, regardless of which type of signal will drive the circuit.

## 2 Theory

Analog dimming is achieved by controlling the current sourced from the ISET pin. This current is directly proportional to the current limit of each current sink input used to drive the LEDs. The DCTRL pin, where the PWM signal is normally applied, should be tied to a logic high signal, effectively a 100% duty cycle PWM signal. With this set-up, the current through the IFB pins will now be controlled by the current limit.

A simple way of controlling the current sourced by the ISET pin is to use an analog voltage as the input to the circuit shown in [Figure 1](#). The voltage at the ISET pin is constant, so changing  $V_x$  will control the current through  $R_{s2}$ . The current through  $R_{s1}$  is constant, so  $V_x$  determines how much current the ISET pin needs to source.

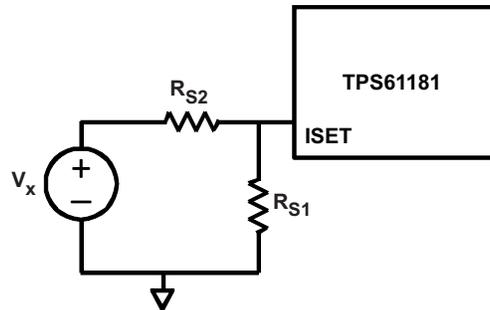

**Figure 1. TPS61181 Analog Dimming Configuration**

By adjusting  $V_x$ , the current being sourced by ISET will change. By modifying equation 1 of the TPS61181 datasheet, the current through the LEDs will be determined by [Equation 1](#).

$$I_{LED} = K_{ISET} \times \left( \frac{V_{ISET}}{R_{s1}} - \frac{V_x - V_{ISET}}{R_{s2}} \right) \quad (1)$$

Where:


$K_{ISET}$  = Current multiple (1000 typical);  
 $V_{ISET}$  = ISET pin voltage (1.229 V typical);  
 $V_x$  = External voltage

For a given input voltage range, the optimum resistor values can be found if the maximum and minimum LED currents are known. The equations for  $R_{s1}$  and  $R_{s2}$  are shown in [Equation 2](#) and [Equation 3](#).

$$R_{s2} = K_{ISET} \times \frac{V_{x(max)} - V_{x(min)}}{I_{LED(max)} - I_{LED(min)}} \quad (2)$$

$$R_{s1} = \frac{K_{ISET} \times R_{s2} \times V_{ISET}}{I_{LED(min)} \times R_{s2} + K_{ISET} \times (V_{x(max)} - V_{ISET})} \quad (3)$$

There are multiple methods of generating the analog signal. One method is to filter a PWM signal to create a smooth analog signal. Even though a PWM signal is used, the current through the LEDs will be at a constant level set by the ISET pin. [Figure 2](#) shows an example of a circuit that uses a PWM signal to generate an analog voltage.

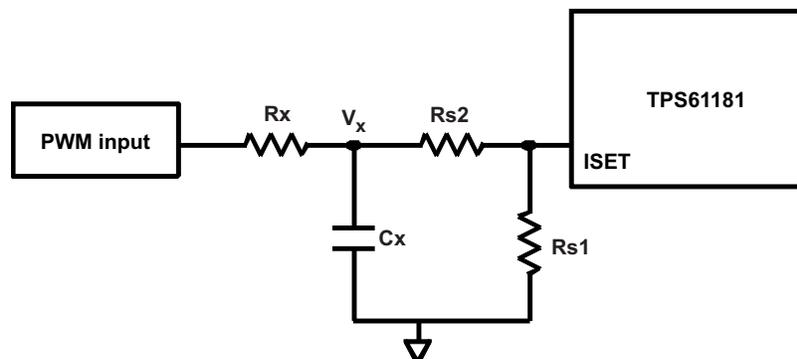

**Figure 2. RC Filter to get the Average Value of PWM Signal**

In this case, the duty cycle of the PWM input controls the current through the LEDs. The RC filter made up of  $R_x$  and  $C_x$  filters the PWM input so that the voltage at  $V_x$  will be the average value of the PWM signal. Increasing the duty cycle of the PWM input increases the voltage at  $V_x$ . Assuming that the PWM signal is switching from 0V to  $V_{PWM}$ , the average value of the PWM signal can be represented as:

$$V_{avg} = V_{PWM} \times D \quad (4)$$

Where:

D = Duty cycle of the PWM signal

Equation 1 can be modified to account for this new circuit configuration. From there, if the minimum and maximum duty cycle of the PWM signal and the minimum and maximum desired LED currents are known, then  $R_{s1}$  and  $R_{s2}$  can be calculated. Equation 5 and Equation 6 show the design equations for  $R_{s2}$  and  $R_{s1}$  respectively.

$$R_{s2} = K_{ISET} \times \frac{D_{max} \times V_{PWM} - D_{min} \times V_{PWM}}{I_{LED(max)} - I_{LED(min)}} \quad (5)$$

$$R_{s1} = \frac{K_{ISET} \times R_{s2} \times V_{ISET}}{I_{LED(min)} \times R_{s2} + K_{ISET} \times (D_{max} \times V_{PWM} - V_{ISET})} \quad (6)$$

The RC filter requires at least 20dB of attenuation at the frequency of the PWM signal. More attenuation can be added to create a smoother signal, or to cause a gradual dimming effect. The minimum capacitor value is given by Equation 7. To minimize the capacitor size, choose  $R_x$  to be equal to  $R_{s2}$ .

$$C_{x(min)} = \frac{1}{2 \times \pi \times (R_x \parallel R_{s2}) \times \frac{f_{pwm}}{10}} \quad (7)$$

Where:

$f_{PWM}$  = frequency of PWM signal

It is recommended that the minimum and maximum duty cycles be chosen as 0% and 100% respectively. Exceeding the maximum duty cycle causes the maximum voltage at  $V_x$  to be exceeded, possibly causing current to be sunk through the ISET pin instead of sourced. This causes an unstable state and could damage the LEDs. Going below the minimum duty cycle increases the LED current above the chosen  $I_{LED(max)}$ . This could damage the LEDs if their maximum current rating is exceeded. Since a DC signal is essentially a 100% duty cycle and a grounded signal is a 0% duty cycle, choosing the proposed duty cycle limits prevents accidental damage to the LEDs during start-up or any other time when the PWM signal may be inactive.

In actual practice, the current matching between all six LED strings gets worse as the current decreases. As long as  $I_{min}$  is chosen to be 5mA or greater, the current matching will be very good. If it is necessary to dim below this level, then a combination of analog and PWM dimming should be used. Consider, if the analog dimming method lowers the LED current to 5mA, then a PWM signal on the DCTRL pin will cause the LED current to jump between 0mA and 5mA. PWM dimming with a lower peak output current helps reduce EMI, and provides better current matching between the strings.

### 3 Design Example


Consider a system that wishes to use an input dimming control voltage that ranges from 0 to 2V, and wishes the LED driving current to range from 5 to 20mA. From this situation, the following variables can be filled out:

$$\begin{aligned} V_{x(max)} &= 2 \text{ V} \\ V_{x(min)} &= 0 \text{ V} \\ I_{LED(max)} &= 20 \text{ mA} \\ I_{LED(min)} &= 5 \text{ mA} \end{aligned}$$

Using Equation 2 and Equation 3 to determine  $R_{s2}$  and  $R_{s1}$  respectively yield:

$$\begin{aligned} R_{s2} &= 133 \text{ k}\Omega \\ R_{s1} &= 113 \text{ k}\Omega \end{aligned}$$

The theoretical relationship between the voltage at  $V_x$  and the LED current is linear. Figure 3 shows this theoretical curve.

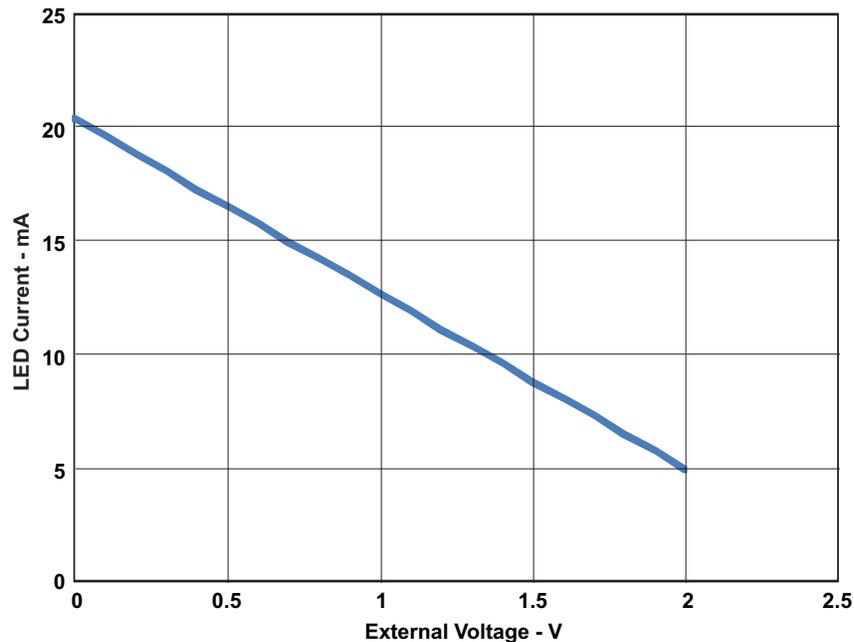

**Figure 3. Theoretical Led Current and External Voltage**

All six strings of LEDs should match this curve; however, at lower LED current levels, the current matching can be unreliable. As long as  $I_{\min}$  is chosen to be 5mA or greater, then  $K_m$  should stay below 2.5%, as specified in the data sheet.  $K_m$  is a measure of the current variation between the six LED current sinks. Equation 8 shows how to calculate  $K_m$ .

$$K_m = \frac{I_{\max} - I_{\min}}{I_{\text{AVG}}} \times 100\% \quad (8)$$

The data shown in Figure 4 was collected from the system shown in Figure 1, with 130k $\Omega$  resistors for  $R_{s1}$  and  $R_{s2}$ . The graph shows the currents of each LED output versus the external voltage applied. Notice that there is a linear relationship up until the LED currents drop below about 5 mA. Below about 5 mA, the current limit matching between the six current sinks suffers.

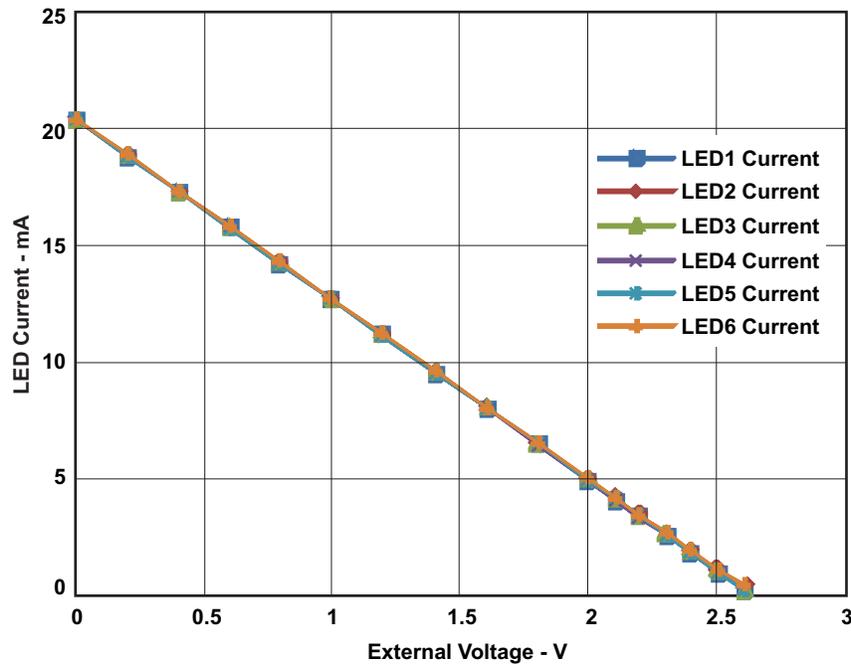


Figure 4. Actual LED Current vs External Voltage

Figure 5 shows how the error increases as the current through the LEDs gets smaller.

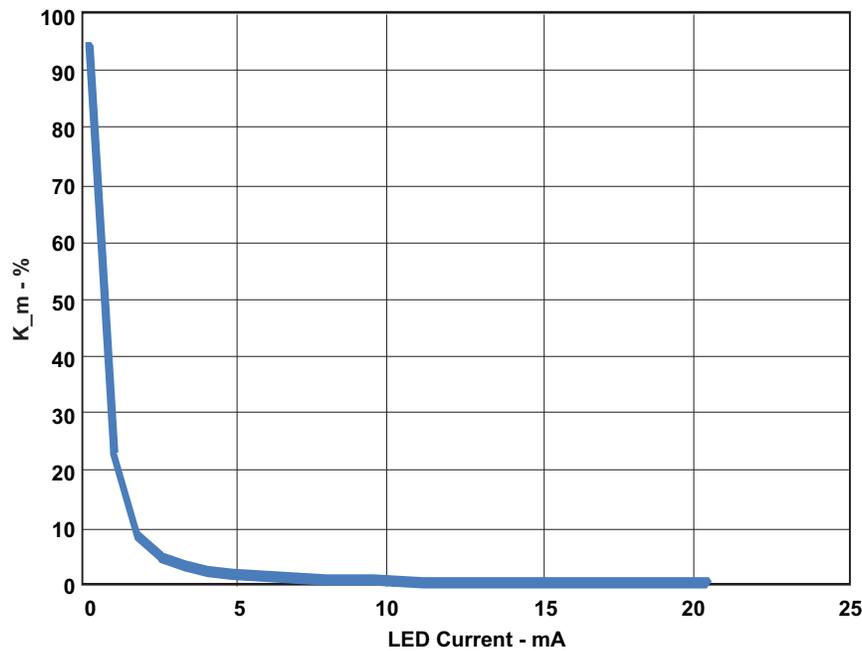


Figure 5. K<sub>m</sub> vs LED Current

If it is necessary to operate at these low current levels it is advisable to use the traditional built-in PWM dimming scheme, either in conjunction with analog dimming or by itself. If PWM dimming causes the LED current to switch between 0 and 5 mA, instead of between 0 and  $I_{LED(max)}$  (20 mA in this example), the EMI noise disruption would be significantly less than if the PWM dimming scheme was used for the entire current range.

## 4 Conclusion

The TPS61181 is a versatile LED driver, offering two different approaches to control the dimming level of the LEDs. PWM dimming and analog dimming are both inherently built into the part. PWM dimming is effective at very low power ranges, but causes much more EMI noise than analog dimming. It also can be less efficient than analog dimming in certain current ranges. Analog dimming is a viable alternative where the current through the LEDs is controlled by adjusting an analog voltage. For the TPS61181, this analog voltage controls the current limit for each LED string. Analog dimming can also be implemented by using a PWM signal to generate the analog signal. This causes much less noise than if PWM dimming was used to directly drive the LEDs because the PWM signal used in analog dimming needs about three orders of magnitude less power than the PWM signal in PWM dimming. Using PWM dimming and analog dimming together reduces the EMI noise while still maintaining precise control over the LED currents during low power operation. Depending on the application and the range of dimming needed, PWM dimming or analog dimming can fulfill the dimming needs of the TPS61181.

## 5 References

1. TPS61181, *WLED Driver for Notebook Display* ([SLVS801C](#))
2. Guibord, Matt; *How to Use Analog Dimming With the TPS6116x* ([SLVA471](#))

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated