



TPS5124 Dual Synchronous Buck Project 3/18/08

The following test report is for the TPS5124 Dual Synchronous Buck.

The tests performed were as follows:

- A. TPS5124 – 3.3V@25A; 5V@20A
 1. Turn-On (No load)
 2. Turn-Off (1A load)
 3. Output Voltage Ripple (full load)
 4. Transient Response (5A to 20A)
 5. Load Regulation (No load to full load)
 6. Efficiency
 7. Switch Node (20MHz Bandwidth Limited with full load)
 8. Bode Plot (Full Load)

1 Startup – (TPS5124 : 3.3V@25A; 5V@20A)

The photo below shows the startup waveform. The input voltage is 12V, the outputs are not loaded. The time-base is set to 5ms/Division.

Channel 1 – Yellow : 3.3V Output – (2V/Division)

Channel 2 – Pink : 5.0V Output – (2V/Division)



2 Shutdown – (TPS5124 : 3.3V@25A; 5V@20A)

The photo below shows the shutdown waveforms. The input voltage is 12V. The outputs are loaded with 1A.

Channel 1 – Yellow : 3.3V Output – (2V/Division)


Channel 2 – Pink : 5.0V Output – (2V/Division)




3 Output Ripple Voltage – (TPS5124 : 3.3V@25A; 5V@20A)

The output voltage ripple is shown in the figure below. The input is 12V. The outputs are fully loaded.

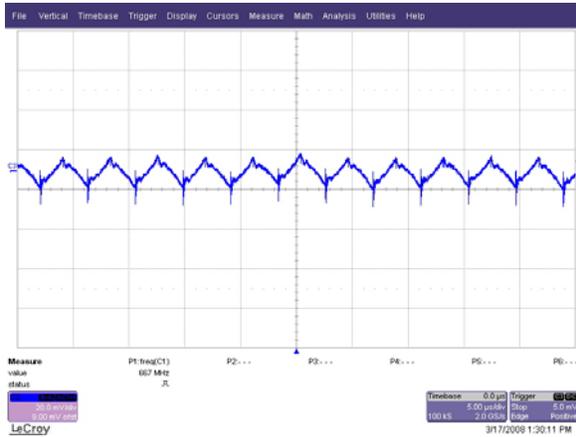Channel 3: Output Voltage – (20mV/Division; AC Coupled)



3.3V@25A

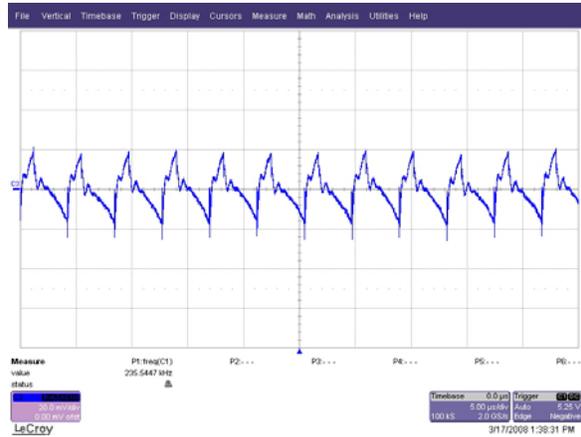



5.0V@20A

4 Transient Response – (TPS5124 : 3.3V@25A; 5V@20A)

The transient response of the converter is shown in the figure below. The input voltage is 12V. The current is pulsed from 1A to 3A.



Channel 3: Output Voltage – (50mV/Division; AC Coupled)

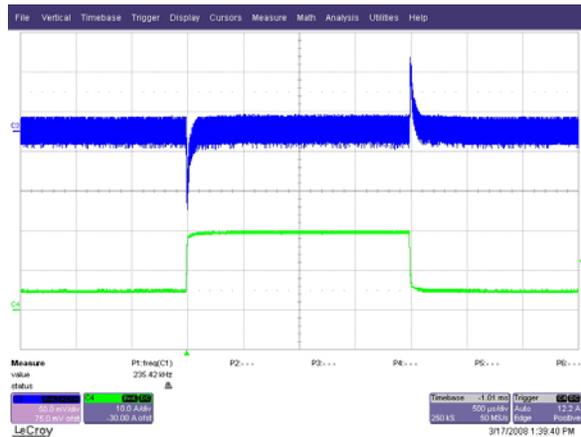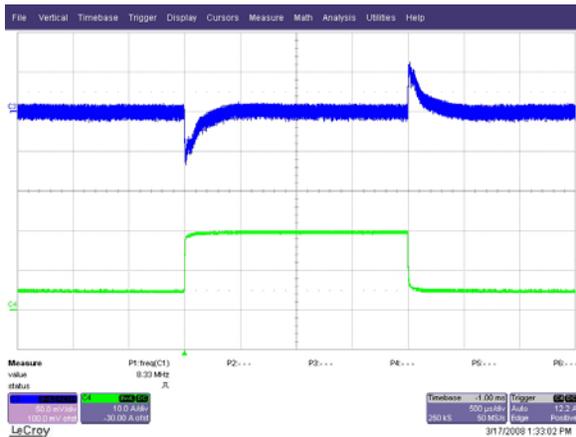Channel 4: Output Current – (10A/Division)




5 Load Regulation – (TPS5124 : 3.3V@25A; 5V@20A)

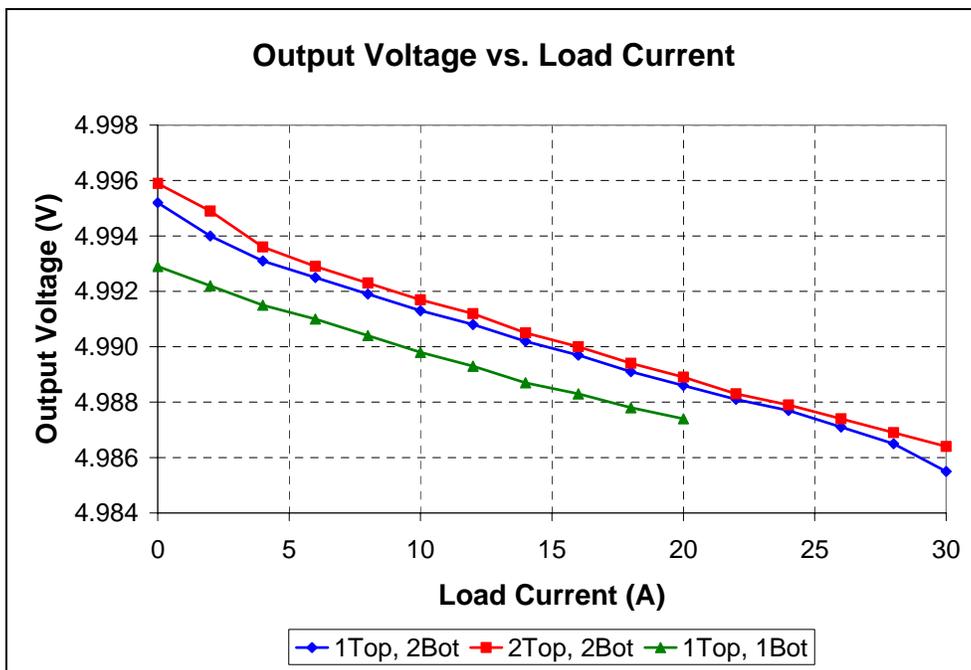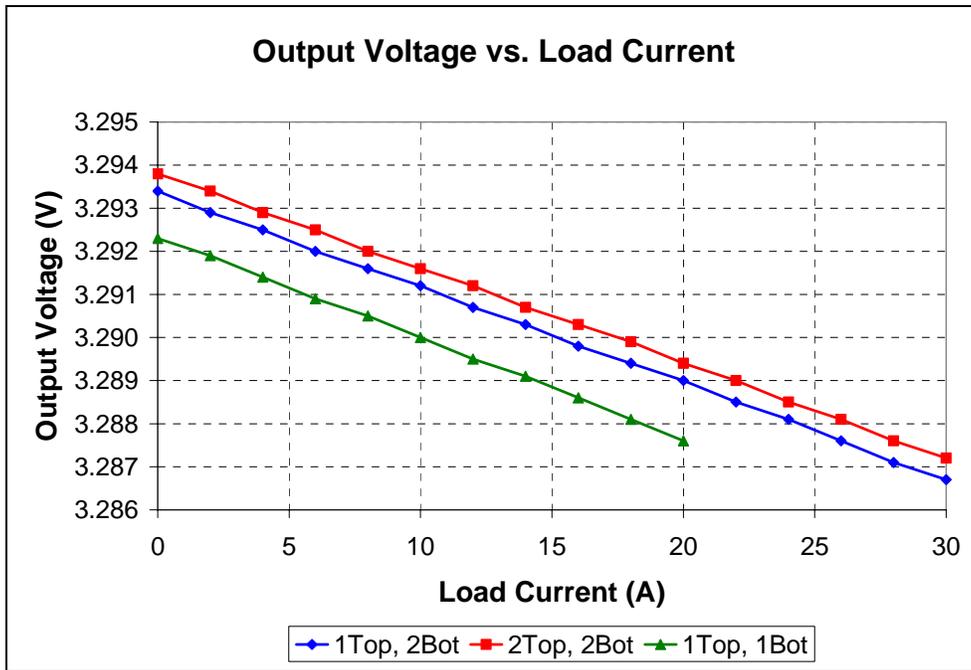The load regulation is shown in the figures below.




6 Efficiency – (TPS5124 : 3.3V@25A; 5V@20A)

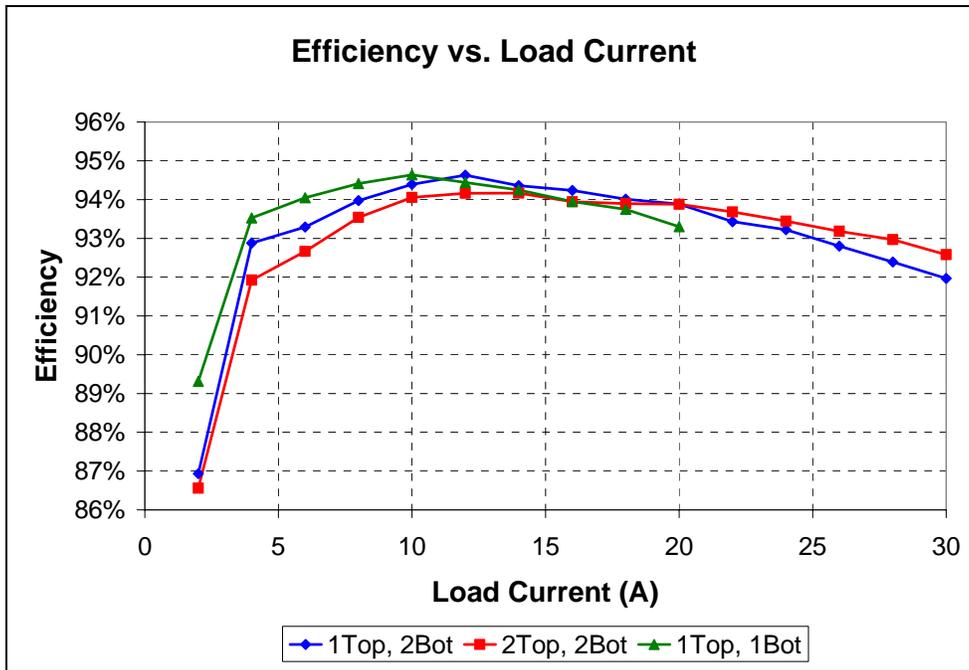The efficiency of the converter is shown in the picture below.



3.3V Output

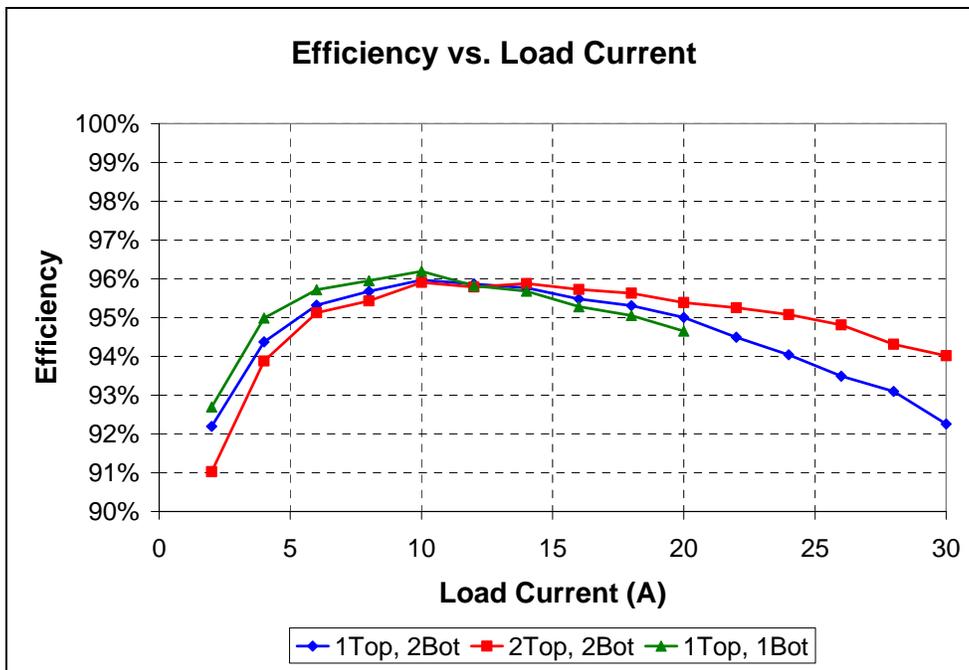

5.0V Output

7 Switching Waveforms – (TPS5124 : 3.3V@25A; 5V@20A)

The waveform below shows the switch node for each output. The input is 12V. The outputs are fully loaded.


Channel 1: Switch Node 5.0V Output – (5V/Division)


Channel 2: Switch Node 3.3V Output – (5V/Division)



8 Bode Plot – (TPS5124 : 3.3V@25A; 5V@20A)

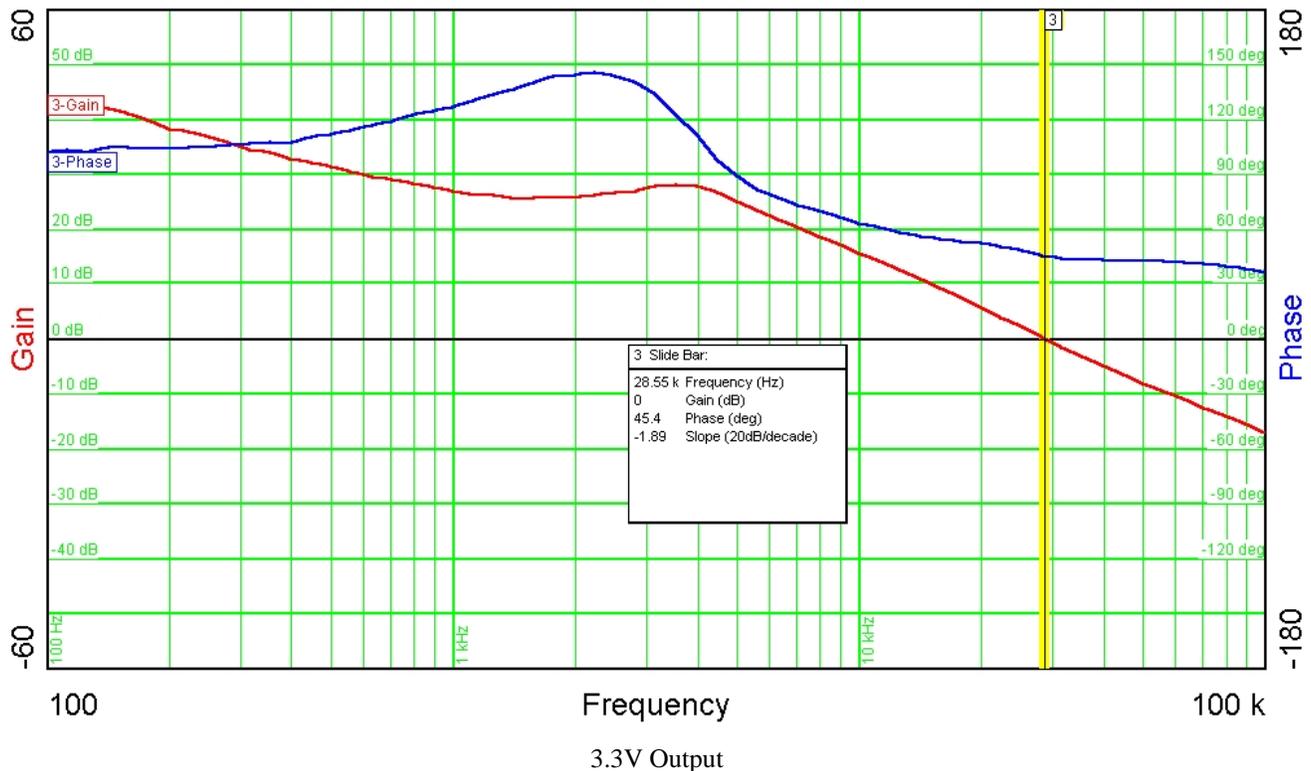The figures below show the frequency response of the converters. The input voltage is 12V, the outputs are fully loaded.



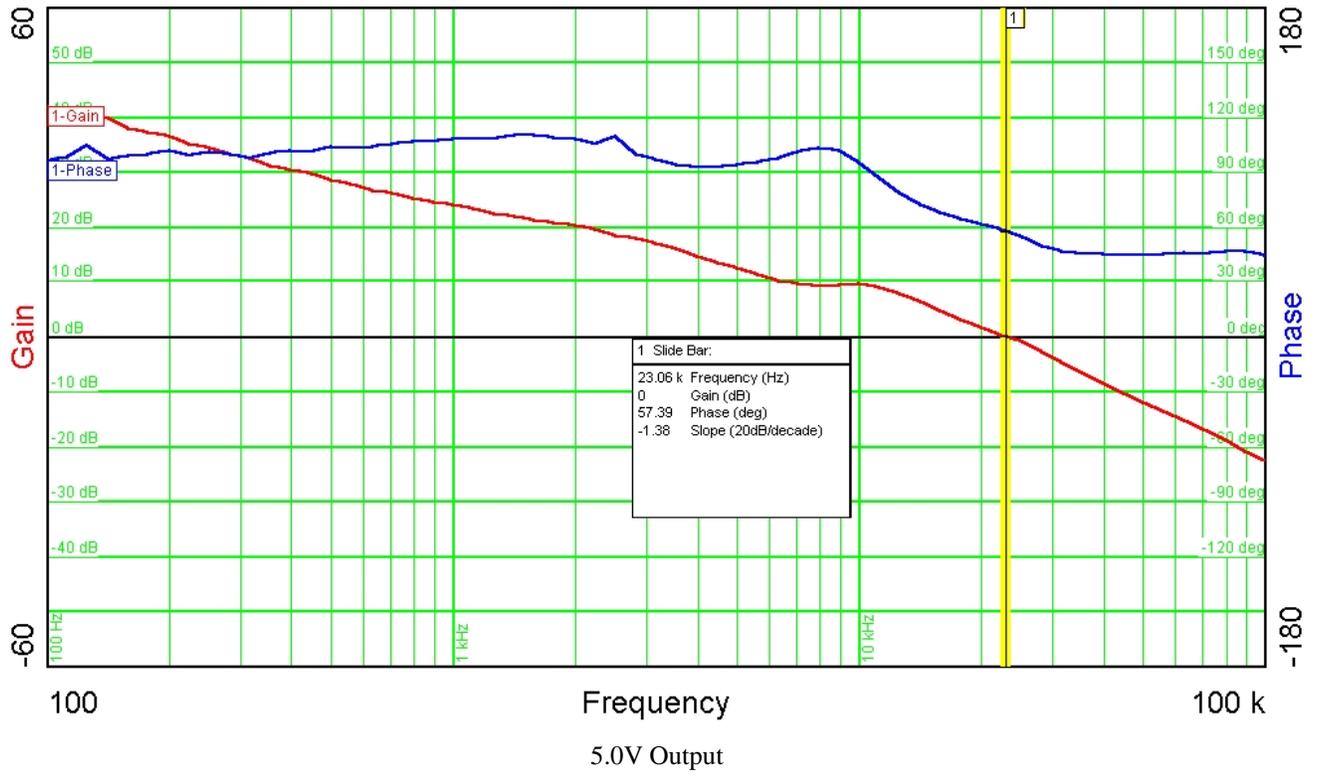

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated