

AN-1414 LM1770 Design Reference

ABSTRACT

This application report presents several reference designs that can be used to implement the Texas Instruments LM1770 Synchronous Buck Controller in a wide variety of configurations.

Contents

1	Introduction	3
2	5V to 3.3V Conversion at 1 MHz (2A Max I_{OUT})	3
3	5V to 3.3V Conversion at 500 kHz (4A Max I_{OUT})	5
4	5V to 2.5V Conversion at 1.5 MHz (3A Max I_{OUT})	7
5	5V to 2.5V Conversion at 378 kHz (2A Max I_{OUT})	9
6	5V to 1V Conversion at 303 kHz (3A Max I_{OUT})	11
7	3.3V to 0.8V Conversion at 242 kHz (2A Max I_{OUT})	13
8	3.3V to 0.9V Conversion at 545 kHz (3A Max I_{OUT}) DDR2 Application	15
9	3.3V to 1.8V Conversion at 272 kHz (2A Max I_{OUT}) All Ceramic Application	17
10	3.3V to 1.8V Conversion at 545 kHz (2A Max I_{OUT})	19

List of Figures

1	5V to 3.3V Conversion at 1 MHz (2A Max I_{OUT})	3
2	Efficiency vs V_{IN}	4
3	V_{OUT} : Output Ripple Voltage, 20mV AC/div	4
4	V_{OUT} : Output Voltage, 200mV AC/div I_{OUT} : Load Current, 1A/div	4
5	5V to 3.3V Conversion at 500 kHz (4A Max I_{OUT})	5
6	Efficiency vs V_{IN}	6
7	V_{OUT} : Output Voltage, 20mV AC/div	6
8	V_{OUT} : Output Voltage, 200mV AC/div I_{OUT} : Load Current, 1A/div	6
9	5V to 2.5V Conversion at 1.5 MHz (3A Max I_{OUT})	7
10	Efficiency vs V_{IN}	8
11	V_{OUT} : Output Voltage, 50mV AC/div	8
12	V_{OUT} : Output Voltage, 100mV AC/div I_{OUT} : Load Current, 1A/div	8
13	5V to 2.5V Conversion at 378 kHz (2A Max I_{OUT})	9
14	Efficiency vs V_{IN}	10
15	V_{OUT} : Output Voltage, 50mV AC/div	10
16	V_{OUT} : Output Voltage, 100mV AC/div I_{OUT} : Load Current, 1A/div	10
17	5V to 1V Conversion at 303 kHz (3A Max I_{OUT})	11
18	Efficiency vs V_{IN}	12
19	V_{OUT} : Output Voltage, 20mV AC/div	12
20	V_{OUT} : Output Voltage, 50mV AC/div I_{OUT} : Load Current, 1A/div	12
21	3.3V to 0.8V Conversion at 242 kHz (2A Max I_{OUT})	13
22	Efficiency vs V_{IN}	14
23	V_{OUT} : Output Voltage, 20mV AC/div	14
24	V_{OUT} : Output Voltage, 100mV AC/div I_{OUT} : Load Current, 2A/div	14

All trademarks are the property of their respective owners.

25	3.3V to 0.9V Conversion at 545 kHz (3A Max I_{OUT}) DDR2 Application	15
26	Efficiency vs V_{IN}	16
27	V_{OUT} : Output Voltage, 20mV AC/div	16
28	V_{OUT} : Output Voltage, 100mV AC/div I_{OUT} : Load Current, 1A/div	16
29	3.3V to 1.8V Conversion at 272 kHz (2A Max I_{OUT}) All Ceramic Application.....	17
30	Efficiency vs V_{IN}	18
31	V_{OUT} : Output Voltage, 20mV AC/div	18
32	V_{OUT} : Output Voltage, 200mV AC/div I_{OUT} : Load Current, 1A/div	18
33	3.3V to 1.8V Conversion at 545 kHz (2A Max I_{OUT})	19
34	Efficiency vs V_{IN}	20
35	V_{OUT} : Output Voltage, 20mV AC/div	20
36	V_{OUT} : Output Voltage, 100mV AC/div I_{OUT} : Load Current, 1A/div	20

List of Tables

1	Bill of Materials (5V to 3.3V Conversion at 1 MHz).....	4
2	Bill of Materials (5V to 3.3V Conversion at 500 kHz)	5
3	Bill of Materials (5V to 2.5V Conversion at 1.5 MHz)	7
4	Bill of Materials (5V to 2.5V Conversion at 378 kHz)	9
5	Bill of Materials (5V to 1V Conversion at 303 kHz)	11
6	Bill of Materials (3.3V to 0.8V Conversion at 242 kHz).....	13
7	Bill of Materials (3.3V to 0.9V Conversion at 545 kHz).....	15
8	Bill of Materials (3.3V to 1.8V Conversion at 272 kHz).....	17
9	Bill of Materials (3.3V to 1.8V Conversion at 545 kHz).....	19

1 Introduction

The LM1770 is a high efficiency synchronous buck controller that drives an external high side PFET and low side NFET. The controller utilizes a constant on-time control scheme which eliminates the need for external compensation components, allowing the power supply designer to minimize necessary board space and reduce costs.

Input voltages range from 3.3V to 5V, and the designs encompass common output voltages between 0.8V and 3.3V. Maximum output currents of 2A, 3A and 4A are demonstrated. Switching frequencies range between 242kHz and 1.5MHz depending on the operating conditions and the LM1770 timing option (for more information on how to determine switching frequency, see *LM1770 Low-Voltage SOT23 Synchronous Buck Controller With No External Compensation (SNVS403)*). Included with an explanation of each design is a bill-of-materials as well as efficiency, output ripple, and transient measurements.

2 5V to 3.3V Conversion at 1 MHz (2A Max I_{OUT})

This higher frequency design enables the use of a small valued inductor ($1 \mu\text{H}$) and a $68 \mu\text{F}$ OSCON output capacitor, reducing component size. A stable design is possible without the use of a feed-forward capacitor, further reducing necessary board space. For the PFET and the NFET, the SI3867DV and the SI3460DV are chosen due to their desirable $R_{DS(on)}$ specifications, current handling capabilities and small footprints. The 1000 ns LM1770 timing option is used to implement the 1 MHz frequency.

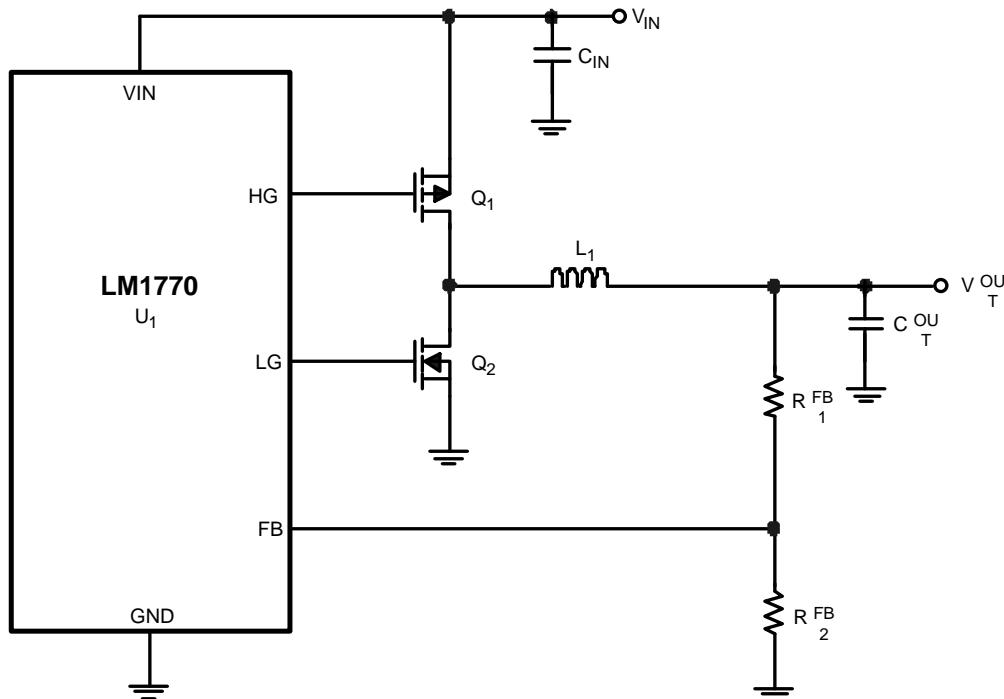
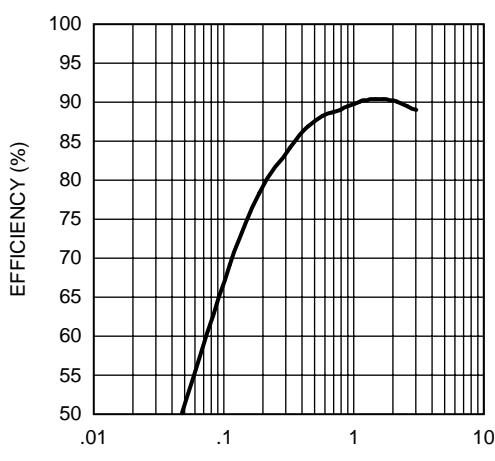
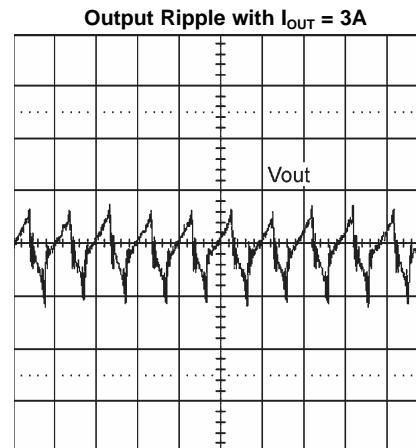
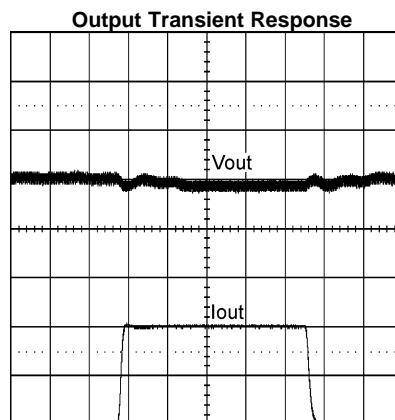


Figure 1. 5V to 3.3V Conversion at 1 MHz (2A Max I_{OUT})

Table 1. Bill of Materials (5V to 3.3V Conversion at 1 MHz)

ID	Part Number	Type	Size	Parameters	Vendor	Qty
U ₁	LM1770T	Synchronous Buck Controller	SOT23-5	1000 ns	Texas Instruments	1
C _{IN}	GRM32ER60J476ME20B	Input Capacitor	1210	47 μ F/X5R/6.3V	muRata	1
C _{OUT}	10SVPA68MAA	Output Capacitor	C6	68 μ F/OSCON/10V	Sanyo	1
L	DO1608C-102MLC	Inductor		1 μ H	Coilcraft	1
R _{FB1}	CRCW08052551	Resistor	0805	2.55 k Ω \pm 1%	Dale	1
R _{FB2}	CRCW08058060	Resistor	0805	806 Ω \pm 1%	Dale	1
Q ₁	SI3867DV	PFET	TSOP-6	SI3867DV	Siliconix	1
Q ₂	SI3460DV	NFET	TSOP-6	SI3460DV	Siliconix	1

**Figure 2. Efficiency vs V_{IN}** **Figure 3. V_{OUT} : Output Ripple Voltage, 20mV AC/div****Figure 4. V_{OUT} : Output Voltage, 200mV AC/div
 I_{OUT} : Load Current, 1A/div**

3 5V to 3.3V Conversion at 500 kHz (4A Max I_{OUT})

This design operates at 500 kHz and utilizes larger valued components to enable a high maximum output current. A 2.2 μ H inductor and a 150 μ F POSCAP output capacitor are used to generate the necessary ripple at the output and a 1 nF feed-forward capacitor is used to help stabilize the design. Due to the large current being switched on the board, a larger 150 μ F electrolytic input capacitor is used. The SI9433BDY PFET and SI4894DY NFET provide the necessary power handling capabilities to switch the large output current in this design, and the 2000 ns LM1770 timing option operates at 500 kHz in this configuration.

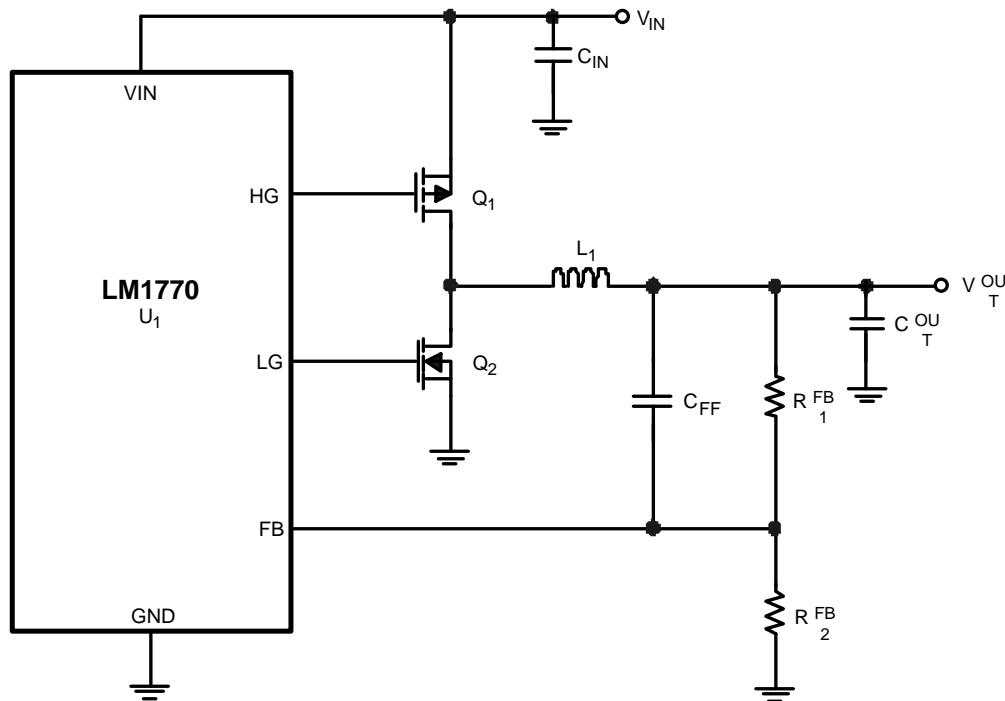
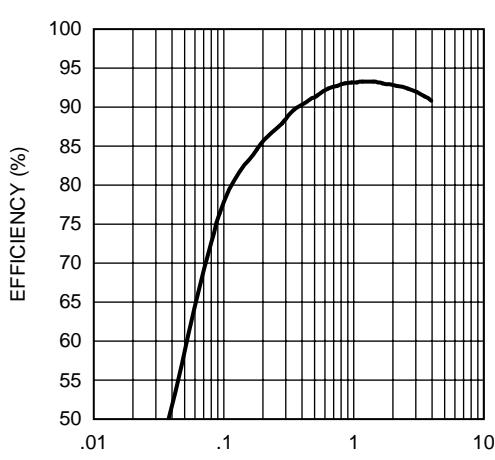
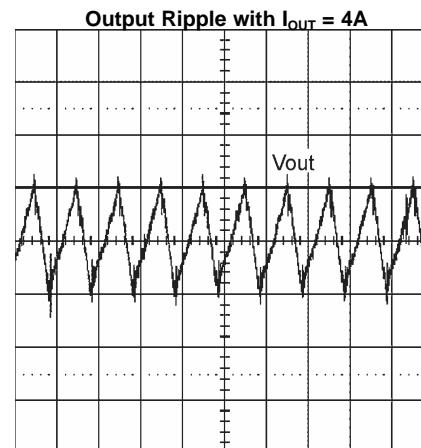
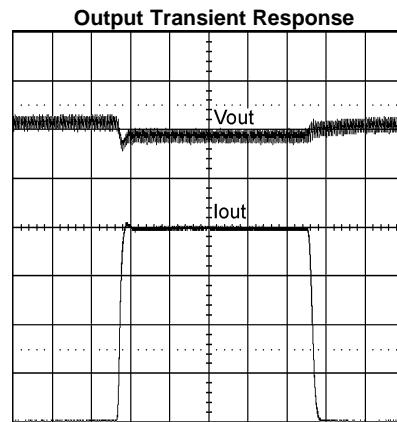


Figure 5. 5V to 3.3V Conversion at 500 kHz (4A Max I_{OUT})

Table 2. Bill of Materials (5V to 3.3V Conversion at 500 kHz)

ID	Part Number	Type	Size	Parameters	Manufacturer	Qty
U ₁	LM1770U	Synchronous Buck Controller	SOT23-5	2000 ns	Texas Instruments	1
C _{FF}	VJ0805Y102KXXM	Capacitor	0805	1 nF/X7R/25V	Vitramon	1
C _{IN}	EEUFC0J151	Capacitor		150 μ F/Electrolytic/6.3V	Panasonic	1
C _{OUT}	4TPB150MC	Capacitor	C	150 μ F/POSCAP/4V	Sanyo	1
L	DO3316P-222ML	Inductor		2.2 μ H	Coilcraft	1
Q ₁	SI9433BDY	PFET	SO-8	SI9433BDY	Siliconix	1
Q ₂	SI4894DY	NFET	SO-8	SI4894DY	Siliconix	1
R _{FB1}	CRCW08052492	Resistor	0805	24.9 k Ω \pm 1%	Dale	1
R _{FB2}	CRCW08058061	Resistor	0805	8.06 k Ω \pm 1%	Dale	1


Figure 6. Efficiency vs V_{IN}

Figure 7. V_{OUT} : Output Voltage, 20mV AC/div

**Figure 8. V_{OUT} : Output Voltage, 200mV AC/div
 I_{OUT} : Load Current, 1A/div**

4 5V to 2.5V Conversion at 1.5 MHz (3A Max I_{OUT})

The use of a small valued inductor (1.5 μ H) is made possible by the high frequency operation. A 68 μ F, low profile, POSCAP output capacitor is used, along with a 10 nF ceramic feed-forward capacitor, to ensure stability. The 500 ns LM1770 timing option allows for the 1.5 MHz switching frequency, and again the SI3867DV and SI3460DV FETs are used.

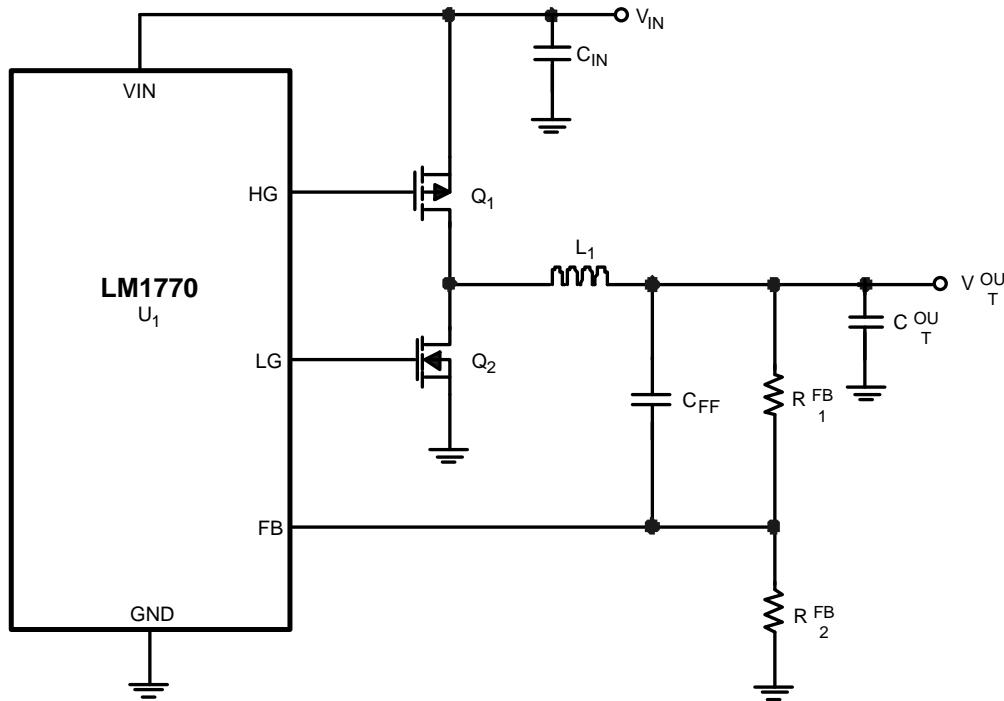
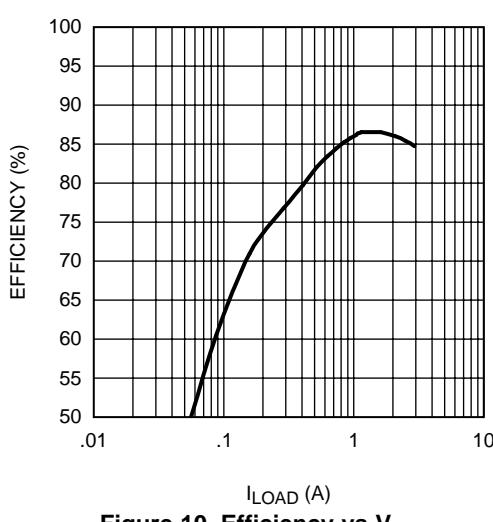
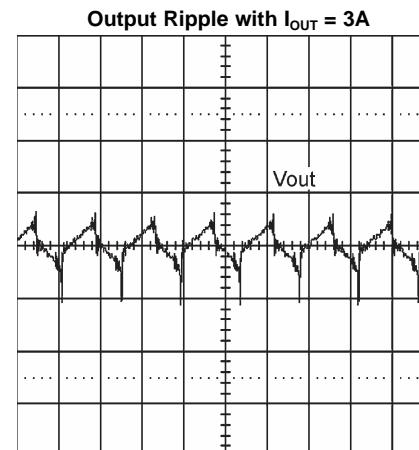
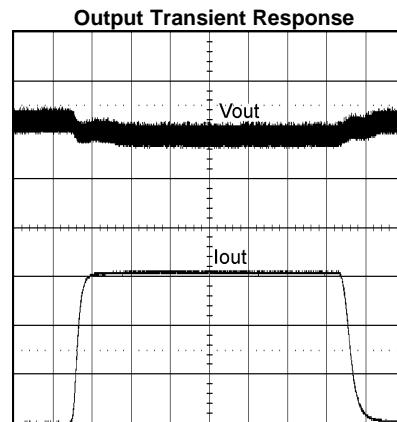


Figure 9. 5V to 2.5V Conversion at 1.5 MHz (3A Max I_{OUT})

Table 3. Bill of Materials (5V to 2.5V Conversion at 1.5 MHz)

ID	Part Number	Type	Size	Parameters	Vendor	Qty
U ₁	LM1770S	Synchronous Buck Controller	SOT23-5	500 ns	Texas Instruments	1
C _{OUT}	4TB68M	Capacitor	B2	68 μ F/POSCAP/4V	Sanyo	1
C _{FF}	VJ0805Y103KXXM	Capacitor	0805	10 nF/X7R/25V	Vitramon	1
C _{IN}	GRM32ER61A226KA65B	Capacitor	1210	22 μ F/X5R/10V	muRata	1
C _{OUT}	4TB68M	Capacitor	B2	68 μ F/POSCAP/4V	Sanyo	1
L	DO3316P-152ML	Inductor		1.5 μ H	Coilcraft	1
Q ₁	SI3867DV	PFET	TSOP-6	SI3867DV	Siliconix	1
Q ₂	SI3460DV	NFET	TSOP-6	SI3460DV	Siliconix	1
R _{FB1}	CRCW08051692	Resistor	0805	16.9 k Ω \pm 1%	Dale	1
R _{FB2}	CRCW080508061	Resistor	0805	8.06 k Ω \pm 1%	Dale	1


Figure 10. Efficiency vs V_{IN}

Figure 11. V_{OUT} : Output Voltage, 50mV AC/div

**Figure 12. V_{OUT} : Output Voltage, 100mV AC/div
 I_{OUT} : Load Current, 1A/div**

5 5V to 2.5V Conversion at 378 kHz (2A Max I_{OUT})

This design utilizes small components allowing a minimally sized complete power supply solution. A 5.0 μ H, small footprint inductor is used along with a 47 μ F POSCAP output capacitor to minimize component size. A 10 nF ceramic feed-forward capacitor helps improve stability, and again the SI3867DV and SI3460DV FETs are used. The 2000 ns LM1770 timing option sets the operating frequency at 378 kHz. This design is identical to the LM1770 Demo Board and more information on the general design as well as the layout of the PCB is available in the *AN-1400 LM1770 Evaluation Board User's Guide (SNVA125)*.

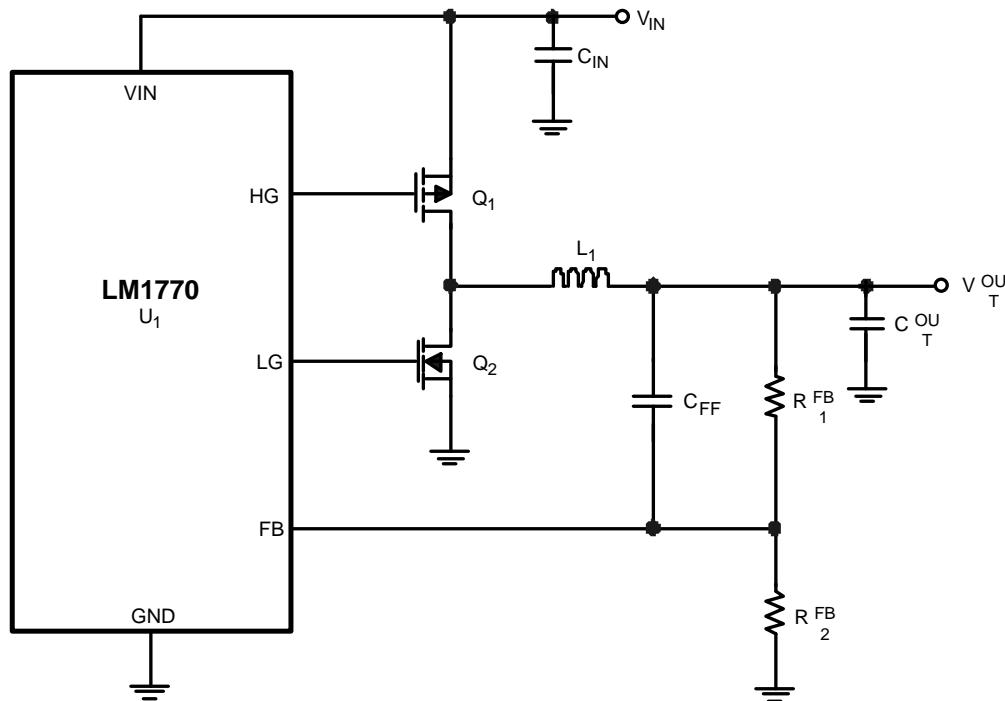
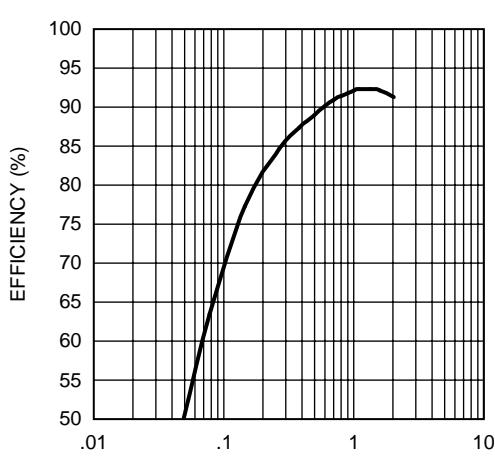
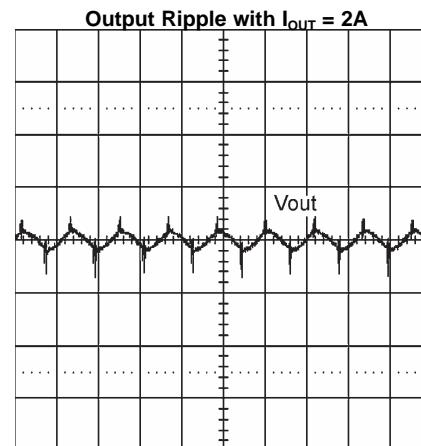
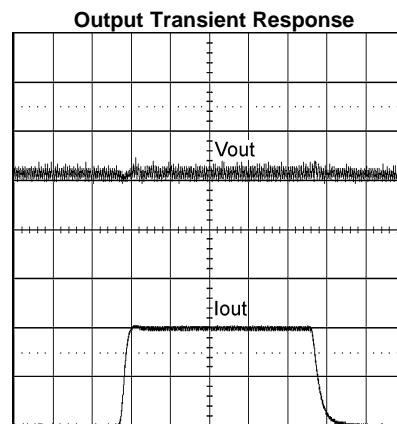


Figure 13. 5V to 2.5V Conversion at 378 kHz (2A Max I_{OUT})

Table 4. Bill of Materials (5V to 2.5V Conversion at 378 kHz)

ID	Part Number	Type	Size	Parameters	Vendor	Qty
U ₁	LM1770U	Synchronous Buck Controller	SOT23-5	2000 ns	Texas Instruments	1
C _{FF}	VJ0603Y103KXXA	Capacitor	0603	10 nF/X7R/25V	Vitramon	1
C _{IN}	GRM21BR60J226ME39B	Capacitor	0805	22 μ F/X5R/6.3V	muRata	1
C _{OUT}	4TPC47M	Capacitor	B1	47 μ F/POSCAP/4V	Sanyo	1
L	MSS7341-502NX	Inductor		5.0 μ H	Coilcraft	1
Q ₁	SI3867DV	PFET	TSOP-6	SI3867DV	Siliconix	1
Q ₂	SI3460DV	NFET	TSOP-6	SI3460DV	Siliconix	1
R _{FB1}	CRCW06032102F	Resistor	0603	21 k Ω \pm 1%	Dale	1
R _{FB2}	CRCW06031002	Resistor	0603	10 k Ω \pm 1%	Dale	1


Figure 14. Efficiency vs V_{IN}

Figure 15. V_{OUT} : Output Voltage, 50mV AC/div

**Figure 16. V_{OUT} : Output Voltage, 100mV AC/div
 I_{OUT} : Load Current, 1A/div**

6 5V to 1V Conversion at 303 kHz (3A Max I_{OUT})

This design illustrates the LM1770's performance at a low frequency of operation as well as a low output voltage. A 6.8 μ H inductor is used along with a low ESR 68 μ F OSCON output capacitor to minimize the voltage ripple at the output, while still ensuring stability. A 10 nF feed forward capacitor is also used, along with the SI3867DV PFET and the SI3460DV NFET. The 2000 ns LM1770 provides the 303 kHz switching frequency.

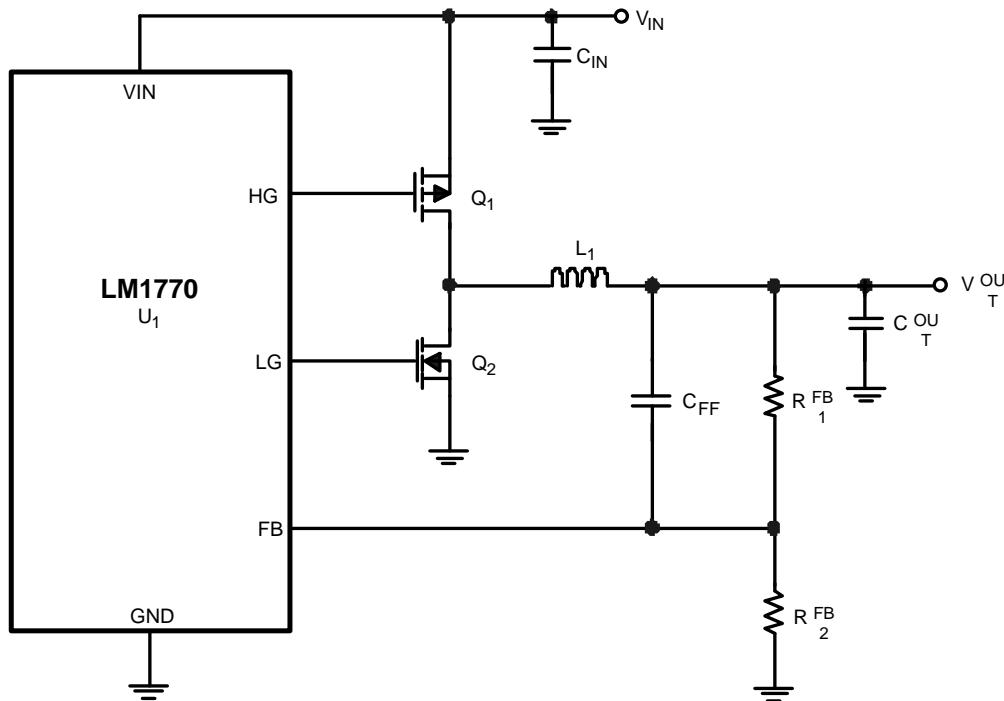


Figure 17. 5V to 1V Conversion at 303 kHz (3A Max I_{OUT})

Table 5. Bill of Materials (5V to 1V Conversion at 303 kHz)

ID	Part Number	Type	Size	Parameters	Vendor	Qty
U ₁	LM1770T	Synchronous Buck Controller	SOT23-5	1000 ns	Texas Instruments	1
C _{FF}	VJ0805Y103KXXM	Capacitor	0805	10 nF/X7R/25V	Vitramon	1
C _{IN}	GRM43SR60J107ME20B	Capacitor	1812	100 μ F/X5R/6.3V	muRata	1
C _{OUT}	6SVPC100M	Capacitor	B6	100 μ F/OSCON/6.3V	Sanyo	1
L	DO3316P-682ML	Inductor		6.8 μ H	Coilcraft	1
Q ₁	SI3867DV	PFET	TSOP-6	SI3867DV	Siliconix	1
Q ₂	SI3460DV	NFET	TSOP-6	SI3460DV	Siliconix	1
R _{FB} ₁	CRCW08052001	Resistor	0805	2 k Ω \pm 1%	Dale	1
R _{FB} ₂	CRCW08058061	Resistor	0805	8.06 k Ω \pm 1%	Dale	1

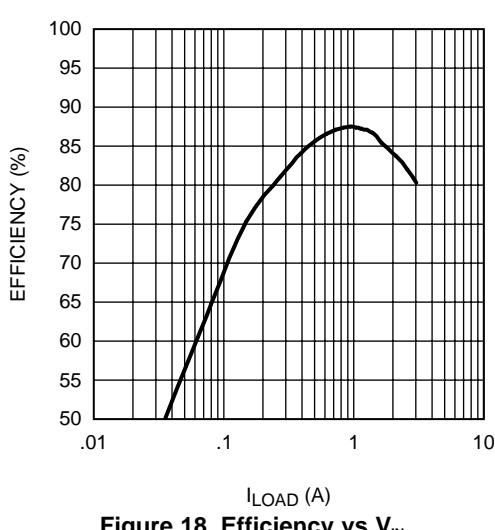


Figure 18. Efficiency vs V_{IN}


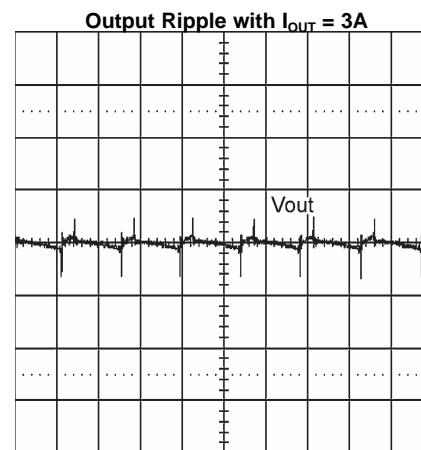


Figure 19. V_{OUT} : Output Voltage, 20mV AC/div

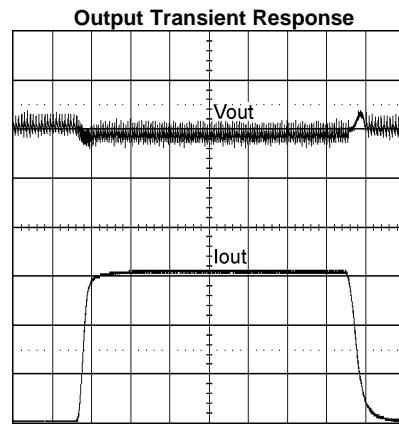

**Figure 20. V_{OUT} : Output Voltage, 50mV AC/div
 I_{OUT} : Load Current, 1A/div**

7 3.3V to 0.8V Conversion at 242 kHz (2A Max I_{OUT})

This design regulates the output at the LM1770's reference voltage. There are no feedback resistors necessary for this design as the output voltage is connected directly to the feedback pin. A 6.8 μ H inductor and a 150 μ F POSCAP output capacitor are used to create enough ripple at the output to ensure stability. No feedforward capacitor is necessary and the SI3867DV and SI3460DV FETs are used.

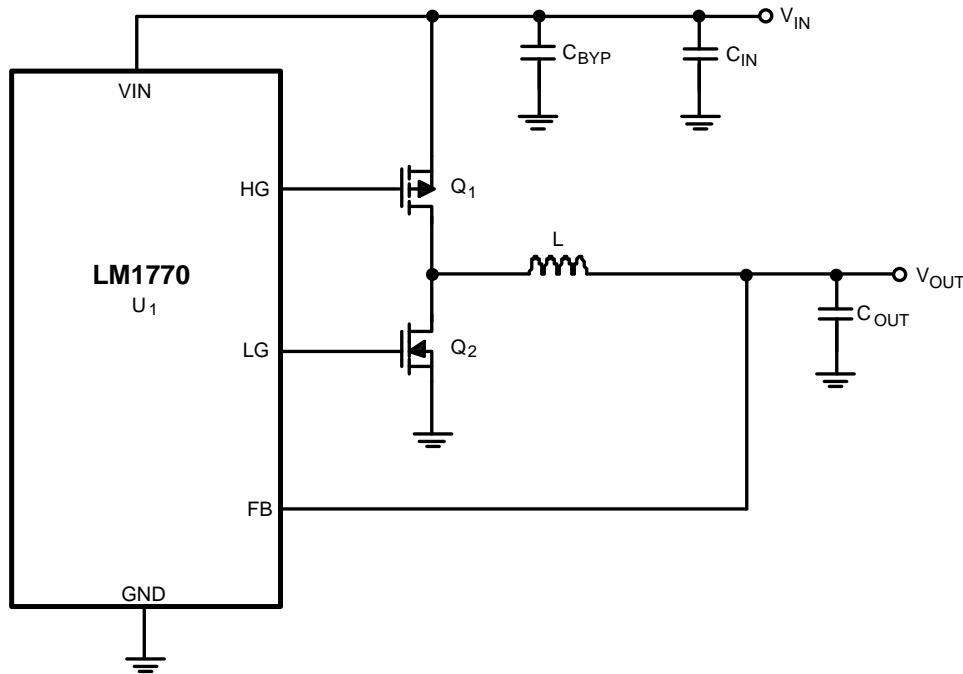


Figure 21. 3.3V to 0.8V Conversion at 242 kHz (2A Max I_{OUT})

Table 6. Bill of Materials (3.3V to 0.8V Conversion at 242 kHz)

ID	Part Number	Type	Size	Parameters	Vendor	Qty
U ₁	LM1770T	Synchronous Buck Controller	SOT23-5	1000ns	Texas Instruments	1
C _{BYP}	VJ0805Y104KXXM	Capacitor	0805	100 nF/X7R/25V	Vitramon	1
C _{IN}	GRM32ER60J476ME20B	Capacitor	1210	47 μ F/X5R/6.3V	muRata	1
C _{OUT}	4TPB150MC	Capacitor	C	150 μ F/POSCAP/6.3V	Sanyo	1
L	DO3316P-682ML	Inductor		6.8 μ H	Coilcraft	1
Q ₁	SI3867DV	PFET	TSOP-6	SI3867DV	Siliconix	1
Q ₂	SI3460DV	NFET	TSOP-6	SI3460DV	Siliconix	1

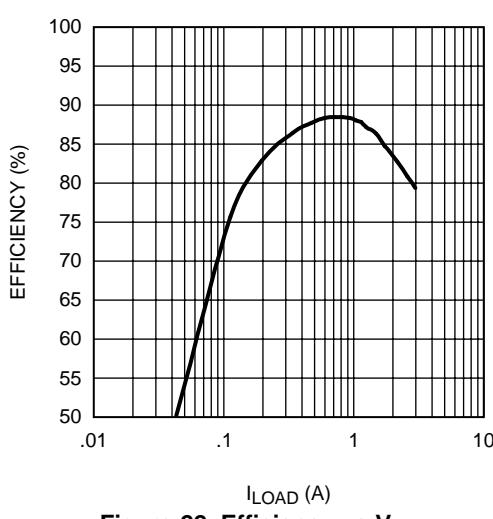


Figure 22. Efficiency vs V_{IN}


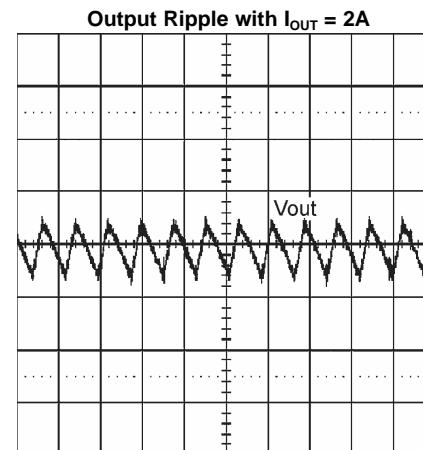


Figure 23. V_{OUT} : Output Voltage, 20mV AC/div

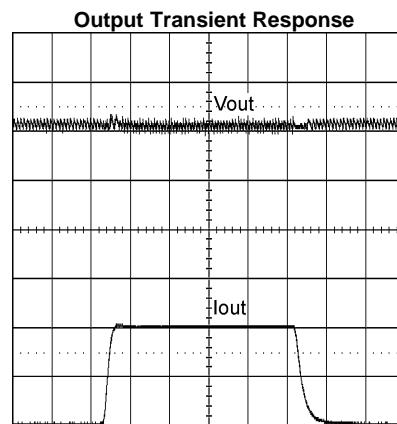

**Figure 24. V_{OUT} : Output Voltage, 100mV AC/div
 I_{OUT} : Load Current, 2A/div**

8 3.3V to 0.9V Conversion at 545 kHz (3A Max I_{OUT}) DDR2 Application

This design operates at a higher frequency as compared to the 0.8V design above. This facilitates the use of a smaller 3.3 μ H inductor that allows the complete power supply to fit on the LM1770 evaluation board PCB. The output is set at 0.9V to provide a VTT voltage for use in DDR2 applications. The design is capable of both sinking and sourcing current. A 100 μ F POSCAP is used as the output capacitor, and again the SI3867DV and SI3460DV FETs are used. The 500 ns LM1770 timing option operates at 545 kHz for this application.

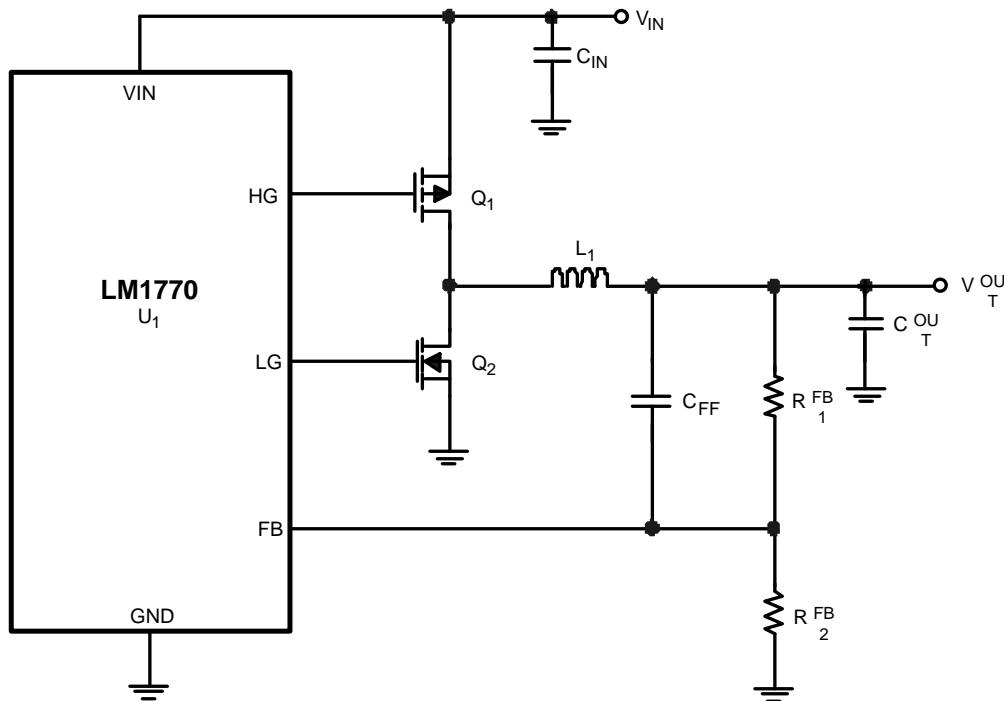


Figure 25. 3.3V to 0.9V Conversion at 545 kHz (3A Max I_{OUT}) DDR2 Application

Table 7. Bill of Materials (3.3V to 0.9V Conversion at 545 kHz)

ID	Part Number	Type	Size	Parameters	Vendor	Qty
U ₁	LM1770S	Synchronous Buck Controller	SOT23-5	500 ns	Texas Instruments	1
C _{FF}	VJ0603Y102KXXM	Capacitor	0603	1 nF/X7R/25V	Vitramon	1
C _{IN}	GRM21BR60J226ME39B	Capacitor	0805	22 μ F/X5R/6.3V	muRata	1
C _{OUT}	6TPB100MA	Capacitor	B2	100 μ F/POSCAP/6.3V	Sanyo	1
L	MSS7341-332NX	Inductor		3.3 μ H	Coilcraft	1
Q ₁	SI3867DV	PFET	TSOP-6	SI3867DV	Siliconix	1
Q ₂	SI3460DV	NFET	TSOP-6	SI3460DV	Siliconix	1
R _{FB1}	CRCW06031001	Resistor	0603	1 k Ω \pm 1%	Dale	1
R _{FB2}	CRCW06038061	Resistor	0603	8.06 k Ω \pm 1%	Dale	1

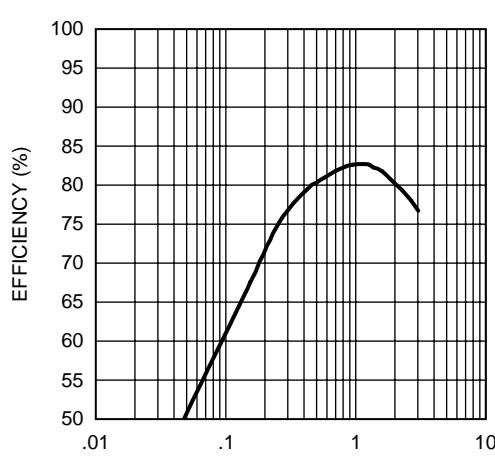


Figure 26. Efficiency vs V_{IN}


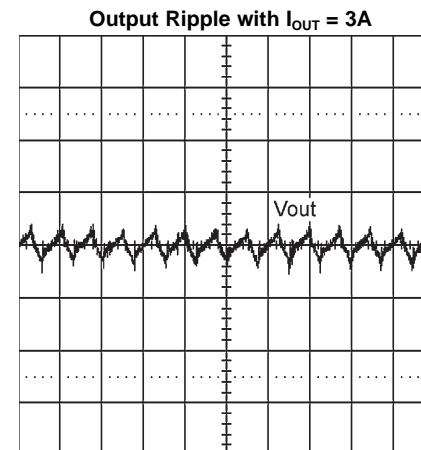


Figure 27. V_{OUT} : Output Voltage, 20mV AC/div

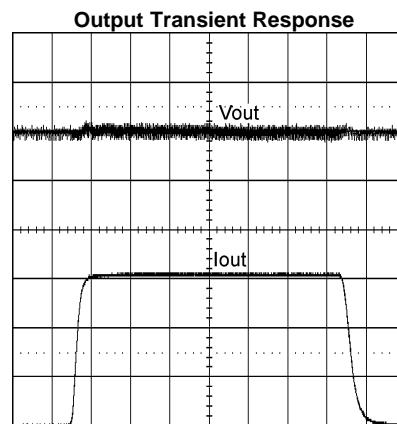

**Figure 28. V_{OUT} : Output Voltage, 100mV AC/div
 I_{OUT} : Load Current, 1A/div**

9 3.3V to 1.8V Conversion at 272 kHz (2A Max I_{OUT}) All Ceramic Application

This design incorporates a 22 μ F ceramic output capacitor. Due of the lack of ESR on ceramic capacitors, a separate 50 m Ω resistor is used for creating sufficient ripple at the output. A 3.3 μ H inductor value is used along with a 10 nF feed-forward capacitor to help ensure stability. The SI3867DV and SI3460DV FETs are again used as the high side and low side switches, respectively. The 2000 ns LM1770 timing option accommodates 272 kHz operation.

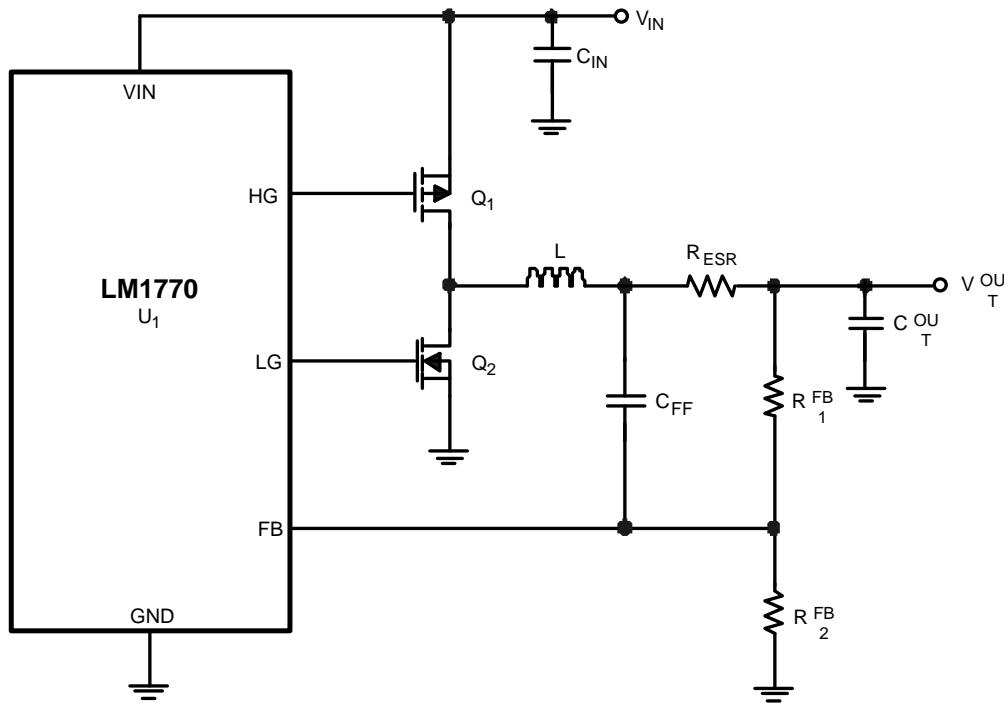
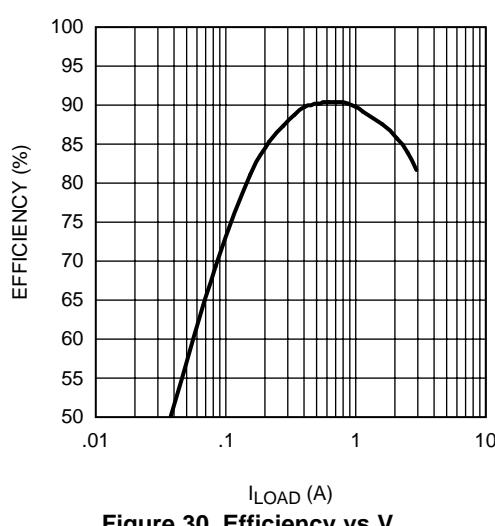
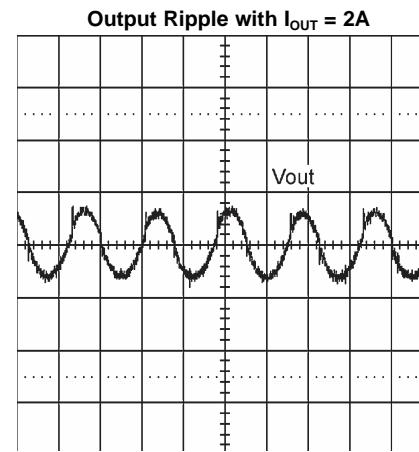
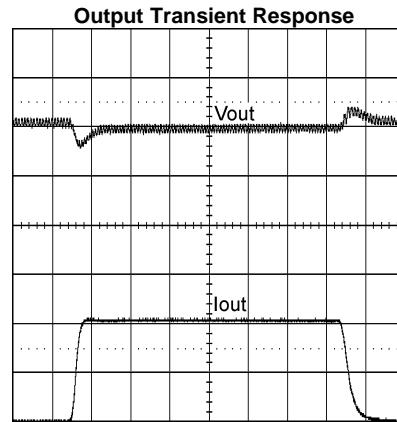


Figure 29. 3.3V to 1.8V Conversion at 272 kHz (2A Max I_{OUT}) All Ceramic Application

Table 8. Bill of Materials (3.3V to 1.8V Conversion at 272 kHz)

ID	Part Number	Type	Size	Parameters	Vendor	Qty
U ₁	LM1770U	Synchronous Buck Controller	SOT23-5	2000 ns	Texas Instruments	1
C _{FF}	VJ0805Y103KXXA	Capacitor	0805	10 nF/X7R/25V	Vitramon	1
C _{IN}	GRM32ER60J476ME20B	Capacitor	1210	47 μ F/X5R/6.3V	muRata	1
C _{OUT}	GRM32ER61A226KA65B	Capacitor	1210	22 μ F/X5R/10V	muRata	1
L	DO3316P-332ML	Inductor		3.3 μ H	Coilcraft	1
Q ₁	SI3867DV	PFET	TSOP-6	SI3867DV	Siliconix	1
Q ₂	SI3460DV	NFET	TSOP-6	SI3460DV	Siliconix	1
R _{ESR}	WSL-1206	Resistor	1206	.05 Ω \pm 1%	Dale	1
R _{FB1}	CRCW08051241	Resistor	0805	1.24 k Ω \pm 1%	Dale	1
R _{FB2}	CRCW08051001	Resistor	0805	1.00 k Ω \pm 1%	Dale	1


Figure 30. Efficiency vs V_{IN}

Figure 31. V_{OUT} : Output Voltage, 20mV AC/div

**Figure 32. V_{OUT} : Output Voltage, 200mV AC/div
 I_{OUT} : Load Current, 1A/div**

10 3.3V to 1.8V Conversion at 545 kHz (2A Max I_{OUT})

This is another design utilizing small sized components chosen to fit on the LM1770 evaluation board PCB. A 6.2 μ H inductor along with a 68 μ F POSCAP capacitor are used to implement the output filter, and a 10 nF feed-forward capacitor is added to help improve stability. Again the SI3867DV and the SI3460DV FETs are used, and the 1000 ns LM1770 timing option accommodates the 545 kHz switching frequency.

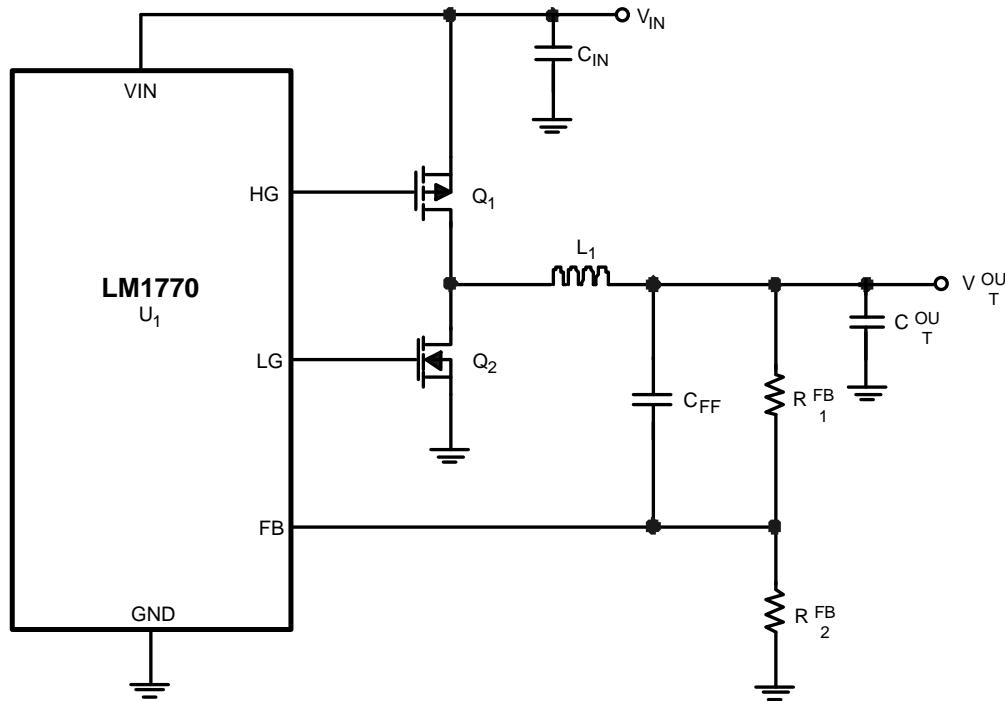
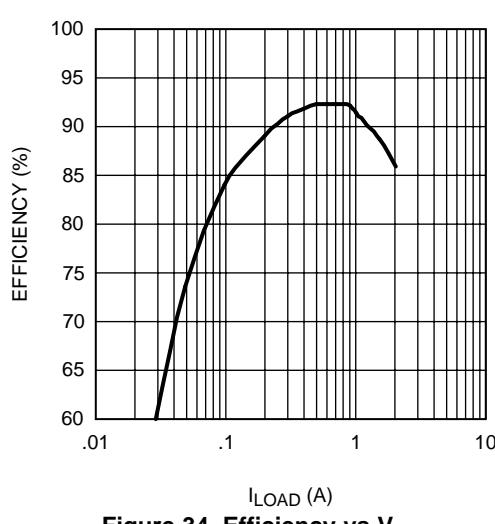
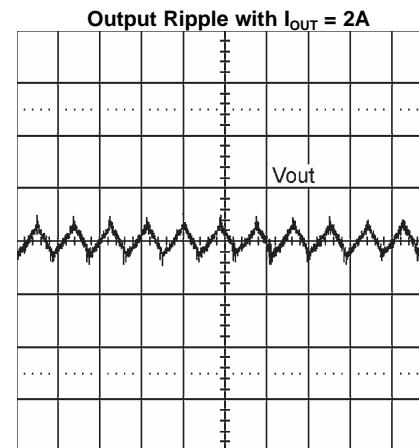
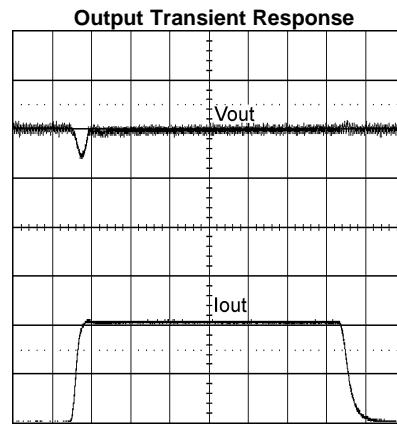


Figure 33. 3.3V to 1.8V Conversion at 545 kHz (2A Max I_{OUT})

Table 9. Bill of Materials (3.3V to 1.8V Conversion at 545 kHz)

ID	Part Number	Type	Size	Parameters	Vendor	Qty
U ₁	LM1770T	Synchronous Buck Controller	SOT23-5	1000 ns	Texas Instruments	1
C _{FF}	VJ0603Y103KXXM	Capacitor	0603	10 nF/X7R/25V	Vitramon	1
C _{IN}	GRM32ER61A226KA65B	Capacitor	0805	22 μ F/X5R/6.3V	muRata	1
C _{OUT}	4TPB68M	Capacitor	B2	68 μ F/POSCAP/4.0V	Sanyo	1
L	MSS7341-622NX	Inductor		6.2 μ H	Coilcraft	1
Q ₁	SI3867DV	PFET	TSOP-6	SI3867DV	Fairchild	1
Q ₂	SI3460DV	NFET	TSOP-6	SI3460DV	Siliconix	1
R _{FB1}	CRCW06031002	Resistor	0603	10 k Ω \pm 1%	Dale	1
R _{FB2}	CRCW06038061	Resistor	0603	8.06 k Ω \pm 1%	Dale	1


Figure 34. Efficiency vs V_{IN}

Figure 35. V_{OUT} : Output Voltage, 20mV AC/div

**Figure 36. V_{OUT} : Output Voltage, 100mV AC/div
 I_{OUT} : Load Current, 1A/div**

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products	Applications		
Audio	www.ti.com/audio	Automotive and Transportation	www.ti.com/automotive
Amplifiers	amplifier.ti.com	Communications and Telecom	www.ti.com/communications
Data Converters	dataconverter.ti.com	Computers and Peripherals	www.ti.com/computers
DLP® Products	www.dlp.com	Consumer Electronics	www.ti.com/consumer-apps
DSP	dsp.ti.com	Energy and Lighting	www.ti.com/energy
Clocks and Timers	www.ti.com/clocks	Industrial	www.ti.com/industrial
Interface	interface.ti.com	Medical	www.ti.com/medical
Logic	logic.ti.com	Security	www.ti.com/security
Power Mgmt	power.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video
RFID	www.ti-rfid.com	TI E2E Community	
OMAP Applications Processors	www.ti.com/omap	e2e.ti.com	
Wireless Connectivity	www.ti.com/wirelessconnectivity		