

**Test Data  
For PMP9386  
3/24/2014**



---

## Table of Contents

1. Design Specifications .....	3
2. Circuit Description.....	3
3. PMP9386 Board Photos .....	4
4. Thermal Data.....	6
5. Efficiency .....	7
5.1 Efficiency Chart .....	7
5.2 Efficiency Data.....	7
6 Waveforms.....	8
6.1 Load Transient Response .....	8
6.2 Startup .....	9
6.3 Output Voltage Ripple and Switch Node Voltage .....	11
7 Loop Frequency Response .....	13

---

## 1. Design Specifications


<b>Vin Minimum</b>	<b>14VDC</b>
<b>Vin Maximum</b>	<b>15.5VDC</b>
<b>Vout</b>	<b>24VDC</b>
<b>Iout</b>	<b>8A Max.</b>
<b>Approximate Switching Frequency</b>	<b>125KHz per Phase (250KHz Effective)</b>

## 2. Circuit Description


PMP9386 is a Dual-Phase Synchronous Boost Converter which accepts an input voltage of 14Vin to 15.5Vin and provides an output of 24Vout capable of supplying a maximum of 8A of current to the load. This design was built on the PMP9309 REVC PCB (4-layered board; 2 oz. Copper on Top and Bottom layers, 1 oz. Copper on two inner layers). Design uses two LM5122 Synchronous Boost controllers and CSD18531Q5A FETs. All tests in this report were performed at the highest input current condition of 14Vin.

### 3. PMP9386 Board Photos

Board Dimensions: 7" x 6.5"

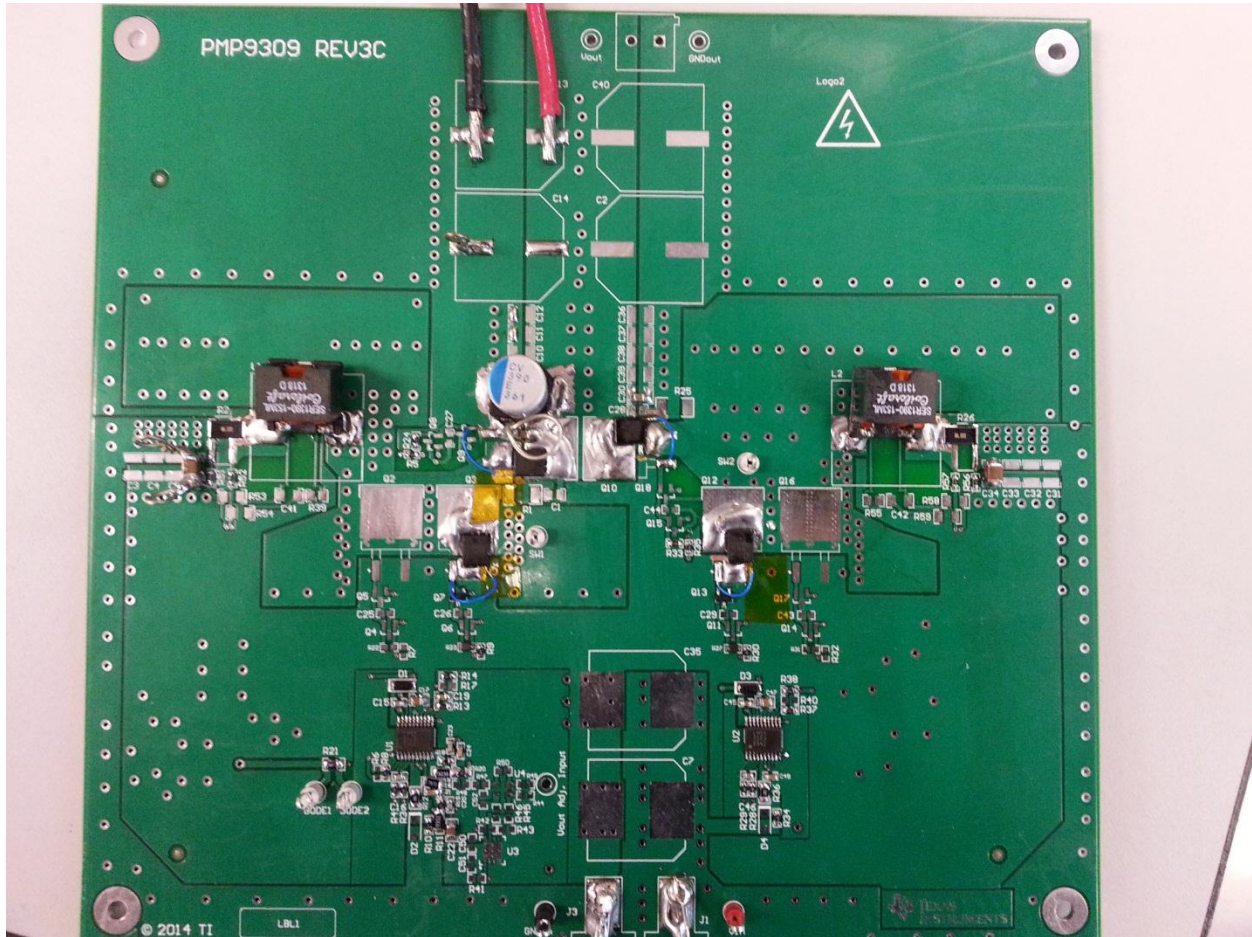


Board Photo (Top)

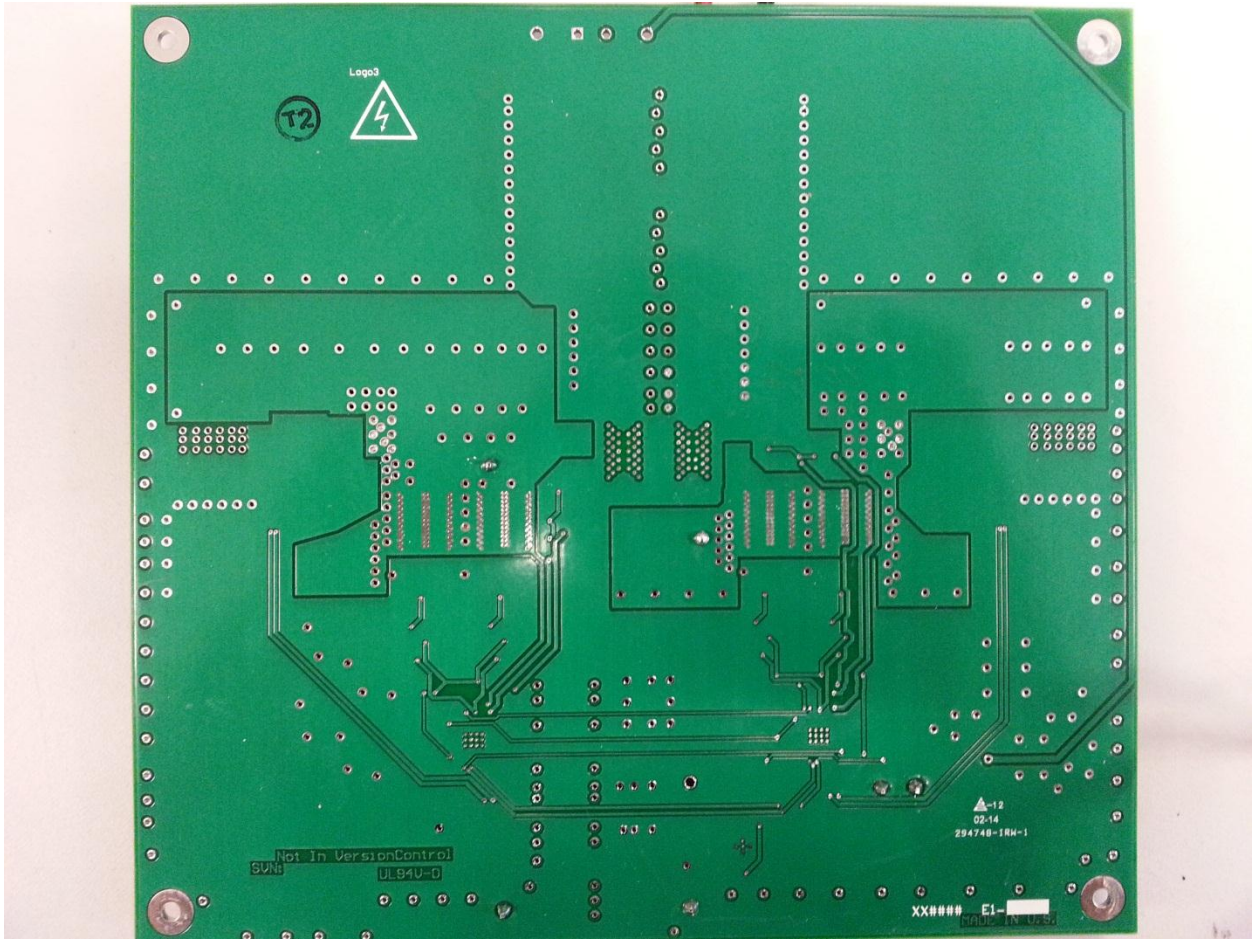

**Board Photo (Bottom)**


#### 4. Thermal Data

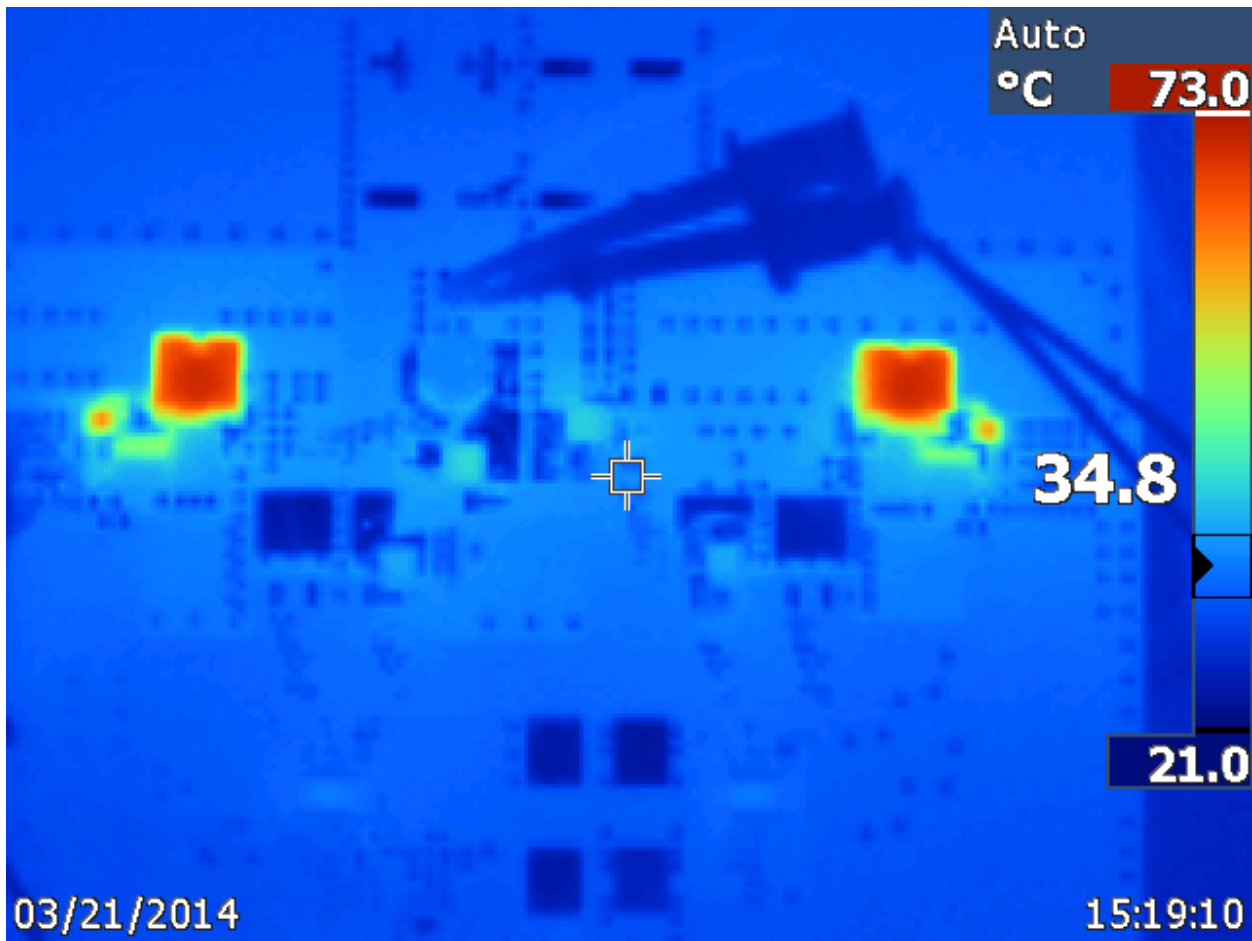

IR thermal image taken at steady state with 14Vin and 8A load (no airflow)

## 5. Efficiency

### 5.1 Efficiency Chart

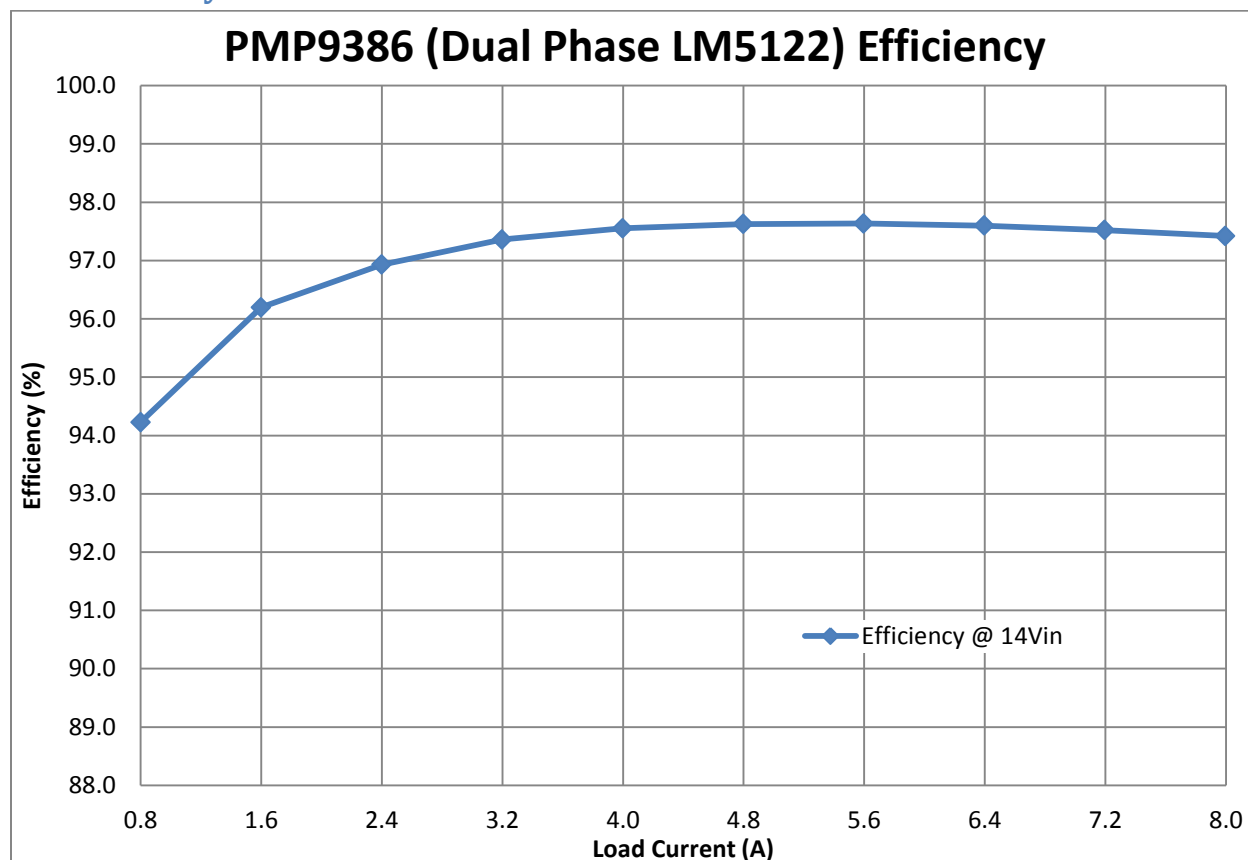


### 5.2 Efficiency Data

Vin (V)	Iin (A)	Vout (V)	Iout (A)	Pin (W)	Pout (W)	Efficiency (%)
14.081	1.457	24.201	0.7988	20.51602	19.33176	94.2
14.056	2.86	24.195	1.5983	40.20016	38.67087	96.2
14.031	4.265	24.193	2.3976	59.84222	58.00514	96.9
14.005	5.672	24.193	3.1968	79.43636	77.34018	97.4
13.98	7.089	24.192	3.9963	99.10422	96.67849	97.6
13.955	8.516	24.192	4.7958	118.8408	116.02	97.6
13.929	9.953	24.192	5.5951	138.6353	135.3567	97.6
13.903	11.401	24.192	6.3948	158.5081	154.703	97.6
13.877	12.86	24.191	7.1942	178.4582	174.0349	97.5
13.861	14.32	24.191	7.9935	198.4895	193.3708	97.4

## 6 Waveforms


### 6.1 Load Transient Response

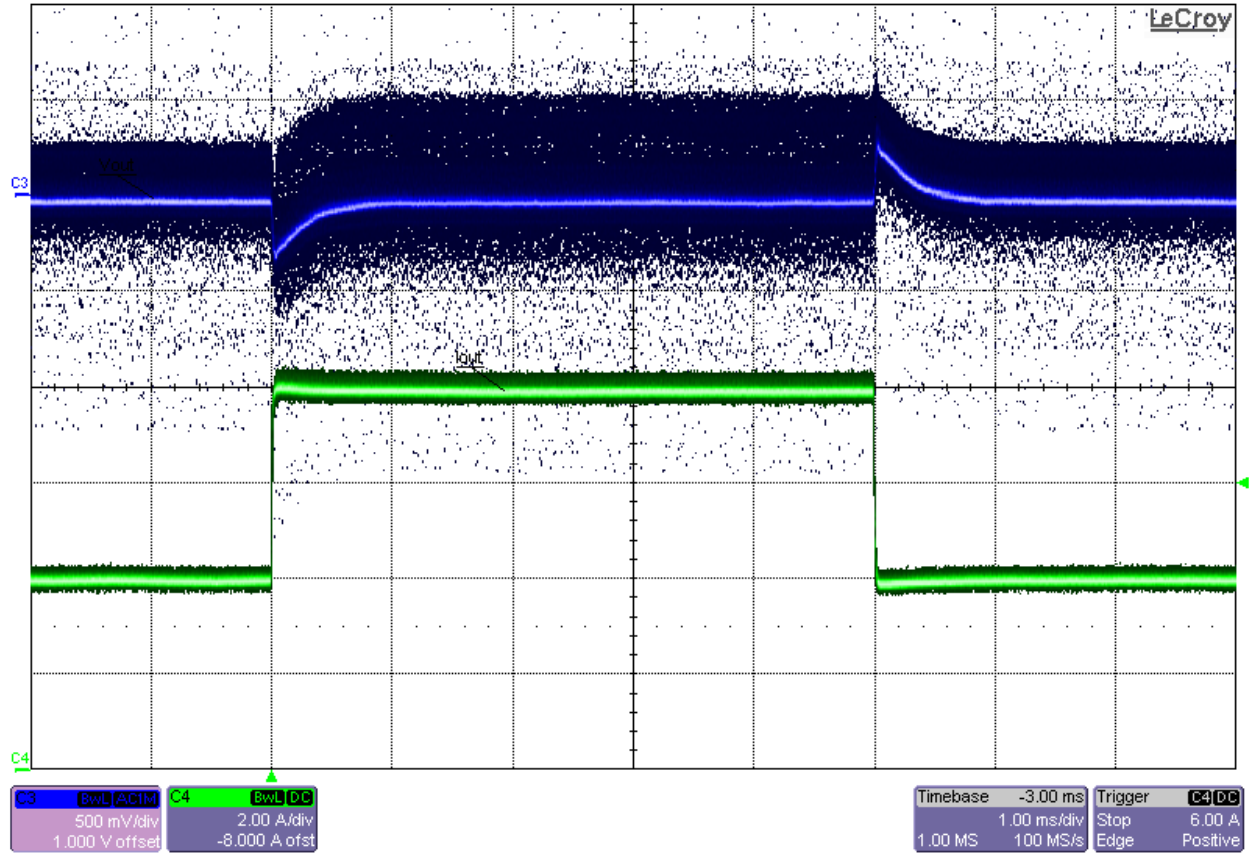


Load Transient Response at 14V<sub>in</sub> and 50%-to-100% (4A-to-8A) Load Step



## 6.2 Startup

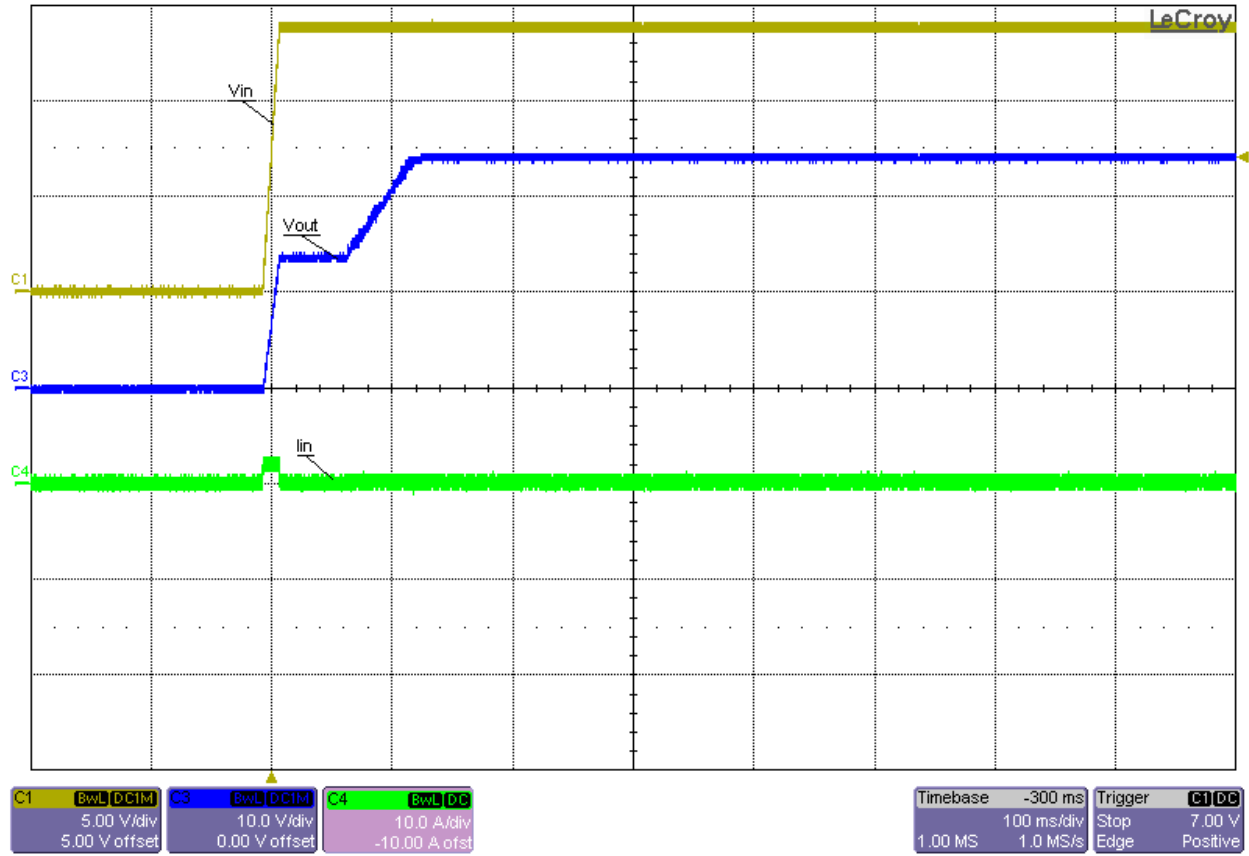


Startup into No Load at 14Vin

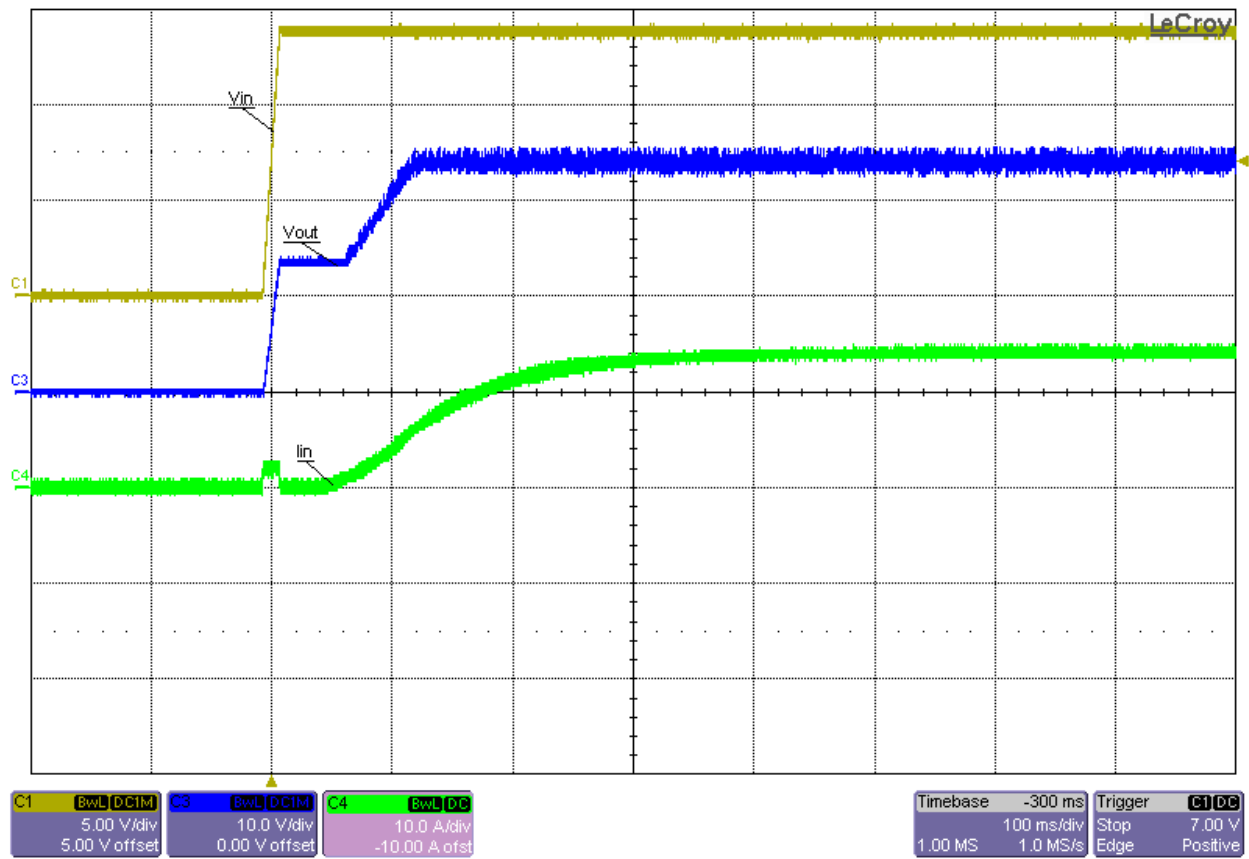


**Startup into Full (8A) Load at 14Vin**
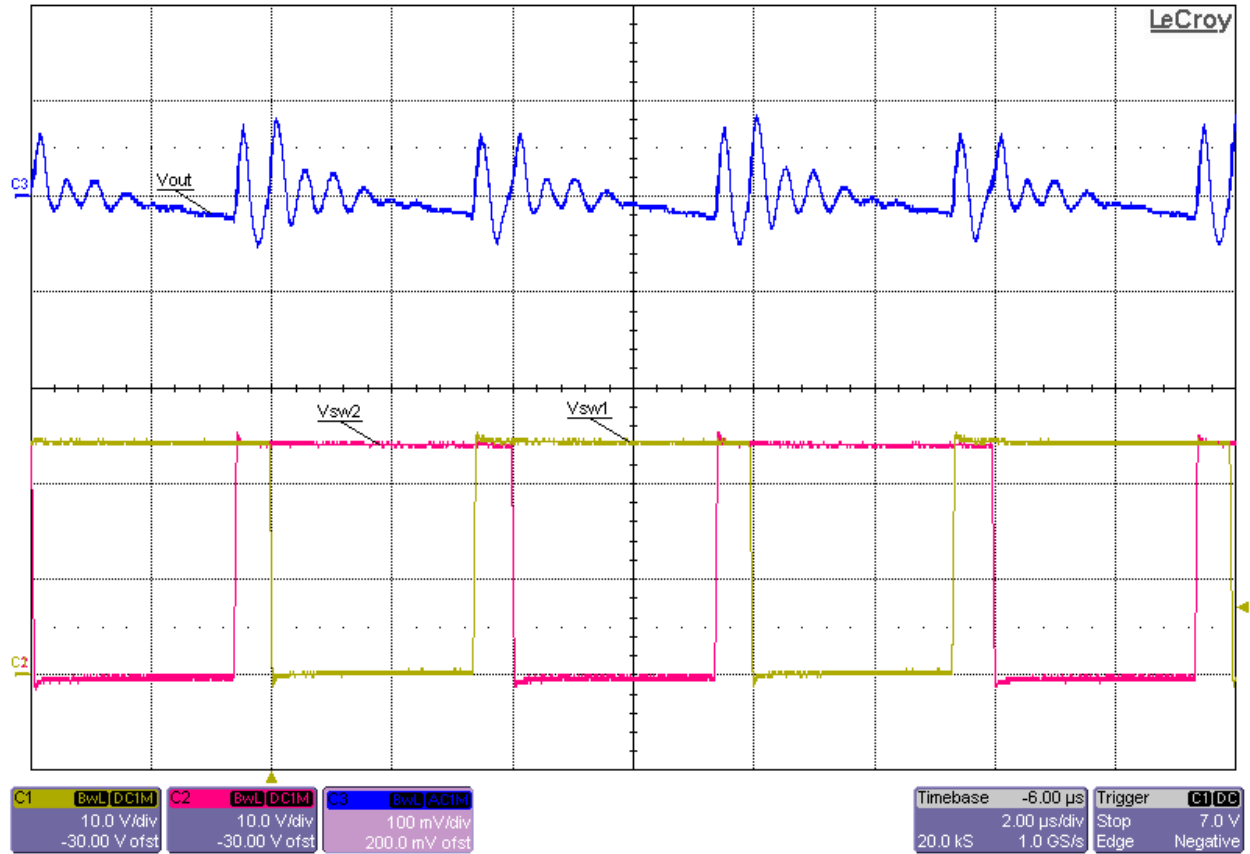
### 6.3 Output Voltage Ripple and Switch Node Voltage




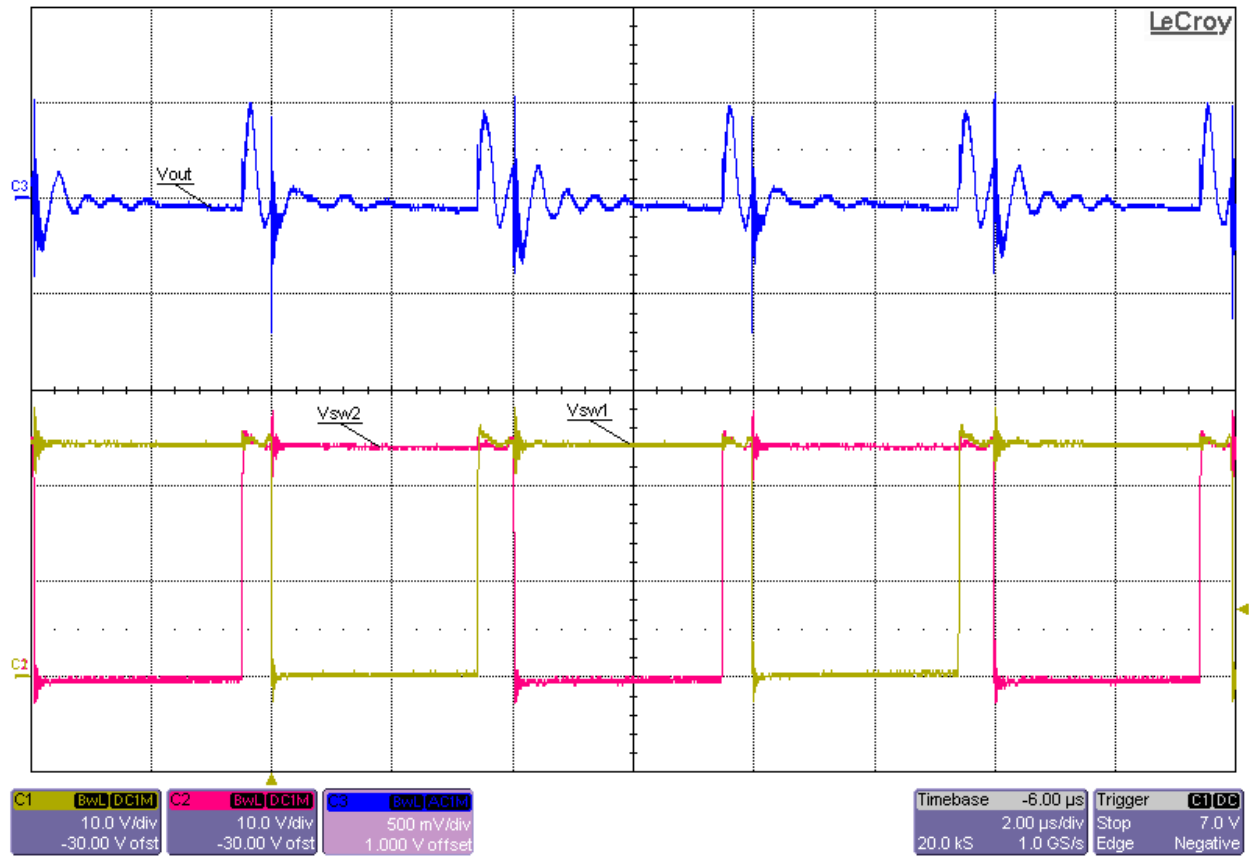Switch Node Voltage and Output Voltage Ripple at 14Vin and No Load ( $V_{ripple} \approx 130mV_{p-p}$ )



Switch Node Voltage and Output Voltage Ripple at 14Vin and Full (8A) Load (Vripple  $\approx$  700mVp-p)

## 7 Loop Frequency Response

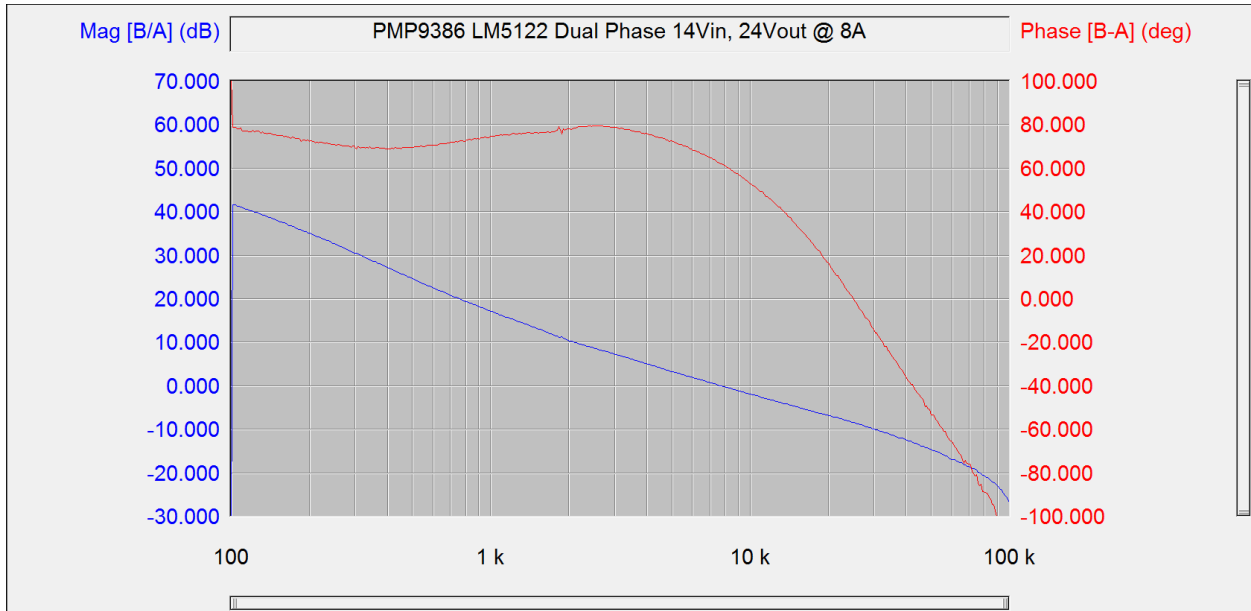

Loop Frequency Response at 14Vin and Full (8A) Load

(Phase Margin  $\approx$  65 degrees; Gain Margin  $\approx$  -8 dB; Cutoff Frequency  $\approx$  8KHz)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated