

Designing Daytime Running Lights, Part 2: Responding to an LED Fault



Chris Suchoski

This is the second installment in a two-part series on designing bright daytime running lights (DRLs) without the need for two LED drivers, a method provided in the [Automotive Daytime Running Light Dual String LED Driver Reference Design with Current Balancing](#).

In the first installment of this series, “Designing daytime running lights, part 1: adding one-fail-all-fail LED fault detection,” I outlined two ways to achieve the desired brightness in LED headlights, provided an overview of the reference design and explained how to detect a fault.

Once a fault is detected, the reference design needs a way to identify when V_{Drain} is greater or lesser than the voltage, given by Equation 1:

$$V_{Drain} = I_{Mirror} * (MOSFET\ r_{dson} + R_0) = V_f + I_{MIRROR} * R_0 \quad (1)$$

You can accomplish this by implementing a window comparator circuit made up of open-drain or open-collector comparators, as shown in [Figure 1](#).

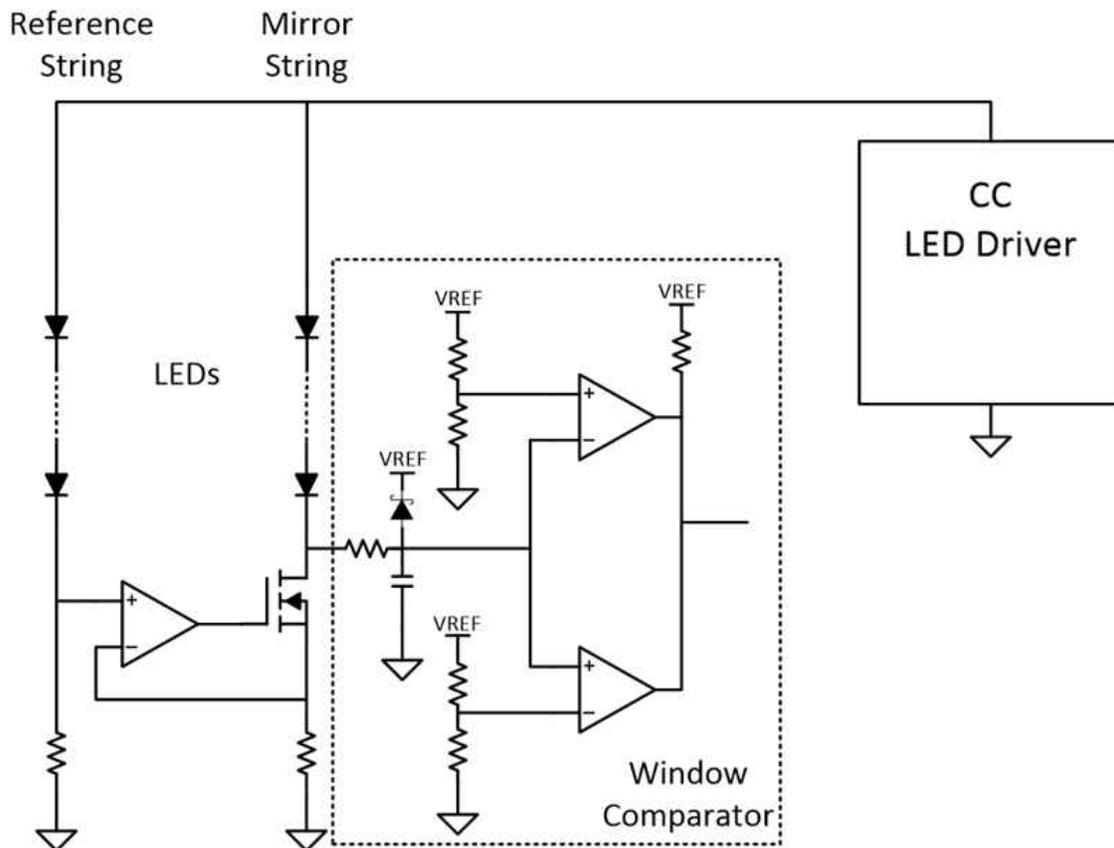


Figure 1. Window Comparator

The resistor dividers on the reference inputs of the top and bottom comparators set the upper and lower limits of the “window,” respectively. When V_{Drain} is between these upper and lower limits, the output of the window comparator is high (V_{REF}). When outside of the limits of the window voltage, the output pulls low to ground. In the reference design, the upper and lower thresholds of the window are $\sim 110\%$ and $\sim 90\%$ of the voltage given by Equation 1, respectively.

The window comparator can detect all of the LED faults mentioned in the first part of this series. However, in the case of an open circuit in the reference string fault, oscillations of V_{Drain} will cause the window comparator to trip repeatedly. Because of this reason, you must latch the window comparator output to ensure that its output remains low the first time V_{Drain} is outside of the window voltage thresholds.

In DRL modules that use microcontrollers, you can use software in the microcontrollers to latch the fault. In DRL modules without microcontrollers, you can use the circuit shown in Figure 2 to latch the window comparator output and disable the LED driver when a fault occurs. The latch circuit in Figure 2 uses a Schmitt trigger and a D flip-flop.

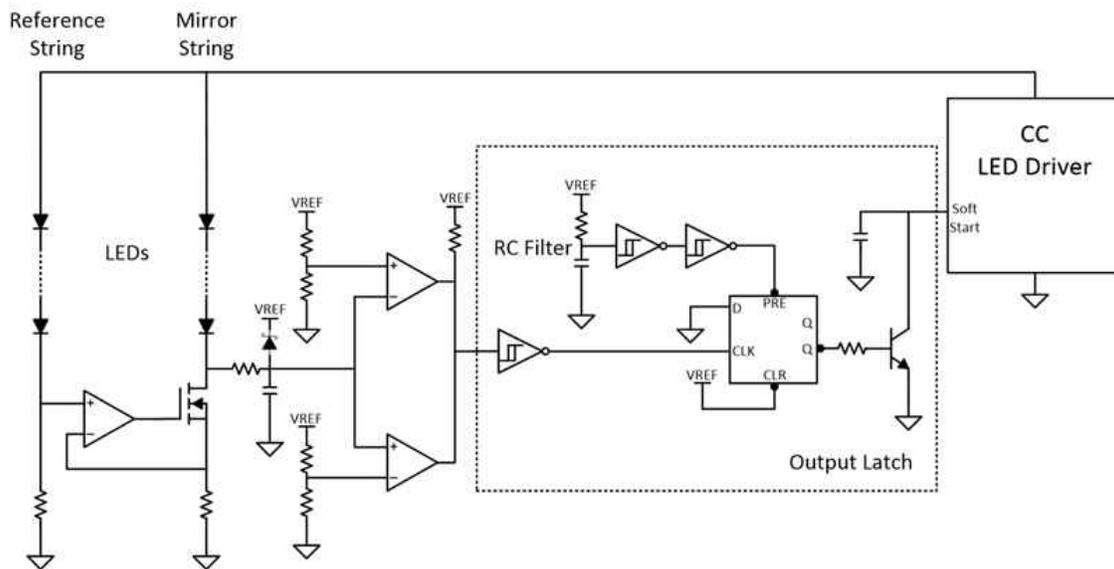


Figure 2. Output Latch

When a fault occurs, the output of the window comparator will transition from high to low. The D flip-flop transfers data from its input D to its outputs Q and \bar{Q} at each rising edge of its CLK input. For this reason, an inverting Schmitt trigger is used to translate a falling edge at the output of the window comparator into the rising edge required by the D flip-flop.

The design uses a D flip-flop with preset and clear pins that enable confirmation of the initial device conditions at startup. The truth table shown in Figure 3 shows that when \bar{Q} is low and Q is high, Q and \bar{Q} are high and low, respectively. With \bar{Q} low, the N-channel P-channel N-channel (NPN) transistor connected to the soft-start pin on the LED driver does not conduct, thus allowing the LED driver to operate as intended at startup.

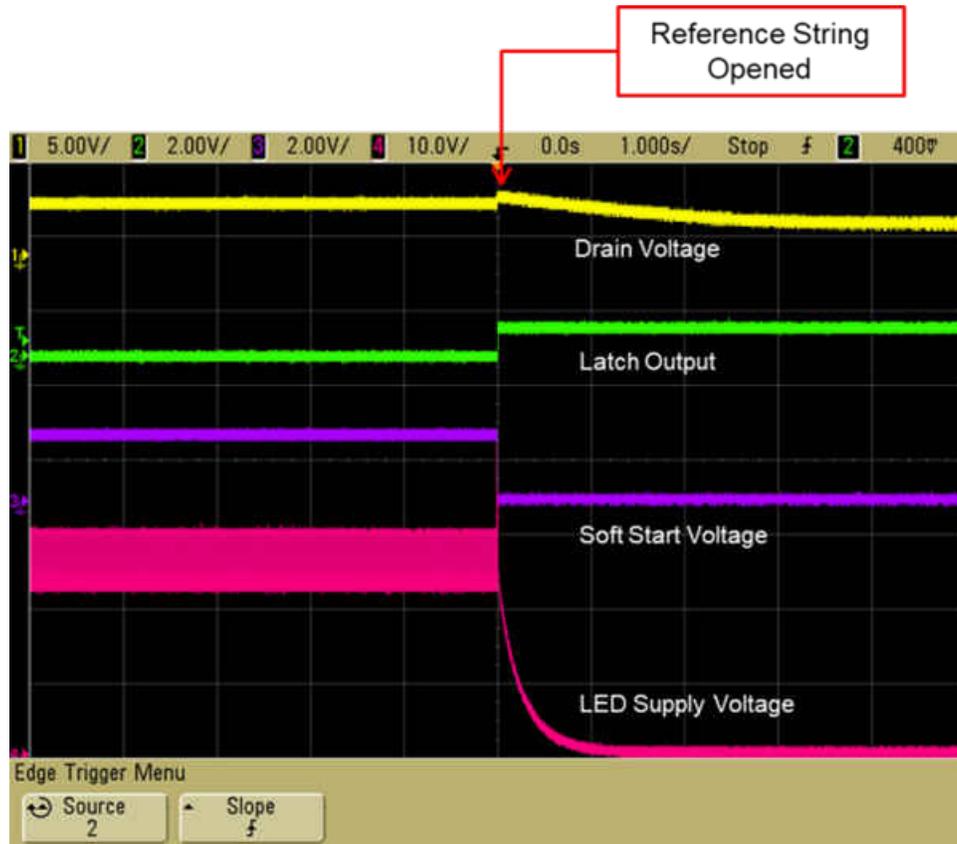


Figure 3. D Flip-flop with Preset and Clear

The resistor-capacitor filter and two series-inverting Schmitt triggers cause the pin to be low at startup. After VCC charges the capacitor to the threshold of the first inverting Schmitt trigger, will transition high and the device will operate as expected.

With low at startup and D tied directly to ground, if a fault occurs you will see a rising edge at the CLK input and will transition from low to high. This causes the NPN transistor to conduct and pull the soft-start pin on the LED driver to ground. As shown in the [TPS92692-Q1](#) data sheet, if the soft-start pin pulls to ground, the driver will stop switching and stop the LED current flow.

Lab Results

I tested this in the lab with hardware from the reference design. [Figure 4](#) shows the result of an open circuit in the reference string.

FUNCTION TABLE (EACH FLIP-FLOP)

INPUTS				OUTPUT	
$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	CLK	D	Q	$\overline{\text{Q}}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H ⁽¹⁾	H ⁽¹⁾
H	H	↑	H	H	L
H	H	↑	L	L	H
H	H	L	X	Q ₀	$\overline{\text{Q}}_0$

- (1) This configuration is non-stable; that is, it does not persist when PRE or CLR returns to its inactive (high) level.

Figure 4. An Open Circuit in the Reference String

You can see a spike in the drain voltage when the reference string opens. This causes the output of the latch to transition high, which in turn pulls the soft-start pin on the LED driver to ground and shuts off current flow to the LEDs. There are no oscillations at the drain because the LED driver shuts off immediately.

Conclusion

LEDs are an energy efficient choice for daytime running lights, and with the reference design for parallel strings, you can achieve optimal brightness without the need of a second LED driver.

Additional Resources

- Review the [Window Comparator Reference Design](#).
- Read the white paper, "[Evolution vs. revolution: the building blocks of automotive body electronics.](#)"

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated