

# Color the World with What's Next in RGBW LED Light Source Technology – Part 1



Seetharaman Devendran

Red, green, blue and white (RGBW) light emitting diode (LED)-based color-tunable luminaires are very common in applications such as stage lighting, entertainment lighting and architectural lighting; [Figure 1](#) shows a couple of examples. In this blog post, we will discuss the key challenges associated with designing such LED light sources and how to resolve them.



**Figure 1. Stage and Architectural Lighting**

In stage-lighting applications, which require the generation of different colors as well as dimming, individual LED strings are generally duty-cycled using a pulse-width modulator (PWM). Although the human eye cannot detect PWM frequencies of more than 200Hz, both video and still cameras can see LED on/off cycles due to the PWM. Capturing video with a complementary metal-oxide semiconductor (CMOS) sensor-based video camera and filming with the “rolling shutter” method, the video will show a dark band moving up or down in the presence of an LED light source with a lower-frequency PWM. A CMOS sensor-based still camera can cause an underexposed band to develop on the image. Such effects are not acceptable; thus, a luminaire design has to include methods that avoid this issue, while also producing excellent color mixing and an immersive user experience.


## **Analog vs. PWM Methods for Generating Colors and Dimming**

To generate a wide range of colors, a common method is to use four LED strings for red, green, blue and white. By changing the current through the LED strings, you can generate the complete color spectrum. The easiest way to change the current is to use a programmable linear current source for each LED string. Unfortunately, this will cause huge power losses and increased thermal-management issues.

Another method is to power up each string using a PWM buck regulator or buck controller and adjust the analog current reference of that device using a programmable digital-to-analog converter (DAC). The advantage of this method is that the buck devices can operate at very high frequencies; the CMOS sensors in still and video cameras will not notice the modulation of the LED lighting. Devices such as the TPS9264, TPS92515 or LM3409 can enable high resolution analog current control for high-current LED strings. However, a drawback with this

method of changing the current through the LED is that the LED string's color temperature will not remain the same over the dimming range.


A third method is to power up each string using a PWM buck regulator or buck controller operating at a few hundreds of kilohertz, set the peak current through the LED string to its recommended operating value, and use a PWM to enable and disable the converter, thereby having the PWM modulate the current through the LED. Using this method, you can control dimming and color generation without much loss, and without changing the LED string's color temperature. Devices such as the LM3404, LM3414, TPS92515, TPS92640 and LM3409 have a built-in PWM modulation pin that enables the modulation of LED current at frequencies well above 10kHz. Figure 2 shows the analog and PWM current control methods for LEDs.

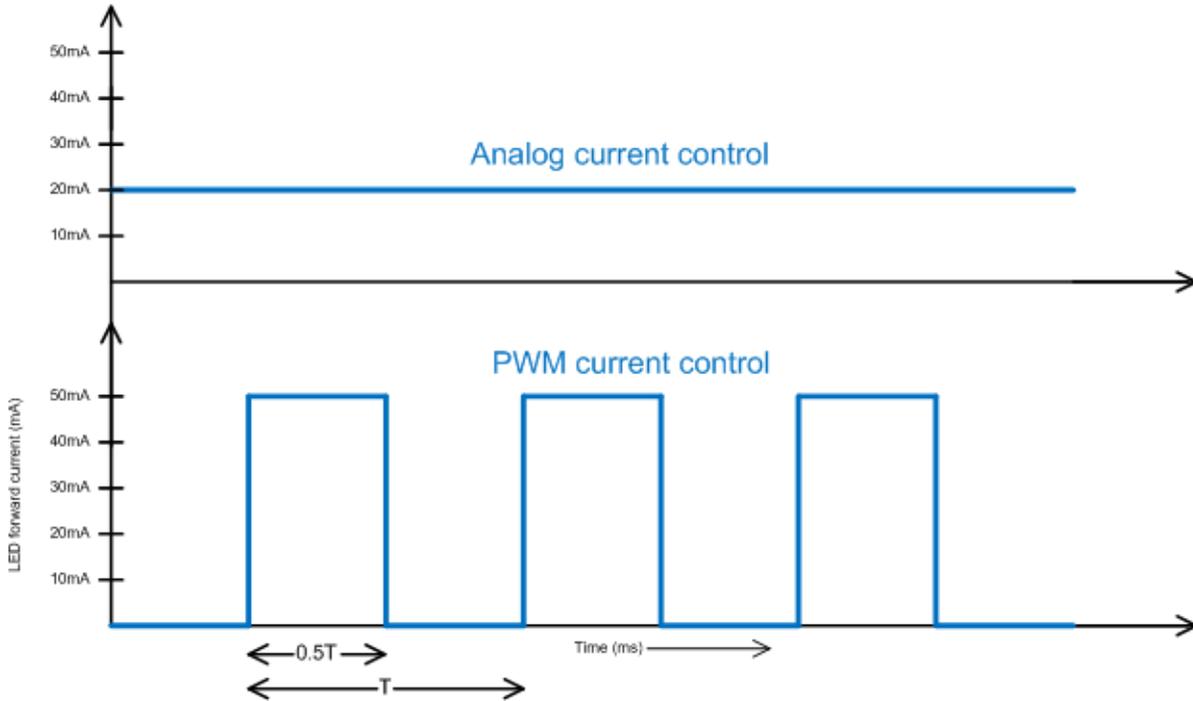

**Figure 2. Analog and PWM Current Control**


### A Shunt FET Dimming Method

Because of delays in the shutdown and startup of a buck converter's output, there is a limit to the PWM dimming frequency and range of duty cycles. To help overcome this delay, you can place an external shunt device such as the FET shown in Figure 3 in parallel with the LED or LED string to quickly bypass the converter's output current around the LED(s). The current in the inductor remains continuous during the LED shutdown time, avoiding the long delay in ramping the inductor current pedestal up and down. The delay time now shifts to the limits of the shunt device's rise and fall times.

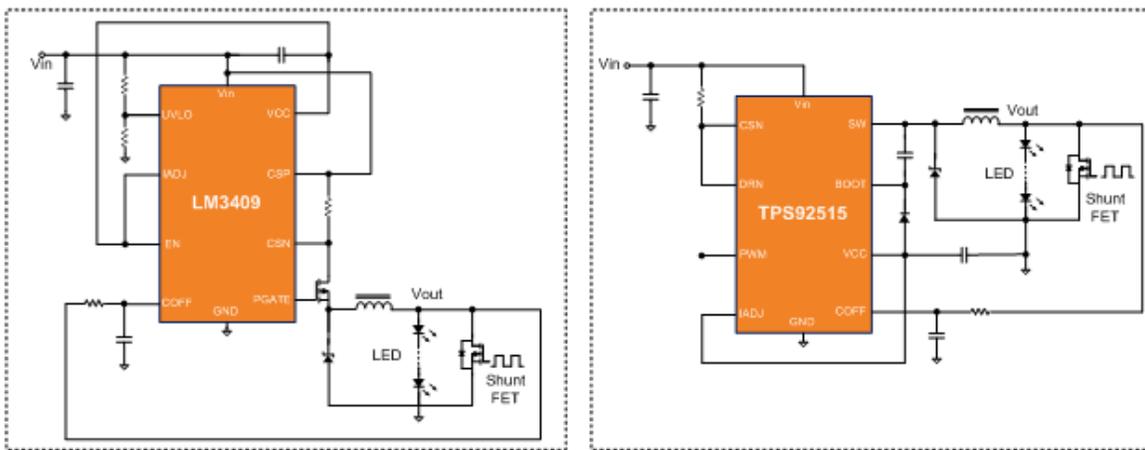

**Figure 3. Shunt FET Dimming**

Figure 4 shows the plots comparing the LED on/off delays when using the PWM dimming function pin vs. the shunt FET. Take precautions when shunting the LED current with current-mode converters because of the overshoot in output current when the FET turns on. The LM340x family of LED drivers are quasi-hysteretic and will not exhibit this overshoot. Keep the output capacitance across the LEDs low in order to maximize the on/off/on transition speed.

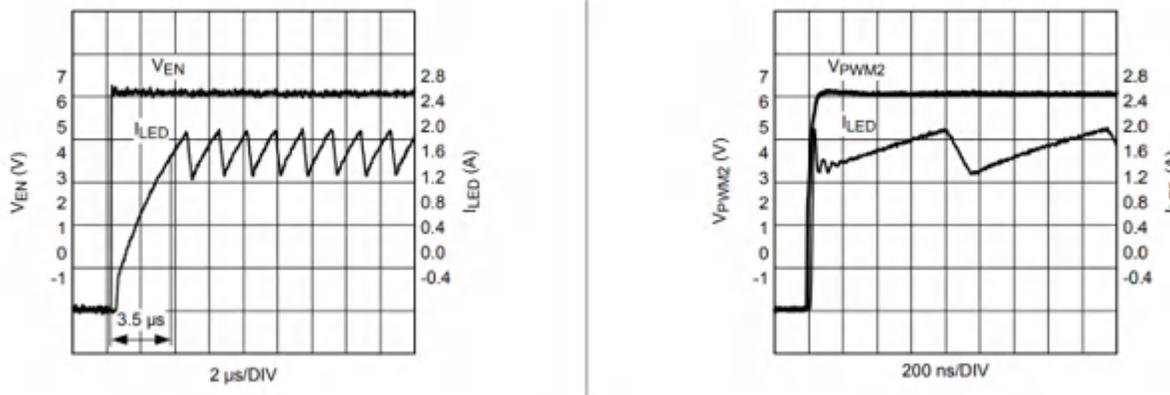

**Figure 4. Comparison of PWM Dimming and Shunt FET Dimming**

A disadvantage to the fast shunt FET dimming circuit vs PWM dimming method is a loss of efficiency. While the shunt device is on, a power dissipation of  $V_{\text{Shunt device}} \times I_{\text{LED}}$  is lost as heat. Using low  $R_{\text{DS(on)}}$  field-effect transistors (FETs) will minimize this efficiency loss. Overall, shunt-FET dimming allows very high frequency PWM dimming without compromising much on the dimming linearity and contrast ratio compared to standard PWM dimming for modulation frequencies above 25KHz.

In the second installment of this two-part series, we will discuss the need for high PWM frequency as well as high resolution in stage-lighting applications, along with a design in the TI Designs reference design library that helps solve system-level challenges.

**Additional Resources:**

- Click here to find more [lighting design resources](#)
- Check out this [100-W, High - Resolution, 16-bit Color - Tunable, 0.15% Dimmable RGBW LED Luminaire Reference Design](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated