

Liberate Your Solenoid or Relay from the Bonds of Supply Voltage



James Lockridge

One of the things I love about my job as an applications engineer is pretending that I'm a TI customer. I spend my days dreaming of all the possible ways customers use solenoids, design solenoids and drive solenoids. Today, I'm considering what concerns TI customers might have regarding voltage supply and solenoid or relay selection.

One customer I can imagine is a valve designer – maybe pneumatics in factory automation or media valves for process automation. Most factory- and process-automation equipment is designed for 24V supplies. However, customers may have control signals for a wide range of AC or DC voltages – 12 V, 24 V, 36 V, 48V, or even 120 or 240 V for some valves and contactors. To accommodate all of these voltages, I would need to design five different coils and have five separate products.

One solution could be to design one coil for 12V, then use a resistor to limit the current into the [solenoid](#) for each voltage option. However, this wastes energy and could dissipate a lot of heat from the resistor, especially if the 12-V coil is used for the 220V design.

Another, more energy-efficient solution is to use pulse-width modulation (PWM) driving and a freewheeling diode to regulate the current in the solenoid. Additionally, you could add current-sense feedback with PWM and control the current in the solenoid. The magnetic force produced by the solenoid to open or close a valve depends on the current flowing through the solenoid coil. The solenoid resistance increases with temperature. With an applied voltage, the increase in resistance will reduce the current in the solenoid, which reduces the magnetic force. At high temperatures, it is possible for the solenoid to de-actuate or for a relay to open its contacts if the current decreases too much. With current control, the solenoid current is always regulated to the required value independent of temperature, which makes the system more reliable and robust over temperature. You could implement current-sense feedback with a microcontroller and discrete signal-chain components, or with an integrated solenoid driver like the [DRV110](#) ([Figure 2](#)) and [DRV120](#) ([Figure 1](#)).

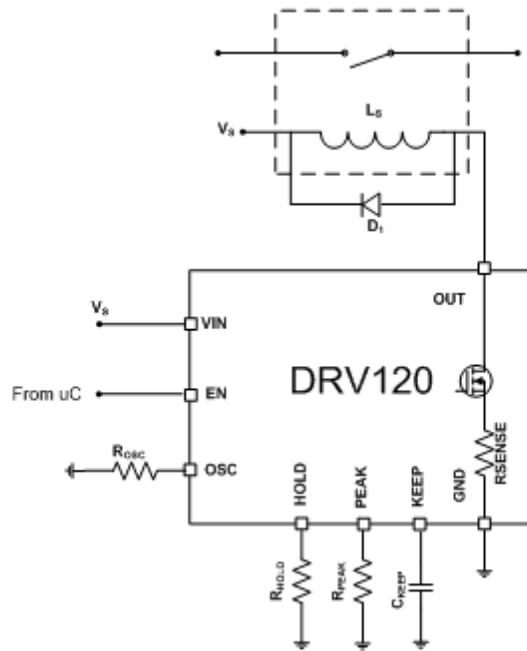


Figure 1. The DRV120 Driving a Relay Using Current Control

Figure 2 shows how you can configure the DRV110 solenoid to accommodate AC voltages that energize solenoid valves or contactors. By using DC to drive the contactor instead of AC, you can simplify the design of the magnetics by eliminating the need for a shaded ring in the core.

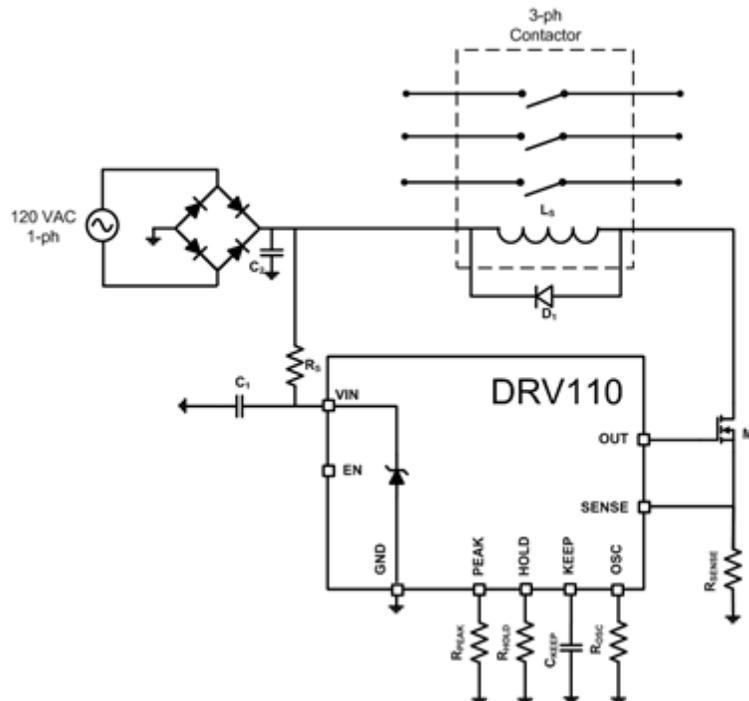


Figure 2. DRV110 Used to Drive the Coil for an AC Contactor

With this current-control technique, you can potentially design only one 12-V coil for the force requirements of the AC or DC 12-V to 48-V valves and the AC 120-V to 220V valves. This allows you to have multiple product offerings for valves while only needing to design one coil.

Another customer situation I can imagine is wanting to use a particular relay in a design, but the only supply rail available is too high. Let's say that the relay is rated for 12 V, but the supply rail is 24V. One solution may be to just switch to a 24V relay for the system. While it sounds easy, perhaps that involves adding the new part number as an approved component. Maybe you can't do this because it is a difficult or lengthy process, and you want to take your product to market quickly. You might also run into the same situation with a solenoid. Perhaps you really like the force of a particular solenoid, but it's rated for 12 V when you have a 24-V rail.

Using current control can also solve this dilemma. You can use your 12V relay or solenoid for both 12-V and 24-V systems. Maybe the next-generation product will only have a 36-V supply rail. Even in that case, current control will allow you to continue using your chosen solenoid or relay. Perhaps by using the same solenoid in all three systems, you can get a volume discount from the solenoid/relay manufacturer for purchasing large volumes of that particular part number.

With current feedback, I solved my imaginary customers' issues for voltage supply rail and solenoid/relay design or part-number selection. Is my imagination accurate to your design experience? Please share your experience in the comments or share any other great solenoid- or relay-driving solutions.

Additional Resources

- Explore a 230V_{AC} [solenoid reference design](#) that illustrates how to integrate current control.
- Check out another reference design that provides a solution to control [solenoid current](#) using a PWM-based controller.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated