

Motor Drive Forum Top FAQs Part 2: How to Estimate Motor Regeneration and VM Pumping



Wilson Zuo

Motor regeneration is a common problem that occurs in motor-drive systems. Many designers have to select a motor supply voltage (VM) rating of twice the nominal level, which adds to the system cost. Fortunately, if you can first understand the pumping details, you can understand the necessary VM margin. In the first post in this series on frequently asked questions, [Nicholas Oborny](#) provided advice on how to read a motor driver datasheet. Today, I'll continue the conversation by introducing a method for estimating the pumping level.

VM Pumping Waveform

Figure 1 shows a typical VM pumping waveform caused by regeneration during a deceleration process. When the input PWM (pulse-width modulation) duty changed from 99% to 70%, the VM voltage was pumping from 24V to 32V. (Tested on TI motor driver device [DRV8840](#), a 5A Brushed DC Motor Driver.)

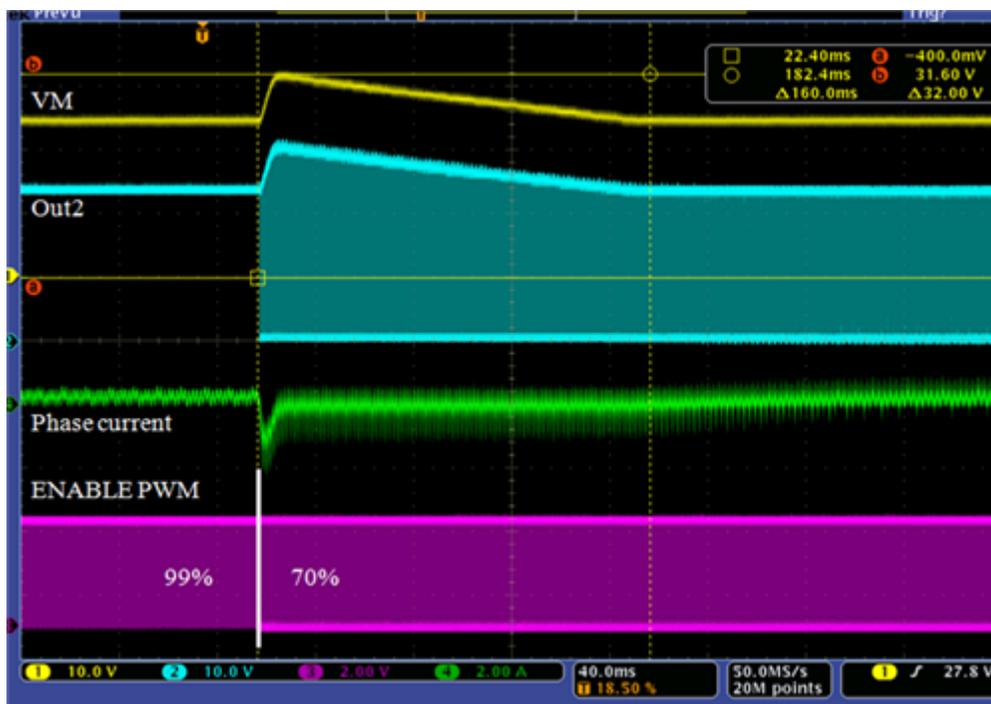


Figure 1. Regeneration and VM Pumping

Pumping Mechanism

We need some DC/DC power management background here to understand the pumping mechanism. So, let's look at how a typical buck-boost circuit works; see [Figure 2](#). What's interesting is that during PWM, driving a motor with an H bridge, you have the buck and boost process together. As shown in [Figure 3](#), during the PWM's driving time, it's a typical buck circuit. In [Figure 4](#), the back electromotive force (EMF) is acting as the boost source during the PWM's off time.

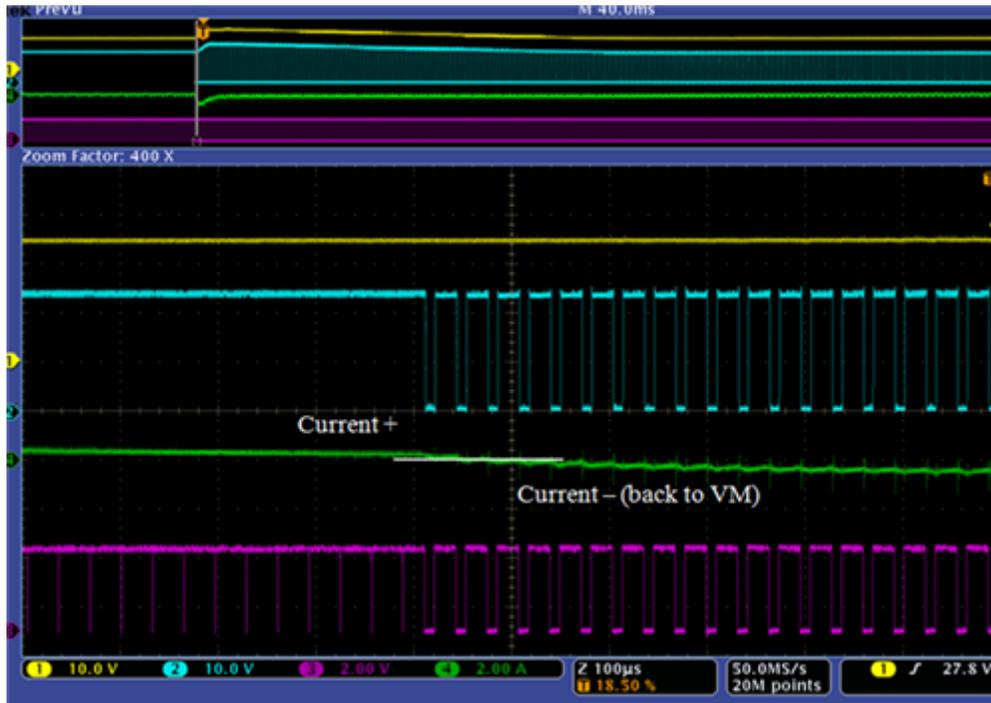


Figure 2. Buck and Boost Circuits

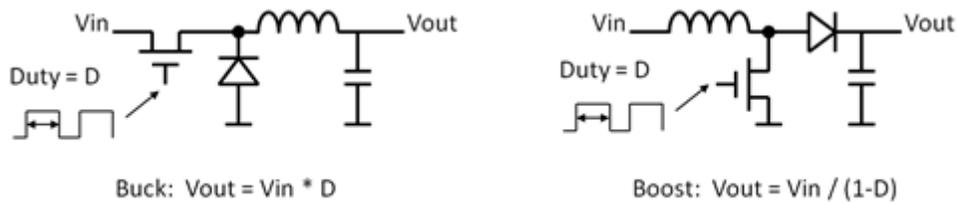


Figure 3. Buck Topology

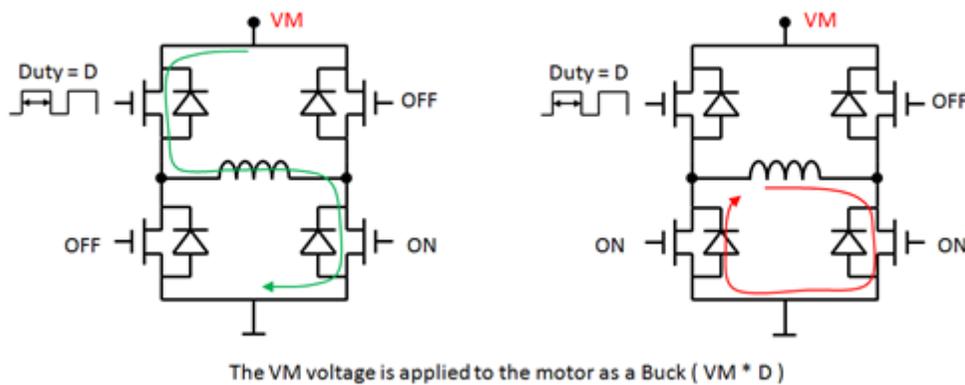


Figure 4. Boost Topology

The running model of the brushed DC motor can be shown as equation [Equation 1](#).

$$V_{VM} = R * i + L * \frac{di}{dt} + V_{BEMF} \quad (1)$$

(1)

In normal driving conditions with a PWM duty cycle = D, the motor will run at a speed driven by a voltage V_{DRV} as shown in equation [Equation 2](#).

$$V_{DRV} = V_{VM} * D \quad (2)$$

Based on [Equation 1](#), we should have

$$V_{BEMF} < V_{DRV} \quad (3)$$

The boost effect will give the V_{BST} as

$$V_{BST} = \frac{V_{BEMF}}{D} \quad (4)$$

From [Equation 2](#), [Equation 3](#), [Equation 4](#), we can get

$$V_{BST} < V_{VM} \quad (5)$$

So, there is no VM pumping in a normal running condition.

When the PWM duty cycle is reduced from D1 to D2, just before the reducing point, we have

$$V_{BEMF1} = K * V_{VM} * D1 \quad (0 < K < 1) \quad (6)$$

Just after the reducing of duty, the speed of the motor can't change suddenly, so the V_{BST} is based on the new duty cycle D2 as

$$V_{BST} = \frac{V_{BEMF1}}{D2} \quad (7)$$

From [Equation 6](#), [Equation 7](#), we can get

$$V_{BST} = \frac{V_{VM} * K * D1}{D2} \quad (8)$$

When $K * D1 / D2 > 1$, we get


$$V_{BST} > V_{VM} \quad (9)$$

V_{BST} will be higher than V_{VM} and causing a pumping effect. Assuming that K is close to 1, any time you reduce the duty cycle with $D2 < D1$, VM pumping will occur. For example, if you go from 100% to 50%, $V_{BST} = 2 * V_{VM}$. And if you go from 90% to 30%, there will be 3x higher pumping voltage seen from VM.

Pumping Tests

In practice, VM pumping may not be seen as high as estimated by the above [Equation 8](#), because the power supply and VM caps will have sinking ability which helps to reduce the pumping level. To verify the estimating

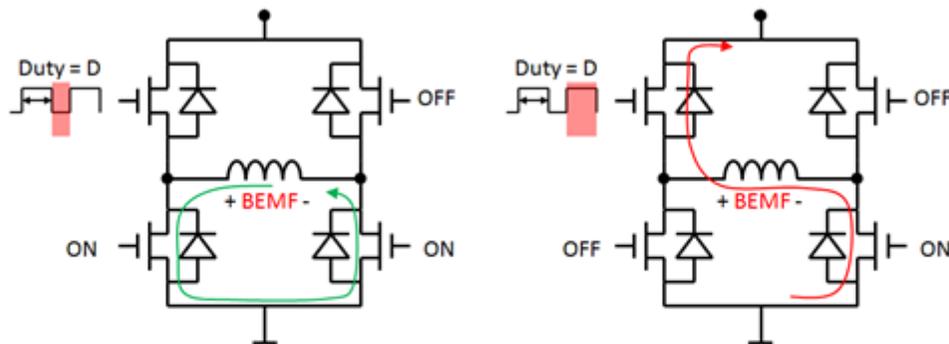method, we add a diode Ts1 from the power supply to the VM, as shown in Figure 5, trying to get the pure pumping effect without power supply sinking.



The BEMF voltage to VM is on a Boost topology
($V_{bst} = V_{BEMF} / D$; Note this "D" means 1-D in Fig 3)

Figure 5. Pumping Voltage Tests

Figure 6 and Figure 7 show the test results. (Note: Some pumping voltage is over the VM spec of the DRV8840 datasheet; this is for test only. The device is never recommended to be used in over-spec conditions.)

Duty Cycle Change D1 to D2	Tested VM pumping level (V)	Calculated MAX pumping VM 24V * D1/D2 (K=1) (V)
100% to 90%	26.6	26.7
100% to 80%	29.4	30
100% to 70%	34.2	34.3
100% to 50%	47.4 (See figure: 7)	48
100% to 40%	57.2	60
90% to 45%	46.2	48
90% to 30%	59.6 (Clamped by Ts1)	72
80% to 60%	30.6	32
80% to 40%	44.4	48

Figure 6. Tested Result and Calculated Result

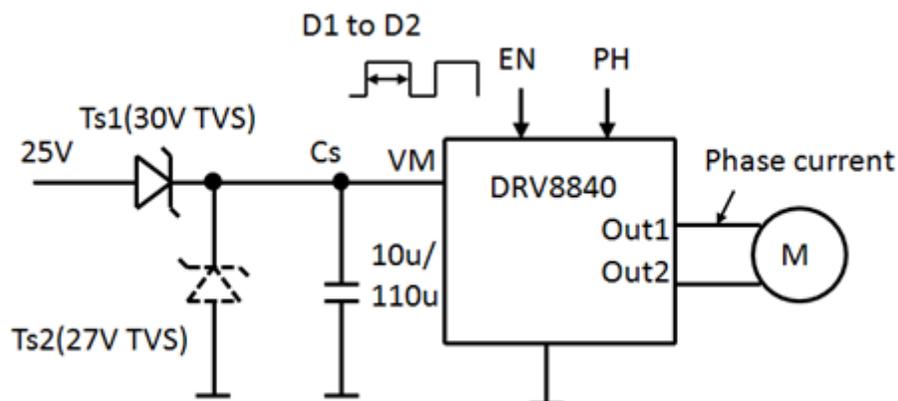


Figure 7. Bar Plot of Results

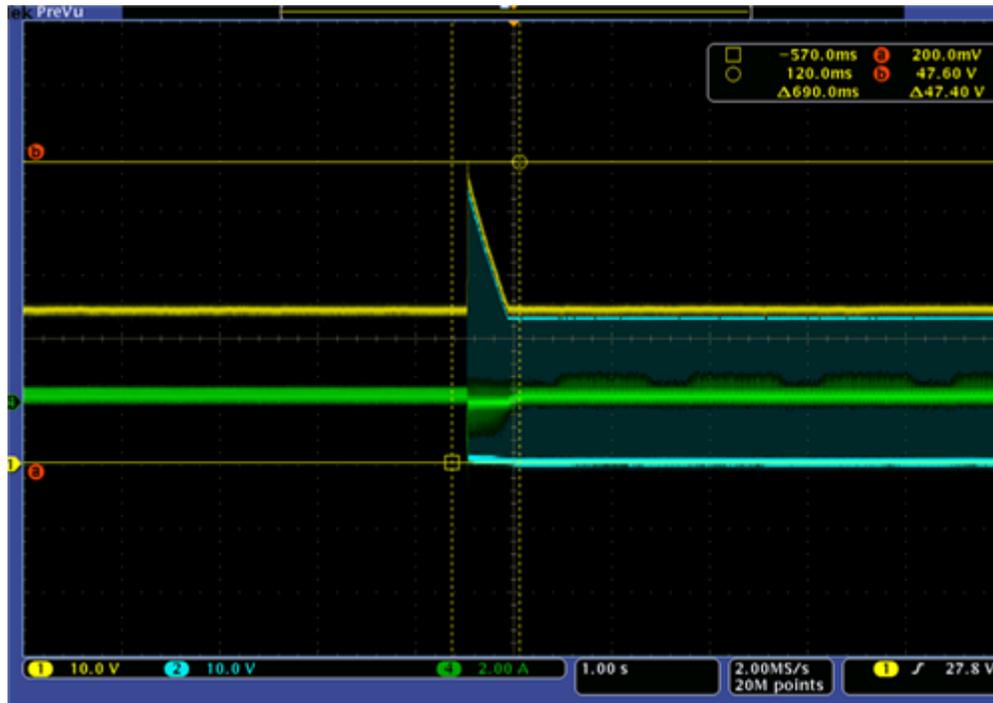


Figure 8. VM Pumping When PWM Reduces from 100% to 50% (with Ts1 on Figure 5)

Reducing Voltage Pumping

There are two ways to control VM pumping:

- Use fast decay. With DRV8840 in fast decay mode, the boost topology shown in Figure 4 is no longer present. The back EMF will always be less than the VM voltage, and VM pumping will not occur at all. It will take a longer time to achieve the targeted speed, as shown in Figure 9.

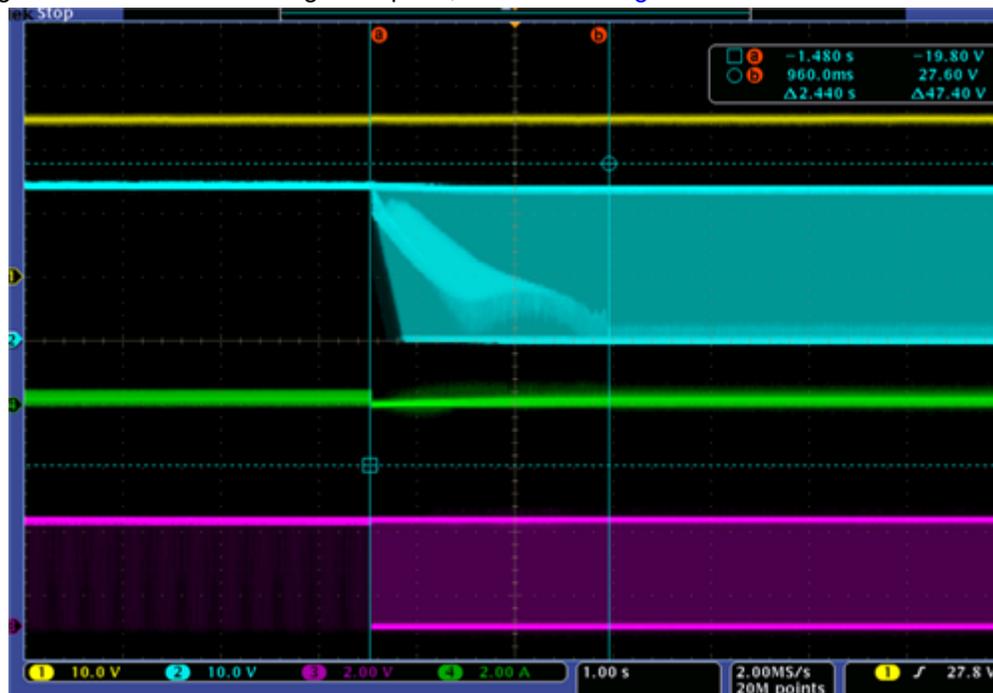


Figure 9. No VM Pumping with Fast Decay

- Use a transient voltage suppressor (TVS) to clamp the VM pumping. If you choose the TVS with clamping voltage a little higher than the nominal VM rating and place it as Ts2, shown in Figure 5, it will clamp the VM

pumping (see Figure 10). I used a 27V TVS and the VM pumping was effectively clamped at 29.6V. The TVS also functioned as dynamic braking so that the motor has a quick deceleration process.

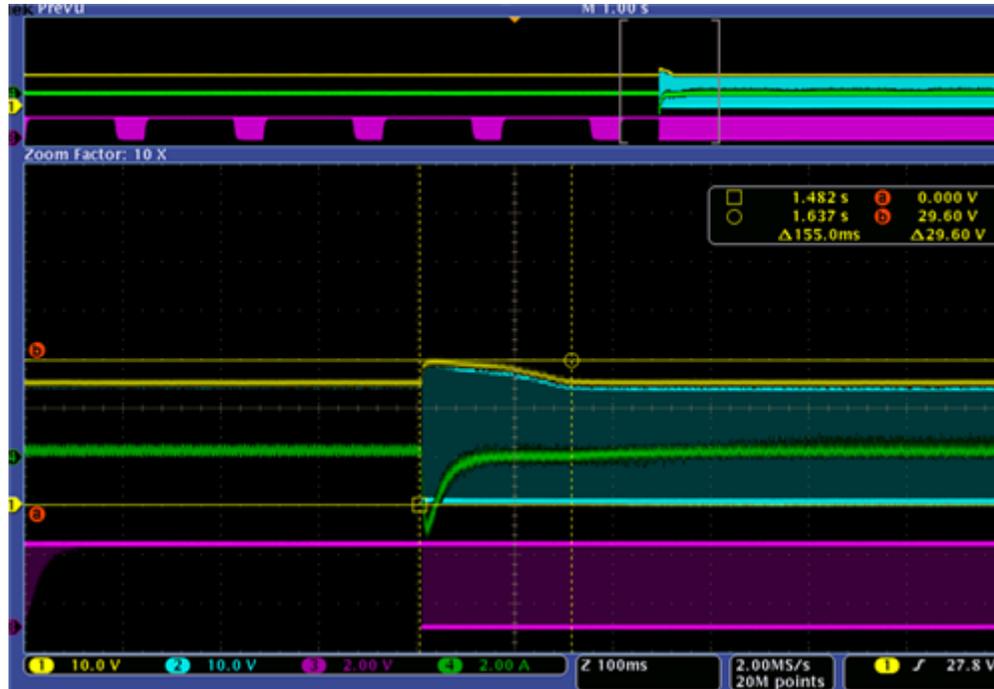


Figure 10. Figure 9

Summary

In a motor deceleration process, VM pumping actually shows the kinetic energy transferring into electrical energy. Consider the below factors:

- The boost topology is a key factor as to why the back EMF can force current back to the VM supply, even when $V_{BEMF} < V_{VM}$. Fast decay will not cause VM pumping during the deceleration section, but it will take a longer time for the motor to slow down.
- A TVS clamping method or other dynamic braking method can be a good way to reduce VM pumping while keeping the fast deceleration rate.

Additional Resources

- Read more blog posts in this series on [frequently asked questions from the forum](#).
- Download the [DRV8840 datasheet](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated