



# Test Report: PMP30308

## Isolated 6-W DCM Flyback Reference Design


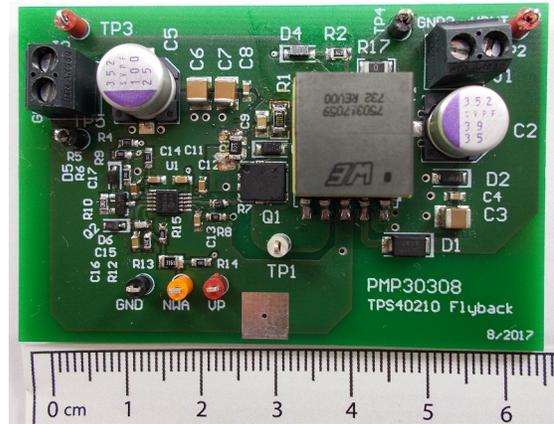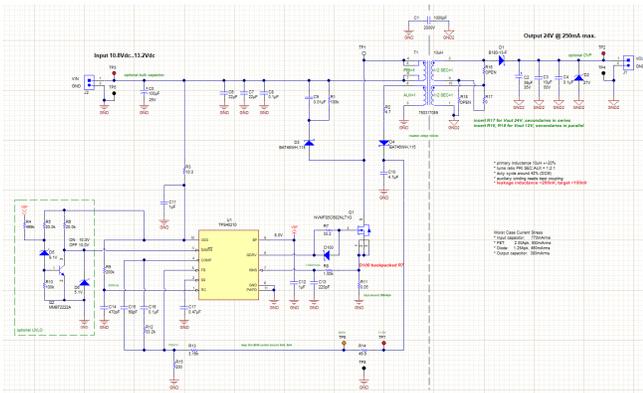
### Description

This reference design converts an input voltage of about 12V to an isolated output voltage of 24V @ 250mA<sub>max</sub>. Low cost due to TPS40210 controller primary side regulation. A typical application may be IGBT-Driver and interface isolation.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

## 1 Test Prerequisites

### 1.1 Voltage and Current Requirements

**Table 1. Voltage and Current Requirements**

PARAMETER	SPECIFICATIONS
$V_{IN}$	10.8V to 13.2V
$V_{OUT}$	12V @ 250mA <sub>max</sub>
Nominal switching frequency	200kHz

### 1.2 Considerations

Optional UVLO switches ON at 10.31V and OFF at about 10.03V input voltage.

Unless otherwise mentioned all measurements were done with 12V nominal input voltage and 0.25A full load output current (resistive load).

#### Primary side regulation

##### Pro

- The optocoupler is omitted. Therefore there are no issues with the aging problem of the optocoupler
- lower part count

##### Cons


- load regulation depends on the coupling of the transformer
- the transformer must have an auxiliary winding (possible workaround is dedicated IC for primary side regulation flyback like LM5180)

## 2 Testing and Results

### 2.1 Efficiency Graphs

Electronic load was used.

Figure 1. Efficiency and Loss vs Output Current

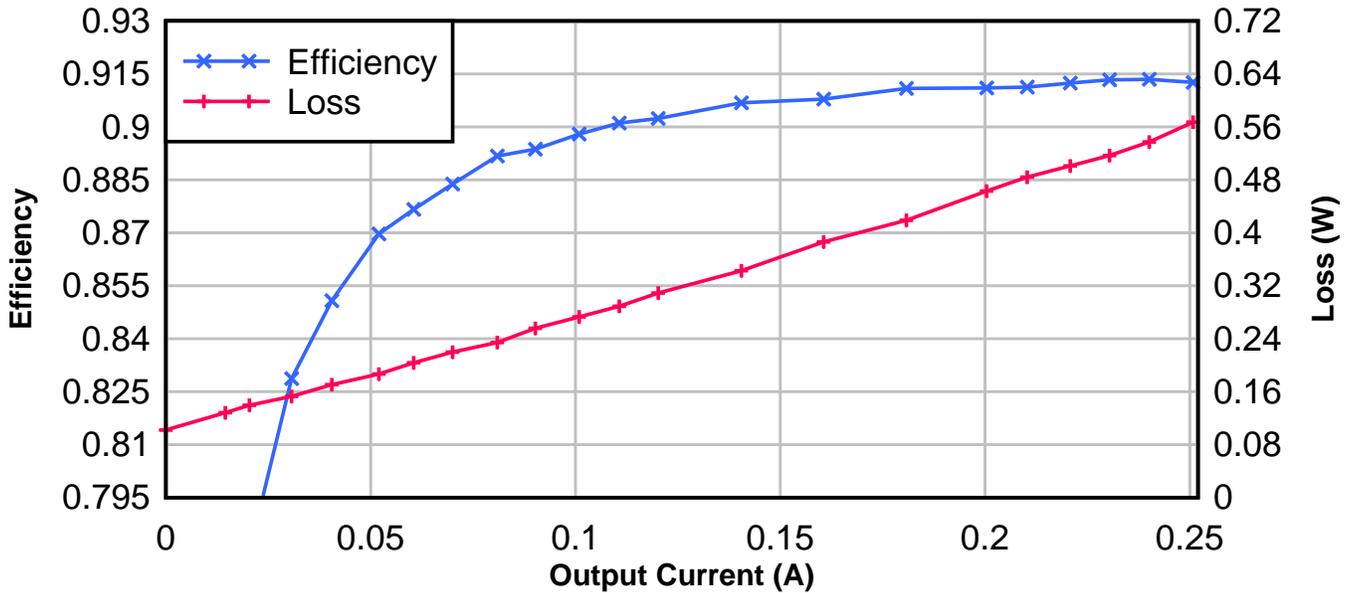


D001

### 2.2 Load Regulation

Electronic load was used.

Figure 2. Output Voltage vs Output Current

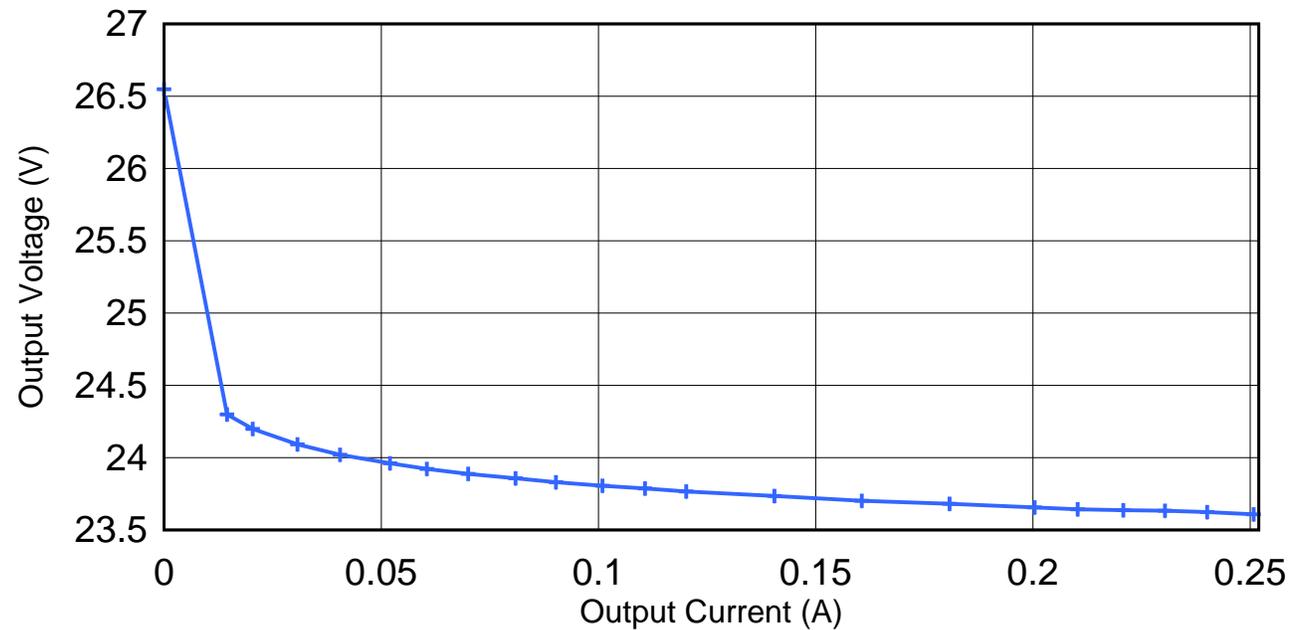


D002

Load regulation in between 10mA and 250mA load current is better than 3% !

### 2.3 Line Regulation


Figure 3. Output Voltage vs Input Voltage

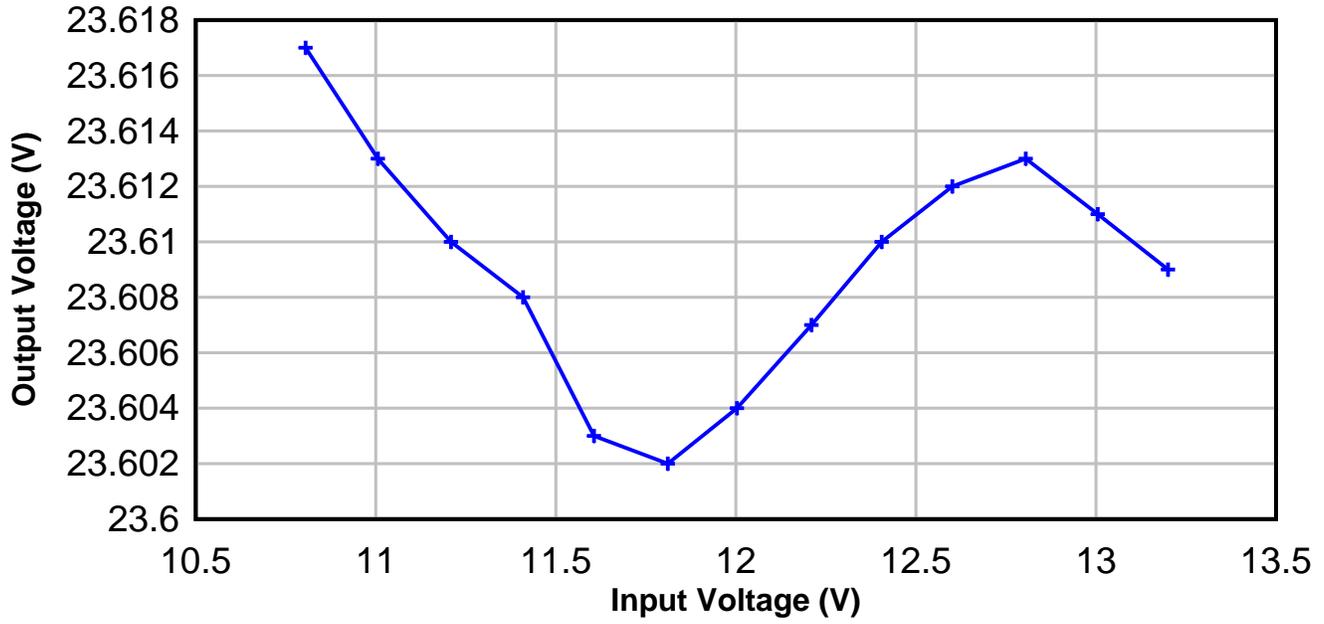

D003

## 2.4 Thermal Images

Figure 4. Thermal Image for 12V Input Voltage and 250mA Output Current

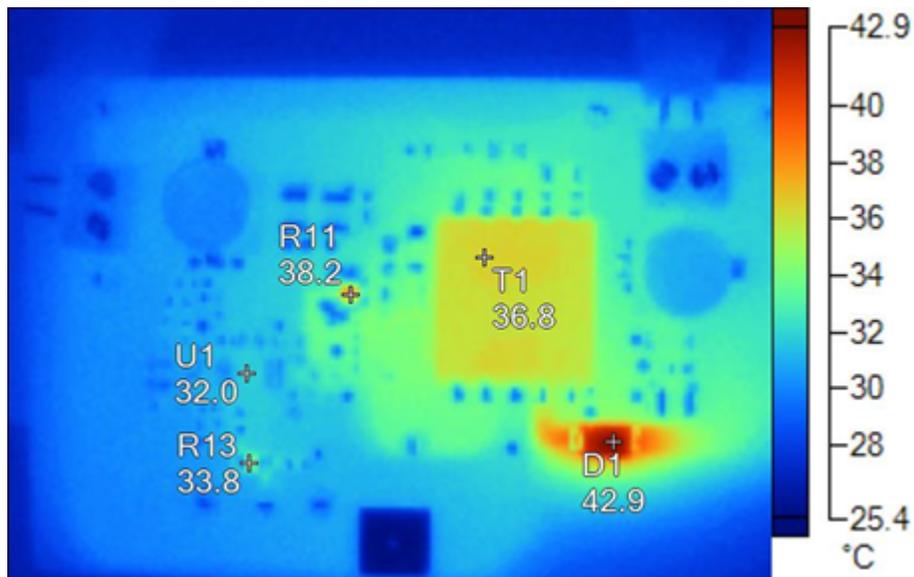

Name	Temperature
D1	42.9°C
R11	38.2°C
R13	33.8°C
T1	36.8°C
U1	32.0°C

The thermal stress at this 6W design is fairly low due to reasonable full load efficiency >91%.


### 3 Waveforms

#### 3.1 Switching


All waveforms in this chapter were done with full bandwidth setting.

##### 3.1.1 Transistor Q1

**Figure 5. Switchnode Voltage Q1 Drain to GND**

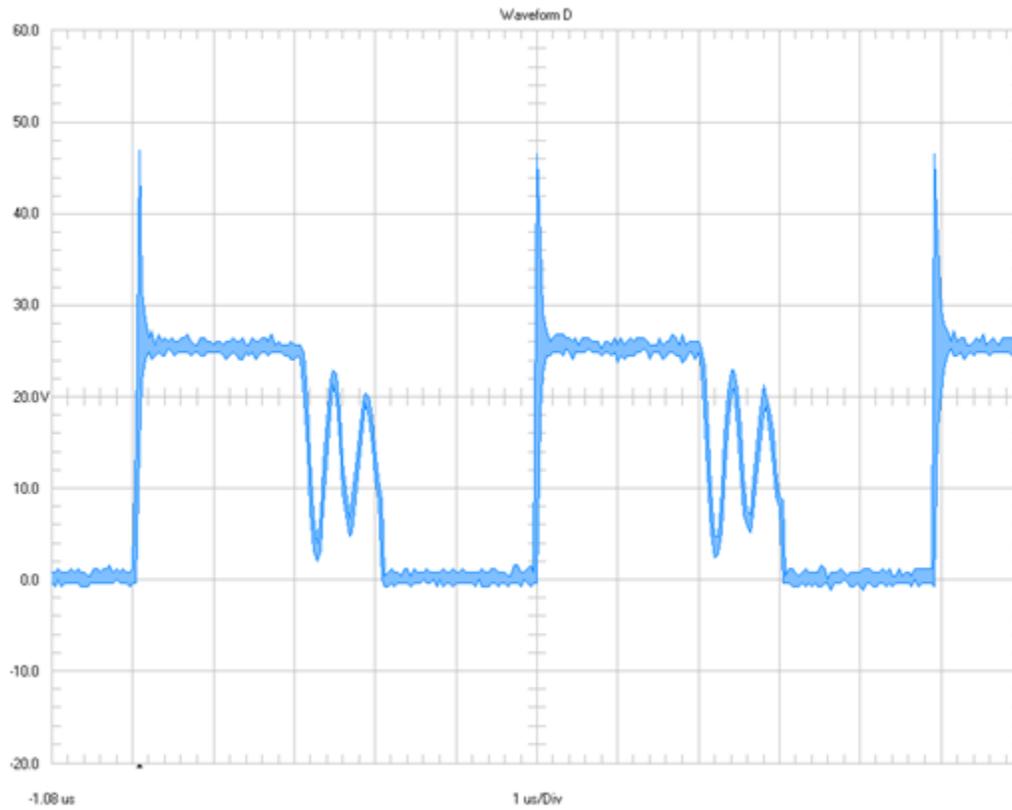


- 10V/div
- 1 $\mu$ s/div

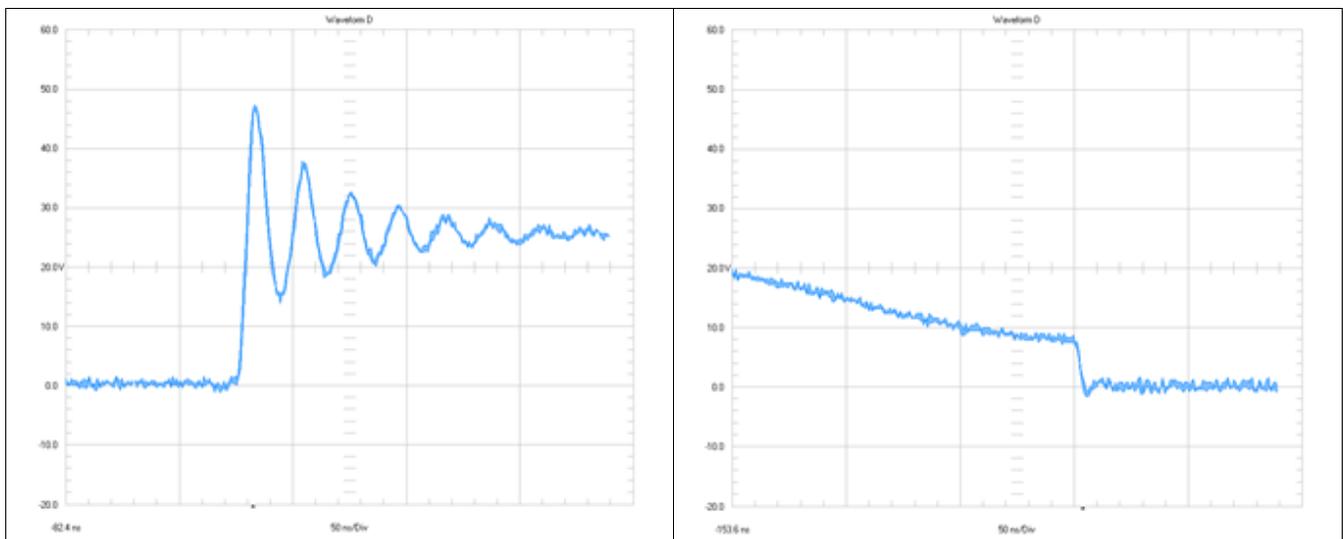


- 50ns/major div

### 3.1.2 Transistor Q1 Gate

**Figure 6. Q1 Gate to GND**

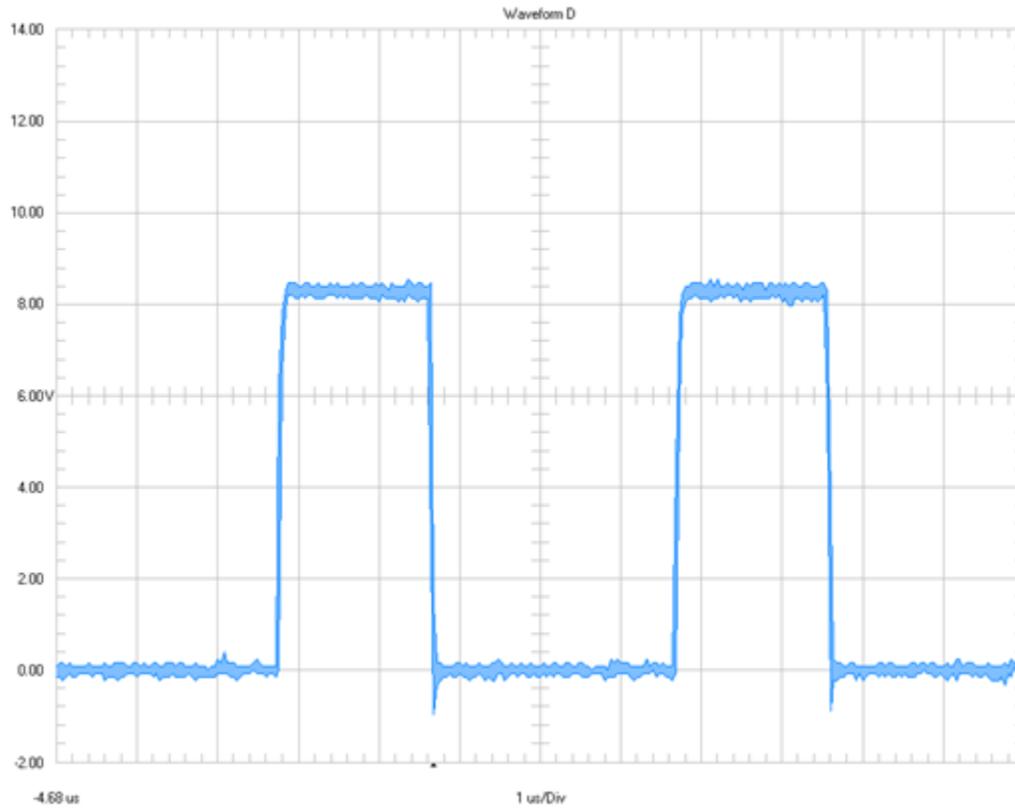


- 2V/div
- 1 μs/div

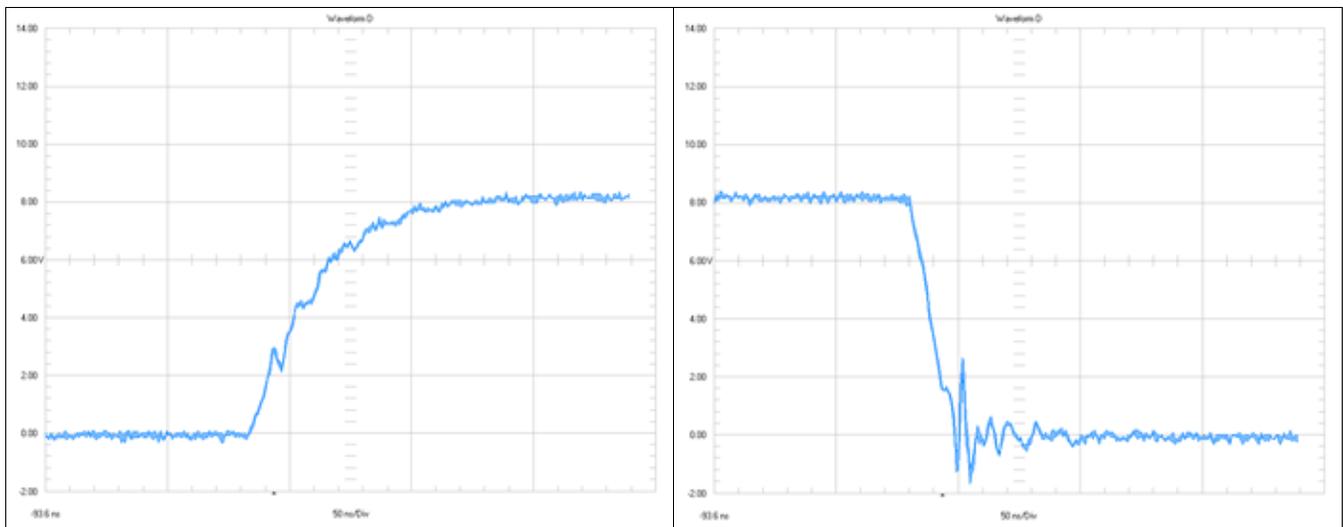


- 50ns/major div

3.1.3 Diode D1

Figure 7. Diode D1 referenced to VOUT

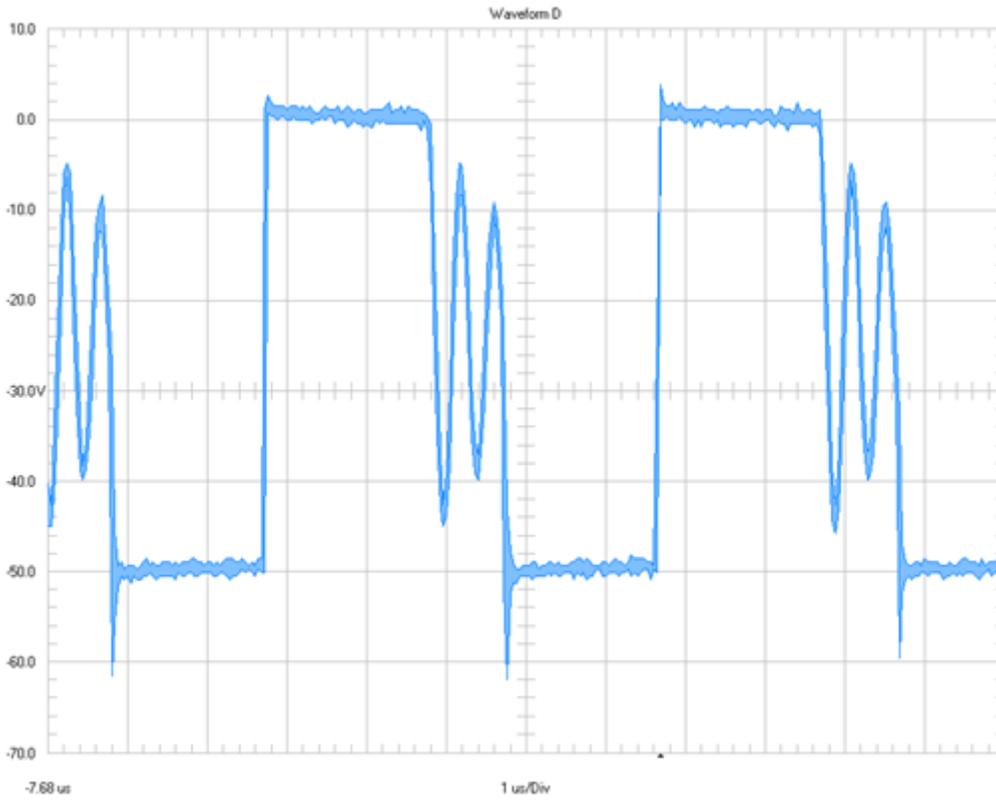


- 10V/div
- 1 $\mu$ s/div

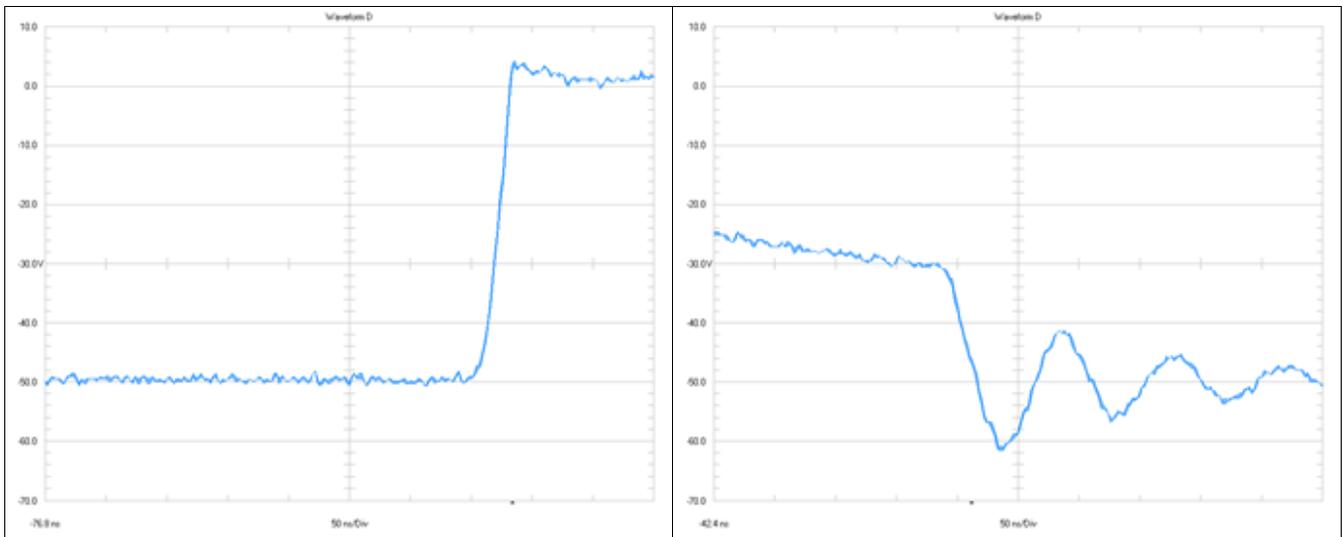

50ns/major div

### 3.2 Output Voltage Ripple

**Figure 8. Output Ripple Voltage (AC Coupled)**

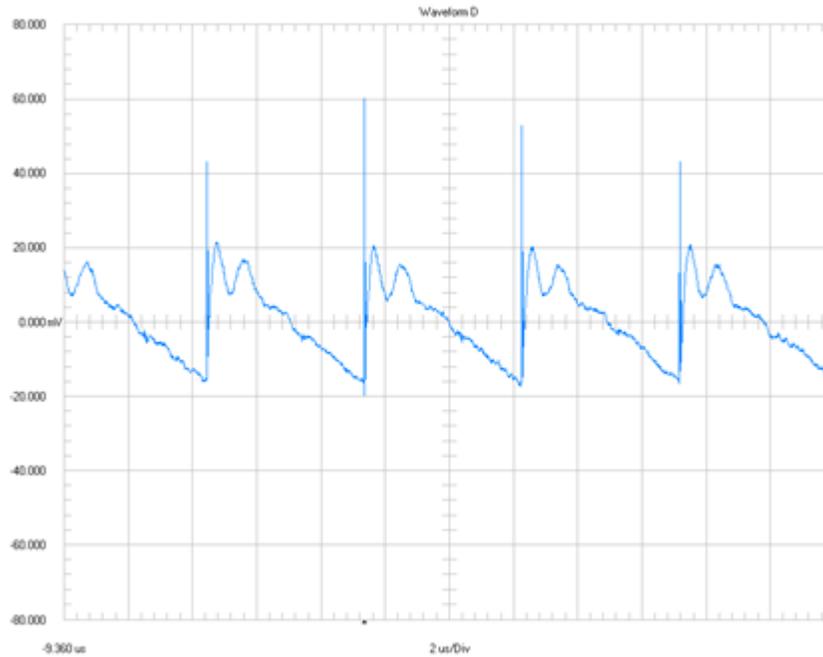


- 20mV/div (20MHz bandwidth setting)
- 2 $\mu$ s/div

The thermal stress at this 6W design is fairly low due to reasonable full load efficiency >91%.

### 3.3 Input Voltage Ripple


**Figure 9. Input Voltage Ripple (AC Coupled)**

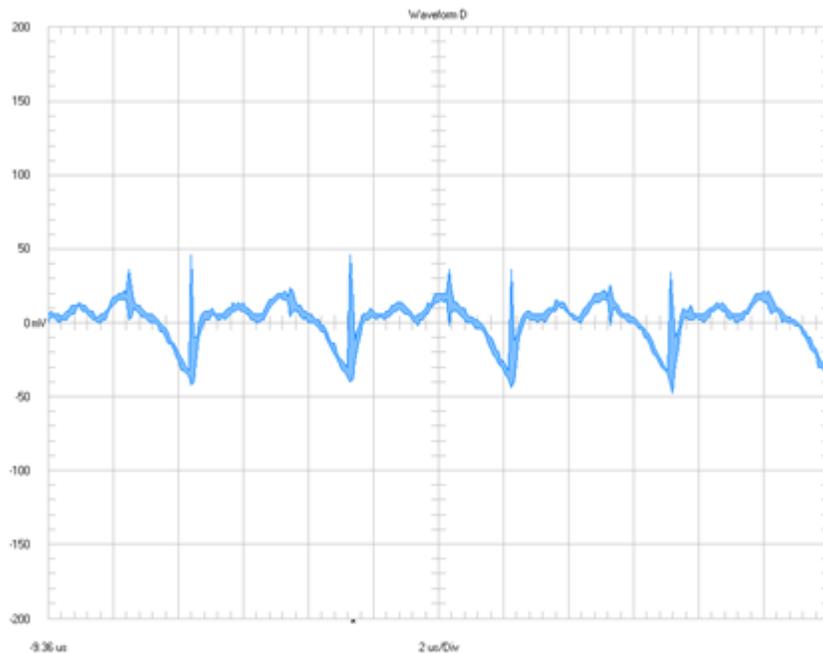

- 50mV/div (20MHz bandwidth setting)
- 2 $\mu$ s/div

### 3.4 Bode Plot


Figure 10. Loop Response with ~0.25A Output Current and ~12V Input Voltage

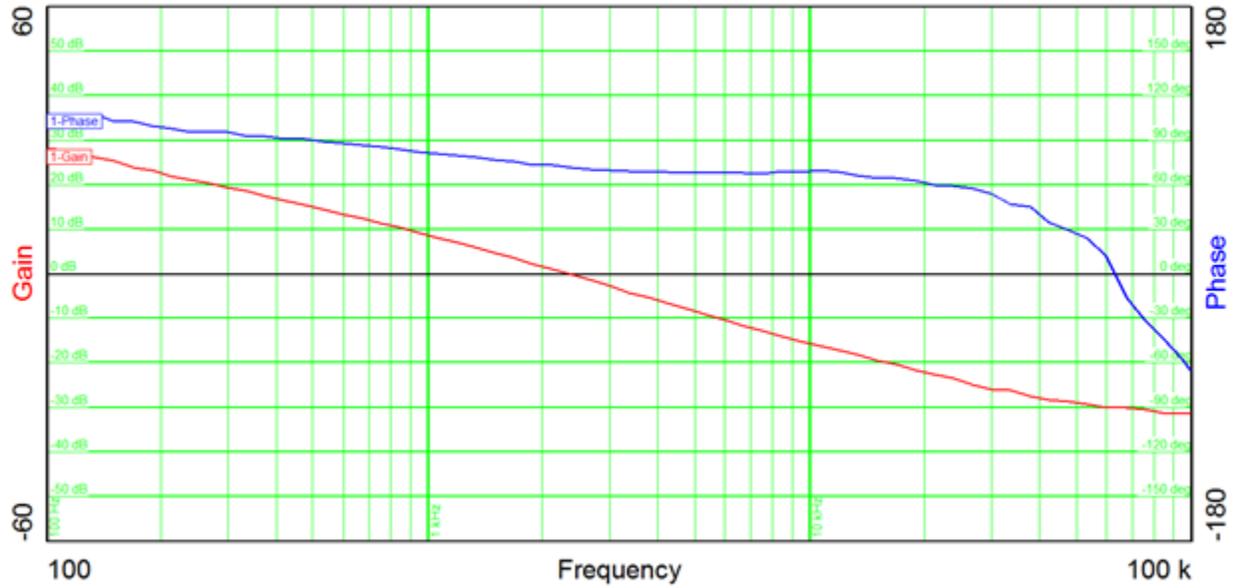

	12V
Bandwidth (kHz)	2.35
Phasemargin	72°
slope (20dB/decade)	-1.23
gain margin (dB)	-30
slope (20dB/decade)	+0.01
freq (kHz)	63

### 3.5 Load Transients

Figure 11. Load Transient (0.125A / 0.25A 50Hz with Electronic Load N3305A)

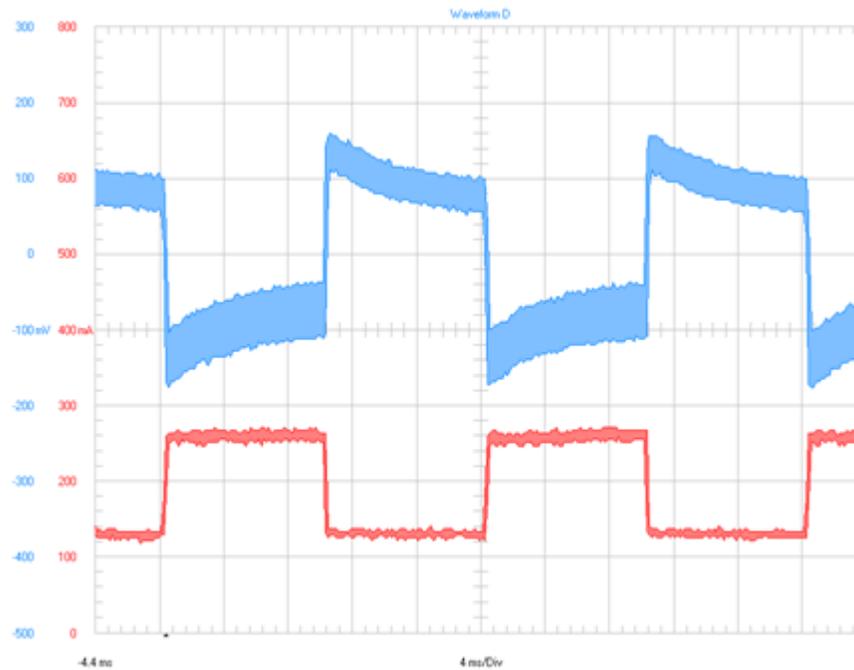


- Channel 1 (blue): output voltage => 100mV/div (20MHz bandwidth setting)
  - Channel 2 (red): Output Current => 100mA/div (10kHz bandwidth setting)
  - 4ms/div
- The DC error is related to limited load regulation by primary side regulation;  
 The dynamic load deviation due to 50% load transient is only 100mV, **so less than 0.5% !**

### 3.6 Start-up Sequence

The power supply was connected.

**Figure 12. Start-up with Electronic Load**

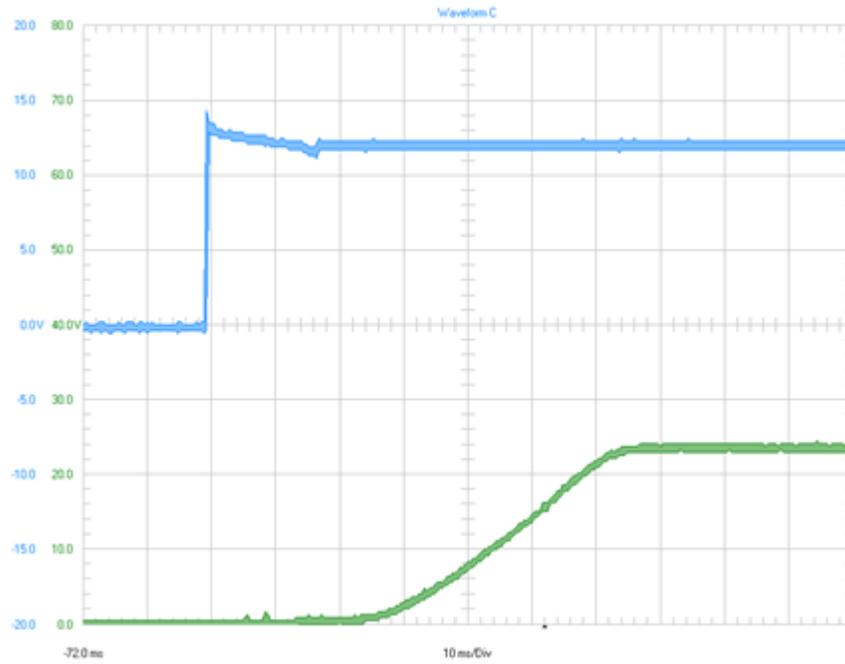


- Channel 1 (blue): input voltage => 5V/div
- Channel 2 (green): output voltage => 10V/div
- 10ms/div

### 3.7 Shut-Down Sequence

The power supply was disconnected

**Figure 13. Shut-down with Electronic Load**

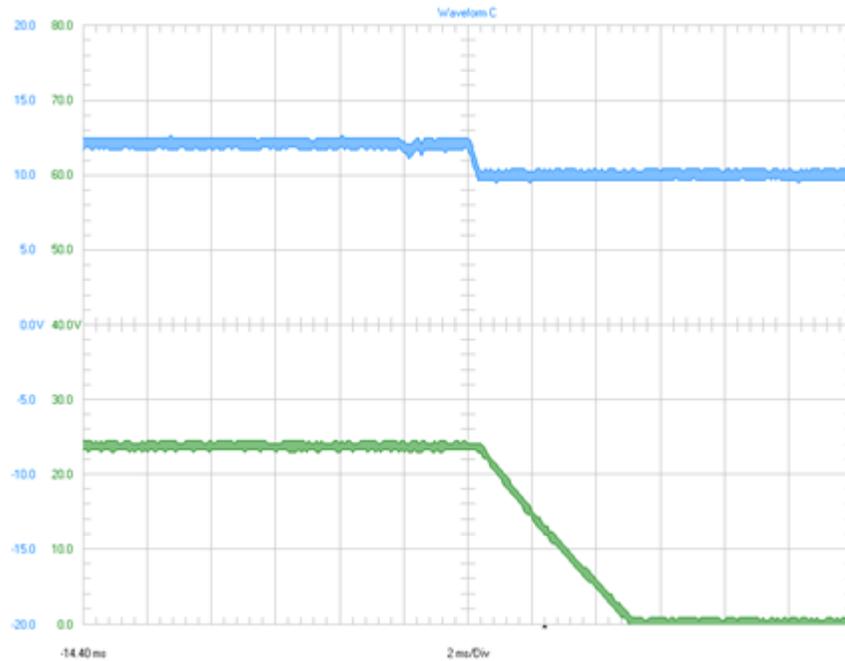

- Channel 1 (blue): input voltage => 5V/div
- Channel 2 (green): output voltage => 10V/div
- 2ms/div

## Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

<b>Changes from Original (October 2018) to A Revision</b>	<b>Page</b>
• Changed Output Voltage vs Output Current graph .....	<b>3</b>

---

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated