

Test Report: PMP30523RevD

Wide Input Range 3 W Power Reference Design with four Outputs



Description


This tiny power supply using LM51551-Q1 generates four output voltages, two of them isolated. On primary side 11 V/100 mA plus 3.3 V/300 mA I/O voltage is available plus another two 11 V/50 mA outputs on secondary side. By using a cost effective discrete linear regulator the input voltage range is expanded up to 60 V; by diode-ORing the controller itself is supplied out of the primary 11 V, means no losses at the LDO that is just used during startup.

The power stage could be configured either in flyback or SEPIC topology; for less EMI here the SEPIC topology is used by implementing flying capacitor C8. Either flyback or SEPIC is working in DCM to use a small transformer and to achieve best dynamic performance by shifting RHPZ into high frequency range.

The loop is closed on primary side to avoid an opto isolator; by using a multiple feedback path the loop could be closed at 11 V primary or 3.3 V primary – or just using both; by using both paths this could be weighted by the demand of the application. Here the feedback current of 1mA is combined by 500 uA out of 3.3 V, another 500 uA out of 11 V. The primary side regulation needs best coupling in between primary output winding and secondary output winding of the transformer; a coupling >99% is mandatory to achieve reasonable cross regulation and load regulation.

The PCB PMP30523 RevB needs transformer revision r01, that is just suited for prototyping purposes.

 For mass production use WE 750 31 80 29 revision r00.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input Voltage (DC)	6 V to 60 V, startup needs >7.5V
Output Voltage 1 (non-isolated)	3.3 V
Output Current 1 (max)	300 mA
Output Voltage 2 (non-isolated)	11 V
Output Current 2 (max)	100 mA
Output Voltage 3 and 4 (both isolated)	11 V
Output Current 3 and 4 (max)	50 mA
Switching frequency	200 kHz

1.2 Considerations

- This circuit switches on at 7.5 V input voltage and switches off at 5.7 V input voltage.
- The regulation is primary side on both non-isolated output voltages (mixed regulation 50% / 50%).
- As load a resistor switchboard was used – 10% / 20% / 50% / 100% load for each output.
- Unless otherwise mentioned the measurements were done with full load at all outputs.
- The converter has been tested at 6V / 24V / 60V input voltage

2 Testing and Results

2.1 Efficiency Graphs

 


Figure 1. Efficiency vs Load

Due to availability BZ096N10LS5 was used in the circuit.
 With BZ146N10LS5 the switching losses will be reduces slightly.
 A bigger core geometry and rework on the transformer windings will improve efficiency further;
 this revision has been designed for smallest size.

 


Figure 2. Loss vs Load

2.2 Load Regulation (feedback weighted 50% out of 3.3V pri and 50% out of 11V pri)

2.2.1 6 V Input Voltage

 


Figure 3. Output Voltage vs Load for the 11 V Outputs

 


Figure 4. Output Voltage vs Load for the 3.3 V Output

2.2.2 24 V Input Voltage

 


Figure 5. Output Voltage vs Load for the 11 V Outputs

 


Figure 6. Output Voltage vs Load for the 3.3 V Output

2.2.3 60 V Input Voltage

 


Figure 7. Output Voltage vs Load for the 11 V Outputs

 


Figure 8. Output Voltage vs Load for the 3.3 V Output

2.3 Cross Regulation 10% load <>100% load

Table 1 shows the cross regulation of all outputs. "0" means 10% of load, "1" stands for 100% of load.

primary				secondary			
11V		3.3V		11V		11V	
0	11.34	0	3.35	0	11.41	0	11.40
0	11.33	0	3.35	0	11.34	1	10.71
0	11.33	0	3.35	1	10.71	0	11.33
0	11.25	0	3.35	1	10.74	1	10.74
0	12.08	1	3.17	0	12.20	0	12.19
0	11.92	1	3.20	0	11.96	1	11.27
0	11.92	1	3.20	1	11.27	0	11.95
0	11.87	1	3.22	1	11.27	1	11.25
1	11.02	0	3.40	0	11.46	0	11.44
1	11.01	0	3.40	0	11.43	1	11.00
1	11.01	0	3.40	1	11.02	0	11.42
1	11.10	0	3.40	1	11.03	1	11.01
1	11.56	1	3.28	0	12.05	0	12.02
1	11.62	1	3.29	0	11.99	1	11.53
1	11.61	1	3.29	1	11.55	0	11.95
1	11.58	1	3.30	1	11.53	1	11.51

Table 1. Cross Regulation

The feedback of the controller is shared between the two non-isolated output voltages by 50% - 50%; this cross regulation has been measured at input voltage 12V; YELLOW is minimum output voltage, ORANGE is maximum output voltage.

2.4 Line Regulation

 


Figure 9. Output Voltage vs Input Voltage for the 11 V Outputs

 


Figure 10. Output Voltage vs Input Voltage for the 3.3 V Output

With the measurement for line regulation efficiency and loss were calculated.

 


Figure 11 Input Voltage vs Efficiency and Loss

2.5 Thermal Images

Name	6 Vin	24 Vin	Temperature
D1	35.2°C	36.9°C	41.2°C
D3	35.8°C	37.6°C	41.6°C
D5	38.6°C	40.6°C	44.8°C
D8	48.9°C	50.1°C	53.8°C
Q1	37.9°C	49.8°C	49.1°C
T1	44.5°C	40.6°C	59.1°C

Table 2 Summary of Thermal Images

2.5.1 6 V Input Voltage

 


Figure 12. IR-Foto @ 6 Vin

2.5.2 24 V Input Voltage

 


Figure 13. IR Foto @ 24 Vin

2.5.3 60 V Input Voltage

 


Figure 14. IR Foto @ 24 Vin

3 Waveforms at Full Load in SEPIC Configuration

3.1 Switching

3.1.1 Q1 Drain to GND

3.1.1.1 6 V Input Voltage

 


Figure 15 Switchnode to GND @ 6 Vin

3.1.1.2 24 V Input Voltage

 


Figure 16. Switchnode to GND @ 24 Vin

3.1.1.3 60 V Input Voltage

3.1.1.3.1 SEPIC Configuration

 


Figure 17 Switchnode to GND @ 60 Vin SEPIC

3.1.1.3.2 **Flyback** Configuration (to be compared w/ prior SEPIC configuration)

 


Figure 18 Switchnode to GND @ 60 Vin Flyback with R200 =10 kOhms
(= hard clamping of Vds, but lossy)

3.1.2 Q1 Gate to GND

3.1.2.1 6 V Input Voltage

 


Figure 19 Gate to GND @ 6 Vin

3.1.2.2 24 V Input Voltage

 


Figure 20. Gate to GND @ 24 Vin

3.1.2.3 60 V Input Voltage

 


Figure 21. Gate to GND @ 60 Vin

3.2 Output Voltage Ripple

3.2.1 3.3 V Output Voltage (Non-Isolated)

 


Figure 22. 3.3 V Output Voltage

3.2.2 11 V Output Voltage (Non-Isolated)

 


Figure 23. 11 V Output Voltage (Non-isolated)

3.2.3 11 V Output Voltage (Isolated VO1)

 


Figure 24. 11 V Output Voltage (Isolated Vo1)

3.2.4 11 V Output Voltage (Isolated VO2)

 


Figure 25. 11 V Output Voltage (Isolated Vo2)

3.3 Input Voltage Ripple

3.3.1 6 V Input Voltage

 


Figure 26. Input Voltage Ripple 6 V

3.3.2 24 V Input Voltage

 


Figure 27. Input Voltage Ripple 24 V

3.3.3 60 V Input Voltage

 


Figure 28. Input Voltage Ripple 60 V

3.4 Bode Plot

3.4.1 Flyback Configuration, 100% feedback 11Vpri

	6 V	24 V	60 V
Bandwidth (kHz)	2.86	2.86	3.18
Phasemargin	80°	79°	80°
slope (20dB/decade)	-1.1	-1.1	-1.1
gain margin (dB)	-24	-34	-36
slope (20dB/decade)	-1.8	0	-0.66
freq (kHz)	78.3	93	101

Table 3. Bodeplots (Flyback)

3.4.1.1 6 V Input Voltage

 


Figure 29. Bode Plot 6 Vin (Flyback 11V FB)

3.4.1.2 24 V Input Voltage

 


Figure 30. Bode Plot 24 Vin (Flyback 11V FB)

3.4.1.3 60 V Input Voltage

 


Figure 31. Bode Plot 60 Vin (Flyback 11V FB)

3.4.2 SEPIC Configuration, 100% feedback 11Vpri

	6 V	24 V	60 V
Bandwidth (kHz)	2.67	2.84	3.18
Phasemargin	79°	79°	80°
slope (20dB/decade)	-1.2	-1.1	-1.1
gain margin (dB)	-25	-35	-37
slope (20dB/decade)	-1.1	+1.4	+3
freq (kHz)	77	93	110

Table 4. Bodeplots SEPIC

3.4.2.1 6 V Input Voltage

 


Figure 32. Bode Plot 6 Vin (SEPIC 11V FB)

3.4.2.2 24 V Input Voltage

 


Figure 33. Bode Plot 24 Vin (SEPIC 11V FB)

3.4.2.3 60 V Input Voltage

 


Figure 34. Bode Plot 60 Vin (SEPIC 11V FB)

3.4.3 SEPIC Configuration, 100% feedback 3V3 pri

	12 V	24 V	60 V
Bandwidth (kHz)	6.29	7.06	8.3
Phasemargin	81°	81°	810°
slope (20dB/decade)	-1.1	-1.0	-1.0
gain margin (dB)	-22	-25	-26
slope (20dB/decade)	-1.0	-1.0	-1.3
freq (kHz)	62	77	93

Table 5 Bodeplots SEPIC

3.4.3.1 12 V Input Voltage

 


Figure 35. Bode Plot 12 Vin (SEPIC 3.3V FB)

3.4.3.2 24 V Input Voltage

 


Figure 36. Bode Plot 24 Vin (SEPIC 3.3V FB)

3.4.3.3 60 V Input Voltage

 


Figure 37. Bode Plot 60 Vin (SEPIC 3.3V FB)

3.5 Start-up Sequence

To get all waveforms in one figure the measurement were done twice with different output connected on one channel (11Vsec).

3.5.1 7.5 V Input Voltage

 


Figure 38. Start-up 7.5 V

3.5.2 24 V Input Voltage

 


Figure 39. Start-up 24 V

3.5.3 60 V Input Voltage

 


Figure 40. Start-up 60 V

3.6 Shutdown Sequence

To get all waveforms in one figure the measurement were done twice with different output connected on one channel (11 Vsec).

3.6.1 6 V Input Voltage

 


Figure 41. Shutdown 6 Vin

3.6.2 24 V Input Voltage

 


Figure 42. Shutdown 24 Vin

3.6.3 60 V Input Voltage

 


Figure 43. Shutdown 60 Vin

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated