



LM27403 Synchronous Buck Converter

TI reference design number: PMP8000

Input: 12V

Output: 5V @ 30A

DC – DC Test Results

Table of Contents

1	Circuit Description.....	3
2	Photos	3
3	Efficiency	5
4	Thermal Tests.....	6
4.1	Test Setup	6
4.2	30A Load, No Airflow	7
5	Startup and Shutdown Behavior	8
5.1	Turn-on and Turn-off from Vin	8
5.2	Turn-on and Turn-off from EN	9
6	Switching and Ripple	10
6.1	Switching and Ripple	10
7	Load Transient Response.....	11
7.1	Load Transient Response.....	11

PMP8000 Test Results


1 Circuit Description


PMP8000 is a single-phase synchronous buck converter rated for 5V output at 30A from an input voltage of 12V. This design uses the LM27403 synchronous buck controller at a switching frequency of 500 kHz. CSD87350Q5D power block MOSFETs provide maximum efficiency when combined with a 250nH ferrite output inductor. The design solution uses all ceramic capacitors to fit into a minimum board area.

All tests were performed at room temperature on an open bench. A 470 μ F, 25V aluminum electrolytic input capacitor was used for input filter damping.

2 Photos

The photographs below show the PMP8000 Rev A assembly as built on PMP7935-A printed circuit board. This is a 4 layer board using 2 ounce copper on external layers and 1 ounce copper on internal layers. Power components are mounted on the top side of the board, with the control circuit on the bottom. The overall board dimensions are 2.5" x 2.5". The solution size component area is 1.1" x 0.65". The maximum component height is set by the inductor at 9.4 mm.

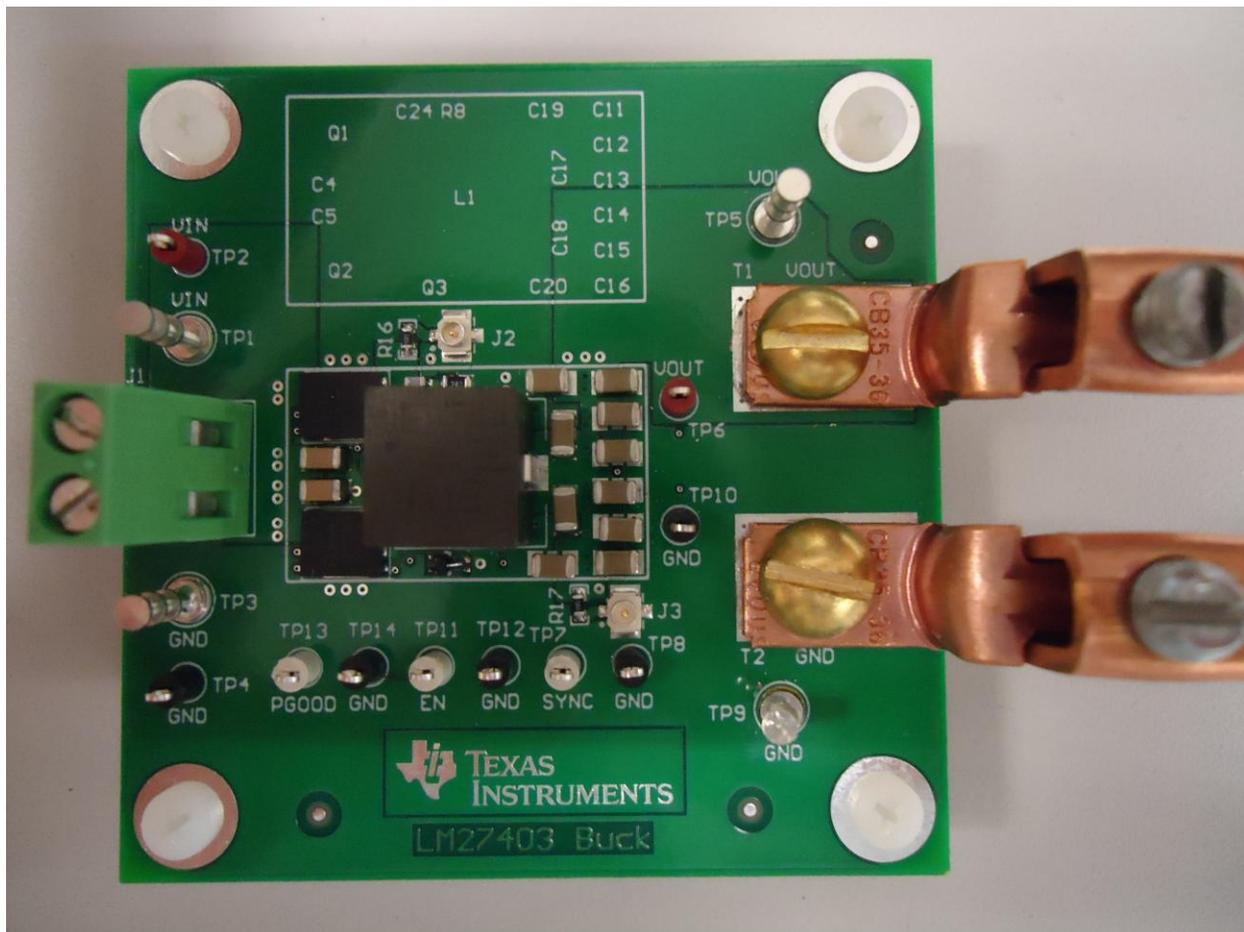


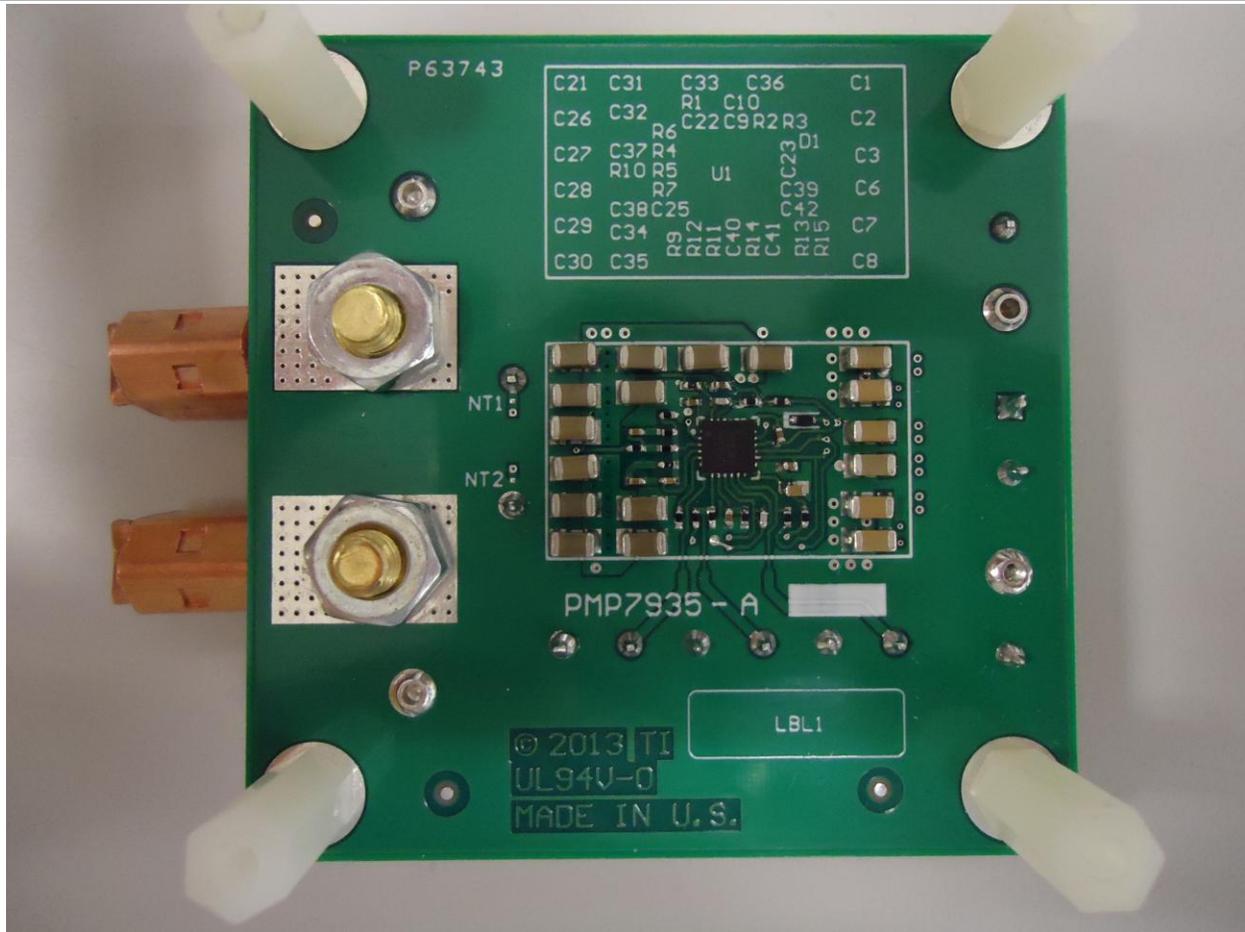

PMP8000 Test Results

3 Efficiency

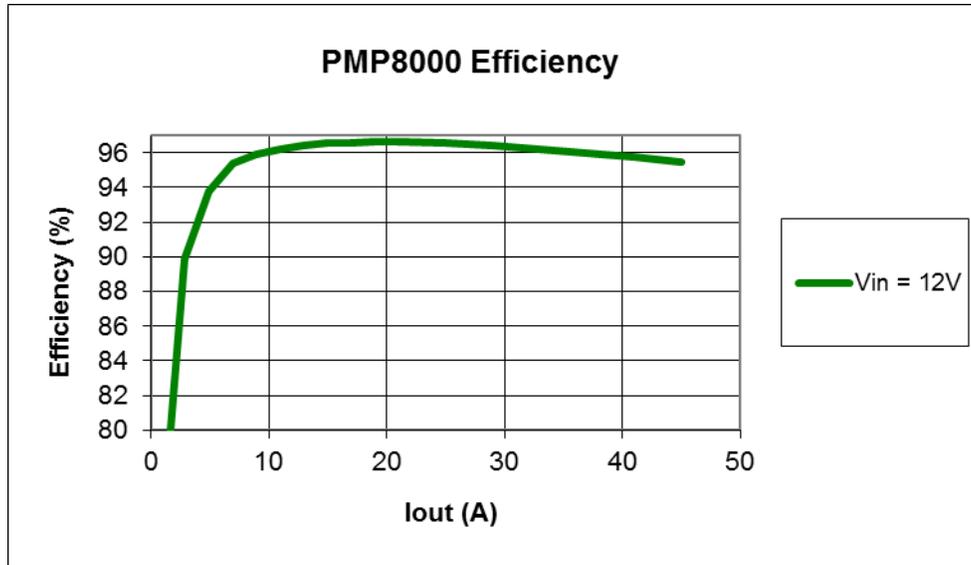The efficiency data is shown in the tables and graph below.




Vin(V)	Iin(A)	Vout(V)	Iout(A)	Efficiency(%)	Pin(W)	Pout(W)	Pdis(W)
12.000	0.135	5.017	0.00	0.000	1.62	0.00	1.62
12.000	0.510	5.018	0.90	73.794	6.12	4.52	1.60
12.000	1.350	5.020	2.90	89.864	16.20	14.56	1.64
12.000	2.195	5.021	4.92	93.786	26.34	24.70	1.64
12.000	3.045	5.024	6.94	95.420	36.54	34.87	1.67
12.000	3.905	5.026	8.94	95.887	46.86	44.93	1.93
12.0000	4.755	5.028	10.92	96.225	57.06	54.91	2.15
11.999	5.625	5.030	12.94	96.435	67.49	65.09	2.41
11.999	6.495	5.031	14.96	96.574	77.93	75.26	2.67
11.999	7.365	5.032	16.96	96.571	88.37	85.34	3.03
11.999	8.240	5.033	18.98	96.616	98.87	95.53	3.35
11.998	9.100	5.034	20.96	96.639	109.18	105.51	3.67
11.998	10.865	5.038	24.98	96.541	130.36	125.85	4.51
11.997	12.635	5.043	28.98	96.414	151.58	146.15	5.44
11.996	14.44	5.051	33.00	96.225	173.22	166.68	6.54
11.995	16.265	5.057	37.02	95.957	195.10	187.21	7.89
11.995	18.08	5.061	41.02	95.727	216.87	207.60	9.27
11.993	19.92	5.063	45.04	95.453	238.90	228.04	10.86

4 Thermal Tests


All tests were performed at room temperature on an open bench.

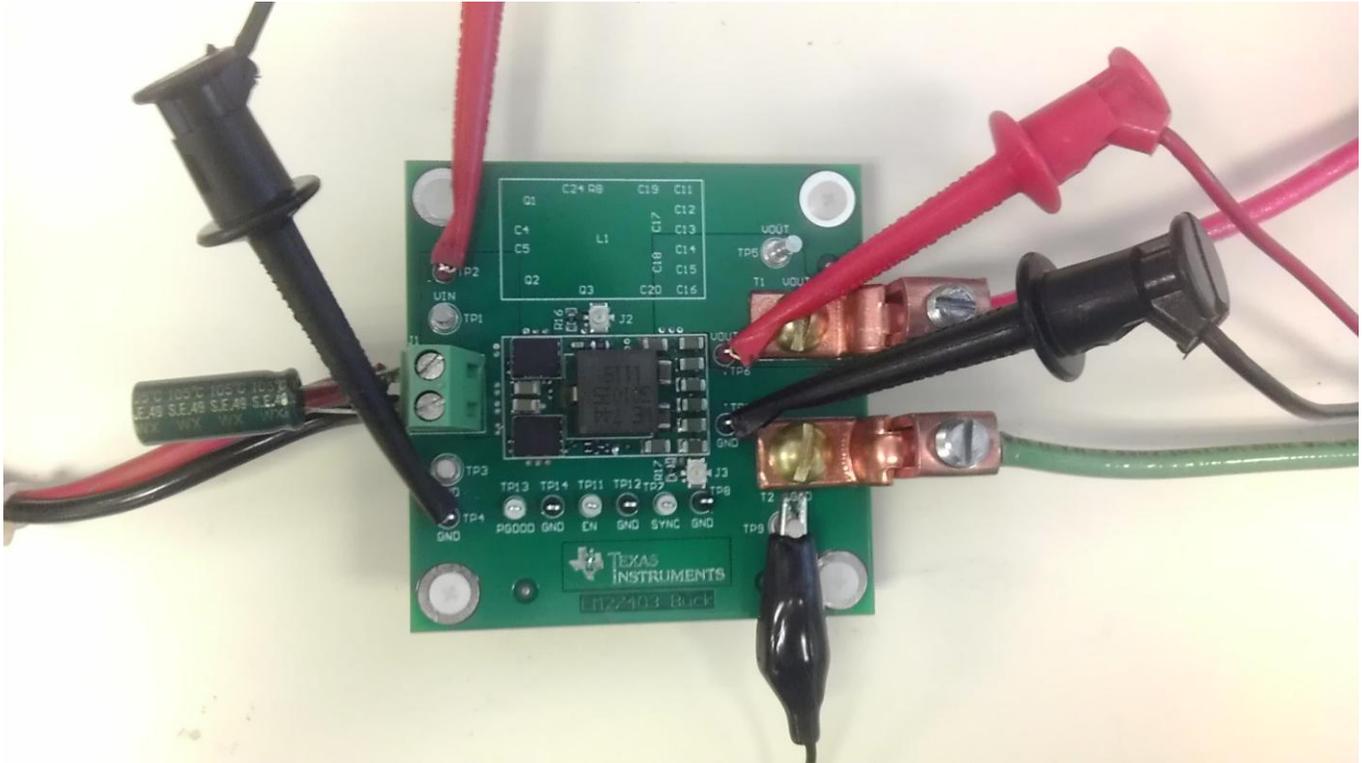4.1 Test Setup

Thermal data was taken with a Fluke handheld thermal camera.





4.2 30A Load, No Airflow

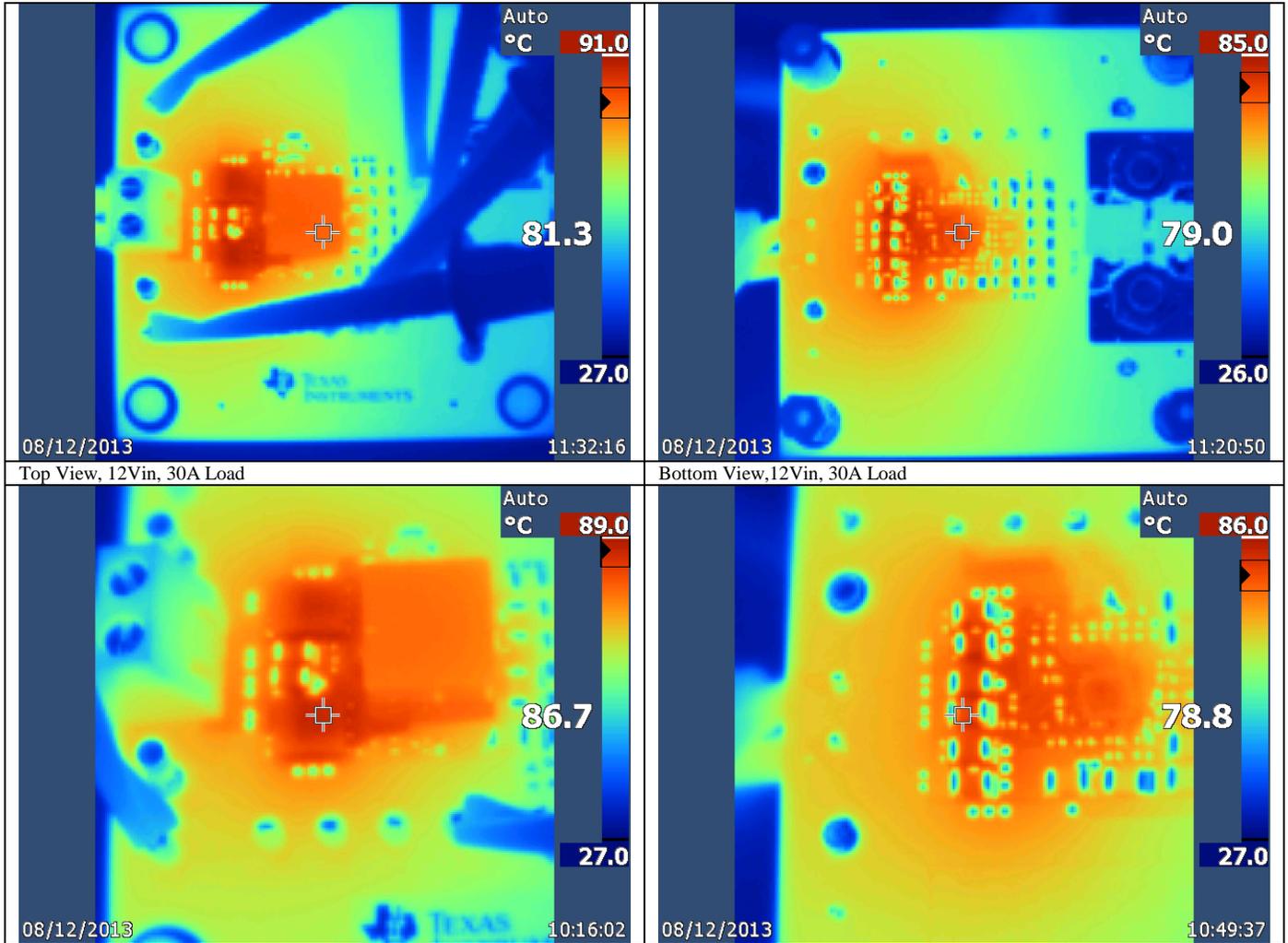

5 Startup and Shutdown Behavior

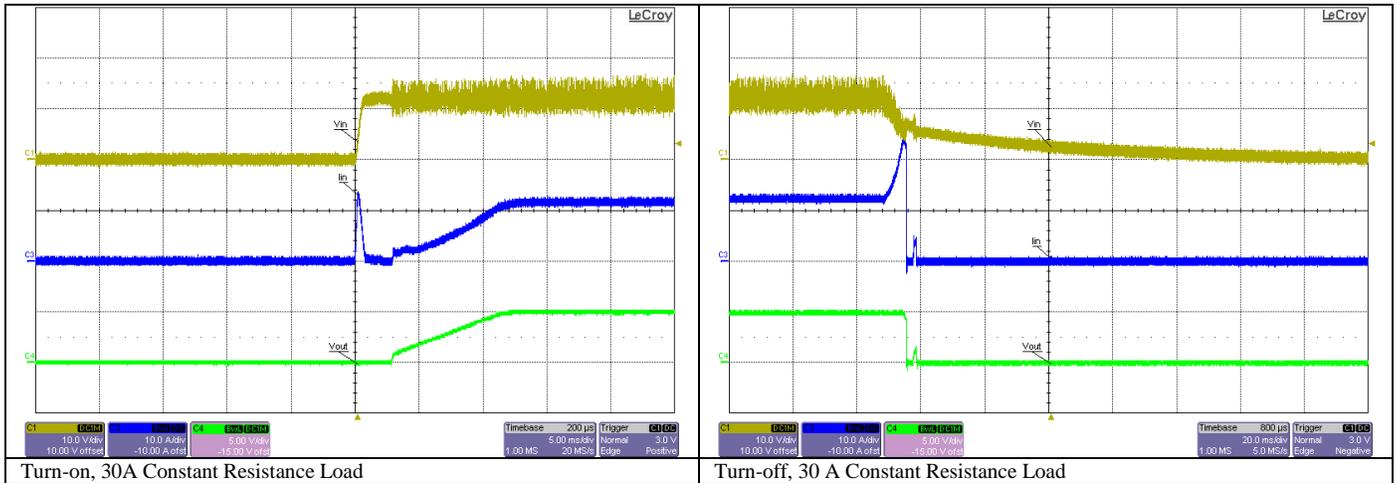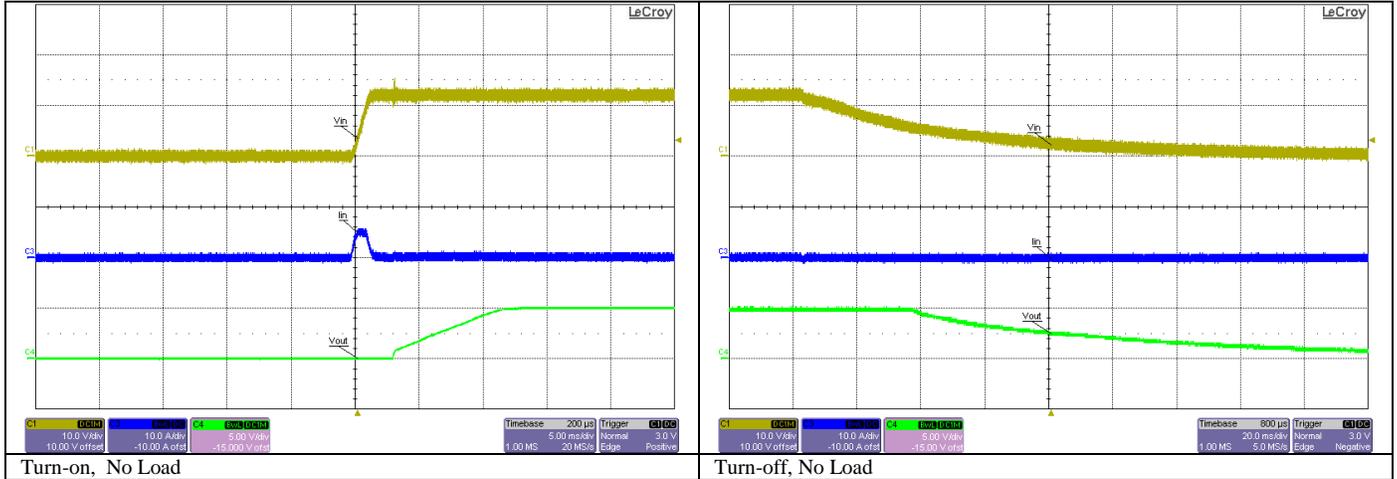5.1 Turn-on and Turn-off from V_{in}



The output voltage is well controlled at turn-on, showing no evidence of over-shoot.



PMP8000 Test Results

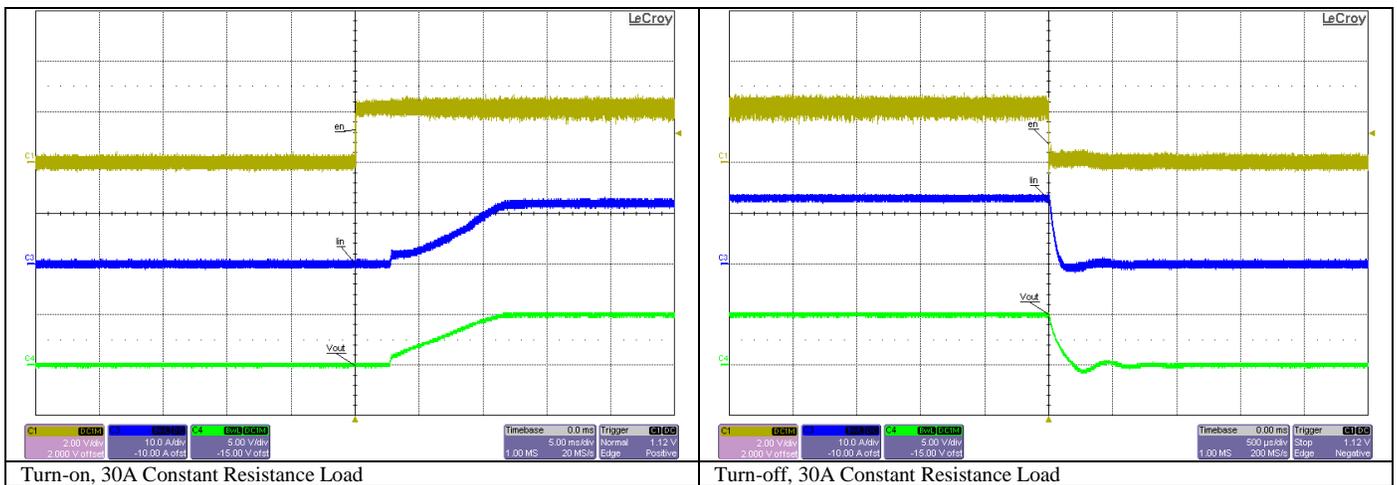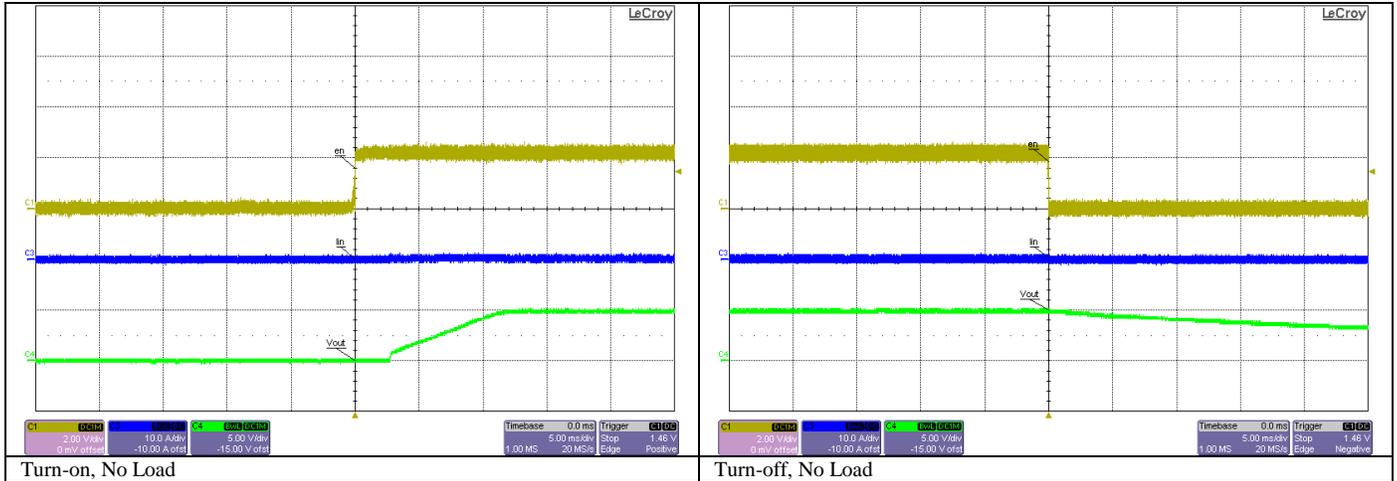5.2 Turn-on and Turn-off from EN


The output voltage is well controlled at turn-on, showing no evidence of over-shoot. Some ringing occurs at turn-off with load due to the output filter resonance.



6 Switching and Ripple

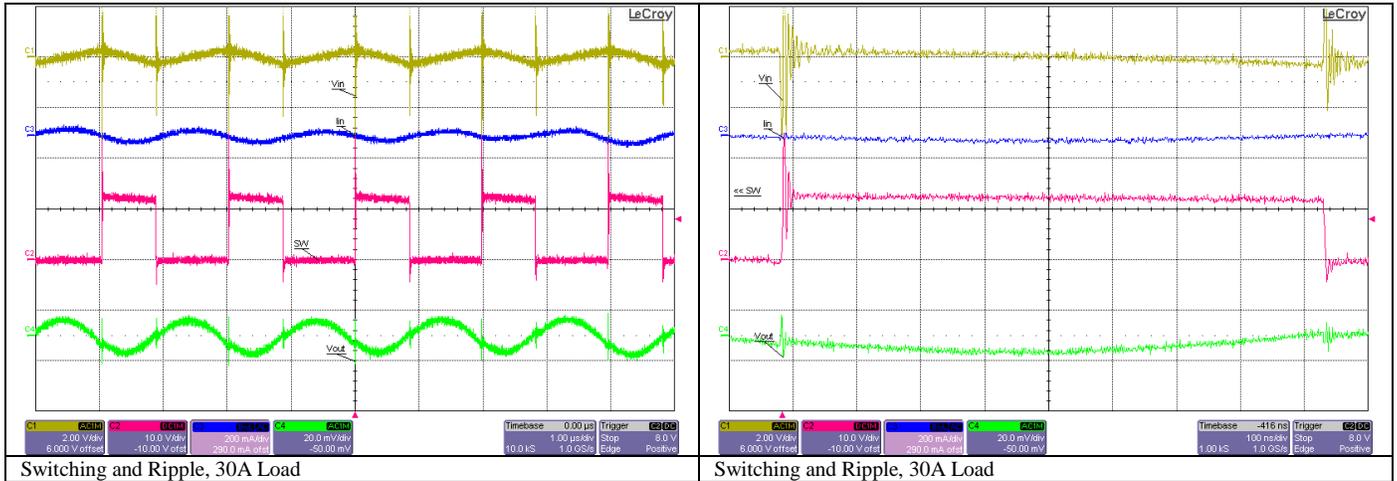6.1 Switching and Ripple

Switching and ripple tests were made with a 470 μ F, 25V aluminum electrolytic input capacitor for input filter damping.





PMP8000 Test Results

7 Load Transient Response

Load transient response for each condition was taken at two points to represent the minimum and maximum deviation. This difference occurs when the transient step coincides with either the converter off-time or on-time interval.

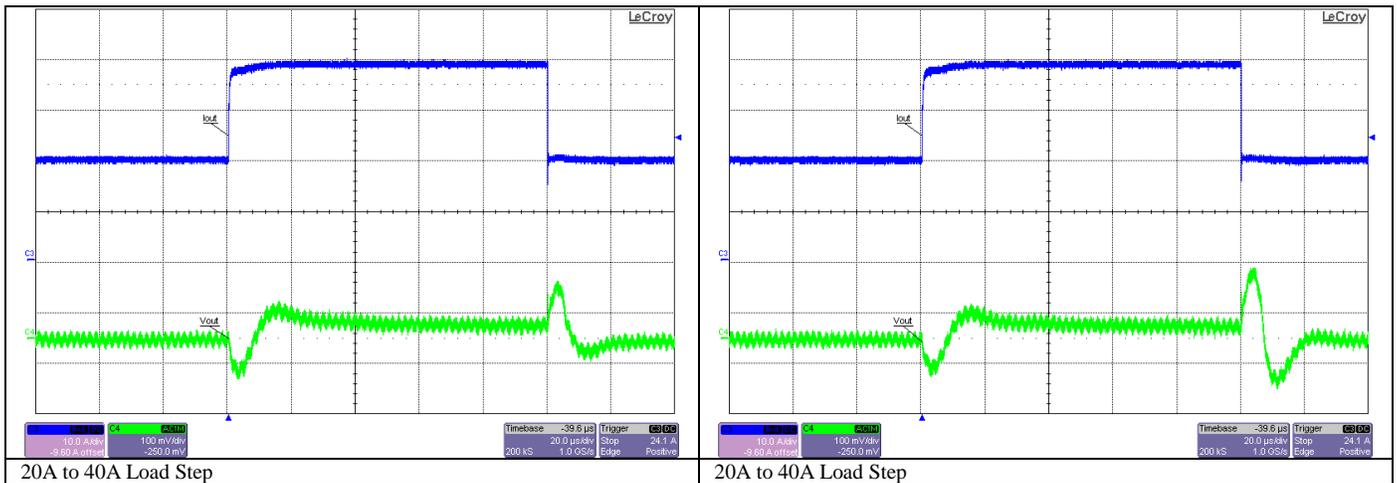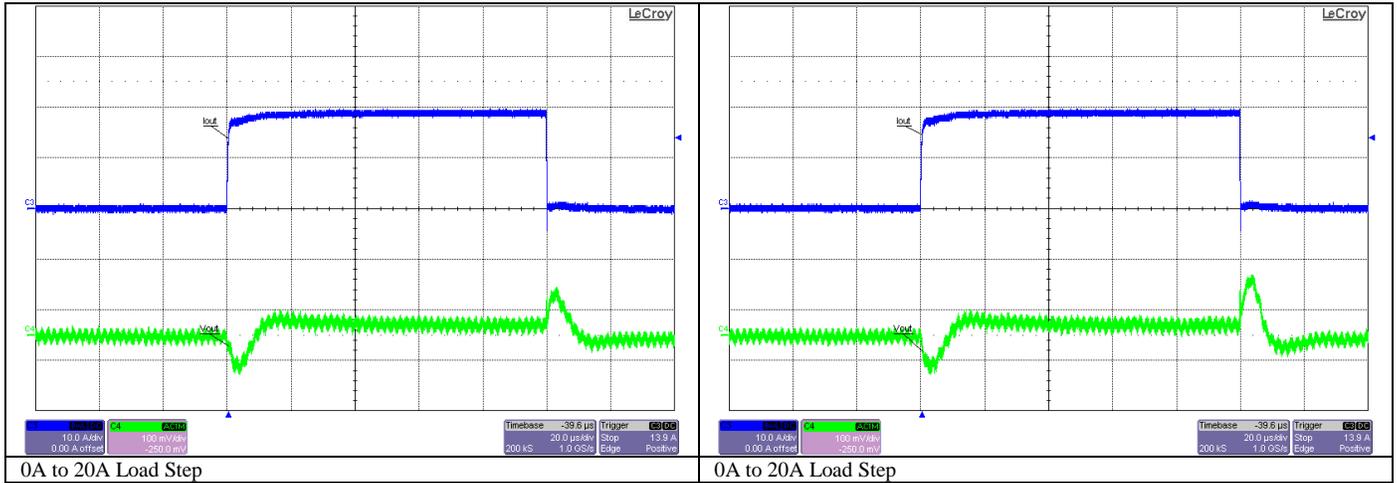7.1 Load Transient Response

The output voltage transient is within 100mV for a 20A load step.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated