
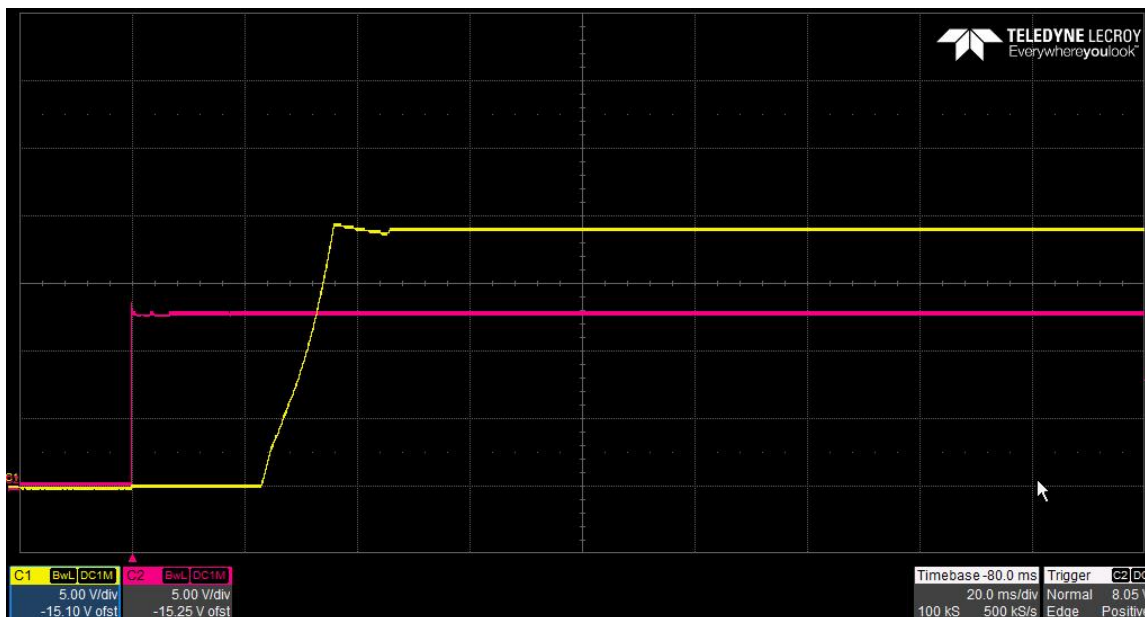


1 Startup

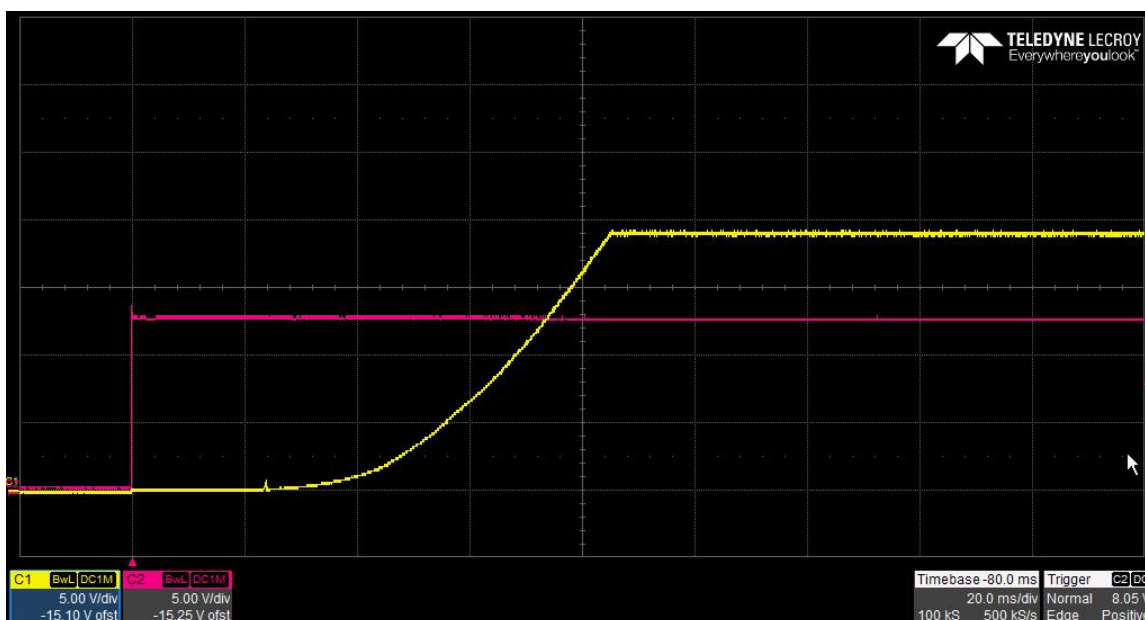
The photo below shows the 18.9V output voltage startup waveform (YELLOW) after the application of 13V in (RED) with the output loaded to 0A. (5V/DIV, 20mS/DIV)




The photo below shows the 18.9V output voltage startup waveform (YELLOW) after the application of 13V in (RED) with the output loaded to 0.6A. (5V/DIV, 20mS/DIV)



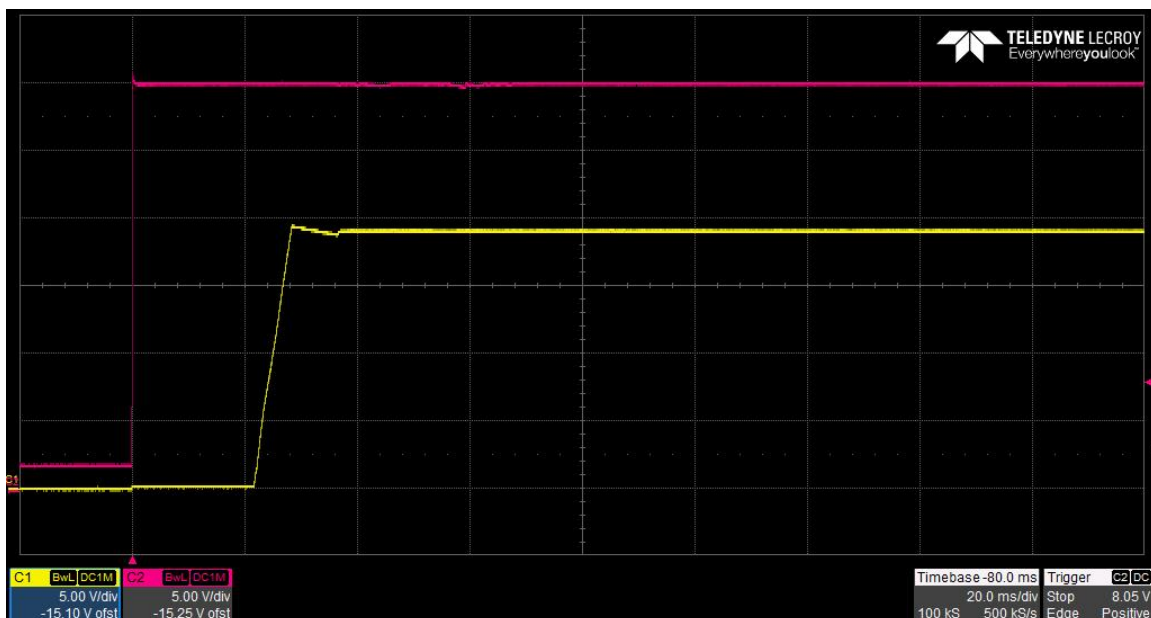The photo below shows the 18.9V output voltage startup waveform (YELLOW) after the application of 30V in (RED) with the output loaded to 0A. (5V/DIV, 20mS/DIV)





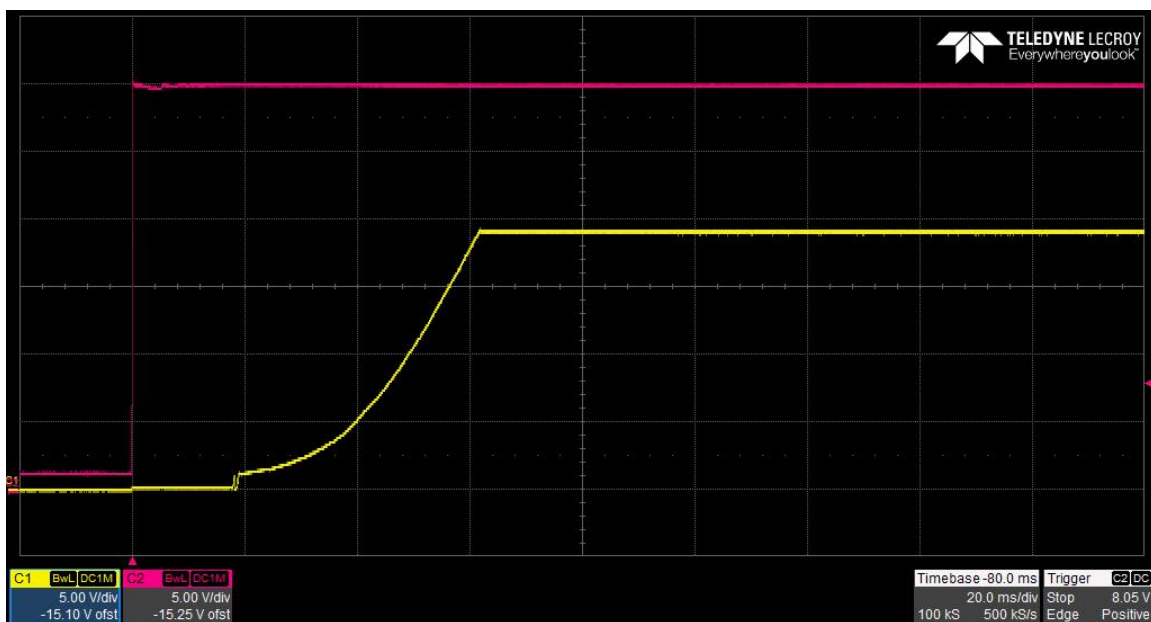
The photo below shows the 18.9V output voltage startup waveform (YELLOW) after the application of 30V in (RED) with the output loaded to 0.6A. (5V/DIV, 20mS/DIV)



2 Efficiency

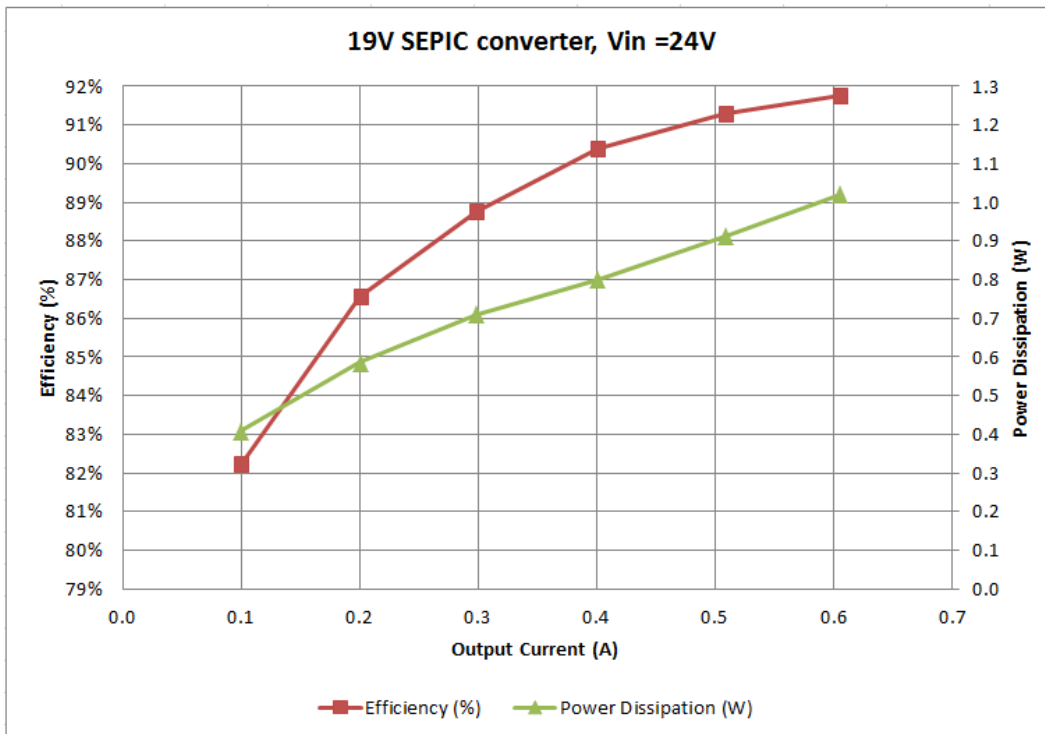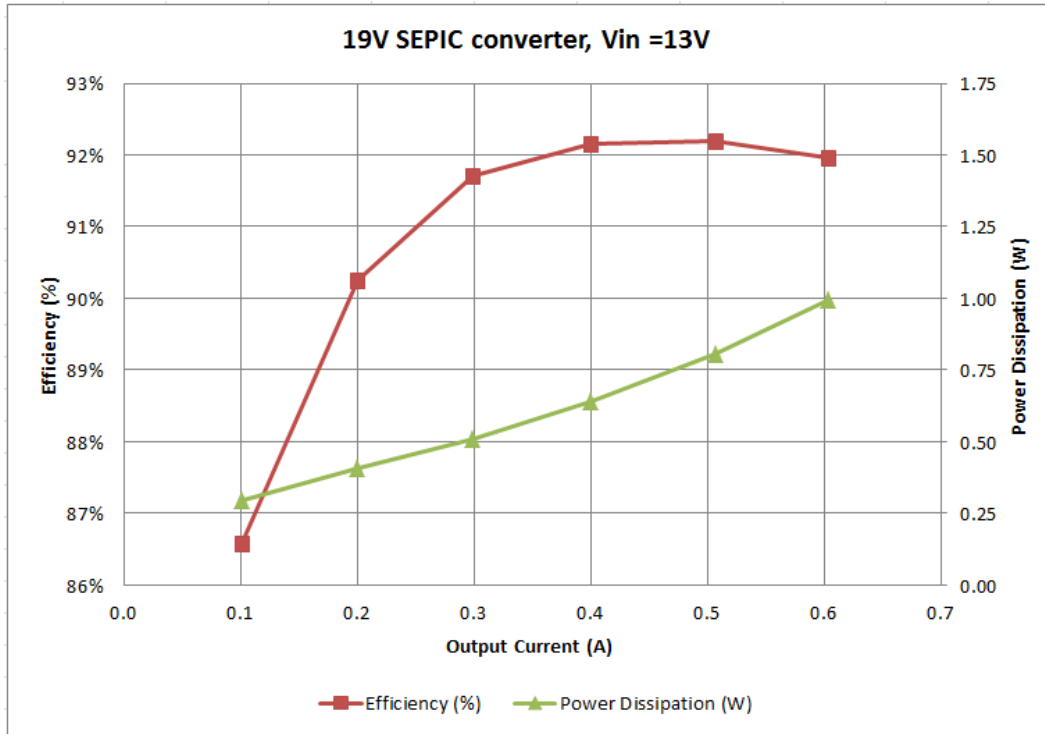
The converter efficiency is shown in the figure below.



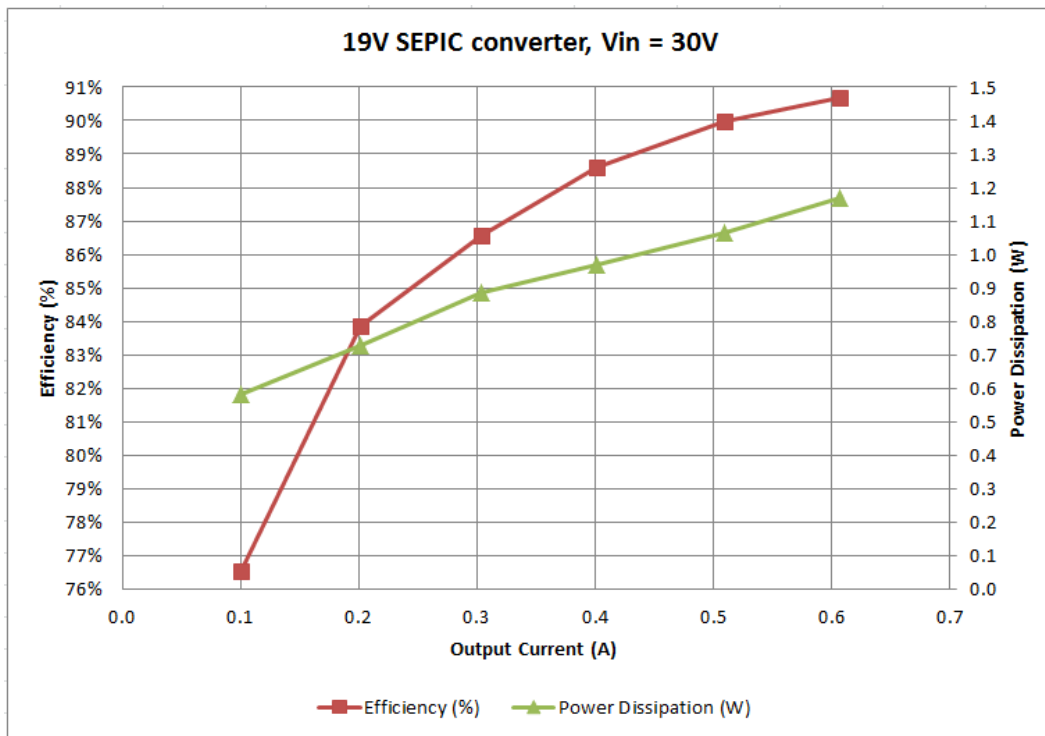


3 Output Ripple Voltage

The 18.9V output ripple voltage (ac coupled) is shown in the figure below. The image was taken with the output loaded to 0.6A. The input voltage is set to 13V. (100mV/DIV, 2uS/DIV)

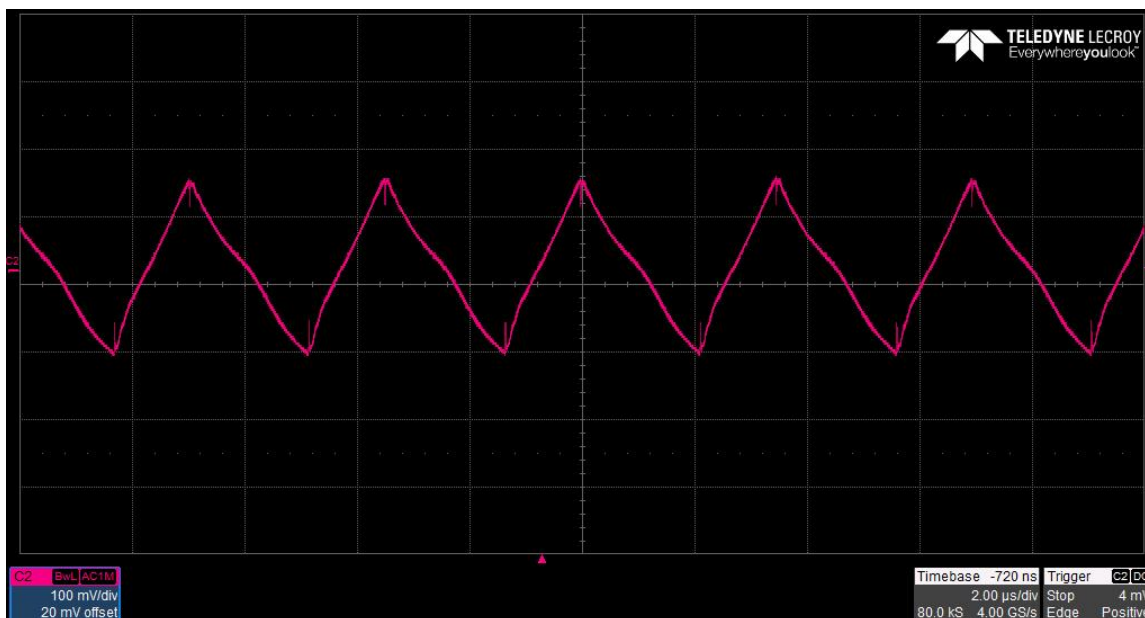


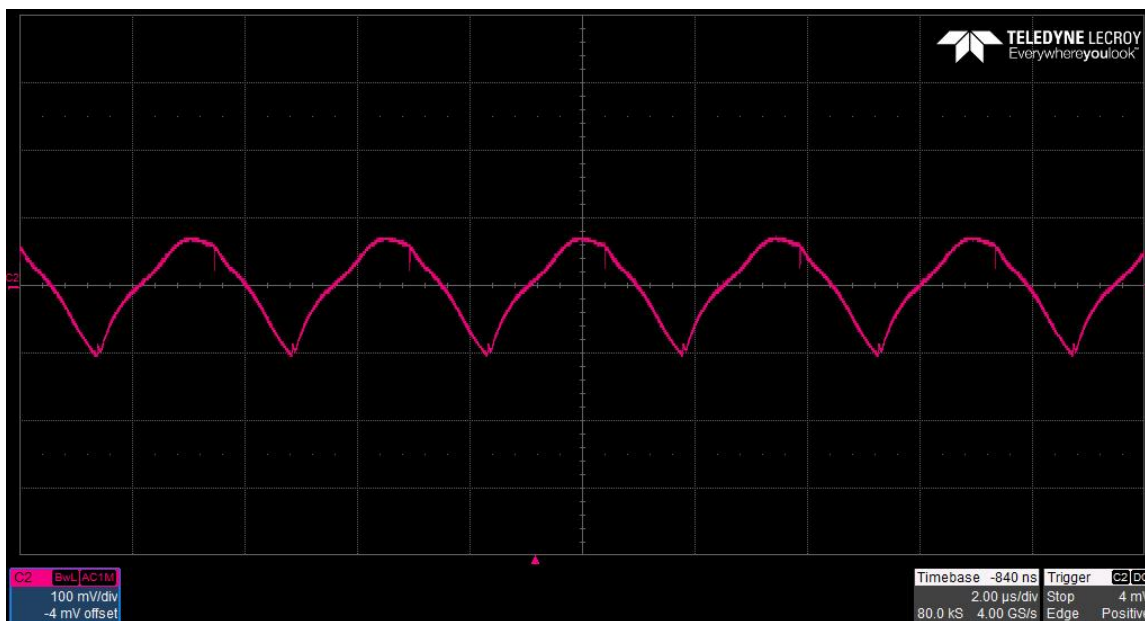The 18.9V output ripple voltage (ac coupled) is shown in the figure below. The image was taken with the output loaded to 0.6A. The input voltage is set to 30V. (100mV/DIV, 2uS/DIV)




4 Load Transients

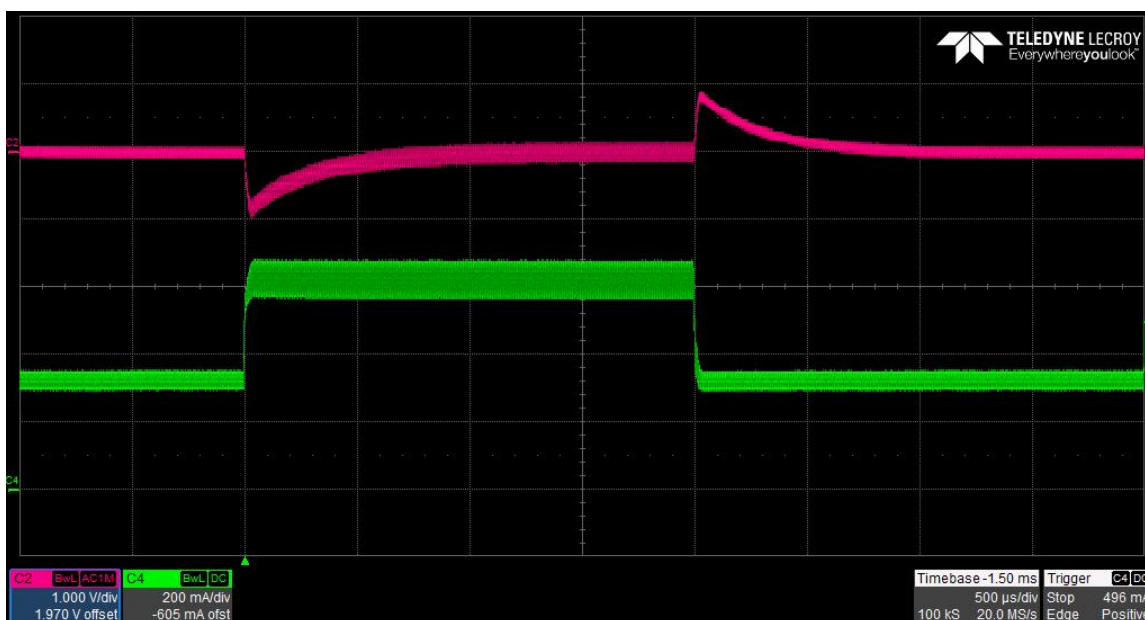The photo below shows the output voltage (ac coupled) when the load current is stepped between 0.3A and 0.6A. $V_{in} = 13V$. (1V/DIV, 200mA/DIV, 500 μ S/DIV)




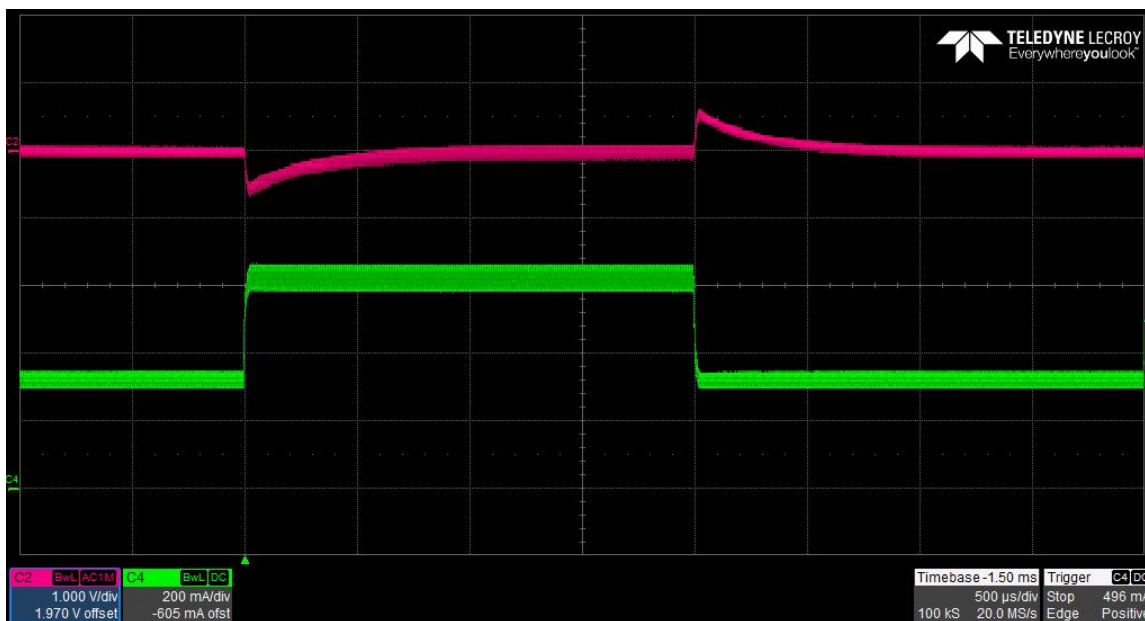The photo below shows the output voltage (ac coupled) when the load current is stepped between 0.3A and 0.6A. $V_{in} = 30V$. (1V/DIV, 200mA/DIV, 500 μ S/DIV)




5 Switch Node Waveforms

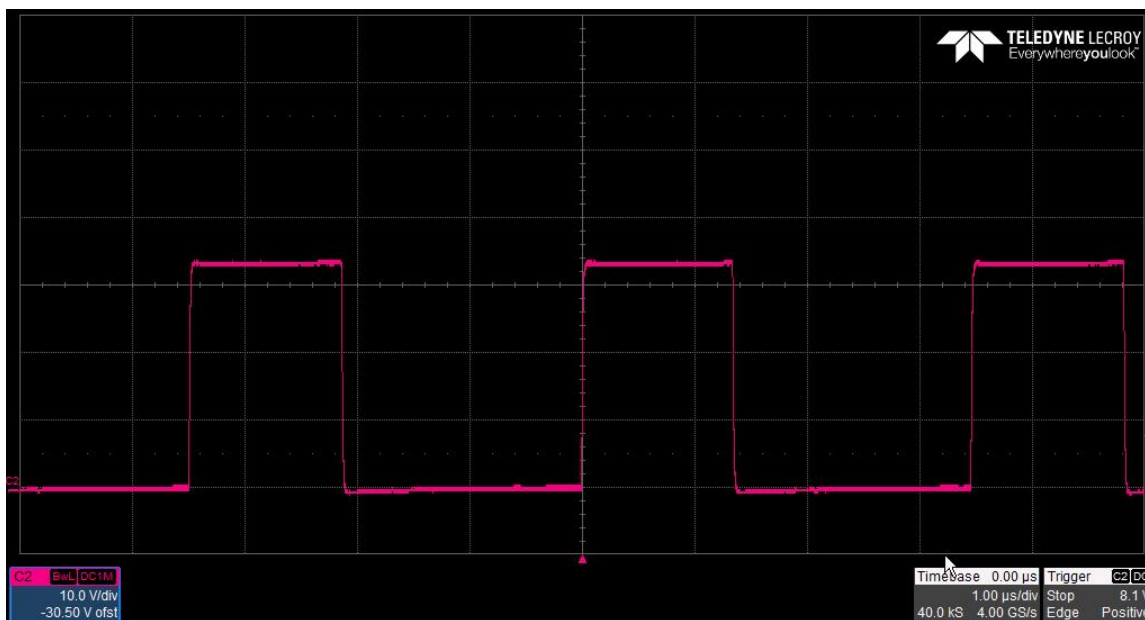
The photo below shows the SEPIC switch node voltage. The input voltage is 13V and the output is 18.9V @ 0.6A. (10V/DIV, 1uS/DIV)



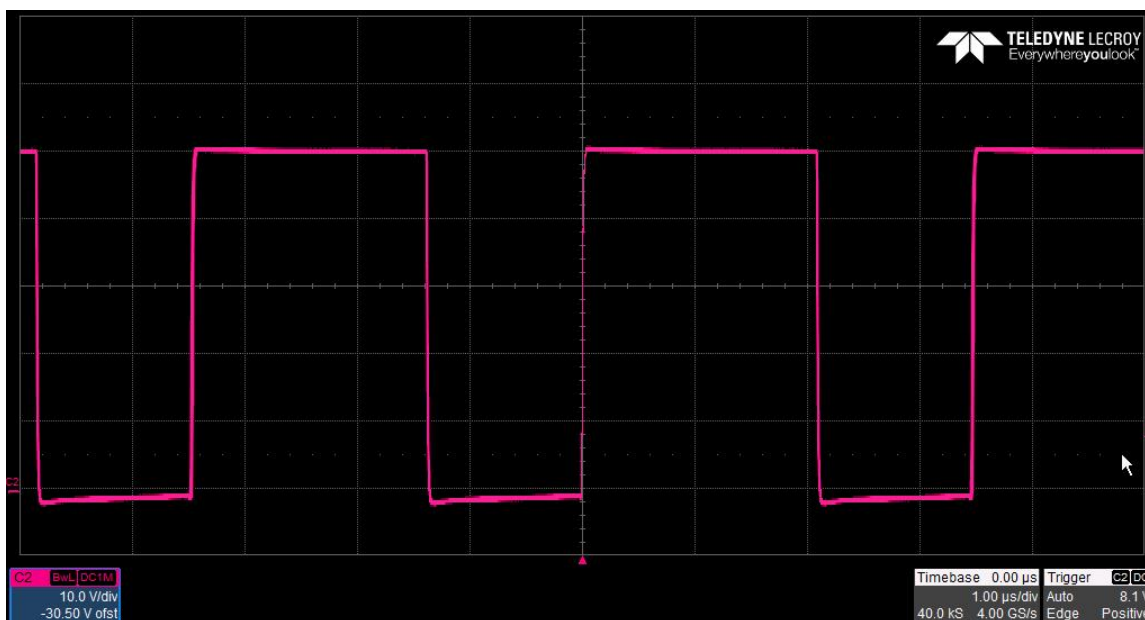
The photo below shows the SEPIC switch node voltage. The input voltage is 30V and the output is 18.9V @ 0.6A. (10V/DIV, 1uS/DIV)



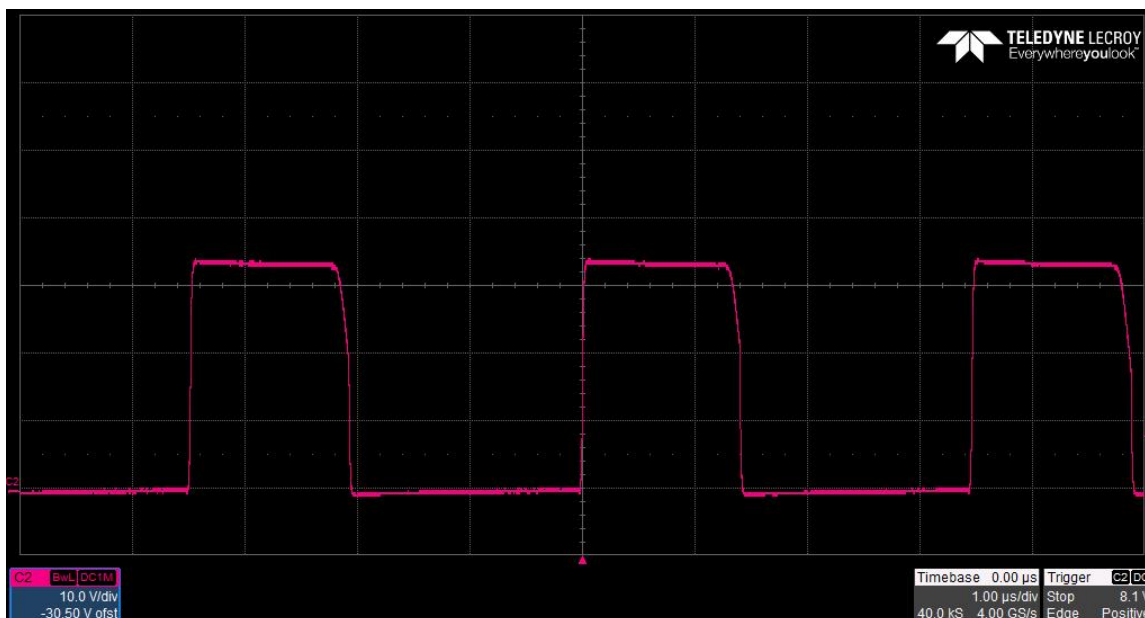The photo below shows the SEPIC switch node voltage. The input voltage is 13V and the output is 18.9V @ 0.1A. The converter is operating in discontinuous mode. (10V/DIV, 1uS/DIV)



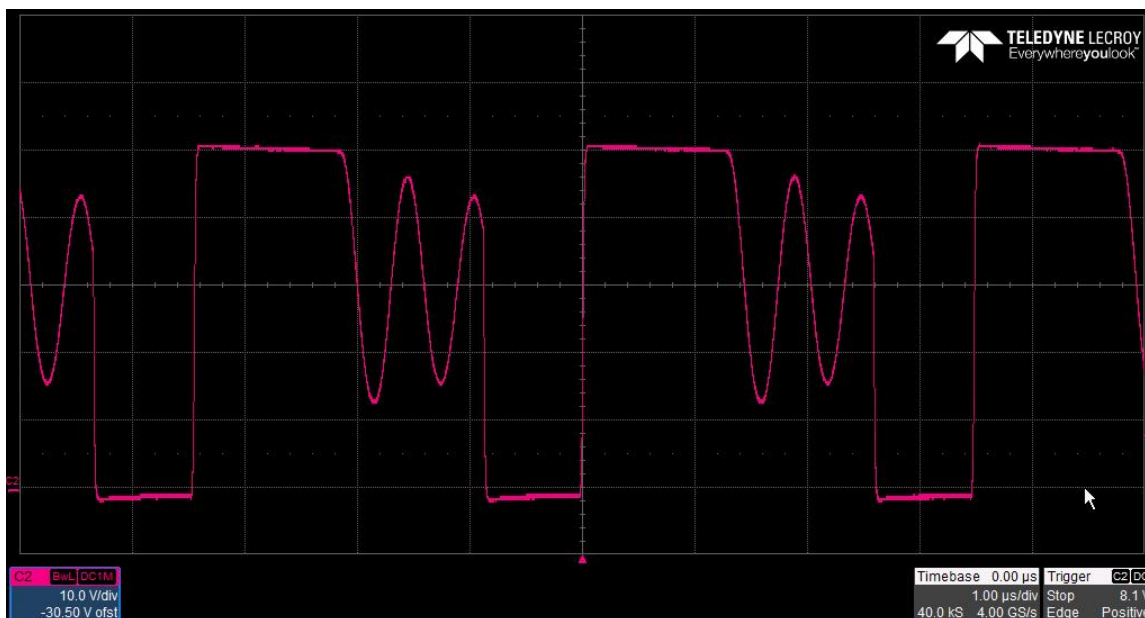The photo below shows the SEPIC switch node voltage. The input voltage is 30V and the output is 18.9V @ 0.1A. The converter is operating in discontinuous mode. (10V/DIV, 1uS/DIV)



6 Control Loop Gain / Stability


The plot below shows the 18.9V loop gain and phase margin with the output loaded to 0.6A.

Band Width = 12.5KHz,
Band Width = 8.31KHz

Phase Margin = 66 degrees
Phase Margin = 61 degrees

(Vin = 30V)

(Vin = 13V)

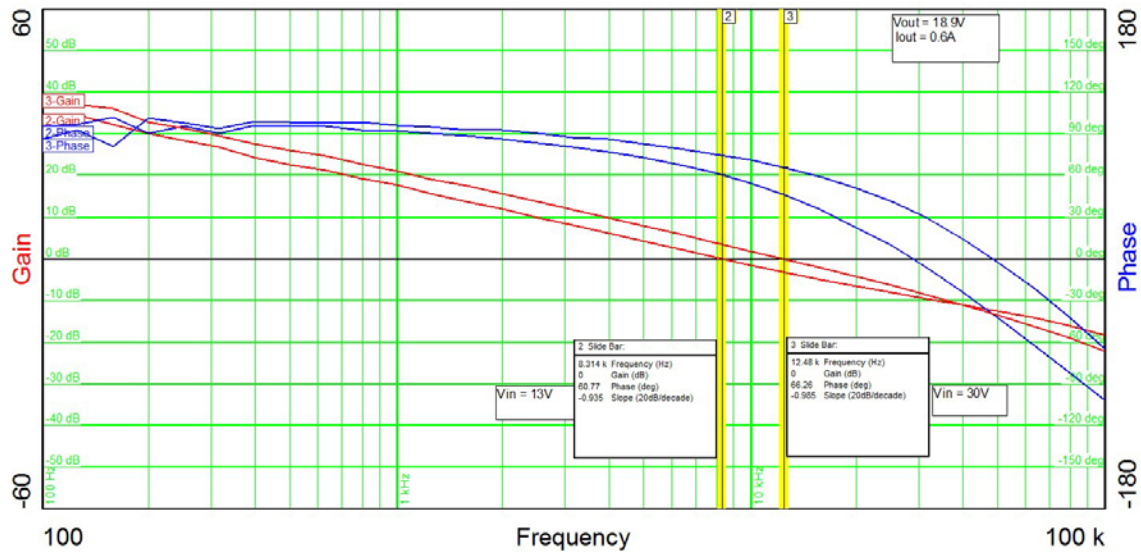


The plot below shows the 18.9V loop gain and phase margin with the output loaded to 0.1A.

Band Width = 4.95KHz,
Band Width = 3.82KHz

Phase Margin = 79 degrees
Phase Margin = 78 degrees


(Vin = 30V)

(Vin = 13V)

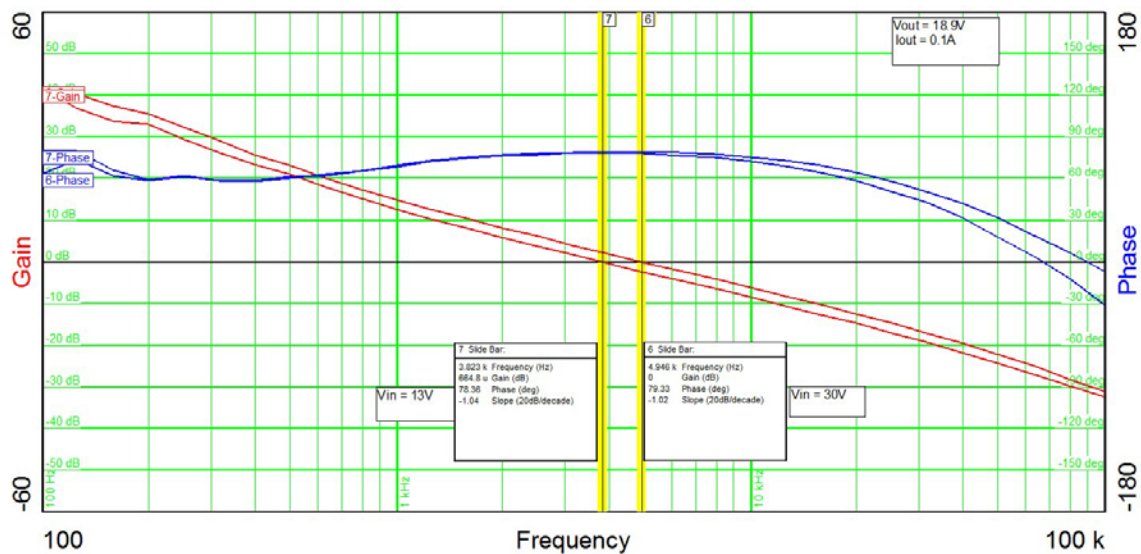


7 Photo

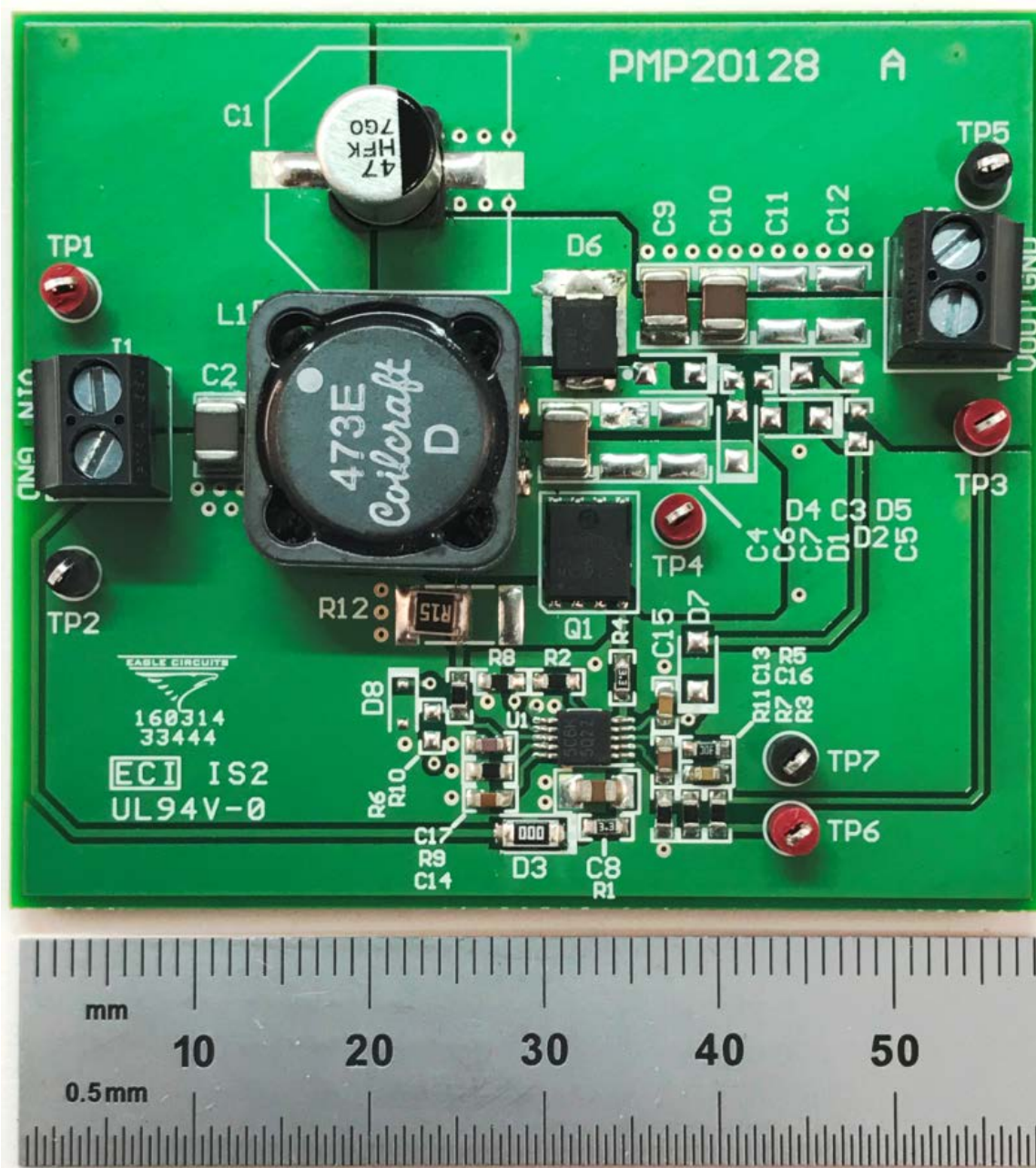The photo below shows the PMP20197 REVC assembly built on the PMP20128 REVA PCB with modifications.



8 Thermal Image

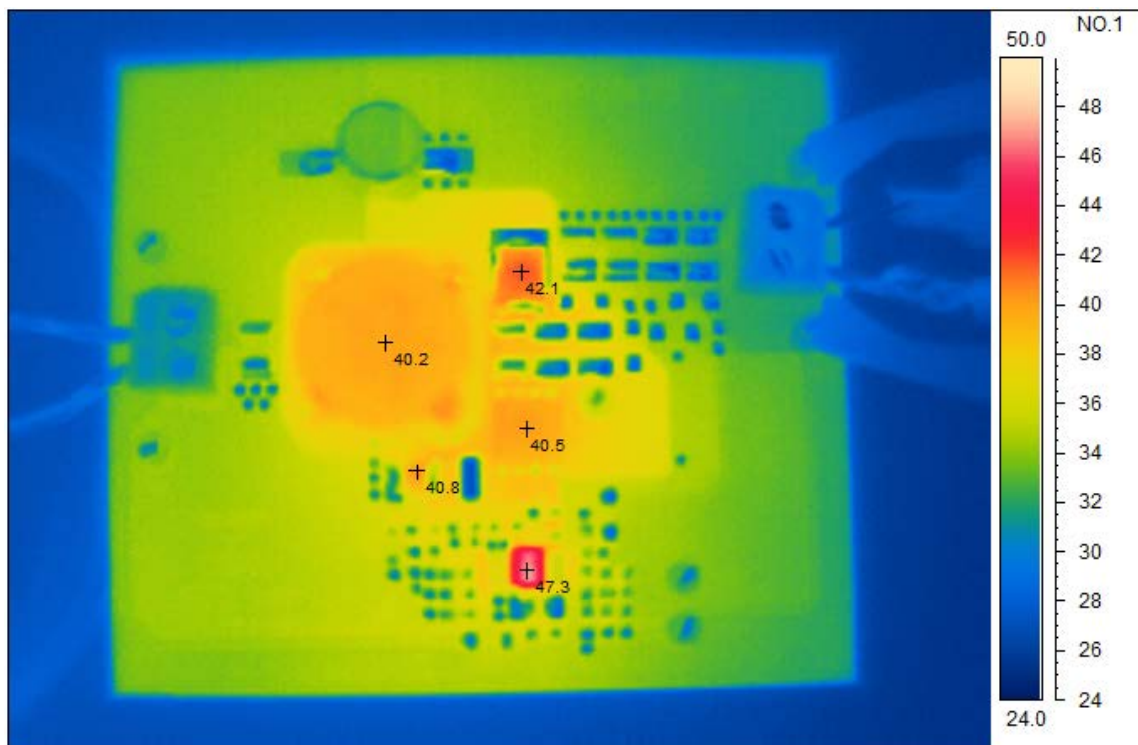A thermal image is shown below with the SEPIC converter operating at 24V input and an 18.9V @ 0.6A output, with no airflow.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated