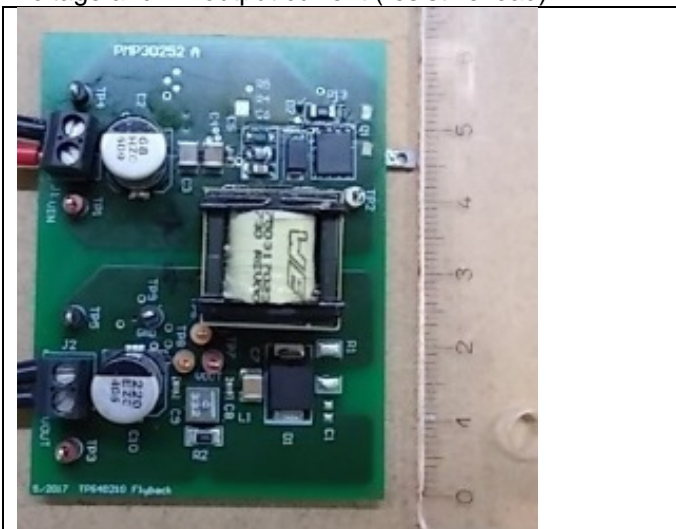


PMP30252RevC Test Results

1	Startup	2
2	Shutdown	2
3	Efficiency	3
4	Loss	3
5	Load Regulation	4
6	Ripple Voltage	5
6.1	Input	5
6.2	Output	5
6.3	Output before Filter	6
7	Control Loop Frequency Response	7
8	Load Transients	8
9	Miscellaneous Waveforms	9
9.1	Switch	9
9.2	Gate to GND	10
9.3	D1	11
10	Thermal Image	12
10.1	Transformer 750317023	12
10.2	Handmade Transformer	12

Topology: DCM Flyback 12W **Device:** TPS40210
 Fsw: typical 130kHz (143kHz at prototype); RevC is same as RevB except:
 commercial transformer T1 750317023 and 100V FET Q1 BSC440N10NS3 G
 For this test report Rev B were reused and efficiency measurements, load regulation and thermal image were redone. Unless otherwise mentioned all measurements were done with 24V input voltage and 1A output current (resistive load).



1 Startup

The startup waveform is shown in the Figure 1. Power supply was connected.

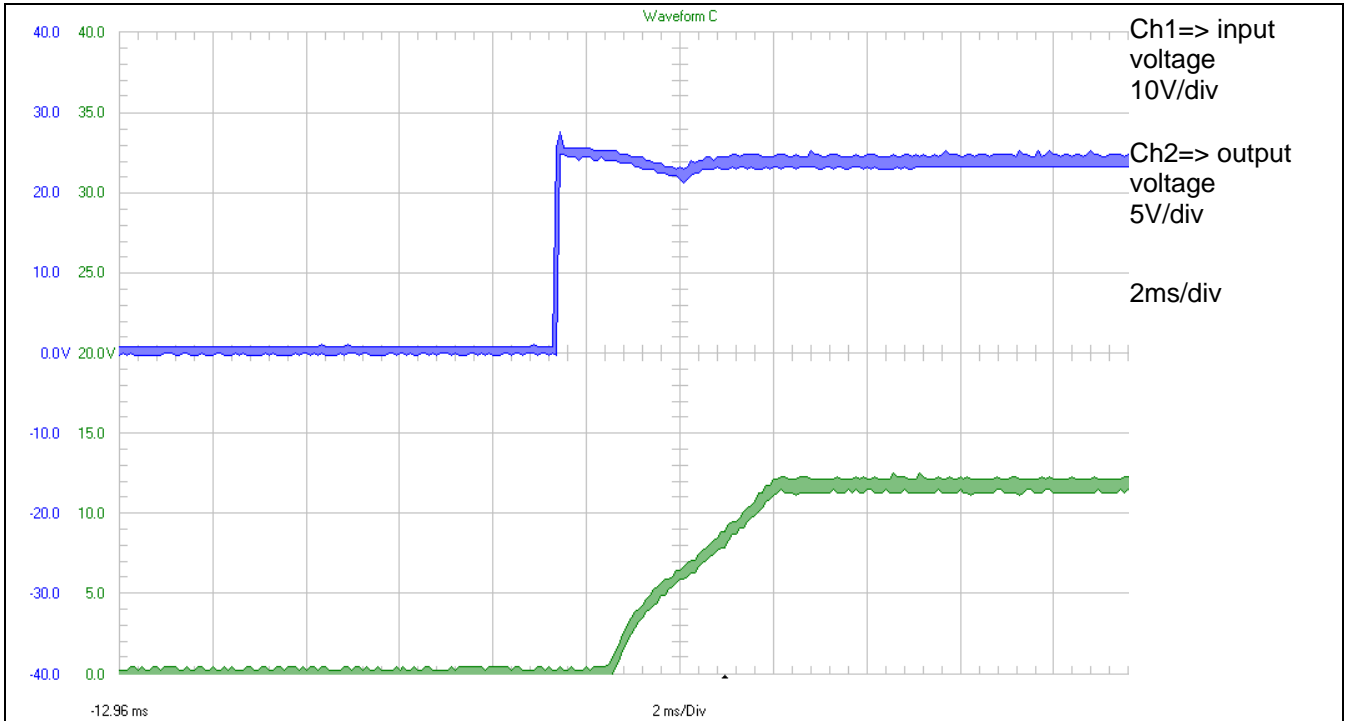


Figure 1

2 Shutdown

The shutdown waveform is shown in the Figure 2. Power supply was disconnected.

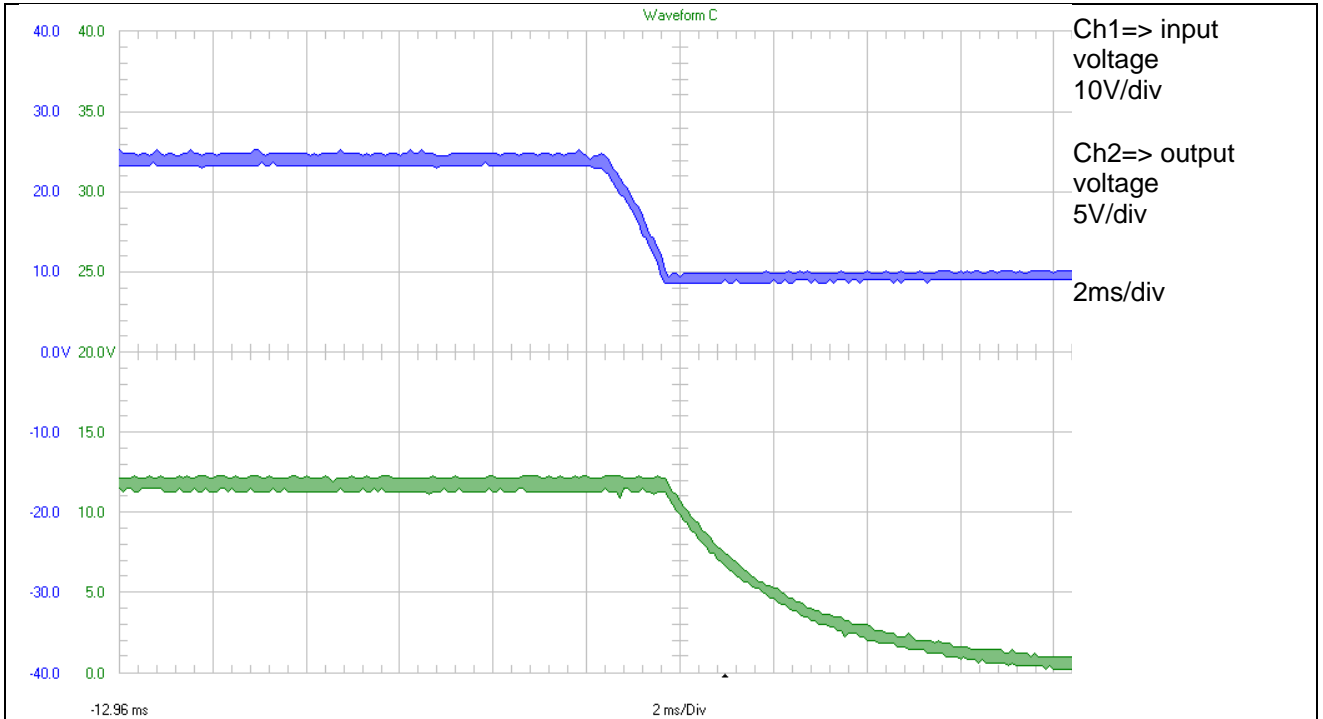


Figure 2

3 Efficiency

The efficiency is shown in the Figure 3 below. The input voltage was set to 24V.

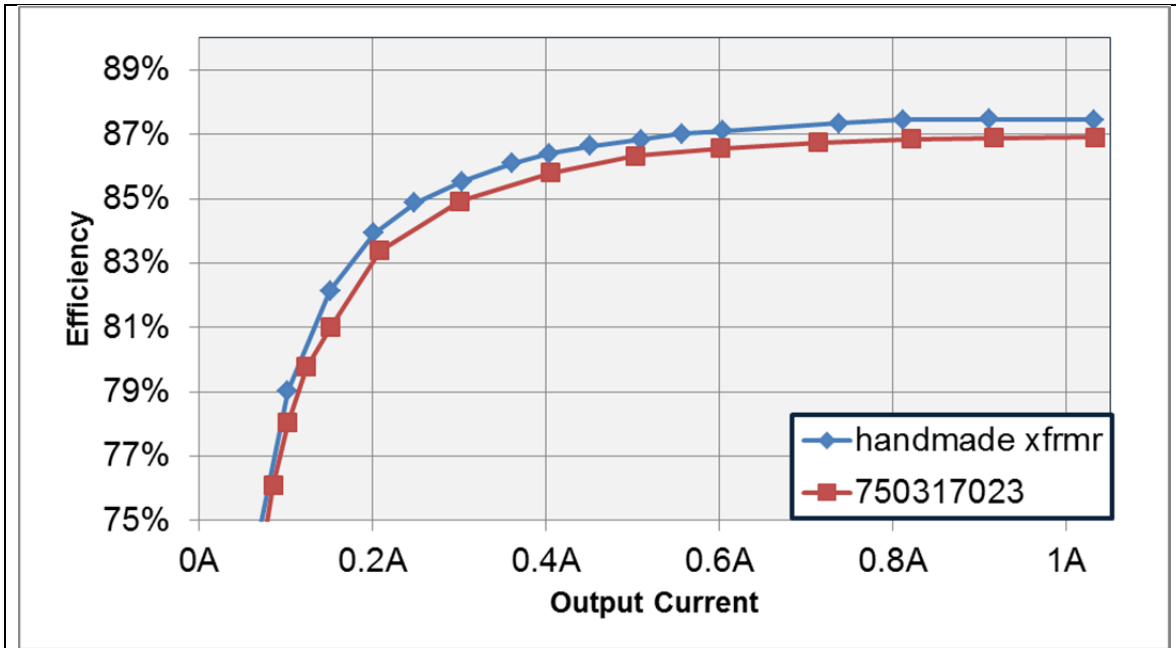


Figure 3

Variable resistor 100R and 1kOhms were used to adjust the output current.

Excellent performance by small commercial WE transformer.

4 Loss

The efficiency is shown in the Figure 4 below. The input voltage was set to 24V.

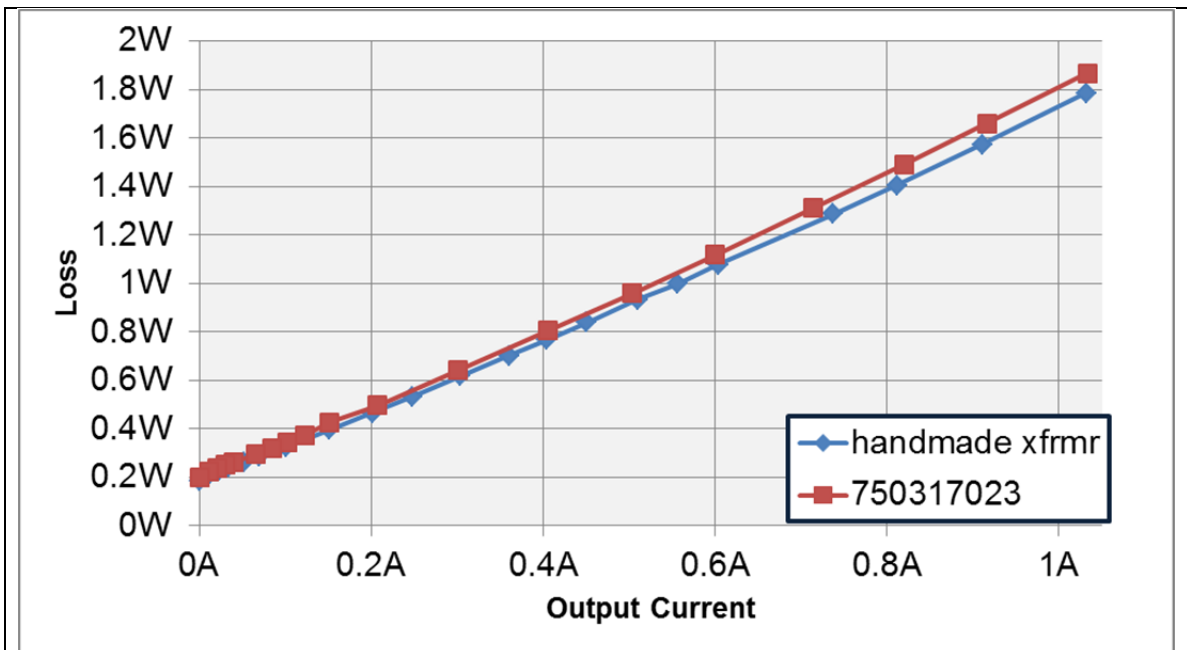


Figure 4

Variable resistor 100R and 1kOhms were used to adjust the output current

5 Load Regulation

The load regulation of the output is shown in the Figure 5 below.

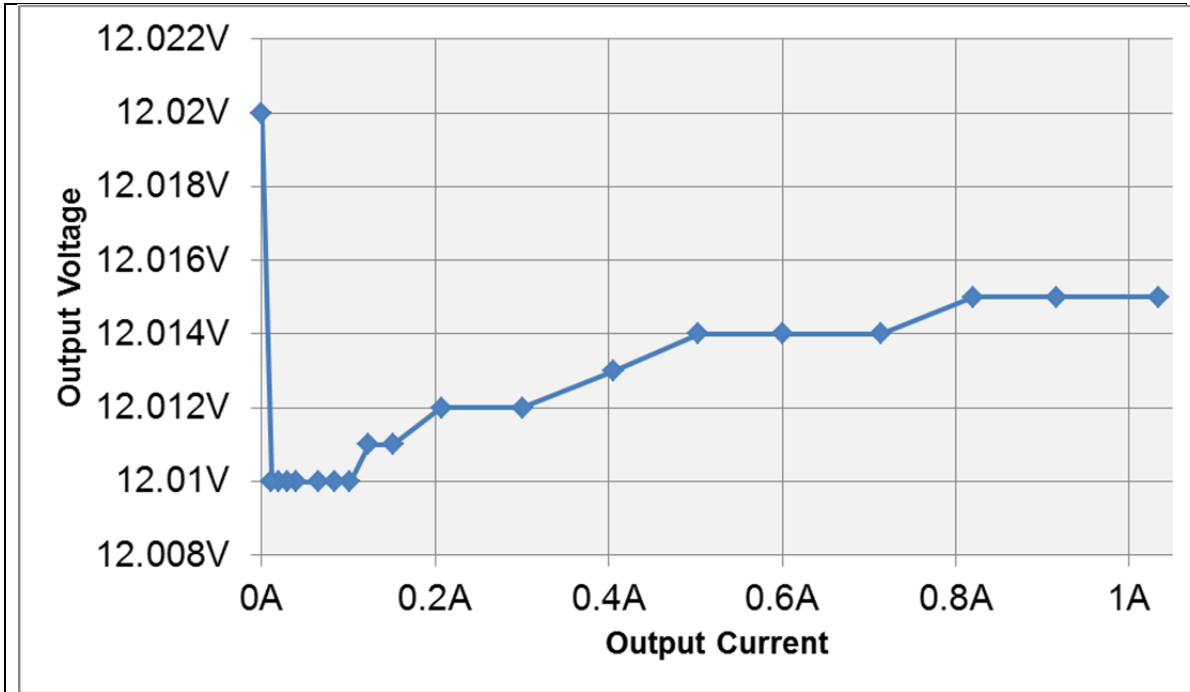


Figure 5

6 Ripple Voltage

6.1 Input

The input ripple voltage is shown in Figure 6.

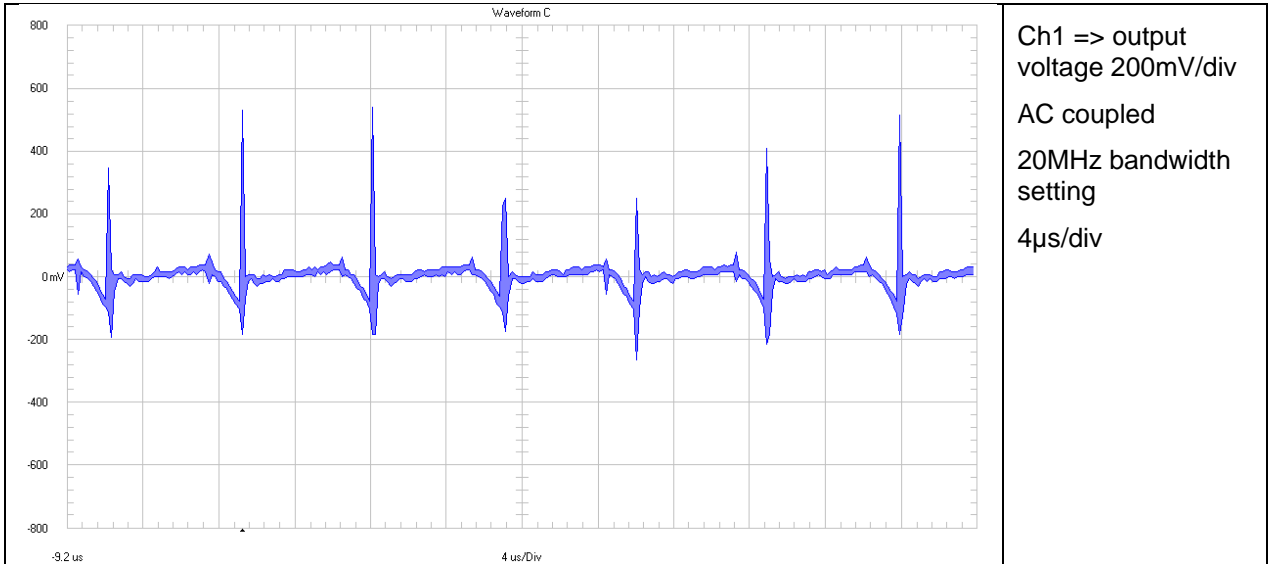


Figure 6

6.2 Output

The output ripple voltage is shown in Figure 7.

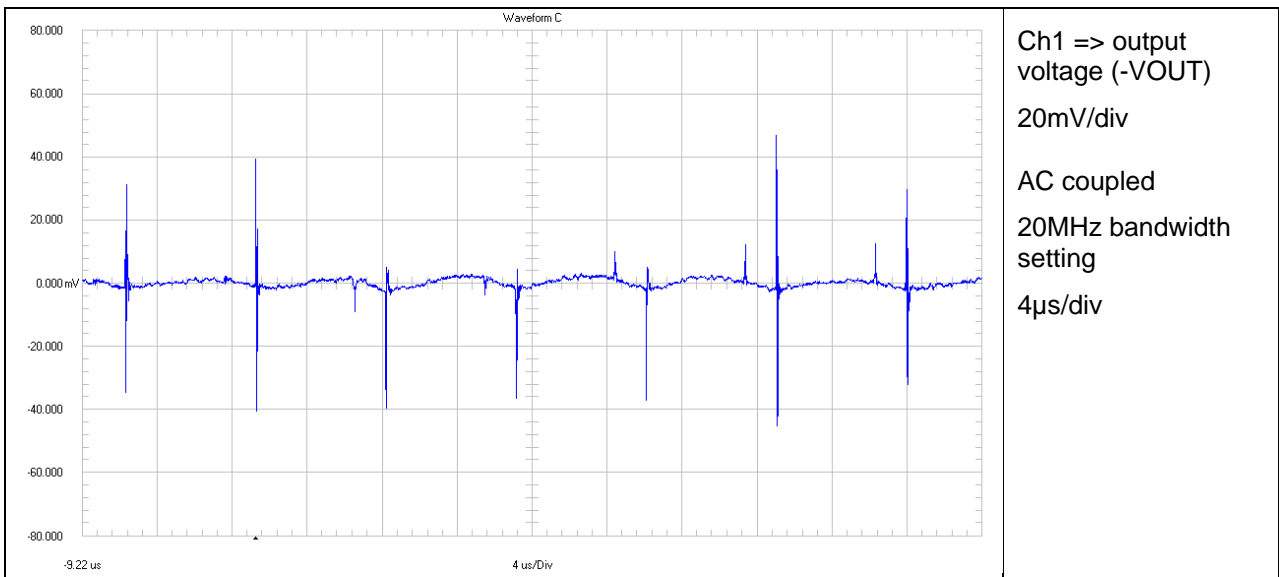


Figure 7

6.3 Output before Filter

The output ripple voltage before filter network is shown in Figure 8.

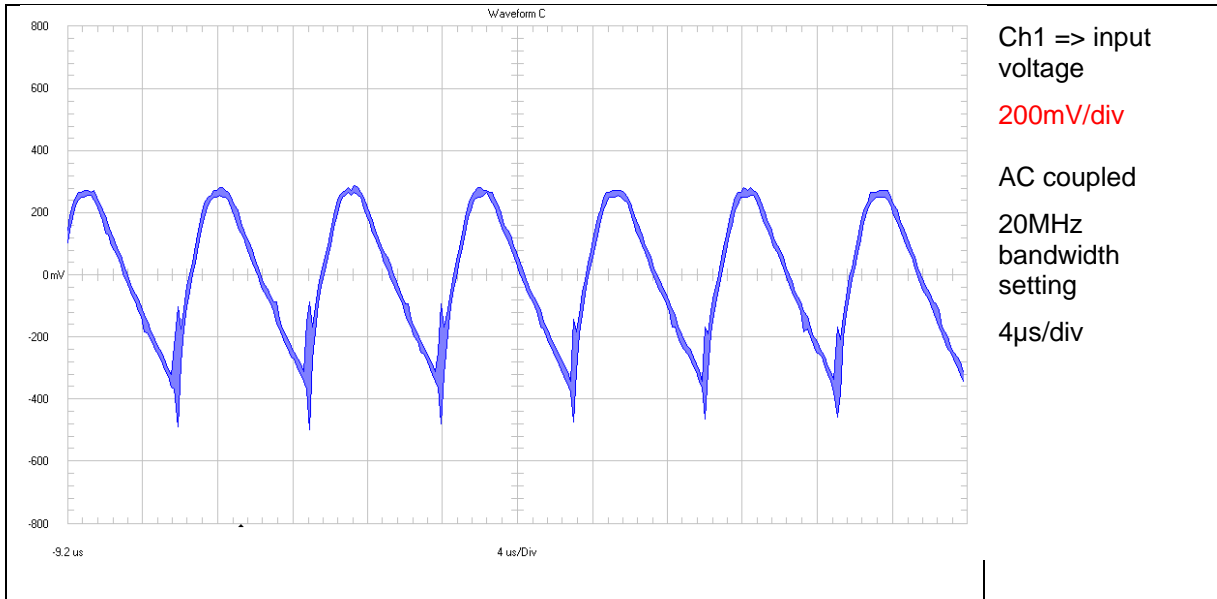


Figure 8

7 Control Loop Frequency Response

Figure 9 shows the loop response with 1A load and 24V input.

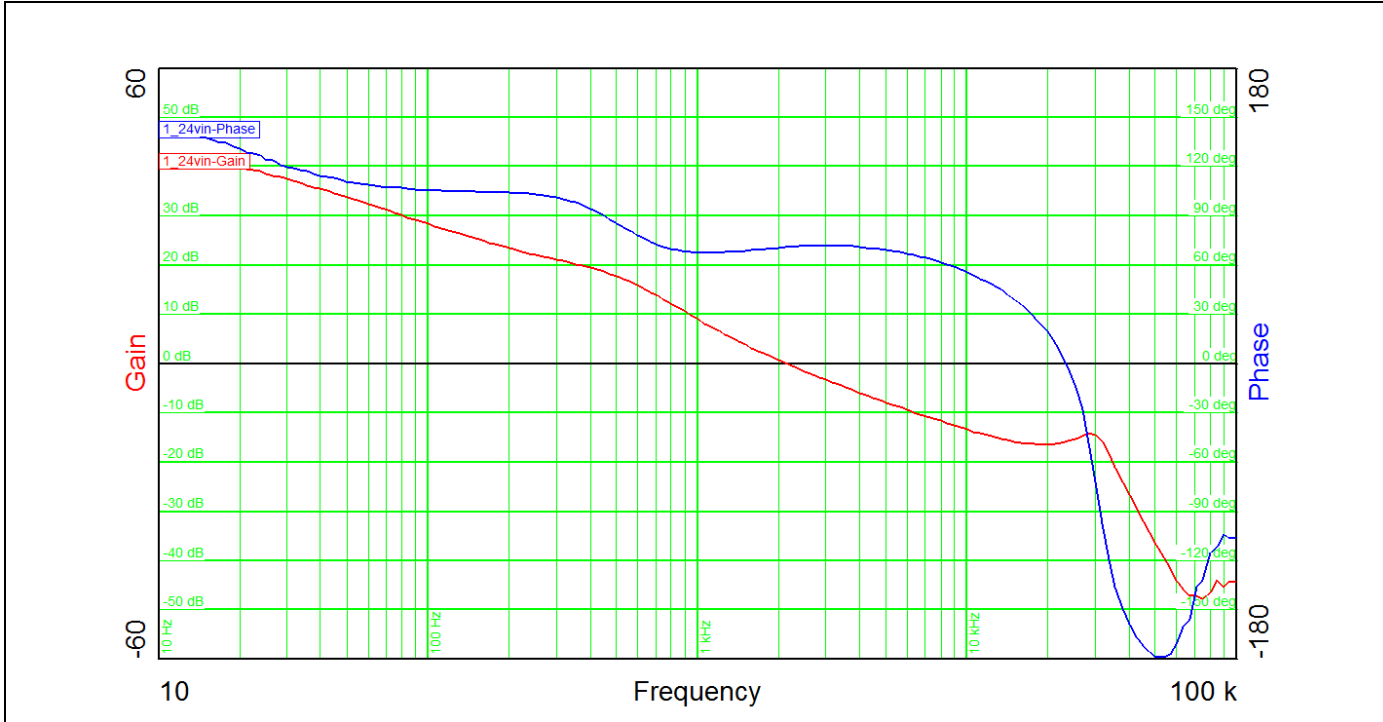


Figure 9

Figure 10 shows the loop response with 1A load and 12V input.

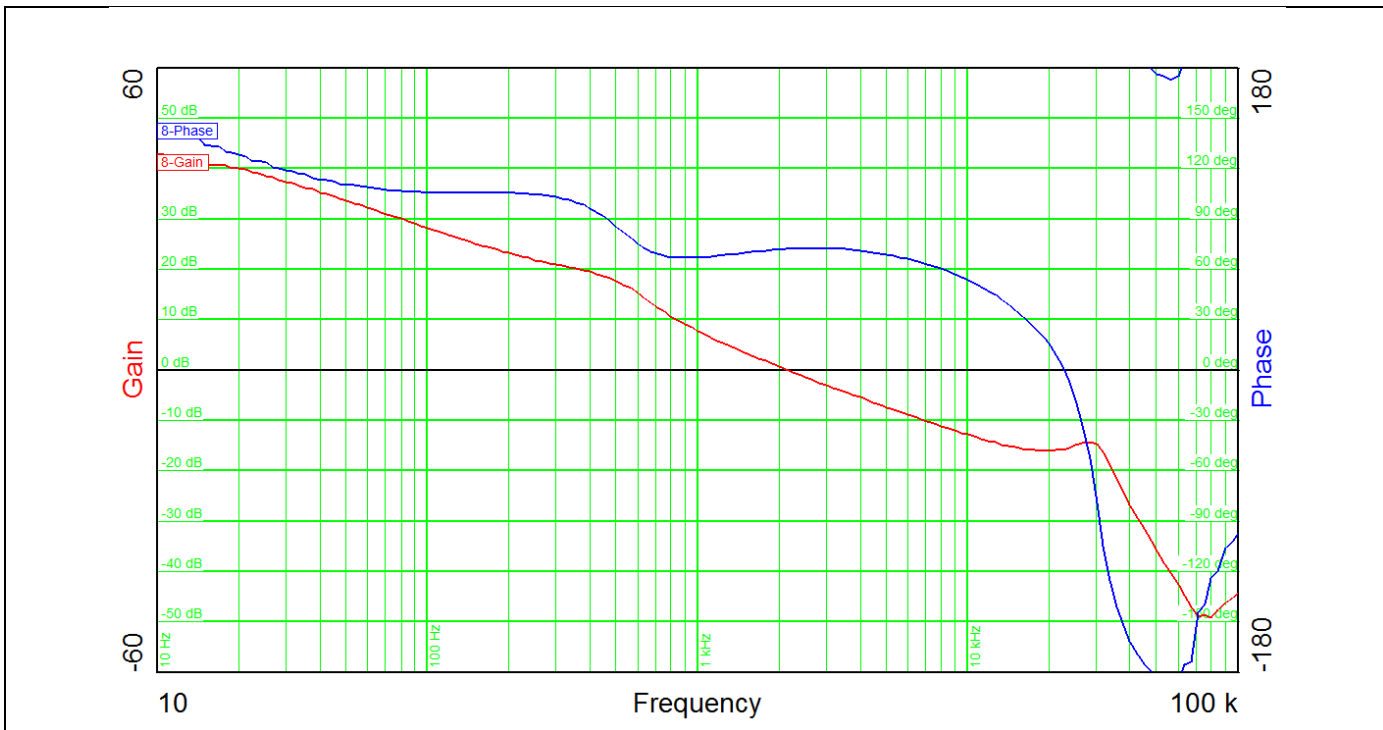


Figure 10

Table 1 summarizes the results:

	24V	12V
Bandwidth (kHz)	2.13	2.15
Phasemargin	70.7°	72°
slope (20dB/decade)	-1.2	-1
gain margin (dB)	-15.8	-15.7
slope (20dB/decade)	-0.74	-0.59
freq (kHz)	23.4	22.8

Table 1

8 Load Transients

The Figure 11 shows the response to load transients. The load is switching from 0.5A to 1A (200 Hz with electronic load 6060B).

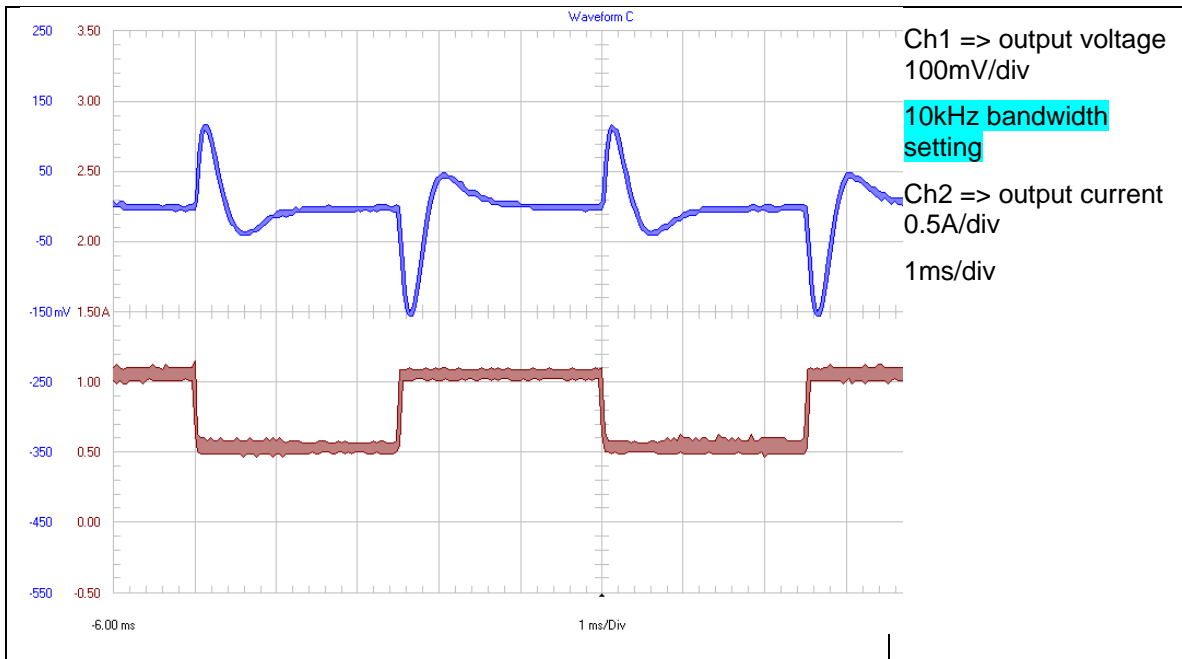


Figure 11

9 Miscellaneous Waveforms

9.1 Switch

Waveform at the switchnode (Q1 to GND) is shown in Figure 12

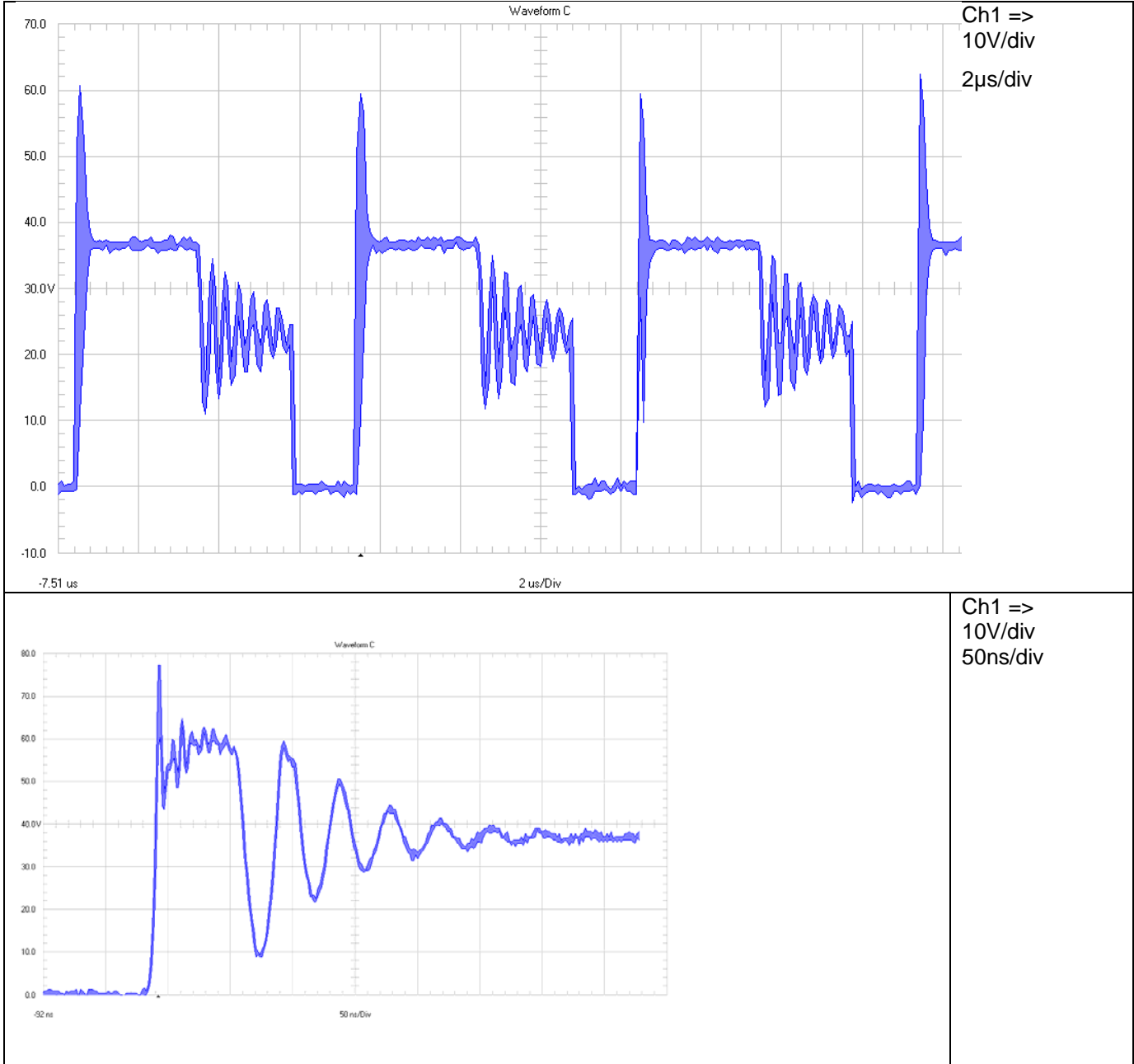


Figure 12

9.2 Gate to GND

Waveform from gate to ground is shown in Figure 13

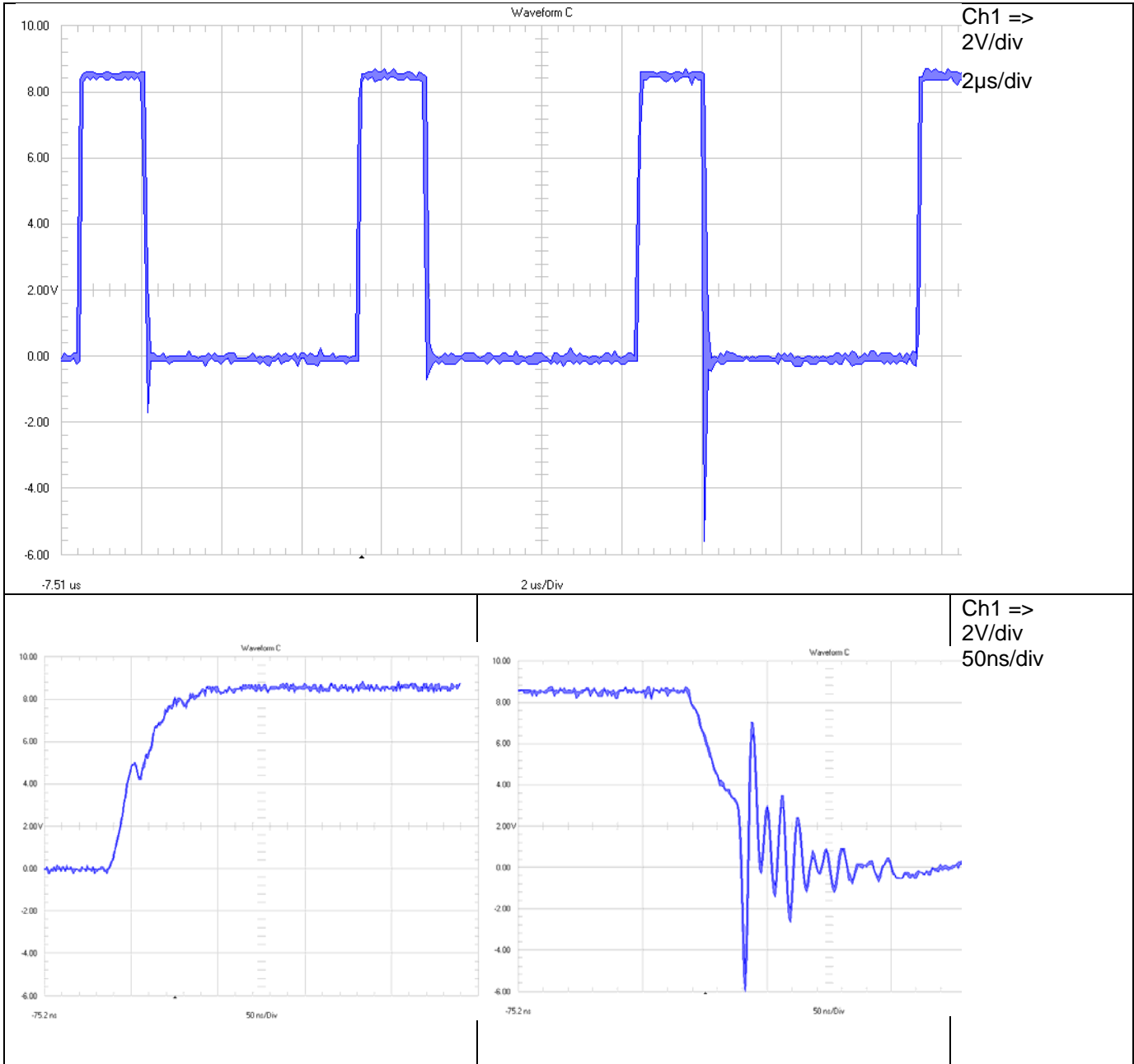


Figure 13

9.3 D1

Waveform at the Diode D1 is shown in Figure 14

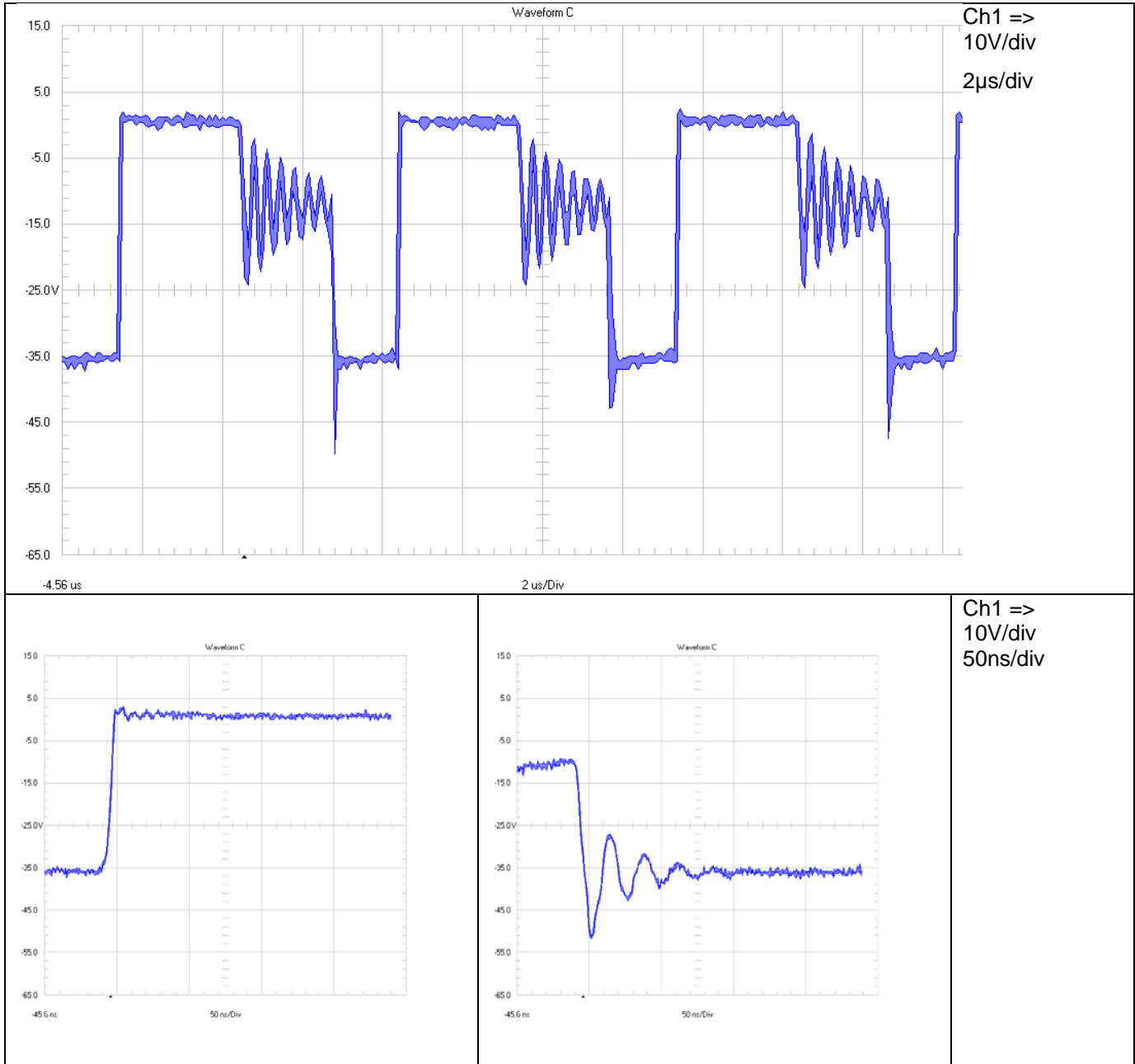


Figure 14

10 Thermal Images at Full Load 1A

10.1 Commercial Transformer WE 750317023 final RevC

Thermal image is shown in Figure 15, 24Vin / 1Aout / >20mins

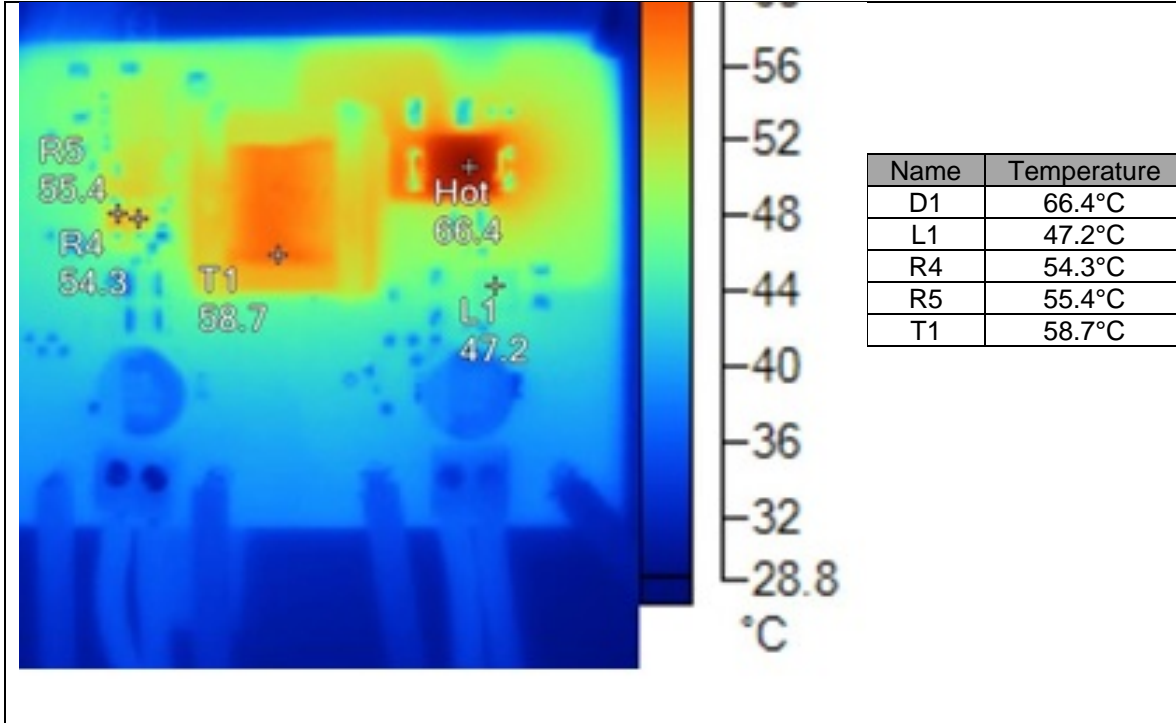


Figure 15, excellent thermal performance by small WE transformer

10.2 Handcrafted Transformer RevB

Thermal image is shown in Figure 16, 24Vin / 1Aout / >20mins

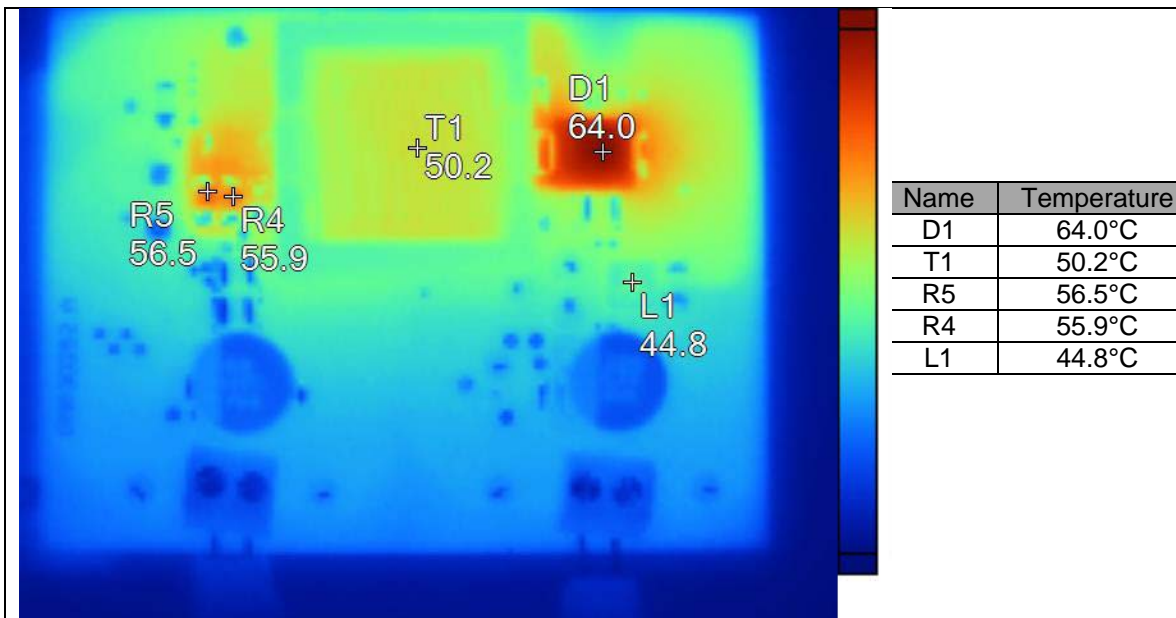


Figure 16

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated