

**Technical Conference Oct 2011**


# **Using Active Clamp Technology to Maximize Efficiency in a Telecom Bus Converter**

**Bernd Geck**

# Agenda


- 1. Basic Operation of Flyback and Forward Converters**
2. Active Clamp Operation and Benefits
3. Active Clamp Forward Design
4. Design Review PMP5711

# Basic Power Stages

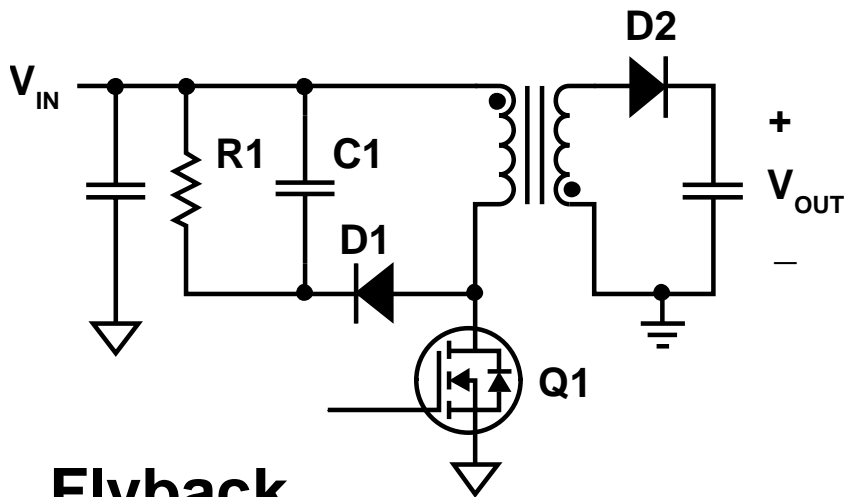
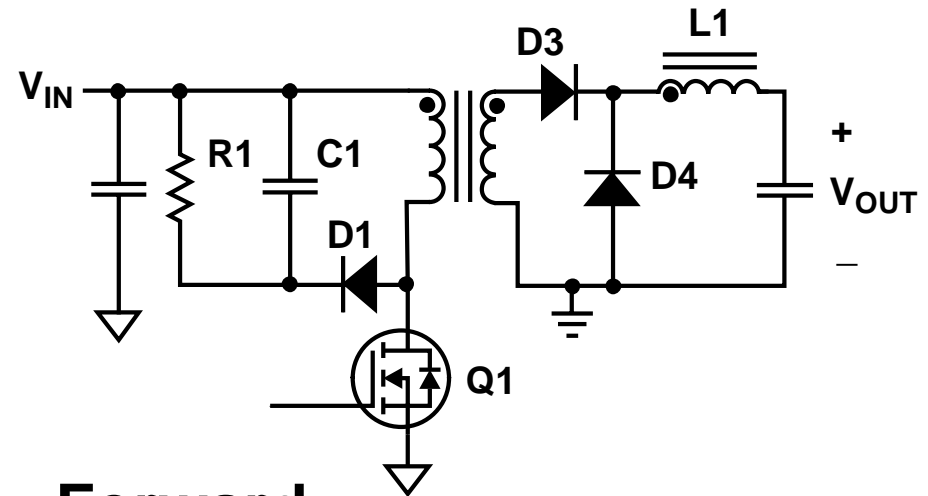
## Flyback

- Transformer stores energy
- R1 dissipates leakage and some magnetizing energy
  - Typically 2 to 5% of output power




## Forward

- Transformer transfers energy
  - Storage is in L1
- R1 dissipates magnetizing plus leakage energy
  - Typically 3 to 10% of output power


How can we avoid loss in R1?

# Secondary Winding Currents

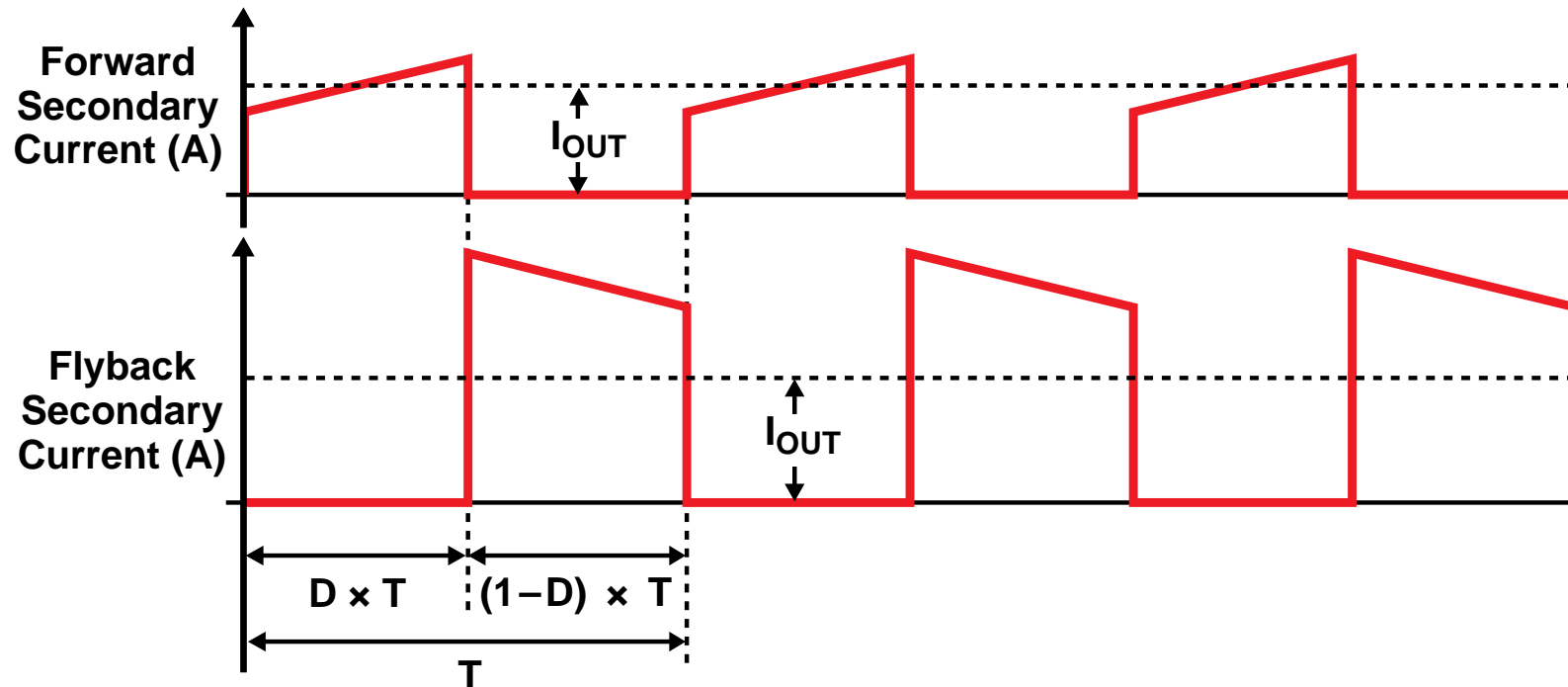

- Assuming 50% duty cycle and CCM
  - Synchronous rectifiers force CCM
- RMS flyback current = 2 X RMS forward current
- For low voltage/high current output, forward is best choice

# Output Capacitor Currents

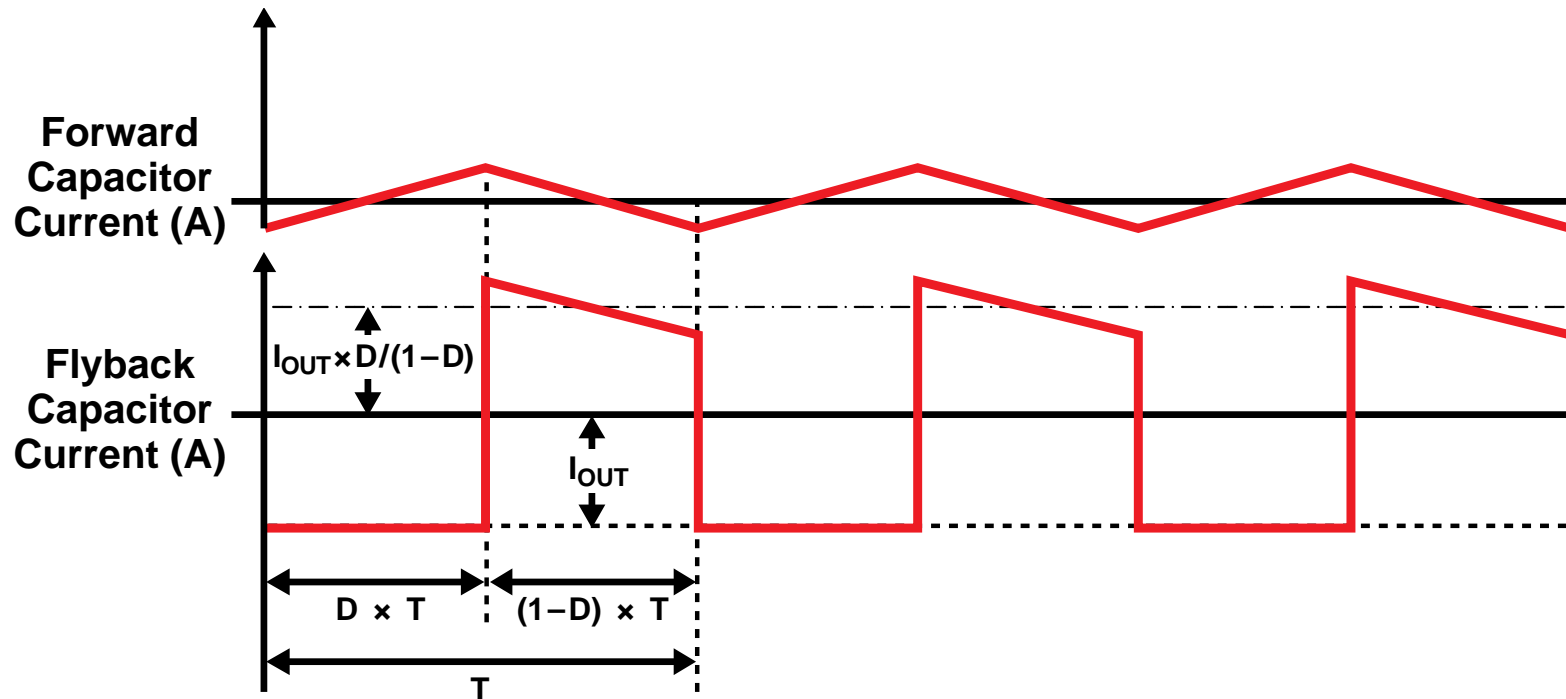


- Flyback output capacitors see much higher current
  - Higher RMS current increases heating
  - Higher peak current requires much lower ESR
- Result is more, higher quality capacitors in flyback


# Agenda

1. Basic Operation of Flyback and Forward Converters
- 2. Active Clamp Operation and Benefits**
3. Active Clamp Forward Design
4. Design Review PMP5711


# Active Clamp Operation

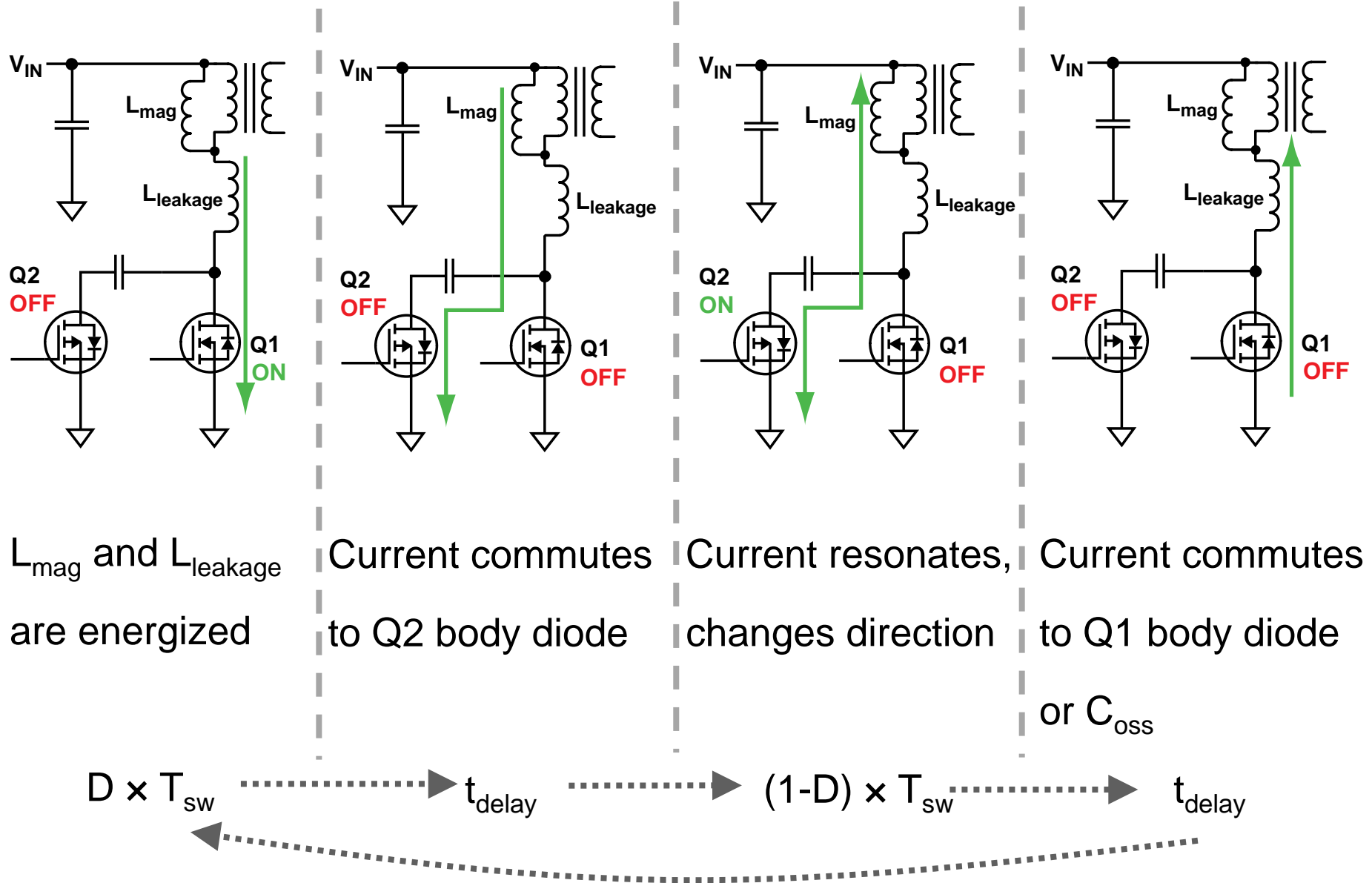

# Active Clamp Configurations

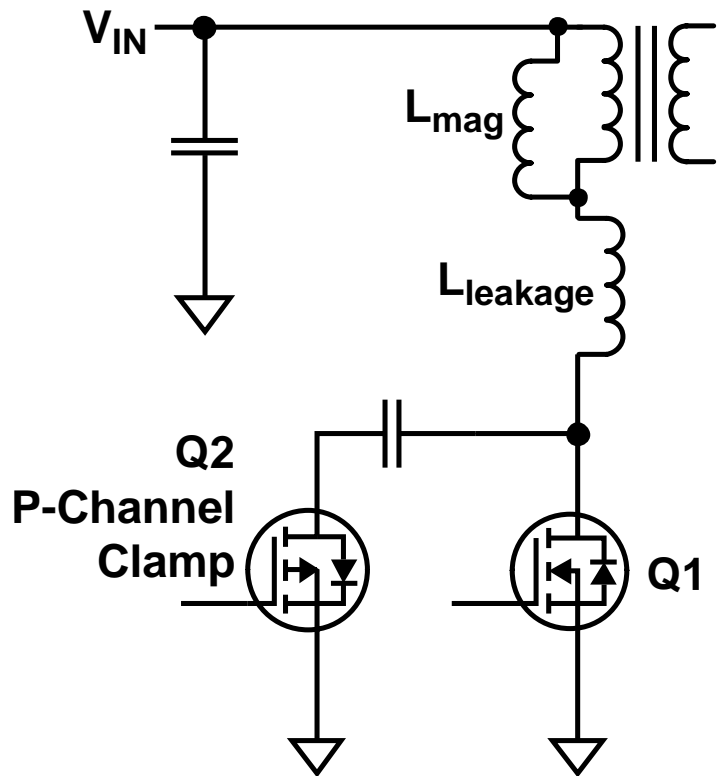

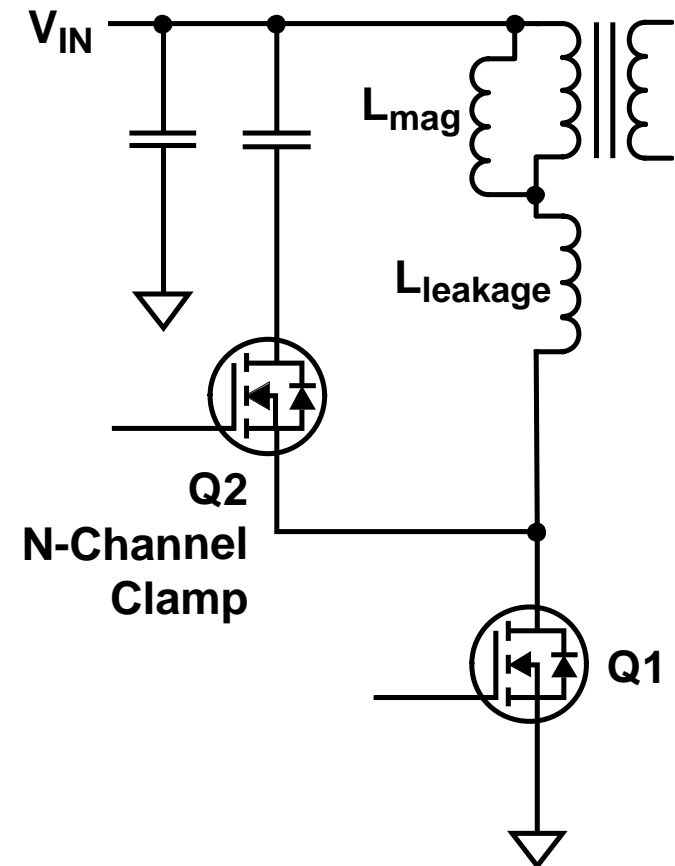- + Easy to drive clamp FET
- Higher capacitor voltage
- P-channel FET



- Floating gate drive
- + Lower capacitor voltage
- + N-channel FET



# Active Clamp Benefits

## RCD Clamp

- Most of leakage energy is dissipated as heat
- “Hard” switching results in power losses
- More difficult implementation of self-driven synchronous rectifiers with Forward
- Voltage spike on Q1 drain at turn off can be EMI issue


## Active Clamp

- Most of leakage energy is reclaimed
- Zero voltage switching reduces losses
- Simple Implementation of self-driven synchronous rectifiers with forward
- No voltage spike on Q1 drain at turn off
- Nearly lossless recovery of magnetizing energy in forward

# Agenda

1. Basic Operation of Flyback and Forward Converters
2. Active Clamp Operation and Benefits
- 3. Active Clamp Forward Design**
4. Design Review PMP5711

# Active Clamp Forward Design

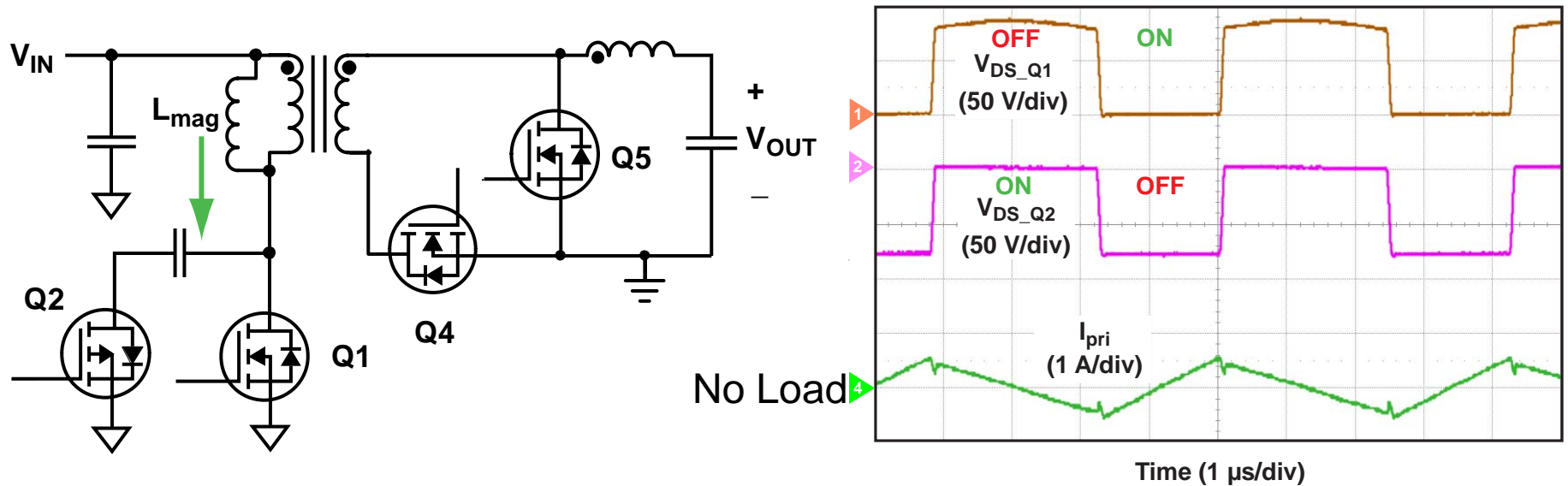

- Reflected primary voltage during reset time allows self driven sync rectifiers
- No leakage spike at  $Q1$  turn off
- Primary current resets to third quadrant resulting in better core utilization
- Unlike flyback, clamp resonant frequency is determined by magnetizing inductance and  $C_{clamp}$

# Forward Clamp Circuit




$$f_{\text{clamp}} = \frac{1}{2 \times \pi \times \sqrt{L_{\text{magnetizing}} \times C_{\text{clamp}}}}$$

$$V_{\text{hump}} = \frac{V_{\text{in}} \times D \times (1 - D)}{8 \times L_{\text{magnetizing}} \times f_{\text{SW}}^2 \times C_{\text{clamp}}}$$

$$I_{\text{Q2\_RMS}} = \frac{V_{\text{in}} \times D \times \sqrt{1 - D}}{2 \times \sqrt{3} \times L_{\text{magnetizing}} \times f_{\text{sw}}}$$

(Peak current is  $I_{\text{mag}}$ ;  
RMS clamp current is  
much less than flyback)



# Forward Soft Switching – Q1 Turn-Off

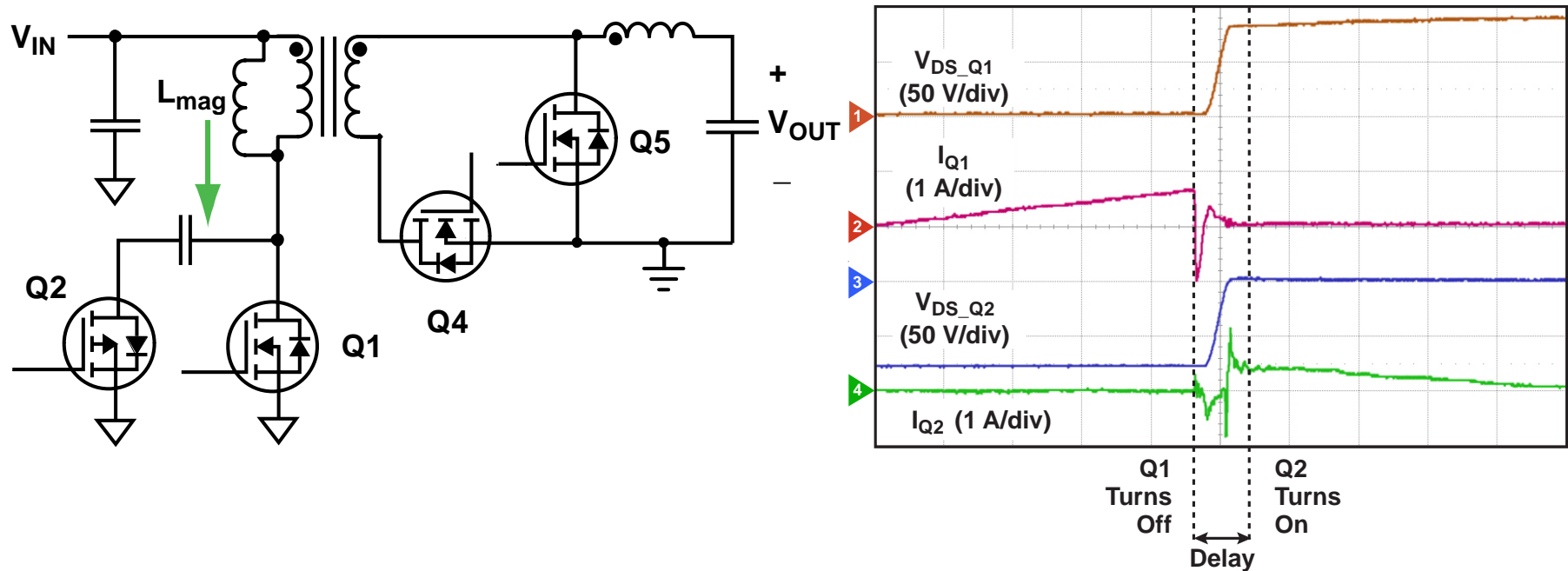

- Magnetizing and reflected load current flowing in Q1
- Transfers to Q2 body diode
  - Delay from Q1 turn-off to Q2 turn-on
- Zero voltage switching of Q2
- Not load or line dependent

# Forward Soft Switching – Q1 Turn-On


## Light Loads

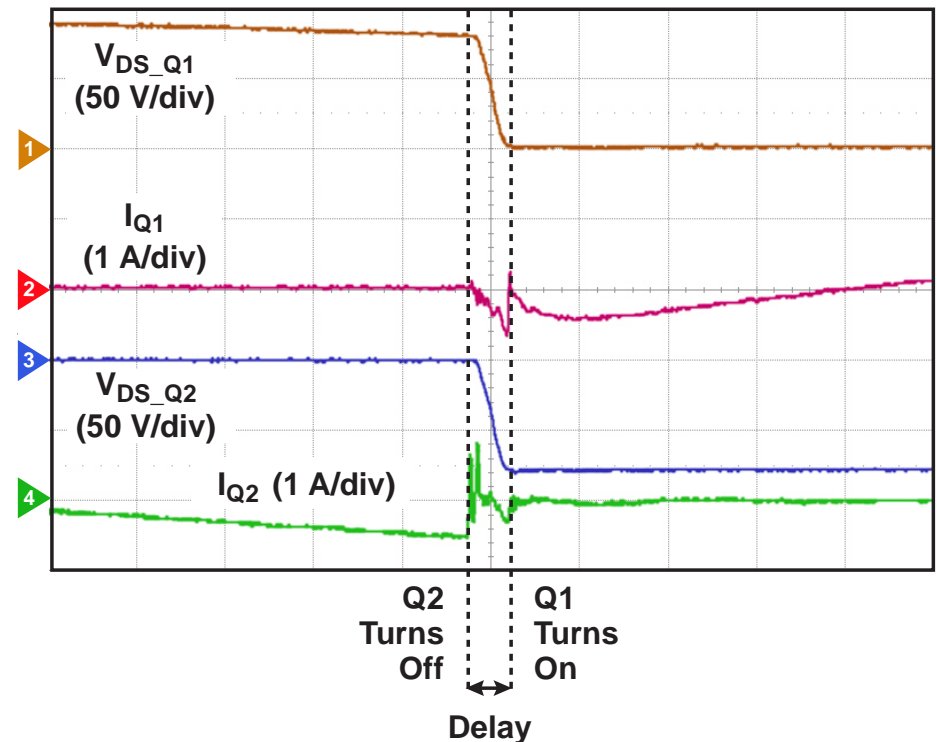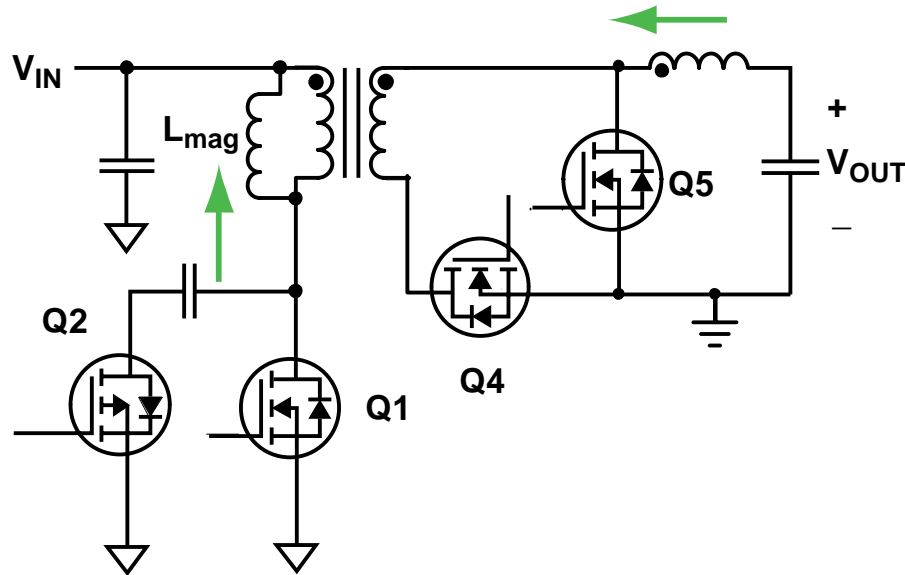

- No current in  $Q4$  or  $Q5$  during delay time
- Allows  $Q1$  to achieve ZVS

# Forward Soft Switching – Q1 Turn-On

## Heavy Loads

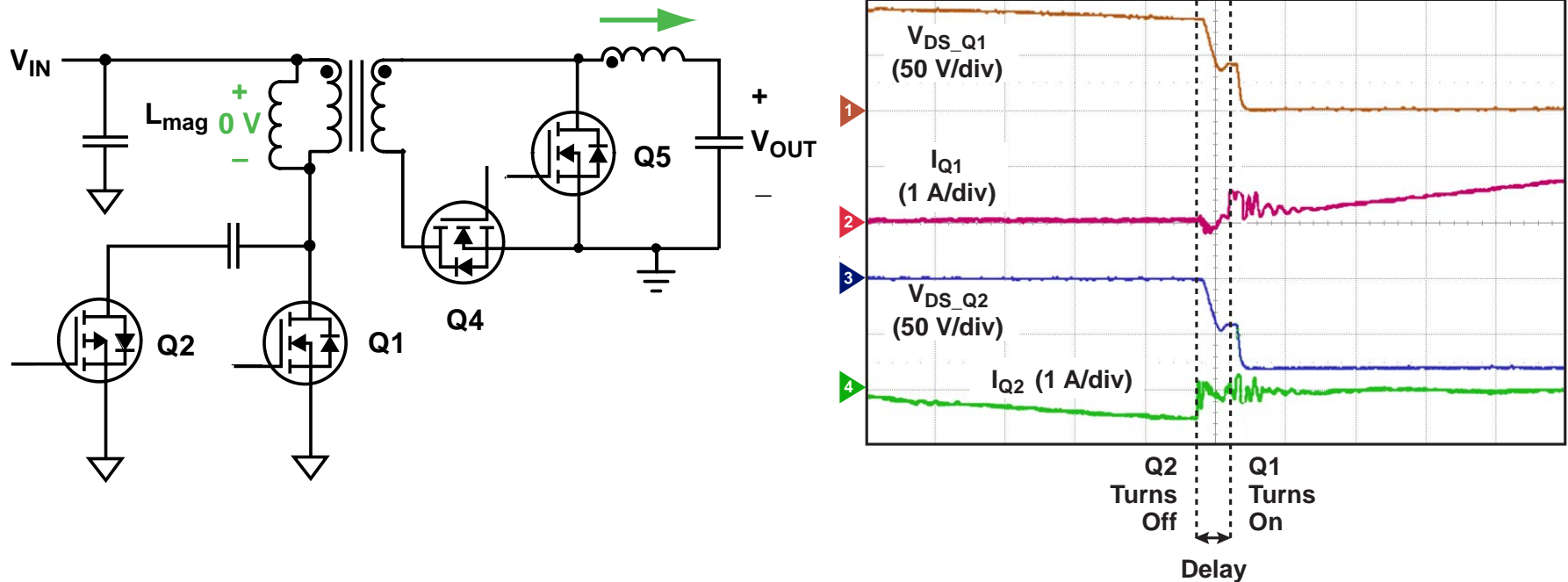


- Current flows in body diodes of Q4 and Q5 during delay time
- Q1 drain voltage =  $V_{IN}$  when Q1 turns On
- Partial zero voltage switching

# Forward Synchronous Rectifiers

Output Voltage	PRI:SEC Turn Ratio	MAX Sync FET $V_{DS}$ Stress	Sync FET $V_{DS}$ Rating
3.3 V	6:1	12.5 V	20 V
5 V	4.5:1	17 V	30 V
12 V	1.88:1	40 V	60 V

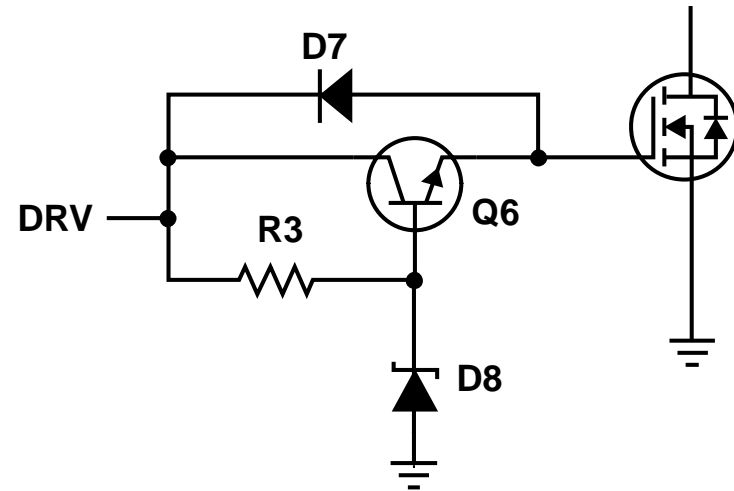- Turn ratios and voltages for telecom 35- to 75-VDC input
- FET gate rating of 20 V or less
- 3.3-V output can be driven directly from transformer winding
- Outputs >3.3 V require gate protection






# Agenda


1. Basic Operation of Flyback and Forward Converters
2. Active Clamp Operation and Benefits
3. Active Clamp Forward Design
- 4. Design Review PMP5711**
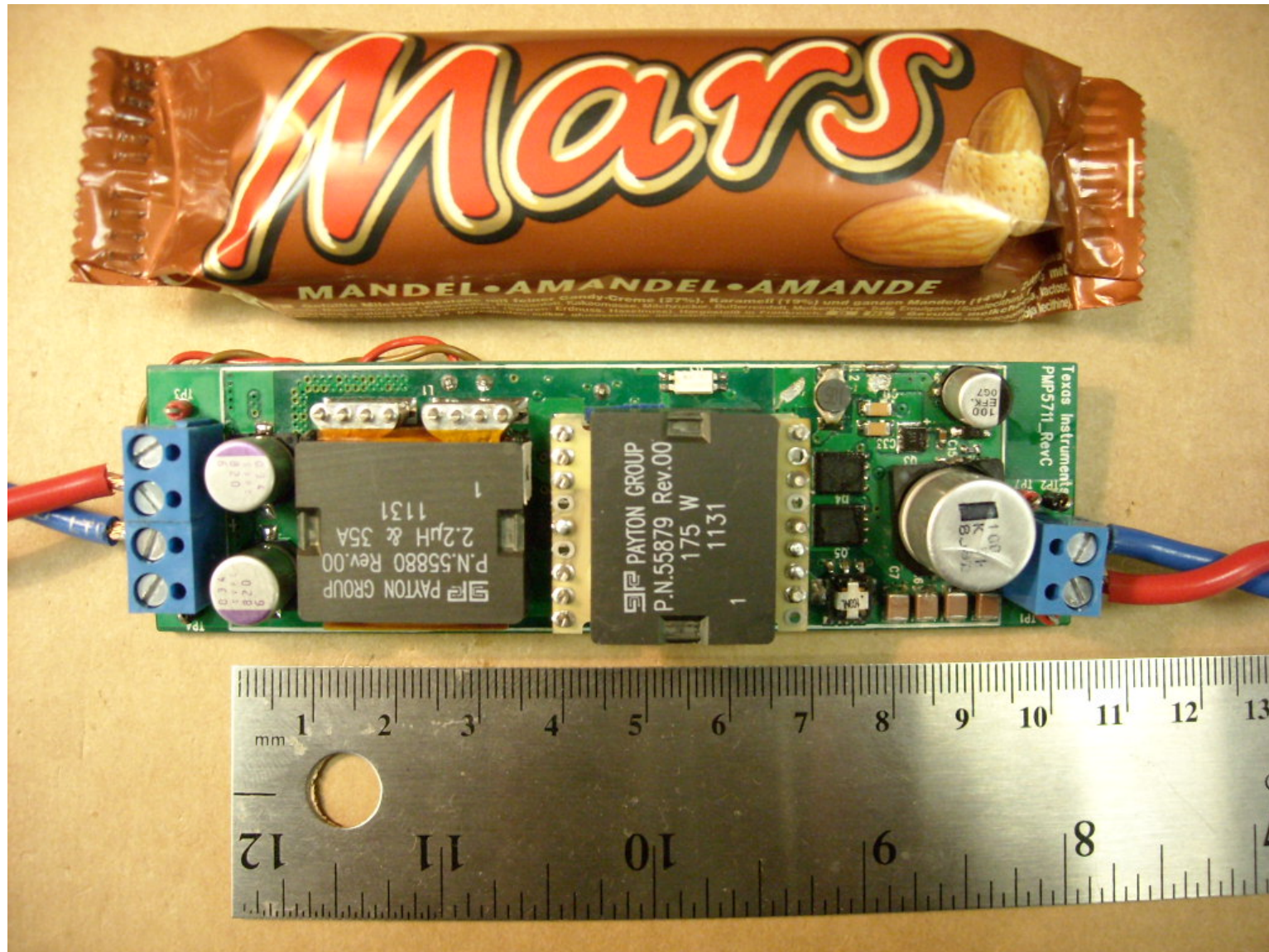
# Physical Size – 5.0V/35A Forward Converter




$L \times W \times H = 93\text{mm} \times 31\text{mm} \times 19\text{mm}$


# Waveforms – 5.0V/35A Forward Converter

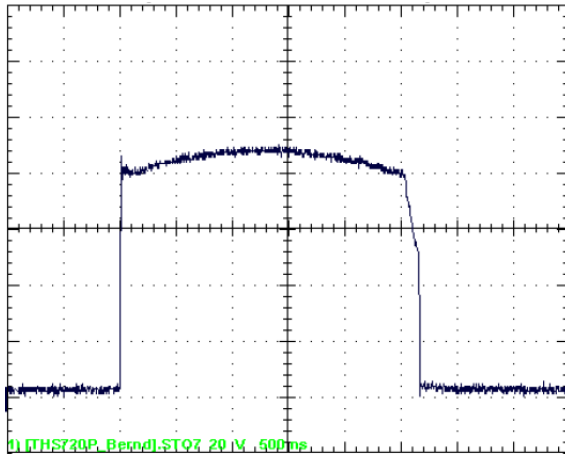


Vds primary NFETs

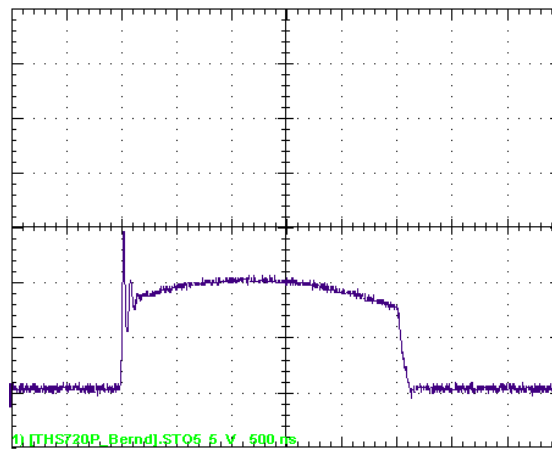


Vds sync. rectifiers

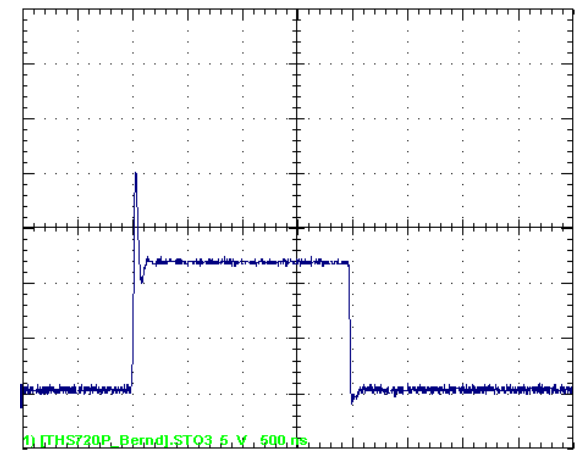


Vds freewheeling FET

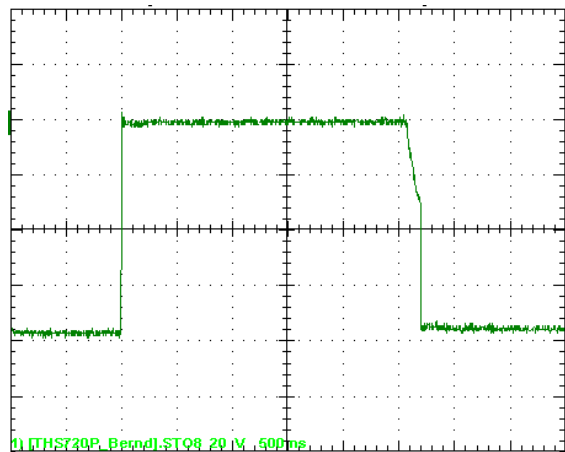

Vds clamping PFET

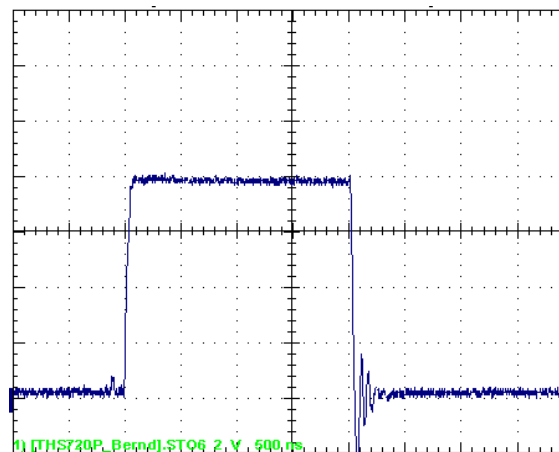


Vgs sync. rectifiers

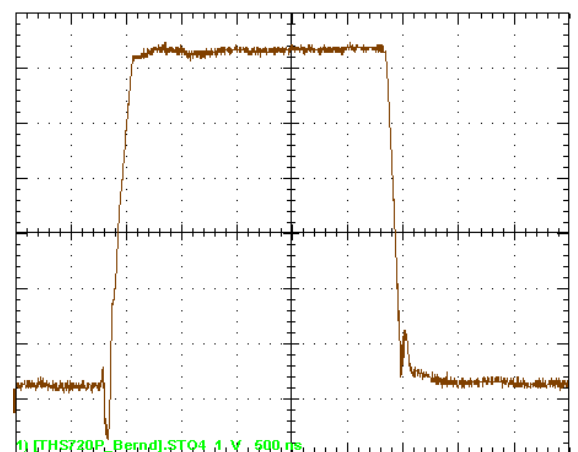


Vgs freewheeling FET
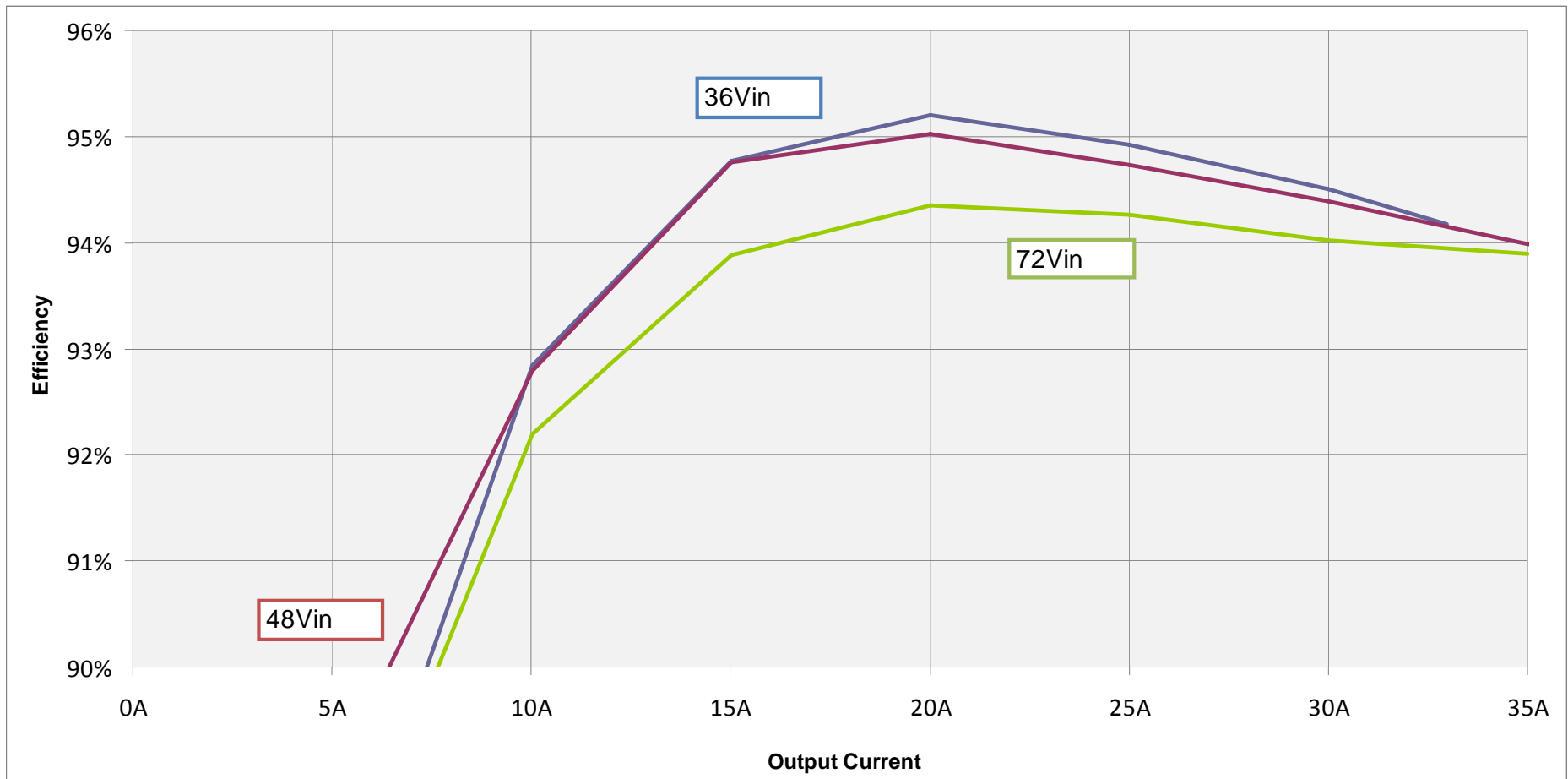
# Efficiency – 5.0V/35A Forward Converter




effcy > 94% in a range of 13A to 35A, 95% around 20A
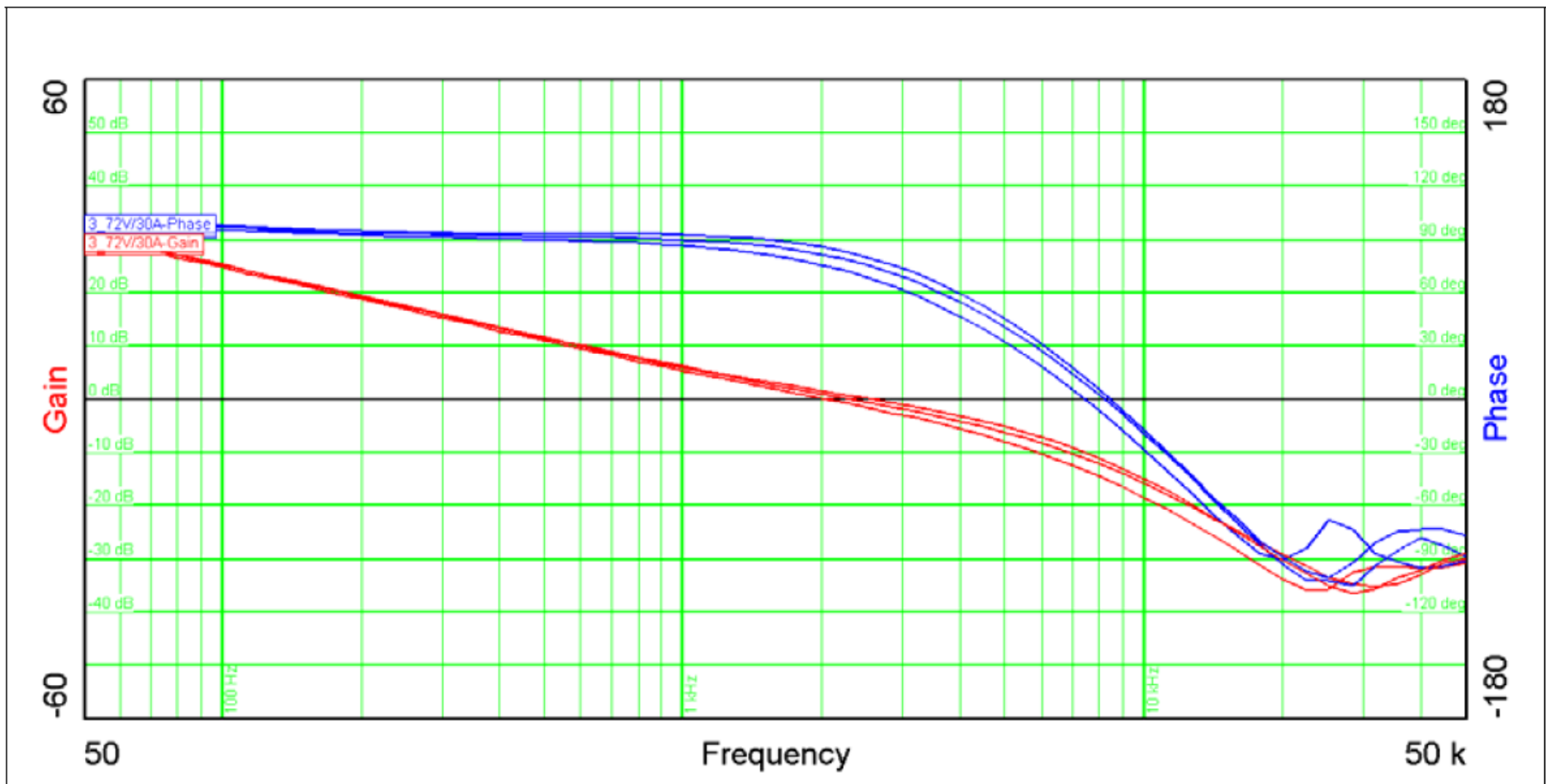
# Dynamic Behavior – 5.0V/35A Forward Conv.




small signal analysis of outer loop w/ network analyzer at 30Amps load, results in:  
bandwidth > 2kHz, phasemargin >70degs, gain margin <-12dB
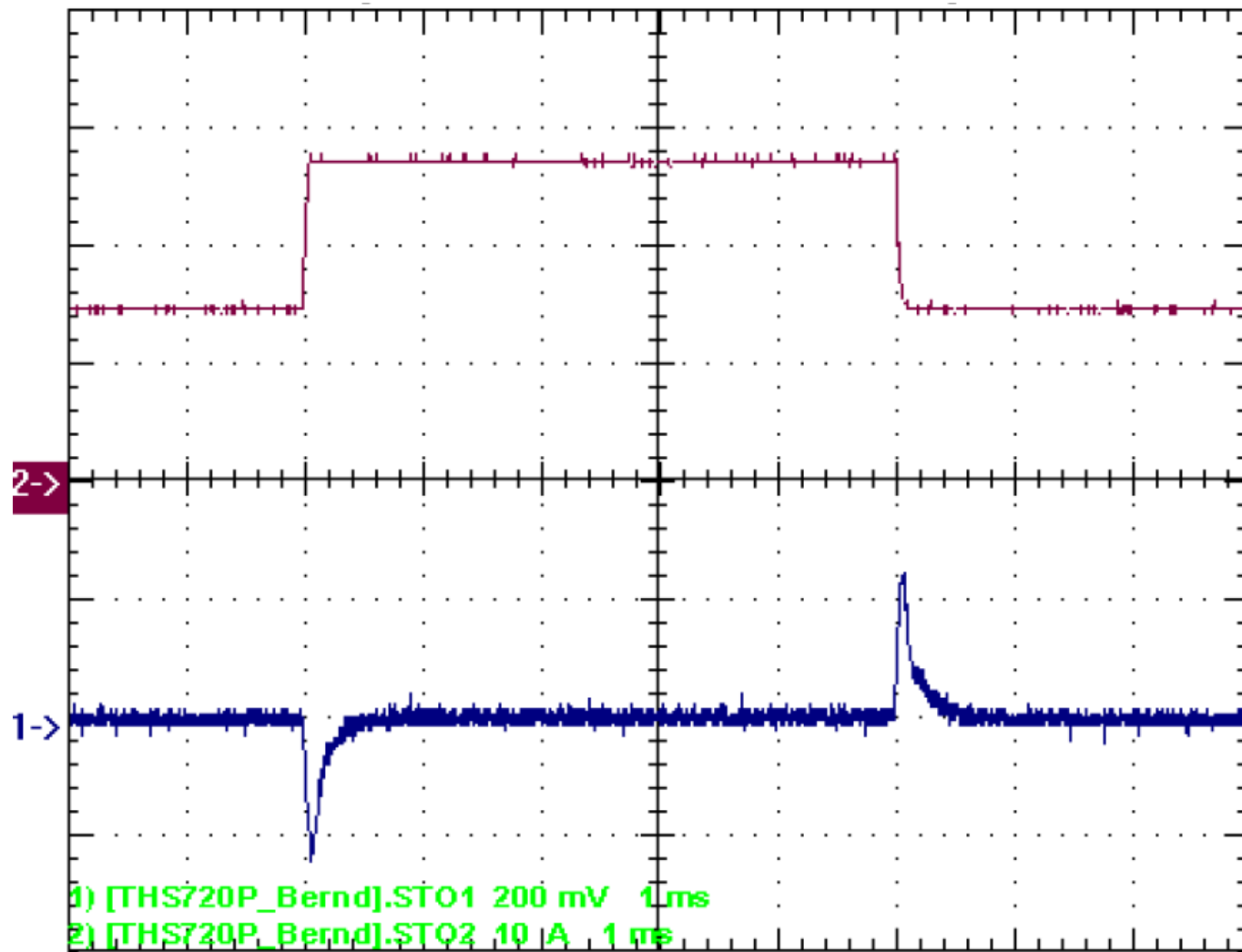
# Dynamic Behavior – 5.0V/35A Forward Conv.



large signal analysis with load step 50%, 15Amps / 30Amps

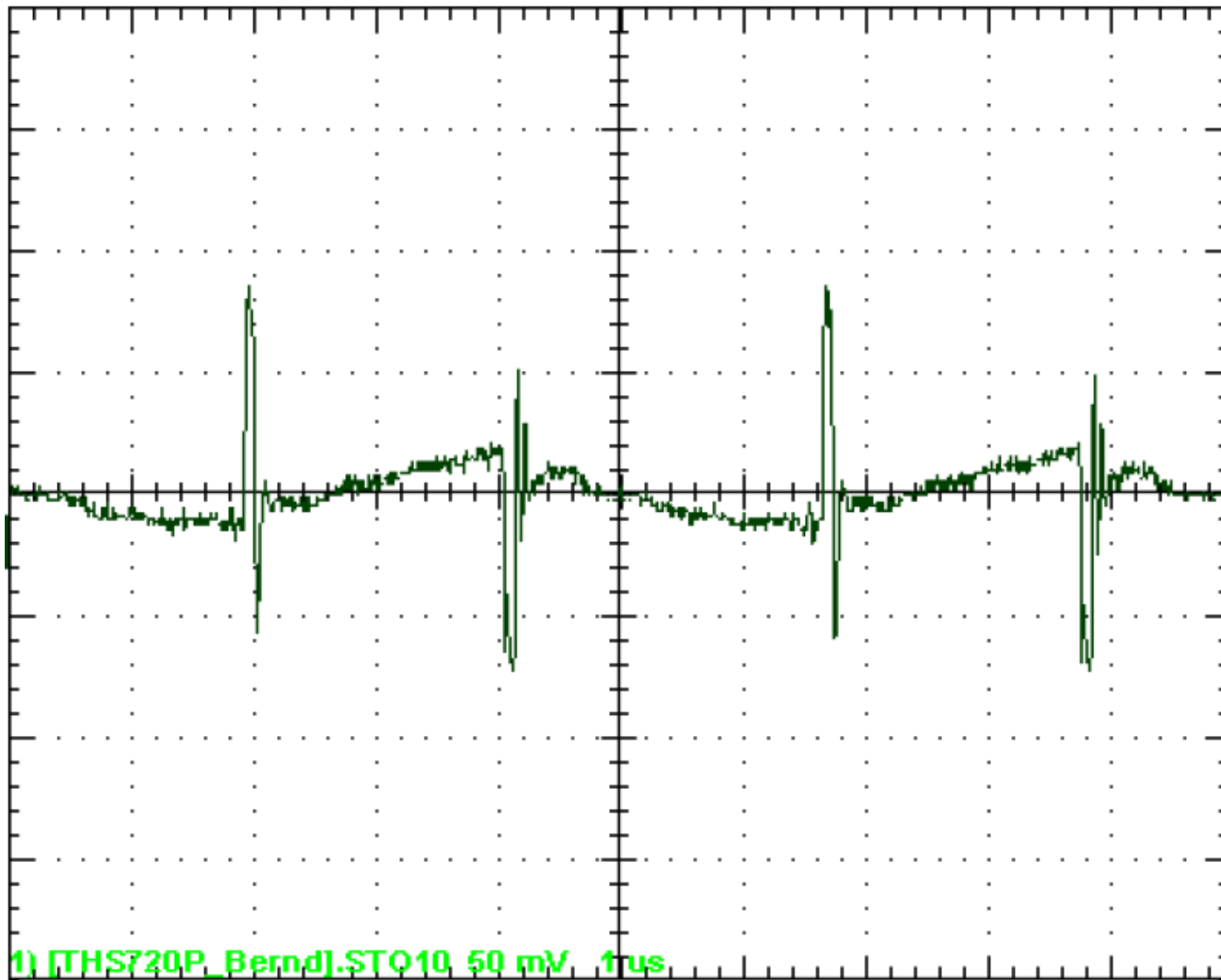
# Ripple & Noise – 5.0V/35A Forward Conv.



ripple 40mVpp, noise 110mVp at max. load 35Amps



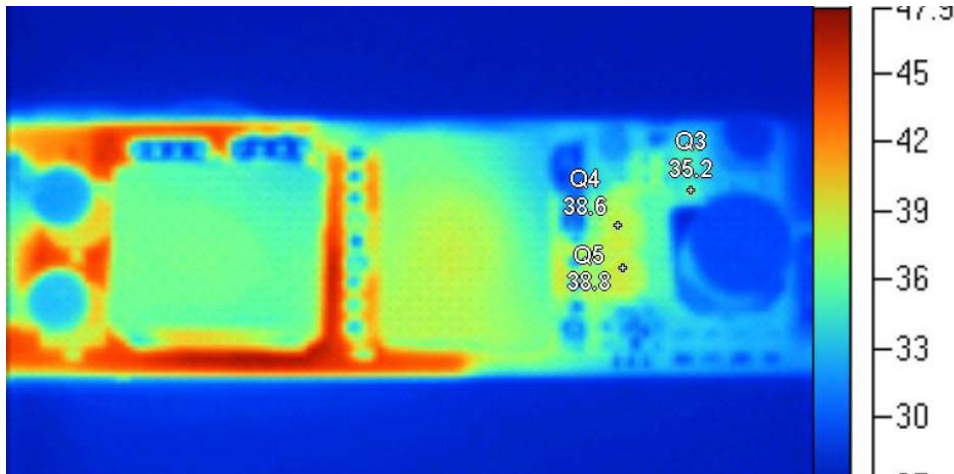
# Thermal Behavior – 5.0V/35A Forward Conv.



Name	Temperature
Q5	38.8°C
Q4	38.6°C
Q3	35.2°C

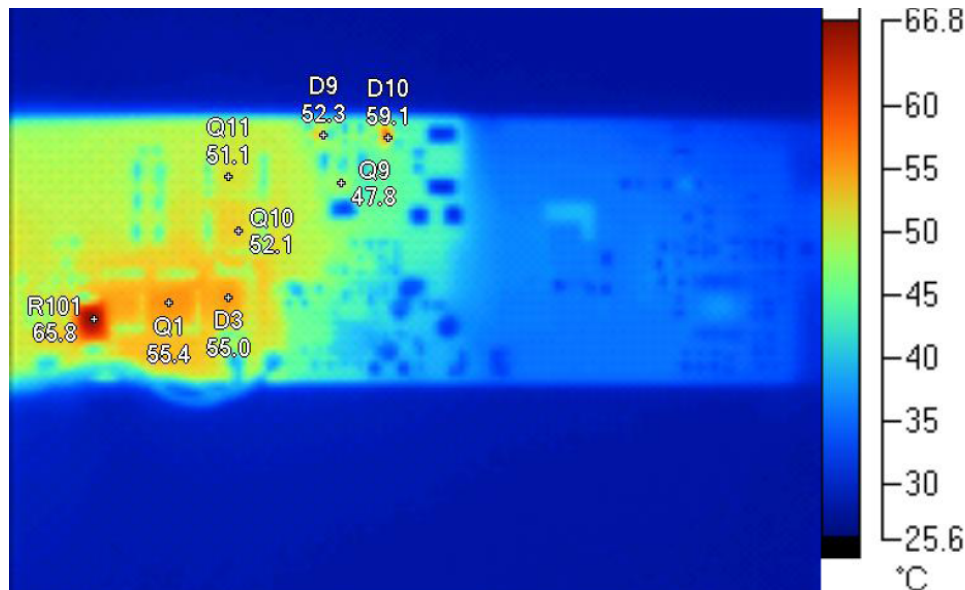top side at max. load 35A  
at forced cooling 400l/m




Name	Temperature
R101	65.8°C
D10	59.1°C
D9	52.3°C
Q1	55.4°C
D3	55.0°C
Q9	47.8°C
Q10	52.1°C
Q11	51.1°C

bottom side at max. load 35A  
at forced cooling 400l/m


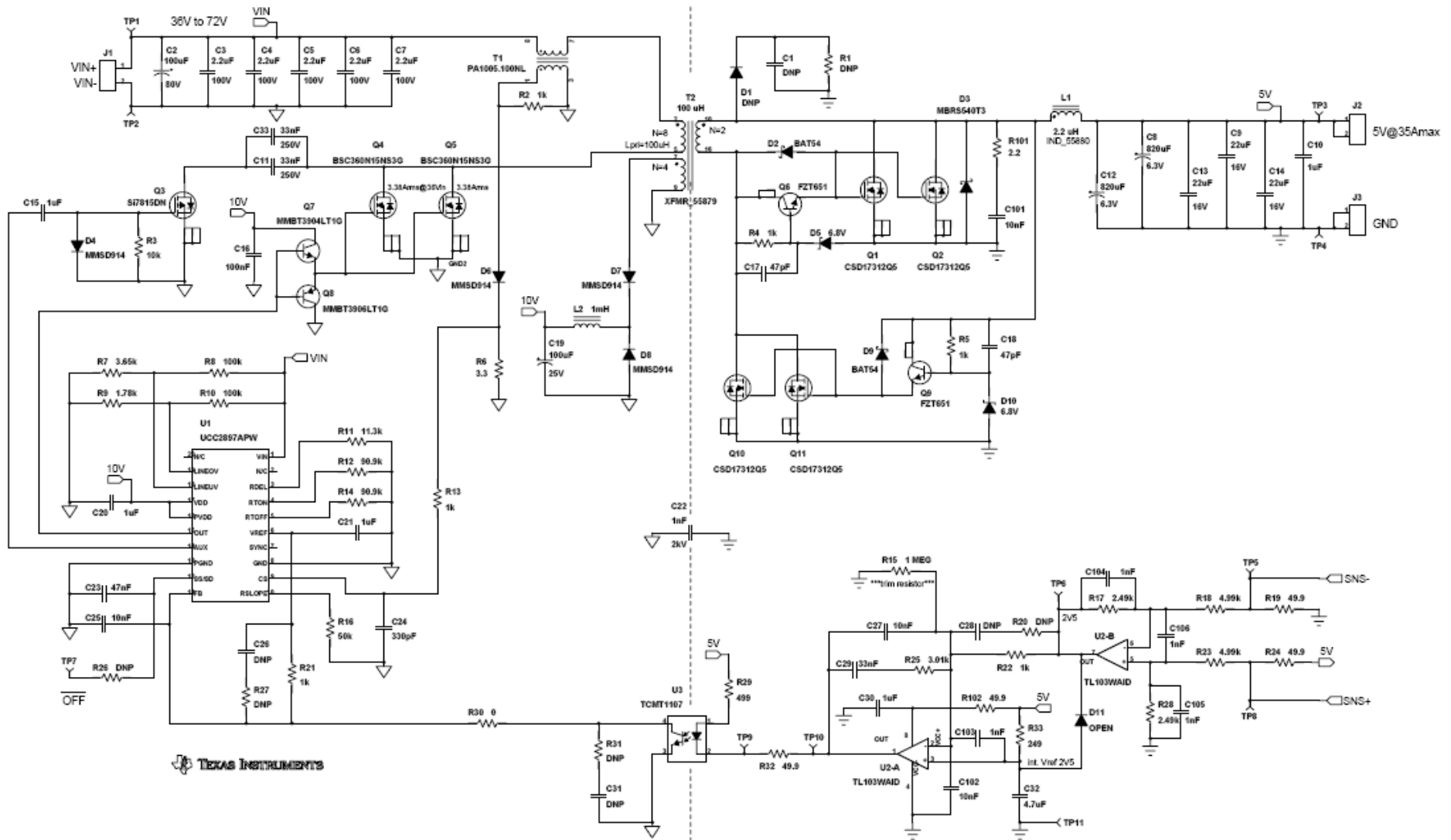
# Active Clamp Forward 5.0V/35A, 175-W Bus Converter Using UCC2897A



# Summary

- Adding active clamp and sync rectifiers improves efficiency of forward (and flyback) up to 5% (Efficiencies >90%, here up to 95%)
- Forward provides best efficiency due to lower conduction losses than flyback
- Forward can be scaled to higher output power with similar results
- Flyback for multiple outputs or when cost is most important

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated