


TIDA-00641 Dual High Resolution Micro-Stepping Driver

Design Overview

TIDA-00641 includes two DRV8848 and a MSP430G2553 as a high resolution micro-stepping driver module using PWM control method. Up to 1/256 micro-stepping can be achieved with smooth current regulation and ultra-low acoustic running noise.

Design Resources

TIDA-00641	Design Folder
DRV8848	Product Folder
MSP430G2553	Product Folder
SN74LVC2G14	Product Folder
LP2985-33	Product Folder
TLV803S	Product Folder

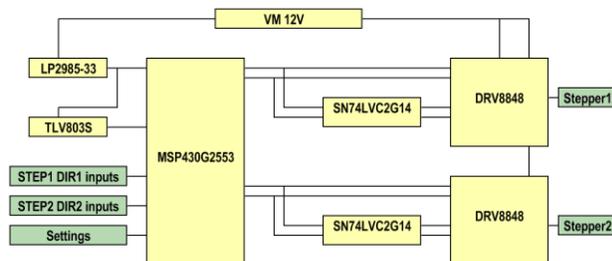


Design Features

- Smooth current and low acoustic noise
- Up to 1/256 micro-stepping level

- Selectable micro-stepping level
- Selectable current level
- Compact dual channel design
- Easy STEP/DIR interface
- Full protections

Featured Applications

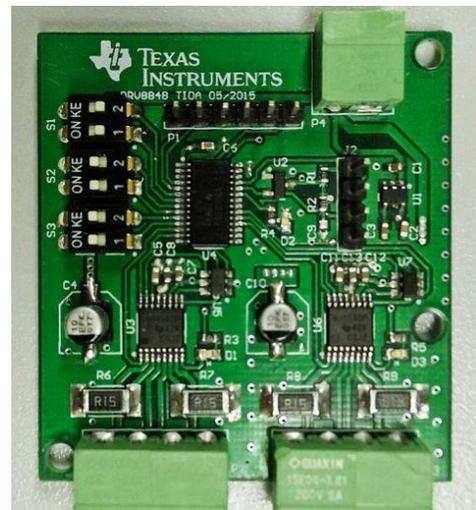- Security camera
- XY moving table
- 3D printer
- POS



1. Introduction

This reference design achieves a dual channel high resolution micro-stepping driver module using PWM current regulation method. Selectable micro-stepping level and current level is provided with the on-board switches. The PWM regulation scheme gives smooth phase current and ultra-low acoustic operation noise. Protections such as over current, over temperature, and short outputs are all provided along with the DRV8848 device.

2. Hardware Block Diagram

The following figures show the hardware block diagram of this design. Figure1 gives the block diagram and figure 2 shows the key control signals and the connection.

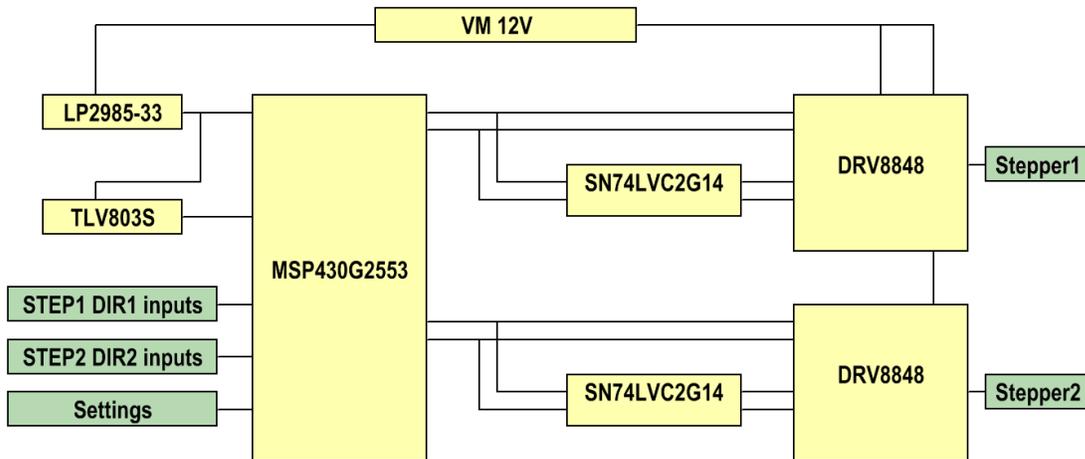


Figure 1. Hardware block diagram

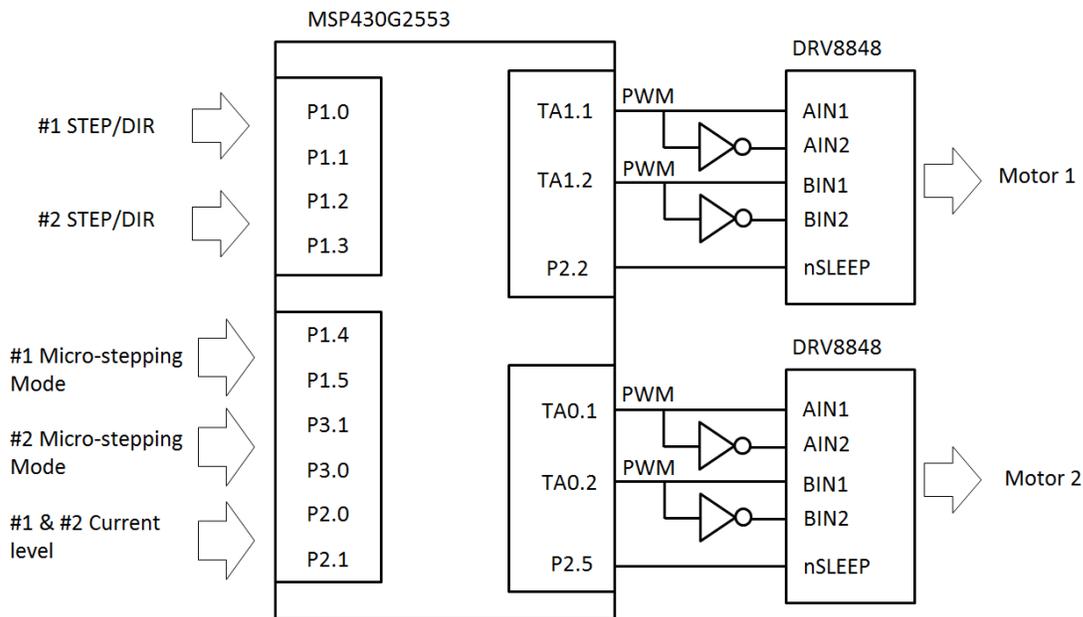


Figure 2. Signals and connection

3. PWM micro-stepping scheme

The following picture shows the PWM micro-stepping scheme. The output of DRV8848 is modulated by the inputs PWM from AINx and BINx. The duty cycle is changing with the micro-stepping index position and controlled by the MCU with an internal preloaded sine table. 50% duty cycle give zero current to the output in this scheme. The MAX duty cycle need to tuned/selected to the needed current level. It is also related on the motor's impedance parameters and the supply voltage. The MIN duty cycle is just

calculated as 1-MAX duty. AIN1 and AIN2 are always complementary in this design. $\pi/2$ phase shift is applied between Phase A and Phase B.

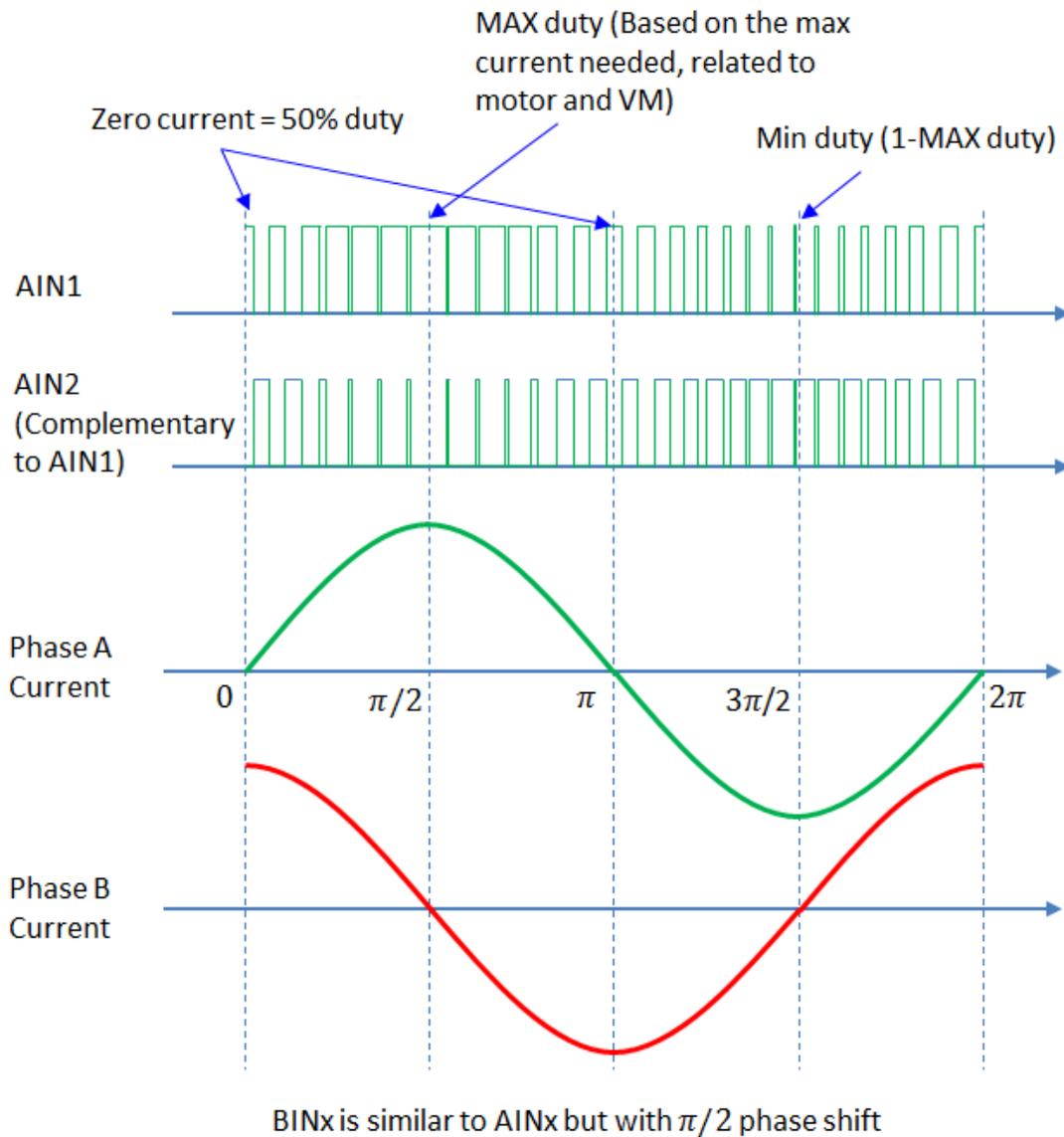


Figure 3. PWM micro-stepping

Although this PWM micro-stepping scheme is using open current control, and the effect of motor back electromotive force is not counted into the model, the output current is tuned out to be very smooth and well controlled with approximate sinusoidal shaping. The most outstanding benefit of the method is to get an ultra-low acoustic noise when the PWM frequency is selected ≥ 20 KHz. In lab test, this module is working much quieter than most other solutions. There is almost no distinguishable audio noise even when put it close to the ear. The PWM micro-stepping method can be applied to any low to mid speed range applications requiring smooth and quiet operation.

4. Flow Chart of the Scheme

This basic flow chart can be applied to any MCU platform. Here we use MSP430G2553 which is very cost effective and matching the application. There are two main loops in the algorithm. The main loop is set to read the inputs BITs switches and update the settings. The IRQ loop is excited at every STEP input rising edge and update the output PWM duty cycle based on the index position and DIR (direction) setting. K in the chart is reflecting a coefficient which determines the MAX/MIN duty cycle.

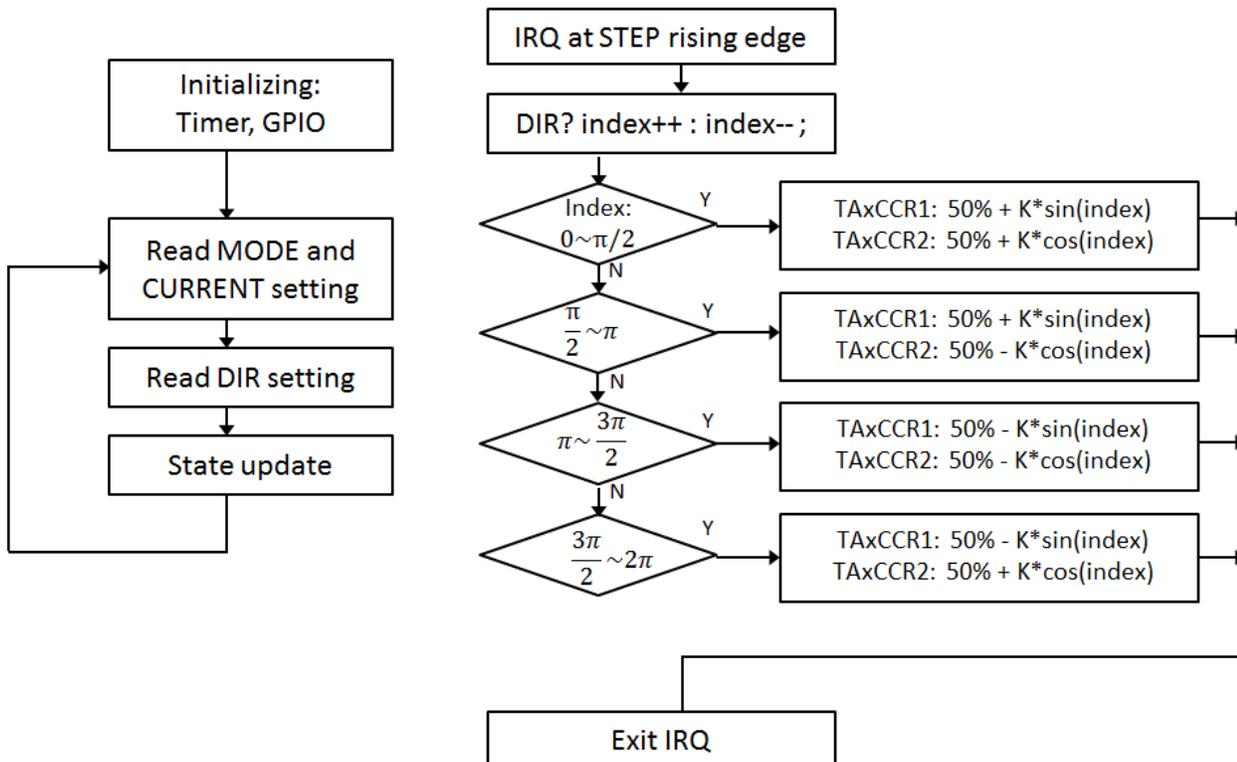


Figure 4. Flow chart

The inputs keys are configured as the following ways.

S1: (for motor 1)

- 00 (00) 1/8 micro-stepping;
- 01 (01) 1/64 micro-stepping;
- 02 (10) 1/128 micro-stepping;
- 03 (11) 1/256 micro-stepping

S2: (for motor 2)

- 00 1/8 micro-stepping;
- 01 1/64 micro-stepping;
- 02 1/128 micro-stepping;
- 03 1/256 micro-stepping

S3: (Current level for both motor 1 and motor2)



- 00 Level-1 Lowest level, about 0.4A at 12V, 5ohm Phase resistor;
- 01 Level-2 Mid-low level;
- 02 Level-3 Mid-high level;
- 03 Level-4 Highest level, about 1.5A at 12V, 5ohm Phase resistor

5. Lab Test Data

Three different kinds of motors are tested with the module.

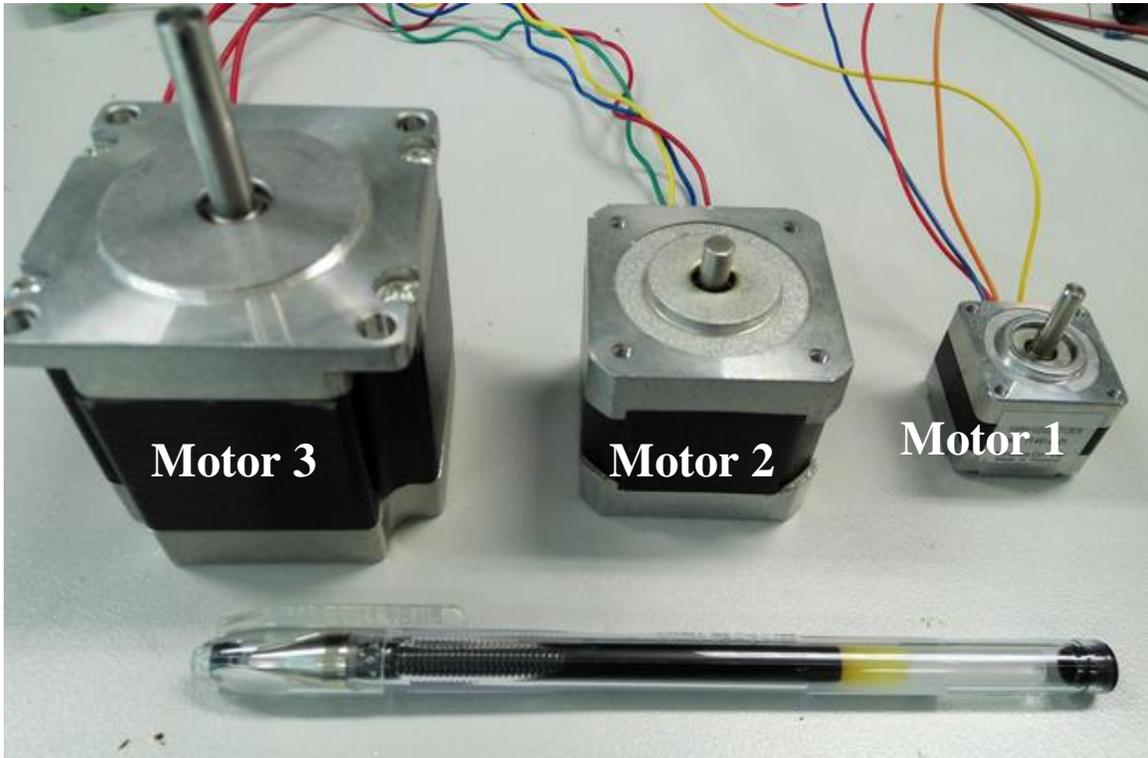


Figure 5. Tested motors

For all the test waveform below, the yellow line is the STEP input. The green line is the phase current. All supply voltage is 12V.

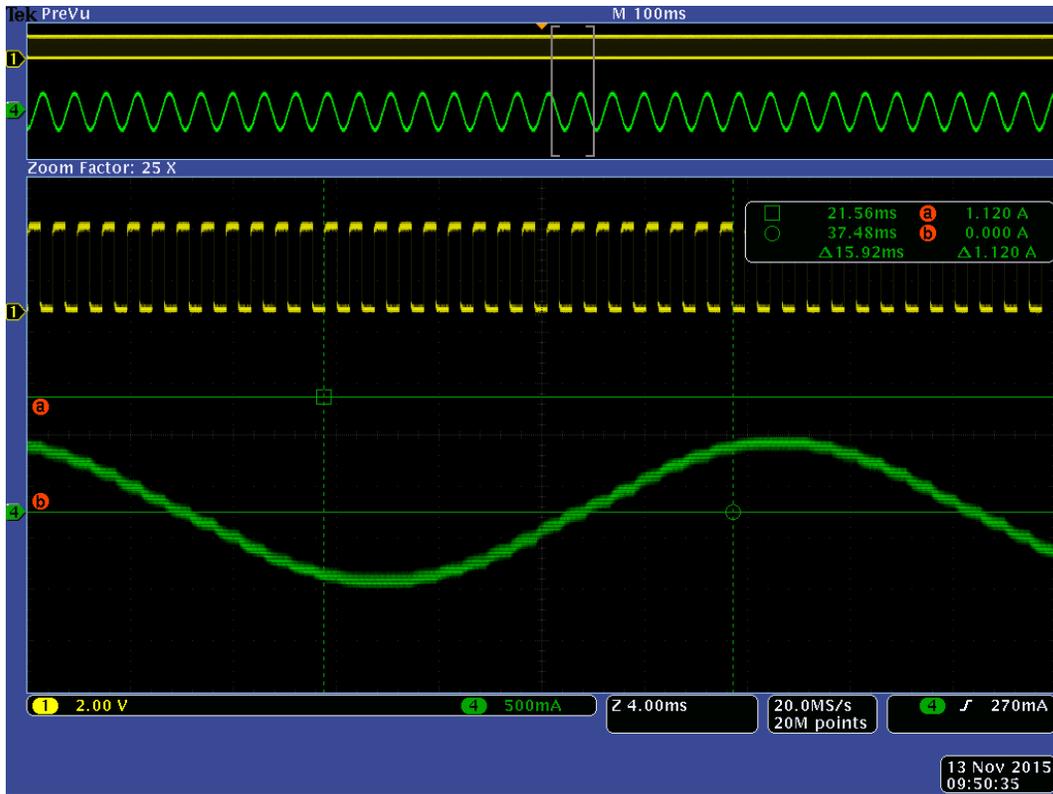


Figure 6. Test waveform (Motor1 1/8 I_level_3)

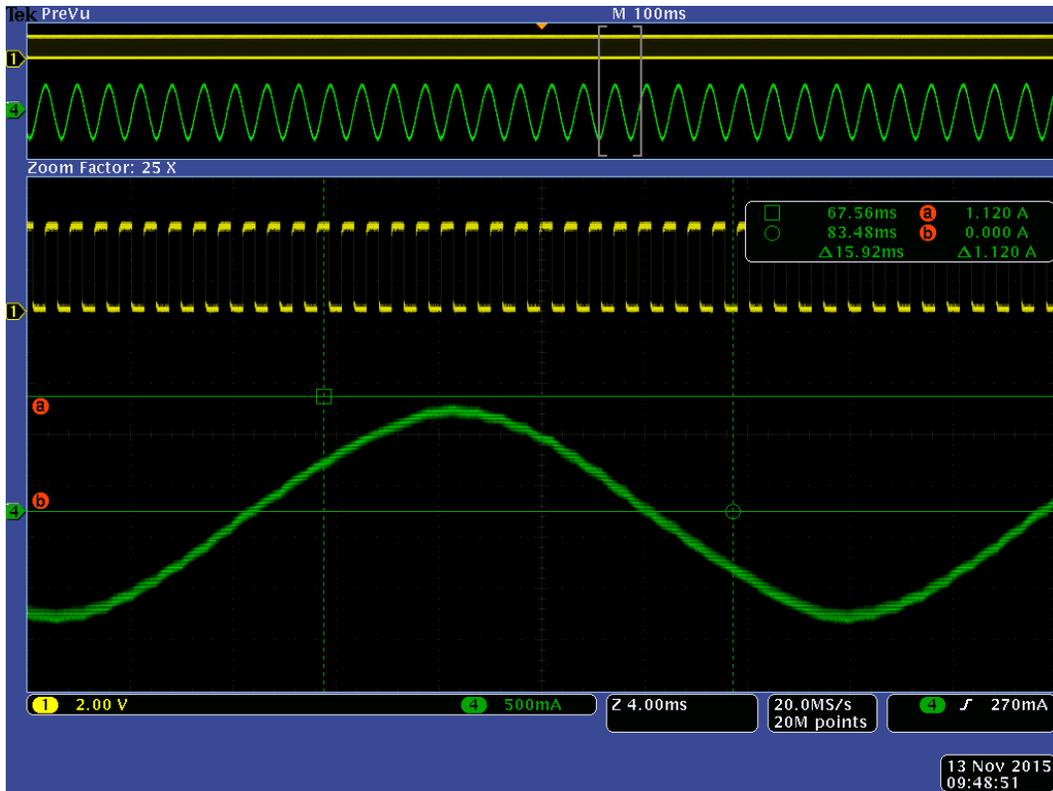


Figure 7. Test waveform (Motor2 1/8 I_level_2)

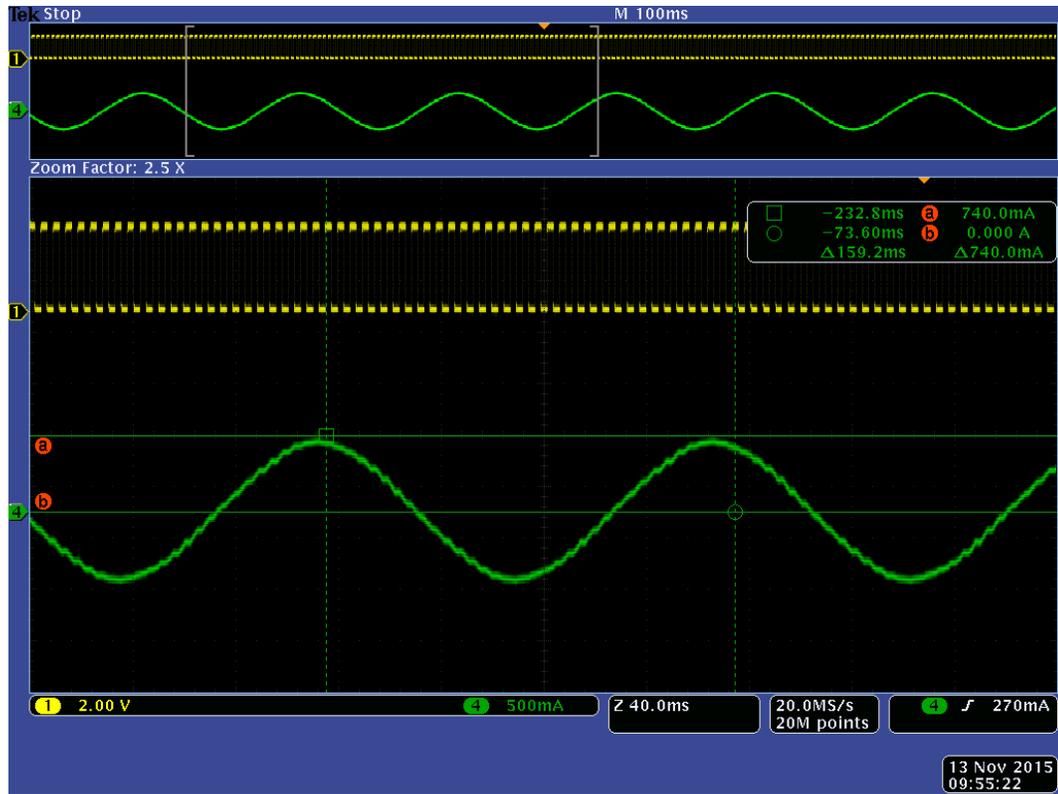


Figure 8. Test waveform (Motor3 1/8 I_level_2)

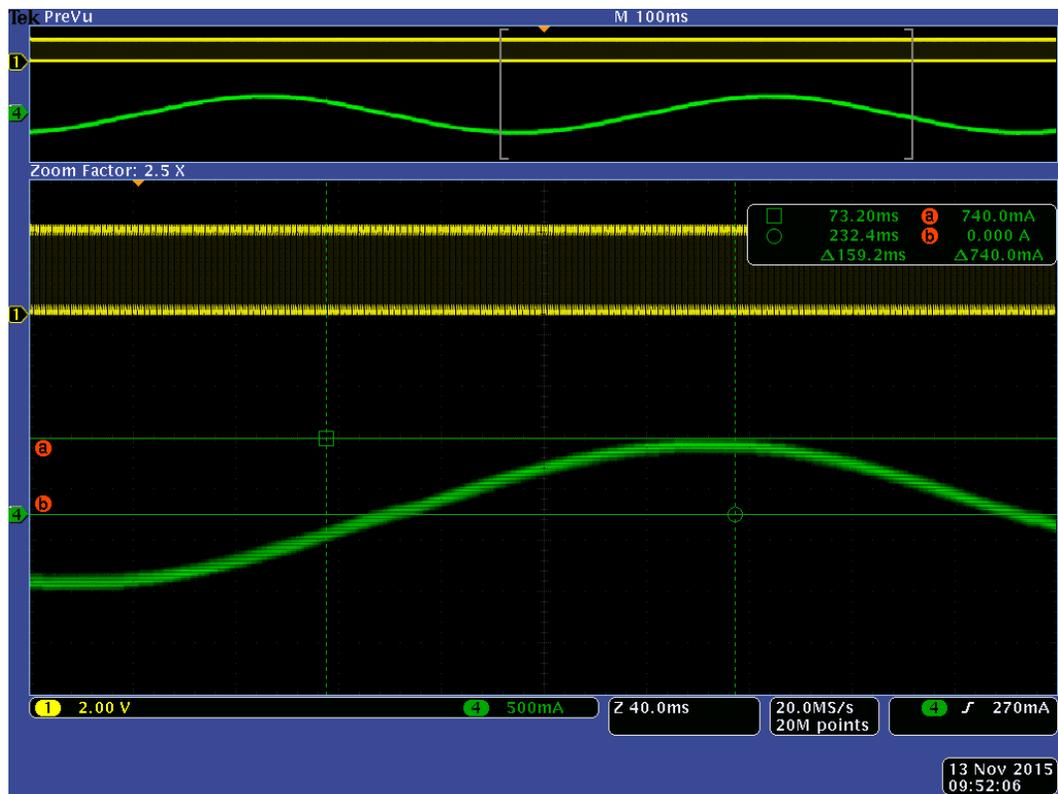


Figure 9. Test waveform (Motor1 1/128 I_level_2)

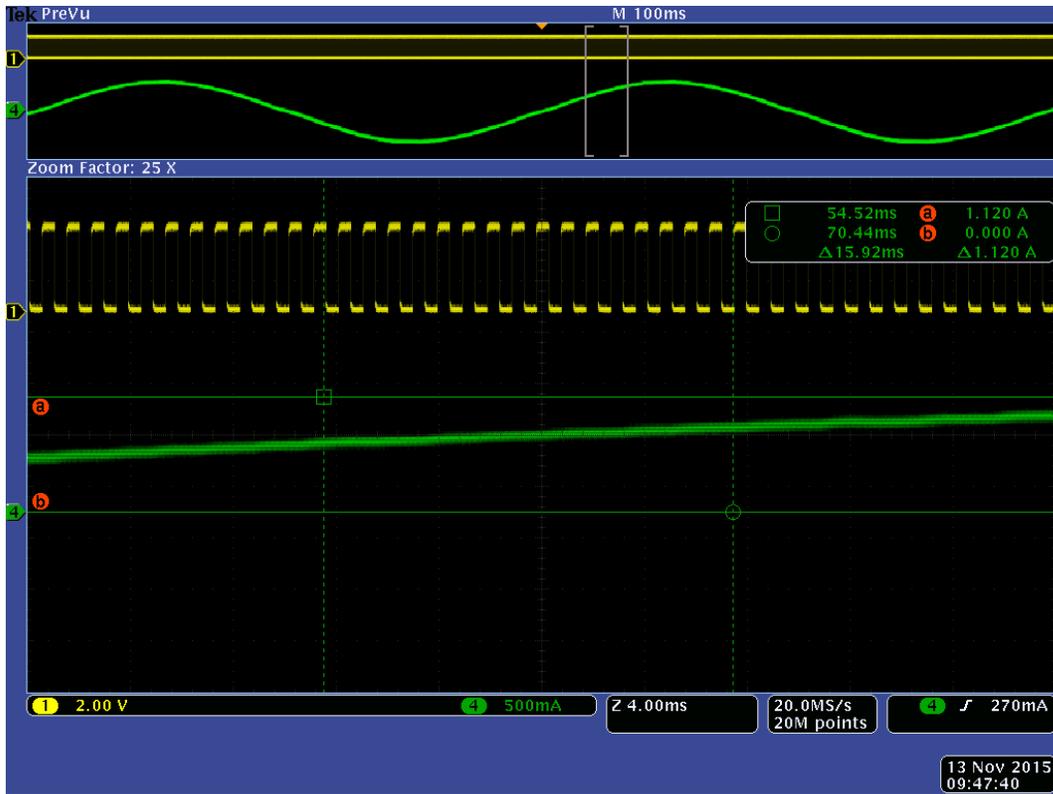


Figure 10. Test waveform (Motor2 1/128 I_level_2)

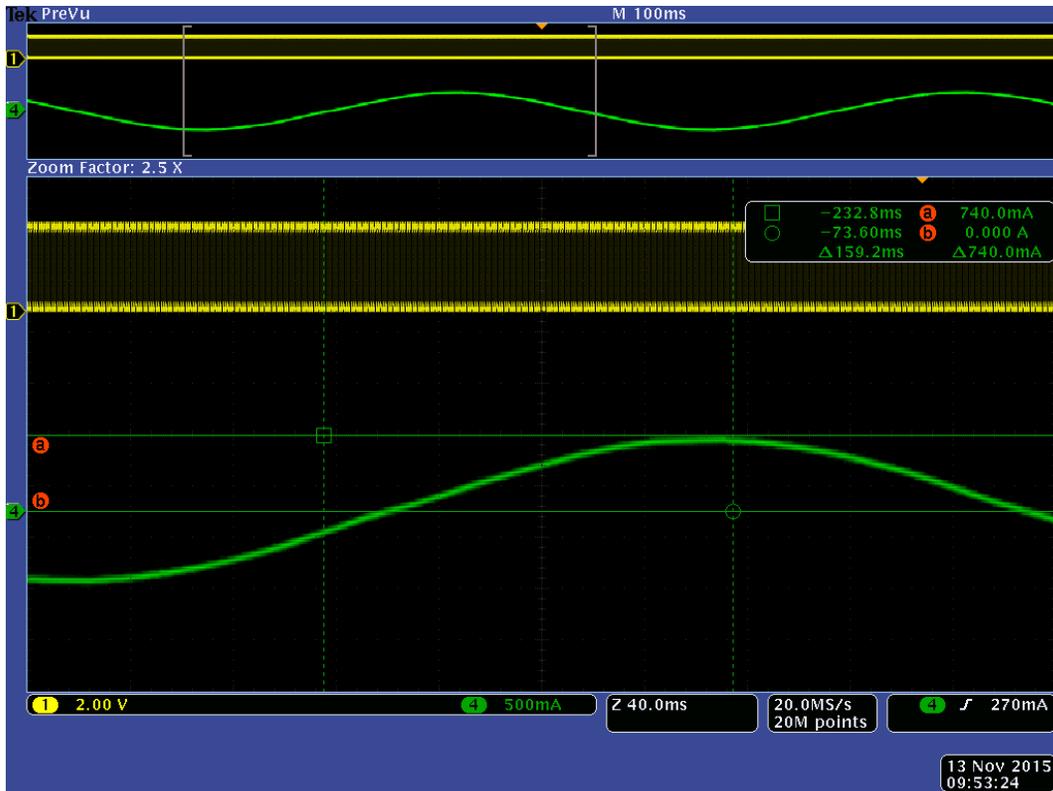


Figure 11. Test waveform (Motor3 1/128 I_level_2)

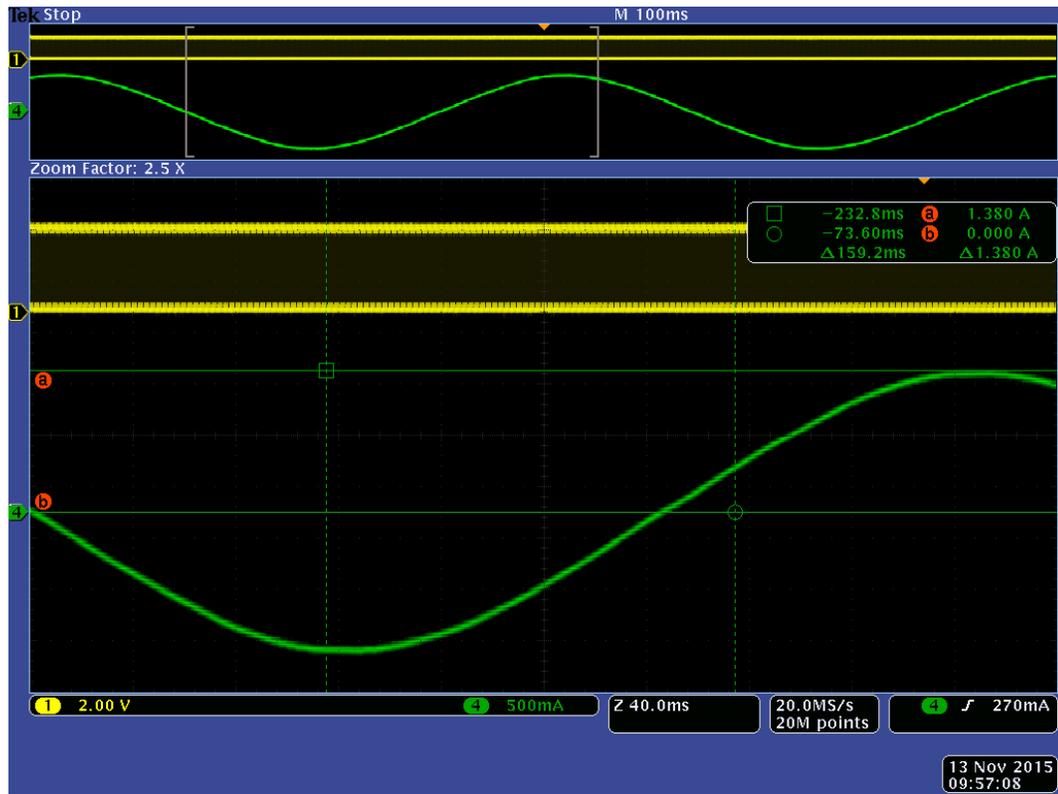


Figure 12. Test waveform (Motor3 1/256 I_level_3)

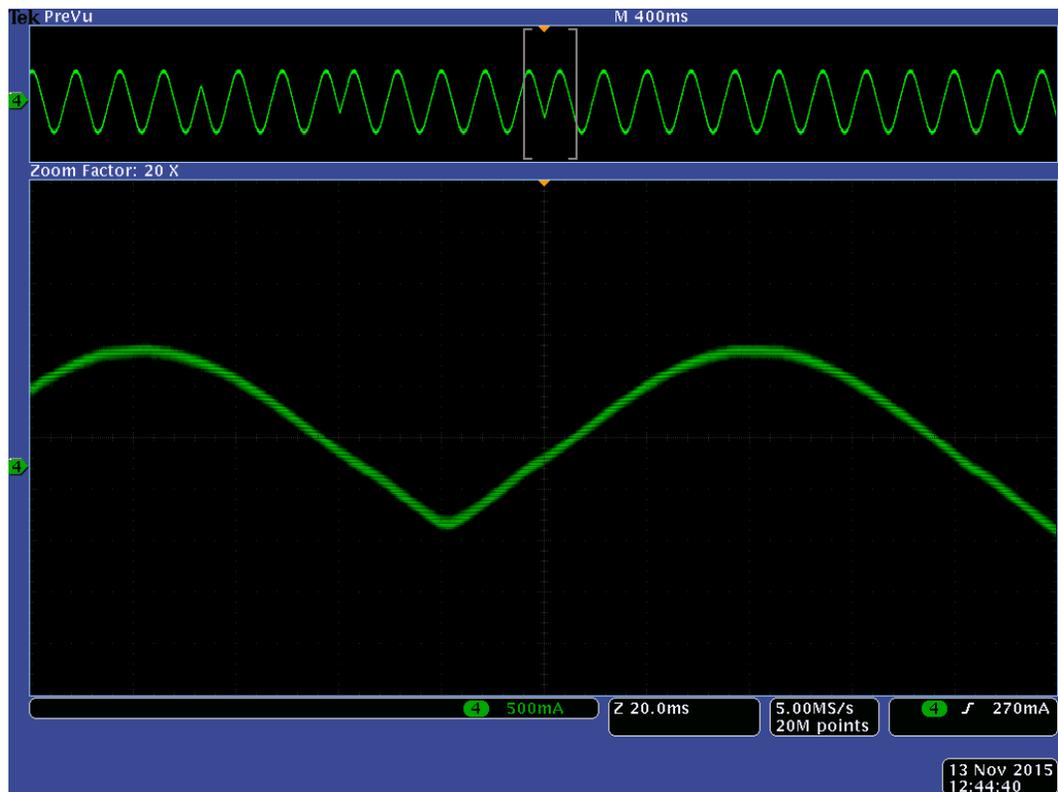


Figure 12. Current waveform when change DIR

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com