

## TI Designs: TIDA-01335

# RTDフロント・エンド搭載の超小型IO-Linkセンサ・トランスマッタのリファレンス・デザイン



## 概要

このリファレンス・デザインでは、6mm幅のPCBという小さな外形で、保護機能とRTDセンサ・フロント・エンドを搭載したIO-Link通信回路を紹介します。高度に統合された小型のIO-Link PHYには、ESD、EFT、サージ保護に加えて、逆極性保護機能があります。組み込みのLDOおよび可変出力電流により、システム実装を簡単かつ柔軟に行え、同時に非常に低い残留電圧から低い消費電力を実現できます。24ビットのシグマ-デルタ、アナログ/デジタル・コンバータ(ADC)によりRTD値(PT100温度センサ)が捕捉され、MCUで変換されて、IO-Link経由でIO-Linkマスターへ送信されます。

## リソース

TIDA-01335	デザイン・フォルダ
TIOL111	プロダクト・フォルダ
MSP430FR5738	プロダクト・フォルダ
ADS1220	プロダクト・フォルダ




E2Eエキスパートに質問

## 特長

- 次の機能を搭載したIO-Link PHY
  - 3.3または5V LDO
  - 逆極性保護
  - IEC 61000-4に従うESD、EFT、サージ保護
- 出力電流制限は50～350mAの範囲で設定可能
- IO-Link V1.1およびV1.0 (TMGスタック)
- 幅6mmの小型PCB基板
- RTD性能: 0.17°C
 
## アプリケーション

- ファクトリ・オートメーション/制御
- 変位トランスマッタ
- 温度トランスマッタ
- 流量トランスマッタ
- レベル・トランスマッタ
- 圧力トランスマッタ



Copyright © 2017, Texas Instruments Incorporated



使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE(重要な注意事項)をご参照くださいますようお願いいたします。英語版のTI製品についての情報を翻訳したこの資料は、製品の概要を確認する目的で便宜的に提供しているものです。該当する正式な英語版の最新情報は、[www.ti.com](http://www.ti.com)で閲覧でき、その内容が常に優先されます。TIでは翻訳の正確性および妥当性につきましては一切保証いたしません。実際の設計などの前には、必ず最新版の英語版をご参照くださいますようお願いいたします。

## 1 System Description

In Factory Automation and Control systems, the IO-Link interface is becoming more and more popular. Applications that usually have a switching output, either NPN or PNP, are upgraded with the IO-Link standard. With this upgrade, two possible scenarios can be addressed:

1. Extend the switching output with the capability to program and configure the field transmitter with IO-Link.
2. Completely communicate with the IO-Link protocol between the field transmitter and PLC.

For the IO-Link communication, a stack is implemented in the MCU, which is also part of this system design. To easily showcase the functionality, a resistance temperature detector (RTD) sensor (in particular, a PT100 element) is connected to the 24-bit ADC, so the sensor data is sent through the IO-Link interface. When the system is connected to an IO-Link master system, the temperature information is shown in the master software.

In addition, this reference design allows one to set a temperature threshold level either with the switch button or configured using IO-Link through the IO-Link master. Two LEDs indicating the status of the system, whether the IO-Link communication is established or in case an error occurs.

The highly integrated IO-Link PHY with a size of only 2.5 mm × 3 mm provides reverse polarity protection and helps designers meet system compliance with the International Electrotechnical Commission (IEC) 61000-4 standard. The built-in EMC protection allows for:

- ±16-kV IEC 61000-4-2 ESD Contact Discharge
- ±4-kV IEC 61000-4-4 Electrical Fast Transient (EFT)
- ±1.2-kV/500-Ω IEC 61000-4-5 Surge

With the capability of using the onboard LDO with either a 3.3-V or 5-V output, the remaining system can be supplied with up to 20 mA. In this reference design, the integrated 3.3-V LDO supplies the MCU and the 24-bit ADC with power from the voltage input, which covers a range from 7 to 36 V with a ±65-V tolerant transient.


This feature set is key for very small field transmitters, like the 6-mm wide PCB in this reference design, which easily fits in a M12-sized tube.

## 1.1 Key System Specifications

PARAMETER	SPECIFICATIONS / COMMENTS
<b>ANALOG FRONT-END</b>	
PT100	3-wire mode
Current excitation	Programmable (10, 50, 100, 250, 500, 1000, 1500 µA)
Reference resistor	3.24 kΩ, Tol = 0.1 %, TC = 10 ppm/C
Resolution	24-bit ADC
<b>DIGITAL PROCESSING</b>	
Temperature calculation	Look up table, based on the Callendar-Van Dusen equation
IO-Link stack	TMG
	V1.1 and V1.0
	Supports COM3
<b>INTERFACE</b>	
Communication	IO-Link
SIO	NPN, PNP
	50- to 350-mA configurable current limit
<b>ALARM</b>	
Fault indicator (open drain)	Overcurrent
	Temperature
	Power supply
<b>POWER SUPPLY</b>	
Operating voltage	7- to 36-V DC
	±65-V transients < 100 µs
LDO	3.3-V output voltage
	20-mA output current

## 2 System Overview

### 2.1 Block Diagram

 

Copyright © 2017, Texas Instruments Incorporated


図 1. TIDA-01335 Block Diagram

## 2.2 Design Considerations

### 2.2.1 IO-Link Interface

The highly integrated IO-Link PHY TIOL111 requires only a small amount of external components. In this reference design, C10, C11, and C13 are placed at the inputs. C9 is the output capacitor of the integrated LDO, and R16 is the resistor setting the maximum output current. The two output signals WAKE and FAULT are open-drain outputs. The needed pullup resistors are inside the MSP430™.

図 2 shows the schematic of the IO-Link interface. J2 is the M12 connector.

 

Copyright © 2017, Texas Instruments Incorporated

**図 2. IO-Link Interface and 3.3-V Output**

The TIOL111 device comes in three different versions:

- TIOL111-3: IO-Link PHY with an integrated LDO, providing 3.3 V
- TIOL111-5: IO-Link PHY with an integrated LDO, providing 5 V
- TIOL111: IO-Link PHY without an integrated LDO

This reference design uses the 3.3-V LDO version, which is capable of providing up to a 20-mA output current. This current is sufficient to power the MCU and ADC as well as to supply the LEDs.

## 2.2.2 RTD Front End

The main focus of this reference design is the realization of the IO-Link interface including the IO-Link stack. To have real world sensor data to transmit using the IO-Link interface, a temperature sensor is also part of this design. The board contains a PT100 element as the temperature sensor.

For the excitation current and to measure the RTD resistance value, this references design uses the ADS1220. With two integrated, programmable excitation current sources and a programmable PGA, the 24-bit ADC is a perfect fit in this application.

 


図 3. Analog Front-End Circuitry

図 3 shows the circuitry of the analog front end. Resistor R9 is only needed for calibration purposes. With  $R9 = 300 \Omega$ , it is used to run a gain calibration. For this purpose, the PT100 element has to be disconnected. This can be realized by removing the short between TP1 and TP2 once calibration is done or not needed. R9 has to be removed and TP1 shorted with TP2.

The excitation current from the ADS1220 is provided through the two diodes D1 and D2, developing a reference voltage across R2. This  $3.24\text{-k}\Omega$  precision resistor has a 0.1% tolerance with a temperature coefficient of 10 ppm/C and generates the reference volatge for the ADC, enabling a ratiometric measurement.

### 2.2.3 Digital Processing

For calculating the temperature, based on the measured RTD resistance, the MSP430FR5738 is part of the design. A look-up table (LUT) translates the measured voltage levels into the respective temperature values according to Calendar-Van Dusen equations. For this, the MCU gets a data set once the ADC provides the data ready (DRDY) information. Once calculated, the temperature data is transmitted through the IO-Link interface.

Also in the MSP430FR5738, the IO-Link stack is running. Once an IO-Link connection is established between the TIDA-01335 reference design and an IO-Link master, the green LED D5 is blinking. With the pushbutton S1, it is possible to set a temperature threshold. Once this threshold is reached, the information is also sent through IO-Link to the master. With the IO-Link master GUI, it is possible to read out this temperature threshold and overwrite the temperature threshold with the GUI. 図 4 shows the schematic of the digital processing section.

 


図 4. Digital Processing Section

## 2.3 Highlighted Products

The following subsections detail each circuit block in the TIDA-00559 block diagram. For more information on each of these devices, see their respective product folders at [TI.com](http://TI.com).


### 2.3.1 TIOL111: IO-Link Device Transceiver With Integrated Surge Protection

The TIOL111 family of transceivers implements the IO-Link interface for industrial bidirectional, point-to-point communication. When the device is connected to an IO-Link master through a three-wire interface, the master can initiate communication and exchange data with the remote node while the TIOL111 acts as a complete physical layer for the communication.

These devices are capable of withstanding up to 1.2 kV (500 Ω) of IEC 61000-4-5 surge and feature integrated reverse polarity protection. A simple pin-programmable interface allows easy interfacing to the controller circuits. The output current limit can be configured using an external resistor. Fault reporting and internal protection functions are provided for undervoltage, overcurrent, and overtemperature conditions.

Key features of this device include:

- 7- to 36-V supply voltage
- PNP, NPN, or IO-Link configurable output
  - IEC 61131-9 COM1, COM2, and COM3 data rate support
- Low residual voltage of 1.75 V at 250 mA
- 50- to 350-mA configurable current limit
- Tolerant to ±65-V transients < 100 μs
- Reverse polarity protection of up to 55 V on L+, CQ, and L-
- Integrated EMC protection on L+ and CQ:
  - ±16-kV IEC 61000-4-2 ESD Contact Discharge
  - ±4-kV IEC 61000-4-4 EFT
  - ±1.2-kV/500-Ω IEC 61000-4-5 Surge
- Fast demagnetization of inductive loads up to 1.5 H
- Large capacitive load driving capability
- < 2-μA CQ leakage current
- < 1.5-mA quiescent supply current
- Integrated LDO options for up to 20-mA current:
  - TIOL111: No LDO
  - TIOL111-3: 3.3-V LDO
  - TIOL111-5: 5-V LDO
- Overtemperature warning and thermal protection
- Remote wake-up indicator
- Fault indicator
- Extended ambient temperature: -40°C to 125°C
- 2.5-mm×3-mm 10-pin VSON package

 

Copyright © 2016, Texas Instruments Incorporated


図 5. TIOL111-3 With 3.3-V Voltage Regulator

### 2.3.2 MSP430FR5738

The TI MSP430FR573x family of ultra-low-power microcontrollers consists of multiple devices that feature embedded FRAM nonvolatile memory, an ultra-low-power 16-bit MSP430 CPU, and different peripherals targeted for various applications. The architecture, FRAM, and peripherals, combined with seven low-power modes, are optimized to achieve extended battery life in portable and wireless sensing applications. FRAM is a new nonvolatile memory that combines the speed, flexibility, and endurance of SRAM with the stability and reliability of flash, all at lower total power consumption. Peripherals include a 10-bit ADC, a 16-channel comparator with voltage reference generation and hysteresis capabilities, three enhanced serial channels capable of I<sup>2</sup>C, SPI, or UART protocols, an internal DMA, a hardware multiplier, an RTC, five 16-bit timers, and digital I/Os.

Key features of this device include:

- Embedded MCU 16-bit RISC architecture up to 24-MHz clock:
  - Wide supply voltage range (2 to 3.6 V)
  - Optimized ultra-low-power modes (81.4 µA/MHz in active and 320 nA in shutdown (LPM4.5))
  - Ultra-low-power ferroelectric RAM
  - 16-KB nonvolatile memory
  - Ultra-low-power writes
  - Fast write at 125 ns per word (16kB in 1 ms)
  - Built-in error coding and correction (ECC) and MPU
  - Universal memory = program + data + storage
  - $10^{15}$  write cycle endurance
- Intelligent digital peripherals:
  - 32-bit hardware multiplier (MPY)
  - Three-channel internal DMA
  - RTC with calendar and alarm functions
  - 16-bit Cyclic redundancy checker (CRC)
  - High-performance analog
  - Enhanced serial communication

 

Copyright © 2016, Texas Instruments Incorporated

**図 6. Functional Block Diagram MSP430FR5738**

### 2.3.3 ADS1220: 24-Bit, 2kSPS, Four-Channel, Low-Power Delta-Sigma ADC With PGA and V<sub>REF</sub> for Small Signal Sensors


The ADS1220 is a precision, 24-bit, ADC that offers many integrated features to reduce system cost and component count in applications measuring small sensor signals. The device features two differential or four single-ended inputs through a flexible input multiplexer (MUX), a low-noise, programmable gain amplifier (PGA), two programmable excitation current sources, a voltage reference, an oscillator, a low-side switch, and a precision temperature sensor.

The device can perform conversions at data rates up to 2000 samples-per-second (SPS) with single-cycle settling. At 20 SPS, the digital filter offers simultaneous 50-Hz and 60-Hz rejection for noisy industrial applications. The internal PGA offers gains up to 128 V/V. This PGA makes the ADS1220 ideally-suited for applications measuring small sensor signals, such as RTDs, thermocouples, thermistors, and resistive bridge sensors. The device supports measurements of pseudo- or fully-differential signals when using the PGA. Alternatively, the device can be configured to bypass the internal PGA while still providing high input impedance and gains up to 4 V/V, allowing for single-ended measurements.

Power consumption is as low as 120  $\mu$ A when operating in duty-cycle mode with the PGA disabled. The ADS1220 is offered in a leadless VQFN-16 or a TSSOP-16 package and is specified over a temperature range of  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$ .

Key features of this device include:

- Low current consumption:
  - Duty-cycle mode: 120  $\mu$ A
  - Normal mode: 415  $\mu$ A
- Wide supply range: 2.3 to 5.5 V
- Programmable gain: 1 to 128 V/V
- Programmable data rates: up to 2 kSPS
- Simultaneous 50-Hz and 60-Hz rejection at 20 SPS with a single-cycle settling digital filter
- Low-noise PGA: 90 nV<sub>RMS</sub> at 20 SPS
- Dual-matched programmable current-sources: 10 to 1500  $\mu$ A
- Internal 2.048-V reference: 5 ppm/ $^{\circ}\text{C}$  (typical) drift
- Internal oscillator: 2% (maximum) accuracy
- Internal temperature sensor
- Two differential or four single-ended inputs
- SPI-compatible interface
- Package: 3.5 mm  $\times$  3.5 mm  $\times$  0.9 mm QFN

 


Copyright © 2016, Texas Instruments Incorporated

**図 7. Functional Block Diagram of ADS1220**
 
### 3 Hardware, Software, Testing Requirements, and Test Results

In [図 8](#), the different building blocks of TIDA-01335 are highlighted.




Copyright © 2017, Texas Instruments Incorporated

**図 8. TIDA-01335 Board Description**


In the bottom view:

- Reference resistor (see 図 9): The resistor R2 is a precise reference resistor. The excitation current develops a voltage across R2, which is used as a reference voltage for the ADC. This approach allows for a ratiometric measurement. It is important to have a stable resistor because the resistor value of the RTD is a ratio to R2. In this reference design, R2 has a tolerance of 0.1% with a temperature coefficient of 10ppm/C.
- Filtering (see 図 9)
- Programming connector (see 図 10)
- Set button: When pressing this button, the current temperature is used as a temperature threshold. The value can also be read out using IO-Link.

 

Copyright © 2017, Texas Instruments Incorporated

**図 9. Reference Resistor and Filtering**

 

Copyright © 2017, Texas Instruments Incorporated

**図 10. Programming Connector**

In the top view:

- Calibration resistor: Resistor R9 is not populated per default. The resistor can be used for gain calibration of the ADC.
- PT100: The PT100 is the temperature sensing element.
- ADS1220: ADC to capture the voltage across the RTD
- MSP430FR5738: The MCU calculates the temperature based on the voltage across the RTD and the look-up table. The MSP430 also has the IO-Link stack for the IO-Link communication.

- TIOL111: This is the IO-Link PHY

### **3.1 Required Hardware and Software**


To get the TIDA-01335 reference design up and running, the following hardware and software is needed:

- TIDA-01335 reference design
- IO-Link master:
  - Example: TMG USB IO-Link Master V2
  - Software for IO-Link master
- M12 cable to connect the reference design and IO-Link master
- MSP430 programmer
  - Example: [MSP-FET](#)
- PC
- IO-Link stack
- IO-Link IODD files
- Optional:
  - Precision reference resistor for calibrating the analog front end
  - Precision digital multimeter (DMM)

### **3.2 Testing and Results**

#### **3.2.1 Test Setup**

図 11 shows how to connect the reference design. The MSP-FET is only required for programming or debugging the MSP430. The M12 cable connects the reference design with the IO-Link master, which is also connected through USB to the PC. The PC has the IO-Link master software installed. For details on the installation of the GUI, see the user manual of the IO-Link master software.

 

Copyright © 2017, Texas Instruments Incorporated

**図 11. Test Setup of Reference Design**

### 3.2.2 Test Results

図 12 through 図 18 show the different steps to configure the IO-Link master GUI. Note that these steps are only valid for the IO-Link master used here. When the reference design is connected as per 図 11, launch the GUI and follow these steps:

1. Click the "Search Master" button (see 図 12).
2. Double-click in the pop-up window on the IO-Link master, which is connected to the system. Typically, this is only one entry as long as only one IO-Link master is connected to the PC (see 図 13).
3. Drag the "TIDA-01335" IODD file and drop it in the "IO-Link" row. See the manual on how to load the specific IODD files (see 図 14).
4. Go to the Vendor and Device information in the IO-Link row. Click on the "Go Online" button to establish a connection between the PC and the IO-Link master. If successful, the color of the button turns green (see 図 15).
5. Double-click in the "Topology" window on "TI Design TIDA-01335" to open the details of this reference design (see 図 16).
6. The green button in the upper left corner indicates a proper connection between the IO-Link master and IO-Link device (see 図 17).
7. By clicking on the "Process Data" tab, the information of the reference design are shown. For this design, the temperature of the RTD sensor is shown, as well as the threshold of the low and high temperature limits (see 図 18).

 


図 12. IO-Link Master GUI 1

 
 
 
 
 
 


図 13. IO-Link Master GUI 2


**図 14. IO-Link Master GUI 3**

**図 15. IO-Link Master GUI 4**

**図 16. IO-Link Master GUI 5**

**図 17. IO-Link Master GUI 6**

**図 18. IO-Link Master GUI 7**

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-01335](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01335](#).

### 4.3 PCB Layout Recommendations

#### 4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01335](#).

#### 4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01335](#).

#### 4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01335](#).

#### 4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01335](#).

## 5 Software Files

To download the software files, see the design files at [TIDA-01335](#).

## 6 Related Documentation

This design did not use any documentation.

### 6.1 商標

MSP430 is a trademark of Texas Instruments.

すべての商標および登録商標はそれぞれの所有者に帰属します。

## 7 About the Author

**ALEXANDER WEILER** is a systems engineer at Texas Instruments, where he is responsible for developing reference design solutions for the industrial segment. Alexander brings to this role his extensive experience in high-speed digital, low-noise analog, and RF system-level design expertise. Alexander earned his diploma in electrical engineering (Dipl.-Ing.(FH)) from the University of Applied Science in Karlsruhe, Germany.

## TIの設計情報およびリソースに関する重要な注意事項

Texas Instruments Incorporated ("TI")の技術、アプリケーションその他設計に関する助言、サービスまたは情報は、TI製品を組み込んだアプリケーションを開発する設計者に役立つことを目的として提供するものです。これにはリファレンス設計や、評価モジュールに関する資料が含まれますが、これらに限られません。以下、これらを総称して「TIリソース」と呼びます。いかなる方法であっても、TIリソースのいずれかをダウンロード、アクセス、または使用した場合、お客様(個人、または会社を代表している場合にはお客様の会社)は、これらのリソースをここに記載された目的にのみ使用し、この注意事項の条項に従うことに合意したものとします。

TIによるTIリソースの提供は、TI製品に対する該当の発行済み保証事項または免責事項を拡張またはいかなる形でも変更するものではなく、これらのTIリソースを提供することによって、TIにはいかなる追加義務も責任も発生しないものとします。TIは、自社のTIリソースに訂正、拡張、改良、およびその他の変更を加える権利を留保します。

お客様は、自らのアプリケーションの設計において、ご自身が独自に分析、評価、判断を行う責任をお客様にあり、お客様のアプリケーション(および、お客様のアプリケーションに使用されるすべてのTI製品)の安全性、および該当するすべての規制、法、その他適用される要件への遵守を保証するすべての責任をお客様のみが負うことを理解し、合意するものとします。お客様は、自身のアプリケーションに関して、(1) 故障による危険な結果を予測し、(2) 障害とその結果を監視し、および、(3) 損害を引き起こす障害の可能性を減らし、適切な対策を行う目的での、安全策を開発し実装するために必要な、すべての技術を保持していることを表明するものとします。お客様は、TI製品を含むアプリケーションを使用または配布する前に、それらのアプリケーション、およびアプリケーションに使用されているTI製品の機能性を完全にテストすることに合意するものとします。TIは、特定のTIリソース用に発行されたドキュメントで明示的に記載されているもの以外のテストを実行していません。

お客様は、個別のTIリソースにつき、当該TIリソースに記載されているTI製品を含むアプリケーションの開発に関連する目的でのみ、使用、コピー、変更することが許可されています。明示的または默示的を問わず、禁反言の法理その他どのような理由でも、他のTIの知的所有権に対するその他のライセンスは付与されません。また、TIまたは他のいかなる第三者のテクノロジまたは知的所有権についても、いかなるライセンスも付与されるものではありません。付与されないものには、TI製品またはサービスが使用される組み合わせ、機械、プロセスに関連する特許権、著作権、回路配置利用権、その他の知的所有権が含まれますが、これらに限られません。第三者の製品やサービスに関する、またはそれらを参照する情報は、そのような製品またはサービスを利用するライセンスを構成するものではなく、それらに対する保証または推奨を意味するものではありません。TIリソースを使用するため、第三者の特許または他の知的所有権に基づく第三者からのライセンス、あるいはTIの特許または他の知的所有権に基づくTIからのライセンスが必要な場合があります。

TIのリソースは、それに含まれるあらゆる欠陥も含めて、「現状のまま」提供されます。TIは、TIリソースまたはその仕様に関して、明示的か暗黙的かにかかわらず、他のいかなる保証または表明も行いません。これには、正確性または完全性、権原、統発性の障害に関する保証、および商品性、特定目的への適合性、第三者の知的所有権の非侵害に対する默示の保証が含まれますが、これらに限られません。

TIは、いかなる苦情に対しても、お客様への弁護または補償を行う義務はなく、行わないものとします。これには、任意の製品の組み合わせに関連する、またはそれらに基づく侵害の請求も含まれますが、これらに限られず、またその事実についてTIリソースまたは他の場所に記載されているか否かを問わないものとします。いかなる場合も、TIリソースまたはその使用に関連して、またはそれらにより発生した、実際的、直接的、特別、付随的、間接的、懲罰的、偶発的、または、結果的な損害について、そのような損害の可能性についてTIが知られていたかどうかにかかわらず、TIは責任を負わないものとします。

お客様は、この注意事項の条件および条項に従わなかつたために発生した、いかなる損害、コスト、損失、責任からも、TIおよびその代表者を完全に免責するものとします。

この注意事項はTIリソースに適用されます。特定の種類の資料、TI製品、およびサービスの使用および購入については、追加条項が適用されます。これには、半導体製品(<http://www.ti.com/sc/docs/stdterms.htm>)、評価モジュール、およびサンプル(<http://www.ti.com/sc/docs/samptersms.htm>)についてのTIの標準条項が含まれますが、これらに限られません。