

Designing High-Side and 3-Phase Isolator MOSFET Circuits in Motor Applications

Garrett Walker, Analog Motor Drive



Introduction

Automotive motor systems, like those in electric power steering (EPS) systems, often utilize isolation switches to disable various parts of the power stage in response to system faults. These isolation switches are most commonly used to isolate the power stage from the battery voltage, or isolate individual motor phases to allow for fail-operational functionality.

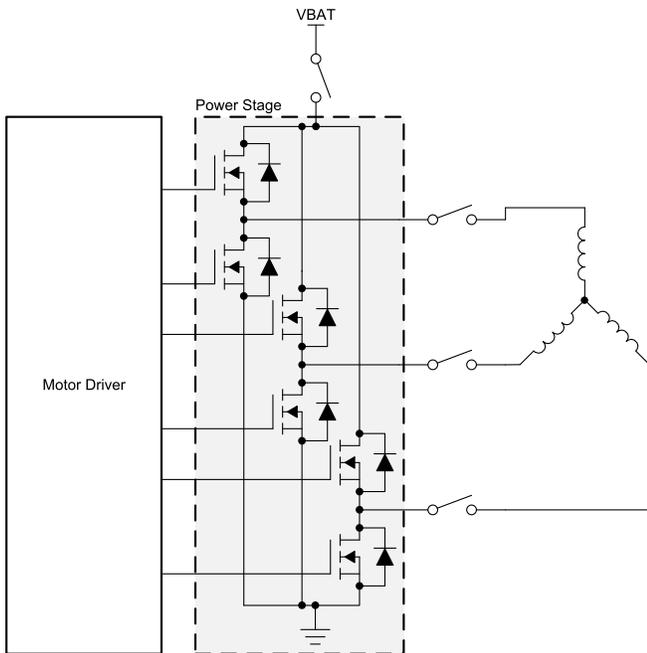


Figure 1. High-Side and Phase Isolation Switches

These switches can be implemented with a variety of components, but NMOS power FETs are usually the preferred option due to their low power dissipation. However, to turn on the NMOSFETs, the system must apply a gate voltage higher than the battery voltage. In motor drivers that utilize a bootstrap architecture, this means that an external voltage source must be provided to supply the overdrive voltage.

However, with TI motor drivers that incorporate an integrated boost converter (like the DRV3205-Q1) or charge pump (like the DRV3245Q-Q1 and DRV8305-Q1), this voltage supply is already available, and can be used to drive the isolation switch FETs with a few external components. While these motor drivers are designed to support these external loads, care must be taken to avoid exceeding the total current limit of the overdrive supply.

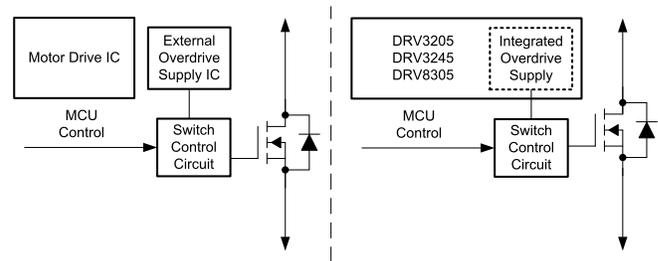


Figure 2. Overdrive Supply Comparison

There are several methods for controlling the isolation switches, with various advantages and drawbacks depending on the circuit topology. The following circuits demonstrate a few different possible control methods.

Topology 1:

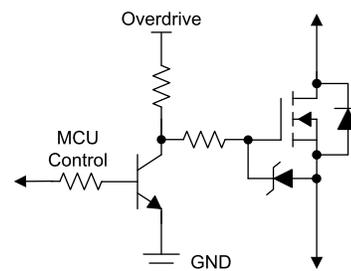


Figure 3. Single Transistor Control Circuit

This simple control method uses a single transistor connected to GND, with a current limiting resistor on the overdrive voltage supply and the gate of the FET. While this topology *does* minimize component count, the turn on and turn off times for the switch will be very slow. This is because the resistor must be sized appropriately to avoid overloading the overdrive supply when the FET is turned off.

Topology 2:

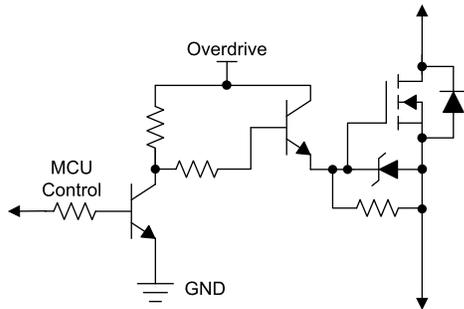


Figure 4. Active Pull-Up Control Circuit

This second circuit uses an additional transistor to provide a faster turn-on for the FET, but the passive pull-down means that the turn-off time will still be relatively long. Additionally, the passive pulldown will cause a constant current load on the overdrive supply when the FET is on.

Topology 3:

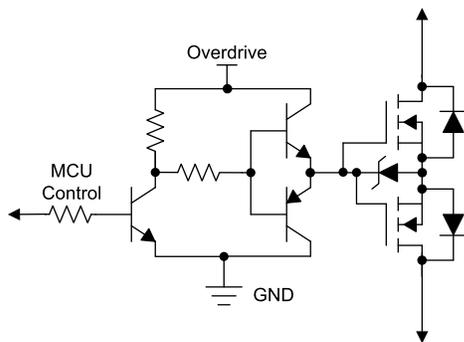


Figure 5. Push/Pull Control Circuit with Bidirectional Switch

This third circuit uses a PNP/NPN BJT stack in order to provide an active pullup and pulldown to the switch, providing a much faster turn-on/turn-off. This architecture will minimize the current load on the overdrive voltage supply in both the on and off states, as the only continuous load on the overdrive supply is through the low-current control transistor. Additionally, this circuit demonstrates the use of two NMOSFETs placed back-to-back to provide a bi-directional cutoff.

Conclusion

Isolation switches allow designers to dynamically control the power stage in response to a variety of system faults, and TI motor drivers with integrated overdrive supplies allow these switches to be implemented in a simple and cost-effective manner. Ultimately, the optimal control circuit for any system will be determined by a combination of speed, cost, and layout space. The above topologies are not an extensive list of every possible architecture, but should serve as a starting point for designing isolation switches in motor drive systems. For more information on the relevant TI motor drivers, check the links in the following table. For any additional questions, please visit the [Motor Drivers Forum](#) on TI's E2E™ online community.

Table 1. Device Recommendations

| Device | Integrated Overdrive Supply: |
|-----------------------------|------------------------------|
| DRV3205-Q1 | Boost Converter |
| DRV3245Q-Q1 | Charge Pump |
| DRV8305-Q1 | Charge Pump |

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated