

126-Watt SMPS for TAS511x Applications

Yong-Gwan Kim

Digital Audio Department

ABSTRACT

The switch-mode power supply (SMPS) featured in this application report is designed for 5.1 bridge-tied load (BTL) digital audio amplifiers using the TAS3103/TAS5111 and TAS5026, with up to 50 W/channel. There are actually two separate power supplies on the board, one working at 72 kHz to power the discrete amplifiers and the other working at 60 KHz to power the integrated PWM and switching controller section. The board operates from an ac input voltage of 110 Vac or 220 Vac, chosen by operating a voltage selector switch. The controllers for both power supplies operate using flyback topology. During conditions of no load or low power output, this supply uses a switch-skipping process to reduce power consumption, thereby increasing overall efficiency.

Contents

| | | |
|----------|---|-----------|
| 1 | Introduction | 2 |
| 1.1 | Flyback Topology | 2 |
| 1.2 | Transformer Design | 3 |
| 1.2.1 | Full-Wave Bridge Operation | 5 |
| 1.2.2 | Voltage Doubler Operation | 6 |
| 2 | Electrical Specification | 7 |
| 3 | Transformer Winding Specifications | 8 |
| 4 | Schematic | 10 |
| 5 | PCB Gerber Files | 12 |
| 6 | Bill of Materials | 14 |
| 7 | SMPS Board | 16 |

List of Figures

| | | |
|----|---|----|
| 1 | Flyback Transformer | 2 |
| 2 | Flyback Schematic Diagram | 3 |
| 3 | Full-Wave Bridge Operation | 5 |
| 4 | Voltage Doubler Configuration Waveforms | 6 |
| 5 | Schematic Diagram | 8 |
| 6 | Schematic Diagram | 9 |
| 7 | PCB Layout | 12 |
| 8 | Component Layout | 13 |
| 9 | Component Side of Board | 16 |
| 10 | Pattern Side of Board | 17 |

1 Introduction

1.1 Flyback Topology

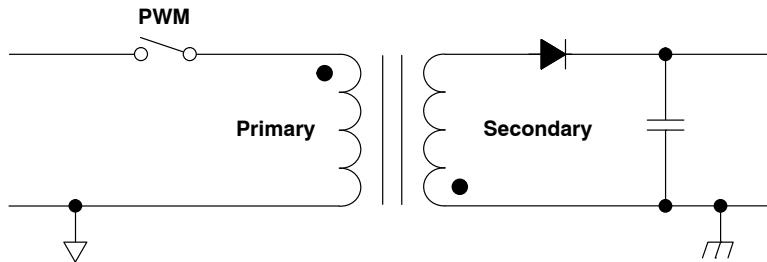


Figure 1. Flyback Transformer

The primary and secondary windings of the first converter transformer have opposite polarities. When the switch is closed, primary current increases, but during this time the output rectifier is reverse-biased and no secondary current flows. When the switch opens, the secondary voltage reverses. The energy stored in the transformer core (or gap) is released, and current flows through the diode to the output. The secondary voltage relative to the primary voltage is in direct proportion to the turns ratio of the transformer. The use of a transformer provides line isolation and allows the designer to select the turns ratio to optimize the duty cycle or switching frequency and to minimize peak primary current.

The flyback topology is amenable to multiple outputs by including additional secondaries with the appropriate turns ratios. The dynamic cross-regulation between these multiple outputs is theoretically good. However, leakage inductance between the secondaries can severely impair the cross-regulation, and considerable care must be applied to the design of the transformer in this respect.

The single-ended flyback circuit is popular at low power levels because of its simplicity and low cost. Its big disadvantage in the discontinuous operating mode is the high peak current in the switch and in the output capacitor, which can overload these components. The continuous mode reduces the peak current almost in half, but brings in other problems, compensation methods, and poor transient response. Many application designers use the flyback technique up to 150–250 W.

1.2 Transformer Design

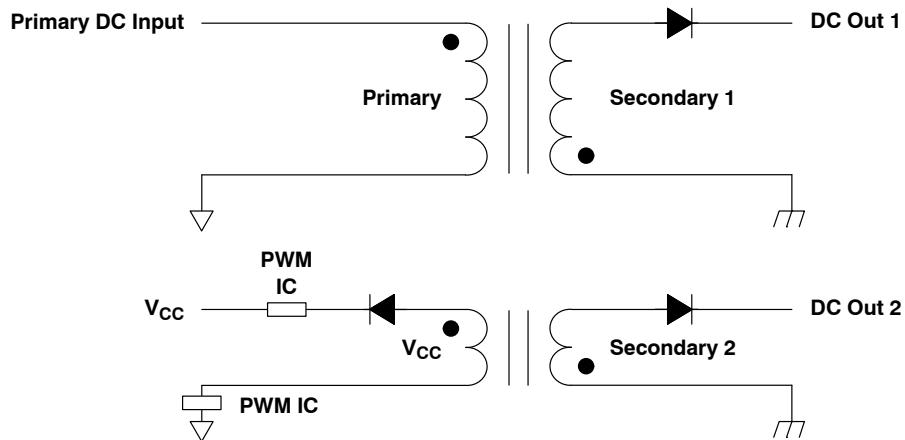


Figure 2. Flyback Schematic Diagram

The normal design method for calculating flyback-transformer turn ratios in the case of 110-Vac to 220-Vac input is as follows. The first step is to determine the total output wattage (total output voltage \times current). Second, estimate the input ac line voltage regulation and voltage drop due to resistance in the etch pattern, connector terminals, etc.

Total output: a W = (output voltage \times output current)

AC input voltage: The input line voltage tolerance is 220 Vac $\pm 20\%$. The minimum input to the board is therefore 220 Vac $-20\% = 176$ Vac. Allowing another 10% voltage drop (worst case) due to resistance in connectors and pattern etch yields 176 Vac $-10\% \approx 158$ Vac.

Main transformer input voltage (B+): The rectifier diode voltage drop for a half-wave bridge is -0.8 V and for a full-wave bridge is -1.6 V. The calculation also must account for the primary capacitor ripple factor, b Vp-p.

$$B+ = (158 \text{ Vac} \times \sqrt{2}) - 2.6 \text{ V} - b \text{ Vp-p.}$$

Switching frequency and maximum on-time: For a switching frequency c kHz and maximum on-duty $d\%$,

$$t = \frac{1}{c \text{ kHz}} \text{ maximum on-time, and}$$

$$\frac{1}{c \text{ kHz}} \times d\% \text{ (on-time duty)} = e \text{ maximum duty.}$$

Energy input current: For a maximum efficiency $f\% = \left(\frac{P_{\text{out}} \text{ (total power output)}}{P_{\text{in}} \text{ (total power input)}} \right)$,

$$\text{the total power input } P_{\text{in}} = \frac{P_{\text{out}} \text{ (total power output)}}{\text{Efficiency } f\%},$$

The average current can now be calculated: $I_{\text{avg}} = \frac{P_{\text{in}}}{B+ \text{ min.}}$

$$\text{Maximum input current, } I_{\text{peak}} = \frac{2 \times I_{\text{avg}}}{e \text{ maximum duty.}}$$

Then, we can get the primary inductance value

$$L_p = \frac{B+ \min (\text{min primary input voltage}) \times e \max \text{ sec/cycle (maximum duty)}}{I_{\max} (\text{max current}) \times c \text{ kHz (switching frequency)}}$$

and the switching-off-time flyback voltage

$$V_{fb} = B+ \min (\text{min primary input voltage}) \frac{e \max \text{ sec/cycle (maximum duty)}}{1 - e \max \text{ sec/cycle (maximum duty)}}$$

$$\text{Turns ratio} = \frac{N_p/N_s}{V_{fb} / V_{out} + V_{dp}}$$

where N_p = primary turns, N_s = secondary turns, V_{fb} = flyback voltage, and V_{dp} = secondary-side diode drop.

After that, we need to calculate primary turns and secondary turns using the core section area, core volume, and material. Hence, if we put $N_p = P$ turns, we can obtain the turns count for each secondary winding by multiplying its output turns ratio times the number of primary turns.

To design for a reference value of new core application, the following equations are needed:

$$L_p = \frac{B+ \min \times e \max (\text{max on duty})}{I_{pk} (\text{max current}) \times f_{sw} (\text{switching frequency})}$$

$$N_p = \sqrt{\frac{L_p (\text{primary } L) \times 10^9}{AL - V (\text{inductance index})}}, \text{ and}$$

$$N_s = \frac{N_p (\text{primary turns}) \times V_{out} (\text{output voltage})}{V_{in} (\text{input voltage})}, \text{ where}$$

V_{in} (input voltage) is at 50% maximum duty.

The last item is the transformer coil diameter calculation method,

$$D_{coil} = \sqrt{2 \times \frac{I_{rms}}{3.14 \times J}}, \text{ where } J = \text{current density, flyback topology 4 or 5.}$$

The secondary side calculations are the same as for the primary side.

1.2.1 Full-Wave Bridge Operation

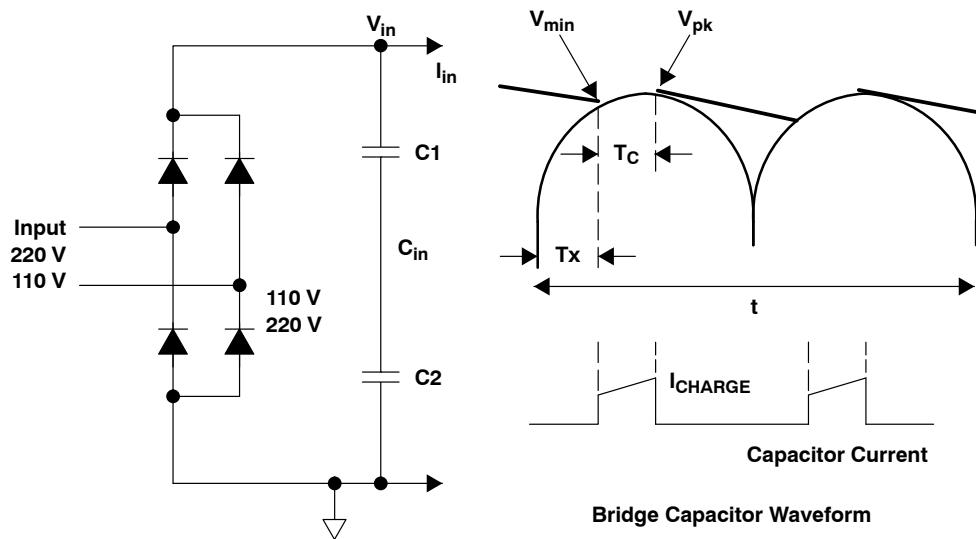


Figure 3. Full-Wave Bridge Operation

In Figure 3, C_{in} (C_1 in series with C_2) charges to peak line voltage each half-cycle. C_{in} then discharges, providing all the energy required by the switching supply until it recharges during the next half-cycle. Energy from C_{in} each half-cycle is:

$$W_{in} = \frac{P_{in} \text{ (power input)}}{f \text{ (AC input frequency)}}, \text{ Joules (watt - seconds)}, f = 60 \text{ Hz, worst case } f = 50 \text{ Hz.}$$

$$\frac{W_{in}}{2} = \frac{1}{2} C_{in} (V_{pk}^2 - V_{min}^2), \text{ Hence, } C_{in} = \frac{W_{in}}{V_{pk}^2 - V_{min}^2}$$

The recharge time, t_c , is fixed by the voltage waveform of the rectified ac line across the capacitor.

$$V_{min} = V_{pk} \cos(2\pi f \cdot t_c), t_c = \frac{\cos^{-1}\left(\frac{V_{min}}{V_{pk}}\right)}{2\pi f},$$

assuming a rectangular charging current pulse of peak amplitude $\Delta Q = I_{chg} \Delta t = C \Delta V$,

$$\text{Hence, } I_{chg} = \frac{C(V_{pk} - V_{min})}{t_c}, \text{ peak charging current.}$$

1.2.2 Voltage Doubler Operation

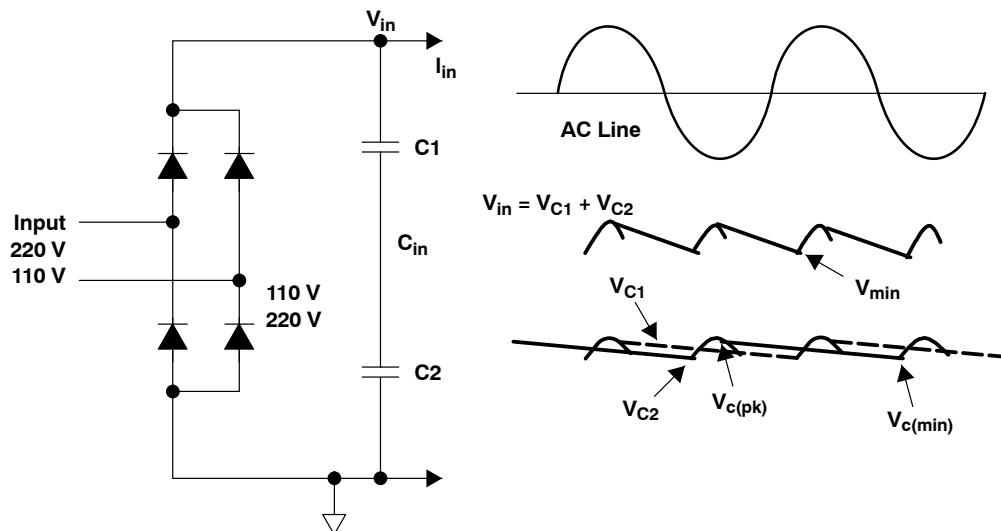


Figure 4. Voltage Doubler Configuration Waveforms

C1 and C2 alternately charge to peak line voltage. Whenever the input voltage, V_{in} , is at instantaneous minimum, one capacitor is at its minimum, but the other capacitor is halfway between peak and minimum voltage. The minimum voltage on each capacitor corresponding to an overall minimum voltage of 200 V can be approximated as follows. Normally V_{c1} and V_{c2} minimum line voltage is 90 V and maximum voltage is 135 V.

$$V_{min} = V_{c1\ min} + V_{c2\ avg} = V_{c\ min} + \frac{V_{c\ min} + V_{c\ pk}}{2}$$

C1 and C2 each discharge for a complete cycle. Each capacitor must supply half the energy required by the switching regulator for an entire line cycle.

$$\frac{W}{2} = \frac{1}{2} C_1 (V_{c\ pk}^2 - V_{c\ min}^2), \quad C_1 = C_2 = \frac{W}{V_{c\ pk}^2 - V_{c\ min}^2}.$$

$$C_{in}, \text{ the series combination of } C_1 \text{ and } C_2, \quad \frac{1}{C_{in}} = \frac{1}{C_1} + \frac{1}{C_2}$$

2 Electrical Specification

1. Input voltage: 110 Vac, 220 Vac
 Option): Input range: 90 Vac~130 Vac (CN83: SHORT) or 165 Vac–265 Vac (CN83: OPEN)
2. UC3844 switching frequency: 72 kHz (transformer T81).

| Output Voltage | Current | Tolerance | Output Ripple Voltage |
|-----------------------|----------------|------------------|------------------------------|
| 25 V | 50 mA–3.5 A | ±5% | 100 mA p-p max |
| 12 V | 0 mA–100 mA | ±5% | |
| 5 V | 10 mA–500 mA | ±5% | |

3. Efficiency at full load 85%.
4. STR-G6352 switching frequency : 60 kHz(transformer T71).

| Output Voltage | Current | Tolerance | Output Ripple Voltage |
|-----------------------|----------------|------------------|------------------------------|
| 5 V (analog) | 50 mA–3.0 A | ±5% | 100 mA p-p max. |
| 5 V (digital) | 0 mA–500 mA | ±5% | |
| 12 V (analog) | 0 mA–500 mA | ±5% | |
| 12 V (digital) | 0 mA–300 mA | ±5% | |
| –12 V | 50 mA–100 mA | ±10% | |
| –16 V | 10 mA–100 mA | ±10% | |
| –20 V | 10 mA–100 mA | ±10% | |
| –26 V | 10 mA–100 mA | ±10% | |

5. Current saturation point

$I_{pk} = 3.3 \text{ A}$ at $R_{cs} = 0.3 \Omega$, $I_{\text{saturation}} = 6.4 \text{ A}$. Using a 25% high-temperature derating factor,
 $I_{\text{saturation}} = 4.8 \text{ A}$, current margin = 45%.

3 Transformer Winding Specifications

- Digital video display (DVD) audio amplifier

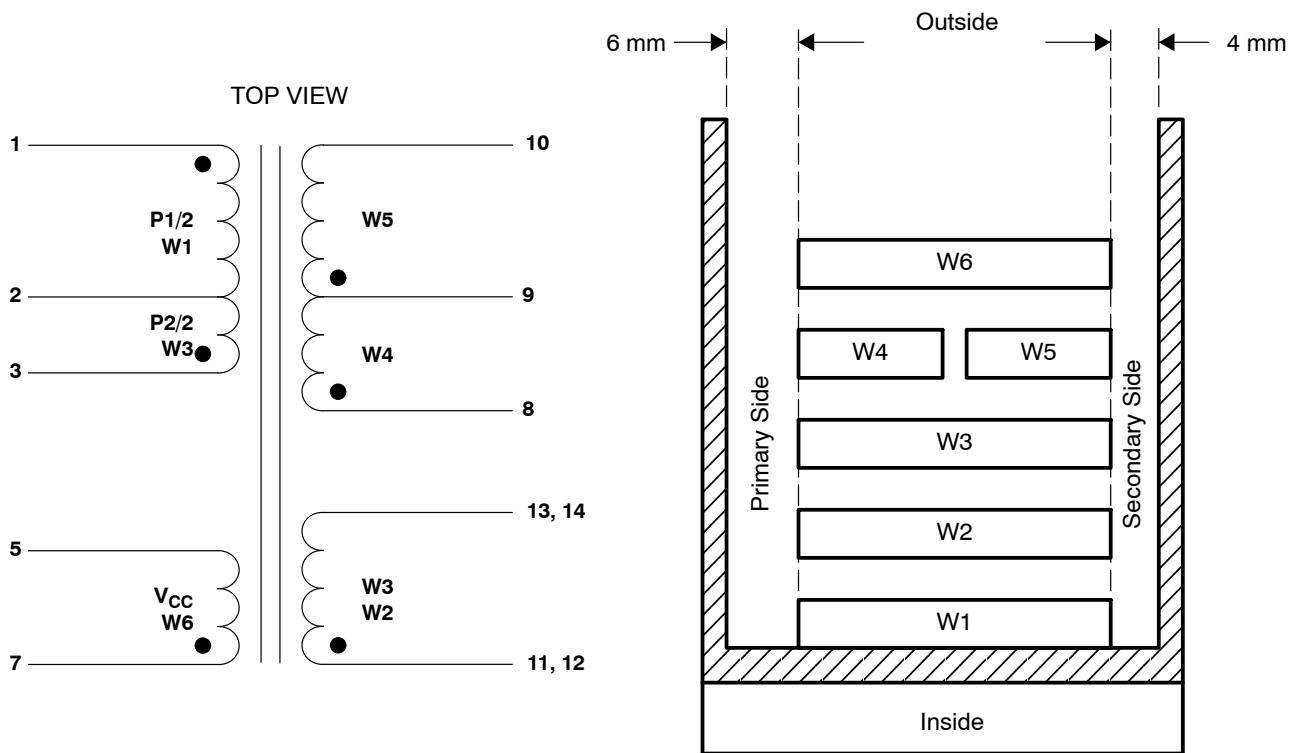


Figure 5. Schematic Diagram

- Winding specification

| WINDING | | TERMINAL | | WIRE DIAMETER (mm) | TURNS | INSULATION | |
|---------|------------|----------|--------|--------------------|-------|------------|---------------------|
| NO. | RATING | START | FINISH | | | TURNS | MATERIAL |
| W1 | P1 | 1 | 2 | 0.5 | 22T | 3T | Polyester film tape |
| W2 | 25 V/3.5 A | 11,12 | 13,14 | 3.5 A Litz | 8T | 3T | Polyester film tape |
| W3 | P2 | 2 | 3 | 0.5 | 22T | 3T | Polyester film tape |
| W4 | 5 V/0.5 A | 8 | 9 | 0.45 | 2T | 3T | Polyester film tape |
| W5 | 12 V/ 0.1A | 8 | 10 | 0.45 | 4T | 3T | Polyester film tape |
| W6 | VCC | 7 | 5 | 0.22 | 5T | 3T | Polyester film tape |

- Core size: EER – 40/42/15 H-type (pin bobbin)

- Electrical characteristic

| CLOSURE | PIN | SPEC. | REMARKS |
|--------------------|-------|------------------------|-------------------------------------|
| INDUCTANCE | 1 – 4 | 400 μ H \pm 5% | 1 kHz, 1 V |
| LEAKAGE INDUCTANCE | 1 – 4 | \pm 10 μ H, max. | All secondary pins shorted together |

- Cut pin: pin 2 (primary side) is not used and is cut from the coil form.

6. DVD receive

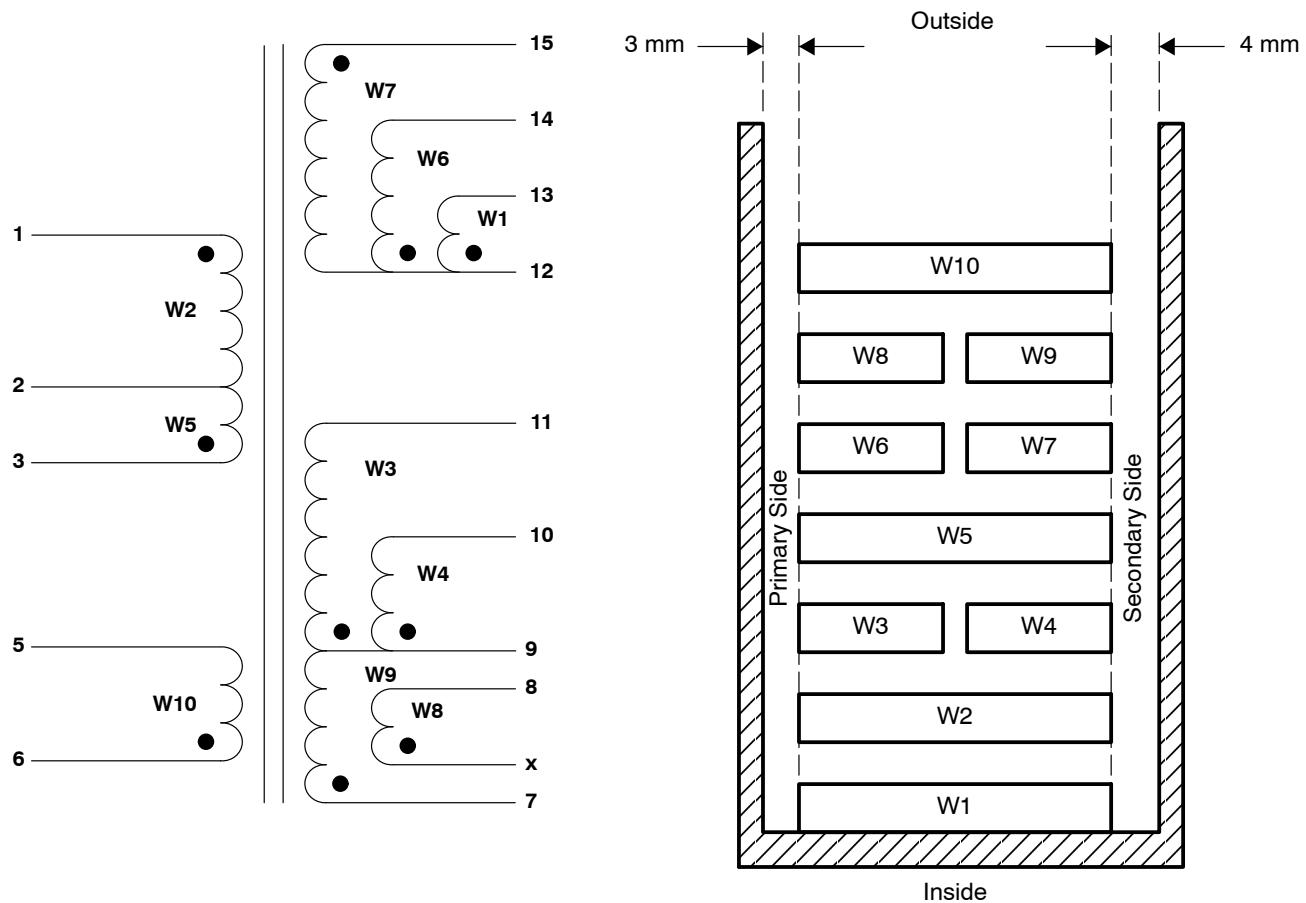


Figure 6. Schematic Diagram

7. Winding specification

8. Core size: EER – 28/28 (5/11 pin bobbin)


9. ELECTRICAL CHARACTERISTIC


| CLOSURE | PIN | SPEC. | REMARKS |
|--------------------|-------|-----------------------------|-------------------------------------|
| Inductance | 1 – 4 | $880 \mu\text{H} \pm 5\%$ | 1 kHz, 1 V |
| Leakage inductance | 1 – 4 | $\pm 20 \mu\text{H}$, max. | All secondary pins shorted together |

10. Cut Pin: Pin 2 and pin 4 (primary side) are not used and are cut from the coil form.

 11. $I_{\text{sat}} = 4.8 \text{ A}$

4 Schematic

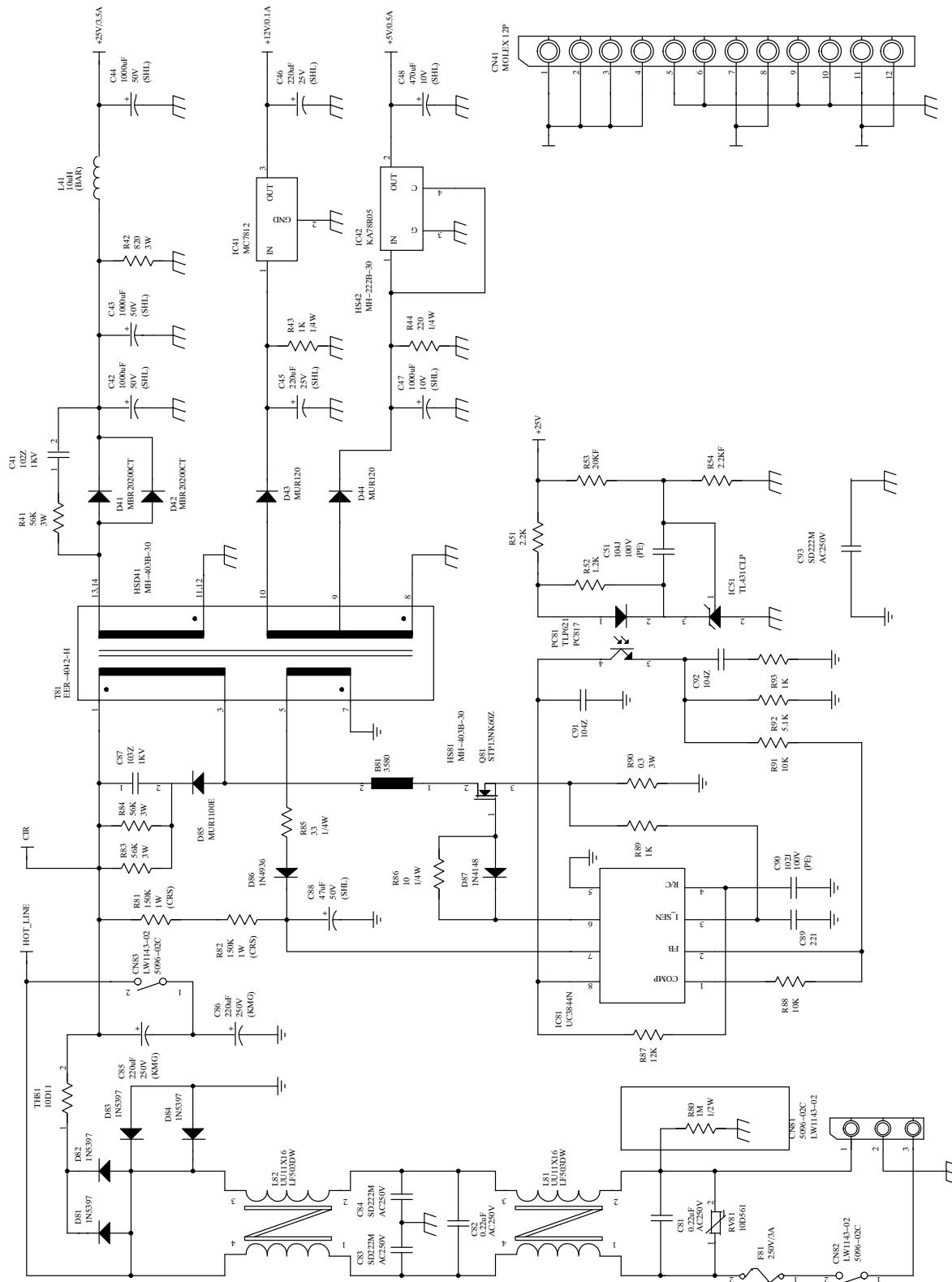

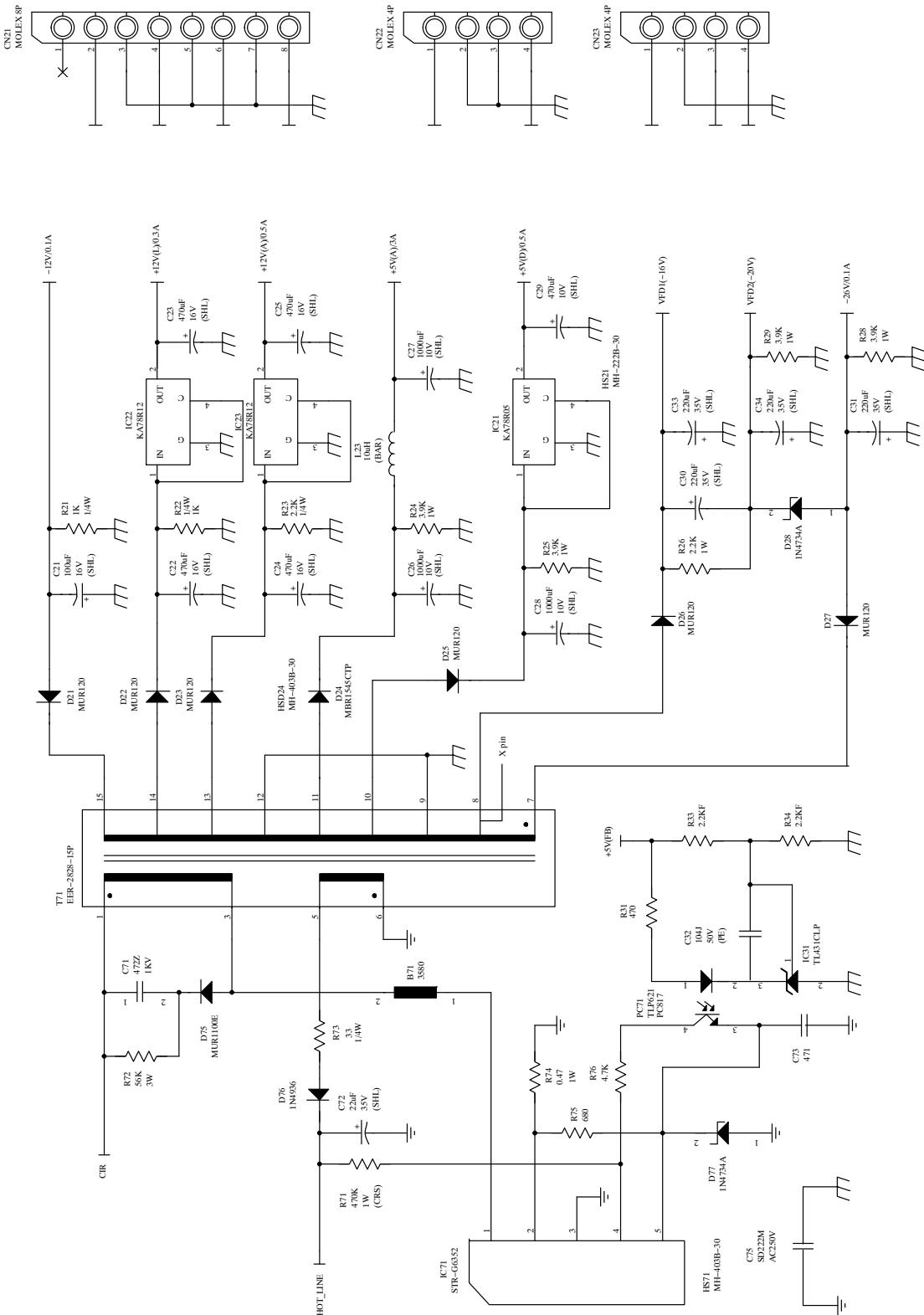

5 PCB Gerber Files

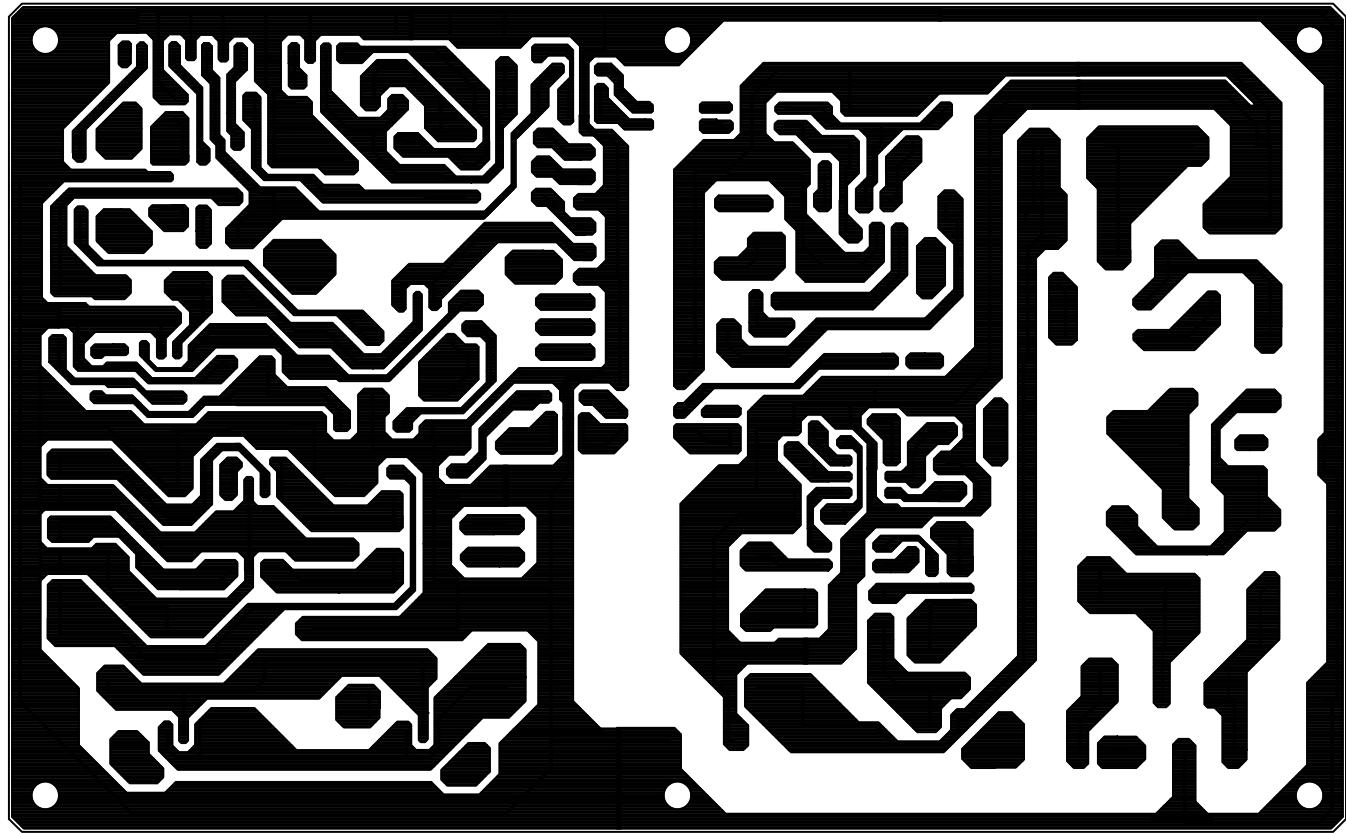


Figure 7. PCB Layout

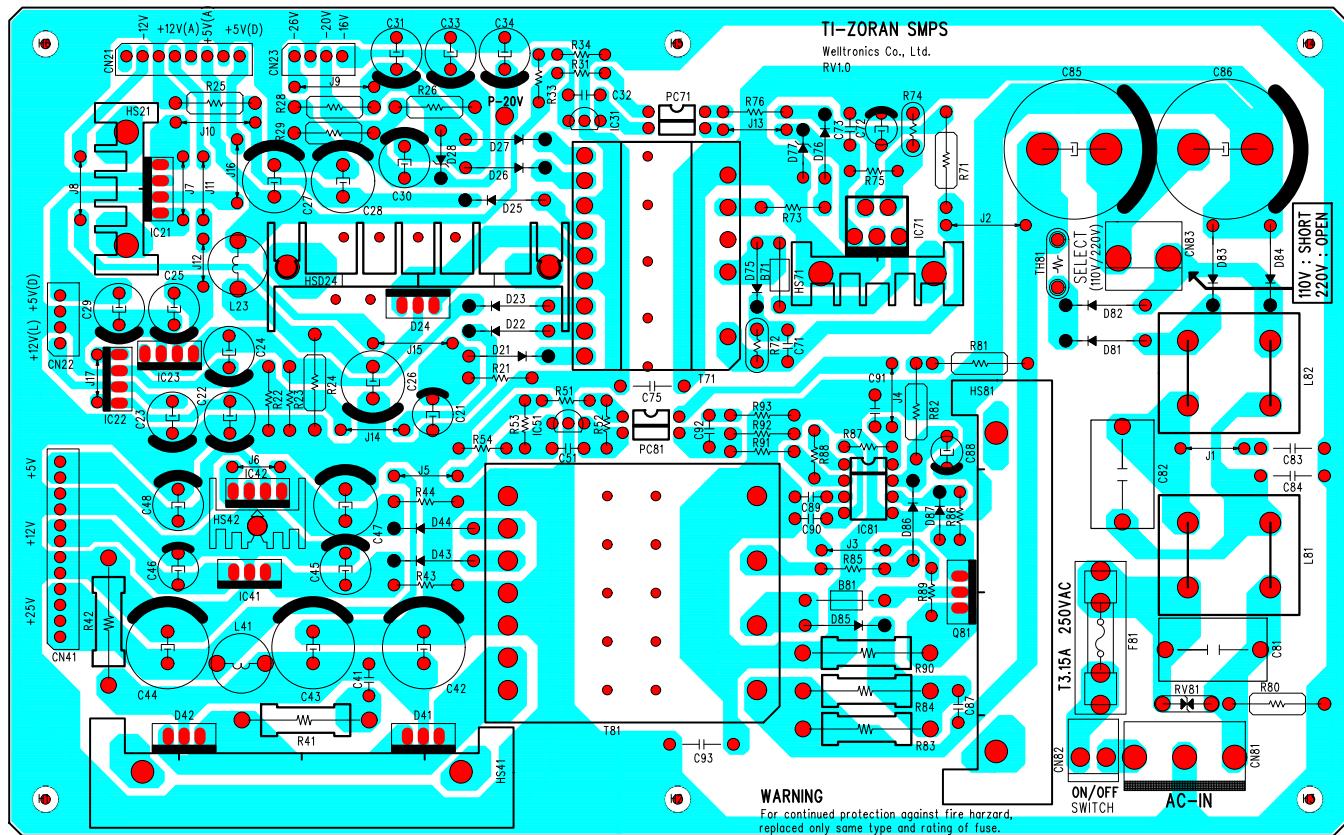


Figure 8. Component Layout

6 Bill of Materials

| NO. | QTY | LOCATION | VALUE | PART NO. | DESCRIPTION |
|-----|-----|--|-------------------|------------|-------------------------|
| 1 | 1 | B71 | 3580 | | Bead |
| 2 | 1 | B81 | 3580 | | Bead |
| 3 | 1 | C21 | 100 μ F/16 V | | Capacitor, electrolytic |
| 4 | 4 | C22, C23, C24, C25 | 470 μ F/16 V | | Capacitor, electrolytic |
| 5 | 3 | C26, C27, C28 | 1000 μ F/10 V | | Capacitor, electrolytic |
| 6 | 1 | C29 | 470 μ F/10 V | | Capacitor, electrolytic |
| 7 | 4 | C30, C31, C33, C34 | 220 μ F/35 V | | Capacitor, electrolytic |
| 8 | 1 | C32 | | 104J | Capacitor, ceramic |
| 9 | 1 | C41 | | 102Z | Capacitor, ceramic |
| 10 | 1 | C42 | 1000 μ F/50 V | | Capacitor, electrolytic |
| 11 | 1 | C43 | 1000 μ F/50 V | | Capacitor, electrolytic |
| 12 | 1 | C44 | 1000 μ F/50 V | | Capacitor, electrolytic |
| 13 | 2 | C45, C46 | 220 μ F/25 V | | Capacitor, electrolytic |
| 14 | 1 | C47 | 1000 μ F/10 V | | Capacitor, electrolytic |
| 15 | 1 | C48 | 470 μ F/10 V | | Capacitor, electrolytic |
| 16 | 1 | C51 | | 104J | Capacitor, ceramic |
| 17 | 1 | C71 | | 472Z | Capacitor, electrolytic |
| 18 | 1 | C72 | 22 μ F/35 V | | Capacitor, electrolytic |
| 19 | 1 | C73 | | 471 | Capacitor, electrolytic |
| 20 | 3 | C75, C83, C84 | | SD222M | Capacitor, ceramic |
| 21 | 2 | C81, C82 | 0.22 μ F | | Capacitor, X2 |
| 22 | 2 | C85, C86 | 220 μ F/250 V | | Capacitor, electrolytic |
| 23 | 1 | C87 | 0.01 μ F/1 kV | 103Z | Capacitor, ceramic |
| 24 | 1 | C88 | 47 μ F/50 V | | Capacitor, electrolytic |
| 25 | 1 | C89 | | 221 | Capacitor, ceramic |
| 26 | 1 | C90 | | 102J | Capacitor, ceramic |
| 27 | 2 | C91, C92 | | 104Z | Capacitor, ceramic |
| 28 | 1 | C93 | | SD222M | Capacitor, ceramic |
| 29 | 1 | CN21 | | MOLEX 8P | |
| 30 | 1 | CN22, CN23 | | MOLEX 4P | |
| 31 | 1 | CN41 | | MOLEX 12P | |
| 32 | 1 | CN81 | | 5096-02C | AC-IN |
| 33 | 2 | CN82, CN83 | | LW1143-02 | ON/OFF, 110/220 |
| 34 | 8 | D21, D22, D23, D25, D26, D27, D43, D44 | 1 A, 200 V | MUR120 | UFD |
| 35 | 1 | D24 | 15 A, 45 V | MBR1545CTP | SCHD |
| 36 | 2 | D28, D77 | 5.6 V | 1N4734A | Zener diode |
| 37 | 1 | D41, D42 | | MBR20200CT | SCHD, 20 A, 200 V |
| 38 | 2 | D75, D85 | | MUR1100E | UFD, 1 A, 1000 V |
| 39 | 2 | D76, D86 | | 1N4936 | SD, 1 A, 400 V |
| 40 | 4 | D81, D82, D83, D84 | 1.5 A, 600 V | 1N5397 | SD |
| 41 | 1 | D87 | 0.15 A, 75 V | 1N4148 | SWD |
| 42 | 1 | F81 | 250 V/3 A | | FUSE |
| 43 | 2 | HS21, HS42 | | MH-222B-30 | |
| 44 | 4 | HS71, HS81, HSD24, HSD41 | | MH-403B-30 | |

| NO. | QTY | LOCATION | VALUE | PART NO. | DESCRIPTION |
|-----|-----|--------------------|---------------------------------|--------------|---------------|
| 45 | 1 | IC21 | 5 V | KA78R05 | REG |
| 46 | 2 | IC22, IC23 | 12 V | KA78R12 | REG |
| 47 | 1 | IC31 | | TL431CLP | |
| 48 | 1 | IC41 | 12 V | MC7812 | REG |
| 49 | 1 | IC42 | 5 V | KA78R05 | REG |
| 50 | 1 | IC51 | TL431CLP | | |
| 51 | 1 | IC71 | | STR-G6352 | PWM+FET |
| 52 | 1 | IC81 | | UC3844N | PWM CTRL |
| 53 | 2 | L23, L41 | 10 μ H | | |
| 54 | 2 | L81, L82 | | UU11X16 | |
| 55 | 2 | PC71, PC81 | | TLP621 | |
| 56 | 1 | Q81 | 13 A, 600 V | STP13NK60Z | N-channel FET |
| 57 | 3 | R21, R22, R43 | $\frac{1}{4}$ W, 1 k Ω | | Resistor |
| 58 | 1 | R23, R51 | $\frac{1}{4}$ W, 2.2 k Ω | | Resistor |
| 59 | 4 | R24, R25, R28, R29 | 1 W, 3.9 k Ω | | Resistor |
| 60 | 1 | R26 | 1 W, 2.2 k Ω | | Resistor |
| 61 | 1 | R31 | $\frac{1}{4}$ W, 470 | | Resistor |
| 62 | 3 | R33, R34, R54 | 1/8 W, 2.2 k Ω | | Resistor |
| 63 | 4 | R41, R72, R83, R84 | 3W, 56 k Ω | | Resistor |
| 64 | 1 | R42 | 3 W, 820 | | Resistor |
| 65 | 1 | R44 | $\frac{1}{4}$ W, 220 Ω | | Resistor |
| 66 | 1 | R52 | $\frac{1}{4}$ W, 1.2 k Ω | | Resistor |
| 67 | 1 | R53 | 1/8 W, 20 k Ω | | Resistor |
| 68 | 1 | R71 | 1 W, 470 k Ω | | Resistor |
| 69 | 1 | R73 | $\frac{1}{4}$ W, 33 Ω | | Resistor |
| 70 | 1 | R74 | 1 W, 0.47 Ω | | Resistor |
| 71 | 1 | R75 | $\frac{1}{4}$ W, 680 Ω | | Resistor |
| 72 | 1 | R76 | $\frac{1}{4}$ W, 4.7 k Ω | | Resistor |
| 73 | 1 | R80 | 1 W, 1 M Ω | | Resistor |
| 74 | 2 | R81, R82 | 1 W, 150 k Ω | | Resistor |
| 75 | 1 | R85 | $\frac{1}{4}$ W, 33 Ω | | Resistor |
| 76 | 1 | R86 | $\frac{1}{4}$ W, 10 Ω | | Resistor |
| 77 | 1 | R87 | $\frac{1}{4}$ W, 12 k Ω | | Resistor |
| 78 | 1 | R88, R91 | $\frac{1}{4}$ W, 10 k Ω | | Resistor |
| 79 | 2 | R89, R93 | $\frac{1}{4}$ W, 1 k Ω | | Resistor |
| 80 | 1 | R90 | 3 W, 0.3 Ω | | Resistor |
| 81 | 1 | R92 | $\frac{1}{4}$ W, 5.1 k Ω | | Resistor |
| 82 | 1 | T71 | | EER-2828-15P | Transformer |
| 83 | 1 | T81 | | EER-4042-H | Transformer |
| 84 | 1 | TH81 | | 10D11 | Thermistor |

7 SMPS Board

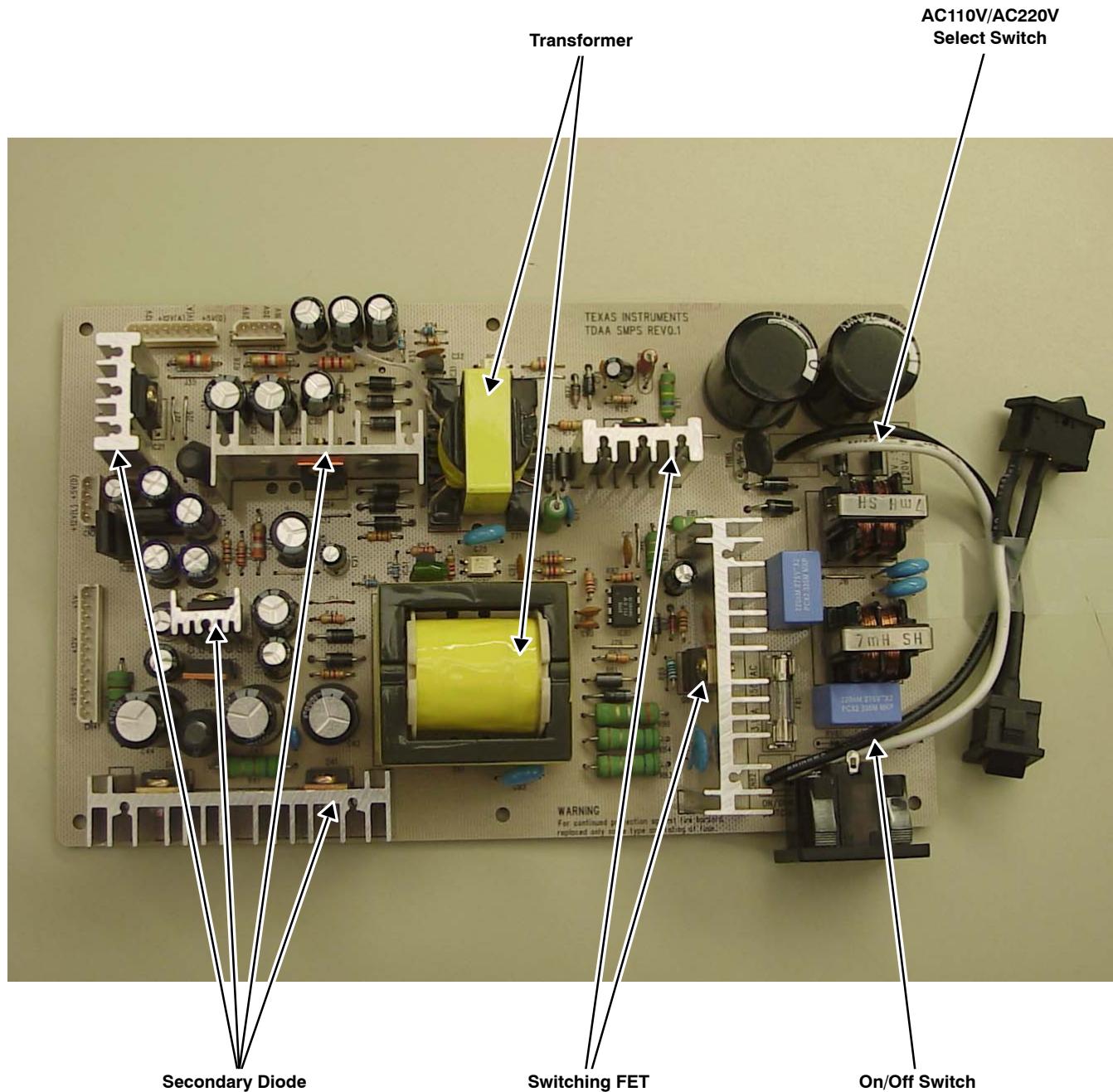


Figure 9. Component Side of Board

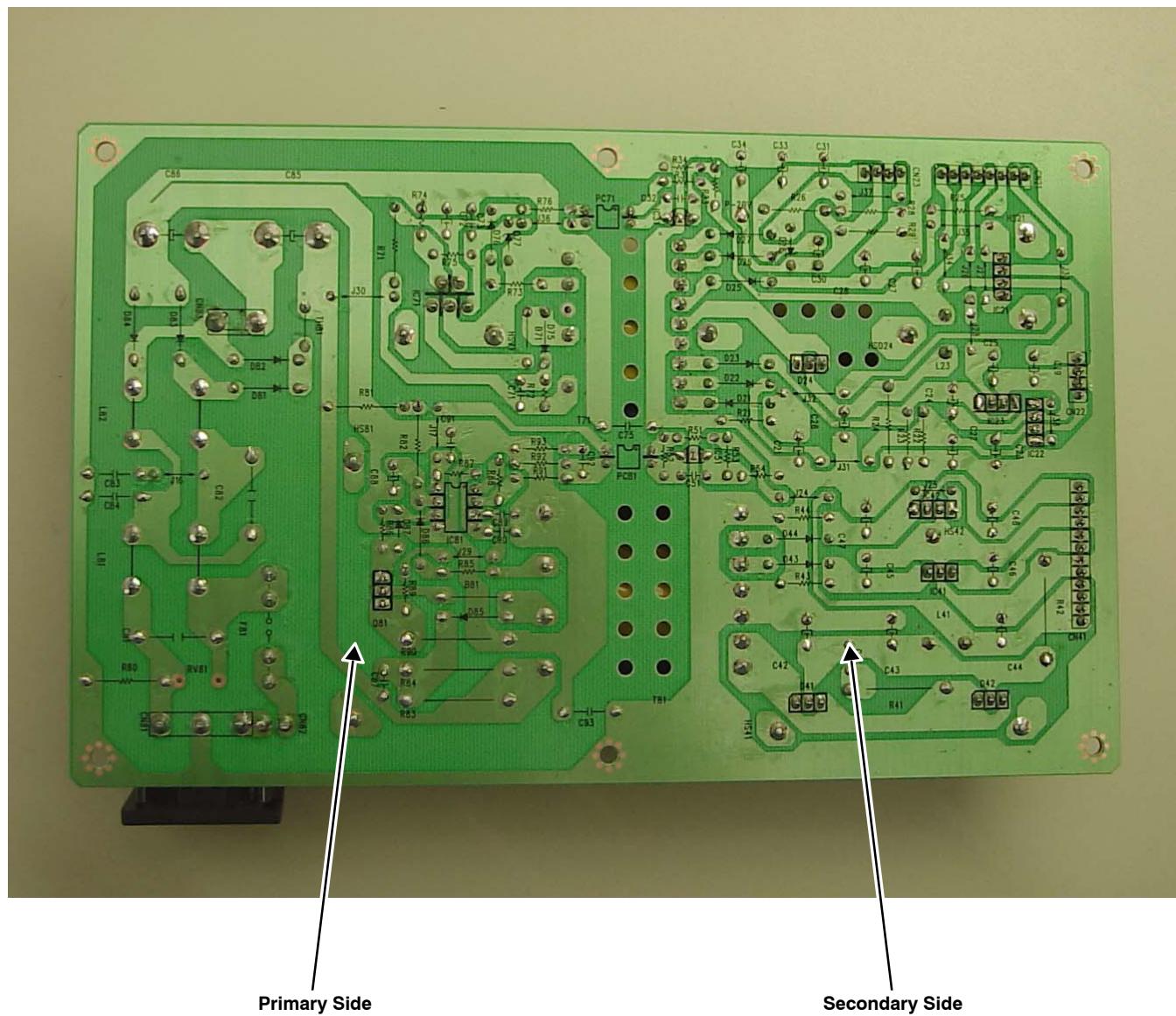


Figure 10. Pattern Side of Board

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

| | |
|------------------------|--|
| Audio | www.ti.com/audio |
| Amplifiers | amplifier.ti.com |
| Data Converters | dataconverter.ti.com |
| DLP® Products | www.dlp.com |
| DSP | dsp.ti.com |
| Clocks and Timers | www.ti.com/clocks |
| Interface | interface.ti.com |
| Logic | logic.ti.com |
| Power Mgmt | power.ti.com |
| Microcontrollers | microcontroller.ti.com |
| RFID | www.ti-rfid.com |
| OMAP Mobile Processors | www.ti.com/omap |
| Wireless Connectivity | www.ti.com/wirelessconnectivity |

Applications

| | |
|-------------------------------|--|
| Automotive and Transportation | www.ti.com/automotive |
| Communications and Telecom | www.ti.com/communications |
| Computers and Peripherals | www.ti.com/computers |
| Consumer Electronics | www.ti.com/consumer-apps |
| Energy and Lighting | www.ti.com/energy |
| Industrial | www.ti.com/industrial |
| Medical | www.ti.com/medical |
| Security | www.ti.com/security |
| Space, Avionics and Defense | www.ti.com/space-avionics-defense |
| Video and Imaging | www.ti.com/video |

[TI E2E Community Home Page](#)

[e2e.ti.com](#)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2012, Texas Instruments Incorporated