



TPS92515-Q1 LED Buck Converter

TI reference design number: PMP20178 Rev A

Input: 9V to 16V

Output: 6V or 9V @ 1A

DC – DC Test Results

Table of Contents

1	Circuit Description.....	3
2	Photos	3
3	Efficiency	5
4	Thermal Tests.....	6
4.1	12V in, 2 LEDs at 1A	6
4.2	12V in, 3 LEDs at 1A	7
5	Startup and Shutdown Behavior	8
5.1	Turn-on from Vin.....	8
6	Switching and Ripple	10
6.1	Switching and Ripple	10
7	Load Transient Response.....	12
7.1	Load Transient Response.....	12
8	PWM Dimming.....	14
8.1	PWM Dimming.....	14
9	No Load Cycling	15
9.1	No load cycling	15


1 Circuit Description


PMP20487 is a hysteretic buck converter which drives LEDs at up to 1A from an input voltage of 9V to 16V. This design uses the TPS92515-Q1 buck LED driver set for a constant off-time of 1 μ s. Features include integrated N-channel FET, high-side current sense, and shunt FET PWM dimming capability.

At tests were performed at room temperature on an open bench. LED loads were CITILIGHT series 773F, three strings of 2 or 3 series LEDs with a 1 ohm ballast resistor in each string.

2 Photos

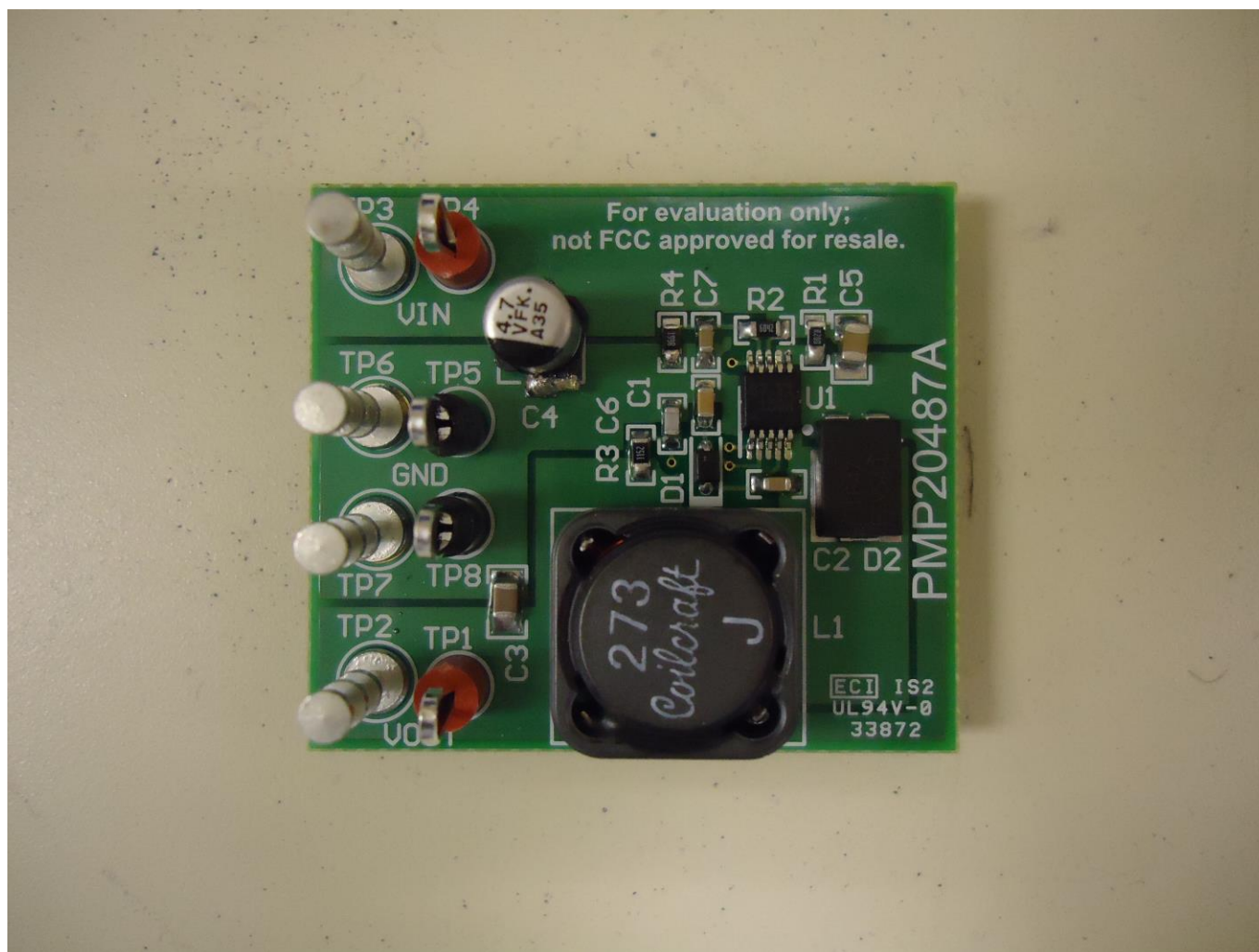
The photographs below show the PMP20487 Rev A printed circuit board assembly. This is a 2 layer board using 1 ounce copper. The overall board dimensions are 30.0 mm x 34.3 mm.



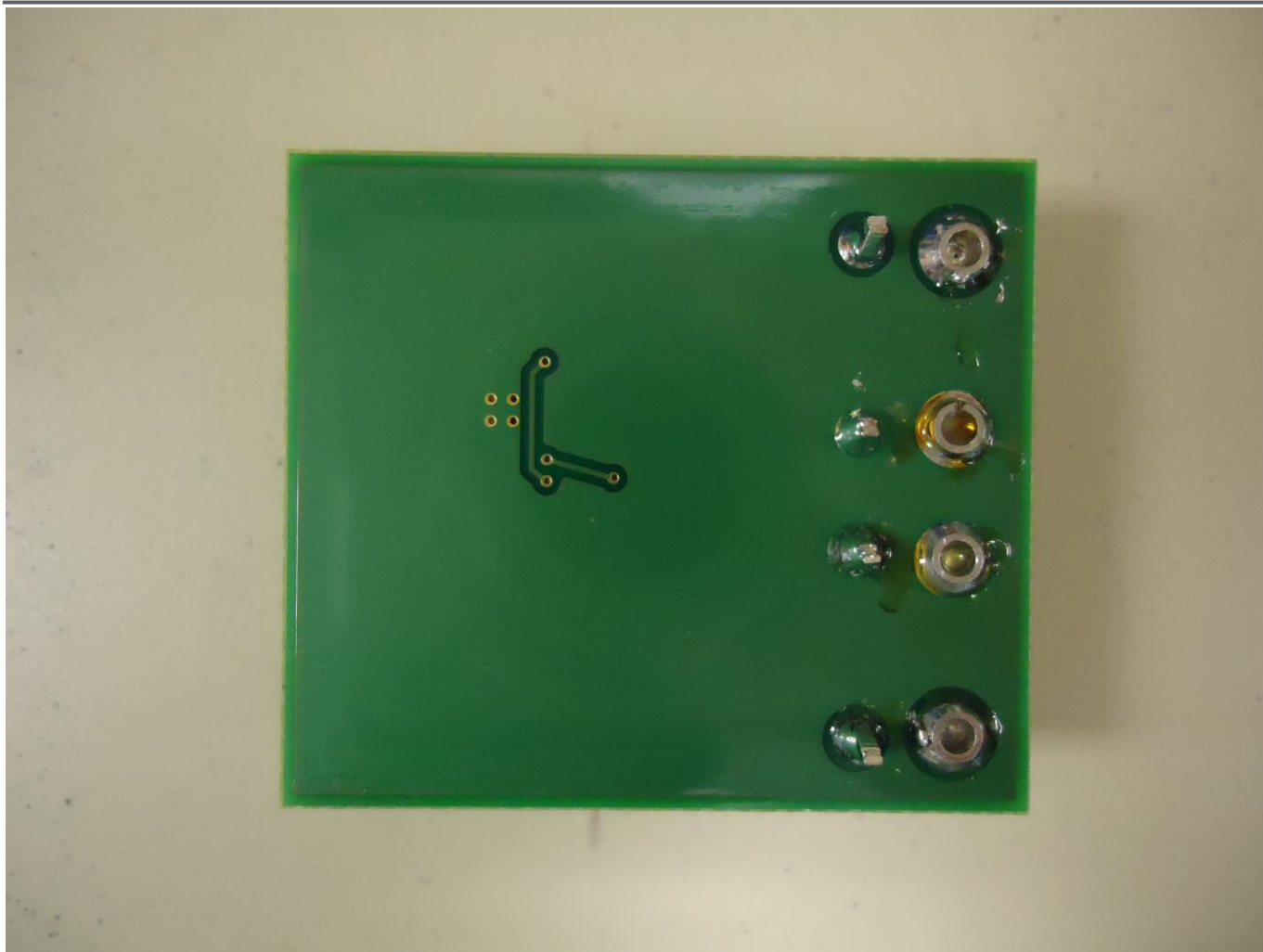

3 Efficiency

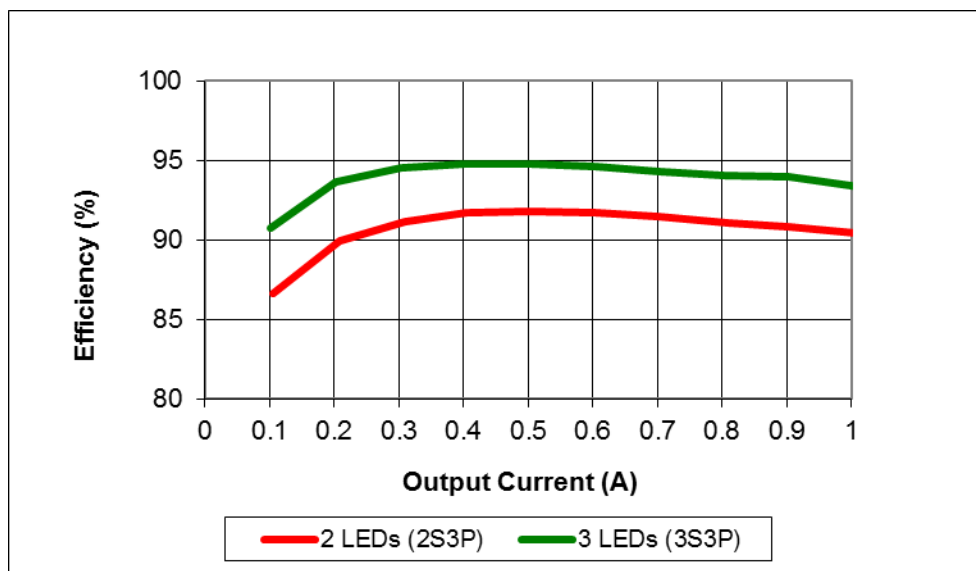The efficiency data is shown in the tables and graph below for 12V input. A 10k linear pot at the IADJ pin was used to set the current.




Vin (V)	Iin (A)	Vout (V)	Iout (A)	Efficiency (%)	Pin (W)	Pout (W)	Losses (W)
12.006	0.0547	5.366	0.1060	86.61	0.657	0.569	0.088
12.006	0.1063	5.527	0.2076	89.91	1.276	1.147	0.129
12.005	0.1603	5.662	0.3099	91.18	1.924	1.755	0.170
12.005	0.2124	5.771	0.4053	91.73	2.550	2.339	0.211
12.005	0.2668	5.874	0.5006	91.81	3.203	2.941	0.262
12.005	0.3281	5.976	0.6043	91.68	3.939	3.611	0.328
12.005	0.3869	6.066	0.7005	91.48	4.645	4.249	0.396
12.004	0.4558	6.158	0.8094	91.10	5.471	4.984	0.487
12.004	0.5166	6.238	0.9031	90.84	6.201	5.634	0.568
12.003	0.6176	6.359	1.0517	90.22	7.413	6.688	0.725

Vin (V)	Iin (A)	Vout (V)	Iout (A)	Efficiency (%)	Pin (W)	Pout (W)	Losses (W)
12.005	0.0754	8.044	0.1021	90.73	0.905	0.821	0.084
12.005	0.1499	8.279	0.2035	93.62	1.800	1.685	0.115
12.005	0.2256	8.458	0.3026	94.50	2.708	2.559	0.149
12.005	0.3039	8.636	0.4003	94.76	3.648	3.457	0.191
12.004	0.3901	8.782	0.5053	94.76	4.683	4.438	0.245
12.003	0.4750	8.908	0.6054	94.59	5.701	5.393	0.309
12.002	0.5620	9.023	0.7050	94.31	6.745	6.361	0.384
12.002	0.6510	9.126	0.8051	94.04	7.813	7.347	0.466
12.002	0.7416	9.255	0.9036	93.96	8.901	8.363	0.538
12.003	0.8861	9.379	1.0553	93.06	10.636	9.898	0.738


4 Thermal Tests

All tests were performed at room temperature on an open bench.

4.1 12V in, 2 LEDs at 1A

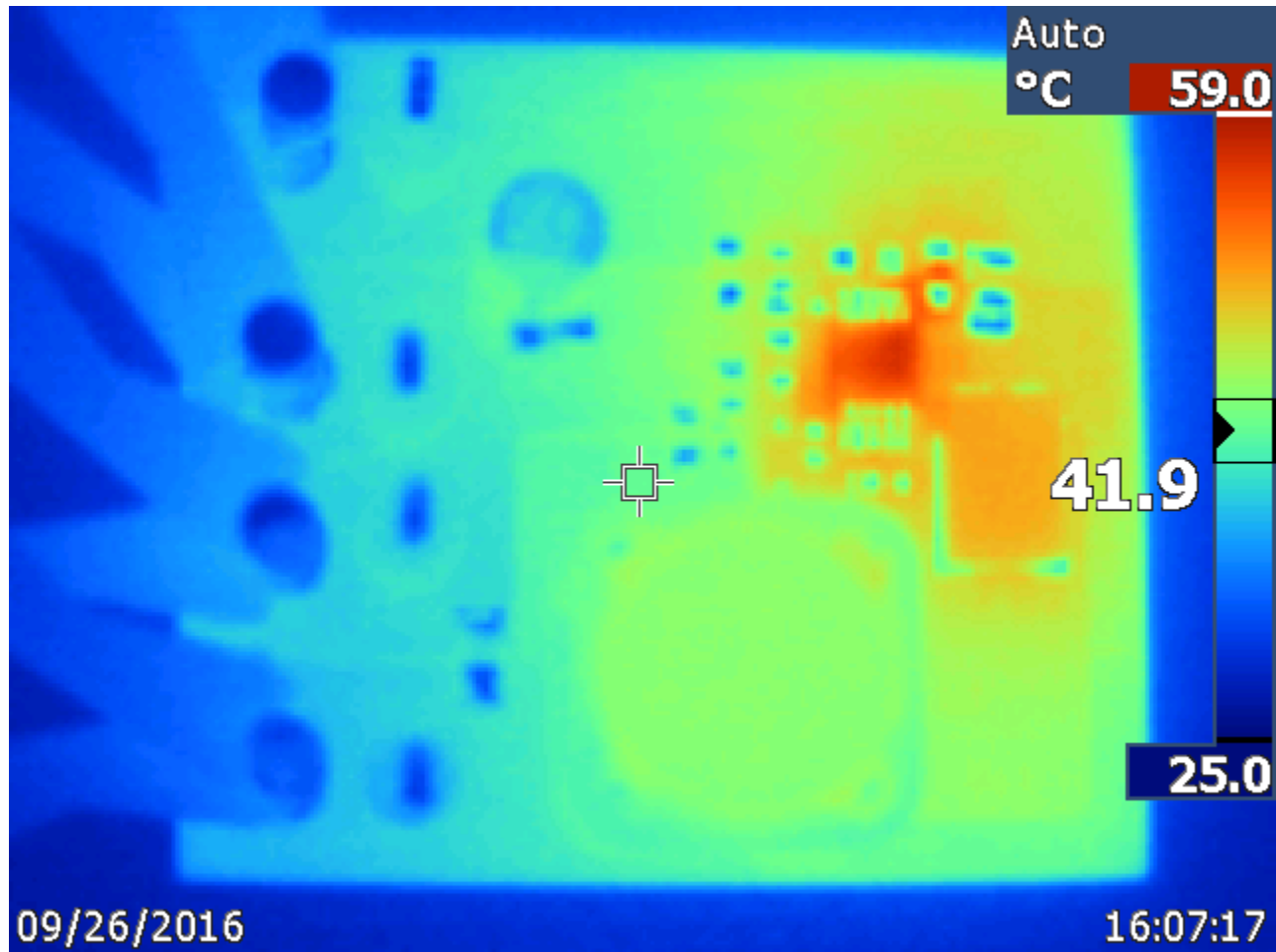



4.2 12V in, 3 LEDs at 1A

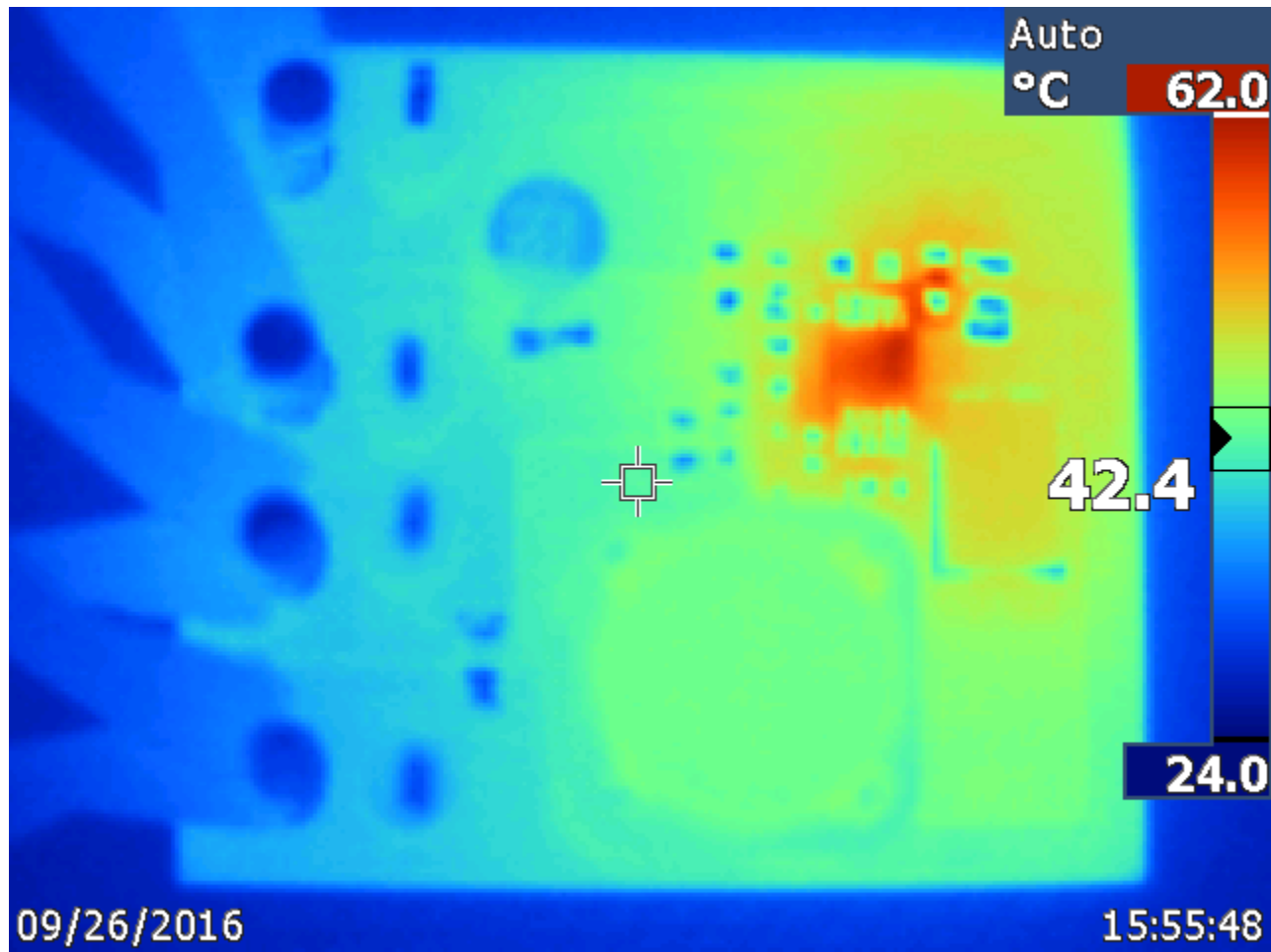


5 Startup and Shutdown Behavior

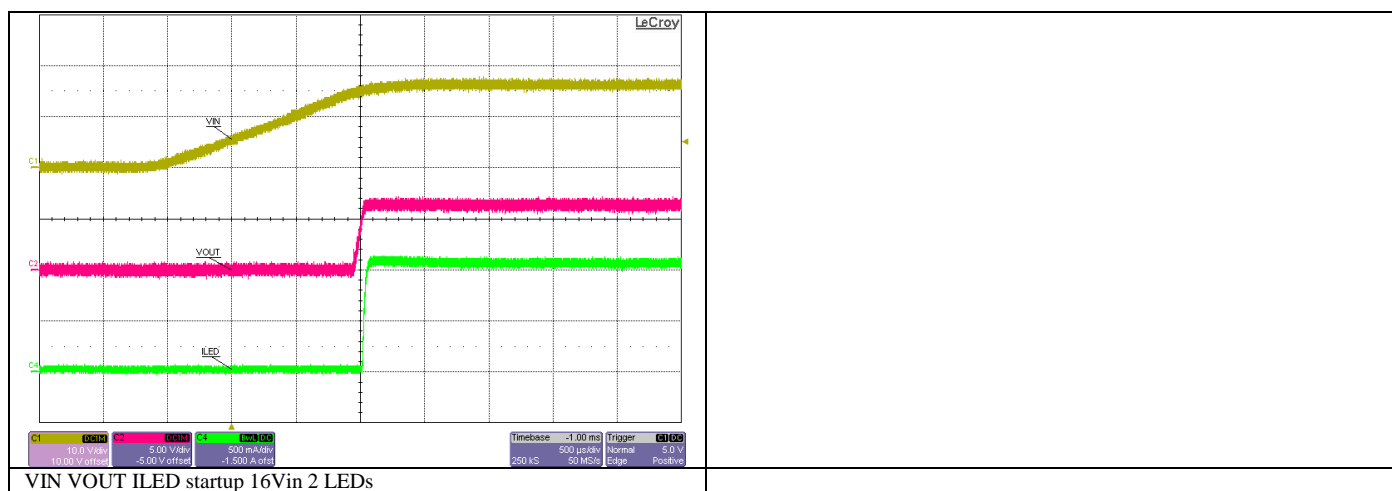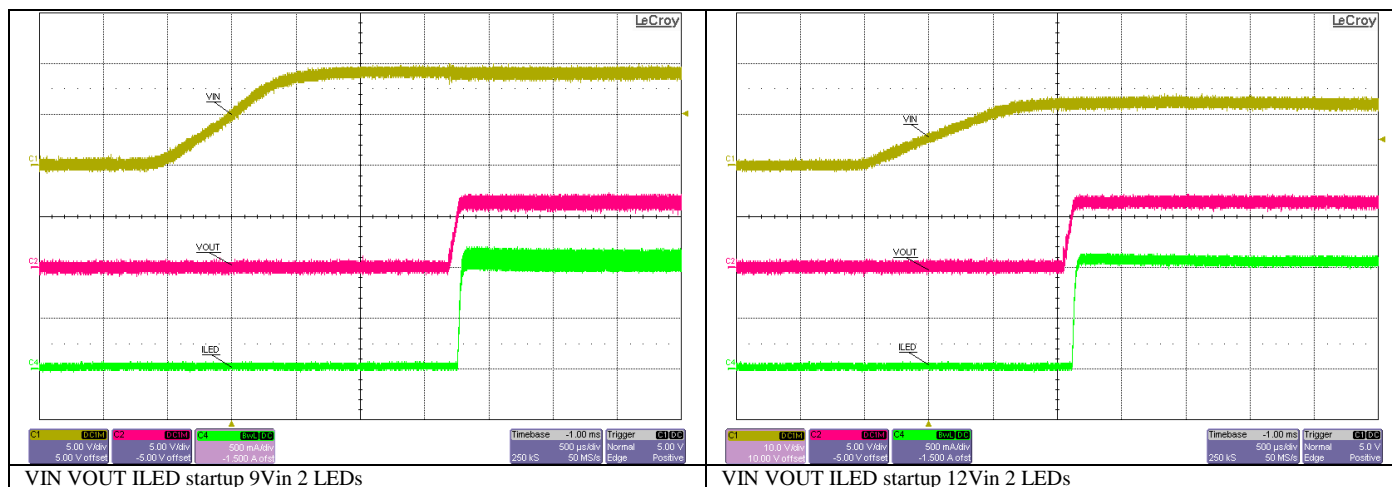5.1 Turn-on from Vin


The output voltage and current is well controlled at turn-on.




PMP20487 Rev A Test Results

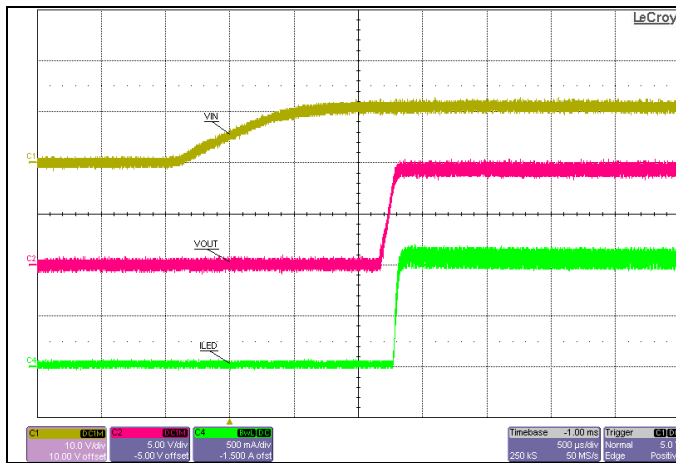

VIN VOUT ILED startup 11Vin 3 LEDs

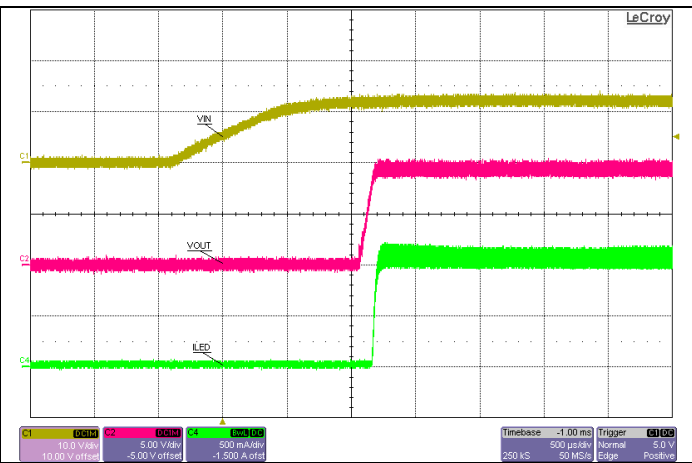

VIN VOUT ILED startup 12Vin 3 LEDs



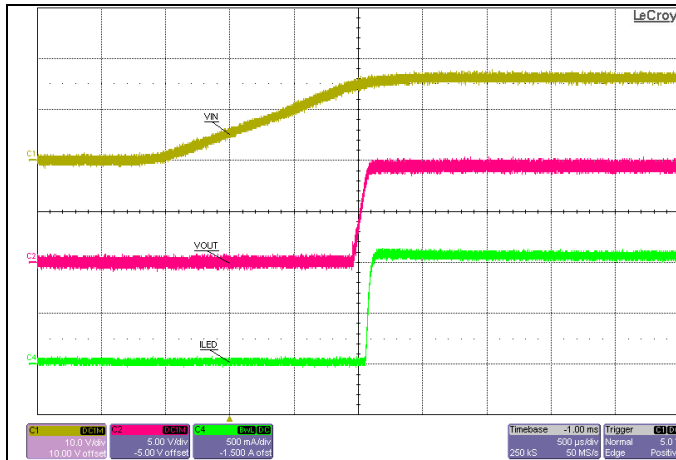


VIN VOUT ILED startup 16Vin 3 LEDs


6 Switching and Ripple

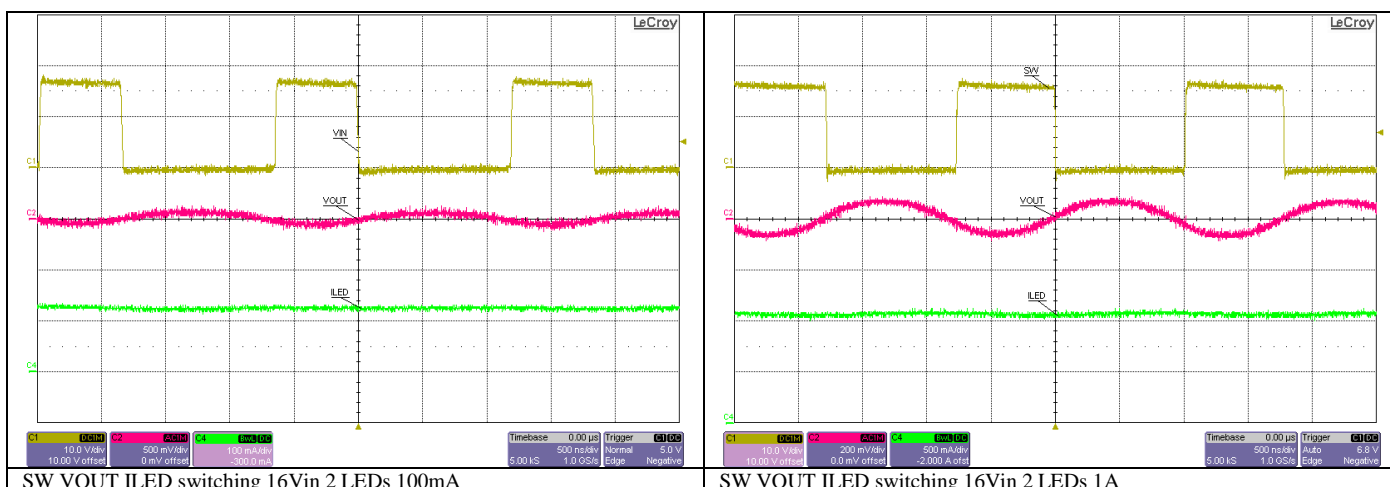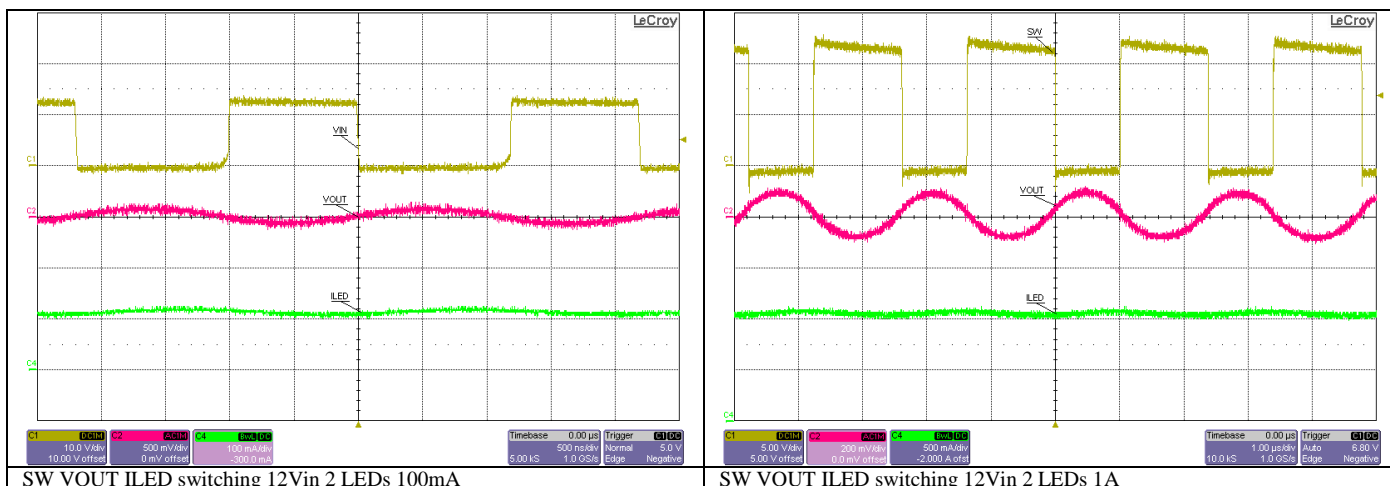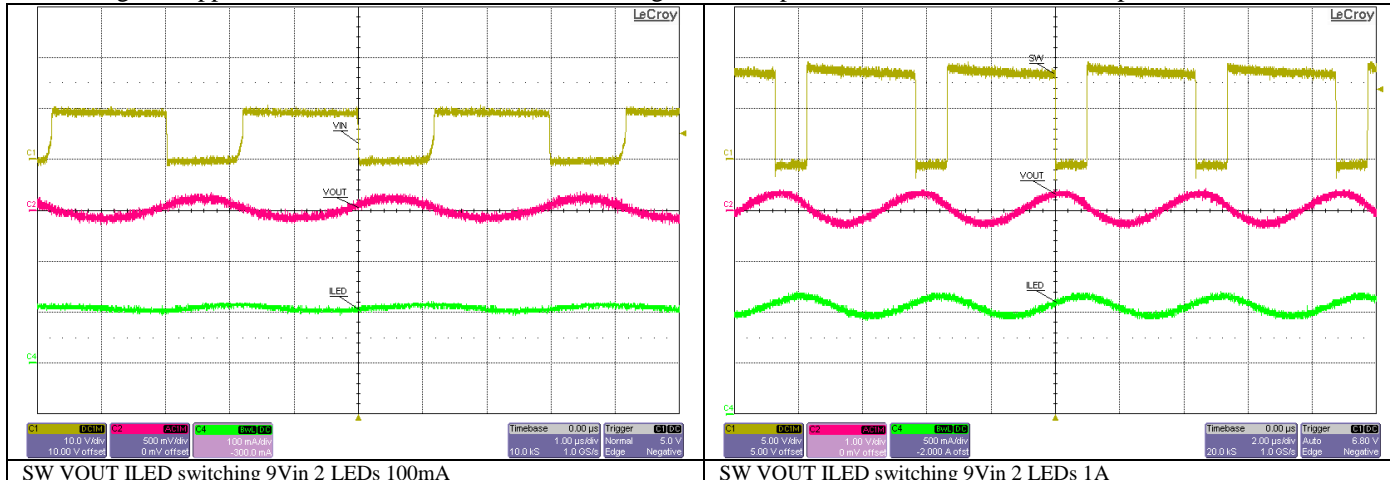6.1 Switching and Ripple


Switching and ripple were measured at full bandwidth using 500 MHz probes and 350 MHz oscilloscope.




PMP20487 Rev A Test Results

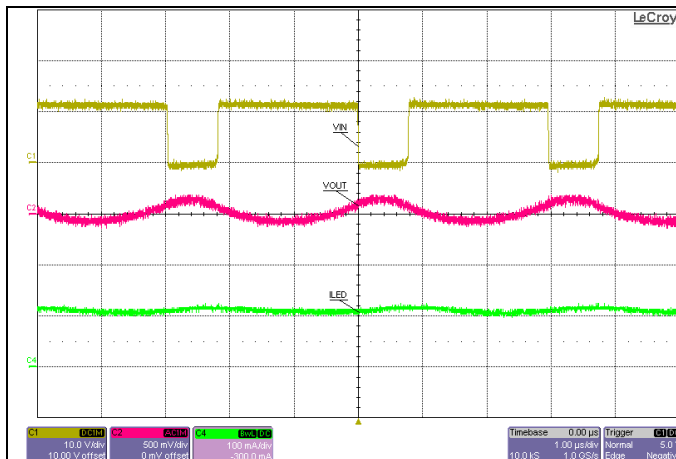

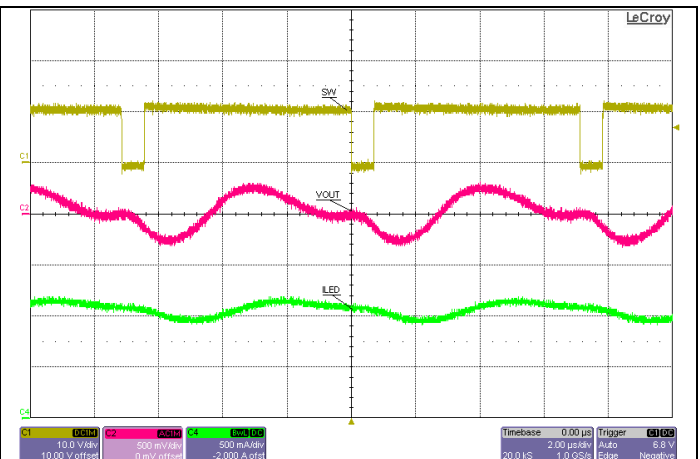
SW VOUT ILED switching 11Vin 3 LEDs 100mA




SW VOUT ILED switching 11Vin 3 LEDs 1A

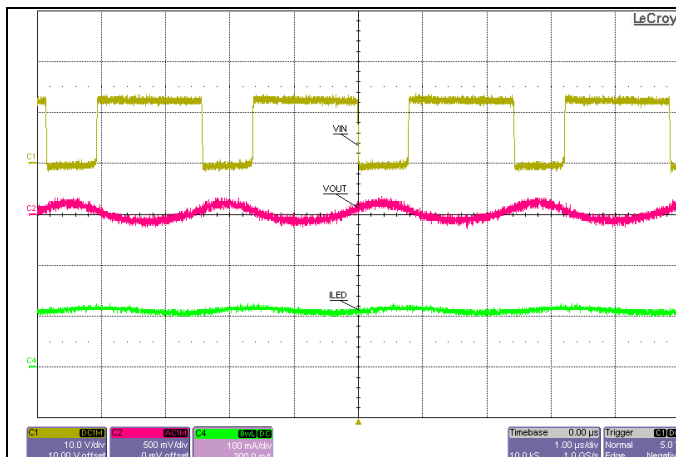

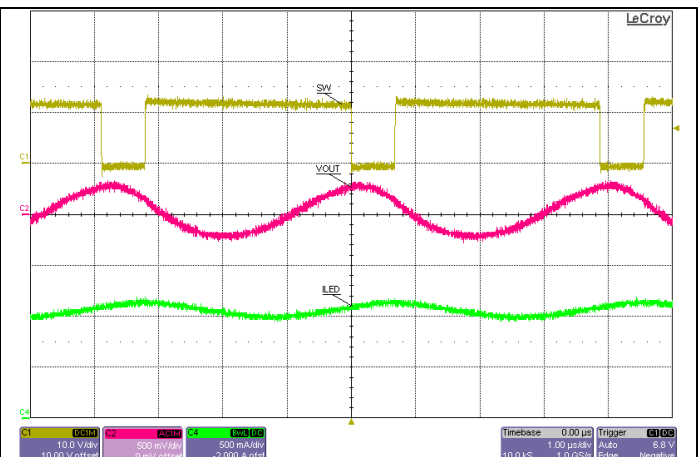
SW VOUT ILED switching 12Vin 3 LEDs 100mA



SW VOUT ILED switching 12Vin 3 LEDs 1A

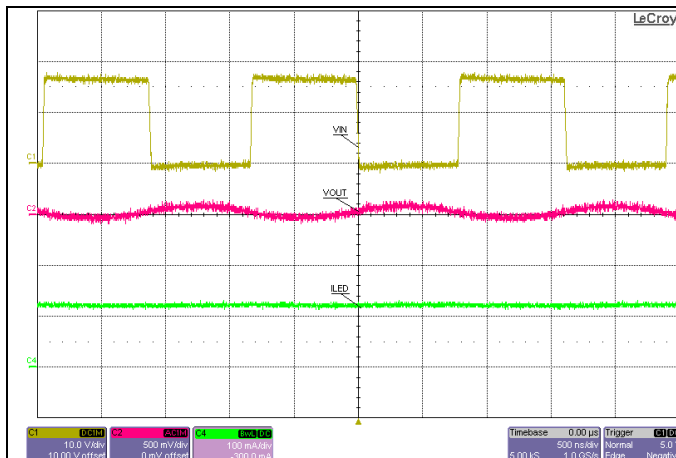

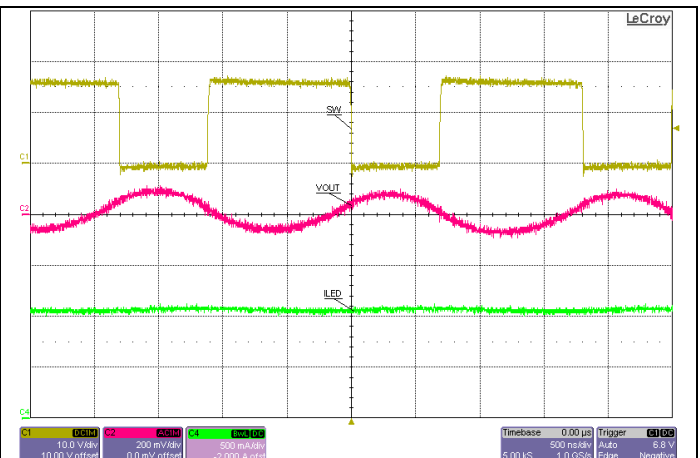SW VOUT ILED switching 16Vin 3 LEDs 100mA





SW VOUT ILED switching 16Vin 3 LEDs 1A


7 Load Transient Response

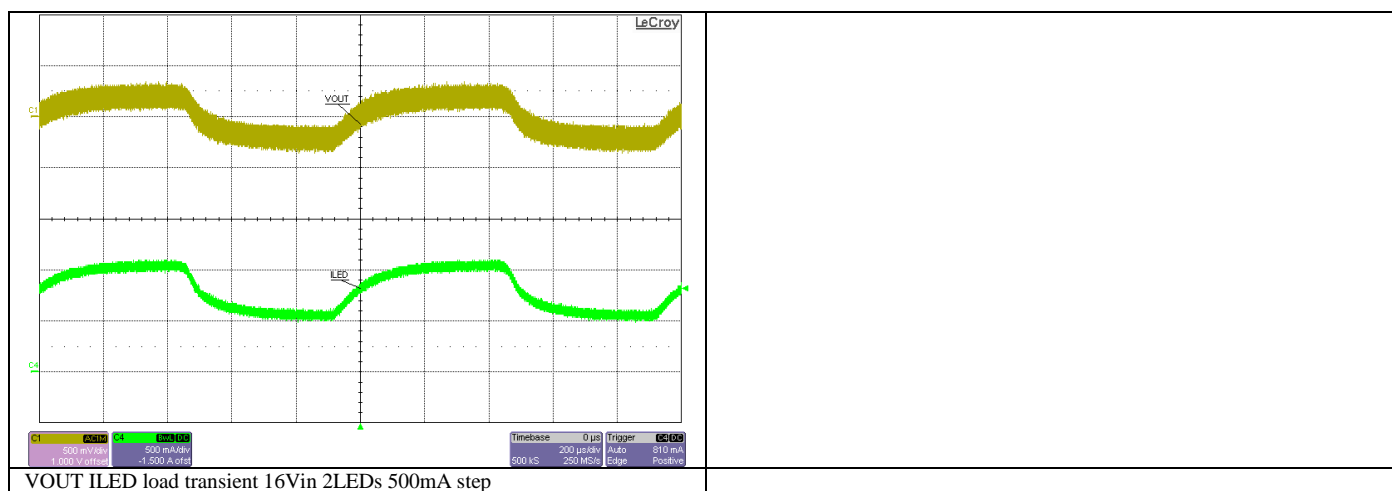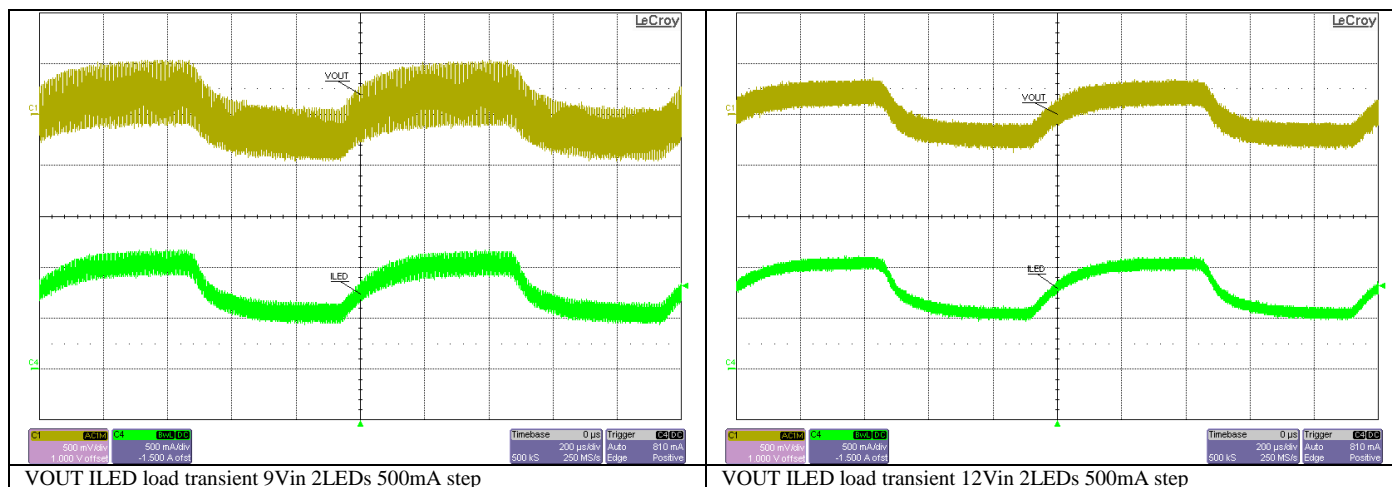7.1 Load Transient Response


A constant current load in parallel with the LEDs was used to step the current.




PMP20487 Rev A Test Results

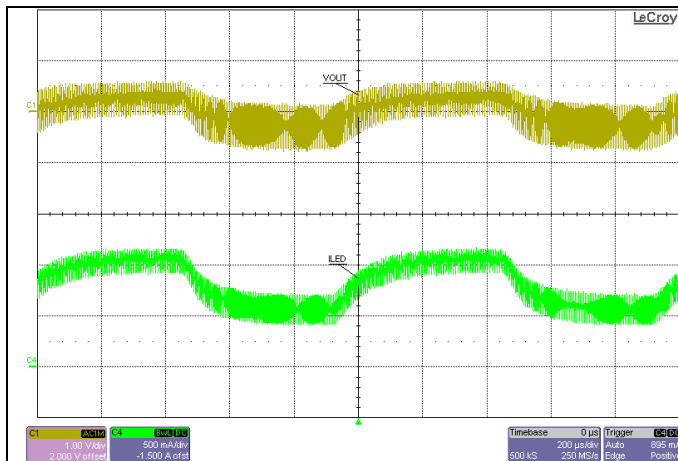

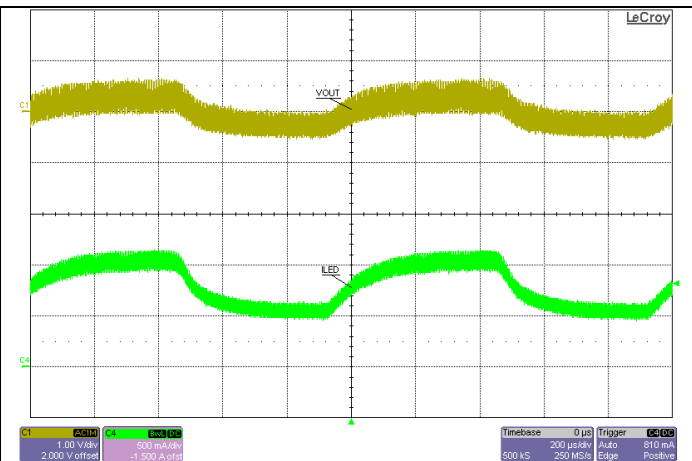VOUT ILED load transient 11Vin 3LEDs 500mA step



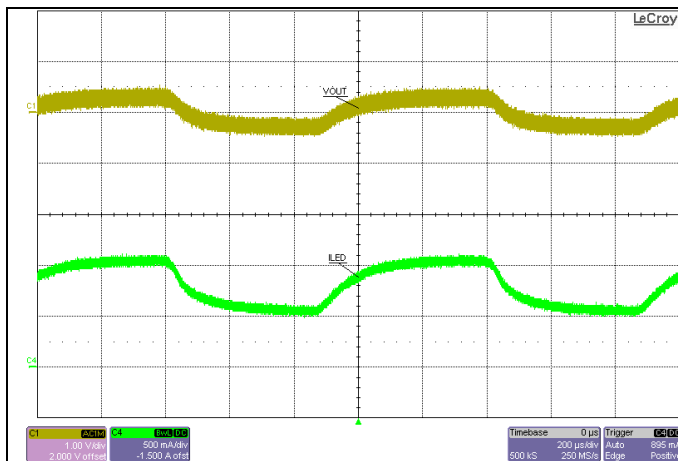VOUT ILED load transient 12Vin 3LEDs 500mA step






VOUT ILED load transient 16Vin 3LEDs 500mA step



8 PWM Dimming

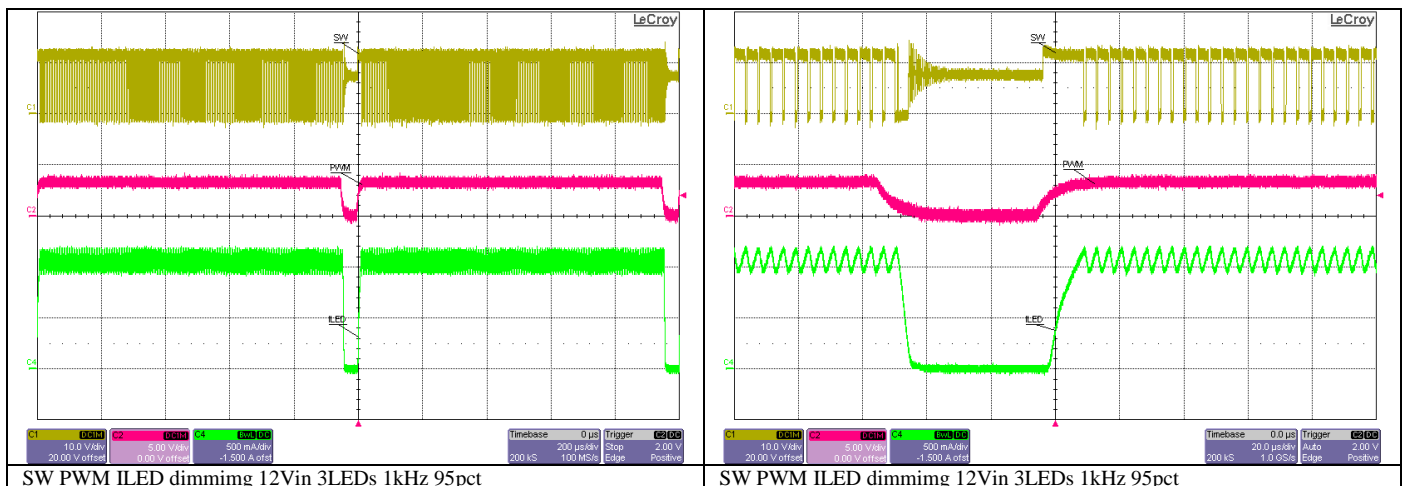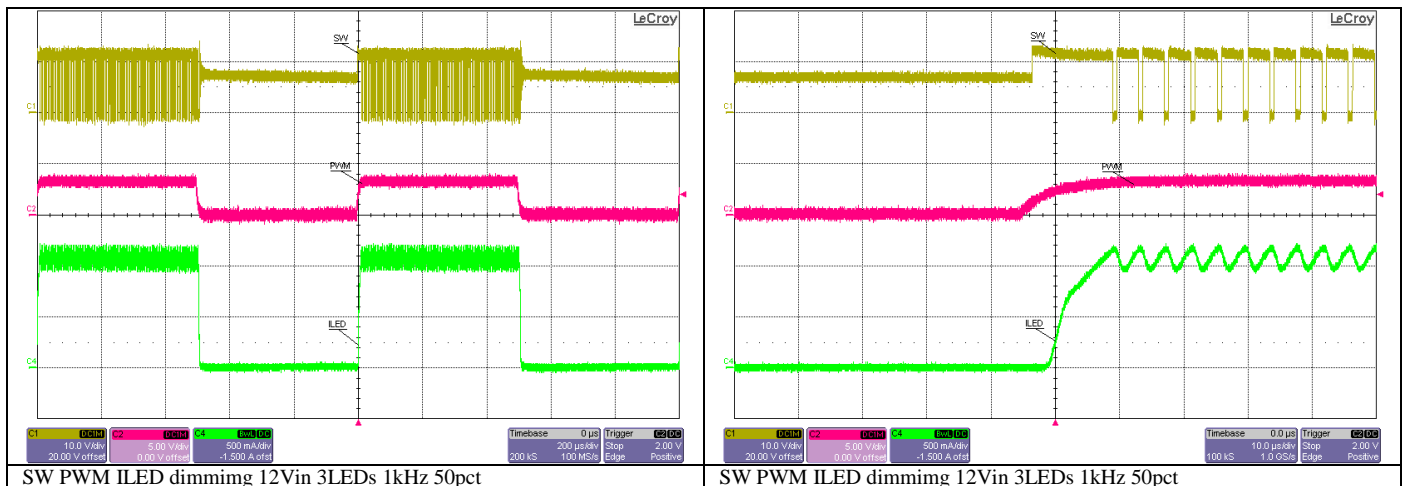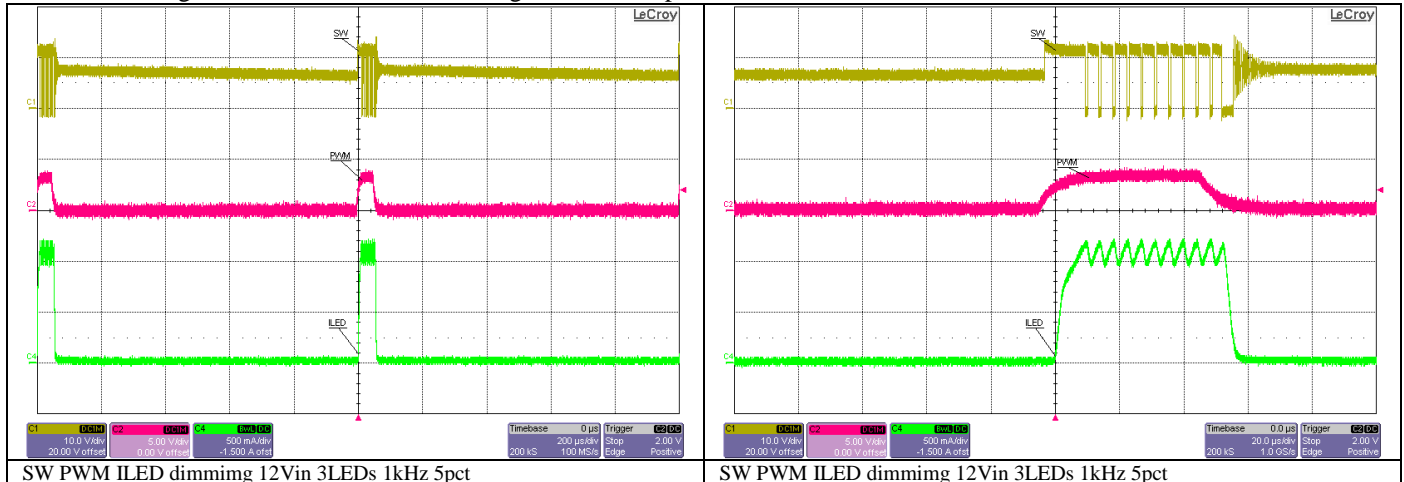8.1 PWM Dimming




A 3.3V 1 kHz generator was used for dimming at the PWM pin.



9 No Load Cycling

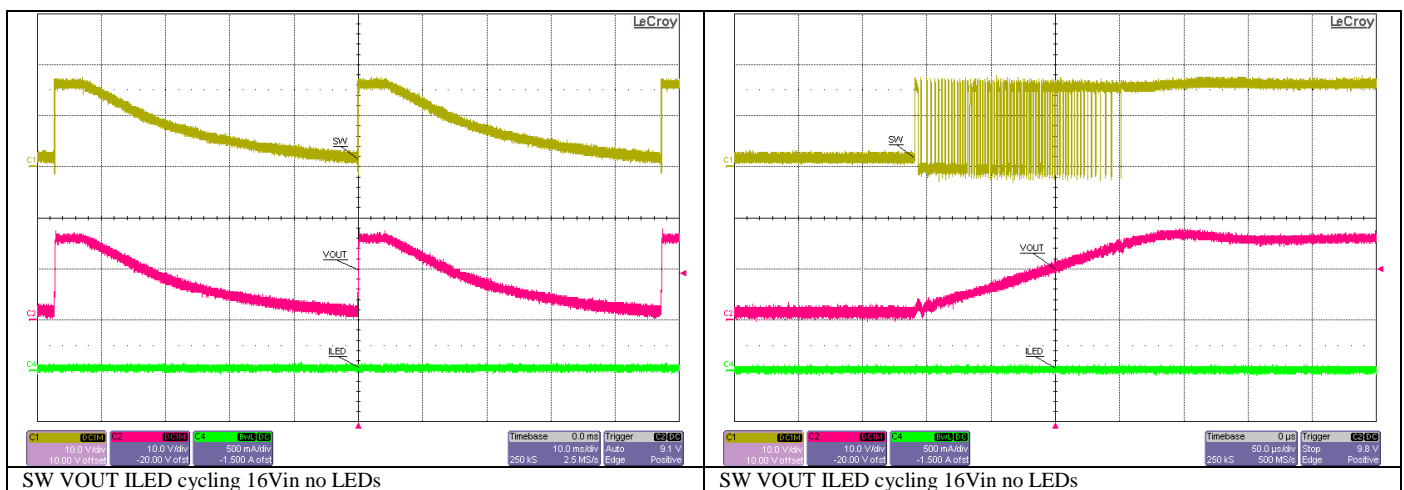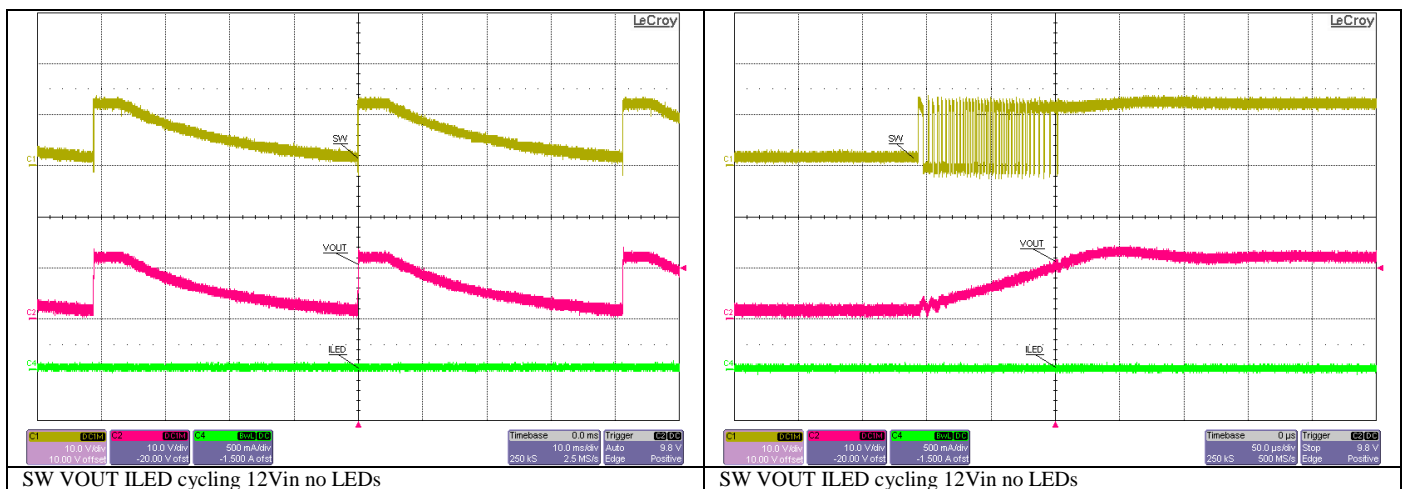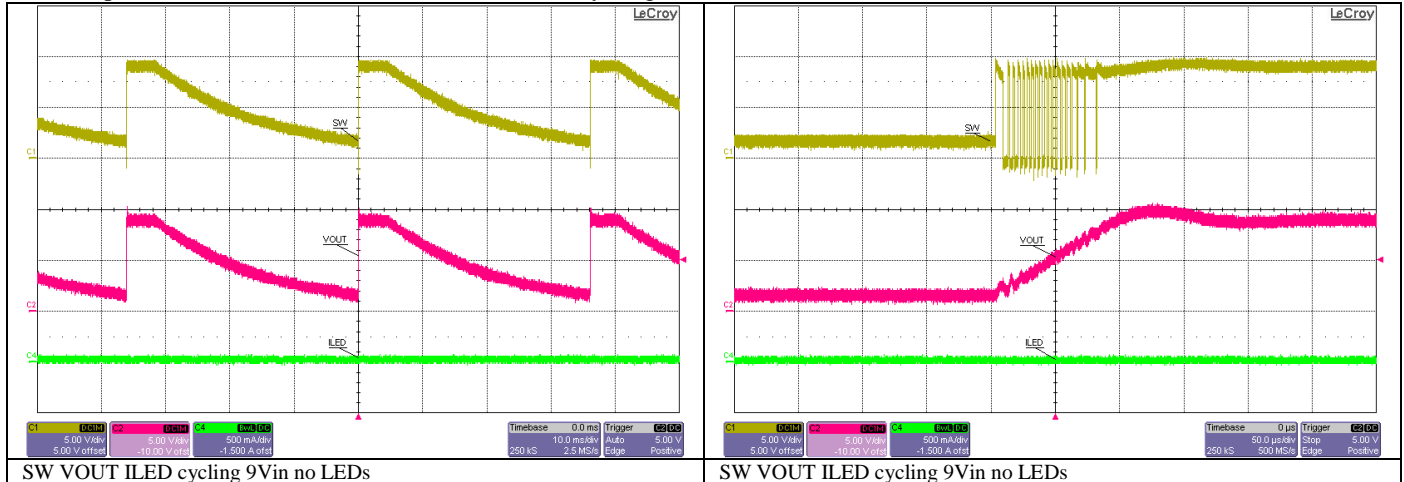9.1 No load cycling

The output was disconnected from the load to show cycling at no load.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated