


# Shunt-Based Current-Sensing Solutions for BMS Applications in HEVs and EVs



Guang Zhou and Dan Harmon

## BMS Topologies and Current Measurement Methodologies

Hybrid electric vehicles (HEV) and electric vehicles (EV) continue to gain share in the overall global automotive market. The battery management system (BMS) for these vehicles carries out the important tasks of keeping the battery inside the safe operating area (SOA), monitoring power distribution, and tracking the state of charge (SoC). In a typical HEV and EV, both high- and low-voltage subsystems are present. The high-voltage subsystem operates at several hundred volts, and interfaces directly with utility grid or high-voltage DC sources. The low-voltage subsystem generally operates at 48 V and 12 V.

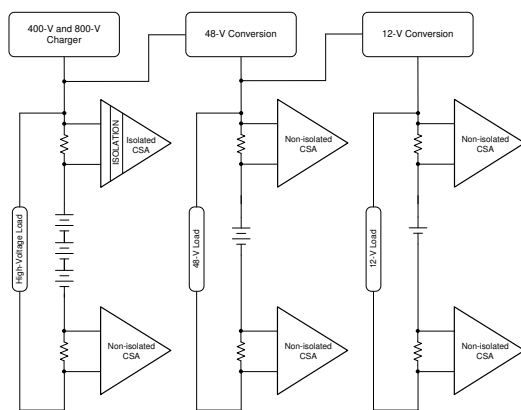

**Figure 1. Topologies of Current Sensing in BMS**

High-voltage battery, top-of-stack measurements require an isolated solution. Magnetic solutions enable the require isolation, but typically will not be able to support the full current range. TI offers isolated shunt-based current sensing solutions, such as the [AMC3301-Q1](#). A summary of other examples of isolated current sensing technology can be found in the [Comparing Shunt- and Hall-Based Isolated Current-Sensing Solutions in HEV/EV application brief](#). Isolation is not typically required for top-of-the-stack 48-V or 12-V battery systems nor in bottom-of-the-stack implementations.

The focus in this document is on non-isolated, shunt-based current-sensing amplifiers (CSA), also called current shunt monitors (CSM), and digital power monitors (DPM) for bottom-of-stack or top-of-stack in 12-V to 48-V BMS subsystems. The advantages of non-isolated shunt-based current sensing include simplicity, low cost, excellent linearity, and accuracy. A drawback of shunt-based current sensing is the power dissipation requirements for the shunt resistor at the maximum current levels.

## Current Sense Amplifiers in an HEV or EV Charger

Battery array is an important component of any HEV or EV. There are mainly two types of rechargeable batteries: the lead acid battery that has been around for over 100 years, and the Li-Ion battery that has only been put into practical use since the 1980s. Both lead acid and Li-Ion batteries follow a certain constant voltage-constant current charging profile. The CSA plays an important role in making sure the battery remains within the SOA.

Operational current for the traction inverter and charging current can be greater than 1000 A in many systems. However, these BMS systems must also be able to measure currents equal to or less than 1 A when the vehicle is off as many systems continue to function such as keyless entry or vehicle-to-world communications. BMS systems must monitor the power distribution as accurately as possible during both operation and vehicle off-state to provide overall system health and safety information. State of charge (SoC), which is the equivalent of a fuel gauge for the battery pack in an HEV or EV, correlates to driving range. Current sensing is one of the important methods to determine SoC. In addition to the precision monitoring of the battery, most automotive BMS systems will require a redundant measurement with relaxed accuracy requirements to enable system level functional safety goals.

The extreme difference between the traction motor current (>1000 A) and the off-vehicle communications current (<1 A) creates a multi-decade, high-precision, bidirectional (charging versus vehicle operation) current measurement challenge.

## Sizing the Shunt Resistor

Historically, measuring the high current with shunt-based topologies has been challenging. However, with the availability of ultra-low resistance shunts, the option is now viable. A typical analog current sense amplifier will have a fixed gain between 20 V/V and 200 V/V and operate from a 5-V supply. This 5-V supply determines the maximum output voltage (ignoring swing to supply limitations), and when we divide by the two gain extremes, we get a full-scale input voltage range of 250 mV to 25 mV. Assuming a bidirectional maximum current measurement of  $\pm 1000$  A, we can calculate a maximum shunt value of 125  $\mu\Omega$  to 12.5  $\mu\Omega$ . As discussed in the [TI Precision Labs - Current sense amplifiers](#) videos, the amplifier offset will dominate the offset error at the low current range. If we use the ultra-precise [INA240-Q1](#) with an offset of 25  $\mu\text{V}$ , we get an error of 20% and 200% respectively on the two shunt resistors. [Table 1](#) summarizes these calculations along with the power dissipation across these shunts at 1000 A.

**Table 1. INA240-Q1 Shunt Resistor Value, Offset Error, and Power Dissipation Calculations for  $\pm 1000$ -A BMS Application**

GAIN OPTION	INA240A1: 20 V/V	INA240A4: 200 V/V
Full scale input	250 mV	25 mV
Maximum shunt	125 $\mu\Omega$	12.5 $\mu\Omega$
Offset error at 1 A	20%	200%
$P_{\text{Dis}}$ at 1000 A	125 W	12.5 W

## Solving the Multi-Decade Challenge

This is where an ultra-precise, low-offset solution is required. TI's DPMs are specialized analog-to-digital converters (ADC) dedicated to measuring current. Most can also monitor bus voltage and can calculate the power as well. The full-scale input range is scaled down from that of a typical ADC to accommodate the typical small signal voltage drop across a shunt resistor. The [INA229-Q1](#) (SPI Interface) and [INA228-Q1](#) (I<sup>2</sup>C interface) are 20-bit DPMs with  $V_{\text{OFFSET}} = 1$   $\mu\text{V}$  and a  $\pm 163.84$ -mV full-scale input range. Having a defined full-scale input range makes calculating the maximum shunt resistor value fairly straight forward, simply divide the full-scale input by the maximum current:  $163.84 \text{ mV} \div 1000 \text{ A} = 163.84 \mu\Omega$ . A more commonly available 100- $\mu\Omega$  shunt resistor is used to calculate a 1% error at 1 A.

The final error check is to verify that the integrated ADC is capable of resolving a signal level less than the offset error level. The [INA228-Q1](#) and [INA229-Q1](#) feature a 20-bit delta-sigma converter with one bit being the sign bit. Dividing the full-scale input of 163.84 mV by 19 bits of resolution results in 312.5 nV per least significant bit (LSB). This corresponds to 3.1

mA on a 100- $\mu\Omega$  shunt resistor, well below the target minimum current level of 1 A.

If even lower current levels are needed to be accurately measured, system calibration may become necessary. *Zero-drift* devices enable single-point calibration, and make such challenging designs possible by offering stable performance over temperature.

For current sensing in HEV and EV BMS subsystems, the [INA229-Q1](#) or [INA228-Q1](#) are excellent choices for any bottom-of-stack implementations or top-of-stack implementations in 48-V or 12-V systems with an 85-V common-mode specification and ultra-low offset of  $\pm 1$   $\mu\text{V}$ . The industry standard digital interface can further simplify the design by taking advantage of an existing communication bus. The [INA240-Q1](#) with its 80-V common mode voltage range could be used in 48-V system top-of-stack measurements for either the redundancy implementation or in applications requiring less total dynamic range. All three devices are manufactured with TI proprietary *Zero-Drift* technology, which enable single temperature calibration, if needed, to address lower current accuracy.

## Automotive Device Recommendations

In addition to the [INA229-Q1](#) and [INA228-Q1](#), TI offers other digital output current, voltage, and power monitors. Some example products and adjacent technical documents are compiled in [Table 2](#) and [Table 3](#).

**Table 2. Alternative Device Recommendations**

DEVICE	DIGITAL INTERFACE	DESCRIPTION
<a href="#">INA239-Q1</a>	SPI	85-V, Bidirectional, <i>Zero-Drift</i> , 16-Bit, Low- or High-Side, SPI Current/Voltage/Power Monitor
<a href="#">INA238-Q1</a>	I <sup>2</sup> C, SMBUS	85-V, Bidirectional, <i>Zero-Drift</i> , 16-Bit, Low- or High-Side, I <sup>2</sup> C Current/Voltage/Power Monitor
<a href="#">INA226-Q1</a>	I <sup>2</sup> C, SMBUS	36-V, Bidirectional, <i>Zero-Drift</i> , 16-Bit, Low- or High-Side, I <sup>2</sup> C Current/Voltage/Power Monitor

**Table 3. Adjacent Tech Notes**

LITERATURE NUMBER	LITERATURE TITLE
<a href="#">SBAA325</a>	Current Sensing With INA226-Q1 in HEV/EV Low Voltage BMS Subsystems
<a href="#">SBOA170</a>	Integrated, Current Sensing Analog-to-Digital Converter

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated