

External PNP Transistor Boosts TPS71501 Output Current

Dennis Hudgins

Power Management Products/Portable Power DC-DC Apps

ABSTRACT

Using an external PNP transistor together with a low-dropout regulator (LDO), such as the TPS71501, supplies a load current of 1A with an output of 9V.

Some applications require an output current capability greater than what is available in the standard low-dropout regulator (LDO) product line. An example of such an application would be a circuit requiring a 9V output capable of supplying 1A from an input voltage range of 10.5V to 12V. Finding a regulator to meet these requirements presents several difficulties. While most general-purpose linear regulators can handle the input voltage range, the dropout specification is difficult to meet. Other low-dropout solutions may have a limited input or output voltage range that restricts their use in such applications. By using an external PNP transistor, some regulators can be adapted to meet these input and output voltage range requirements. For example, although the TPS71501 output current is only 50mA, using an external PNP transistor increases the output current capability to 1A, as shown in Figure 1.

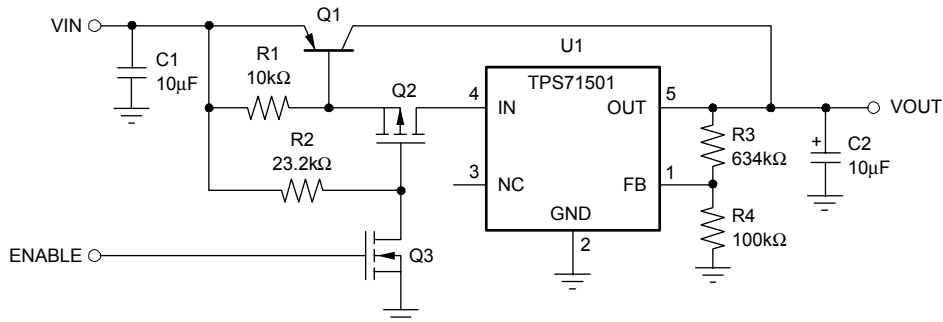


Figure 1. Output Current Boost and Enable Circuit for the TPS71501

In Figure 1, resistors R3 and R4 set the output voltage just as in a non-current-boosted design. Resistor R1 and transistor Q1 increase the output current capability. Resistor R2, together with transistors Q2 and Q3, implements an output enable/disable feature. C2 should be a tantalum capacitor; a ceramic capacitor may also be used, as long as a series resistor is added to achieve a similar series resistance (ESR). The circuit in Figure 1 is not suited for output voltages below 9V due to poor transient response and stability concerns.

The base current of Q1 (as well as the current to generate the V_{BE} voltage across R1) must go through the TPS71501 to the output. The total dropout voltage of the design is calculated by adding the V_{BE} voltage of transistor Q1 to the dropout voltage of the TPS71501. Note that the dropout voltage of the LDO in the circuit depends on the current flowing through the IC, not on the total output current delivered to the load. For this design, the output current of the TPS71501 is shown in Equation (1):

$$I_{LDO} = \frac{V_{BE}}{R1} + \frac{I_{LOAD}}{\beta + 1} \quad (1)$$

To minimize the dropout voltage, the current flowing through the LDO regulator should be as small as possible. Equation (1) shows that increasing the value of R1 and choosing a high beta transistor for Q1 can reduce the LDO current, thus decreasing the dropout voltage. Since the V_{BE} voltage of Q1 is approximately 0.7V, increasing R1 above 10k Ω does little to reduce the regulator current. The most important parameter for reducing current through the TPS71501 is the beta of transistor Q1. Since beta is dependent on the V_{CE} of Q1, the selected transistor should have a low saturation voltage with high beta at the desired dropout voltage. The Zetex ZXT2M322 transistor provides good performance in a small package, making it ideal for this scenario. If a different transistor for Q1 is used in the design, the output stability should be re-evaluated over the entire load range.

Once the current through the LDO is known, the designer can calculate the dropout of the LDO. The TPS71501 has a maximum specified dropout voltage of 750mV at 50mA. Since the I/V characteristic in dropout is linear, an equivalent on-resistance of the pass device can be calculated by dividing the rated dropout voltage by the specified output current. This resistance is approximately 15 Ω for the TPS71501. The dropout at a lower current can be determined by multiplying the output current by the 15 Ω on-resistance of the pass device.

Assuming the voltage across Q2 is negligible, the dropout voltage of the complete design can be calculated by adding the dropout of the TPS71501 with the V_{BE} voltage for Q1. The V_{BE} voltages for transistors are usually around 0.7V. However, this voltage has a temperature coefficient of -2.2mV/ $^{\circ}$ C, so at cold temperatures the V_{BE} voltage increases. The required V_{BE} -on voltage also increases with load current. When selecting Q1 for lowest dropout, the characterization curve in the transistor data sheet showing the V_{BE} -on voltage versus collector current should be examined to select the transistor with the lowest V_{BE} voltage at the desired load current.

Since many applications require the ability to enable and disable the LDO output, transistors Q2 and Q3 were added to the design. When the enable signal shown in Figure 1 is low, transistor Q3 is off and the Q2 gate is pulled high. This turns off Q2, which greatly reduces the quiescent current and disables the LDO output. When the enable signal is high, the Q2 gate is pulled low, which turns on transistor Q2. If an open drain output is available, transistor Q3 may be omitted. The enable circuit increases the quiescent current while operating, depending on the input voltage and the value of R2. However, with the enable circuit omitted, the quiescent current of the 1A solution shown in Figure 1 is only 17.2 μ A typically.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265