

Programming Fun Lights With the TI TCA6507

Sujatha Vadlamani and A.J. Irby

1.1 Examples of Fun Lights

Historically, end-equipment manufacturers have used lighting as a way to differentiate their product over that of their competition and to satisfy market needs. A subset of lighting, known as fun lights, has emerged and is growing in popularity in battery-powered portable applications.

Fun lights can be used to decorate the external appearance of a product and supplement its functionality. The end application may also require different colors and include a variety of blinking or dimming options. Typically, fun lights are implemented using external light emitting diodes (LEDs). See [Figure 1-1](#) for an example of fun light applications.

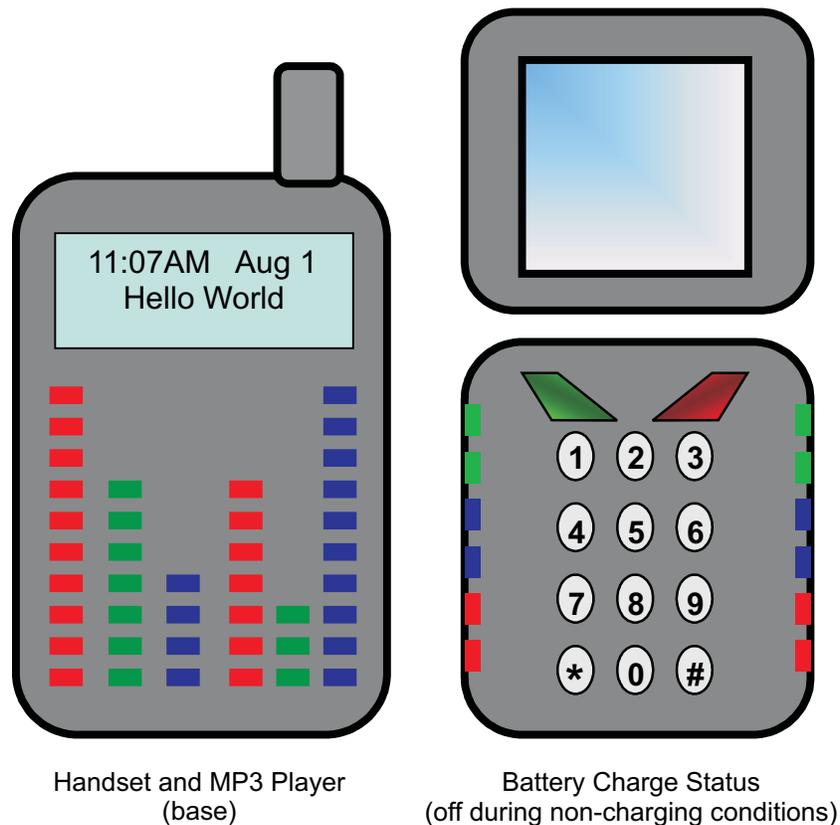


Figure 1-1. Examples of Fun Lights

Because fun lights typically are implemented in portable applications, it is essential that the processor be minimally involved in this part of the design to conserve power, and also allow the processor to focus on the critical functions of the application. In addition, the design architect must decide on the types and colors of LEDs that are utilized, the drive levels required to support these LEDs, and voltage tolerances that the design can sustain. The sequence of the fun lights, which includes the blink modes and brightness of the LEDs, also must be determined.

1.2 I²C LED Drivers for Fun Light Applications

I²C LED drivers are a growing product segment that has been optimized to support fun lights. This type of device is designed to control (or dim) LEDs via the I²C interface. Without this device, the processor or I²C master must be actively involved in turning on and off the LEDs (per the required dimming rate), which uses valuable processor time and overloads the I²C bus. I²C LED drivers alleviate this issue by limiting the number of operations required by the processor in blinking LEDs creating more efficient system. An example of an I²C LED driver for fun lights is the TCA6507 from Texas Instruments.

The TCA6507 is the first I²C LED driver released in TI's new TCA family and is a 7-bit I²C LED driver. This device is ideal for fun light applications for five reasons:

1. The TCA6507 is the first device of its kind in this product segment that can control both the brightness and blink modes with automatic gradual fading of the LEDs it drives.
2. The TCA6507 has a supply voltage range of 1.65 V to 3.6 V, which allows it to interface with next-generation microprocessors, where supply levels are dropping down to conserve power.
3. The TCA6507 also has superior drive capability. Each output can support up to 40 mA of sink current to drive an LED. This output drive is much higher than what a processor or CPLD can offer.
4. The TCA6507 has seven open-drain outputs and each output can support a voltage of 6.5 V (absolute maximum rating), which allows the user to drive red, green, blue, or white LEDs.
5. The TCA6507 has very low power consumption. The maximum supply current (I_{CC}) value is 25 μ A in the operating mode at 400 kHz. The standby current is 10 μ A. When the I²C bus is idle, and intensity control is not used, the TCA6507 can be put into shutdown mode by setting its enable (EN) pin low. This mode provides additional power savings when the LEDs are off. A low signal on the enable pin also resets the registers and I²C/SMBus state machine in the TCA6507 to their default state.

The TCA6507 features an oscillator that can control two pulse-width modulation (PWM) modules that provide independent, widely programmable blink/fade patterns. The TCA6507 also offers five steady levels of brightness (including on and off) for each LED. The user can program each of the seven LEDs to one of the two blink/fade patterns and/or one of the five brightness levels offered. There are 16 discrete PWM levels of brightness for all LEDs with 256 intensity steps during fading for smooth perceived transition.

[Figure 1-2](#) shows a simplified block diagram of the TCA6507.

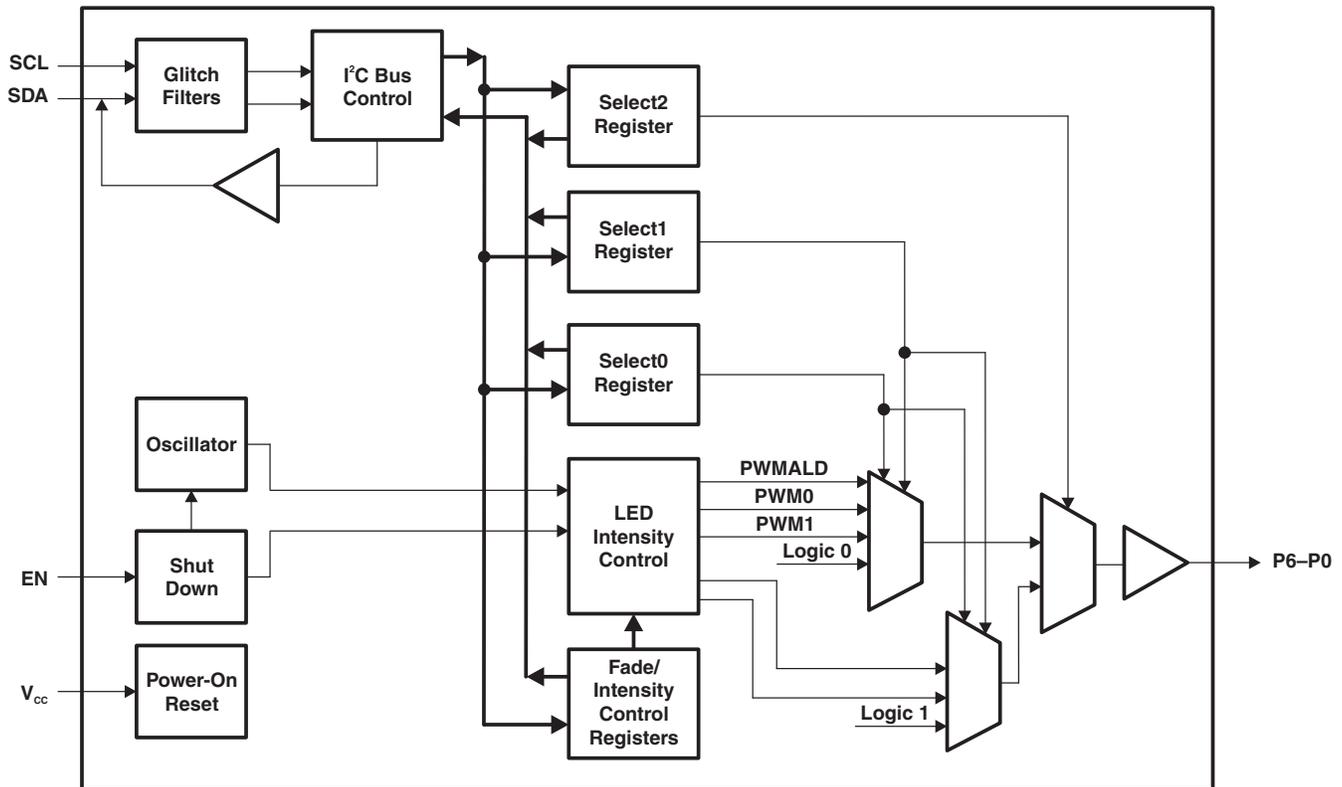


Figure 1-2. TCA6507 Block Diagram

The TCA6507 includes 11 registers that control the function and intensity of the LED. An initial setup command must be sent from the I²C master to the TCA6507 to program the dimming rate and intensity of these registers, which in turn affect the outputs (or LEDs). From then on, only one command from the bus master is required to turn each individual output ON, OFF, or to cycle at the programmed dimming rate.

To drive LEDs, the designer must first program the state of the LED. The TCA6507 offers three options: on state, off state, or blinking mode. This is achieved through the Select2, Select1 and Select0 registers, which are 8-bit registers. These registers are designed such that bit 0 or the least significant bit (LSB) of the Select0 register, bit 0 of the Select1 register, and bit 0 of the Select2 register program the state of the LED at the output P0. Similarly, bit 1 of the Select0 register, bit 1 of the Select1 register, and bit 1 of the Select2 register control the function of the LED at the output P1. See [Table 1-1](#) for more information.

Table 1-1. Select2, Select1, and Select0 Registers

	MSB							LSB
Select0	X ⁽¹⁾	0	0	0	0	0	0	0
Select1	X ⁽¹⁾	0	0	0	0	0	0	0
Select2	X ⁽¹⁾	0	0	0	0	0	0	0
Output or LED affected	X ⁽¹⁾	P6	P5	P4	P3	P2	P1	P0

⁽¹⁾ X = don't care

Depending on the values of the bits programmed in the Select2, Select1, and Select0 registers, the LEDs can be set to have one of five brightness levels and one of two blink modes. See [Table 1-2](#) for the seven possible states of each LED.

Table 1-2. Possible States of LEDs

SELECT2	SELECT1	SELECT0	STATE
0	0	0	LED off (high impedance)
0	0	1	LED off (high impedance)
0	1	0	LED on steadily with maximum intensity value of PWM0
0	1	1	LED on steadily with maximum intensity value of PWM1
1	0	0	LED fully on (output low). Can be used as general-purpose output.
1	0	1	LED on at brightness set by One Shot/Master Intensity register
1	1	0	LED blinking with intensity characteristics of PWM0
1	1	1	LED blinking with intensity characteristics of PWM1

After the state of the LED is set, the designer must program the blink cycle and brightness of the two PWMs (PWM0 and PWM1) for the modes required in the application. This is done through writing to the Fade-On Time, Fully-On Time, Fade-Off Time, First Fully-Off Time, Second Fully-Off Time, and Maximum Intensity registers. Figure 1-3 shows how these registers affect the blink mode and intensity of the PWMs and, in turn, the LEDs. Each of these six registers has eight bits where the top four bits are dedicated to BANK1 or PWM1 and the bottom four bits are for BANK0 or PWM0. The user can program the value of these registers. The maximum time value that can be set in these registers is approximately 16 seconds. This provides a very flexible method to program fun lights and LEDs.

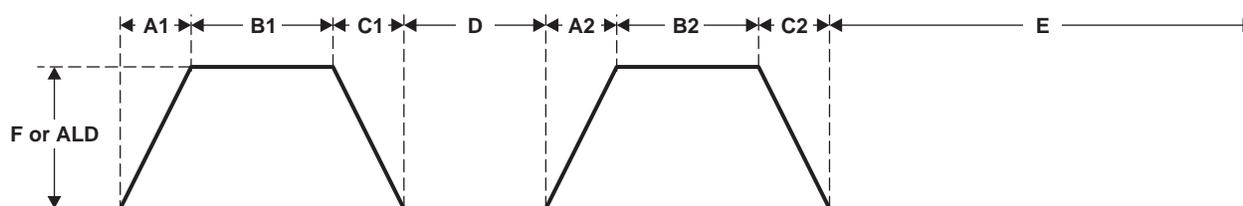


Figure 1-3. Programming for Blink Modes and Intensity

REGION	PARAMETER NAME	PARAMETER RANGE	REGISTER RANGE	REGISTER NAME	REGISTER
A1, A2	Fade-on time	0 to 16320 ms (exponential trend)	0 to 15	Fade-On Time	2
B1, B2	Fully-on time	0 to 16320 ms (exponential trend)	0 to 15	Fully-On Time	3
C1, C2	Fade-off time	0 to 16320 ms (exponential trend)	0 to 15	Fade-Off Time	4
D	First fully-off time	0 to 16320 ms (exponential trend)	0 to 15	First Fully-Off Time	5
E	Second fully-off time	0 to 16320 ms (exponential trend)	0 to 15	Second Fully-Off Time	6
F	Maximum intensity	0 to 100%	0 to 15	Maximum Intensity	7

When used to drive LEDs, the seven outputs can be configured into two banks of outputs (BANK0 and BANK1 based on the two PWMs). Each bank of outputs can be independently controlled for dimming rate and intensity through the I²C bus. The dimming and blink rates are fully programmable. The intensity of each bank of LEDs is controlled by dynamically varying the duty cycle of the signal, which has a period of approximately 8 ms and a pulse rate of 125 times per second, driving the outputs.

For example, the designer can program a blink mode as shown in [Figure 1-4](#). Assume that this blink mode relates to PWM0 or BANK0. By comparing this cycle with that in [Figure 1-3](#), it is noted that the LED does the following:

1. Fades on for 192 ms (value of 3 in Fade-On Time register)
2. Stays fully on for 384 ms (value of 5 in Fully-On Time register)
3. Fades off for 192 ms (value of 3 in Fade-Off Time register)
4. Stays fully off in the first half of the cycle for 512 ms (value of 6 in First Fully-Off Time register)
5. Stays fully off in the second half of the cycle for 1024 ms (value of 8 in Second Fully-Off Time register)
6. Is at 100% intensity in the fully-on state (value of 15 in the Maximum Intensity register)

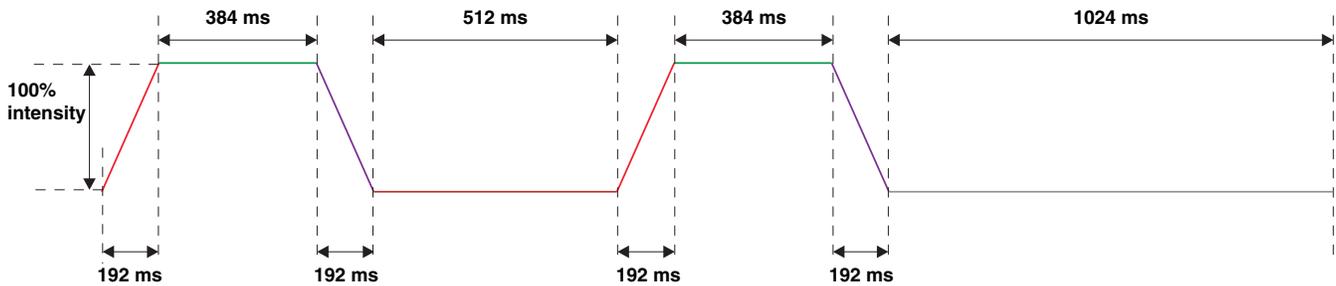


Figure 1-4. LED Blink Cycle Example

Thus, the TCA6507 is very versatile and flexible and can be used in a wide range of fun light applications.

In addition to supporting fun lights, the TCA6507 can be used for indicator lighting. [Figure 1-5](#) shows an application where the TPS61052 boost converter and high-power LED driver and the TCA6507 can be used in combination for applications requiring flashlight functionality and/or high-brightness indicator/backlight LEDs.

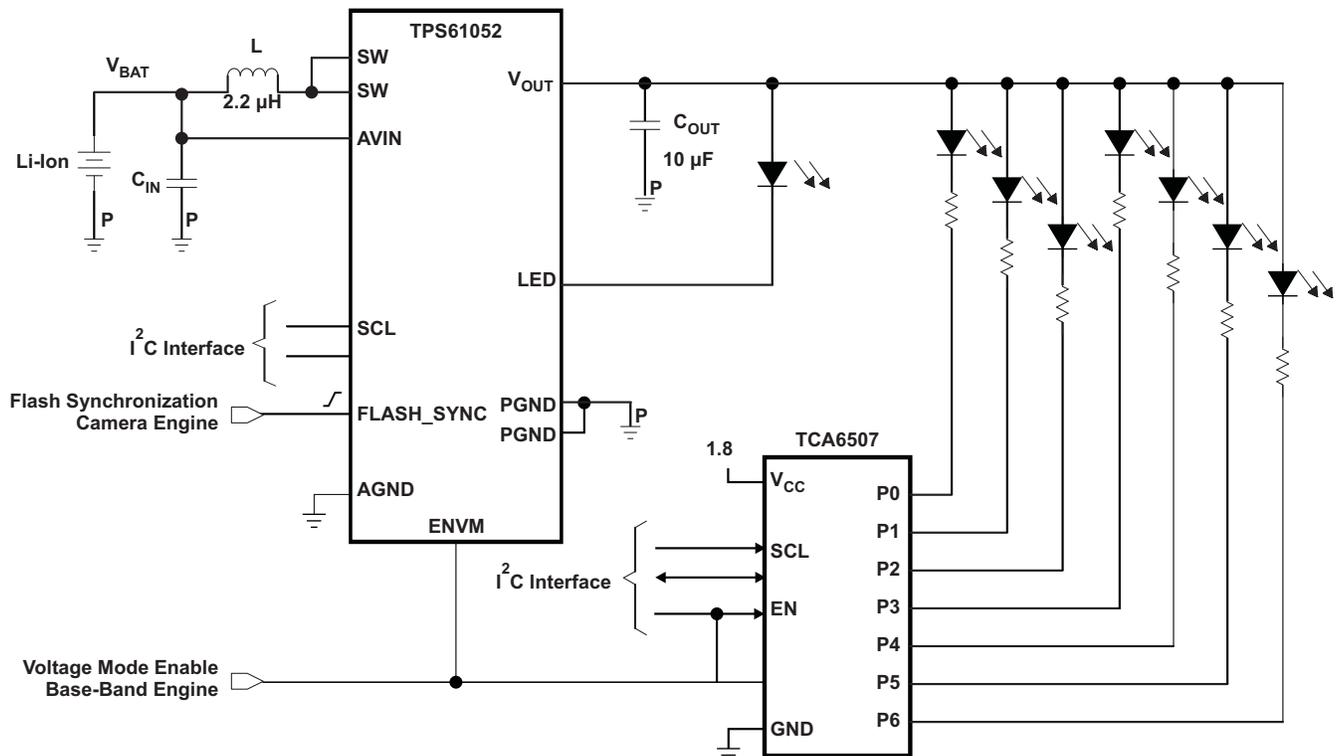


Figure 1-5. TCA6507 for Indicator Lights

The TCA6507 is a great fit for lighting applications in battery-powered portable systems. As previously mentioned, the TCA6507 is ideal for fun lights, enhancing the feature set of an application and for indicator lights. This device allows the core processor to concentrate its processing time and energy toward more critical functions such as communication, audio, or downloading wireless content. The possibilities for using the TCA6507 and I²C LED drivers are limited only to the number of applications engineers can design.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Telephony	www.ti.com/telephony
Low Power Wireless	www.ti.com/lpw	Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2007, Texas Instruments Incorporated