

# Practical Consideration on Choosing a Crystal for CDCE(L)9xx Family

Torsten Jung

## ABSTRACT

This Application Note focuses on the explanation of the practical use of crystals with a CDCE9xx device. No detailed knowledge about crystals is required. A more detailed explanation is found in the Application Note [SCAA085.pdf](#) “VCXO Application Guideline for CDCE(L)9xx Family”.

## Contents

1	Crystal Parameters to be Considered .....	1
2	Measurements on the Crystal.....	3

## List of Figures

1	Equivalent Circuit of a Crystal .....	1
2	Equivalent Circuit of the CDCE9xx Crystal Stage With Attached Crystal and External Load Capacitors.....	2

## 1 Crystal Parameters to be Considered

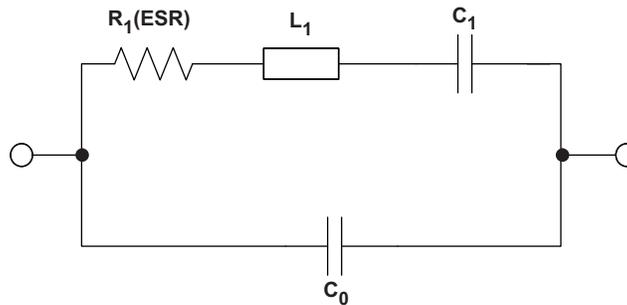



Figure 1. Equivalent Circuit of a Crystal

### 1.1 Crystal Load

The crystal load is one of the most basic parameters to be considered when selecting a crystal. The load capacitance is needed to build a working oscillation circuit. Therefore, it is used to fine tune the oscillation frequency. The CDCE9xx family offers build in load capacitance of up to 20pF selectable in steps of 1pF through the I<sup>2</sup>C™ register 05h bits [7:3]. If a higher load is required, external capacitors can be used. Figure 2 shows the equivalent circuit of the CDCE9xx crystal stage attached to the crystal and possible external load capacitors. Possible load capacitors are switched in parallel to the internal capacitors, so the load capacitance is calculated as follows:

$$CL = \frac{CL_1 \times CL_2}{CL_1 + CL_2} \quad \text{where} \quad C_{Lx} = C_{Lx\text{internal}} + C_{Lx\text{external}} \Big|_{x=1,2} \quad (1)$$

I<sup>2</sup>C is a trademark of Philips Electronics.

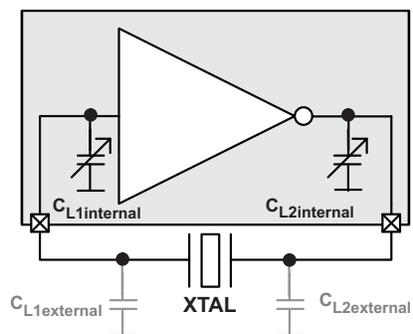

**Figure 2. Equivalent Circuit of the CDCE9xx Crystal Stage With Attached Crystal and External Load Capacitors**

### 1.2 Equivalent Series Resistance (ESR)

The ESR resembles the resistive losses of the crystal. Since the ESR attenuates a signal, it has to be overcome by the crystal stage of the attached device to start an oscillation. For the CDCE9xx Family, the maximum ESR that can be overcome is 100 Ω. Any ESR value below 100 Ω provides a stable oscillation.

Another effect of the ESR is the generation of heat due to resistive losses.

Every crystal has an absolute limit in terms of power dissipation. Exceeding this limit results in damage to the crystal, or in unwanted distortions or perturbations at the oscillation.

Besides this absolute limit, the crystal frequency drifts when the crystal is heated. In addition to the short term frequency drift, a heated crystal can age faster than a crystal at normal operation.

To reduce the heating, the crystal stage of the CDCE9xx family is specially designed for minimum heat dissipation. This means that the crystal stage itself controls the oscillation voltage to ensure an optimized working point for the crystal as well as for the crystal stage.

Therefore, a voltage measurement on the crystal or the crystal stage shows low amplitude by default. This low amplitude is intended and is normal. (see the *Measurements on the crystal* section)

The crystal stage of the CDCE9xx Family is designed to work with crystals with a maximum allowed power dissipation as low as 50μW. A crystal with maximum heat dissipation lower than 50μW can not be used. Crystals with higher maximum allowed power dissipation can be used.

### 1.3 Frequency

A CDCE9xx is designed to work with a crystal input frequency between 8MHz and 32MHz. It does not support 3rd overtone crystals.

### 1.4 Pullability

The device also supports VCXO operation. A crystal with maximum pullability should be selected. Since most vendors do not give information on the pullability of crystals on their web pages or catalogs, the vendors must be contacted for a specific crystal. To help in selecting the correct crystal for VCXO applications, the TIProClock Software for the CDCE9xx devices has a built-in Pulling Range Calculator (under Tools/ Pulling Range calculator). For the software to work, the major parasitics of the crystal must be known. The Application Note SCAA085.pdf gives a more detailed introduction on the pullability of crystals.

## **2 Measurements on the Crystal**

Measurements on the crystal stage are delicate and the results might not reflect the reality. If done, a probe with a high impedance and low parasitic capacitance (<0.1pF) should to be used. However, the parasitics of the probe changes the resonance frequency of the Oscillation circuit.

Measurements on the Xin Pin results in a collapse of the oscillation, only a DC signal is seen here.

Measurements on the Xout Pin usually show a low amplitude. (The reasons are explained in the Equivalent Series Resistance Section)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2008, Texas Instruments Incorporated