

Audio Power Amplifier Operation with Transformer Load

Stephen Crump

Audio and Imaging Products

ABSTRACT

A Class-D audio power amplifier (APA) driving an output transformer with inadequate low-frequency performance may sometimes shut down because of saturation of the transformer core. This paper explains the cause of this sort of shutdown and provides strategies for avoiding it.

Introduction

A product with a Class-D audio power amplifier (APA) driving an output transformer with inadequate low-frequency performance may shut down when its output is stepped from zero to maximum at the start of a sine cycle. Shutdown is triggered by short circuit protection (SCP), after the first half cycle of the sine output. The root cause is saturation of the transformer core.

If shutdown is avoided the transformer input and output voltages and currents settle to steady-state levels after a few cycles, as expected. But with or without shutdown there is a large transient in the primary current of the transformer during the second quarter cycle after transformer primary signal is applied.

To demonstrate this problem a TPA3123D2 in bridge-tied-load (BTL) mode was used to drive the primary of a transformer that has this sort of saturation. The input to the TPA3123D2 was a sine from a function generator at 50Hz, the transformer's minimum rated input frequency. To demonstrate the transient as clearly as possible it was first generated with the load disconnected, as shown in Figure 1.

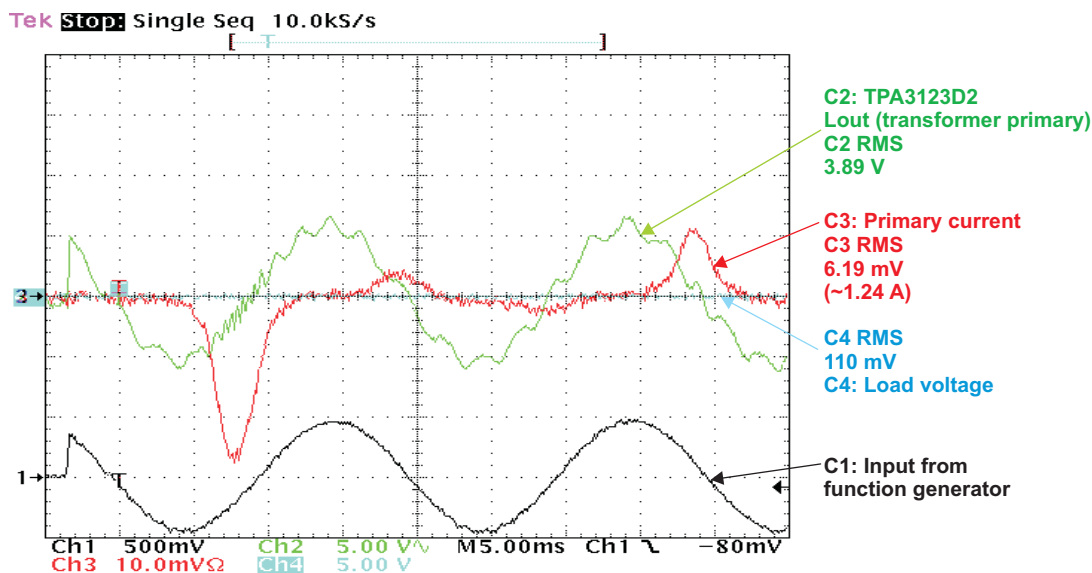


Figure 1. Transformer Primary Voltage and Saturation Current Without APA Shutdown

Ripples in TPA3123D2 Lout are aliased ripple from the switching signal after the LC filter.

In cases like the preceding case the product avoided shutting down. In others it shut down as shown in Figure 2. (Nominal SCP threshold for TPA3123D2 is 6A, with a range from 4A to 8A.)

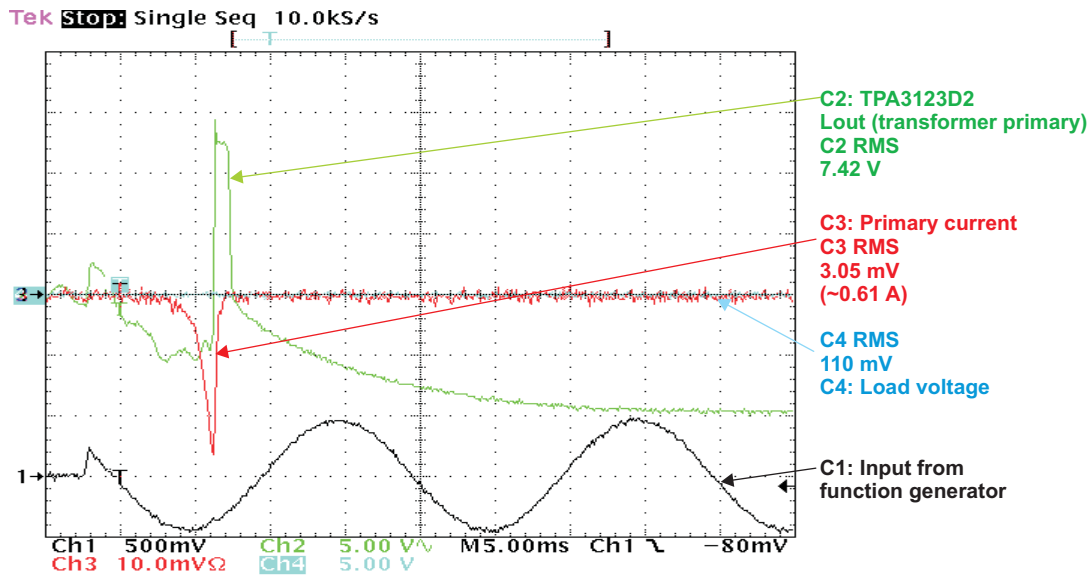


Figure 2. Transformer Primary Voltage and Saturation Current With APA Shutdown

SCP shutdown was a function of magnetizing current, and it did not depend on loading on the transformer secondaries.

With a load the initial transient is still clearly apparent, as shown in Figure 3. (The load in this case is a parallel pair of 5-Ω resistors fed through bridge rectifiers, one on each secondary of the transformer; see the schematic, Figure 4).

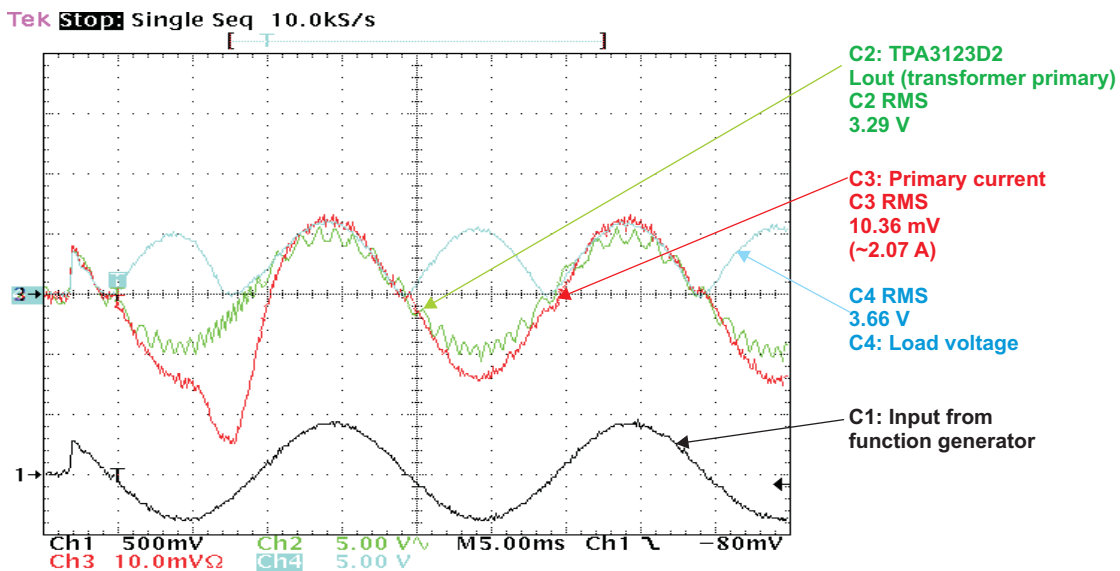


Figure 3. Transformer Primary and Load Voltages and Saturation Current Without APA Shutdown

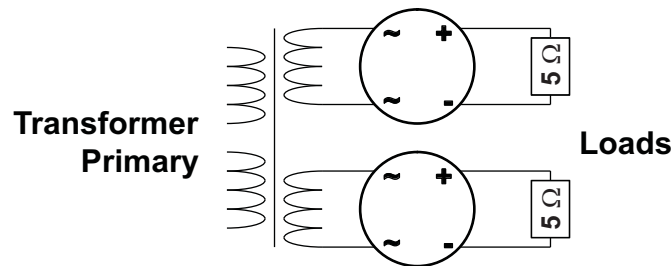


Figure 4. Transformer and Load Circuit Schematic

The reason for transformer core saturation during the first quarter to half cycle is that the transformer is exposed to unipolar volt-seconds during that interval, so magnetizing current builds up to a level above its steady-state value. In steady-state operation the input is bipolar, and magnetizing current lags primary voltage and avoids this effect.

Note that the input signal in graphs above does not start exactly at zero crossing but anticipates it by a fraction of a cycle. The function generator used in these measurements does not permit exact control over signal starting phase, and its starting point has some drift. At the start of these measurements the typical starting point was closer to the zero crossing, and shutdowns were more frequent. This appears to mean that an initial period of primary volt-seconds with opposite phase from the first full half cycle tends to compensate that half cycle, reducing the depth of saturation and so making shutdown less likely.

This suggests a possible cure for the problem. The existing program makes the transition from the low level input to the high level input precisely at a zero crossing. Making the transition a fraction of a cycle before the zero crossing, perhaps a quarter cycle, might compensate just as the initial fraction of a cycle produced by the function generator seems to.

Another alternative is to make the transition from zero to maximum output in more than one step, allowing the magnetizing current to stabilize each time to avoid saturation.

A third alternative is to design the transformer to avoid saturation under these conditions. A simple criterion for achieving success may be to design the transformer so it will not saturate in steady-state operation with full rated primary voltage at a frequency that is half the minimum input frequency that will be applied. Magnetizing current is essentially proportional to both magnitude and frequency of driving voltage. Then, when primary voltage is stepped from zero to maximum at the start of a cycle at the minimum applicable input frequency, peak magnetizing current during the first half cycle will be equal to peak magnetizing current in steady-state operation at half the minimum applicable input frequency, and saturation will be avoided.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated