

# **Fault Monitoring for High-Availability Systems Using the bq769x0**

Marcoo Zamora

BMS-BMP

## ABSTRACT

The bq769x0 monitor family provides a complete solution of monitoring and protection for battery voltage and current related faults, but also protects the battery system by self-monitoring for internal hardware faults. There are high-availability applications, such as in a drone battery management system, where this unexpected FET turn off is undesirable. In such applications, faults like XREADY, which are caused by an internal hardware fault but turns off the power FETs, are undesirable. This document covers an example how one might add additional conditions to faults, such as XREADY in the bq76930 and bq76940, and presents design considerations to help designers implement them.

## Contents

|   |                             |   |
|---|-----------------------------|---|
| 1 | Introduction .....          | 1 |
| 2 | Circuit Block Diagram ..... | 2 |
| 3 | Faults and Delays.....      | 2 |
| 4 | Recovery .....              | 5 |
| 5 | References .....            | 6 |

## List of Figures

|   |                                 |   |
|---|---------------------------------|---|
| 1 | Circuit Block Diagram .....     | 2 |
| 2 | Programming Logic Example ..... | 3 |
| 3 | Overvoltage Fault.....          | 3 |
| 4 | Undervoltage Fault .....        | 4 |
| 5 | XREADY Fault .....              | 4 |
| 6 | Short-Circuit Fault .....       | 5 |
| 7 | SC Logic Example .....          | 6 |

## List of Tables

### Trademarks

All trademarks are the property of their respective owners.

## 1 Introduction

The bq769x0 monitor family can protect the battery from faults but it lacks the ability to mask those faults. This can become an issue when it comes to the XREADY fault protection present in the bq76930 and bq76940 as it will disable both the CHG and DSG FETs, which cuts the power to the load. Because the bq769x0 cannot mask a fault, any protection implemented by this monitor might be undesirable. With the addition of an MCU host it is possible to bypass the faults and create system-appropriate responses. This allows the bq769x0 to monitor the status of the battery but not interrupt its function without meeting additional criterion.

## 2 Circuit Block Diagram

Figure 1 shows a block-level implementation of bypassing XREADY. This circuit implements the bq769x0 as a monitor with an MSP430 as the MCU for the host. This circuit also implements the bq2970 for short-circuit protection. In this application, the bq769x0 does not control the power FETs but instead the MSP430 is the power FET controller. This is evident by having the CHG and DSG pins of the bq769x0 open and not powered. By having the MCU control the power FETs, its processing capability can be used to add additional requirements before opening or closing the CHG and DSG FETs. With the MSP430 controlling the power FETs, there is additional level translation and driver logic that is needed due to the voltage requirement needed to drive power FETs with a high-current capability.

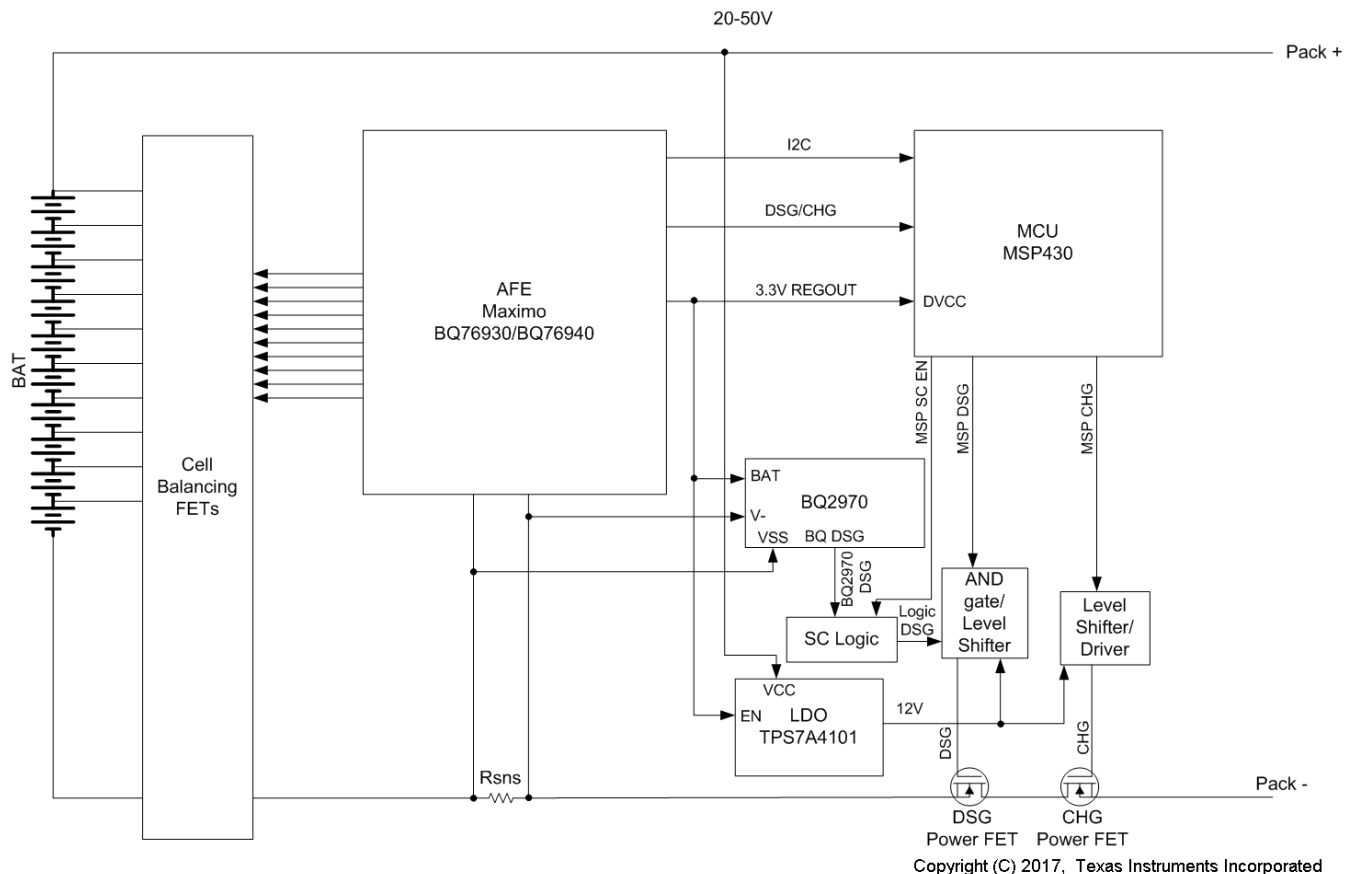


Figure 1. Circuit Block Diagram

## 3 Faults and Delays

When using an MSP430 as the FET controller, the delays for fault protection are different because of latency of the MSP430 code. This comes into effect when checking for an XREADY fault situation prior to any FET changes. Depending on how the XREADY fault was triggered, there can be situations where multiple faults are on in addition to XREADY and therefore, faults need to be ranked according to importance. Since XREADY can fault due to the upper cells in a battery, it is necessary for the ADC to have read and verified the voltage readings prior to proceeding. Depending on the application, there might be a need for a delay after reading the initial signal to ensure that XREADY was not triggered along with other faults. The MCU can provide different levels of protection depending on the system mode of operation.

Using the MSP430 as a FET controller we gain the benefit of adding different conditions for faults. While this document is focused on masking XREADY, in certain systems one might want to change the conditions for different faults, or the system response to the fault, or both. For example, in a drone application an undervoltage (UV) or overvoltage (OV) fault might not warrant a shutdown, instead letting the user decide the appropriate action. For those situations, similar techniques can be applied as presented in this document. In this system the main communication for fault checking is the MSP430 polling the SYS\_STAT register of the bq769x0. It is also possible to use the DSG and CHG pins as interrupts for the MSP430 for a quicker response time. Figure 2 shows a possible example of a fault procedure to mask XREADY.

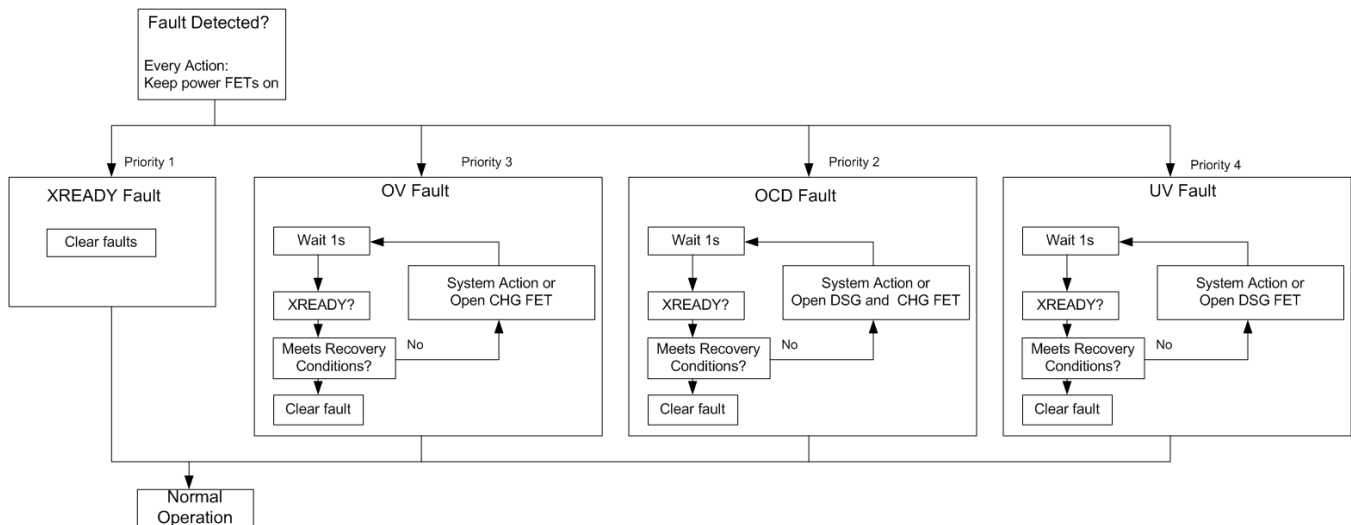


Figure 2. Programming Logic Example

The MSP430 is able to adequately protect the battery by switching the appropriate FETs on or off. In terms of an OV or UV it can toggle adequately, as shown in Figure 3 and Figure 4. In these graphs the FET pins of the bq769x0 CHG and DSG pins are turned on for display purposes to show the difference in timings of the FETs, but would otherwise remain off because the MCU is doing the power FET control. It is important to note that the SYS\_STAT registers in the bq769x0 toggle after the set delay for each fault. For quicker response time from the MSP430 it would be necessary to lower the delays on the bq769x0. For accuracy, it might be necessary to take into the account the processing delays and register data acquisition methods.

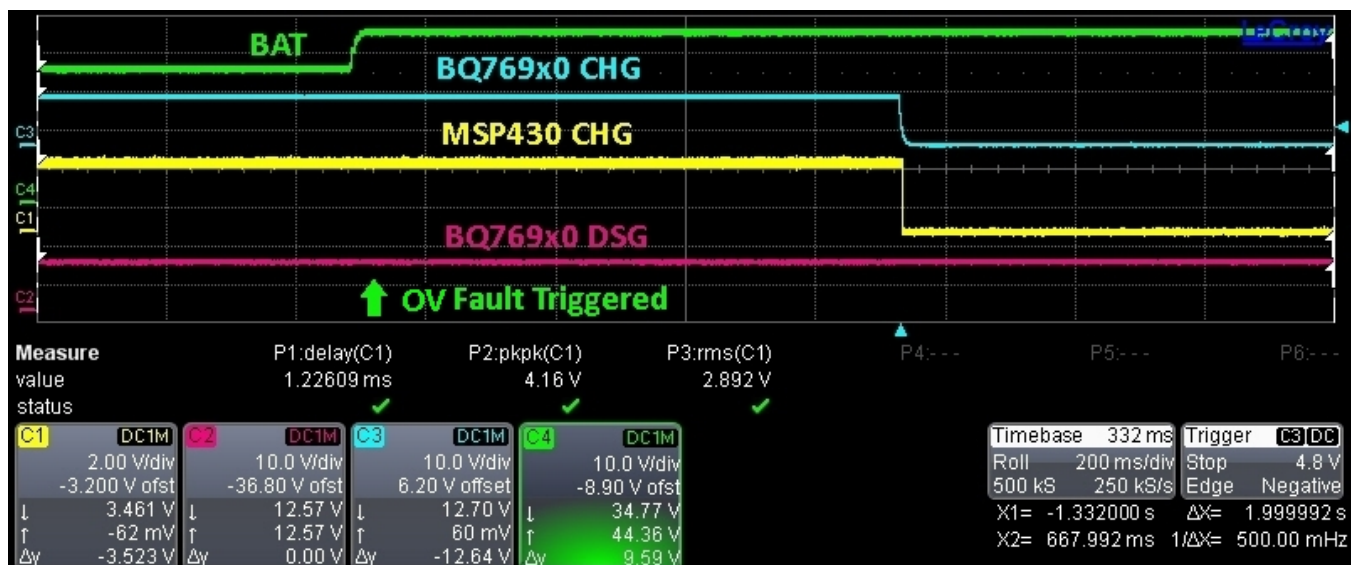


Figure 3. Overvoltage Fault

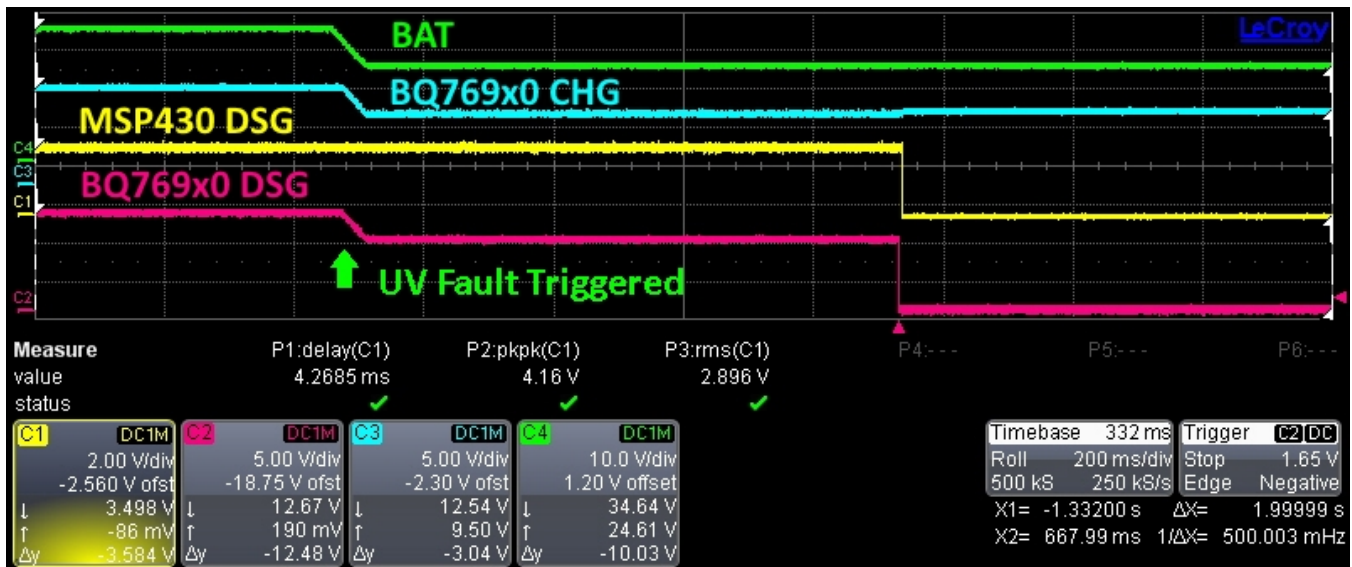


Figure 4. Undervoltage Fault

The main goal of the circuit in Figure 1 is to keep XREADY from turning off the FETs. Without an MSP430 to control the FETs, the bq769x0 would toggle both the charge and discharge FETs off in the event of an XREADY fault. When given adequate time, the MSP430 is able to see this fault and act accordingly. In Figure 5 the MSP430 was able to detect that an XREADY fault had occurred but did not turn off the FETs and therefore ignored the fault. Note that the delay between XREADY and the CHG and DSG outputs going low is expected.

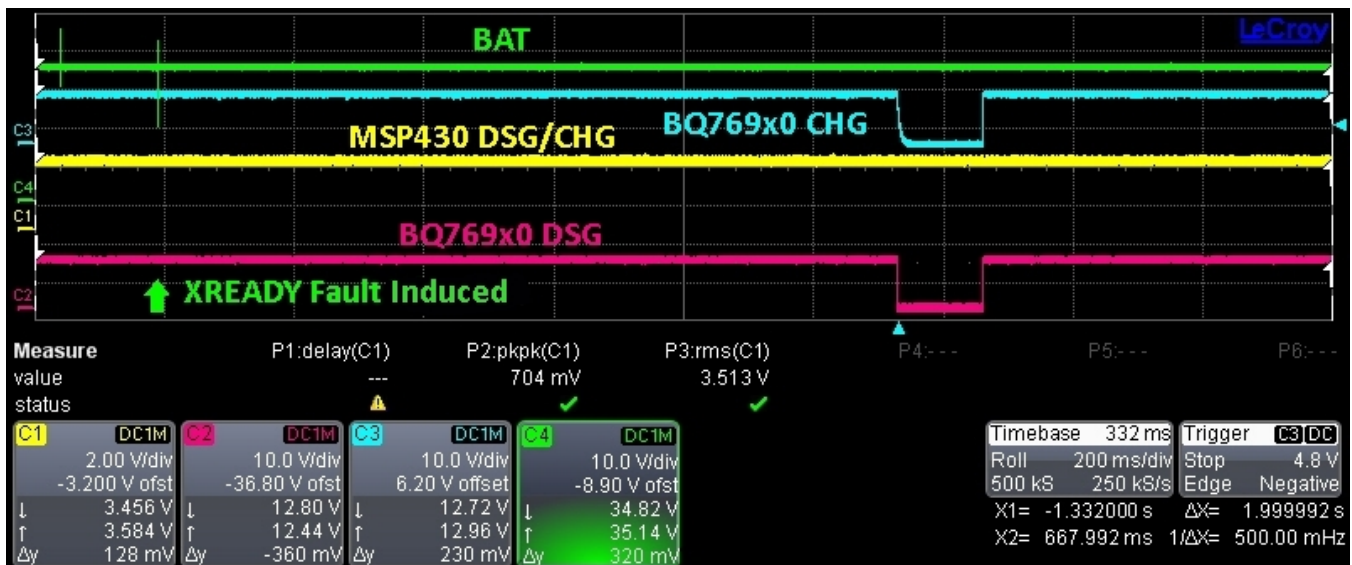


Figure 5. XREADY Fault

Due to the additional delays because of the MCU latency, short-circuit (SC) faults that need a 1 ms or quicker response time will not be able to trigger within the time frame. Due to this, a bq2970 is implemented to run in parallel to check for SC faults. The bq2970 in this application has the same functionality as a current sense amplifier with a comparator but in a smaller size and lower cost. One of the benefits of using a bq2970 is that it is able to run off of the REGOUT pin of the bq769x0 along with the MSP430. This removes any additional power converters needed to power these devices. The OV and UV faults of the bq2970 will never trigger since the BAT input of the device is connected to REGOUT of the bq769x0. As the bq2970 is used only for its SC fault capability in this application, it is necessary to raise the OCD threshold so that it does not trigger.

The bq2970 SC fault detection works by comparing  $V_{SNS}$ , measured between VSS and the V- pin, to a preprogrammed threshold in the bq2970. If the threshold is reached, then the bq2970 will turn off its DSG pin which will turn off the power DSG FET. In this situation the sense resistor ( $R_{SNS}$ ) of the bq769x0 is used to create this voltage difference to trigger the bq2970. This device has a short 250- $\mu$ s SC delay which is comparable to the bq769x0 SC delay.


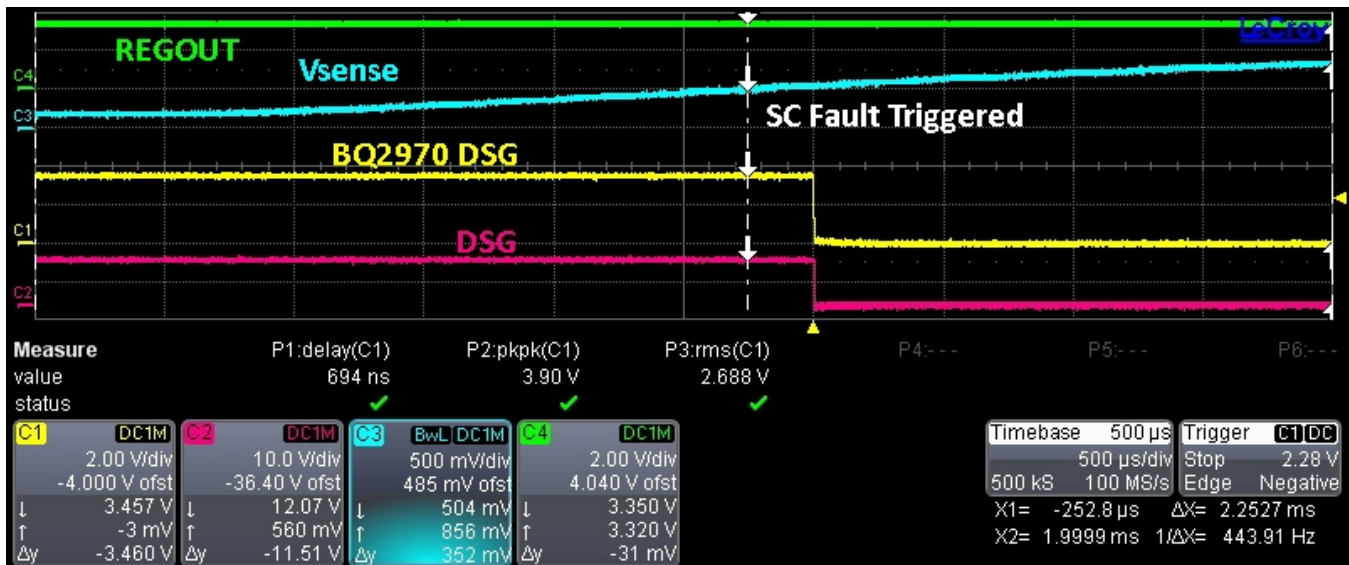


Figure 6. Short-Circuit Fault

One additional consideration is that the bq2970 and MSP430 pins are limited by REGOUT. This causes the FET pins to toggle at a max of 3.3 V which is not enough to drive a power FET to saturation and so the use of a level shifter is needed. This makes it necessary to include an LDO to power the voltage translation circuitry. In the circuit diagram (Figure 1), this is shown as a TPS7A4101, this is an LDO that is connected to the top battery cell with an enable feature for lower power consumption.
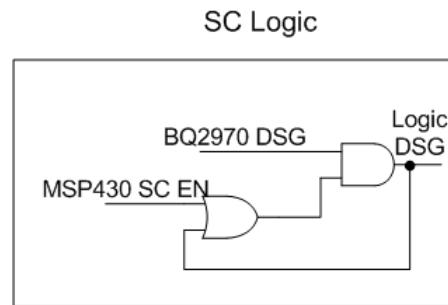
#### 4 Recovery

The MCU is the host of the bq769x0 and is responsible for clearing the registers and toggling the power FETs by using its GPIO. This part of the host's responsibility is left unchanged in this application. In the SC protection side, the bq2970's autorecovery feature might create issues if it is not taken into account. This is because the bq2970 SC fault recovery feature tries to recover 8 ms after the fault occurred and might turn on the power FETs prematurely. With 2 protection devices, the MSP430 and the bq2970, working in parallel, the additional logic to combine both of the controls is shown in the Figure 1 as SC Logic. This example recovery logic takes advantage of the bq2970 autorecovery and makes sure the MSP430 is required for recovery.



Copyright © 2017, Texas Instruments Incorporated

**Figure 7. SC Logic Example**

## 5 References

For additional information, refer to the following documents, available at [www.ti.com](http://www.ti.com).

- *bq769x0 3-Series to 15-Series Cell Battery Monitor Family for Li-Ion and Phosphate Applications* data sheet ([SLUSBK2](#))
- *bq76930 and bq76940 Evaluation Module* ([SLVU925](#))
- *10s Battery Pack Monitoring, Balancing, and Comprehensive Protection. 50A Discharge Reference Design* ([TIDUAR8](#))



## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated