

Disabling the Watchdog Timer for TI's Family of Supervisors

Dennis Hudgins
PMP Portable Power

ABSTRACT

In many microprocessor applications where a watchdog supervisor, such as the TPS3306, is required, it may be necessary to disable the watchdog. This is particularly true when software boot times exceed the watchdog time-out period. This application note describes a circuit that can be used to selectively disable the watchdog timer.

The watchdog timer in many of TI's supervisory circuits can be disabled by leaving the WDI pin open. In this mode, an internal signal is provided to periodically reset the watchdog time-out timer. If the WDI pin is grounded or pulled high, the internal trigger is disabled and watchdog time-outs occur. Table 1 shows several supervisors that feature a watchdog timer that is easily disabled, as well as their minimum time-out periods.

Table 1. Minimum Watchdog Time-Outs for Supervisor Devices

Device	Minimum Watchdog Time-out (seconds)
TPS36xx	0.48
TPS3820	0.112
TPS3823/4/8	0.9
TPS3305/3705	1.1
TPS3306	0.5
TPS3705	1.1

Applications that require a watchdog timer must make sure the software boot time does not exceed the minimum watchdog time-out period. If the boot time does exceed the watchdog time-out period, the application loops through the boot cycle indefinitely. However, if the circuit shown in Figure 1 is used, the watchdog timer time-out period is effectively extended as long as the boot time requires. This circuit is ideal in applications that have long boot times, but require a watchdog with a short time-out period. Shorter watchdog time-out periods are generally preferred in applications that need to respond quickly to processor fault conditions.

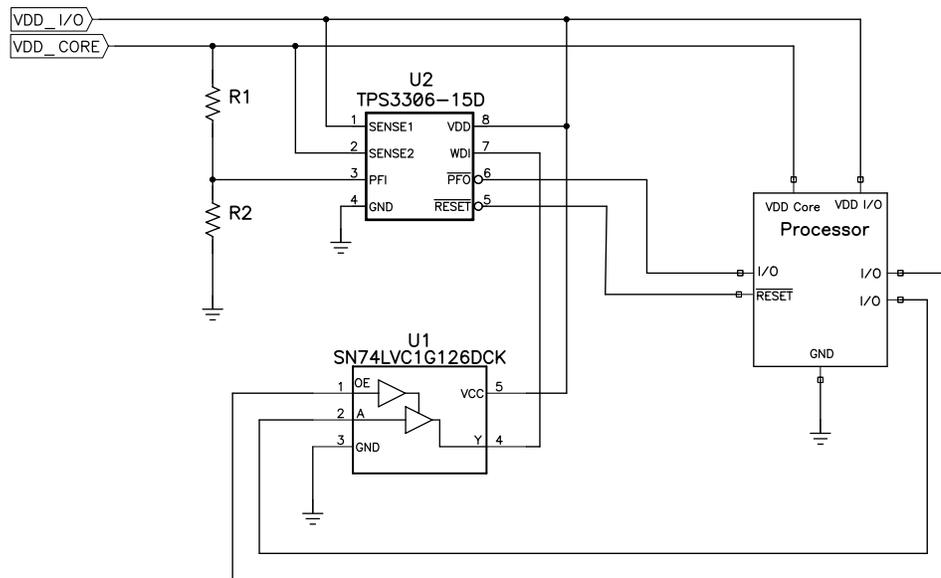


Figure 1. Typical Supervisor Application With 3-State Buffer to Disable Watchdog

In Figure 1, the output enable (pin 1) of the SN74LVC1G126DCK is set low on power-up. This disables the output of the buffer, effectively disconnecting the WDI pin on the TPS3306-15. This allows the software boot time of processor to exceed the normal watchdog time-out period. After the software is loaded, the output of the buffer can be enabled by the processor and normal watchdog time-out conditions apply. However, since the internal watchdog counter is not synchronized to the buffer enable signal, a logic high voltage needs to be present on the input of the buffer before it is enabled. This makes a low to high transition occur on the WDI input as soon as the buffer is enabled. The immediate transition on the WDI input resets the internal watchdog counter. It, also, synchronizes the internal watchdog timer with the external watchdog pulses, thus, preventing a possible watchdog timeout condition.

If the default state of the I/O on power-up is pulled up to Vdd, the SN74LVC1G125DCK can be used in place of the SN74LVC1G126DCK. This device is identical to the SN74LVC1G125DCK except that the output enable pin is inverted. On start-up, the buffer used must stay in the off state to prevent the possibility of overriding the self-generated watchdog trigger of the supervisor.

If a different 3-state buffer is desired, the output leakage when disabled must not exceed 10 μ A. If a solid state switch is used the switch must have off leakage of less than 10 μ A and be capable of bidirectional current flow.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2003, Texas Instruments Incorporated