

Low Quiescent Current with Asynchronous Buck Converters at High Temperatures

ABSTRACT

This application report provides a summary of the Low Quiescent Current with Asynchronous Buck Converters at High Temperatures for TPS65320/1-Q1 devices.

1 Introduction

Many modern Buck Converters are advertised with very low quiescent currents (I_q) in the order of between 10 and 40 μA . In reality, the *no-load input current* is significantly higher. At elevated temperatures, the input current may even change by orders of magnitude.

This application report discusses the contributors to no-load input current in addition to the I_q of the converter itself and associated temperature dependency. Furthermore, this analyzes when this effect is of concern and what to do about it.

1.1 Contributors to No-Load Input Current

The I_q of a converter is one contributor only and its definition and test conditions also indicate that, in reality, the converter will show a higher-current consumption at no load. Quiescent current of a converter refers to the supply current drawn at no load, non-switching by biasing the feedback pin at reference voltage, or slightly above, and potentially at room temperature only. Consequently, non-switching indicates that no switching losses are accounted for, even though a converter will switch occasionally at no load. There will be some leakage and also a recharge of the boot-capacitors or a charge-pump is likely required, which adds to the losses. A drift of the quiescent current over temperature may, or may not, be specified separately. Luckily, the temperature drift of most converters is expected in the order of an approximately 10% increase at higher temperatures. For test-purposes to specify the I_q of a converter, the feedback is biased to the reference voltage. Thus, this eliminates the feedback-divider to sense the output voltage. Consequently, the current flowing through it (mostly in the order of 10 μA ..50 μA) as well as switching of the FETs is prevented and associated losses saved. In reality, those effects do contribute to the *no-load input current*. [Figure 1](#) illustrates the contributors that, in addition to the quiescent current, draw current from the supply.

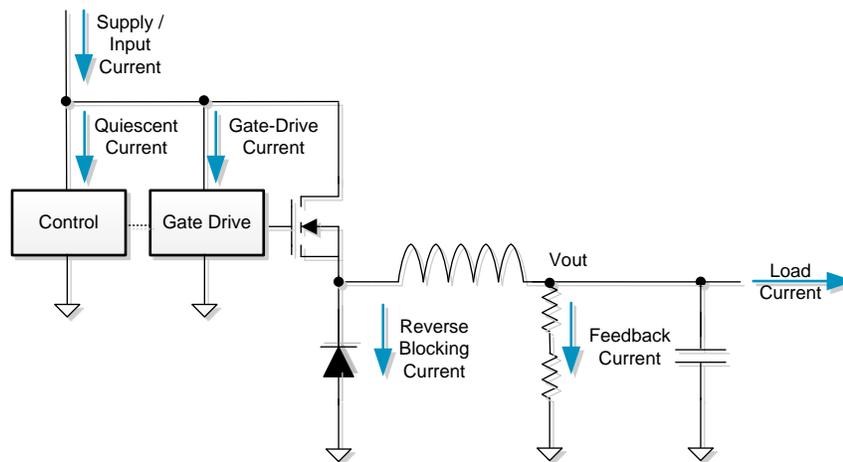


Figure 1. Asynchronous Buck Converter and Associated Currents

A step-down converter with a specified quiescent current of 30 μA will – at room-temperature – most likely draw in excess of 50 μA of no load-current, which accounts for feedback-divider-current and switching losses.

However, this does not explain the orders of magnitude of increase with higher temperature as observed with asynchronous converters: here, the catch-diode plays a significant role in this case: the majority of diodes show an increased reverse current, mostly about 100 times higher at higher temperatures (85°C or higher) compared to room temperature.

For low-voltage and low-current diodes (for example: 10 V, 500 mA), one can find diodes with as low as 1 μA -rated reverse current at room temperature, which consequently rises to about 100 μA at higher temperatures. Unfortunately, for low loads, blocking will be the diode status for the vast majority of the time. For higher-voltage and higher-current diodes (40 V, 4 A), the few microamperes or few dozen microamperes at room temperature will account for several milliamperes at elevated temperatures.

Another factor to consider is the increase in reverse current with increased reverse voltage. Here a rise of about one decade has to be expected from low voltages to maximum-rated voltages. However, clearly defined diode data sheets usually specify the maximum-reverse current at maximum-rated blocking voltage (and at discrete temperatures). Consequently, any asynchronous converter will exhibit a significantly higher no-load current at higher temperatures, heavily dominated by the catch-diode and its increase of reverse current with temperature.

1.2 When This is a Concern

Obviously, if the respective system is not exposed to relatively high temperatures, this is of no concern. Similarly, if the system is only operating in normal mode, hence normal switching operation as opposed to power-save or no-load mode at higher temperatures, this may be negligible. An example could be an automotive application, where a unit such as the front-view-camera, is either off when hot, like for a car parked in the sun, or in normal operation when the car is running and the alternator is working, and therefore a small loss in efficiency can be tolerated. Similarly in industrial applications, a system is hardly ever in standby mode, but either off or in normal mode. For consumer systems that are battery driven, it could be applicable depending on the expected temperatures. To what extent the effect is seen also depends on the blocking voltage, hence the battery voltage in most cases and load-current that drives the diode selection.

1.3 What to Do if This Effect is of Concern

Keep cool! Admittedly, this is easier said than done. A more appropriate solution is to choose a synchronous converter, which eliminates the diode and replaces it with an active FET. A slight increase in quiescent current still needs to be expected with temperature, but it is approximately 10% with a synchronous converter, rather than orders of magnitude with the asynchronous converter and catch diode.

1.4 Conclusion

The quiescent current is only one contributor to the no-load-current consumption. For an asynchronous converter, the catch-diode's reverse current is a significant contributor, in particular at high temperatures. In some applications, this may be irrelevant or tolerable. In case a low-quiescent current at elevated temperatures is of concern, a synchronous converter is likely the better choice.

2 References

- [IQ: What it is, what it isn't, and how to use it](#)
- [Efficiency of synchronous versus nonsynchronous buck converters](#)
- [Low Quiescent Current with Asynchronous Buck Converters at High Temperatures?](#)

Revision History

DATE	REVISION	NOTES
August 2016	*	Initial release

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com