

UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 1

By Michael O'Loughlin (Email: Michael_Oloughlin@ti.com)

Member, Applications Engineering Staff

Introduction

Power factor corrected (PFC) preregulators are generally used in offline ac/dc power converters with a power level higher than 75 W or to meet line harmonic requirements such as EN61000-3-2. PFC is typically done with a boost converter ac/dc topology due to the continuous input current that can be manipulated through average current-mode control to achieve a near-unity power factor (PF). However, due to the high output voltage of a boost converter, a second dc/dc converter is generally needed to step down the output to a usable voltage. In the past this has been accomplished with two pulse-width modulators (PWMs). One PWM controlled and regulated the PFC

power stage, while the second was used to control the step-down converter. The UCC28517 controller reduces the need for two PWMs and combines both of these functions into one control-integrated circuit. The UCC28517 operates the second converter at twice the switching frequency of the PFC stage, which reduces the size of the boost magnetics and the ripple current in the boost capacitor. For more information on this device, please see Reference 7. This article reviews the design of a 100-W ac/dc power stage with power factor correction. A review of the second stage can be found in a future issue of TI's *Analog Applications Journal*.

Variable definitions

ΔI	Change in boost inductor current	P _{OUTB}	Output B maximum power
η_1	Output A efficiency	P _{Q1}	Total FET losses
η_2	Output B efficiency	P _{semi}	Power dissipated by a semiconductor device
C _{DIODE}	Boost diode capacitance	Q _{GATE}	FET gate charge
Comp	Dynamic range of the multiplier comp pin	R _{θcs}	Thermal impedance case-to-sink
C _{OSS}	FET drain-to-source capacitance	R _{θjc}	Thermal impedance junction-to-case
f _c	Voltage-loop crossover frequency	R _{θsa}	Thermal impedance sink-to-air
f _{iline}	Input line frequency	R _{DS(on)}	On resistance of the FET
f _p	Single-pole filter frequency	R _{IAC}	Multiplier input resistance
f _R	Ripple frequency	R _{SENSE}	Current sense resistor
f _S	Minimum switching frequency	s(f)	Frequency domain (2πf)
f _{SA}	Output A switching frequency	T _{amb}	Ambient temperature
f _{SB}	Output B switching frequency	t _{blank}	Amount of leading-edge blanking time
G _{ID(s)}	Power stage gain	t _f	FET fall time
G _{CA}	Current amplifier gain	t _{holdup}	Boost capacitor hold-up time
G _{c(s)}	Control transfer function	T _{jmax}	Maximum semiconductor temperature
G _{co(s)}	Control to output transfer function	t _{on}	Boost inductor energizing on time
g _m	Transconductance amplifier gain	t _r	FET rise time
G _{vea}	Voltage amplifier gain	T _{s(f)}	Voltage loop frequency response
H _(s)	Voltage divider gain	V _c	Control voltage
I _{IAC}	Multiplier input current	V _{CSENSE}	Maximum current sense voltage
I _{MOUT}	Multiplier output	V _{drop}	Amount of voltage the boost capacitor has to hold up
I _{PK}	Peak inductor current, peak diode current, peak switch current	V _{dynamic}	Current sense voltage range
I _{RMS}	RMS device current	V _{ea}	Voltage amplifier output
I _{SS}	UCC28517 soft-start current of 10 μA	V _f	Forward voltage of a diode
K	Constant typically equal to 1/V	V _{GATE}	Gate-drive voltage
P _{COND}	Device conduction losses	V _{IN}	RMS input voltage
P _{COSS}	Power dissipated by the FET's drain-to-source capacitance	V _{OUTA}	Boost output voltage
P _{DIODE}	Total loss in the boost diode	V _{OUTB}	Auxiliary output voltage
P _{DIODE_CAP}	Loss due to boost diode capacitance	V _p	Oscillator ramp voltage
P _{FET_TR}	FET transition losses	V _{pp}	Output peak-to-peak ripple voltage
P _{GATE}	Power dissipated by the FET gate	V _{ripple}	Output B ripple voltage
P _{OUTA}	Output A maximum power	V _{REF}	UCC28517 internal reference
		V _{VFF}	Multiplier feed-forward voltage
		Z _{OUT}	Compensation impedance

Table 1. Design specifications

	MAXIMUM	TYPICAL	MINIMUM
V _{IN}	265 V _{rms}		85 V _{rms}
Output A (V _{OUTA})	410 V	390 V	370 V
Output B (V _{OUTB})	12.6 V	12 V	11.4 V
Output A efficiency (η1)		85%	
Output B efficiency (η2)		50%	
P _{OUTA}	100 W		10 W
P _{OUTB}	8 W		4 W
Output ripple A (V _{pp})	12 V		
Output ripple B (V _{ripple})	750 mV		
Output A THD (% THD)	10%		
PF	1		
Output A switching frequency (f _{SA})		100 kHz	
Output B switching frequency (f _{SB})		200 kHz	

The following design example was generated using typical parameters rather than worst-case values. Please refer to Table 1 and Figures 1–3 for design specifications and component placement. All variables are defined in the sidebar on page 13.

PFC boost ac/dc regulator design (OUTA)

Inductor selection

The boost inductor is selected based on the maximum ripple current at the peak of minimum line voltage. The following equations can be used to calculate the required inductor for the boost power stage, assuming that the boost inductor ripple current is 25% of the maximum input current.

$$\Delta I = \frac{P_{OUTA} \times 0.25 \times \sqrt{2}}{V_{IN(min)} \eta_1}$$

$$D = 1 - \frac{V_{IN(min)} \times \sqrt{2}}{V_{OUTA}}$$

$$L_1 = \frac{V_{IN(min)} \times \sqrt{2} \times D}{\Delta I \times f_{SA}}$$

Figure 1. PFC power stage schematic

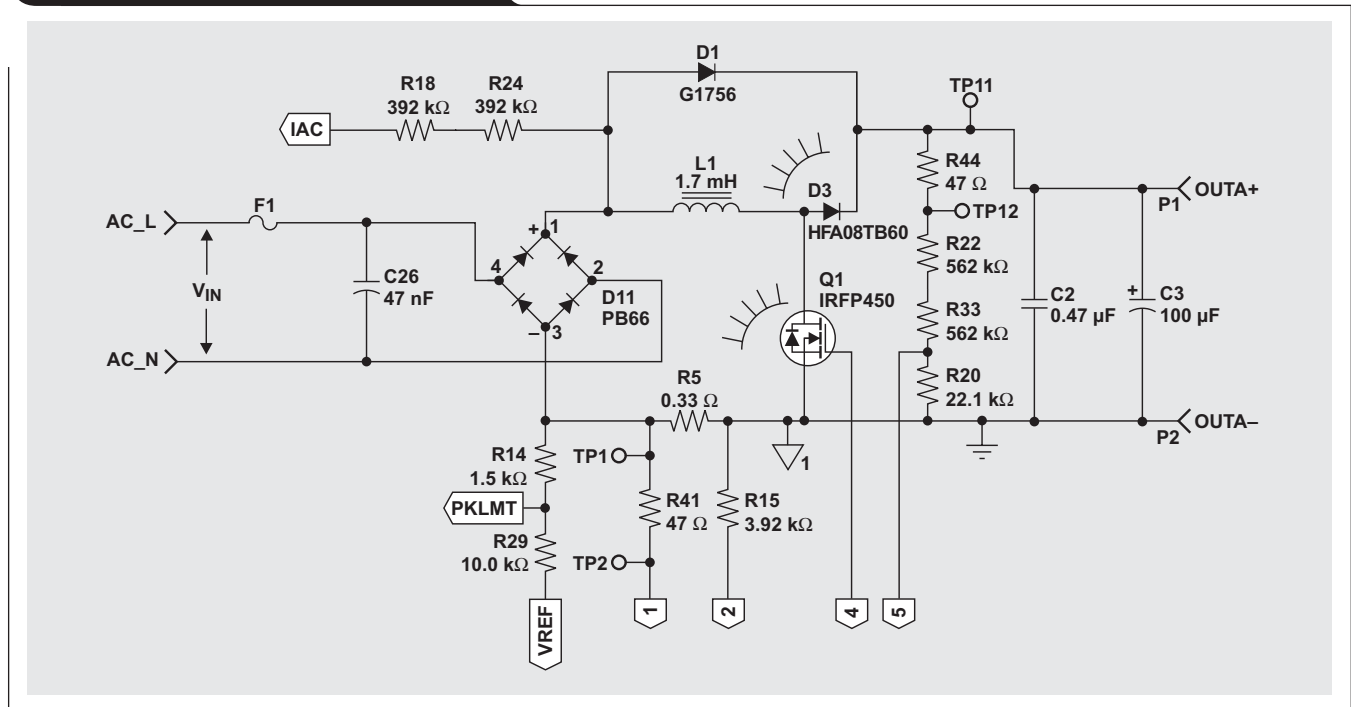


Figure 2. dc/dc power stage schematic


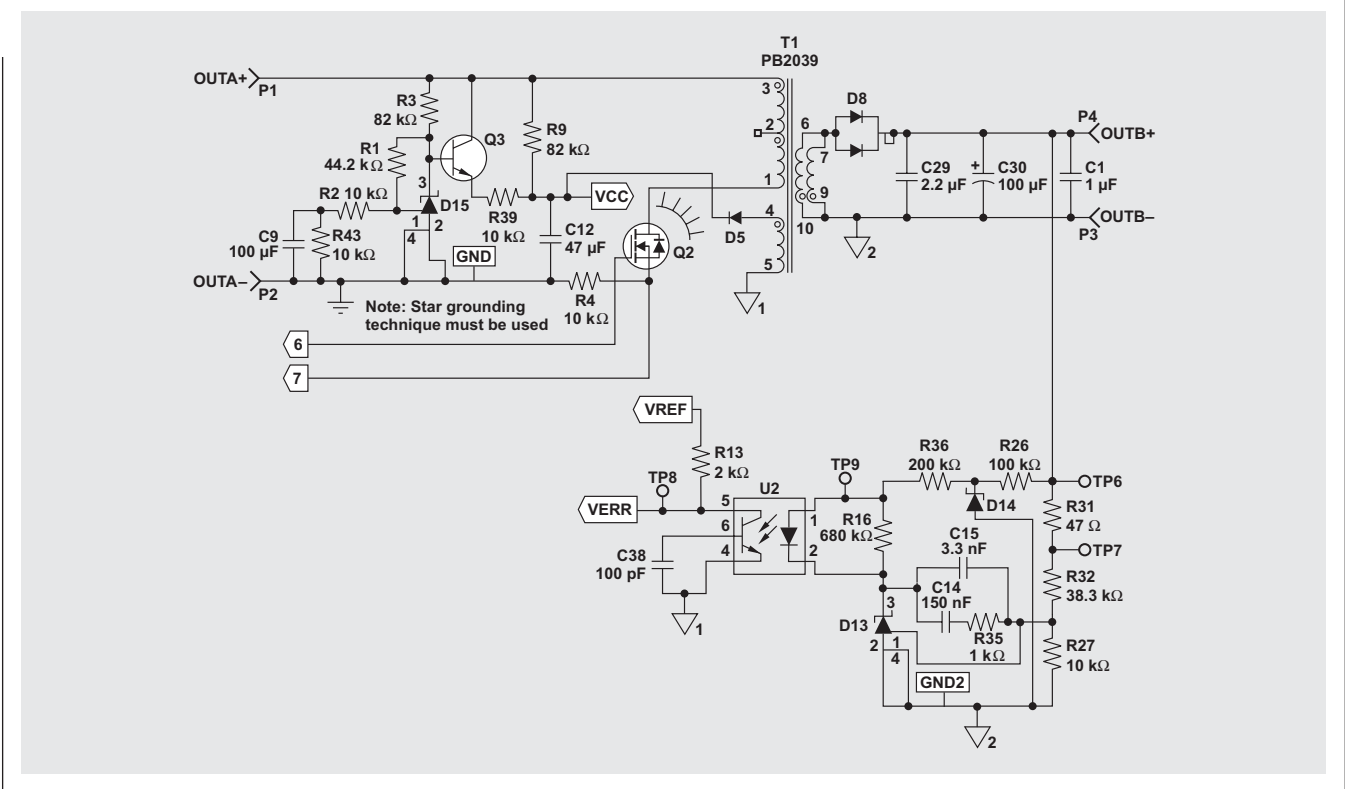


Figure 3. Controller schematic

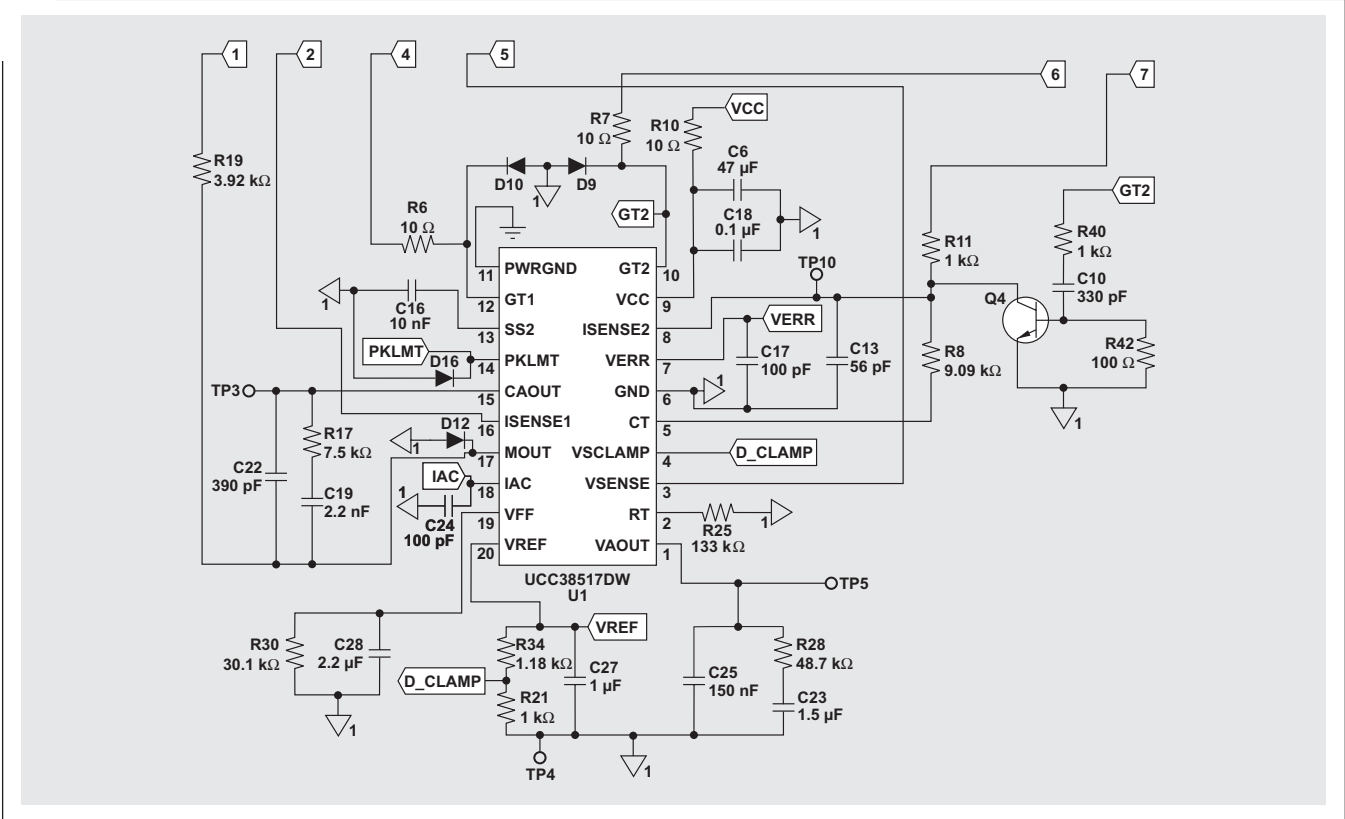

The calculated inductance for this design was roughly 1.7 mH. To make the design process easier, Cooper Electronics designed the inductor (part number CTX08-14730).

Boost switch (Q1) and boost diode (D3) selection

To select Q1 and D3 properly, a power budget is generally set for these devices to maintain the desired efficiency goal. To meet the power budget for this design, an IRFP450 HEX FET and an HFA08TB60 fast-recovery diode from International Rectifier were chosen.

Equations used to calculate the loss in Q1 were:

$$I_{\text{RMS_FET}} = \frac{P_{\text{OUTA}}}{\eta_1 \times V_{\text{IN(min)}}} \times \frac{V_{\text{OUTA}}}{V_{\text{IN(min)}}} \times \sqrt{2 - \frac{16 \times \sqrt{2} \times V_{\text{IN(min)}}}{3\pi \times V_{\text{OUTA}}}}$$

$$I_{\text{RMS_L}} = \frac{P_{\text{OUTA}} \times \sqrt{2}}{\eta_1 \times V_{\text{IN(min)}}} \times \frac{V_{\text{OUTA}}}{V_{\text{IN(min)}}}$$

$$P_{\text{GATE}} = Q_{\text{GATE}} V_{\text{GATE}} \times f_s$$

$$P_{\text{COSS}} = \frac{1}{2} C_{\text{OSS}} V_{\text{OUTA(min)}}^2 \times f_s$$

$$P_{\text{COND_FET}} = R_{\text{DS(on)}} \times I_{\text{RMS_FET}}^2$$

$$P_{\text{FET_TR}} = \frac{1}{2} V_{\text{OUTA}} \times I_{\text{RMS_L}} \times t_r \times f_s$$

$$P_{\text{Q1}} = P_{\text{GATE}} + P_{\text{COSS}} + P_{\text{COND_FET}} + P_{\text{FET_TR}}$$

$$I_{\text{PK}} = \frac{P_{\text{OUTA}} \times \sqrt{2}}{\eta_1 \times V_{\text{IN(min)}}}$$

$$I_{\text{RMS_DIODE}} = \frac{P_{\text{OUTA}}}{\eta_1 \times V_{\text{IN(min)}}} \times \sqrt{\frac{16 \times V_{\text{OUTA}}}{3\pi \times \sqrt{2} \times V_{\text{IN(min)}}}}$$

$$P_{\text{COND_DIODE}} = V_f \times I_{\text{RMS_DIODE}}^2$$

$$P_{\text{DIODE_CAP}} = \frac{C_{\text{DIODE}}}{2} \times V_{\text{OUTA}}^2 \times f_{\text{SA}}$$

$$P_{\text{DIODE}} = P_{\text{COND_DIODE}} + P_{\text{DIODE_CAP}}$$

Heat sinks

The following equation can be used to calculate the minimum required thermal impedance of the heat sinks ($R_{\theta\text{sa}}$) for this design for Q1 and D3.

$$R_{\theta\text{sa}} = \frac{T_{\text{jmax}} - T_{\text{amb}} - P_{\text{semi}} \times (R_{\theta\text{cs}} + R_{\theta\text{jc}})}{P_{\text{semi}}}$$

The heat sink was designed to ensure that the junction temperature would not go above 75% of these devices' rated maximum with convection cooling, assuming a maximum ambient temperature of 60°C. The heat sink required for Q1 was an AVVID, part number 513201 B 0 25 00.

Output hold-up capacitor (C3) selection

The following equations were used to estimate the minimum hold-up capacitor (C3) size and the maximum allowable RMS current through the boost capacitor ($I_{\text{RMS_C3}}$).

$$C3 \geq 2 \times P_{\text{OUTA}} \times \frac{t_{\text{holdup}}}{V_{\text{OUTA}}^2 - (V_{\text{OUTA}} - V_{\text{drop}})^2}$$

$$I_{\text{RMS_C3}} = \frac{P_{\text{OUTA}}}{V_{\text{OUTA}}} \times \sqrt{\frac{16 \times V_{\text{OUTA}}}{3\pi \times V_{\text{IN(min)}} \times \sqrt{2}} - 1}$$

The hold-up capacitor was designed for 16.7 ms of hold-up time (t_{holdup}), allowing an output voltage drop (V_{drop}) of 85 V.

Peak-current limit for the boost power stage

Resistor dividers R14 and R29, along with current sense resistor R5, set up the peak-limit comparator of the UCC28517 that is used to protect the boost switch Q1 from excessive currents. This comparator should be set up so that it does not interfere with the boost converter's power limit or with the pulse-by-pulse current limiting of the step-down converters. For this design example, the flyback converter was designed to go into pulse-by-pulse current limiting at roughly 130% of maximum output power, and the power limit of the boost converter was set at 140% of the maximum output power. The peak-current limit for the boost stage was selected to engage at 150% of the maximum output power to ensure circuit stability.

The current sense resistor R5 was selected to operate over a 1-V dynamic range (V_{dynamic}) with the following equation.

$$R5 = R_{\text{SENSE}} = \frac{V_{\text{dynamic}}}{I_{\text{PK}} + 0.5 \times \Delta I}$$

The following equation can be used to size resistor R14 properly if R29 is first selected as a standard resistance value.

$$R14 = \frac{\left(\frac{P_{\text{OUTA}} \times 1.5 \times \sqrt{2}}{V_{\text{IN(min)}} \times \eta_1} + \Delta I \right) \times R5 \times R29}{V_{\text{REF}}}$$

Multiplier

The multiplier output of the UCC28517 is a signal representing the desired input line current. It is an input to the current amplifier, which programs the current loop to control the input current to give high-PF operation. As such, the proper functioning of the multiplier is key to the success of the design. The output of the multiplier, I_{MOUT} , can be expressed as

$$I_{MOUT} = I_{IAC} \frac{V_{ea(max)} - 1}{K \times V_{VFF}^2},$$

where K is a constant typically equal to $1/V$.

The I_{IAC} signal is obtained through a high-value resistor ($R_{IAC} = R18 + R24$) connected between the rectified ac line and the IAC pin of the UCC28517. This resistor is sized to give the maximum I_{IAC} current at the highest expected line voltage. For the UCC28517 the maximum I_{IAC} current is about $500 \mu A$. A higher current than this can drive the multiplier out of its linear range. A smaller current level is functional; but noise can become an issue, especially during low line voltages, assuming a universal line operation of 85 to 265 Vac gives an R_{IAC} value of 750 k Ω . Because of voltage-rating constraints of standard $\frac{1}{4}$ -W resistors, two or more lower-value resistors connected in series are needed to give roughly a 750-k Ω value and to distribute the high voltage across them.

The current through R_{IAC} is mirrored internally to the VFF pin, where it is filtered to produce a voltage feed-forward signal proportional to line voltage that is free of the 120-Hz ripple component. This second harmonic ripple component at the VFF pin is one of the major contributors to harmonic distortion in the system, so adequate filtering is crucial (see Reference 4). Assuming that an allocation of 1.5% total harmonic distortion from this input is allowed, and that the second harmonic ripple is 66% of the input ac line voltage, the amount of attenuation required by this filter is

$$\frac{1.5\%}{66\%} \approx 0.022 \text{ (see Reference 5).}$$

A ripple frequency (f_R) of 120 Hz and an attenuation of 0.022 gives us a single-pole filter with

$$f_p = 120 \text{ Hz} \times 0.022 = 2.6 \text{ Hz.}$$

The voltage at the VFF pin not only supplies a voltage feed-forward signal but also activates input current fold-back when the V_{VFF} drops below 1.5 V. Please see Reference 2 for a detailed explanation of how these control ICs provide power limiting. The following equations were used to size resistor R30 and filter capacitor C20.

$$R30 = \frac{1.5 \text{ V}}{\frac{V_{IN(min)} \times 0.9}{(R18 + R24) \times 2}}$$

$$C20 = \frac{1}{2\pi \times 30 \text{ k}\Omega \times 2.6 \text{ Hz}}$$

This results in a single-pole filter, which adequately attenuates the harmonic distortion and provides power limiting.

The multiplier's output resistor R19 is sized to match the maximum current through the sense resistor (R5) to the maximum multiplier current. R15 is sized to balance the offset current in the current amplifier and needs to be set to the same value as R19. The following equations were used to size R15 and R19.

$$I_{MOUT(max)} = \frac{I_{IAC} @ V_{IN(min)} \times (V_{ea(max)} - 1 \text{ V})}{K \times V_{VFF}^2}$$

$$R19 = R15 = \frac{V_{dynamic}}{I_{MOUT(max)}}$$

Current loop compensation for the boost converter

The following equation defines the gain of the power stage, where V_P is the maximum voltage swing of the UCC28517 oscillator ramp, roughly 5 V.

$$G_{ID}(s) = \frac{V_{OUTA} \times R5}{s \times L1 \times V_P}$$

To have a good dynamic response, the crossover frequency of the current loop was set to $\frac{1}{10}$ the switching frequency. This can be achieved by setting the gain of the current amplifier (G_{CA}) to the inverse of the current loop power-stage gain at the crossover frequency. For this design the current amplifier required a gain of 2.581 at 10 kHz. The following equations were used to compensate the current amplifier of the boost power stage.

$$G_{CA} = \frac{1}{G_{ID}(s)} = 2.581$$

$$R17 = G_{CA} \times R19$$

$$C19 = \frac{1}{2\pi \times R17 \times \frac{f_{SA}}{10}}$$

$$C22 = \frac{1}{2\pi \times R17 \times \frac{f_{SA}}{2}}$$

Voltage loop compensation for the boost converter

Figure 4 shows the small-signal-control block diagram for this application. The following equations describe small-signal gain as well as the voltage loop frequency response, $T_S(f)$.

$$H(s) = \frac{R20}{R20 + R32 + R32}$$

$$G_{c(s)} = g_m \times \frac{s(f) \times R28 \times C23 + 1}{s(f) \times (C23 + C25) \times \left(\frac{s(f) \times C23 \times C25}{C23 + 25} + 1 \right)}$$

$$G_{co(s)} = \frac{\Delta V_{OUTA}}{\Delta V_c} = \frac{P_{OUTA}}{V_{ea(max)} \times s \times V_{OUTA} \times C3}$$

$$T_S(f) = -H(s) \times G_{c(s)} \times G_{co(s)}$$


To reduce third-harmonic distortion, the voltage loop typically crosses over at roughly 10 to 12 Hz. For this design, the voltage-loop crossover frequency (f_c) was selected to be roughly 10 Hz. The following equations were used to select the components to compensate the voltage loop, $T_S(f)$, to cross over at the desired f_c with 45 degrees of phase margin.

$$R28 = 2\pi \times V_{ea(max)} \times f_c \times C3 \times \frac{V_{OUTA} \times \eta1}{g_m \times P_{OUTA} \times H(s)}$$

$$C23 = \frac{1}{2\pi \times R28 \times f_c}$$

C25 was selected to attenuate the 120-Hz output ripple voltage (V_{pp}) to 1.5% (% THD) of the voltage amplifier's dynamic output range.

Figure 4. dc/dc converter control loop

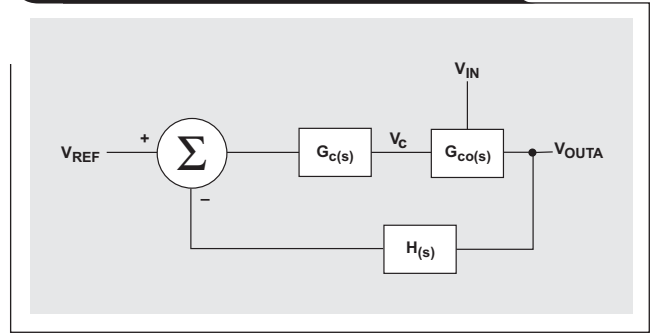

$$V_{pp} = \frac{P_{OUTA}}{\pi \times 120 \text{ Hz} \times C3 \times V_{OUTA}}$$

$$G_{vea} = \frac{\% \text{THD} \times V_{ea(max)}}{V_{pp} \times 100}$$

$$Z_{OUT} = \frac{G_{vea}}{H(s) \times g_m}$$

$$C25 = \frac{1}{2\pi \times Z_{OUT}}$$

After the design was complete, the frequency response of the voltage loop, $T_S(f)$, was measured with a network analyzer; and the results are shown in Figure 5. It can be observed that f_c was roughly 8 Hz with a phase margin of roughly 50 degrees.

Figure 5. Frequency response of power stage A

 


Figure 6. Output A THD vs. output power

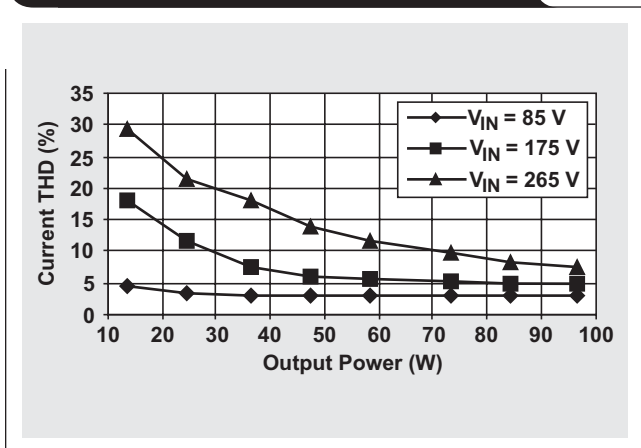


Figure 7. Output A efficiency vs. output power

 


Figure 8. Output A PF vs. output power


 


Figure 9. Output B efficiency vs. output efficiency

 

Summary

This article reviewed the design of a 100-W PFC ac/dc preregulator, which is the first stage in a two-stage power converter. The UCC2851X family of combination PWM controllers is perfect for offline applications that require PFC and auxiliary power supplies to meet different system requirements. The performance of this two-stage power converter is shown in Figures 6–9.

References

For more information related to this article, you can download an Acrobat Reader file at www-s.ti.com/sc/techlit/litnumber and replace “litnumber” with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. Laszlo Balogh, “Design Review: 140W, Multiple Output High Density DC/DC Converter,” p. 6-9	.slup117
2. Laszlo Balogh, “Unitrode – UC3854A/B and UC3855A/B Provide Power Limiting With Sinusoidal Input Current for PFC Front Ends,” Unitrode Design Note	.slua196

Document Title	TI Lit. #
3. Lloyd Dixon, “Control Loop Cookbook,” p. 5-17	.slup113
4. Lloyd Dixon, “Optimizing the Design of a High Power Factor Switching Preregulator,” pp. 7-11–7-12	.slup093
5. James P. Noon, “A 250kHz, 500W Power Factor Correction Circuit Employing Zero Voltage Transitions,” pp. 1-11–1-14	.slup106
6. “Practical Considerations in Current Mode Power Supplies,” Unitrode Application Note	.slua110
7. “Advanced PFC/PWM Combination Controllers,” Data Sheet	.slus517
8. “UCC28517 EVM User’s Guide”	.sluu117

Related Web sites

analog.ti.com
www.ti.com/sc/device/TL431
www.ti.com/sc/device/UCC28517

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page
support.ti.com

TI Semiconductor KnowledgeBase Home Page
support.ti.com/sc/knowledgebase

Product Information Centers

Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	support.ti.com/sc/pic/americas.htm		

Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 7850415
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	1800 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	support.ti.com/sc/pic/euro.htm		

Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	support.ti.com/sc/pic/japan.htm		
Domestic	www.tij.co.jp/pic		

Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	New Zealand	0800-446-934
China	800-820-8682	Philippines	1-800-765-7404
Hong Kong	800-96-5941	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Malaysia	1-800-80-3973		
Fax	886-2-2378-6808	Email	tiasia@ti.com
Internet	support.ti.com/sc/pic/asia.htm		ti-china@ti.com

C011905

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

Trademarks: All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

© 2005 Texas Instruments Incorporated

SLYT097