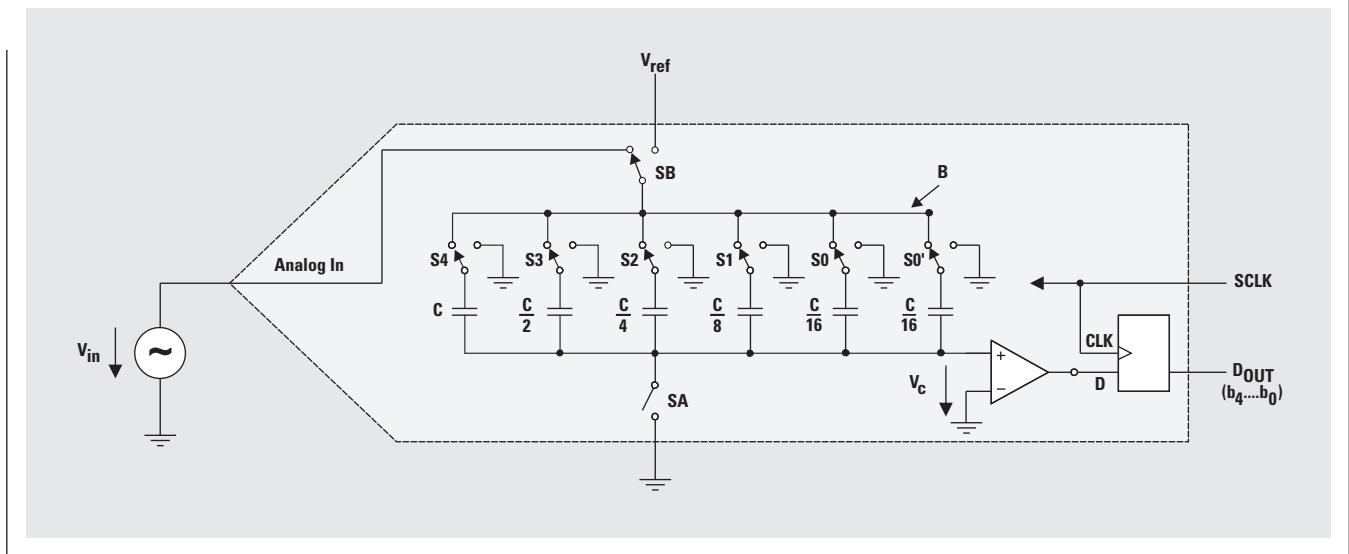


# The operation of the SAR-ADC based on charge redistribution

By Thomas Kugelstadt

Application Manager

Figure 1. Five-bit SAR-ADC based on charge redistribution



All Texas Instruments TLV- and TLC-series sequential serial analog-to-digital converters perform successive approximation based on charge redistribution. This article explains the operation of the SAR (successive approximation register)-ADC (analog-to-digital converter). It provides a concise description of a model SAR-ADC based on charge redistribution. Figure 1 shows the simplified circuit of a 5-bit charge redistribution converter using switched capacitor architecture.

All capacitors have binary weighted values, i.e.,  $C$ ,  $C/2$ ,  $C/4$ , ...,  $C/2^{n-1}$ . The last two capacitors having the value  $C/2^{n-1}$  are connected so that the total capacitance of the  $n+1$  capacitors is  $2C$ . MOS-transistors are used to implement the required  $n+3$  switches, and the voltage comparator provides the appropriate steering of the switches via auxiliary logic circuitry. The conversion process is performed in three steps: the sample mode, the hold mode, and the redistribution mode (in which the actual conversion is performed).


## Sample mode

In the sampling mode (Figure 2), switch SA is closed and SB is switched to the input voltage  $V_{in}$ . The remaining switches are turned to the common bus B. Due to charging, a total charge of  $Q_{in} = -2C \times V_{in}$  is stored on the lower plates of the capacitors.

## Hold mode

During the hold mode (Figure 3), switch SA is opened while the switches  $S4 \dots S0'$  are connected to ground,

Figure 2. Sample mode

 

thereby applying a voltage of  $V_c = -V_{in}$  to the comparator input. This means that the circuit already has a built-in sample-and-hold element.

### Redistribution mode

The actual conversion is performed by the redistribution mode. The first conversion step, shown in Figure 4, connects C (the largest capacitor) via switch S4 to the reference voltage  $V_{ref}$ , which corresponds to the full-scale range (FSR) of the ADC.

Capacitor C forms a 1:1 capacitance divider with the remaining capacitors connected to ground. The comparator input voltage becomes  $V_c = -V_{in} + V_{ref}/2$ . If  $V_{in} > V_{ref}/2$ , then  $V_c < 0$ , and the comparator output goes high, providing the most significant bit MSB (bit 4) = 1. On the other hand, if  $V_{in} < V_{ref}/2$ , then  $V_c > 0$ , and bit 4 = 0.

The second conversion step connects C/2 to  $V_{ref}$ . If the first conversion step resulted in bit 4 = 1, switch S4 is turned to ground again to discharge C as shown in Figure 5; otherwise it remains connected to  $V_{ref}$  if bit 4 = 0 (Figure 6), resulting in a comparator input voltage  $V_c = V_{in} + \text{bit } 4 - V_{ref}/2 + V_{ref}/4$ .


According to this voltage, the next most significant bit (bit 3) is obtained by comparing  $V_{in}$  to  $1/4 V_{ref}$  or  $3/4 V_{ref}$  through the different voltage dividers. Switch S3 is then either turned to ground if bit 3 = 1, thereby discharging C/2, or S3 remains connected to  $V_{ref}$  if bit 3 = 0.

This process continues until all bits are generated, with the final conversion step being performed at a comparator input voltage of  $V_c = -V_{in} + \text{bit } 4 \times V_{ref}/2 + \text{bit } 3 \times V_{ref}/4 + \text{bit } 2 \times V_{ref}/8 + \text{bit } 1 \times V_{ref}/16 + \text{bit } 0 \times V_{ref}/32$ .


### Related Web site

[www.ti.com/sc/docs/products/msp/dataconv/index.htm](http://www.ti.com/sc/docs/products/msp/dataconv/index.htm)


**Figure 3. Hold mode**

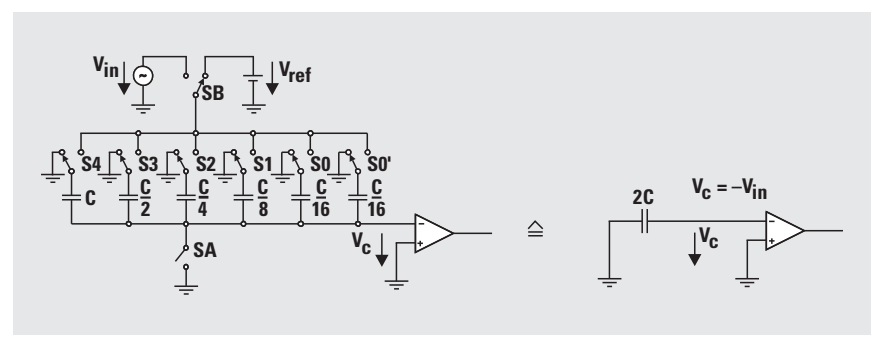


**Figure 4. Conversion Step 1 determines the MSB (bit 4)**

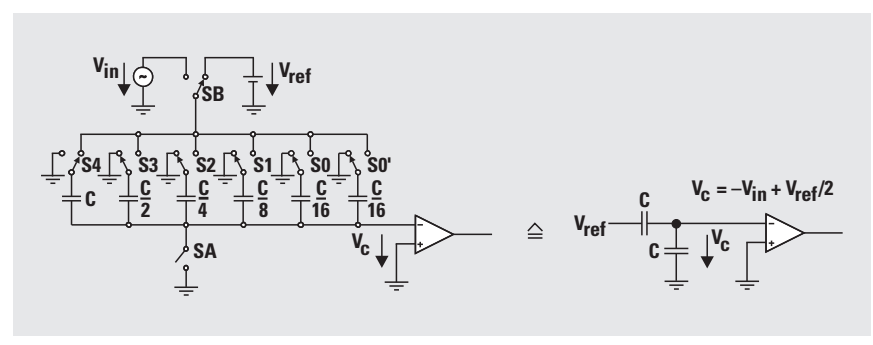

**Figure 5. If bit 4 = 1,  $V_{in}$  is compared with  $3/4 V_{ref}$**

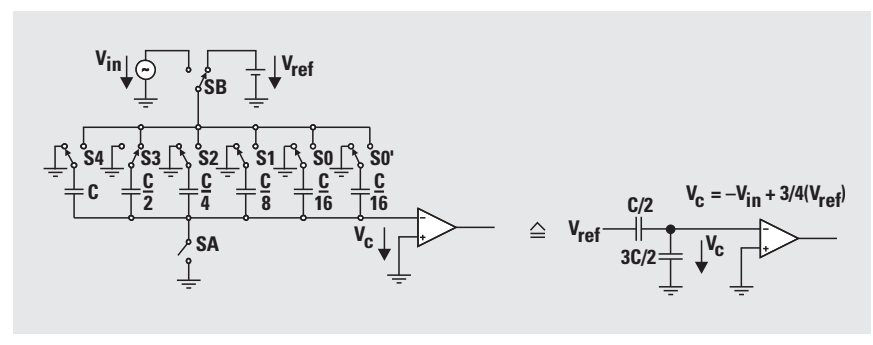

**Figure 6. If bit 4 = 0,  $V_{in}$  is compared with  $1/4 V_{ref}$**

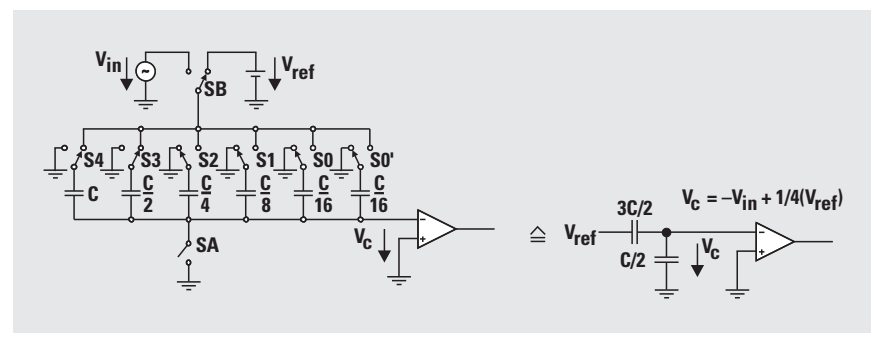

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2019, Texas Instruments Incorporated