

Migrating from the TI TL770x to the TI TLC770x

By Benjie Balsler

Application Specialist, Product Information Center

Device functionality

The TI TL770x is a proven processor supervisory circuit built in bipolar technology, however, one of the consequences of using bipolar technology is the requirement for high supply current. To meet the demand of low supply current in battery applications, Texas Instruments introduced the CMOS TLC770x family of supervisors. Since the TL770x and TLC770x are not drop-in compatible, some modifications must be made to convert a design for the bipolar part to a CMOS-based design. Those modifications are detailed in this application note. With the exception of pin 1, the devices are pin-for-pin compatible.

Circuit changes

Pin 1 of the TL770x is a reference pin and a 0.1- μ F capacitor is recommended to reduce the influence of fast transients in the supply voltage. This was not deemed necessary for the TLC770x, so the part was given added functionality. On the TLC770x, pin 1 adds power-down support for static RAM. When the TLC770x's pin 1 (CONTROL) is left floating (there is an internal pull-down resistor), RESET will act as active high. The voltage monitor contains additional logic intended for control of static memories with battery backup during power failure. Figure 2 shows the configuration for driving the chip select (/CS) of the memory circuit with the RESET output of the TLC770x while the CONTROL input is driven by the microprocessor's memory bank select signal (/CSH1). The memory circuit is automatically disabled during a power loss. In most applications, this function is not needed and leaving the pin floating retains the part's normal functionality.

Timing


The delay timing of the two parts is also different due to their internal current sources. Figure 3 shows the timing equations used to determine the time delay (t_d) for the A and B version of the bipolar TL770x and for the TLC770x CMOS device.

Another difference between the TL770x and TLC770x is the requirement for pull-up and pull-down resistors on the TLC770x reset outputs; the TLC770x does not have

Figure 1. Different functionality of pin 1

	TLC77XX			TL77XX			
CONTROL	1	8	VDD	REF	1	8	VCC
RESIN	2	7	SENSE	RESIN	2	7	SENSE
CT	3	6	RESET	CT	3	6	RESET
GND	4	5	RESET	GND	4	5	RESET


Figure 2. Data retention during power-down

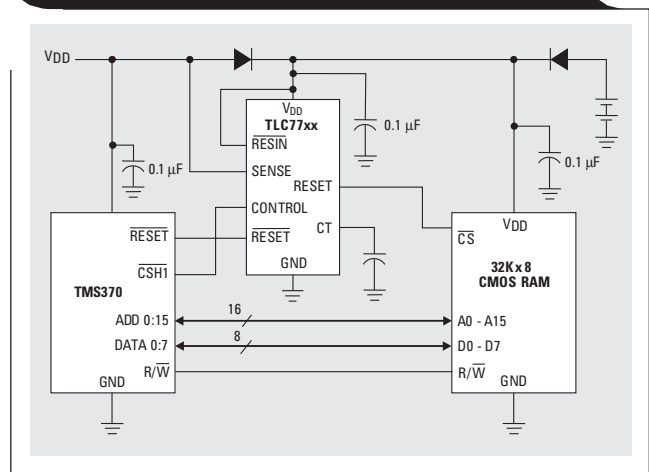

this requirement. The bipolar device uses open collector outputs and the CMOS device has push-pull outputs (see Figure 4).

Finally, the internal reference voltage is different for the two devices. The reference voltage on the bipolar part is 2.5 V, whereas the reference voltage for the CMOS part is 1.1 V. This will only affect the design of the adjustable part when selecting the resistor divider values between the supply and sense lines.

Figure 3. Definition of delay time, t_d

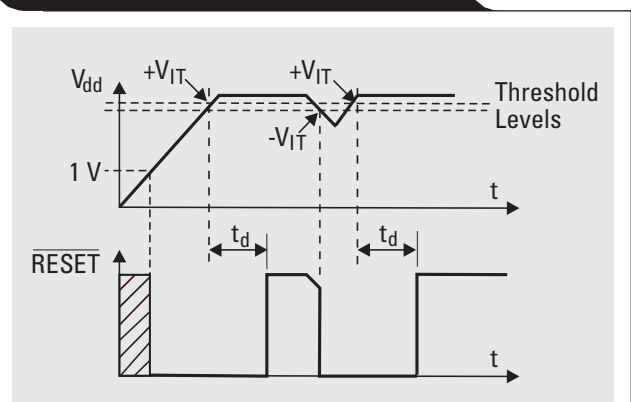

- TL770xA: $t_d = 1.3 \times 10E4 \times C_T$ (1)
- TL770xB: $t_d = 2.6 \times 10E4 \times C_T$ (2)
- TLC770x: $t_d = 2.1 \times 10E4 \times C_T$ (3)

where t_d = delay time in seconds and C_T = capacitance in farads.

Figures 5 and 6 show a comparison of the functional block diagrams of both circuits.

Summary

To convert a design from the bipolar TL770x to the CMOS TLC770x, the following circuit changes must be made:

1. Remove the capacitor on pin 1.
2. Change the value of the timing capacitor according to the timing equations.
3. Remove the pull-up and pull-down resistors on the reset outputs.
4. Recalculate the resistor divider based on the different reference voltage (only necessary for the adjustable part).

Figure 4. Totem-pole vs. open collector outputs

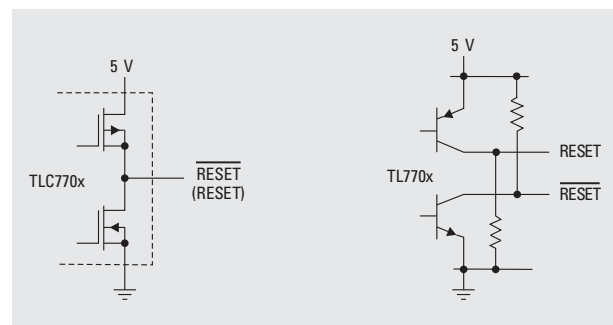


Figure 5. Internal functional diagram of the CMOS TLC770xx


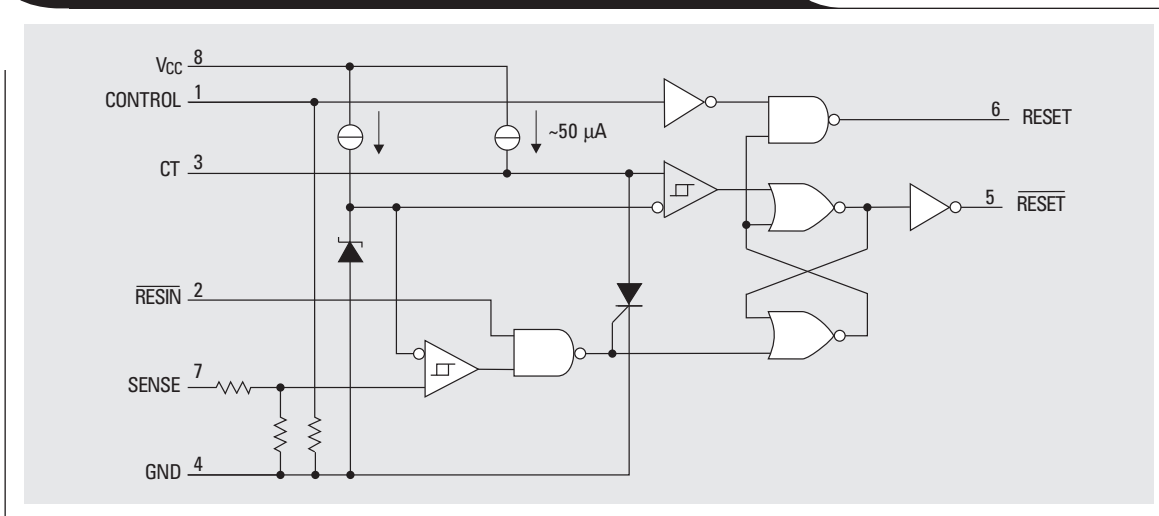


Figure 6. Internal functional diagram of the bipolar TL770xx

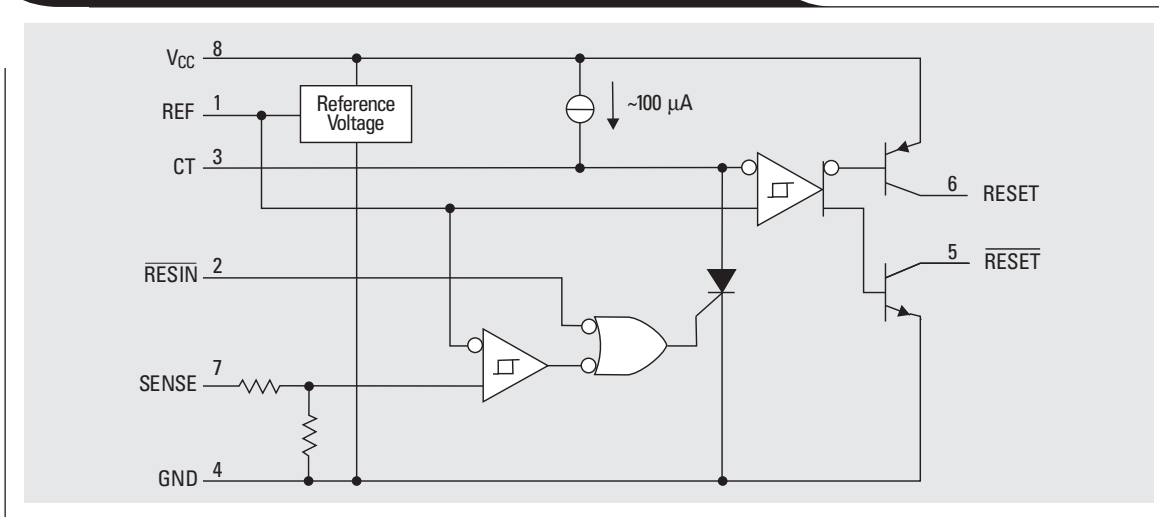

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page
support.ti.com

TI Semiconductor KnowledgeBase Home Page
support.ti.com/sc/knowledgebase

Product Information Centers

Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	support.ti.com/sc/pic/americas.htm		

Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 7850415
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	1800 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	support.ti.com/sc/pic/euro.htm		

Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	support.ti.com/sc/pic/japan.htm		
Domestic	www.tij.co.jp/pic		

Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	New Zealand	0800-446-934
China	800-820-8682	Philippines	1-800-765-7404
Hong Kong	800-96-5941	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Malaysia	1-800-80-3973		
Fax	886-2-2378-6808	Email	tiasia@ti.com
Internet	support.ti.com/sc/pic/asia.htm		ti-china@ti.com

C011905

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

Trademarks: All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

© 2005 Texas Instruments Incorporated