

AN-914 Understanding Power Requirements in RS-232 Applications

ABSTRACT

This application note covers the RS-232 circuit functions, an explanation of hardware handshaking, a step by step analysis of the hardware handshaking between a local and remote terminal, and power requirements/dissipation of the DS14C335.

Contents

1	Introduction	2
2	RS-232 Handshaking Circuits	2
3	Hardware Handshake Flow	3
4	Power Consumption	4
5	DS14C335 and Power Consumption	5
6	Other Industry Standards (RS-232)	7
7	Conclusion	8
8	References	8

List of Figures

1	Direction of Flow from DTE/DCE	2
2	DTE to DCE Interface	3
3	Graphical Illustration of Hardware Handshaking.....	4
4	Load Seen by the Driver	4
5	Simultaneous Conduction and I_{CC}	5
6	DS14C335 Supply Current vs Frequency vs Driver Loads, All Driver and Receiver Switching.....	6
7	DS14C335 Supply Current vs Frequency vs Driver Loads, One Driver (TXD) Switching.....	6
8	DS14C335 Supply Current vs Frequency (Receiver), One Receiver (RXD) Switching	6
9	DS14C335 Supply Power vs Data Rate	7
10	Noise Margin Comparison	8

1 Introduction

As the popularity of asynchronous serial communication became widely accepted by the industry, the RS-232 standard gained very wide acceptance. The use of this standard is visible in almost all Industrial, Portable, Desktop, Data Acquisition and Test Measurement applications using a serial port for communication. Even though the standard specifies a maximum data rate for RS-232 of 20 kbps, some applications need for higher speed is overwhelming. More and more applications today require at least 120 kbps to support Laplink, a popular communication software used by Laptop/Desktop computers for fast file transfer between two computers. RS-232 type Drivers and Receivers must also support this higher data rate to be Laplink compatible.

2 RS-232 Handshaking Circuits

In a Terminal (DTE-Data Terminal Equipment) to Modem (DCE-Data Circuit Terminating Equipment) application, as shown in [Figure 2](#), commonly only eight dedicated lines are required. Even though the standard defines a 25 pin connection, the de-facto 9 pin connector is very popular. These lines are DCD, RXD, TXD, DTR, DSR, RTS, CTS, RI and GND and are shown in [Figure 1](#). Note that ON is defined as a positive voltage and OFF is a negative voltages on the cable. [Table 1](#) lists these dedicated lines along with their respective functions.

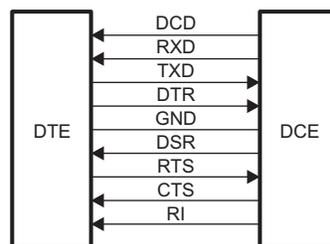


Figure 1. Direction of Flow from DTE/DCE

Table 1. Dedicated Lines and Functions

Signal Name	Description
DCD: Data Carrier Detect (DCE to DTE)	When this circuit is OFF locally, it indicates to the local terminal that the remote DTE has not switched its RTS circuit ON yet and the local terminal can gain control over the carrier line if needed. When this circuit is ON locally, it indicates to the local terminal that the remote modem has received a RTS ON condition from its terminal and the remote DTE is in control over the carrier line
RXD: Receive Data (DCE to DTE)	Receive data circuit from modem to DTE.
TXD: Transmit Data (DTE to DCE)	Transmit data circuit from DTE to modem.
DTR: Data Terminal Ready (DTE to DCE)	The DTR pin is generally ON when the terminal is ready to establish communication channel through its modem. By keeping the DTR circuit ON the DTE lets an "auto answer" modem accept the call unattended. The DTR circuit is OFF, only when the DTE does not want its modem to accept calls from remote locations. This is known as <i>local mode</i> .
DSR: Data Set Ready (DCE to DTE)	Both modems switch their DSR circuit ON when a communication path has been established between the two sites (local and remote modem)
RTS: Request To Send (DTE to DCE)	When a terminal is ready to transmit data, it switches the RTS circuit ON, indicating to the local modem that it is ready to transmit data. This information also gets passed to the remote modem. The RTS line controls the direction of data transmission. During transmit mode, the line is ON and during receive mode it's OFF.
CTS: Clear To Send (DCE to DTE)	When CTS switches ON, the local modem is ready to receive data from its DTE and the local modem has control over the telephone lines for data transmission.
RI: Ring Indicator (DCE to DTE)	When the modem receives a call, the RI circuit switches ON/OFF in sequence with the phone ringing informing the DTE that a call is coming in. This indicates that a remote modem is requesting a dial-up connection.
GND	Ground, signal common

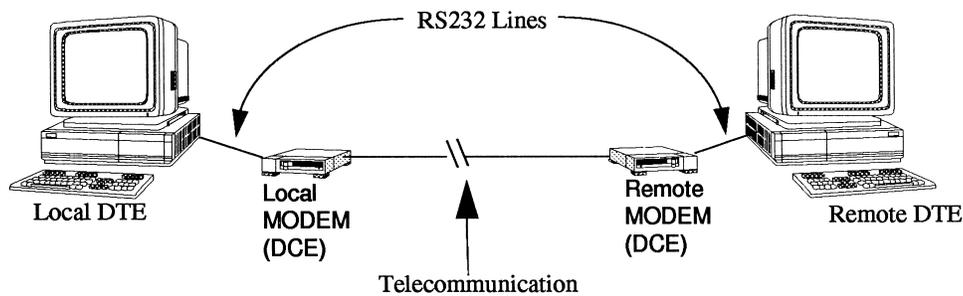


Figure 2. DTE to DCE Interface

3 Hardware Handshake Flow

A step by step analysis of handshaking illustrates how each circuit is used to establish communication between a local and a remote site. To keep the subject simple, assumption has been made that transmission is from Local to Remote only. Hardware handshaking is shown in [Figure 3](#) .

1. Local DTE switches DTR ON and local modem dials the phone number of the remote modem.
2. If DTR at remote location is ON, the remote modem's RI turns ON/OFF in sequence with the phone ringing, indicating a call coming in.
3. The remote modem returns an answer-back tone to the local modem. Upon detection of this tone, the local modem and the remote modem establishes the on-line connection. At this point both modems switch their DSR pins ON indicating that a connection has been established.
4. The local DTE switches RTS ON indicating that it is ready to send data. This signal gets passed on to the remote modems DCD circuit.
5. The local modem checks to make sure that local DCD is OFF, which indicates that the remote modem is not in control of the carrier line.
6. The local modem then switches CTS ON to the local DTE to inform that it can start sending data. Locally the DCD circuit stays OFF. On the remote modem DCD stays ON. RTS is held ON by the local DTE throughout the duration of the connection.
7. The local DTE sends data through TXD to modem for transmittal.
8. The remote modem receives the data and sends the data to its terminal via the RXD circuit.
9. When data transmittal is finished, local DTE drops RTS, which drops the DCD at remote modem and CTS at local modem. Transmission of data can be discontinued by hanging up the phone line, by the DTE dropping its DTR circuit, by disconnecting the modem cable from the DTE.
10. Now, either DTE is ready to start all over again and gain control of the telecommunication line.

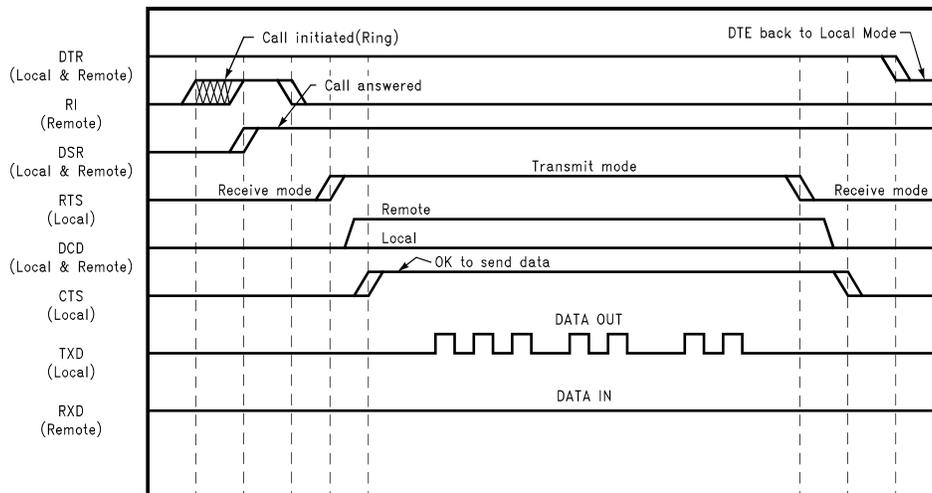


Figure 3. Graphical Illustration of Hardware Handshaking

From the above explanations, in half-duplex communication, we can derive that in transmit mode, only one driver (TXD) is switching (up to 120 kbps) while the other drivers/receivers are at some known steady state (not switching). Similarly, on a receive mode, only one receiver (RXD) is switching while other lines maintain known steady state levels.

4 Power Consumption

Based on the above observations, let's determine how I_{CC} , frequency, internal/external capacitance and load resistance play a role in power consumption for the DS14C335. Total power consumption is the static and the dynamic power combined. CMOS devices typically consume minimal power in a static condition. This can be calculated simply by multiplying I_{CC} with V_{CC} .

Under a loaded condition, the external loading of the driver directly effects the power dissipation of the device and application. The RS-232 driver is normally connected to a cable and a receiver at the far end. Since the transition time of the driver is set to be substantially longer than the cable delay, the cable load represents a lumped capacitive load and a series resistance. The series resistance on short cables (< 200 feet) can be neglected since it is very small compared to the receiver input resistance. This means the cable may be modeled as a lumped capacitive load equal to the capacitance per unit length multiplied by the length of the cable. 1000 pF is commonly used to represent a 20 foot cable, and 2500 pF is used as the maximum specified cable load. The receiver input resistance is specified to be between 3 kΩ and 7 kΩ, 5 kΩ is used as a typical, and 3 kΩ is the worst case from a power point of view. This equivalent load is illustrated in [Figure 4](#).

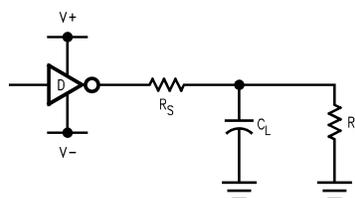


Figure 4. Load Seen by the Driver

Where: — R_S = Cable series resistance.

- C_L = Cable load capacitance.
- R_{IN} = Input resistance of the Receiver.

A channel that is in a steady state is loaded by the receiver's input impedance since the cable capacitance has charged up. The output current of the driver is determined by the output voltage of the driver (V_{OH} or V_{OL}) divided by the input resistance of the receiver. For example, a 7V level, across the 3 k Ω load, requires 2.3 mA.

Dynamic power consumption has three major components. The switching current (spike current, also commonly called Conduction Overlap Current) during transitions, external load resistance and external load capacitance transient dissipation.

When the voltages to an NMOS/PMOS pair are in transition, both transistors turn on partially, creating a relatively low impedance path between the supply rails ($V+$ and $V-$). This is known as simultaneous conduction and is illustrated in Figure 5. As input frequency increases, the period decreases. At some point the output transistors fail to charge and discharge fully causing both upper and lower output transistor to stay on momentarily. This simultaneous conduction increases I_{CC} as the input signal's frequency is increased.

The charging and discharging of the large load capacitance C_L contributes to power consumption as well. The external load capacitance increases power in the same manner as the internal capacitance. A channel that is switching at speed is affected by all the components described previously. These new components contribute to the increased output current sourced or sunk by the driver to charge or discharge the capacitive load. This component of the load current will increase if the external capacitance is increased and also if the switching rate of the device is increased.

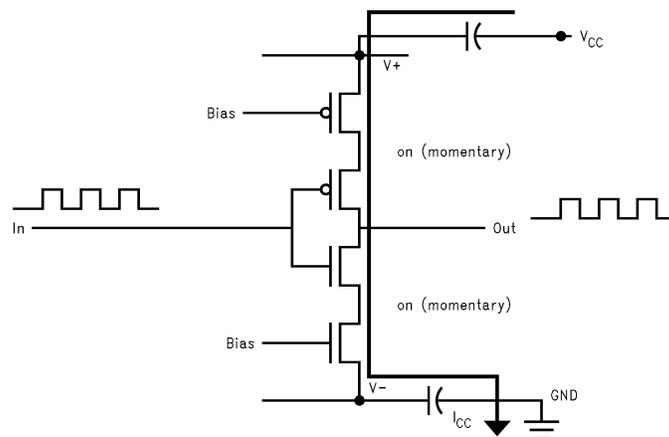


Figure 5. Simultaneous Conduction and I_{CC}

5 DS14C335 and Power Consumption

TI's DS14C335 is a 3 X 5 Driver/Receiver combination providing a one-chip solution for a 9 pin RS-232 DTE application. Figure 6 shows a worst case situation where all 3 drivers and 5 receivers are switching under different loading conditions. Under this worst case condition, at 10 kHz (20 kbps), supply current is 30 mA (2500 pF). Under a no load condition, supply current stays relatively flat. Figure 7 shows a true RS-232 application where one driver (TXD) is switching while the other two (DTR and RTS) remain High (loaded) as shown in Figure 3. At 10 kHz, supply current reads 26 mA (2500 pF), under this real world RS-232 application. Decreasing the capacitive load also decreases the supply current as shown in Figure 7. Figure 8 illustrates one receiver (RXD) switching. Supply current is almost constant under this operating condition.

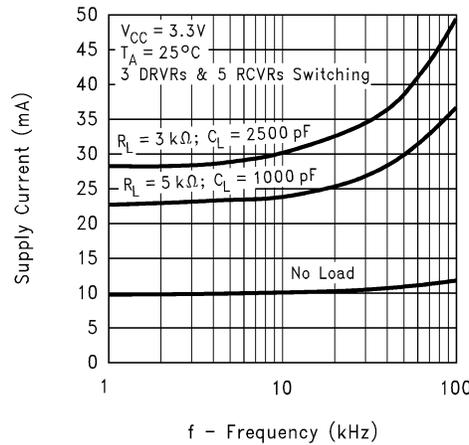


Figure 6. DS14C335 Supply Current vs Frequency vs Driver Loads, All Driver and Receiver Switching

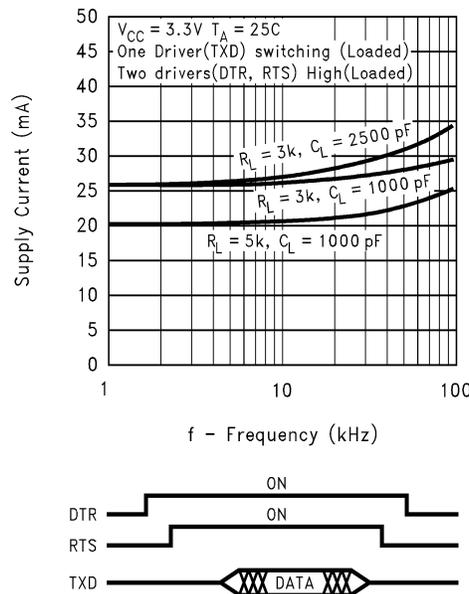


Figure 7. DS14C335 Supply Current vs Frequency vs Driver Loads, One Driver (TXD) Switching

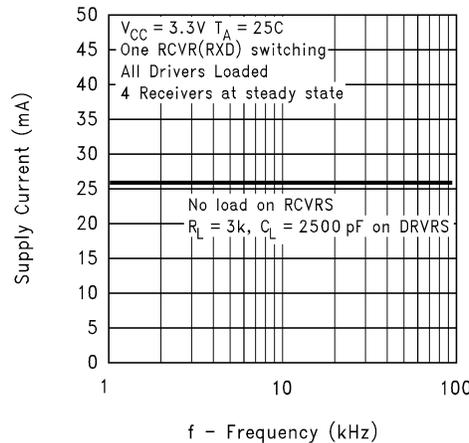


Figure 8. DS14C335 Supply Current vs Frequency (Receiver), One Receiver (RXD) Switching

Looking at the Supply Power vs Data Rate (Figure 9) we can see that under multiple driver switching and at a maximum data rate of 120 kbps, the supply power is 120 mW (2500 pF load). With one driver switching and the other two driver output at High (RS-232 Application), the supply power at maximum data rate of 120 kbps drops to 103 mW (2500 pF load).

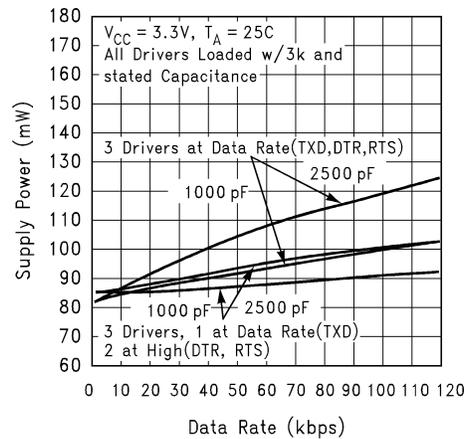


Figure 9. DS14C335 Supply Power vs Data Rate

The DS14C335 also offers a SHUTDOWN (SD) feature where the device can be de-activated by applying a logic High on the SD pin. This will lower the supply current to less than 1 μ A (typical). In addition, in this mode one receiver (R5) remains active to monitor R1 (Ring Indicator). This active receiver can sense incoming calls and inform the power management circuit to activate the device. SHUTDOWN mode saves battery life when the serial port is not used. In this mode, power dissipation is only 3.3 μ W allowing battery charge to be used by other active circuitry.

6 Other Industry Standards (RS-232)

RS-562 is another standard that is gaining popularity in the Industry. RS-562 is compatible to RS-232, however, there are some trade-offs. Table 2 illustrates a comparison and the major differences between the two standards.

Table 2. Comparison and Major Differences between RS-232 and RS-562

Specifications	RS-232	RS-562
Mode of Operation	Single-ended	Single-ended
Receiver Input Resistance (Ω)	3 k Ω to 7 k Ω	3 k Ω to 7 k Ω
Receiver Sensitivity	± 3 V	± 3 V
Driver Output Current (Powered Off, ± 2 V)	± 6.67 mA (300 Ω)	± 6.67 mA (300 Ω)
Driver Output Short Circuit Current Limit	≤ 100 mA	≤ 60 mA
Number of Drivers and Receivers Allowed	1 Driver 1 Receiver	1 Driver 1 Receiver
Max Cable Length	$\sim 50'$ (2500 pF)	2500 pF (20 kbps) 1000 pF (64 kbps)
Max Data Rate	20 kbps	64 kbps
Driver Output	± 5V Min ± 15V Max	± 3.7V Min ± 13.2V Max
Driver Load	3 k Ω to 7 k Ω	3 k Ω to 7 k Ω
Driver Slew Rate	≤ 30 V/ μ s	≤ 30 V/ μ s

Even though RS-562 standard specifies data rates greater than RS-232, the DS14C335 (RS-232) far exceeds the 64 kbps of RS-562. The most significant difference between the two standards is the noise margin. As shown in Figure 10, RS-232 devices have a noise margin of 2V or greater. Typically for DS14C335, the noise margin is 4.5V (7.5V – 3V) whereas RS-562 has a noise margin as low as 700 mV (3.7V – 3V). A lower noise margin (RS-562) means limited rejection of external noise, crosstalk and ground potential differences which can all commonly occur in RS-232 type communication.

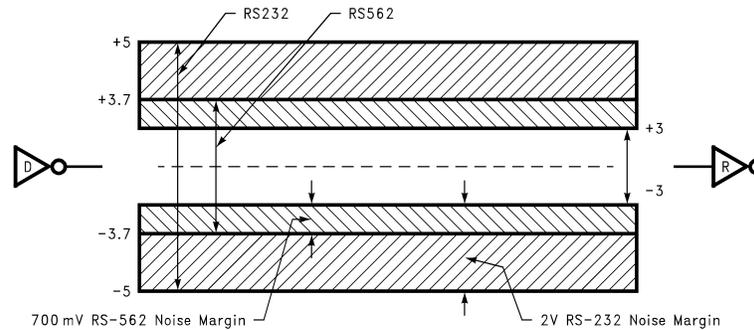


Figure 10. Noise Margin Comparison

7 Conclusion

Design Engineers are plagued with ground shift, noise problems and a noise margin of only 700 mV is not acceptable in many applications. RS-232 ensures a 2V noise margin and TI's DS14C335 is the preferred choice for applications requiring data rates pushing 120 kbps. Also, we have observed that in a half-duplex RS-232 DTE to DCE application, the supply current of the device is lower than simultaneous switching of all drivers and receivers as the application only requires one driver (TXD) or one receiver (RXD) switching at a time while the rest of the drivers/receivers maintain known steady state levels. Along with the power dissipation calculations, a discussion of the SHUTDOWN feature was also presented. This SHUTDOWN mode is highly desirable for any application that is battery powered, as it saves battery charge when the serial port is inactive.

8 References

Piecewise analysis and accurate emulation yield precise power estimates, William Hall and Ray Mentzer, *EDN March 16, 1992*.

CMOS, the Ideal Logic Family, Stephen Calebotta, Texas Instruments, *Application Note AN-77*.

54C/74C Family Characteristics, Thomas P. Redfern, Texas Instruments, *Application Note AN-90*.

HC-MOS Power Dissipation, Kenneth Karakotsios, Texas Instruments, *Application Note AN-303*.

RS-232 Made Easy: Connecting Computers, Printers, Terminals and Modems, Martin D. Seyer.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com