

# COP8ACC

*Application Note 1075 Smart Battery Charging with COP8ACC*



Literature Number: SNOA001

# Smart Battery Charging with COP8ACC

National Semiconductor  
Application Note 1075  
Sayeed Rahman  
May 1997



## INTRODUCTION

The availability of embedded controllers with increased functionality, and performance for fewer dollars has resulted in their tremendous proliferation in virtually every electronic gadget we own in our households today. Many of these applications require a high resolution A/D converter for precision measurements of analog signals from the real world. A rapid conversion is often a necessity to allow ample time for the controller to sort, sample, analyze, and transmit the continuously varying analog signals. In today's battery chargers, the temperature, voltage, and charge current are often monitored to determine the state of the charge, and consequently, how to charge the batteries. These batteries require precision charging, for a slight overcharge can significantly reduce battery life. National's COP8ACC microcontroller with high resolution, high speed, and single slope A/D converter is well suited for the battery charger application.

## BATTERY CHARGING

In the past few years, many new battery technologies have emerged. High demand has driven the technology toward lighter weight batteries with higher capacities. This has resulted in the evolution of many new battery chemistries and their emergence in portable applications, making chargers increasingly complex. We often see one application using multiple chemistries. This added complexity has induced a migration from chargers based solely on discrete components to chargers with embedded intelligence in low-cost 8-bit microcontrollers.

Inherent nonlinear characteristics of battery chemistries impose significant challenges to charger designers. Researchers have developed various intelligent charging algorithms that accurately charge batteries, providing maximum capacity after each charge, and increased overall battery life (increased number of cycles). Charging time has been reduced significantly. These algorithms require the microcontroller to monitor charge status as well as battery parameters. These parameters include, but are not limited to, battery voltage, temperature, and charge current. This information is manipulated by the algorithm to determine the required charge current, and to terminate charging accurately. Accurate charge termination is critical, for premature termination means less usage time, and over-charge results in significant battery damage.

## FEATURES OF COP8ACC

The COP8ACC integrates up to 6 channels of a high resolution, single slope A/D converter, a key feature for intelligent chargers. This device also offers a processor-independent PWM timer for easy, accurate control of the charge current. Up to 4 kbytes of program memory suffices to embed complex intelligent charge control algorithms. Often, chargers display the state of charge with LEDs. High sink/source capability on up to 4 pins provides that capability. The Microwire circuit allows simple serial communication to the battery pack's internal circuitry, or an EEPROM. Additionally, two low power-consumption modes (halt and idle) provide all the necessary ingredients for a battery charging application.

## ANALOG TO DIGITAL CONVERSION

Figure 1 shows a block diagram of the single slope, comparator based A/D converter. Using this approach an A/D converter can be configured by using only a single external capacitor. This capacitor provides the designer flexibility in controlling the resolution and conversion time. The external capacitor should be grounded on one side, and the positive terminal should be reset to 0V by momentarily shorting the capacitor through software control. An internal  $V_{CC}/2$  reference can be used to calibrate the A/D conversion. For a more accurate reference, the designer has the option to use one of the available analog input channels for this purpose, by supplying to it a known external voltage. At the beginning of a conversion cycle, the constant current source starts charging the capacitor. The voltage across the capacitor increases linearly. When this voltage exceeds the sampled voltage at the positive terminal of the comparator, the comparator output toggles to stop the capture timer. The value in the capture timer is analogous to the sampled voltage. The capture timer is clocked directly by CKI (the clock input of the COP8ACC) at up to 10 MHz frequency. This provides a high speed conversion time.

The slope of the increasing voltage can be controlled by controlling the size of the capacitor. This in turn controls the time it takes for the comparator output to toggle. Longer time to toggle translates to a more accurate or a higher resolution conversion.

The resolution of this A/D converter can be calculated by,

$$X_{res(min)} = \log_2 (CdV / I_{max} tc), \text{ where } C = \text{value of capacitance (nF)} \quad (2)$$

$I_{max}$  = max. current from current source (A)

$dV$  = range of channel input voltage (V)

$tc$  = ext. clock cycle time or period (CKI = < 10 MHz) (sec)

$X_{res}$  = resolution of conversion (bits)


Based on the above formulas, a minimum resolution of approximately 10 bits can be reached, when using 4 nF capacitor, with an external clock of 4 MHz, a  $dV$  of 2.5V, and a maximum current of 35  $\mu$ A. The constant current on this device is specified to be in the range of 7  $\mu$ A to 35  $\mu$ A. A typical value for this current is about 20  $\mu$ A. The conversion time for the above scenario can be calculated using the following formula,

$$t_{conversion} = 2^{X_{res(min)}} \cdot tc \quad (3)$$

The conversion time for this scenario turns can be calculated to be approximately 0.26 ms. Table 1 shows various clock speeds versus conversion time, resolution, and achievable accuracy. The accuracy of the conversion depends on noise, drifting of RC clock, inaccuracies in the voltage reference, etc.

**TABLE 1. Clock Speed vs Resolution, Conversion Time, and Achievable Accuracy**

Clock Speed	Resolution	Conversion Time	Achievable Accuracy
10 MHz	12 Bits	0.410 ms	±2.0 LSB
10 MHz	8 Bits	0.026 ms	±1.0 LSB
5 MHz	13 Bits	1.640 ms	±2.5 LSB
4 MHz	10 Bits	0.260 ms	±1.5 LSB
2 MHz	11 Bits	1.300 ms	±1.5 LSB
1 MHz	12 Bits	4.100 ms	±1.5 LSB
1 MHz	10 Bits	1.025 ms	±1.0 LSB
1 MHz	8 Bits	0.260 ms	±1.0 LSB

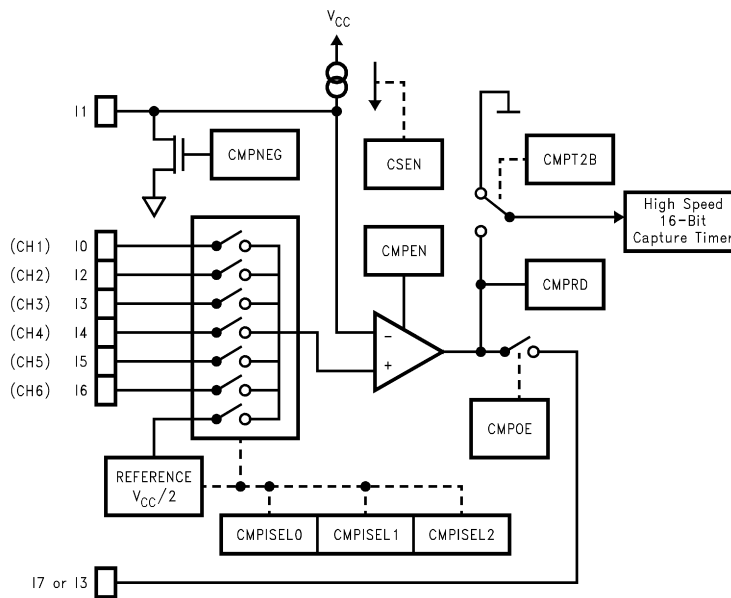

**FIGURE 1. Analog Function Block**

AN100027-1

**USING THE COP8ACC IN A BATTERY CHARGER**

Here we present a NiMH/NiCd dual chemistry charger as an example. The COP8ACC A/D channels monitor battery pack voltage, and temperature. These are two essential parameters used in most battery charging algorithms. A temperature sensor in the battery pack provides one of the inputs, and reading the battery terminal voltages provide the other. The rest of the analog input pins can optionally be used as general purpose digital inputs. Intelligent charge control algorithm can be embedded in the COP8ACC. Based on the current battery voltage and temperature, the COP8ACC controls the current source to feed the required amount of current into the battery pack. Both Ni based chemistries exhibit a drop in voltage and a sudden rise in temperature as the battery begins to over charge. The temperature effect is more pronounced in NiMH batteries. This slope of the voltage drop and/or the slope of the temperature rise can be monitored to determine the charge termination point. However, detection of such events signify that the battery is already in a state of overcharge, and some damage has been


done. More advanced algorithms exist to determine more accurate termination points. Such algorithms are beyond the scope of this paper.

Up to four D port pins provide high source/sink capability to drive LEDs, which are often used to display the state of the charge. Various techniques exist to determine the state of the charge. These could range from a very crude determination based upon the battery voltage, or a more sophisticated mechanism where the sum of current into and out of the battery is monitored to determine a more accurate state. Often a mixture of these two parameters are used to determine very accurately how much charge is left in the battery.

Even for a given battery chemistry, the batteries from different manufacturers show significantly different behavior. More advanced battery chargers store specific manufacturer or pack specific information to enable better charging. Manufacturer specific chemistry related information can be obtained by testing/characterizing many batteries from the same manufacturer. These parameters can be stored in an

external EEPROM as shown in the block diagram. The Microwire feature on the COP8ACC requires minimal software overhead to communicate with the EEPROM. Optionally, a reference for the A/D converter can be stored here for more


accurate conversion. On the other hand, some battery packs contain intelligence in them to monitor its status. Battery abuse, battery age, and other parameters can be monitored by the battery itself.

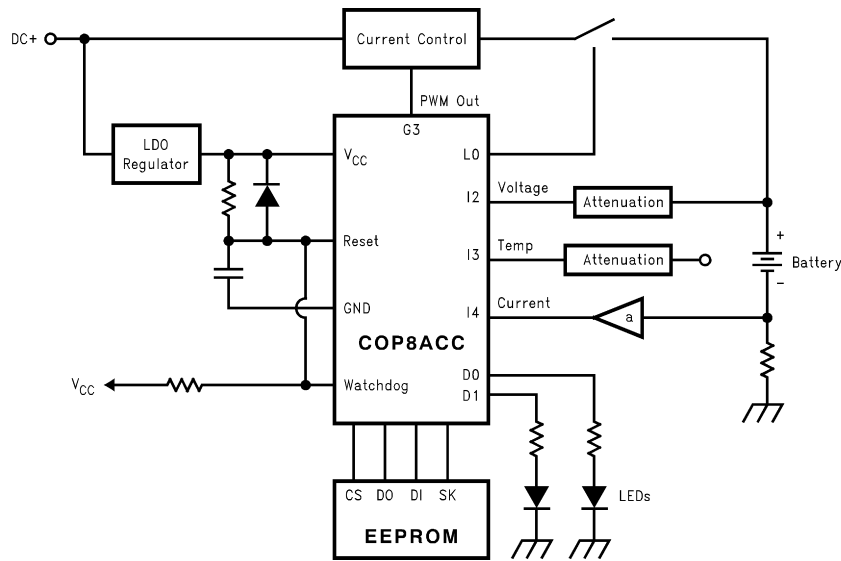

**FIGURE 2. Block Diagram of a Battery Charger Application**

AN100027-2

Figure 3 shows the flow chart of the embedded software for a battery charging application.

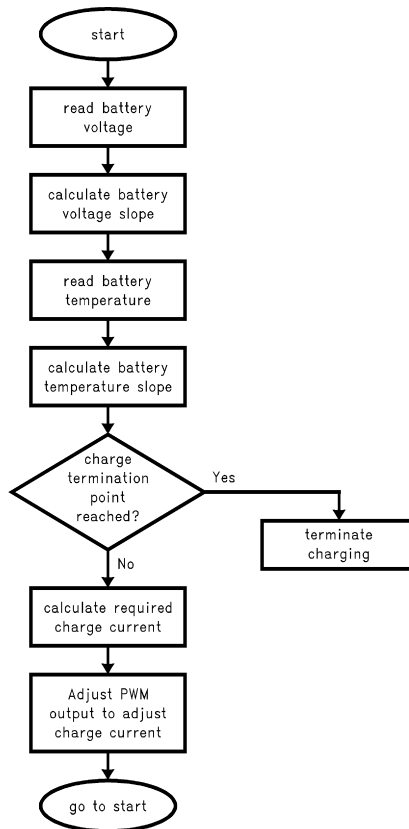


AN100027-3

**FIGURE 3. Flow Chart of The Software for A Battery Charger Application**
 
#### CONCLUSION

The features of the COP8ACC were tailored for intelligent battery charging applications. The A/D converter provides a highly efficient, high resolution, cost effective A/D conversion required for such applications. Many algorithms exist for charging the various chemistries available. These algorithms

offer various tradeoffs to the application engineer. However, a growing demand for long battery life and faster charge times have spawned new research for more intelligent algorithms. These algorithms are often more complex and require sufficient programming space. The 4k ROM space can be used to embed various intelligent algorithms.



**LIFE SUPPORT POLICY**

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component in any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
Americas  
Tel: 1-800-272-9959  
Fax: 1-800-737-7018  
Email: support@nsc.com

[www.national.com](http://www.national.com)

**National Semiconductor Europe**  
Fax: +49 (0) 1 80-530 85 86  
Email: europe.support@nsc.com  
Deutsch Tel: +49 (0) 1 80-530 85 85  
English Tel: +49 (0) 1 80-532 78 32  
Français Tel: +49 (0) 1 80-532 93 58  
Italiano Tel: +49 (0) 1 80-534 16 80

**National Semiconductor Hong Kong Ltd.**  
13th Floor, Straight Block,  
Ocean Centre, 5 Canton Rd.  
Tsimshatsui, Kowloon  
Hong Kong  
Tel: (852) 2737-1600  
Fax: (852) 2736-9960

**National Semiconductor Japan Ltd.**  
Tel: 81-3-5620-6175  
Fax: 81-3-5620-6179

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated