

AN-1853 COT Drivers Control LED Ripple Current

ABSTRACT

The constant on-time (COT) control method used by the LM3402 and LM3404 constant-current buck regulators provides a balance between control over switching frequency and fast transient response. Normally this "quasi-hysteretic" control senses the input voltage and adjusts the on-time t_{ON} of the power MOSFET as needed to keep f_{SW} constant. Investigating a little more deeply reveals that t_{ON} is in fact proportional to the current flowing into the R_{ON} pin. The addition of a single, general purpose PNP transistor forces t_{ON} to be proportional to $(V_{IN} - V_O)$ and provides two benefits that are particularly useful to LED drivers: improved tolerance of the average LED current, I_F , and constant LED ripple current, ΔI_F .

Contents

1	Benefits of Constant Ripple	2
2	Circuit Performance	2
3	Making a "Universal" Current Source	2
4	Design Procedure	3
5	Switching Frequency Changes	3
6	Conclusion	4

List of Figures

1	Constant Ripple LED Driver Using the LM3404 Buck Regulator	2
2	Ripple Current vs. Output Voltage	3
3	Switching Frequency vs. Output Voltage	3

List of Tables

1	Bill of Materials	4
---	-------------------------	---

1 Benefits of Constant Ripple

The luminous flux and dominant wavelength (or color temperature for white LEDs) of LED light are controlled by average current. The constant-ripple LED driver in [Figure 1](#) is much better at controlling average LED current over changes in both input voltage and changes in output voltage because it fixes the valley of the inductor current and also fixes the current ripple.

Controlling LED ripple current implies control over peak LED current, which in turn affects the luminous flux of an LED. All LEDs have a relationship between their luminous flux and forward current, I_F , that is linear up to a point. Beyond that point, increasing I_F causes more heat than light. High ripple current forces the LED to spend half of the time at a high peak current, putting it in the lower lm/W region of the flux curve. This reduces the light output when compared to a purely DC drive current even though the average forward current remains the same.

Close inspection of LED datasheets also reveals that the absolute maximum ratings for peak current are close to or often equal to the ratings for average current. High current density in the LED junction lowers lumen maintenance, providing yet another incentive for keeping the ripple current under control.

2 Circuit Performance

The circuit of [Figure 1](#) uses the PNP-based constant ripple concept to take an input voltage of 24VDC $\pm 10\%$ and drive 1A through as many LEDs in series as the maximum output voltage will allow. For a circuit with 'n' LEDs of forward voltage V_F in series, the output voltage is:

$$V_O = 0.2 + n \times V_F$$

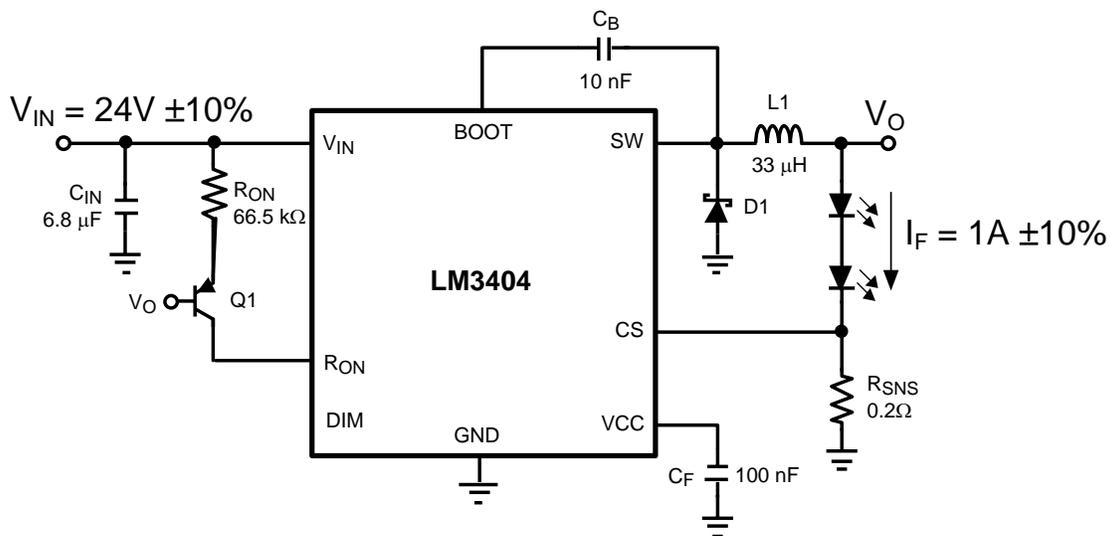


Figure 1. Constant Ripple LED Driver Using the LM3404 Buck Regulator

The maximum voltage that can be achieved is then:

$$V_{O-MAX} = V_{IN-MIN} \times (1 - f_{SW} \times 300 \text{ ns})$$

In the above equation, the 300 ns term reflects the minimum off-time of the LM3402 and LM3404 buck regulators.

3 Making a "Universal" Current Source

[Figure 2](#) and [Figure 3](#) show the dependence of ripple current and switching frequency against output voltage. This change in output voltage is effectively a change in the number of series-connected LEDs that the circuit drives.

One circuit with both average current and ripple current controlled independently of V_O can now power anything from a single infrared LED (V_{F-TYP} of $\sim 1.8V$) to as many as five white LEDs in series, yielding a V_O of $\sim 18V$. Such a circuit would be ideal for an LED-driving power-supply module. Many of the existing, commercial AC-input 'brick' modules for driving LEDs are specified to provide a constant current of 'x' mA at a voltage up to 'y' volts. Depending on the need for galvanic isolation and/or power factor correction, the LM3402 or LM3404 buck regulator could be paired with an existing AC-DC regulator to provide the 24V, resulting in a high-quality universal current source.

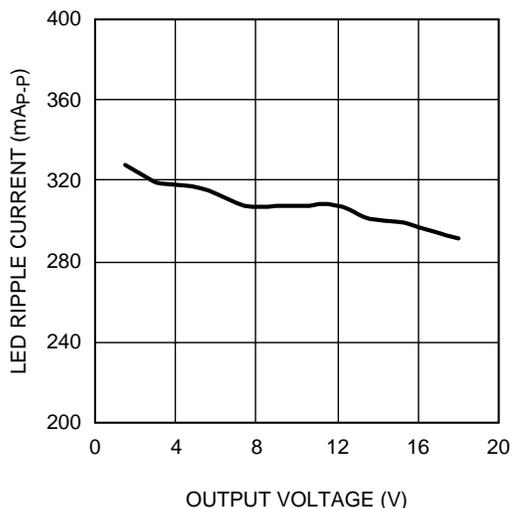


Figure 2. Ripple Current vs. Output Voltage

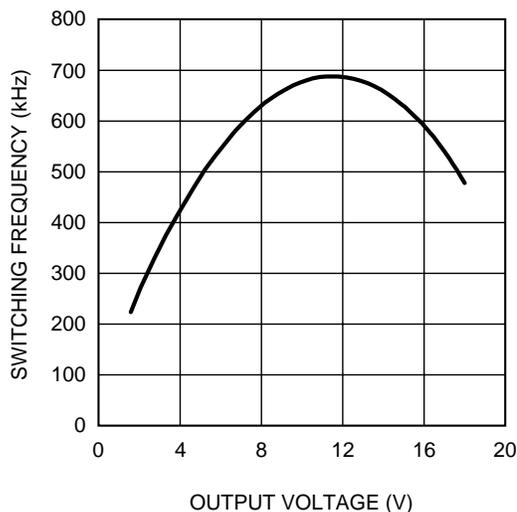


Figure 3. Switching Frequency vs. Output Voltage

4 Design Procedure

Designing for constant ripple in a COT converter requires a change in the selection of the on-time setting resistor R_{ON} :

1. Start with the typical input voltage, V_{IN-TYP} , and an output voltage that is at the center between the minimum and maximum expected value, V_{O-CTR} . Use the maximum permissible switching frequency, f_{SW-MAX} , and the desired peak-to-peak inductor ripple current, ΔI_L . The required inductance is

$$\text{then: } L = \frac{(V_{IN-TYP} - V_{O-CTR}) \times V_{O-CTR}}{V_{IN-TYP} \times f_{SW-MAX} \times \Delta I_L}$$

2. Select the closest standard inductor value to L and call it L_{STD} . R_{ON} can then be calculated with the

$$\text{following expression: } R_{ON} = \frac{\Delta I_L \times L_{STD}}{1.34 \times 10^{-10}}$$

3. Use the closest 1% resistor value for R_{ON} .
4. Design for the remaining components (input capacitor, Schottky diode, etc.) remains the same, and is outlined in the LM3402 and LM3404 data sheets.

5 Switching Frequency Changes

When using the LM3402 and LM3404 buck regulators in the constant-ripple configuration, the switching frequency will change with V_{IN} and V_O . Careful attention to PCB layout and proper filtering must be employed will all switching converters, and particular care is needed for systems where f_{SW} changes. The following steps can be used to predict the switching frequency:

1. Calculate the on-time at the minimum and maximum values of V_{IN} and V_O using the actual 1% resistor

$$\text{value of } R_{ON} \text{ and the following equation: } t_{ON} = \frac{0.134 \times R_{ON}}{V_{IN} - V_O + 0.6}$$

2. The switching frequency can then be determined using t_{ON} and the following expression: $f_{SW} = \frac{V_O}{V_{IN} \times t_{ON}}$

6 Conclusion

A pure DC LED drive current would be ideal for LEDs, but in practice the majority of LED lighting is powered from the AC mains and includes at least one switching regulator between the wall and the LEDs. Even battery or solar-powered systems are likely to employ a switching regulator in the interest of power efficiency. Therefore, some amount of ripple current will be present in almost every LED driver design. Allowing higher ripple current reduces the size and cost of the drive circuit, but comes at the expense of light output and reliability. Armed with the ability to control both LED ripple current and switching frequency, the LED lighting designer can make his/her own trade-offs between solution size, cost, and quality based on the needs of the application.

Table 1. Bill of Materials

ID	Part Number	Type	Size	Parameters	Qty	Vendor
U1	LM3404	LED Driver	SOIC-8	42V, 1.2A	1	NSC
Q1	CMPT3906	PNP	SOT23-6	40 V_{CE} , 10 mA	1	Central Semi
L1	VLF10040T-330M2R1	Inductor	10 x 10 x 4.0 mm	33 μ H, 2.1A, 80 Ω	1	TDK
D1	CMSH2-40M	Schottky Diode	SMA	40V, 2A	1	Central Semi
C_F	VJ0603Y104KXXAT	Capacitor	0603	100 nF, 10%	1	Vishay
C_B	VJ0603Y103KXXAT	Capacitor	0603	10 nF, 10%	1	Vishay
C_{IN}	C4532X7R1H685M	Capacitor	1812	6.8 μ F, 50V	1	TDK
R_{SNS}	ERJ8RQFR20V	Resistor	1206	0.2 Ω , 1%	1	Panasonic
R_{ON}	CRCW06035762F	Resistor	0603	57.6 k Ω , 1%	1	Vishay

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com