

Precision Output Current Limiting Using Average Current Monitor Feature

— By Eric Lee, Applications Engineer and Robert Bell, Design Center Director

Introduction

Traditionally, current limiting of a buck regulator is accomplished by monitoring the switch current. This method protects the switch effectively, but the maximum output current limit will vary widely. In some emerging applications such as battery/super-capacitor chargers, USB power supplies, or LED drivers, very tight control of the maximum output current is now mandatory. Achieving higher accuracy of current limit/regulation is a competitive advantage.

In this article, a unique average output current monitor feature of National Semiconductor's LM5117 synchronous buck controller will be introduced and a method to use this feature in order to implement precise current limiting will be shown. An example of a constant current regulator providing output over-voltage protection will also be presented.

Output Current Limit Variation When Using Peak Current Limit

Shown in *Figure 1* is a block diagram of a current mode -controlled buck regulator implementing traditional cycle-by-cycle peak current limiting. This popular current limiting scheme senses the current through the MOSFET during the on-time. The current can be sensed using the MOSFET's 'on' resistance, inductor resistance, a dedicated sense resistor, or a Sense FET.

The current limit comparator turns off the MOSFET if the sensed current (and the addition of slope compensation) exceeds the current limit threshold.

Once the MOSFET is turned off, the inductor current will decay during the balance of the clock period to a valley level. The MOSFET will be turned on again at the start of the next clock period and if the overload condition still exists, the current will rise again to the peak limiting level.

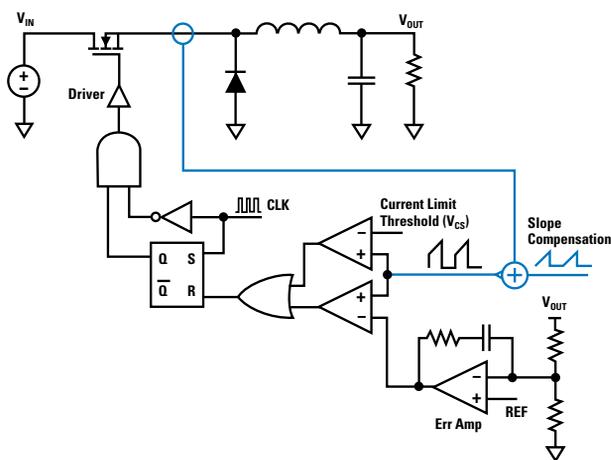


Figure 1. Traditional Cycle-by-Cycle Peak Current Limiting

In applications where the input voltage is relatively large in comparison to the output voltage, controlling narrow pulse widths and short duty cycles are necessary for regulation. However, traditional peak current-mode control needs a blanking time which blanks large leading edge spikes during turn-on of the high-

Precision Output Current Limiting Using Average Current Monitor Feature

side switch. Controlling narrow pulse widths will be limited by this blanking time. Emulated peak current-mode control is free of this limit and allows control of narrow pulse widths because the inductor current information is sensed—across the low-side switch or a low-side sense resistor—during off-time. *Figure 2* shows a simplified block diagram of a buck regulator implementing emulated peak current mode control with peak cycle-by-cycle current limiting.



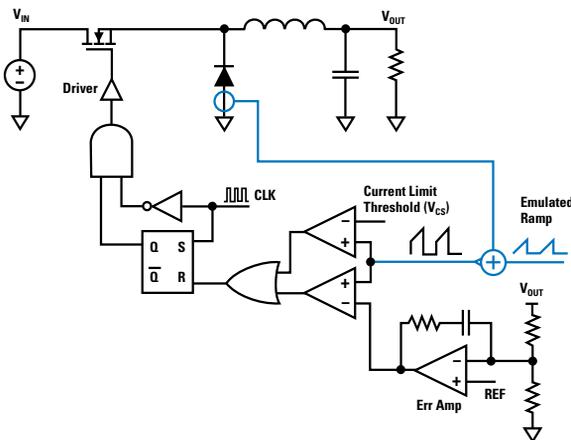


Figure 2. Emulated Peak Current Limit

The LM5117 emulated current-mode controller does not actually measure the MOSFET switch current but rather reconstructs the signal as shown in *Figure 3(b)*. The MOSFET switch current waveform can be broken down into two parts, a base or pedestal and a ramp. The pedestal represents the minimum inductor current value (or valley) over the switching cycle. The inductor current is at its minimum the instant the free-wheel diode turns off, as the buck switch turns on. The buck switch and the diode have the same minimum current value, occurring at the valley of the inductor current. A sample and hold measurement of the free-wheel diode current, sampled just prior to the turn-on of the buck switch, can be used to capture the pedestal level information. A ramp signal which emulates the positive slope of the inductor current is added to the sample-and-hold DC level.

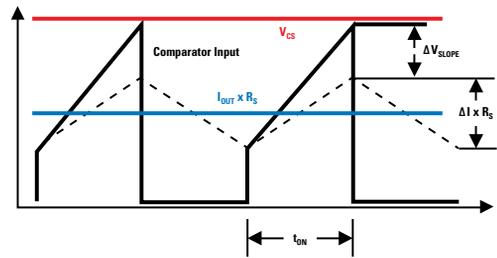

(a) Traditional Peak Current Limit

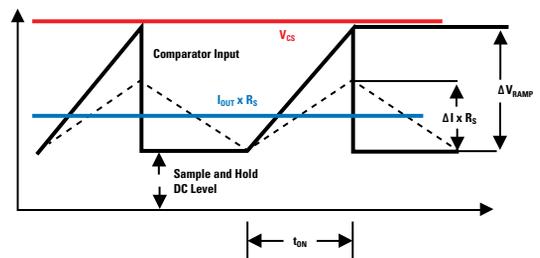

(b) Emulated Peak Current Limit

Figure 3. Current Limit Comparator Input

While both traditional and emulated current mode control protect the MOSFET switch effectively, the maximum output current will vary widely when operating with varying input and output voltages. The relationship between input/output voltage and the maximum output current can be calculated as follows:

$$I_{OUT(MAX)} = \frac{V_{CS}}{R_S} - \frac{\Delta I}{2} - \frac{\Delta V_{SLOPE}}{R_S}$$

Traditional Peak Current Limit

$$I_{OUT(MAX)} = \frac{V_{CS}}{R_S} + \frac{\Delta I}{2} - \frac{\Delta V_{RAMP}}{R_S}$$

Emulated Peak Current Limit

Where V_{CS} is the current limit threshold, R_S is the resistance of the sensing resistor, ΔV_{RAMP} is the amount of emulated ramp, ΔV_{SLOPE} is the amount of slope compensation, and ΔI is a peak-to-peak inductor current ripple, defined as:

$$\Delta I = \frac{V_{OUT}}{V_{IN} \times F_{SW}} \times \frac{(V_{IN} - V_{OUT})}{L_{OUT}}$$

The relationship between the maximum output current and the input voltage in emulated peak current limit is illustrated in *Figure 4*, with output voltage of 5V.

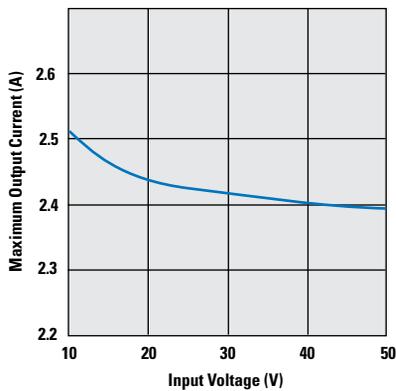


Figure 4. Maximum Output Current vs Input Voltage

The relationship between the maximum output current and the output voltage using emulated peak current limit is shown in *Figure 5*, with input voltage of 48V.

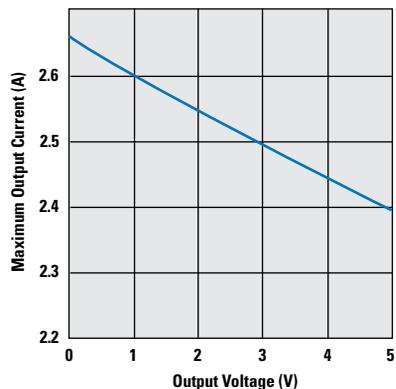


Figure 5. Maximum Output Current vs Output Voltage

Average Output Current Monitor Feature

In steady-state, the output current of the buck regulator is equal to the average of inductor current. A unique feature of the LM5117 is an analog telemetry feature that averages the inductor current and provides a voltage proportional to the output (inductor) current. The current monitor signal is updated every clock cycle.

Figure 6 illustrates the LM5117 current monitor. A current amplifier samples the voltage across the sense resistor with a gain of 10 to form the pedestal for the emulated ramp. The conditioner averages the amplified current sense signal. Finally, a buffer amplifier with a gain of 2 is used to buffer and minimize loading effects.

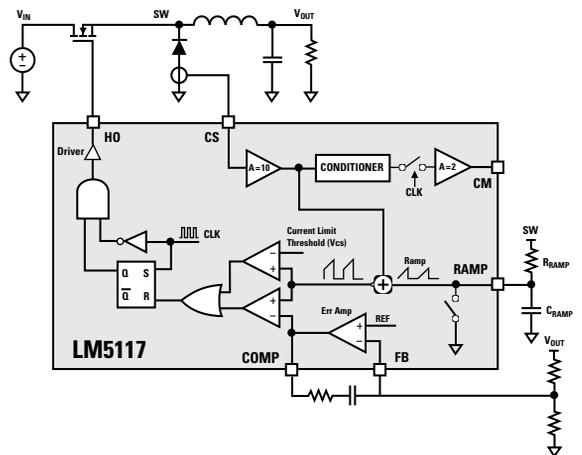


Figure 6. Block Diagram of Current Monitor and Ramp Generator

The output of the buffer amplifier is updated every clock cycle as shown in *Figure 7*. The current monitor can be used as an input to an A to D converter to digitally monitor the output current or calculate power in order to check system performance. The current monitor can also be used as an accurate current feedback for precise output current limiting.

Precision Output Current Limiting Using Average Current Monitor Feature

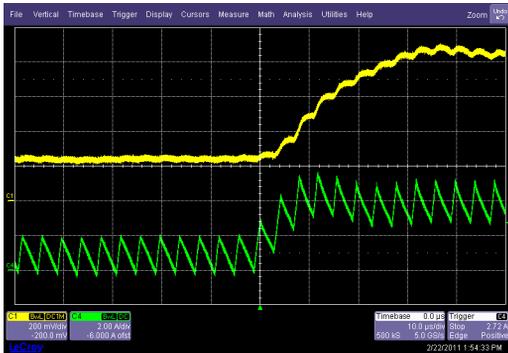


Figure 7. Current Monitor Output—Upper: CM output, measured through 5 kΩ and 1 nF RC filter; Lower: Inductor Current

Constant Voltage Regulator with Precision Current Limit

In applications such as battery/super-capacitor chargers, both accurate voltage and current regulation are required. The LM5117 can be configured as a constant voltage with precision current limit as shown in *Figure 8*. In this configuration, there is much less variation in the output current limiting when compared to the traditional cycle-by-cycle peak current limiting. The LMV431 shunt regulator and the PNP transistor configure a voltage-to-current amplifier in a closed current loop. This amplifier circuitry does not affect the normal operation when the output current is less than the set-point. When the output current rises to the set-point, the PNP transistor starts to source current into C_{RAMP} . The PNP current increases the positive slope of emulated ramp, providing a feedback path into the controller to limit the maximum output current.

As a result, the output can be connected directly to a battery and be charged as a constant current source when the battery voltage is less than the output voltage set-point. Once the battery potential reaches the output voltage set-point, the controller will smoothly transition to voltage regulation mode, as shown in *Figure 9*. The V_{OUT} vs. I_{OUT} curves shown in *Figure 10* illustrate the accuracy of the current limit circuit shown in *Figure 8*.

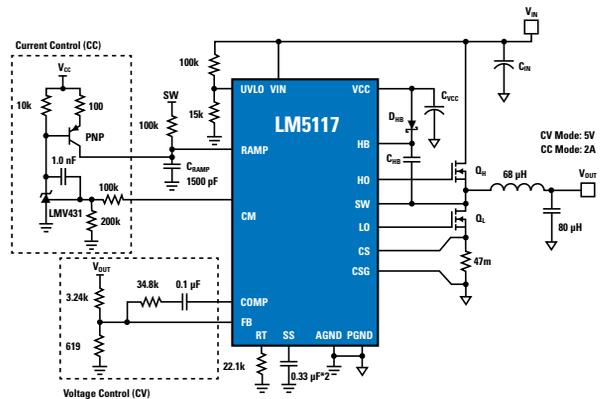


Figure 8. Constant Voltage Regulator with Precision Current Limit

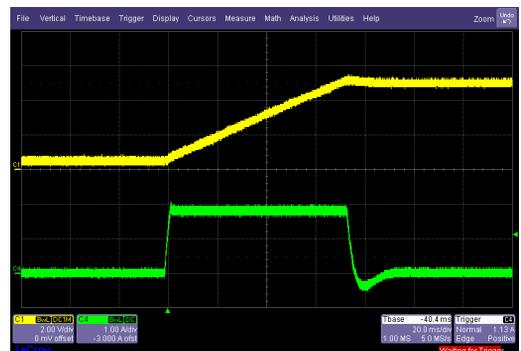


Figure 9. CC and CV Regulation Waveforms (Upper : Output Voltage, Lower: Output Current)

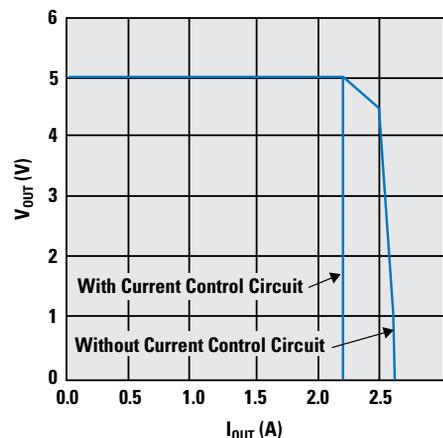


Figure 10. Output Voltage vs Output Current

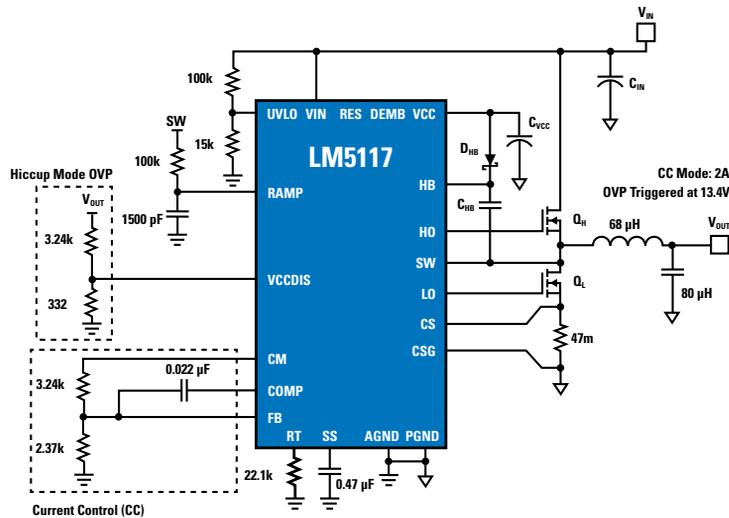


Figure 11. Constant Current Regulator with Hiccup-Mode Over-Voltage Protection

Constant Current Regulator with Hiccup-Mode Over-Voltage Protection

In applications such as LED drivers, a constant current output is required, while output over-voltage protection is required as a protection function. The LM5117 can also be configured as a constant current regulator by using the current monitor feature (CM) as the feedback (FB) input as shown in *Figure 11*. A voltage divider at the VCCDIS pin from V_{OUT} to AGND can be used to protect against output over-voltage, if required. When the VCCDIS pin voltage is greater than the VCCDIS threshold, the controller disables the VCC regulator and the VCC pin voltage decays. When the VCC pin voltage is less than the VCC UVLO threshold, both HO and LO outputs stop switching. Due to the time delay required for VCC to decay below the VCC UVLO threshold, the over-voltage protection operates in hiccup-mode.

Conclusion

While traditional cycle-by-cycle peak current limiting protects the MOSFET effectively, maximum output current varies widely with changes in input and output voltage. In applications requiring tight regulation of output current, using the LM5117 current monitor feature as feedback allows easy configuration of a constant current regulator or precision current limiting. The current monitor feature can also enable various value-added features by providing the average output current monitoring information to the system.

Additional Resources

LM5117 Datasheet
LM5117 Evaluation Board

Power Design Tools



Design, build, and test analog circuits in this online design and prototyping environment.
national.com/webench



Expand your knowledge and understanding of analog with our free online educational training tool.
national.com/training



National's monthly analog design technical journal.
national.com/edge

Tools for Energy-Efficient Designs

Access white papers, reference designs, and application notes on PowerWise® products and systems.

national.com/powerwise

National Semiconductor
2900 Semiconductor Drive
Santa Clara, CA 95051
1 800 272 9959

Mailing address:
PO Box 58090
Santa Clara, CA 95052

Visit our website at:
national.com

**For more information,
send email to:**
new.feedback@nsc.com

Don't miss a single issue!

Subscribe now to receive email alerts when new issues of Power Designer are available:

national.com/powerdesigner

Read our Signal Path Designer® online today:

national.com/spdesigner



IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2012, Texas Instruments Incorporated