

# Powering drones with a wide $V_{IN}$ DC/DC converter

Timothy Hegarty



Drone applications require high cell count battery packs to support longer flying distances and flight times. As an example, consider a 14-series (14s) Li-ion battery pack architecture where the working voltage is 50 V to 60 V. When designing a DC/DC power supply for such a system, one of the challenges is how to select the maximum input voltage rating. A large voltage excursion can occur at the node designated  $V_M$  in Figure 1.

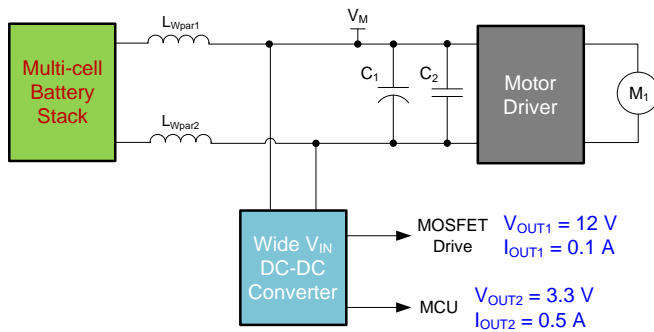


Figure 1. Drone system block diagram

To understand the modes of operation of a motor driver, consider the schematic diagram of Figure 2. The battery stack powers a brushed-DC (BDC) motor,  $M_1$ , through the forward current path designated as loop 1, and electric power converts to the rotational kinetic energy of the motor during this period.

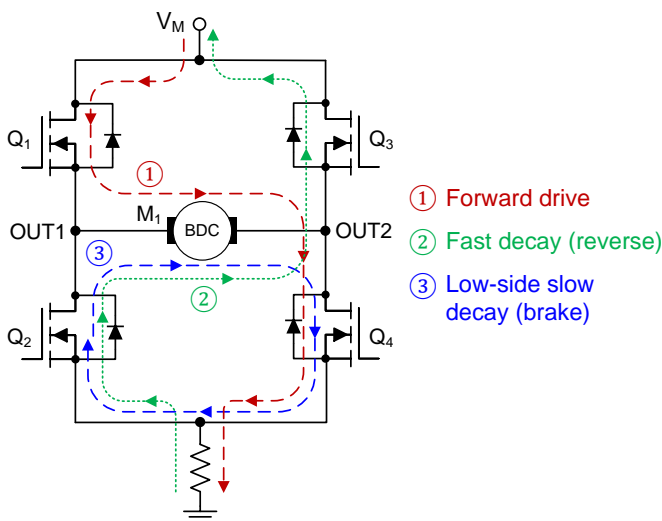


Figure 2. BDC motor H-bridge driver forward current paths

Conversely, when the motor decelerates or changes its direction of rotation, it acts as a generator and the resultant back EMF returns energy to the input through the driver using current loop 2. Although this regenerative behavior may be considered advantageous in terms of improving overall system efficiency, it can result in a large reverse current and consequent voltage overshoot at the supply input.

To manage this voltage excursion and ensure the system runs safely, system designers can use an electrolytic bulk capacitor for  $C_1$  to absorb the energy or, alternatively, to add a TVS diode to clamp the voltage to a safe range. Consider the Rubycon 2200- $\mu$ F, 63-V electrolytic capacitor for example. With a diameter and height of 18 mm and 33 mm, respectively, the capacitor is too large for most drone implementations where footprint and profile are important constraints. More important is that the E-cap, with its finite, rated lifetime, represents an acknowledged limitation in terms of system reliability and robustness. A TVS diode also entails space, cost, and reliability concerns for the whole system and can be difficult to select because its clamping voltage varies with current.

## Choosing a Power Solution

Another option is to use a DC/DC power converter IC solution. The choice hinges initially on input voltage and output current specifications. However, solutions specifically with a wide input voltage range (wide  $V_{IN}$ ) and high line transient immunity offer outsized voltage rating and operating margin to accommodate the peak voltage transient during the regenerative action of the drone motor.

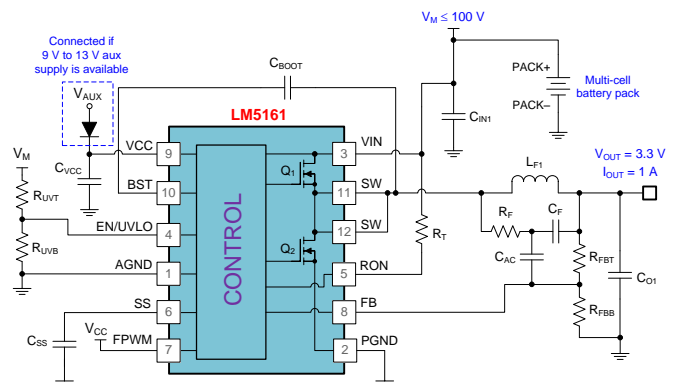



Figure 3. LM5161 synchronous buck converter

Selecting a converter with a wide  $V_{IN}$  range, such as the **LM5161**, a 100-V, 1-A synchronous buck converter, shown in **Figure 3**, lets designers eliminate the bulk capacitor or TVS protection, saving time, cost, and board space. If an auxiliary rail between 9 V and 13 V is available to supply VCC bias power as indicated in **Figure 3**, the quiescent current of the LM5161 input reduces to 325  $\mu$ A at 50-V input, to uphold battery life during standby operating conditions.

Moreover, the LM5161 converter offers a large degree of flexibility in terms of platform design. Not only does the converter support a nonisolated output, but it can also deliver one or more isolated outputs using a Fly-Buck™ circuit design (see **Figure 4**) if needed in the drone system, to break a ground loop or to decouple different voltage domains.

### Fly-Buck Topology

In general, a **Fly-Buck** converter represents an easy way to provide galvanically-isolated positive or negative voltage rails while keeping cost and complexity to a minimum. And, at the same time, the converter meets a diversity of challenges tied to the wide input voltage range, multiple outputs, small solution size, reliability, and electromagnetic interference (EMI).

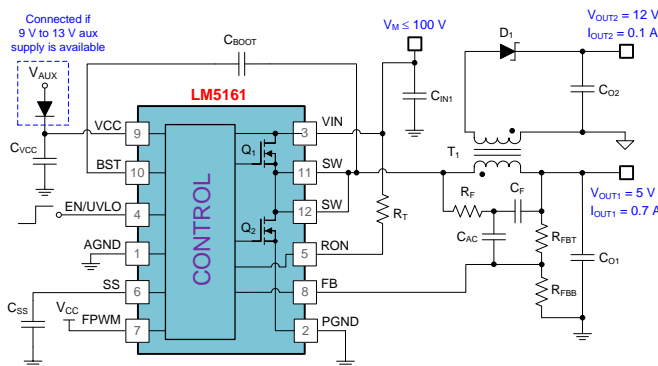

**Figure 4. LM5161 Fly-Buck converter**


Built from the synchronous buck regulator which has specific features to facilitate Fly-Buck functionality (including a current limit hiccup off-timer, negative primary-side current limit, and forced-PWM operation), the Fly-Buck stage has neither loop compensation nor feedback opto-coupler components. A compensated error amplifier is not needed, and a constant on-time (COT) control approach gives nearly-instantaneous response for excellent line and load transient dynamics. Feedback regulation is from the primary side through a standard resistor divider.

The Fly-Buck is ideal for auxiliary and bias rails, floating supplies for digital isolators, and **bipolar supplies** for powering high-precision op-amps and data converters in the drone system.

To customize for additional outputs, add a transformer secondary winding with the requisite number of turns, a rectifier diode, and an output capacitor.

### Fly-Buck-Boost Topology

Related to the Fly-Buck, the **Fly-Buck-Boost** is another useful circuit for drone applications, especially if low input voltage operation or a negative-polarity output is required. **Figure 5** shows the **LM5017**, a 100-V, 0.6-A synchronous buck converter configured to provide nonisolated  $\pm$ 12-V rails.

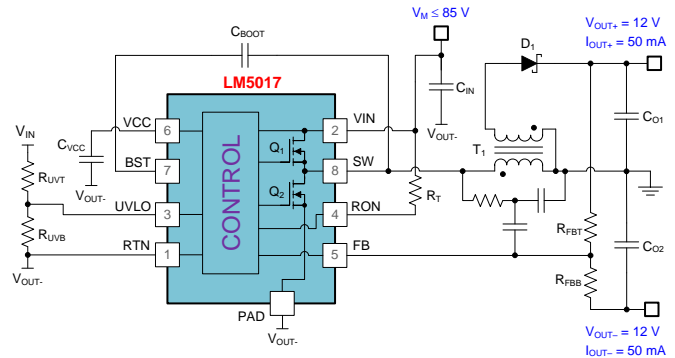

**Figure 5. LM5017 Fly-Buck-Boost converter**

In **Figure 5**, the GND of the LM5017 device is referenced to  $V_{OUT-}$ , and the feedback loop regulates the total of  $V_{OUT+}$  and  $V_{OUT-}$ , for balanced and symmetric startup and transient response behavior. Using an off-the-shelf unity turns ratio coupled inductor yields good load regulation performance and a low overall bill of materials cost. Moreover, the absence of a switch (SW) node voltage spike related to leakage inductance reduces **EMI filtering** requirements.

**Table 1. Alternate converter recommendations**

Device	$V_{IN}$ Range, Rated $I_{OUT}$	Performance Feature	Package
LM5164	6 V to 100 V, 1 A	Wide $V_{IN}$ , low $I_Q$	SO-8
LM5018	7.5 V to 100 V, 0.3 A	Buck and Fly-Buck capable	WSO-8, SO-8
LM5019	7.5 V to 100 V, 0.1 A	Buck and Fly-Buck capable	WSO-8, SO-8
LM5160A	4.5 V to 65 V, 2 A	Buck and Fly-Buck capable	WSO-12
LM5180	4.5 V to 65 V, 1.5 A ( $I_{SW-MAX}$ )	PSR flyback	WSO-8
LM5166	3.5 V to 65 V, 0.5 A	Low EMI, low $I_Q$	VSON-10
LM5165	3.5 V to 65 V, 0.15 A	Low EMI, low $I_Q$	VSON-10, VSSOP-10

**Table 2. Related TI application notes**

SNVA802	Improving RF power amplifier efficiency in 5G radio systems using an adjustable DC/DC buck regulator
SNVA803	Improving EMI for free with PCB layout

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2019, Texas Instruments Incorporated