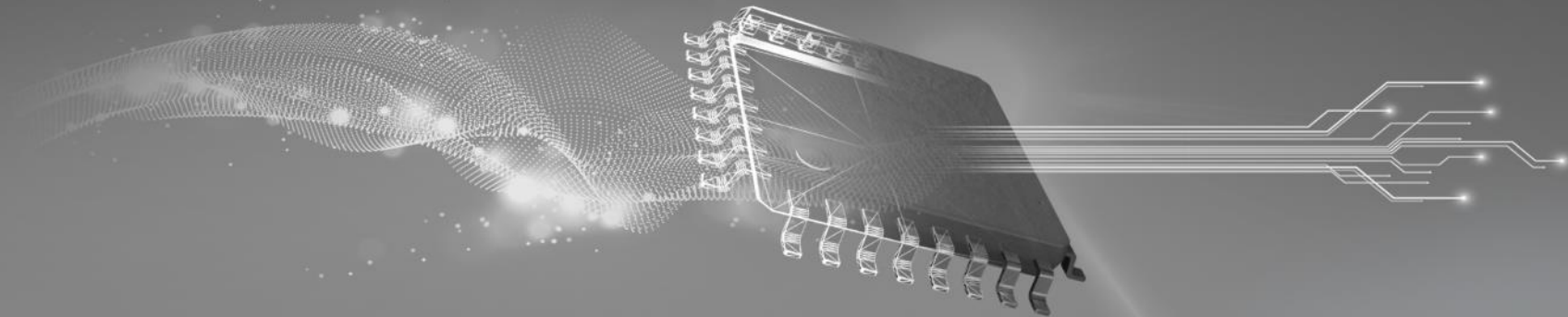


TI TECH DAYS



Increasing system robustness with integrated protection and diagnostics by using TI high-side switches


Shreyas Dmello

APP-PSIL-PS

Agenda


- What is a High-side switch?
- Where do I use a smart High-side switch?
- Applications of a smart High-side switch
 - Capacitive/Inductive load driving
 - Short circuit/Overload protection
 - Diagnostics/Current sensing

Power switches | Use cases

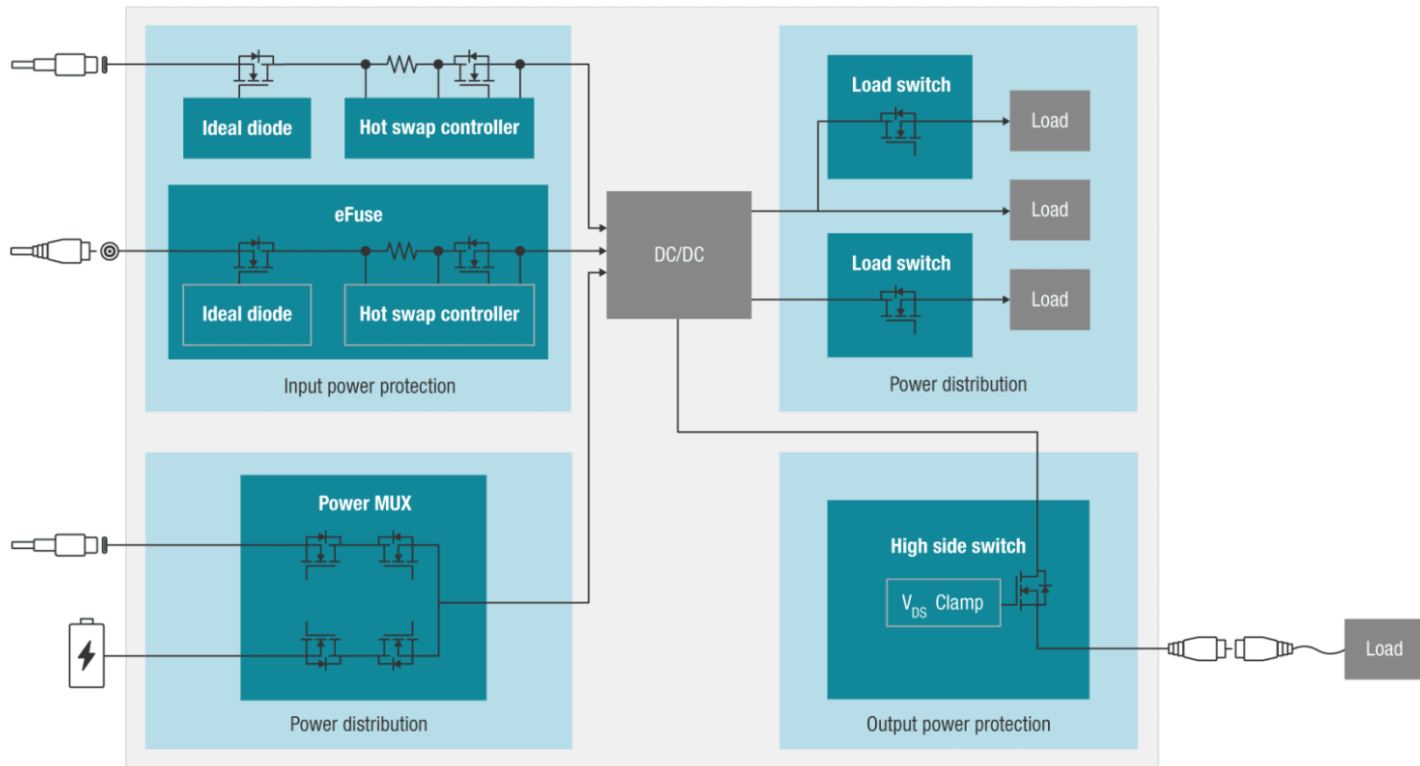

Learn more at: [Products](#) → [Power Management](#) → [Power Switches](#) → [Power Switches portal Page](#)

Power switches | High-side switches

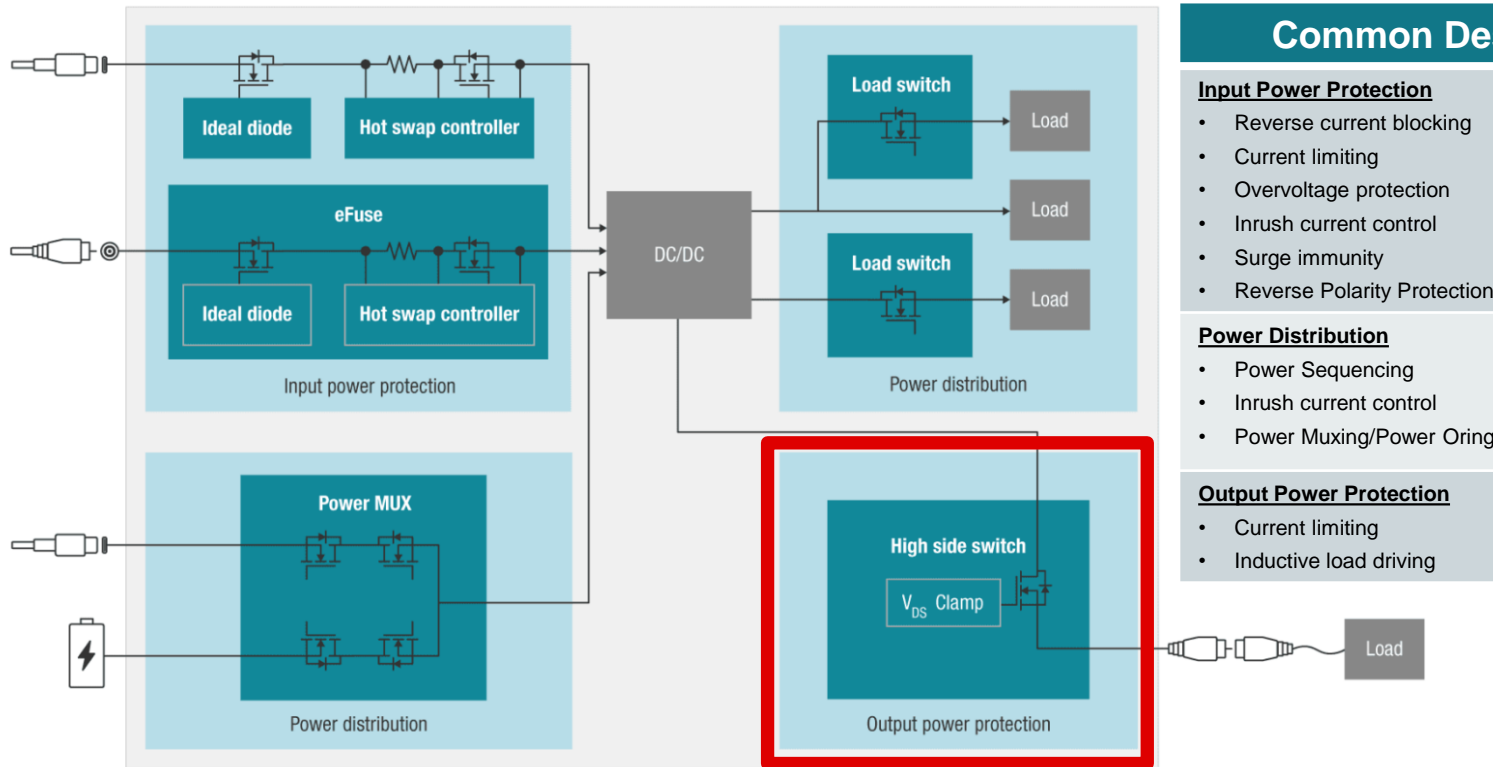

Common Design Challenges

Input Power Protection

- Reverse current blocking
- Current limiting
- Overvoltage protection
- Inrush current control
- Surge immunity
- Reverse Polarity Protection

Power Distribution

- Power Sequencing
- Inrush current control
- Power Muxing/Power Oring

Output Power Protection

- Current limiting
- Inductive load driving


Learn more at: [Products](#) → [Power Management](#) → [Power Switches](#) → [Power Switches portal Page](#)

Agenda

- **What is a High-side switch?**
- Where do I use a smart High-side switch?
- Applications of a smart High-side switch
 - Capacitive/Inductive load driving
 - Short circuit/Overload protection
 - Diagnostics/Current sensing

What is a High-side switch?

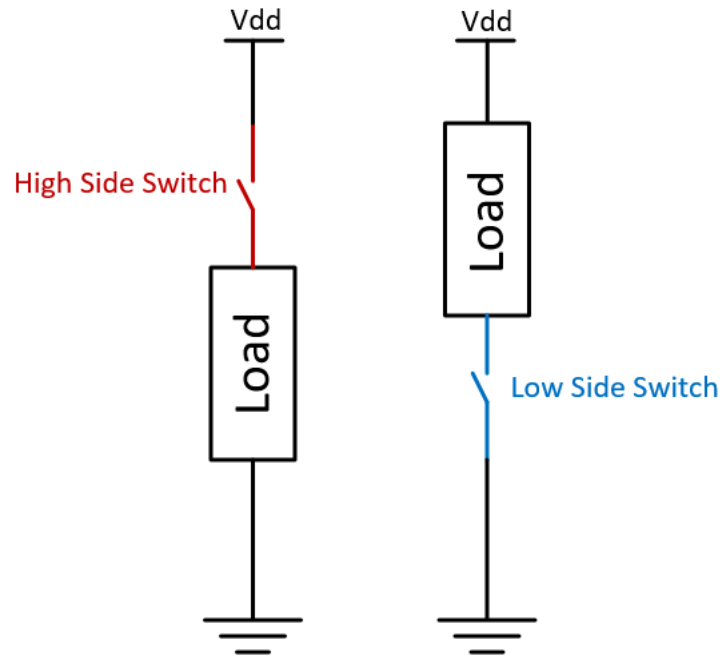
High-side switches placed between source and load. Using these devices allow for no floating nodes when the system is off. The load is safely pulled to GND.



What is a High-side switch?

High-side switches placed between source and load. Using these devices allow for no floating nodes when the system is off. The load is safely pulled to GND.

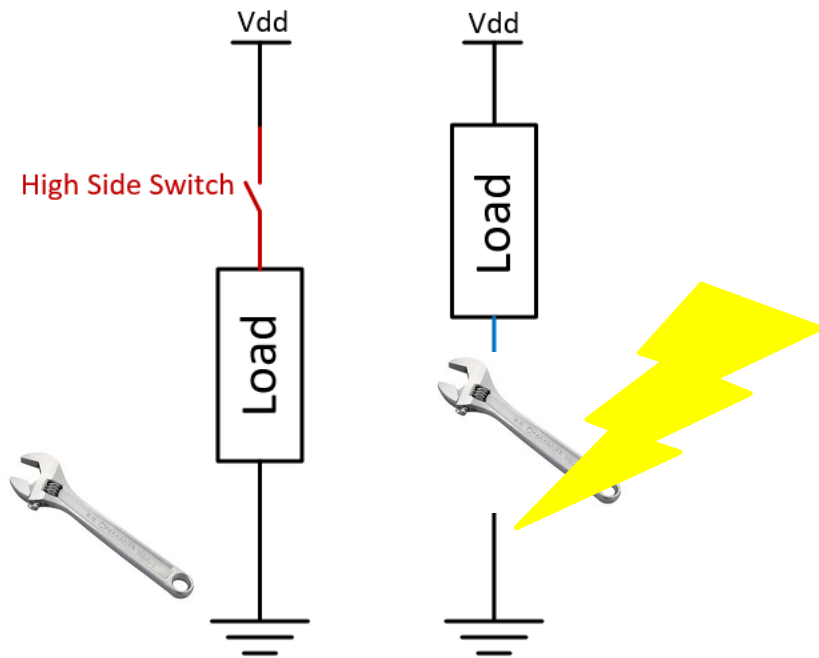
In the event of a failure, High-side switches are preferred as they disconnect the power source from the system rather than the system GND.



What is a smart High-side switch?

- A **smart High-side switch** is a power management device that connects to a power supply input and **switches** on/off downstream loads, **protects** against faults, and provides output **diagnostics**

Module Type	Device	Description
≤ 100mA	TPS4H000	4-CH, 40V, 1Ω, TSSOP
≤ 500mA	TPS1H200	1-CH, 40V, 200mΩ, TSSOP
≤ 750mA	TPS4H160	4-CH, 40V, 160mΩ, TSSOP
	TPS27S100	1-CH, 40V, 100mΩ, TSSOP
≤ 2A	TPS27S100	1-CH, 40V, 100mΩ, TSSOP

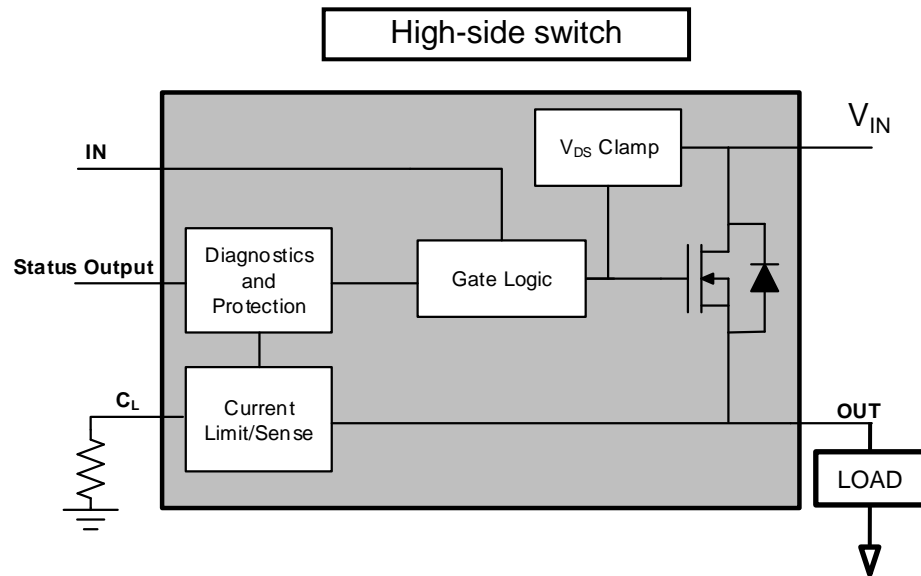


Learn More: [11 Ways to Protect Your Power Path](#)

Agenda

- What is a High-side switch?
- **Where do I use a smart High-side switch?**
- Applications of a smart High-side switch
 - Capacitive/Inductive load driving
 - Short circuit/Overload protection
 - Diagnostics/Current sensing


Where do we use a smart High-side switch?

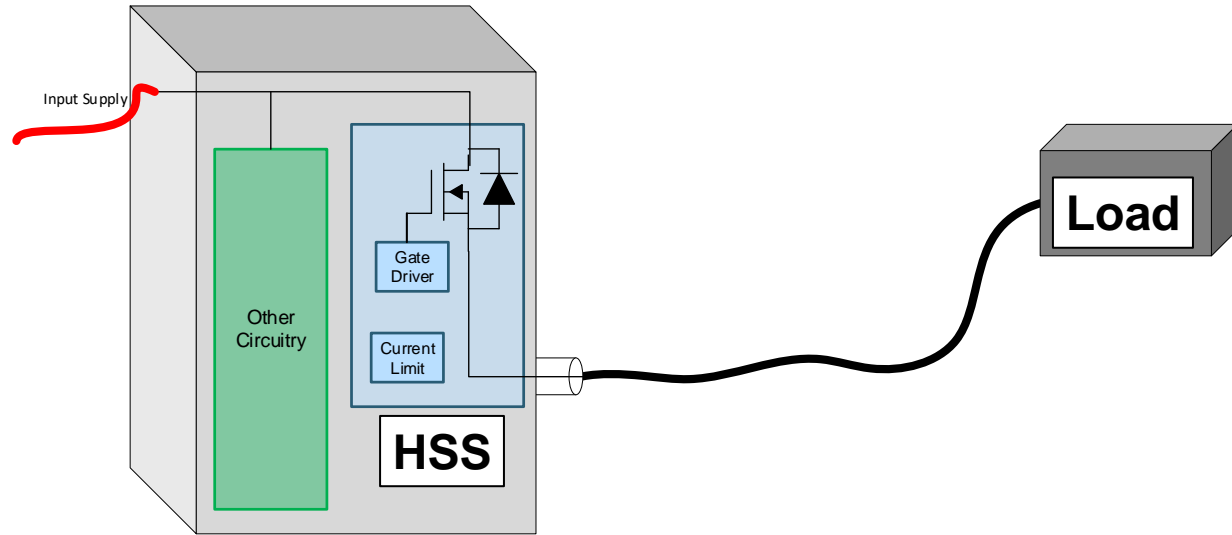- Smart High-side switches are ON/OFF switches that sit on the high-side of the load




Where do we use a smart High-side switch?

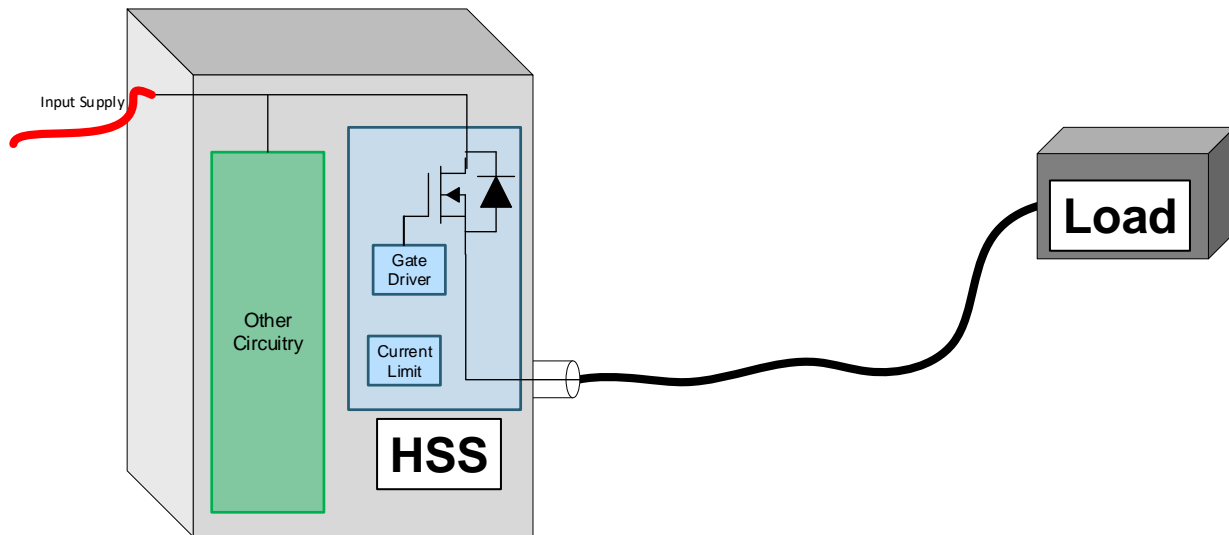- Smart High-side switches are ON/OFF switches that sit on the high-side of the load
- Smart High-side switches are used anywhere where **output** power protection is required



Where do we use a smart High-side switch?

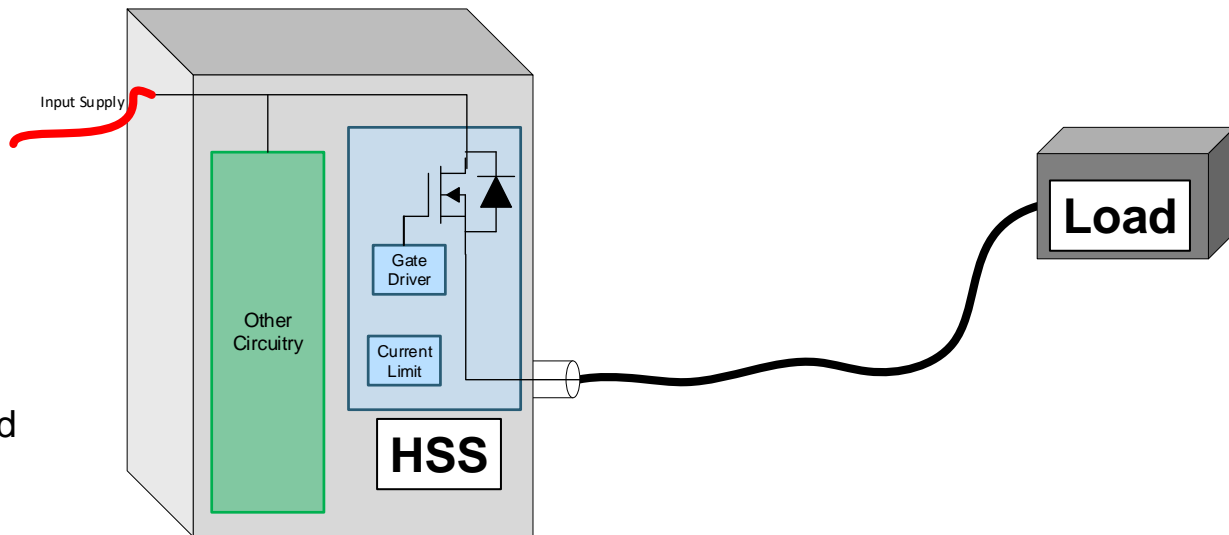- Smart High-side switches are ON/OFF switches that sit on the high-side of the load
- Smart High-side switches are used anywhere where **output** power protection is required
- Any system powering an off-board load runs the risk of a load failure that the primary board cannot control
 - Short-Circuit
 - Load Current Overload
 - Inductive Kickback



High-side switches: Inside a wide range of industrial systems



Factory Automation and Control

Digital outputs provide power to sensors, motors, and valves throughout the factory floor



Motor Drives

Brakes, sensors, and general purpose I/O's communicate between the motor drive and the motor



Building Automation


Centralized building control systems distribute power to subsystems like fire, alarm, and HVAC systems.

Distributed Power Outputs

Agenda

- What is a High-side switch?
- Where do I use a smart High-side switch?
- **Applications of a smart High-side switch**
 - **Capacitive/Inductive load driving**
 - **Short circuit/Overload protection**
 - **Diagnostics/Current sensing**

Smart High-side switch | Applications

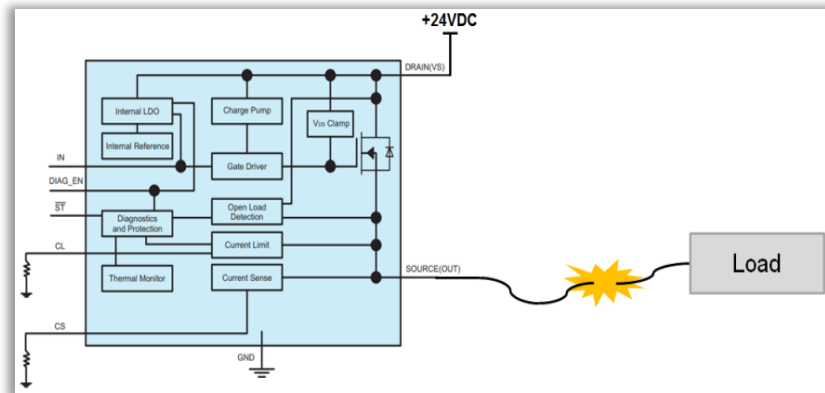


Safe inductive and capacitive load driving through integrated clamp and adjustable current limiting

Short Circuit and current limiting protection improves system reliability and reduces system costs

Integrated **current sense** and **open-load detection** enables the detection and diagnosis of faults

High-side switch | Inductive load

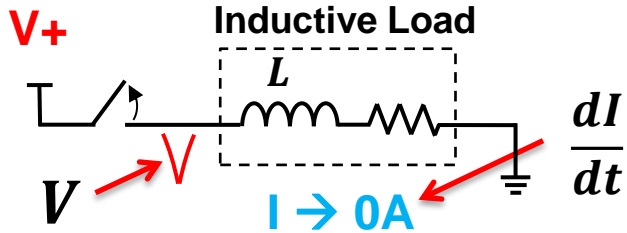
Safe inductive and capacitive load driving through integrated clamp and adjustable current limiting



- As the current flows through the inductor, energy is stored in it according to $E=1/2LI^2$
- When the High-side switch opens, the current through the inductive load jumps from I to $0A$
- An inductor wants to resist the change in current so a large negative voltage transient appears at the output of the switch according to the below equation

High-side switch | Inductive load

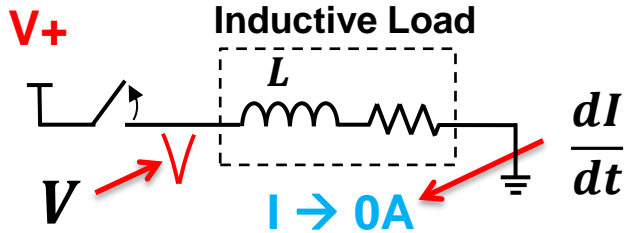Safe inductive and capacitive load driving through integrated clamp and adjustable current limiting




- As the current flows through the inductor, energy is stored in it according to $E=1/2LI^2$
- When the High-side switch opens, the current through the inductive load jumps from I to $0A$
- An inductor wants to resist the change in current so a large negative voltage transient appears at the output of the switch according to the below equation

$$V = -L \times \frac{dI}{dt}$$


High-side switch | Inductive load

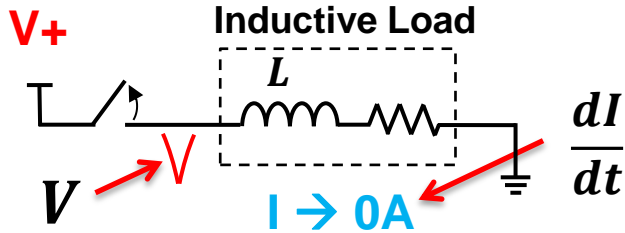Safe inductive and capacitive load driving through integrated clamp and adjustable current limiting



- As the current flows through the inductor, energy is stored in it according to $E=1/2LI^2$
- When the High-side switch opens, the current through the inductive load jumps from I to $0A$
- An inductor wants to resist the change in current so a large negative voltage transient appears at the output of the switch according to the below equation

$$V = -L \times \frac{dI}{dt}$$

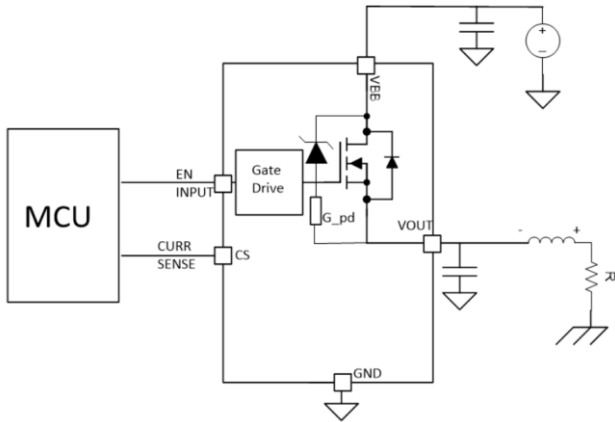


What is the High-side switch's role in driving inductive loads?

- TI's smart High-side switches have an integrated VDS clamp which clamps the negative voltage swing to a safe level to prevent damage to its output.
- Depending on the load, it also helps to dissipate the energy stored in the inductive element by turning on its MOSFET and dissipating the energy through it.


High-side switch | Inductive load

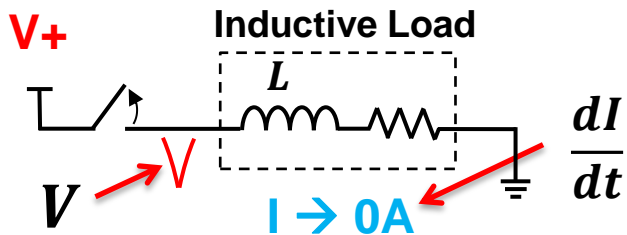Safe inductive and capacitive load driving through integrated clamp and adjustable current limiting



- As the current flows through the inductor, energy is stored in it according to $E=1/2LI^2$
- When the High-side switch opens, the current through the inductive load jumps from I to $0A$
- An inductor wants to resist the change in current so a large negative voltage transient appears at the output of the switch according to the below equation

$$V = -L \times \frac{dI}{dt}$$

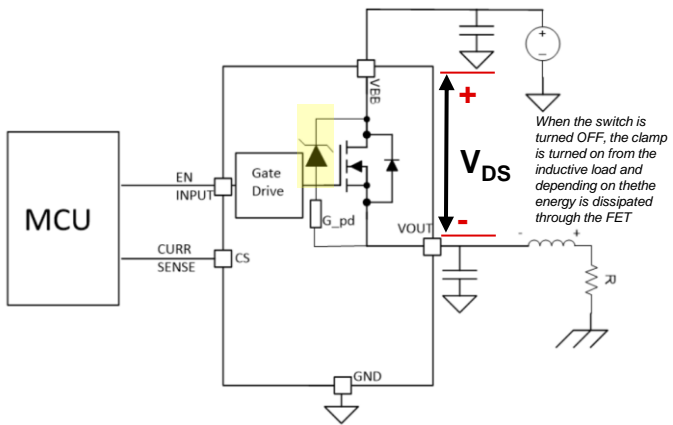


What is the High-side switch's role in driving inductive loads?

- TI's smart High-side switches have an integrated VDS clamp which clamps the negative voltage swing to a safe level to prevent damage to its output.
- Depending on the load, it also helps to dissipate the energy stored in the inductive element by turning on its MOSFET and dissipating the energy through it.


High-side switch | Inductive load

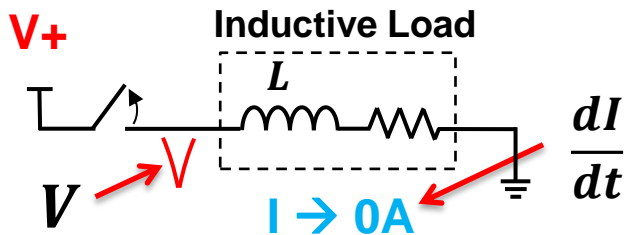Safe inductive and capacitive load driving through integrated clamp and adjustable current limiting



- As the current flows through the inductor, energy is stored in it according to $E=1/2LI^2$
- When the High-side switch opens, the current through the inductive load jumps from I to $0A$
- An inductor wants to resist the change in current so a large negative voltage transient appears at the output of the switch according to the below equation

$$V = -L \times \frac{dI}{dt}$$

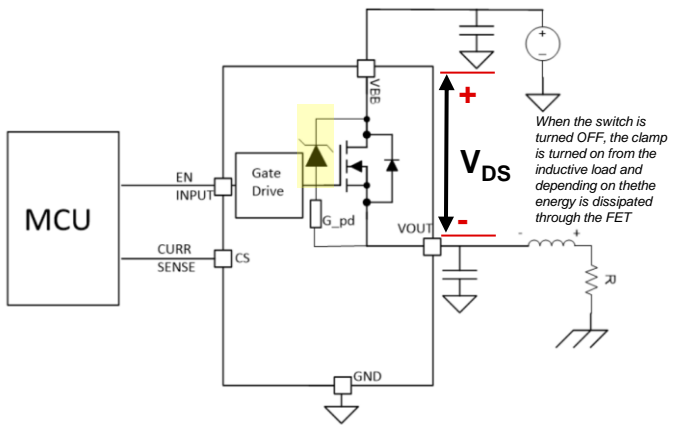

What is the High-side switch's role in driving inductive loads?

- TI's smart High-side switches have an integrated VDS clamp which clamps the negative voltage swing to a safe level to prevent damage to its output.
- Depending on the load, it also helps to dissipate the energy stored in the inductive element by turning on its MOSFET and dissipating the energy through it.

High-side switch | Capacitive load

Safe inductive and capacitive load driving
through integrated clamp and adjustable current
limiting

TI Smart High-side switches enable systems to limit the inrush current through the adjustable current limit I_{LIM}

Advantages:

- **High Reliability** – protects power supply during short circuit or inrush current, prevents upstream supply collapse
- **Lower System Costs** – Reduces the PCB trace and connector size as well as reduces the input power supply

High-side switch | Capacitive load

Safe inductive and capacitive load driving through integrated clamp and adjustable current limiting


TI Smart High-side switches enable systems to limit the inrush current through the adjustable current limit I_{LIM}

Advantages:

- **High Reliability** – protects power supply during short circuit or inrush current, prevents upstream supply collapse
- **Lower System Costs** – Reduces the PCB trace and connector size as well as reduces the input power supply


With no current limit, 330 μ F charged to 13.5V creates significant supply droop.

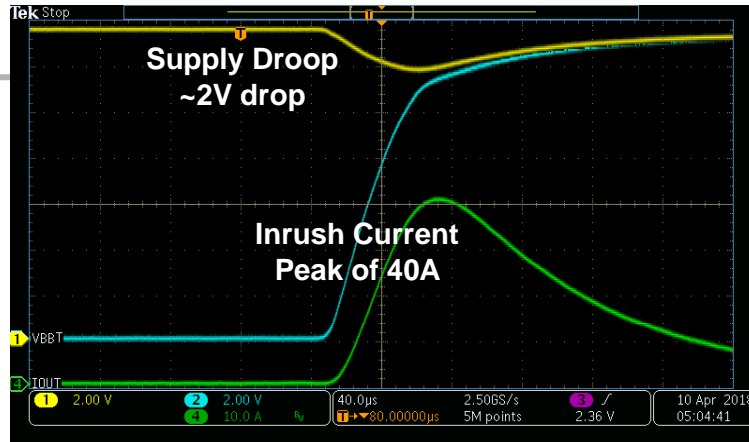During current limiting, the FET regulates the $R_{DS(ON)}$ to increase the V_{DS} and create a constant current source



High-side switch | Capacitive load

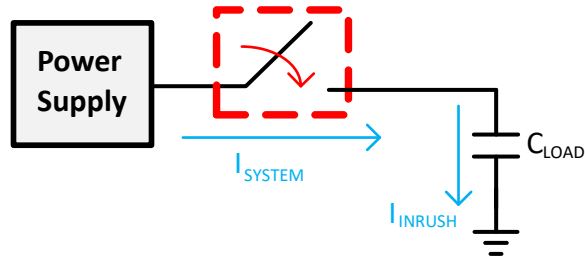Safe inductive and capacitive load driving through integrated clamp and adjustable current limiting



$$I_{SYSTEM} = I_{INRUSH} + I_{LOAD}$$

$$I_{INRUSH} \approx C_{LOAD} \times \frac{dV_{OUT}}{dt}$$

$I_{CL} = I_{INRUSH}$, where I_{CL} equals the current of the High-side switch


$$dt \approx C_{LOAD} \times \frac{V_{OUT}}{I_{CL}} \approx 2 \text{ ms}$$

The max charging current is set by the current limit ($I_{INRUSH}=I_{CL}$), linearly charging the capacitor.

- Peak current from transient overshoot is limited to <4A due to the Smart High-side switch
- Lower charging current results in lower peak currents during inrush which minimizes supply droop and reduces component current handling requirements.
- Charging time is increased as a function of the lower current limit

High-side switch | Capacitive load

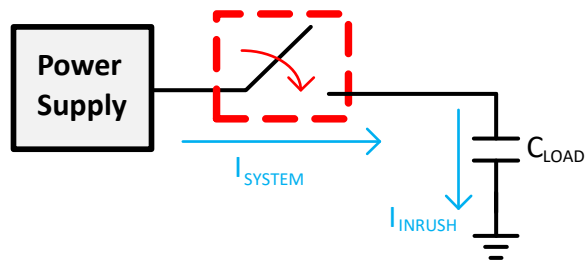Safe inductive and capacitive load driving through integrated clamp and adjustable current limiting




$$I_{SYSTEM} = I_{INRUSH} + I_{LOAD}$$

$$I_{INRUSH} \approx C_{LOAD} \times \frac{dV_{OUT}}{dt}$$

$I_{CL} = I_{INRUSH}$, where I_{CL} equals the current of the High-side switch

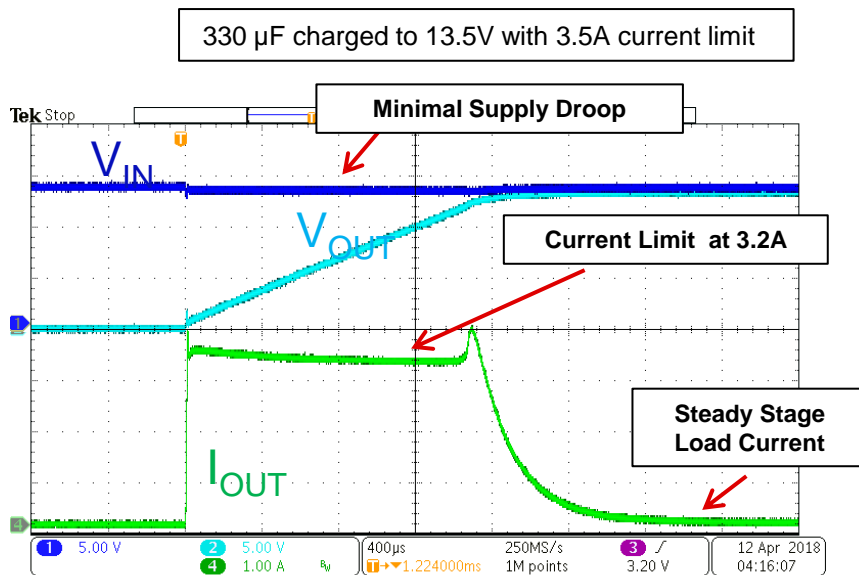
$$dt \approx C_{LOAD} \times \frac{V_{OUT}}{I_{CL}} \approx 2 \text{ ms}$$



The max charging current is set by the current limit ($I_{INRUSH}=I_{CL}$), linearly charging the capacitor.

- Peak current from transient overshoot is limited to <4A due to the Smart High-side switch
- Lower charging current results in lower peak currents during inrush which minimizes supply droop and reduces component current handling requirements.
- Charging time is increased as a function of the lower current limit

Smart High-side switch | Applications

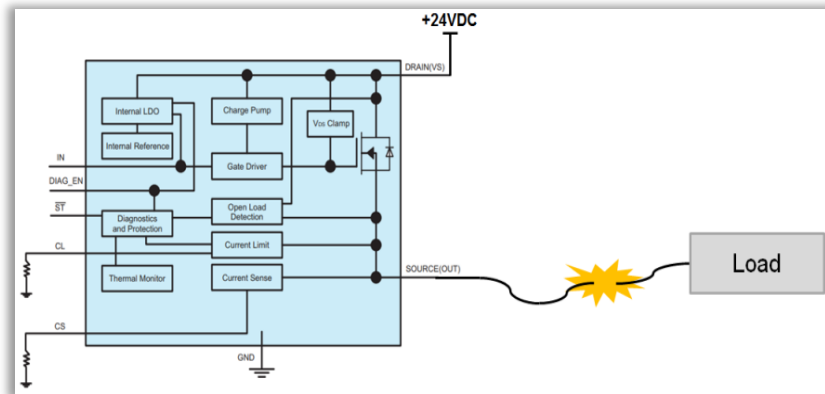

Safe inductive and capacitive load driving through integrated clamp and adjustable current limiting

Short Circuit and current limiting protection improves system reliability and reduces system costs

Integrated **current sense** and **open-load detection** enables the detection and diagnosis of faults


High-side switch | Short circuit



Short Circuit and current limiting improves system reliability and reduces system costs

- Short Circuit protection for outputs prevents damage caused when the output has a low impedance path to ground

High-side switch | Short circuit

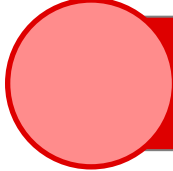



Short Circuit and current limiting improves system reliability and reduces system costs

- Short Circuit protection for outputs prevents damage caused when the output has a low impedance path to ground
- This is typically a customer requirement and cause serious damage if the protection is not implemented properly

High-side switch | Short circuit


Short Circuit and current limiting improves system reliability and reduces system costs

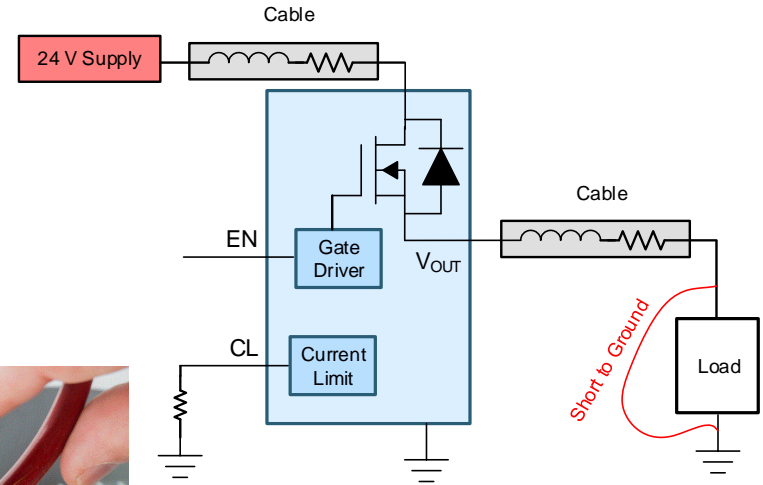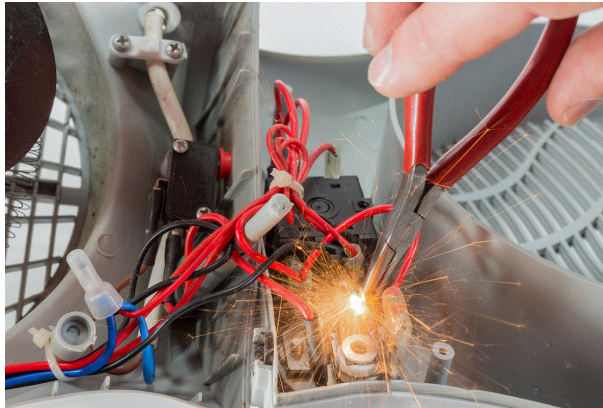- Short Circuit protection for outputs prevents damage caused when the output has a low impedance path to ground
- This is typically a customer requirement and cause serious damage if the protection is not implemented properly



High-side switch | Current limit

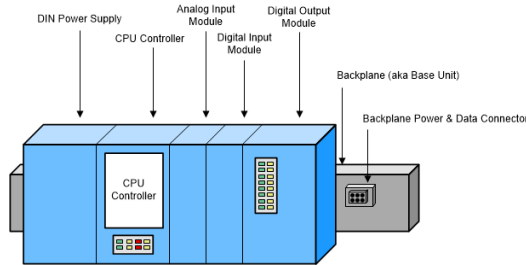Short Circuit and current limiting improves system reliability and reduces system costs




- Below are some technical specifications for an example digital output module

Parameter	Value	Unit
Voltage (typ)	24	V
# of Channels	16	-
I_{OUT} , per CH	0.5	A
Short-circuit threshold (typ)	1	A

- Picking power supply based on load current is insufficient in case of faults and overcurrent events

High-side switch | Current limit

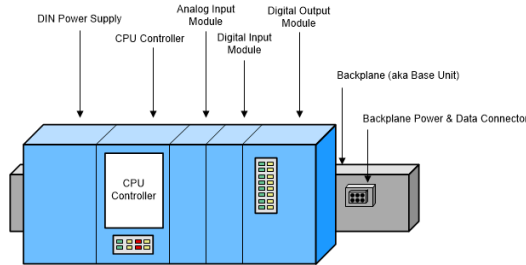Short Circuit and current limiting improves system reliability and reduces system costs




- Below are some technical specifications for an example digital output module

Parameter	Value	Unit
Voltage (typ)	24	V
# of Channels	16	-
I_{OUT} , per CH	0.5	A
Short-circuit threshold (typ)	1	A

- Picking power supply based on load current is insufficient in case of faults and overcurrent events
- The **adjustable current limit of TI's High-side switches** can help to reduce the short circuit trip point which can help to reduce the requirements for the power supply

High-side switch | Current limit

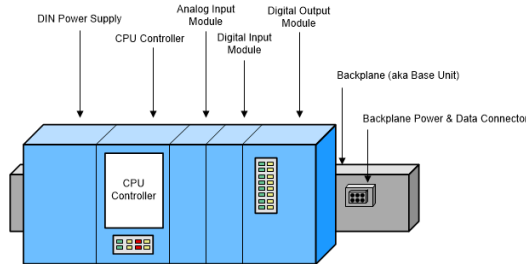Short Circuit and current limiting improves system reliability and reduces system costs



- Below are some technical specifications for an example digital output module

Parameter	Value	Unit
Voltage (typ)	24	V
# of Channels	16	-
I_{OUT} , per CH	0.5	A
Short-circuit threshold (typ)	1	A

Power Supply Output Current Requirements @ 24VDC			
Use cases	# of channels	I_{OUT} , per CH (A)	Total I_{OUT} (A)
Case #1 - nominal current	16	0.5	8
Case #2 - fault case	16	1	16
Case #2 - fault case w/ TPS27S100	16	0.75	12

- Picking power supply based on load current is insufficient in case of faults and overcurrent events
- The **adjustable current limit of TI's High-side switches** can help to reduce the short circuit trip point which can help to reduce the requirements for the power supply

How is I_{LIM} set?

An external resistor generates a reference current from an internal reference voltage that is compared to I_{LOAD}


High-side switch | User set CL

Short Circuit and current limiting improves system reliability and reduces system costs

How is I_{LIM} set?

An external resistor generates a reference current from an internal reference voltage that is compared to I_{LOAD}

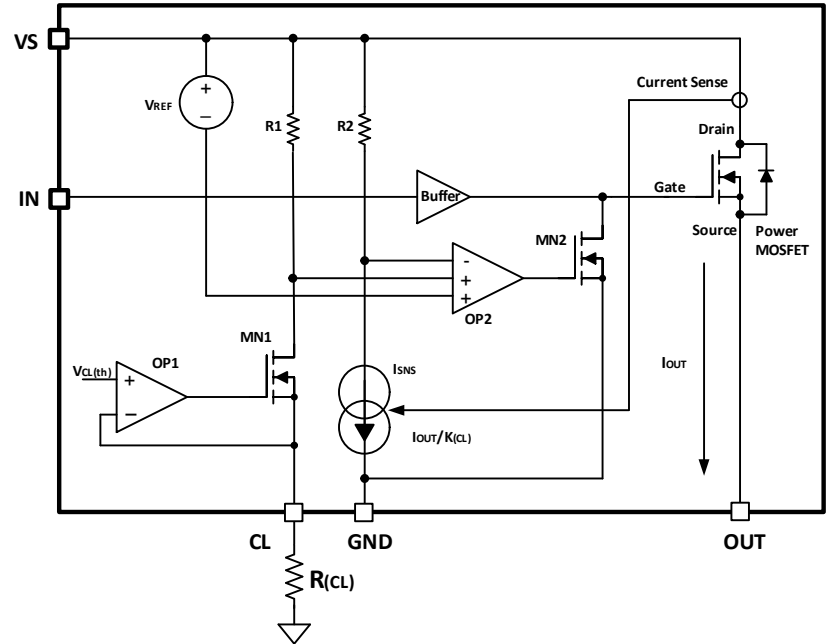During current limiting, the FET regulates the $R_{DS(ON)}$ to increase the V_{DS} and create a constant current source



High-side switch | User set CL


Short Circuit and current limiting improves system reliability and reduces system costs

How is I_{LIM} set?


An external resistor generates a reference current from an internal reference voltage that is compared to I_{LOAD}

During current limiting, the FET regulates the $R_{DS(ON)}$ to increase the V_{DS} and create a constant current source
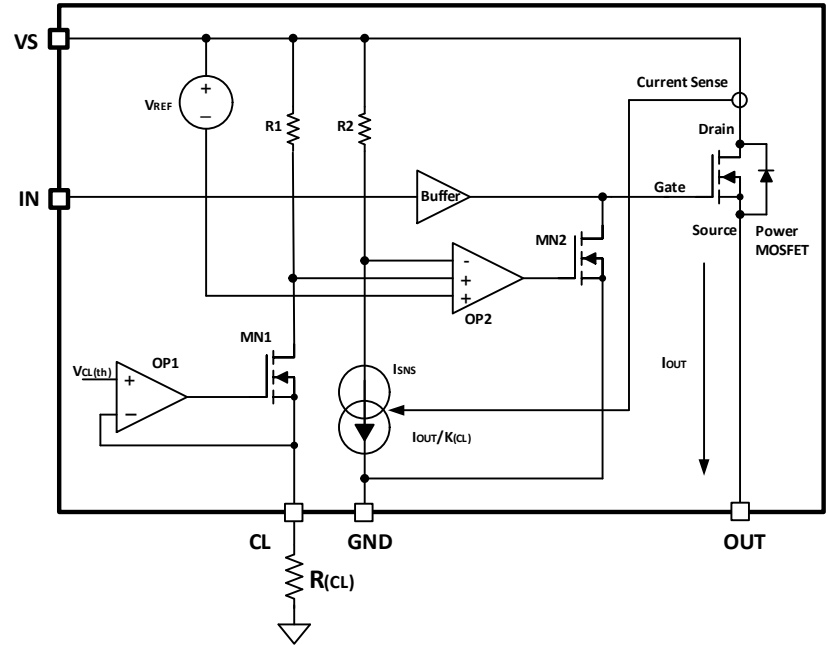
$$I_{CL} = \frac{V_{CL,th}}{R_{CL}} = \frac{I_{out,lim}}{K}$$



High-side switch | Applications

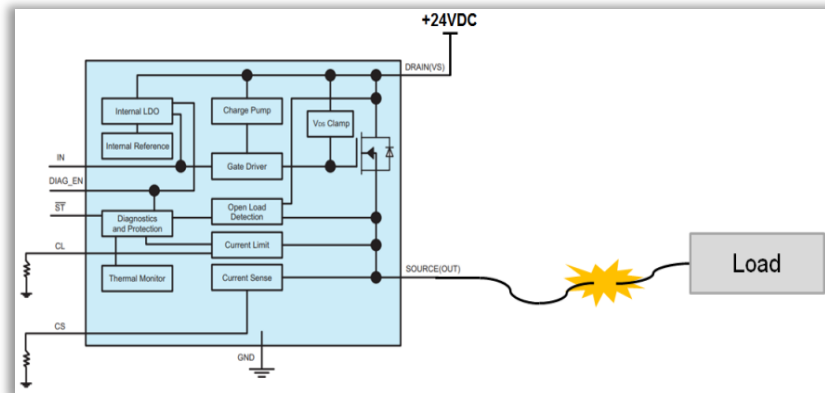

Safe inductive and capacitive load driving through integrated clamp and adjustable current limiting

Short Circuit and current limiting protection improves system reliability and reduces system costs

Integrated **current sense and open-load detection** enables the detection and diagnosis of faults

Smart High-side switch | Diagnostics

Integrated **current sense** and **open-load detection** enables the detection and diagnosis of faults

- Increasing safety and reliability requirements are driving the need for smarter outputs that can detect and respond to fault conditions




Smart High-side switch | Diagnostics

Integrated **current sense** and **open-load detection** enables the detection and diagnosis of faults

- Increasing safety and reliability requirements are driving the need for smarter outputs that can detect and respond to fault conditions
- Smarter outputs enable:
 - Reduce system downtime
 - Smart power management
- High-side switches integrate **load current sense and open load detection** functionality to meet requirements



Smart High-side switch | Diagnostics

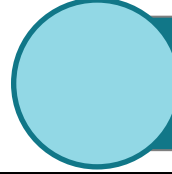

Integrated **current sense** and **open-load detection** enables the detection and diagnosis of faults

- High-side switches can output multiple system variables to the system
 - Load Current
 - Temperature Sense
 - Supply Voltage Sense




Smart High-side switch | Diagnostics

Integrated **current sense** and **open-load detection** enables the detection and diagnosis of faults

- High-side switches can output multiple system variables to the system
 - Load Current
 - Temperature Sense
 - Supply Voltage Sense

CURRENT MONITOR AND CURRENT LIMIT			
$K_{(IMON)}$	Current sense current ratio	500	
$K_{(ILIM)}$	Current limit current ratio	2000	
$dK_{(IMON)}/K_{(IMON)}$	$i_{load} \geq 5 \text{ mA}$	-80	80
	$i_{load} \geq 25 \text{ mA}$	-12	12
	$i_{load} \geq 50 \text{ mA}$	-8	8
	$i_{load} \geq 0.1 \text{ A}$	-5	5
	$i_{load} \geq 1 \text{ A}$	-3	3

MCU
DIGITAL
SNS_OUT

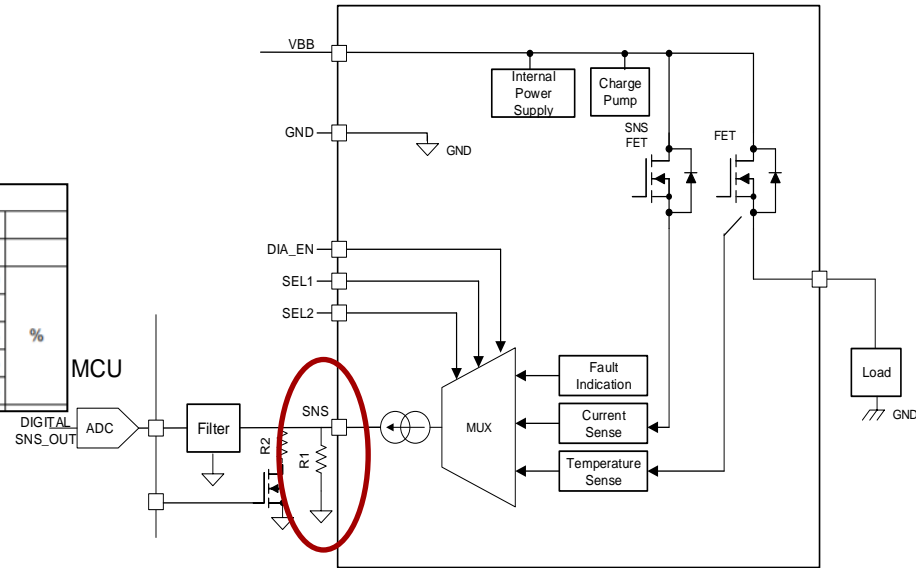


Smart High-side switch | Diagnostics

Integrated **current sense** and **open-load detection** enables the detection and diagnosis of faults


- High-side switches can output multiple system variables to the system
 - Load Current
 - Temperature Sense
 - Supply Voltage Sense

CURRENT MONITOR AND CURRENT LIMIT			
$K_{(IMON)}$	Current sense current ratio	500	
$K_{(ILIM)}$	Current limit current ratio	2000	
$dK_{(IMON)}/K_{(IMON)}$	$i_{load} \geq 5 \text{ mA}$	-80	80
	$i_{load} \geq 25 \text{ mA}$	-12	12
	$i_{load} \geq 50 \text{ mA}$	-8	8
	$i_{load} \geq 0.1 \text{ A}$	-5	5
	$i_{load} \geq 1 \text{ A}$	-3	3

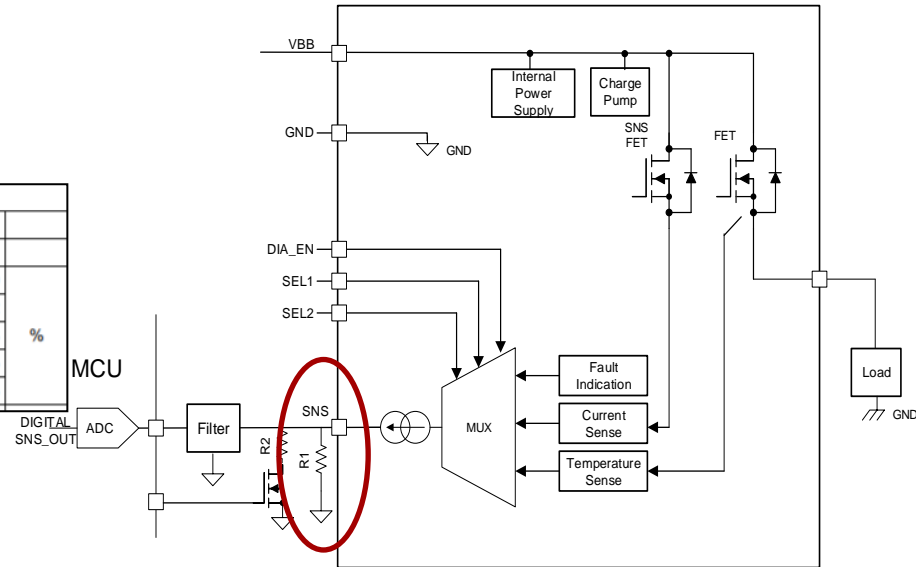- Values are output as an analog current on the SNS pin



Smart High-side switch | Diagnostics

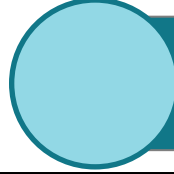

Integrated **current sense** and **open-load detection** enables the detection and diagnosis of faults

Open load detection enables detection of broken cables or mis-wiring conditions.

Smart High-side switch | Diagnostics

Integrated **current sense** and **open-load detection** enables the detection and diagnosis of faults

Open load detection enables detection of broken cables or mis-wiring conditions.

On State Detection

If load current drops below the threshold in datasheet, the device will register a fault.

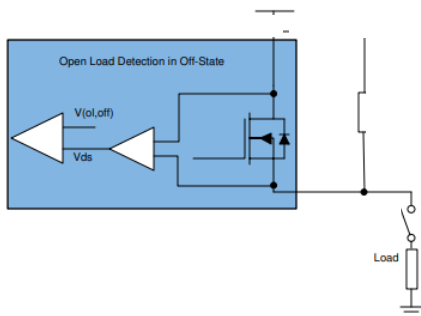


Figure 29. Open-Load Detection Circuit in Off-State

I _{ol,on} Open load detection threshold in ON-state	2	5	8	mA
T _{ol,on} Open load detection threshold deglitch time in on state	200	250	300	us

Smart High-side switch | Diagnostics

Integrated **current sense** and **open-load detection** enables the detection and diagnosis of faults

Open load detection enables detection of broken cables or mis-wiring conditions.

On State Detection

If load current drops below the threshold in datasheet, the device will register a fault.

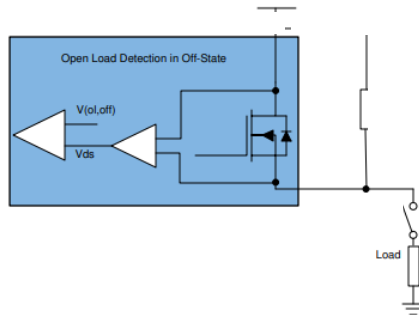



Figure 29. Open-Load Detection Circuit in Off-State

I _{ol,on} Open load detection threshold in ON-state	2	5	8	mA
T _{ol,on} Open load detection threshold deglitch time in on state	200	250	300	us

Off State Detection

Open Load Detection requires a pull up resistor on the output. If $V_{OUT} > \text{threshold}$ the device recognizes that there is no load attached.

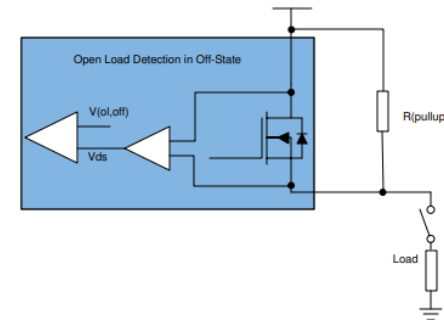Choose pull-up resistor to overcome any pulldown including leakage other than the load. (A resistor divider for V_{OUT} monitoring is shown)



Learn More: 11 Ways to Protect Your Power Path



11 Ways to Protect Your Power Path

Design Tips and Tradeoffs Using TI's Power Switches



Introduction: Basics of Power Switches

Table 1. Power Switch Topology Table

	POWER DISTRIBUTION		INPUT POWER PROTECTION			OUTPUT POWER PROTECTION	
	Load Switch	Power MUX (2 input, 1 output)	eFuse (Internal FET)	Hot Swap (External FET)	Ideal Diode (Offing Controller)	Smart High-Side Switch	Low-Side Switch
Voltage Range	0 V to 18 V	2.8 V to 22 V	2.7 V to 60 V	±60 V	±75 V	6 V to 40 V	0 V to 100 V
Max Operating Current	15 A	4.5 A	15 A	N/A	N/A	12 A	1 A
Functions							
Inrush Current Control	✓	✓	✓	✓		✓	
Adjustable Current Limit	✓	✓	✓	✓		✓	
Reverse Current Blocking	✓	✓	✓	✓	✓		
Current Sense Monitoring	✓	✓	✓	✓	✓	✓	
Short-Circuit Protection	✓ ⁽¹⁾	✓	✓	✓	✓	✓	
Overvoltage Protection		✓	✓	✓		✓	
Reverse Polarity Protection		✓	✓	✓	✓	✓	
Power Good Signal	✓	✓	✓	✓	✓	✓	
Inductive Load Compatibility			✓	✓	✓	✓	✓
Load-Dump Compatibility			✓	✓	✓	✓	✓
Thermal Shutdown	✓	✓	✓	✓	✓	✓	✓

⁽¹⁾ Self-protected load switch

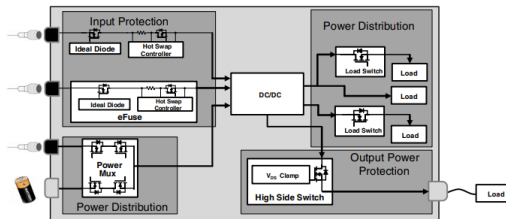


Figure 1. Typical Power Switch Use Cases

Chapter 10: Safely Driving an Inductive Load

Author: Mahmoud Hamouch

Abstract

Inductive loads are relays, solenoids, electric motors and even loads connected through a long cable. Their impedance consists of both a resistance (R) and an inductance (L) in series. The R value determines the steady-state current, and the L value determines the stored magnetic energy. This stored magnetic energy in the inductor can cause system- or component-level damage if not properly dissipated.

The opening or closure of a magnetic contact in a relay or solenoid requires the storage or dissipation of magnetic energy. In the case of an electric motor, this stored energy is necessary for mechanical rotation. Inductive loads are continuously energized and de-energized for opening or closing contacts (relays and solenoids) and rotation or idle (electric motors). Disconnecting an inductive load from an energized state creates a high-voltage spike that can lead to system damage. Safely de-energizing an inductive load requires the implementation of an appropriate clamp.

Introduction

When encountering an inductive load, you must take into account the amount of energy stored, as this energy can damage components in the system if not properly managed.

There are two states to consider when driving an inductive load:

- Energizing or connecting the inductive load to a voltage source such as a battery.
- De-energizing or disconnecting the inductive load from the voltage source.

You can reach either state by using switches such as a bipolar junction transistor, a power field-effect transistor, or an integrated switch that connects one side of the switch to the voltage source (the high-side switch) or to ground (the low-side switch). In some instances, the integrated switch option may integrate a voltage clamp.

In the energizing state, the switch drives the steady-state load current and the inductance stores magnetic energy equal to half the L value and the square of the load current.

In the de-energizing state, the current decays from the steady-state value to zero; a voltage spike proportional to the current slope appears across the switch. The voltage spike must be limited and safely dissipate the stored energy, or it can damage the system.

This chapter focuses on calculating inductive load parameters for optimizing drive circuit capability. For both high- and low-side switches, the energizing and de-energizing mechanism is the same.

Challenges of Inductive Loads

The voltage across an inductive load is time-dependent.

Equation 1 calculates the inductive load parameters necessary for selecting a reliable drive circuit:

$$V(t) = R I(t) + L \frac{dI(t)}{dt} \quad (1)$$

Equation 1 shows that an overvoltage spike can occur when disconnecting an inductive load due to a sudden change in current—the $dI(t)/dt$ component. The magnitude of this overvoltage spike is the element that can cause component damage, and, if necessary, should be clamped.

Energizing an Inductive Load

An inductive load is energized when connected to a voltage source. The current ramps up exponentially to a steady-state value and magnetic energy is stored in the coil. **Figure 1** illustrates this behavior, using a high-side switch to drive the load.

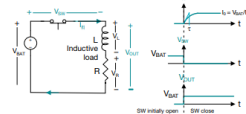


Figure 1. Energizing an inductive load waveform.

When energizing an inductive load in a resistor-inductor (RL) circuit, the voltage loop is a first-order differential equation (**Equation 2** on the following page):



©2020 Texas Instruments Incorporated. All rights reserved.

The material is provided strictly "as-is" for informational purposes only and without any warranty.
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated