

# **TIDA-00961 – TRM/CRM/BCM TTPL PFC**

**(Transition Mode/Critical Conduction Mode/Boundary Condition Mode Totem-Pole PFC)**


# Agenda

- Introduction
- Challenges & Solutions
- Implementation Details
- Experimental Results

# System Introduction
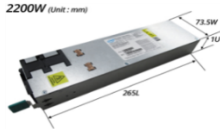
## Target Systems for the design

- Network & Server Power Supply Unit (PSU)
- Telecom Rectifier
- Industrial Power Supply
- Automotive



Smaller Size


Higher Efficiency

Fewer components

Bridgeless topology

Higher frequency


Totem-Pole + GaN + C2000 = TIDA-00961

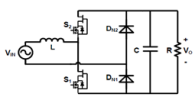

## System Trends
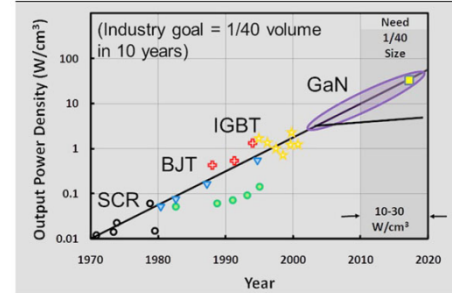
### Higher Energy Density

- Industry targets 1/6 reduction in vol in 10 yrs
- Smaller size need Higher switching freq.
- ~100/200 KHz today: expected 5 to 10 fold jump with GaN.




### Higher Efficiency

- Regulatory standards
- Thermal management
- Complex topologies need digital control
- Bridgeless topology in PFC, and hence GaN

80 Plus Performance Specification – Efficiency Requirements

	80 PLUS	80 PLUS BRONZE	80 PLUS SILVER	80 PLUS GOLD	80 PLUS PLATINUM	80 PLUS TITANIUM
10%						
20%	80%	82%	85%	87%	90%	92%
50%	80%	85%	88%	90%	92%	94%
100%	80%	82%	85%	87%	89%	90%
PF	≥ 90	≥ 90	≥ 90	≥ 90	≥ 95	≥ 95
	at 100%	at 50%	at 50%	at 50%	at 50%	at 20%
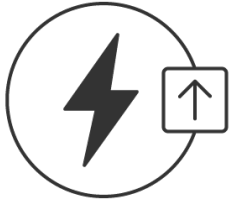
# Benefits of the **LMG341x GaN** power stage




## Maximum power density and efficiency

GaN power stage enables **double power density and 80% lower losses** than silicon MOSFET with high-speed, MHz switching frequency


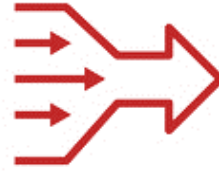
## Devices for every power level

Fully integrated driver, FET and protection in **50 m $\Omega$ , 70 m $\Omega$  and expanding portfolio** offer a single-chip solution for applications ranging from sub-100 W to 10 kW



## Simplifies design

Comprehensive portfolio of designs for AC-DC, isolated DC-DC and inverter topologies enables ease of design and **faster time to market**




## System reliability

Backed by **20 million device reliability hours** and features built-in intelligence for over-temperature, over-current and under voltage lockout protection

View the LMG3410R070 [datasheet](#)
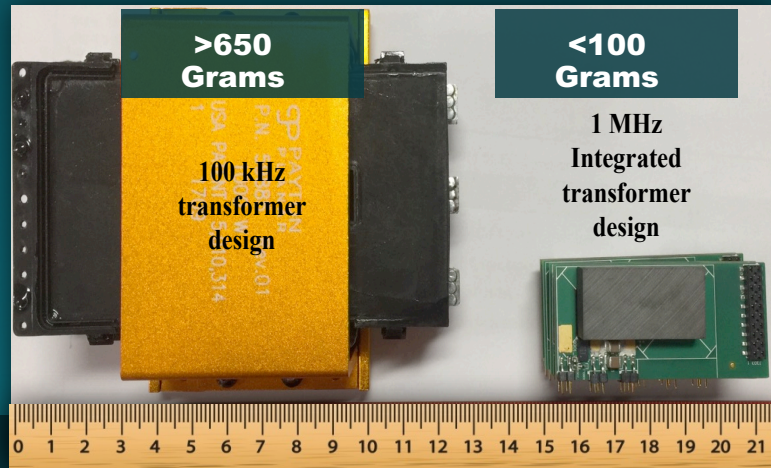
# Maximized efficiency + power density for industrial and telecom designs



Compared with a 100kHz silicon design, the GaN design is **6X** smaller



The **Highly Efficient, 1.6kW High Density GaN Based 1MHz CrM Totem-pole PFC Converter Reference Design** is a high density (165 x 84 x 40 mm) design that achieves 98.7% efficiency at full load and 230-V AC input for many space constrained applications such as server, telecom, and industrial power supplies.

- [TIDA-00961 and tools folder](#)
- [Design guide](#)

# Highly Efficient, Compact, 1.6 kW Bridgeless ZVS Transition Mode GaN PFC Reference design for Server PSU / TI Design: TIDA-00961



## Features

- TMS320F28004x controller based fully programmable solution
- Two phase interleaved operation
- Output Power: 1.6 KW, 4.1A @ 390V
- Efficiency: ~ 99% ; Power Factor : >0.99
- Switching frequency range from 200kHz to 1.2MHz
- Compact Form Factor (165 x 84 x 40 mm for the full board and 65 x 40 x 40 mm for the power stage)
- High Power Factor > 0.99 and low THD; Meets Current THD Regulations as per IEC 61000-3-2
- Wide input voltage range: 85 – 265 VAC

## Target Applications

- Telecom Rectifiers
- Server & Industrial supplies
- EV OBC

## Tools & Resources


### Board Image




- **TIDA-00961 and Tools Folder**
- **Design Guide**
- **Design Files:** Schematics, BOM, Gerber
- **Device Datasheets:**
  - [LMG3410](#), [TMS320F280049](#), [UCC27712](#), [ISO7740](#), [ISO7720](#), [LMV612](#), [OPA237](#), [UCC28740](#), [TPS62153](#)
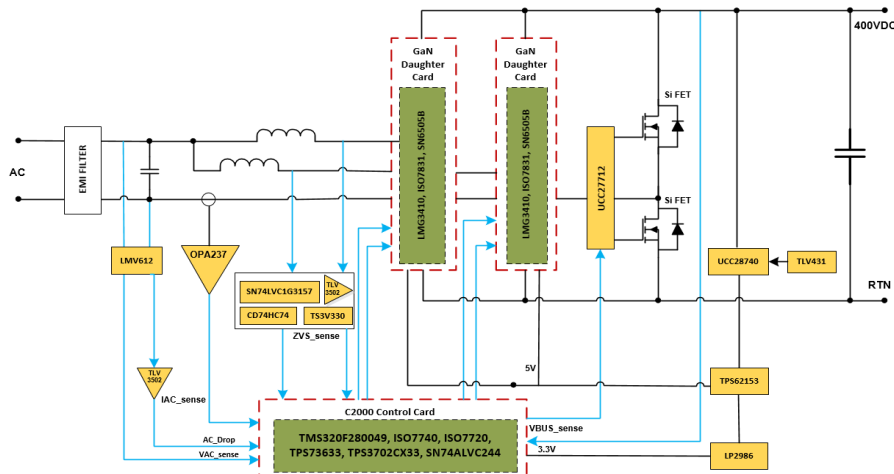
## Benefits

- **Super High Efficiency** makes thermal design simpler
- **Extremely compact** solution with low component count
- Makes compliance with **80 Plus Titanium specs** easier
- Addresses universal AC input requirements
- Integrated GaN FET and driver eases layout constraints
- Provides a ready platform of GaN based transition mode totem pole PFC to address various power supplies up to 2 kW




# PFC Modes of Operation

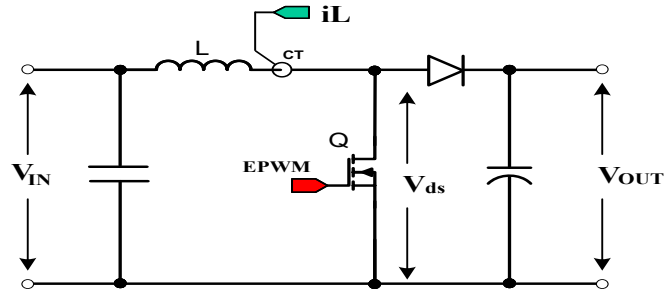


Variable  
Frequency  
Operation


**CCM Mode of operation**

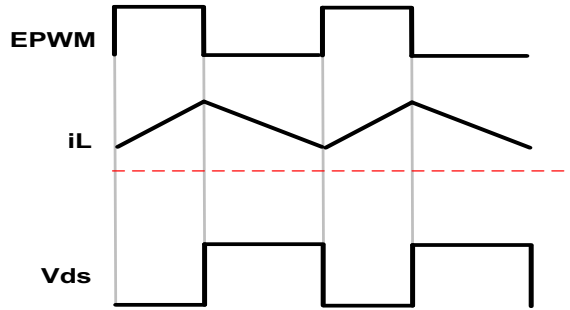


**DCM Mode of operation**

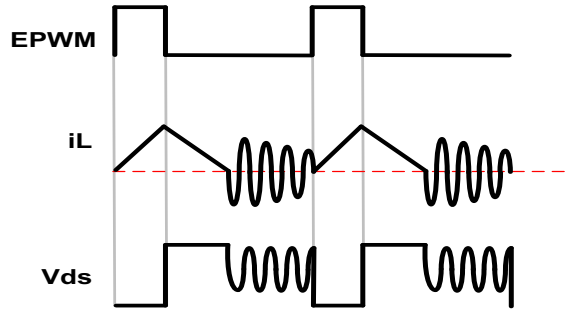


**TRM/CRM Mode of operation**

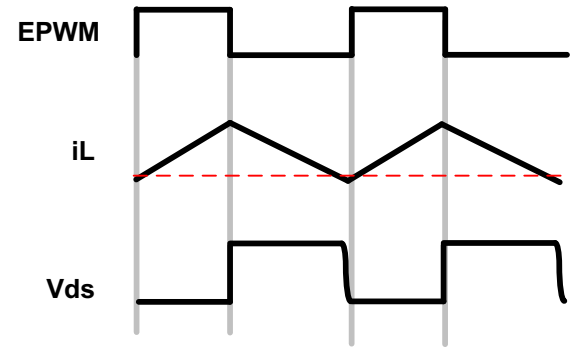


# Totem-Pole PFC (CRM or TRM)

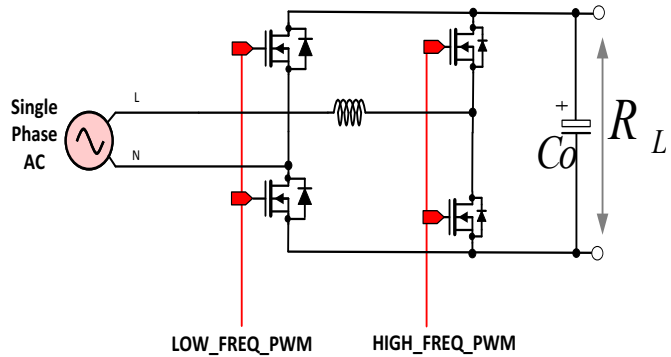


# 2 Ph IL TP PFC (CRM or TRM)

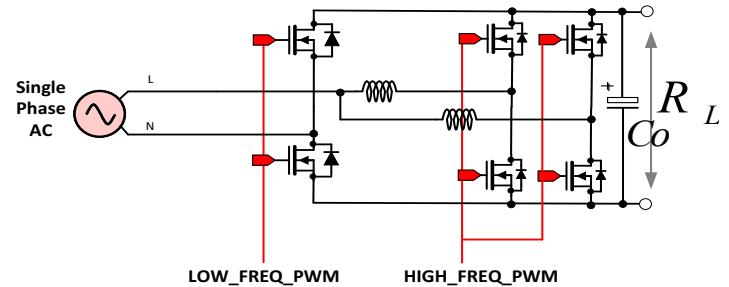

# Positive Half Cycle

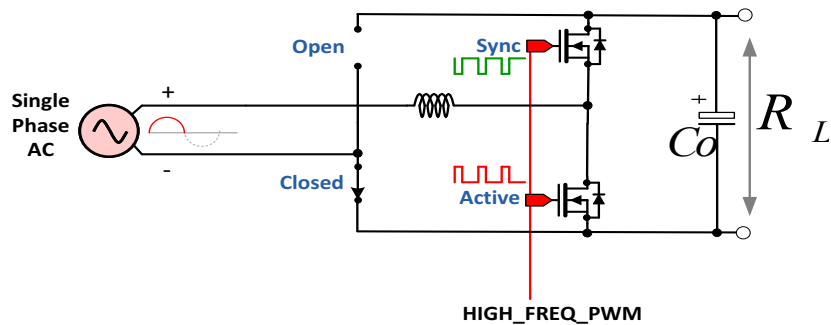

# Negative Half Cycle

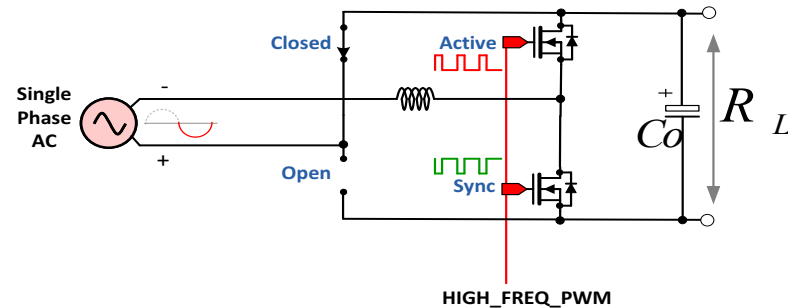





# Key Challenges & Solutions
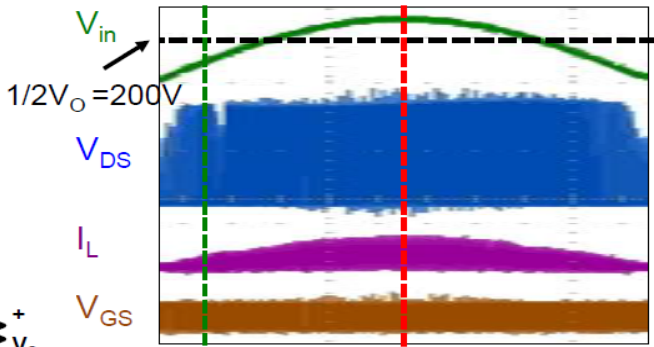
# #1 Achieving ZVS across line-load and over full AC cycle


$V_{IN\_RMS}=230V, V_O=400V, \text{ Full Load, } F_S=1\text{-}3\text{MHz}$





Line-cycle Averaged Non-ZVS

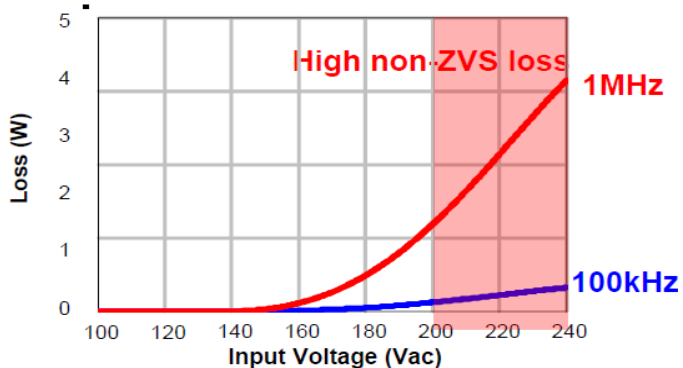





Totem-pole PFC

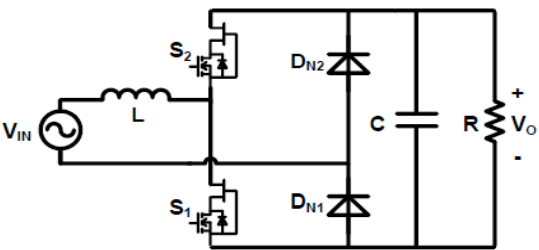

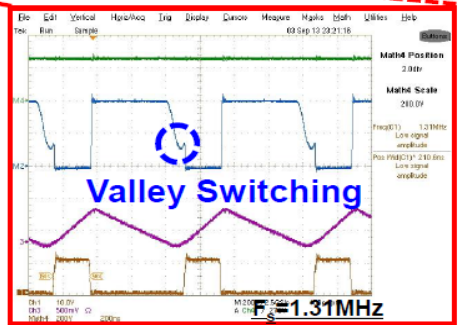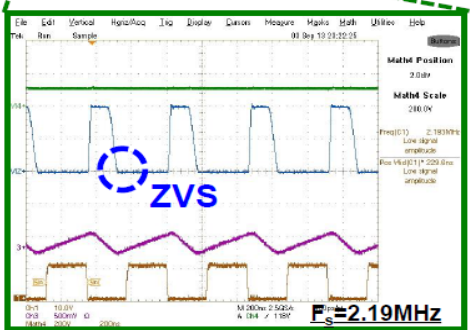$V_{in}$  (200V/div)  
 $V_{DS}$  (200V/div)  
 $I_L$  (10A/div)  
 $V_{GS}$  (10V/div)


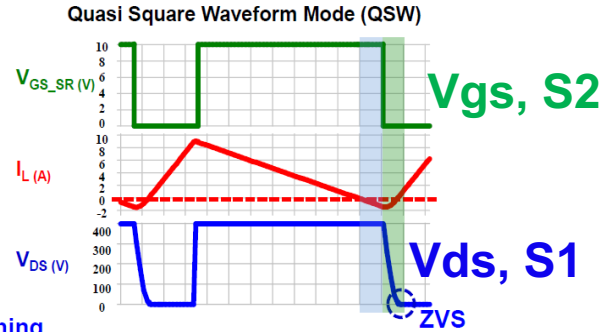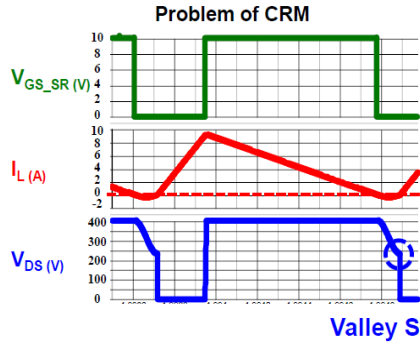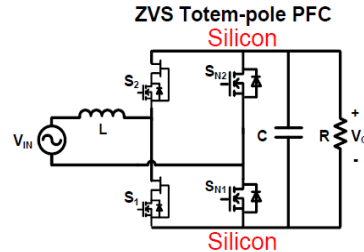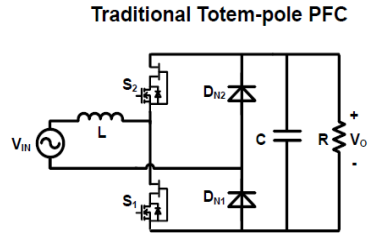
# ZVS Extension – Inductor Current Sensing



## Conventional Solution

- Inductor current zero crossing sensing

- Low SNR
- Worse under high-line low-load

## C2000 Solution





- Sensing voltage across the inductor
- On-chip CMPSS and type-4 PWM features on C2000 are used to solve this

\* Bin Su, Junming Zhang, and Zhengyu Lu, "Totem-Pole Boost Bridgeless PFC Rectifier With Simple Zero-Current Detection and Full-Range ZVS Operating at the Boundary of DCM/CCM", IEEE Transactions on Power Electronics, Vol. 26, No. 2, pp. 427 – 435, Feb 2011

\* Christoph Marxgut, Florian Krismer, Dominik Bortis, and Johann W. Kolar, "Ultraflat Interleaved Triangular Current Mode (TCM) Single-Phase PFC Rectifier", in IEEE Transactions on Power Electronics, Vol. 29, No. 2, pp. 873 – 882, Feb 2014

\* Source: CPES, Virginia Tech

# ZVS with AC Input

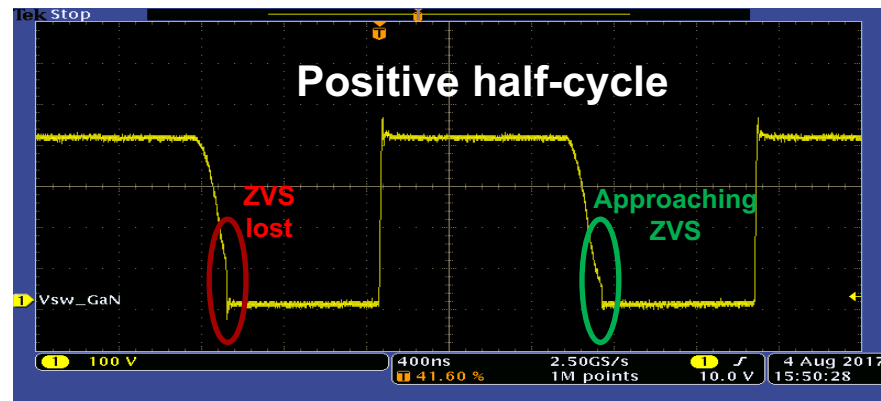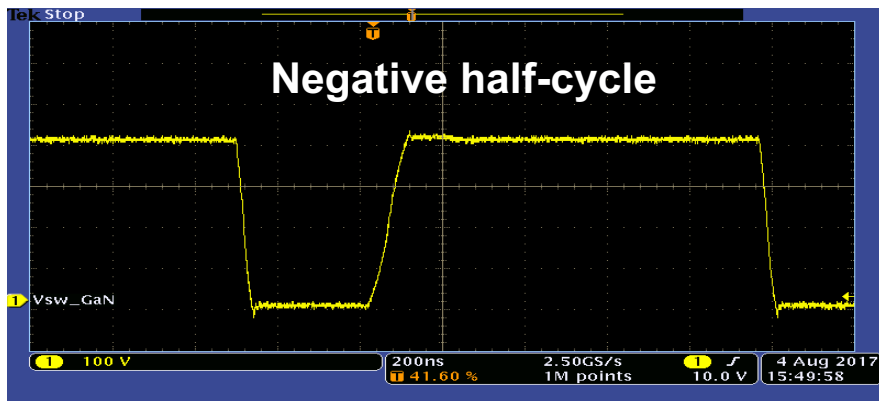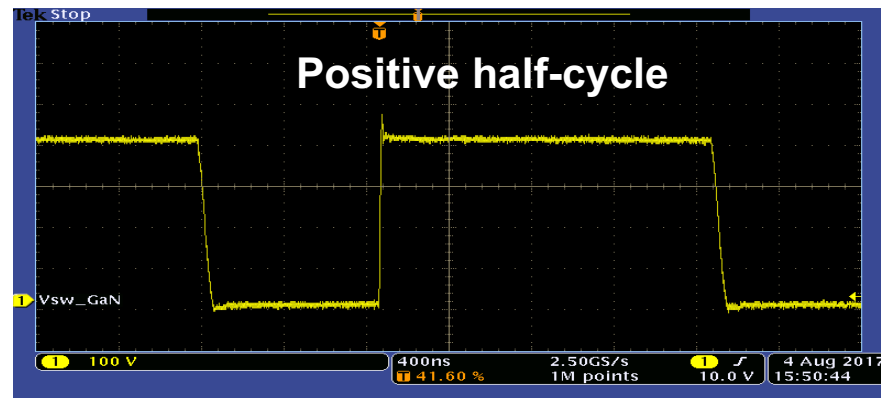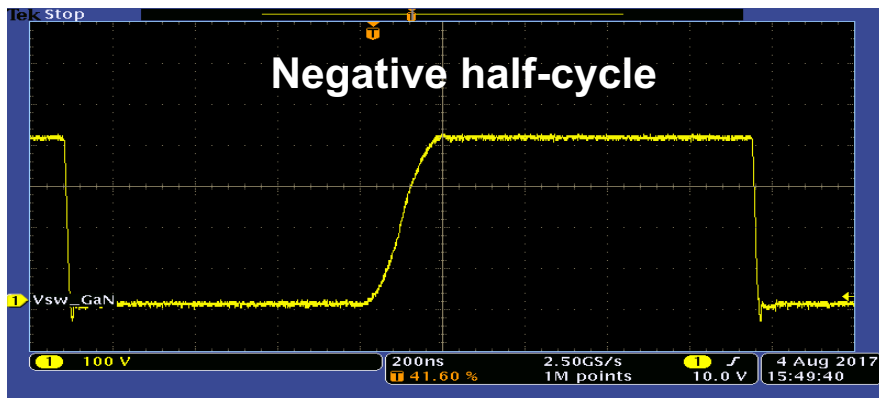

# #2 Cycle Intensive Calculations

- Calculating correct turn-on and turn-off durations at every switching/control instant

## Solution

- C2000's TMU helps reduce the MIPS requirements considerably  
Example: From possible > 10us calculation time to <0.5us calculation time

### Ton Calculations

$$f_1(T_{on}) = \frac{V_{in}V_o}{(V_o - V_{in})L} \cdot \frac{T_{on}^2}{2I_{ref}\sqrt{2LC_{oss}}} - \frac{T_{on}}{\sqrt{2LC_{oss}}} - \sqrt{\frac{V_{in}^2}{(V_o - V_{in})^2} \left(1 + \frac{T_{on}^2}{2LC_{oss}}\right) - 1}$$

$$f_2(T_{on}) = \frac{(V_o - V_{in})T_{on} + \sqrt{V_{in}^2 T_{on}^2 + 2LC_{oss}(2V_{in}V_o - V_o^2)}}{(V_o - V_{in})\sqrt{2LC_{oss}} - (V_o - V_{in})T_{on}\sqrt{V_{in}^2 T_{on}^2 + 2LC_{oss}(2V_{in}V_o - V_o^2)}}$$

$$C = \frac{V_o^2(2V_{in} - V_o)}{V_{in}(V_o - V_{in})} \cdot \frac{1}{2I_{ref}} \sqrt{\frac{2C_{oss}}{L}} - 2\pi - \frac{\sqrt{V_o^2 - 2V_{in}V_o}}{V_{in}} + \tan^{-1} \frac{\sqrt{V_o^2 - 2V_{in}V_o}}{V_{in}}$$

### Dead-time Calculations

$$t := \sqrt{L_o \cdot 2 \cdot C_{oss}} \cdot \left[ 3.14159 - \operatorname{atan} \left[ \frac{\sqrt{(2V_{in} - V_o) \cdot V_o}}{V_o - V_{in}} \right] \right]$$



- Possibility of negative current/current spikes
- Body diode losses

# #3 Clean cross-over transitions



- TRM/CRM PFC uses a small PFC inductance
- Current goes discontinuous
- As a result any voltage that builds-up across silicon FET, discharges at a very high rate the moment silicon FET and/or the GaN sync FET are turned ON
- This can cause huge current spikes around the zero crossing point
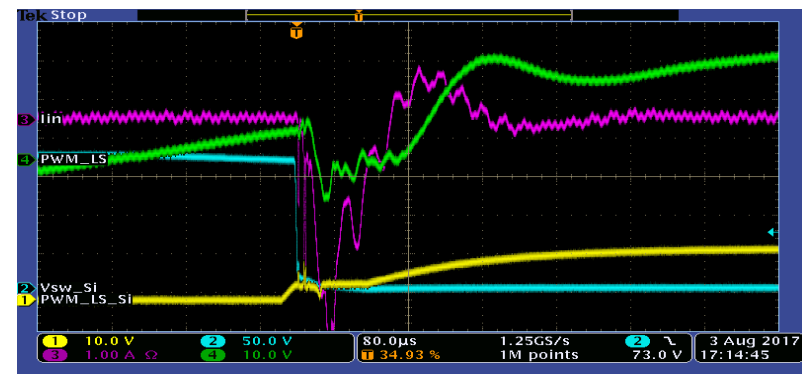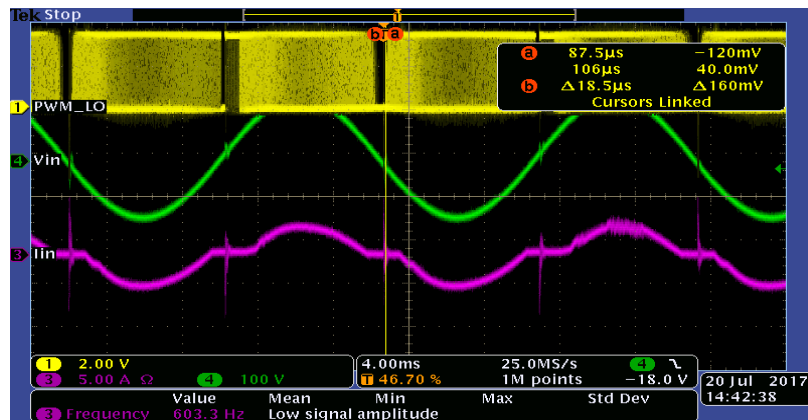
## Solution

- Soft-start for active FETs
- Proper turn-on sequence
- These are implemented using a software state-machine



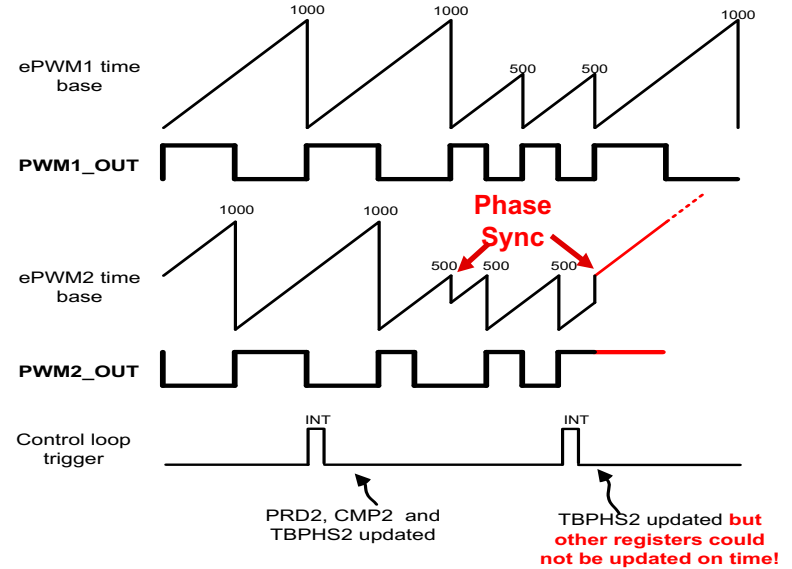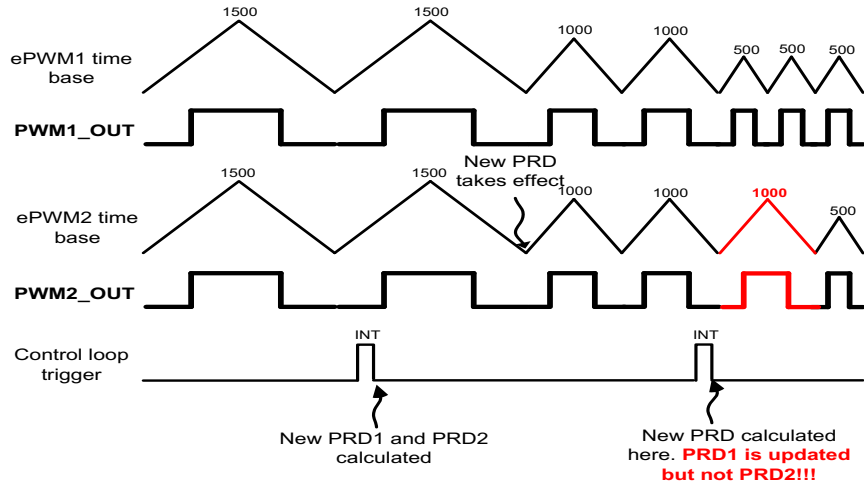
# #4 Correct PWM waveform generation with HRDB



## What is missing?

- A clean and easy way to update multiple registers in a PWM module
- A clean and easy way to update registers in multiple PWM modules
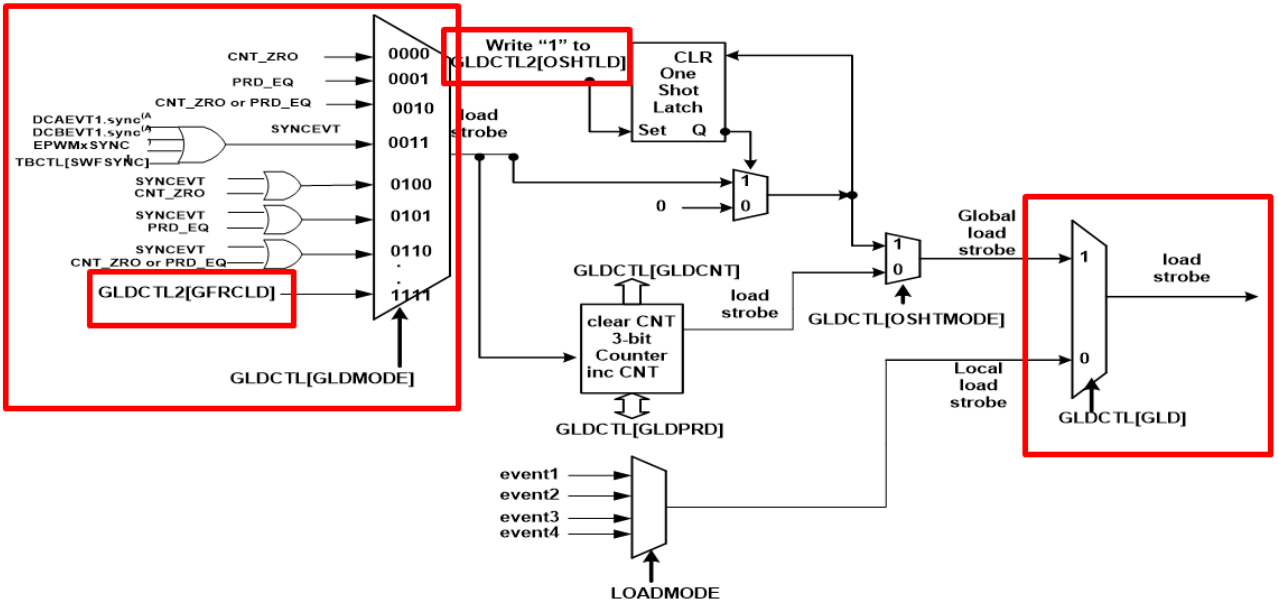
# Solution: One Shot & Global Reload (Type-4 PWMs)



## One shot reload usage

### Initialization

- Enable global reload
- Link GLDCTL2 registers

### Run Time

- Update all registers
- Write '1' to GLDCTL2[OSHTLD]
- Write '1' to GLDCTL2[GFRCLD], if desired


TRM PFC operating at high switching frequencies also requires **hi-res dead-band (HRDB)** between the turn-off of the active FET and the turn-on of the sync FET



# Software Flowchart

## C Environment


### System Level Management

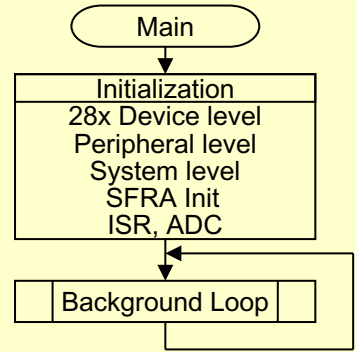

# Processor Resource Utilization

## • CPU Bandwidth

	Execution time	Description
Slow Control ISR	20.8us	10 kHz, voltage loop, phase shedding
Fast Control ISR	12.4us	50 kHz current loop, AC cycle state machine, phase re-enable, PLL
PWM ISR	2.04us	$f_{sw}/3$ ZVS loop, phase shifting

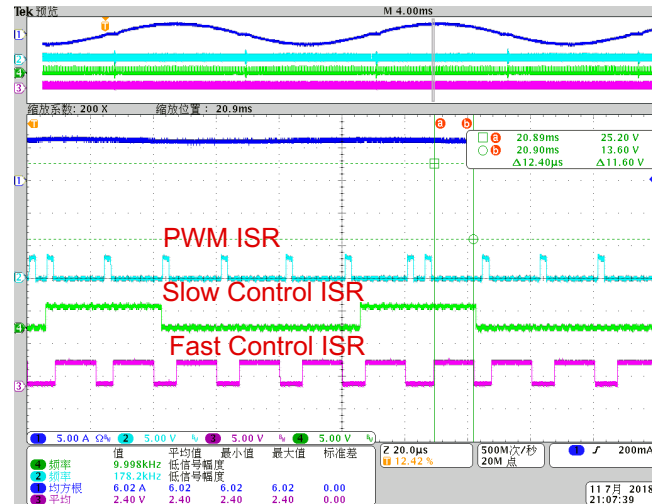

## • F280049 Peripheral Usage


- 4 PWM Modules, 2 CMPSS for OCP&ZVS, 4 ADC channels

## • Memory Usage

- FLASH: 14KW, RAM: 7KW (for F280049, 128 KW Flash, 50KW RAM in total)
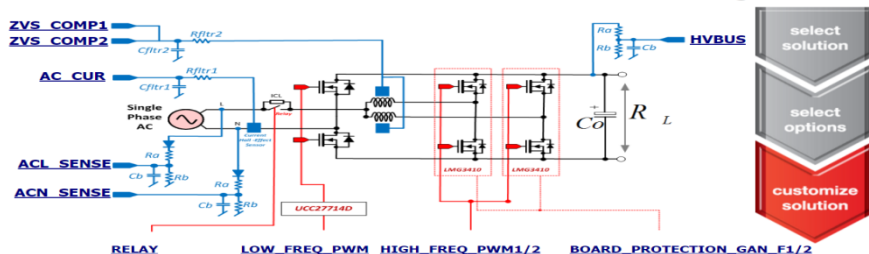
# PowerSUITE – Interleaved TRM TP PFC

2-PH Interleaved TRM Totem Pole PFC using F28004x



Project Options

**INCR\_BUILD** 1: Open Loop **Input** AC **Control Running on** C28x

**Phase Shedding** Enabled **Non-linear loop** Disabled **Auto run** Disabled

Control Loop Design

**Tuning** None **Comp Number** - **Comp Style** -

**SFRA** Current **Current Loop Frequency** Current Loop ISR runs at Fsw **Voltage Loop Frequency** Voltage Loop runs at 10KHz

Power Stage Parameters

**PWM :** Min. Switching Freq (Fsw in kHz) 200 Max. Switching Freq (Fsw in kHz) 1000

**Nominal Voltage :** Output Vbus (V) 390.0

Min. Input VL-L(Vrms) 90.0 Max Input VL-L(Vrms) 245.0

**Power :** Rated (W) 1600.0 Operating (W) 768.0

**Inductor (Li):** Inductance (uH) 0.481

**Output Cap (Co):** Capacitance (uF) 1410.0 ESR (Ohm) 0.365

Voltage And Current Sensing Parameters

Refer to calculations.xlsx file located in the install package for more details



**Voltage Sense :** Max Vbus (V) 536.85 Max Vin (+-V) 677.51

**Current Sense :** Max (+-Amp) 22.295 Trip Set (+-Amp) 15.0


**Sense Filter:** Rftr (Ohm) 47.0 Cftr (uF) 0.047

Cut-off Freq (kHz) 72.085



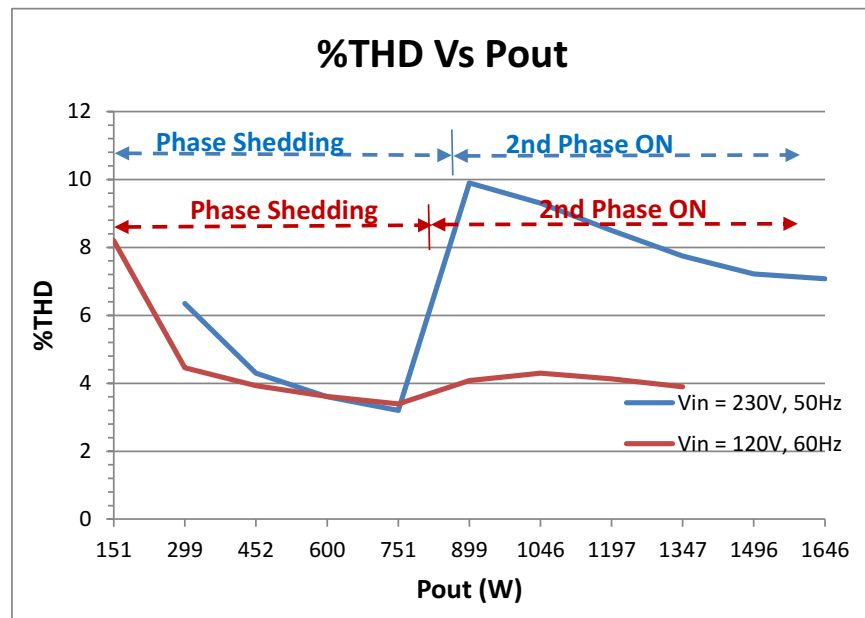
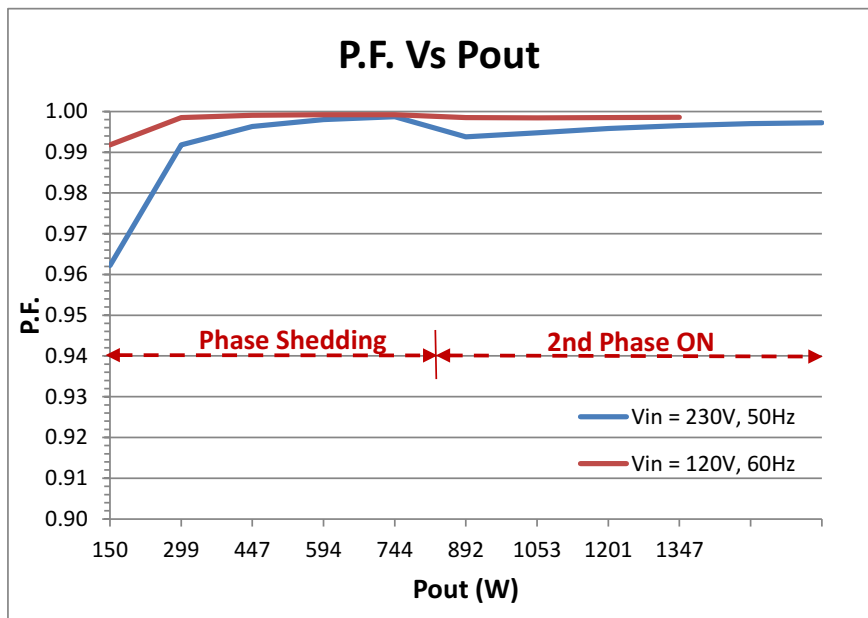
# Input Current THD & Power Factor (2 Phase Interleaved)







# PFC Efficiency (2 Phase Interleaved)

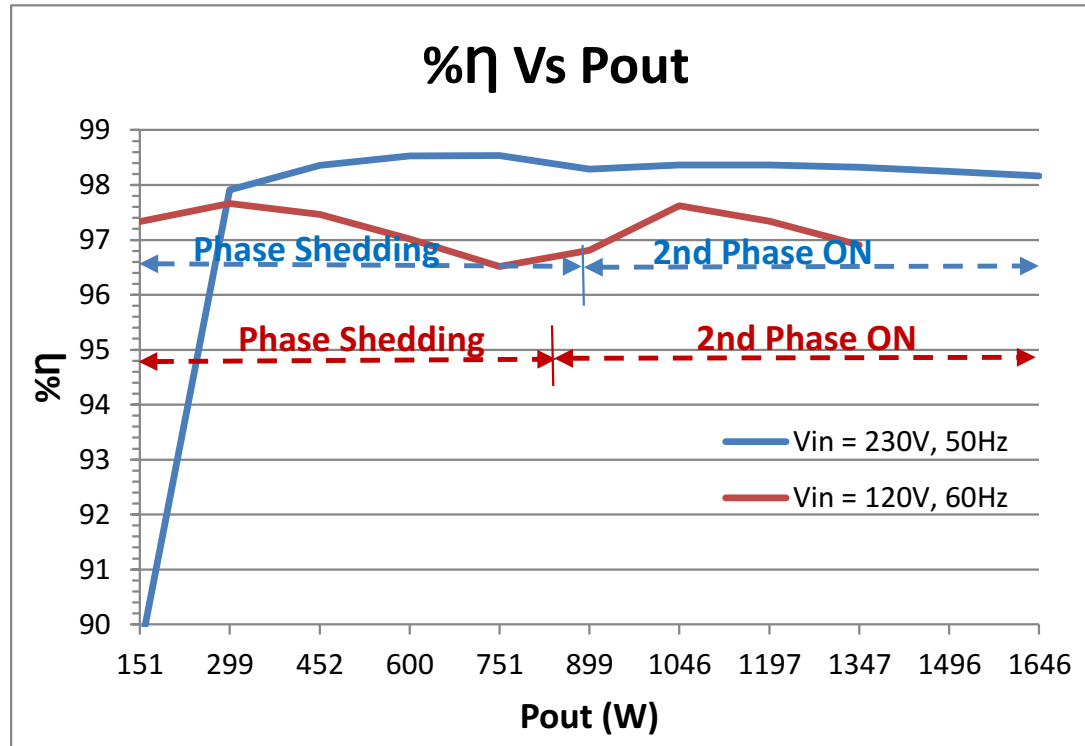
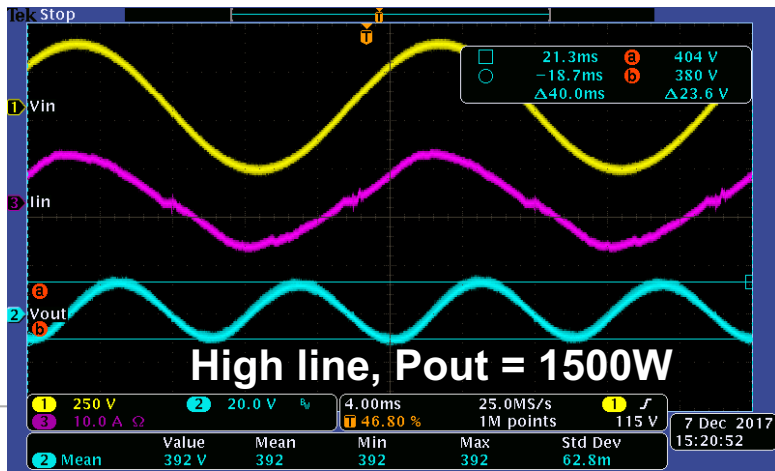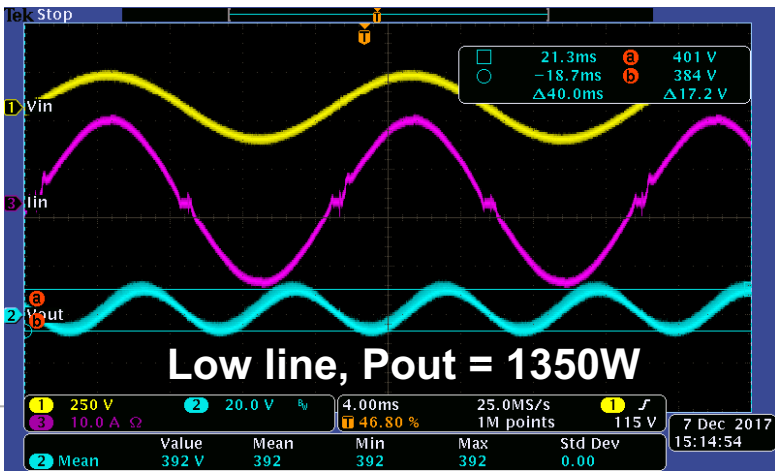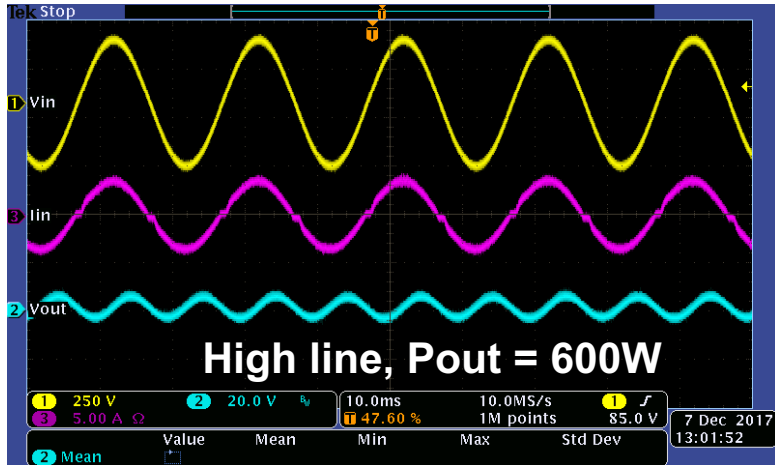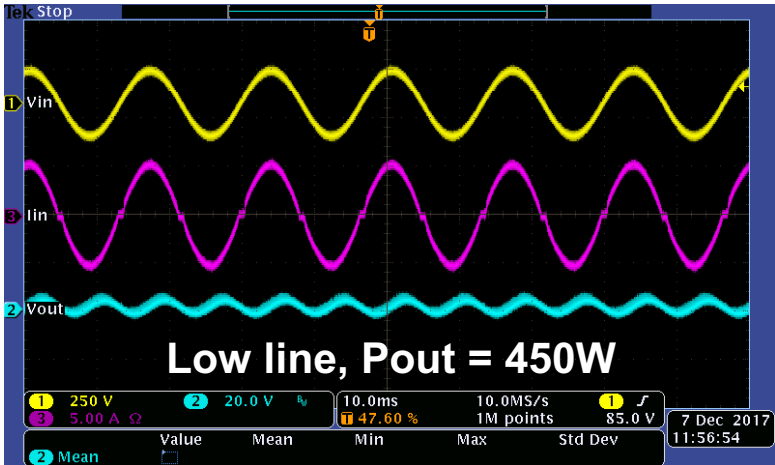
# Input Voltage, Current and Output Ripple



# Phase Shedding – Low Line

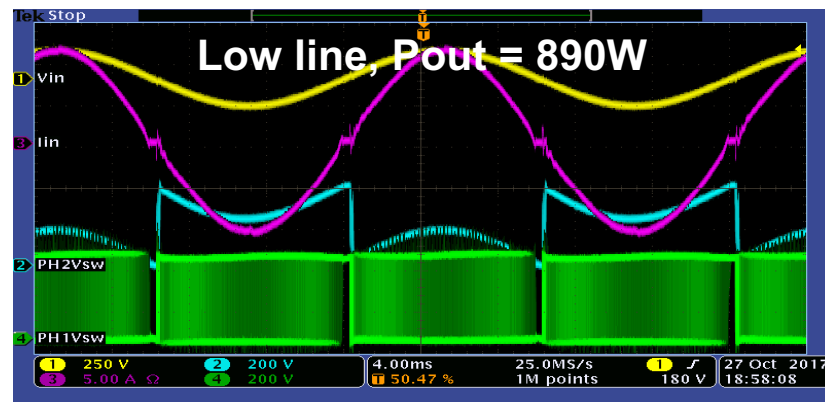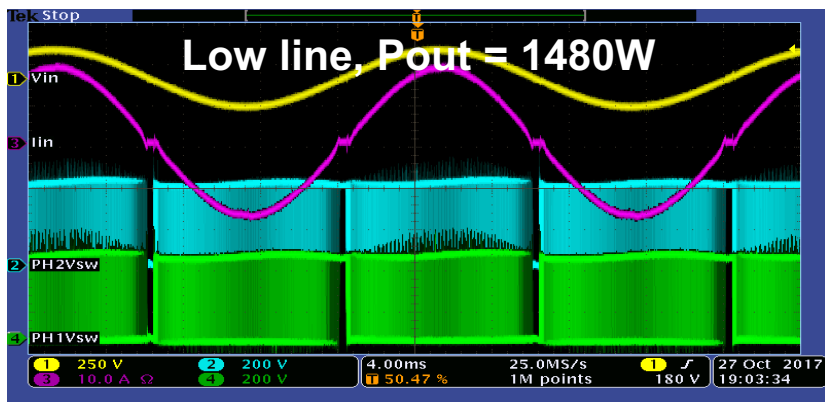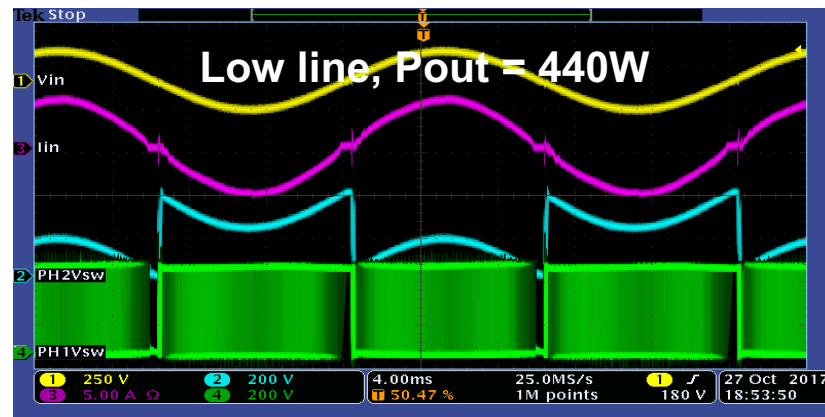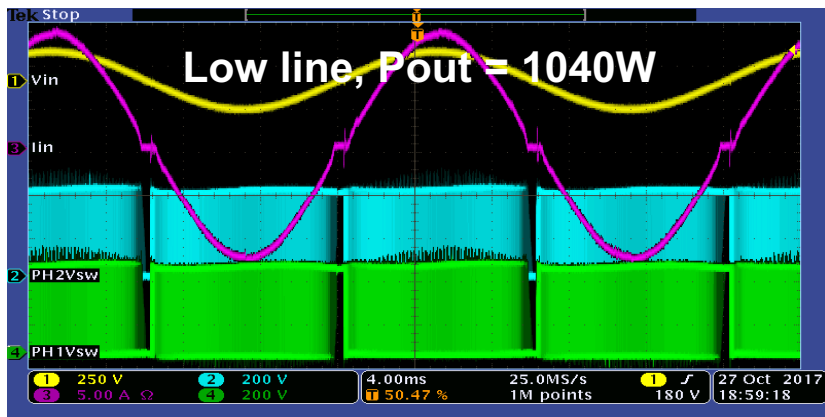

Two Phase Interleaved

Phase-2 OFF

# C2000 Product Roadmap

C2000™  
Delfino™ MCUs

**F28M3x**  
125+125 MHz/250 MIPS  
1.5MB FLASH

**C2834x**  
300 MHz  
516KB RAM

**F2833x**  
150 MHz/150 MIPS  
512KB FLASH

**F2837xS** ⚠️  
200 MHz/400 MIPS  
1MB FLASH

**F2837xD** ⚠️  
200 MHz/800 MIPS  
1MB FLASH

Q100 RTM: Available Now  
Safety Collateral: FSM & Detailed FMEDA Now

Pin-to-Pin & SW Compatibility

C2000™  
Piccolo™ MCUs

**F2807x** ⚠️  
120 MHz/240 MIPS  
512KB FLASH

**F2806x**  
90 MHz/180 MIPS  
256KB FLASH

**F28004x** ⚠️  
100 MHz/200 MIPS  
256KB FLASH

**F2803x**  
60 MHz/120 MIPS  
128KB FLASH

**F2805x**  
60 MHz/120 MIPS  
128KB FLASH

**F2802x**  
60 MHz/60 MIPS  
64KB FLASH

## IP Technology Roadmap

**FPU<sub>64</sub>** **64-bit Floating Point Unit**  
Improved floating point precision for higher performing applications

**Position Manager**  
Configurable decoding of position sensors such as EnDAT, BiSS, SinCos, Resolver, and more.

**Fast Serial Interface**  
High data-rate serial communications interface with error detection technology.

**EtherCAT Connectivity**  
Real-time industrial ethernet communications support for industrial systems

**CAN-FD Connectivity**  
Extending our existing CAN support to the latest "flexible data rate" standard

---

**Processing**

- CLA Real-time Co-processor
- Trigonometric Math Unit
- VCU

**Actuation**

- High Resolution PWMs

**Sensing**

- 16-bit ADC
- Programmable Gain Amplifiers
- Sigma Delta Filters

**Connectivity**

- Ethernet Connectivity

**Technology**

- InstaSPIN Motor Technology

Safety Collateral






# LMG3410R070

Integrated 600-V GaN FET power stage in compact 8x8mm split-pad QFN package


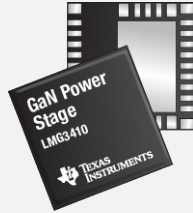
## Features

- 70-m $\Omega$  typical RDS<sub>(ON)</sub>
- 20-ns typical propagation delay
- Integrated over-temperature, over-current protection and UVLO
- High edge-rate tolerance
- Externally-adjustable drive strength for switching
- Performance and EMI control: supports 30 to 100 V/ns
- Targeted towards high-speed operation: up to 1-MHz steady-state operation




## Applications

- Watts to Kilowatts solution for every application:
  - Personal electronics
  - Motor drives and robotics
  - Telecom and network power
  - Grid infrastructure
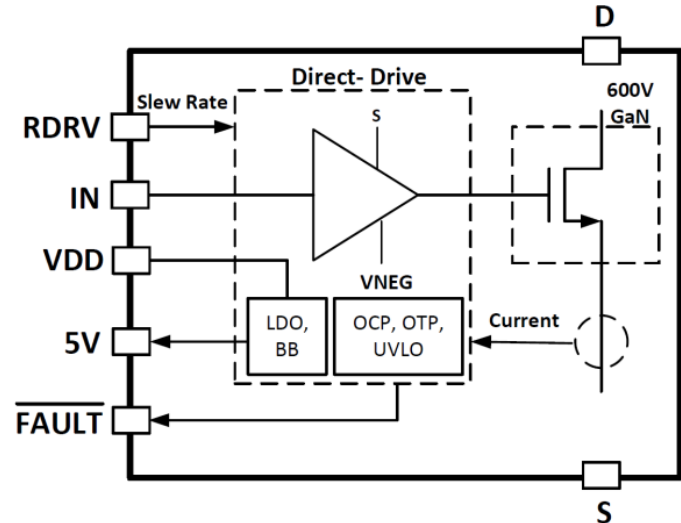
## Benefits

- Integrated direct gate driver with zero common source inductance
- Built-in 5V LDO to power external digital Isolator
- Integrated bias supply – only +12V unregulated supply needed
- High speed over current protection with <100ns response time



# Summary

- TIDA-00961 is a fully programmable two phase interleaved TRM PFC solution
- Innovative ZVS scheme provides good ZVS performance across line and load
- C2000 controller features and TI GaN devices allow a switching frequency range from 200kHz to 1.2MHz
- Compact design – about **80W/in<sup>3</sup>** power density
- Phase shedding for performance improvements under low load operation
- Released TI design - <http://www.ti.com/tool/TIDA-00961>
- E2echina: 基于 GaN 的高效率 1.6kW CrM 图腾柱PFC参考设计 TIDA-00961 FAQ

**Thank you!**

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2018, Texas Instruments Incorporated