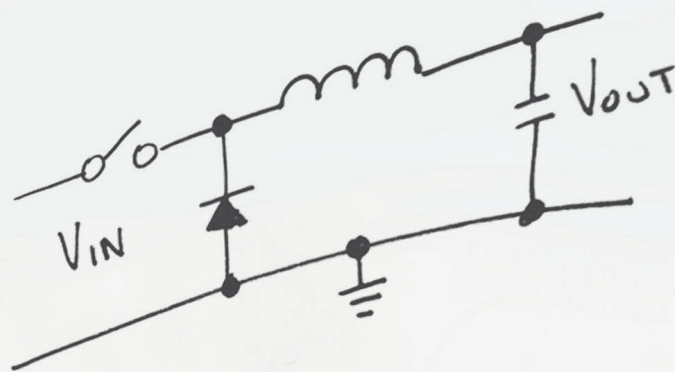



# Power Topologies Quick Reference Guide




Buck  
 $V_{OUT} < V_{IN}$   $V_{OUT} = D \times V_{IN}$






$V_{OUT} = \frac{V_{IN}}{1-D}$

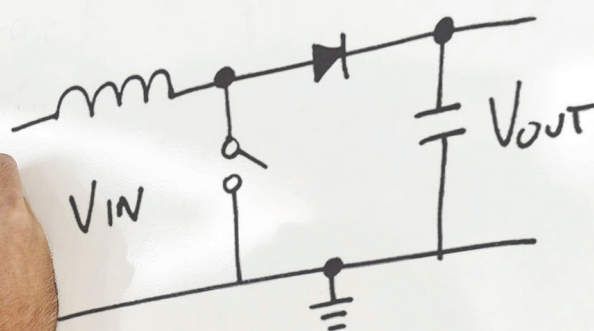

Buck Boost

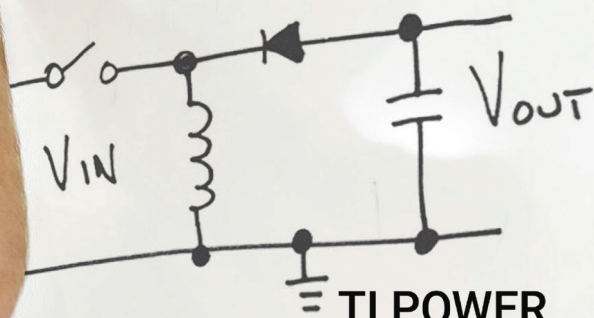

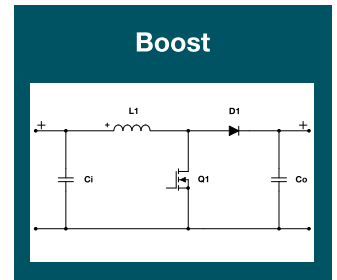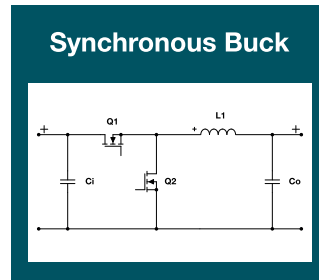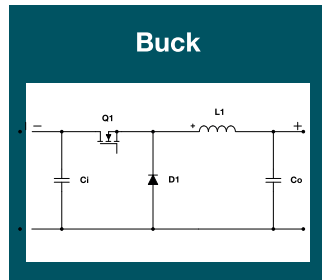

**Duty Cycle**

$$D = \frac{V_{out} + V_f}{V_{in} + V_f}$$

$$D = \frac{V_{out}}{V_{in}}$$

$$D = \frac{V_{out} + V_f - V_{in}}{V_{out} + V_f}$$

**Q1 FET Voltage**

$$V_{Q1} = V_{in} + V_f$$

$$V_{Q1} = V_{in}$$

$$V_{Q1} = V_{out} + V_f$$




**D1 Diode Voltage**

$$V_{D1} = V_{in}$$




$$V_{Q2} = V_{in}$$

$$V_{D1} = V_{out}$$




**PWM**

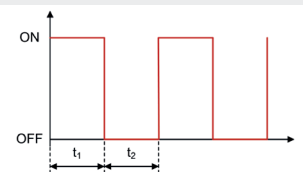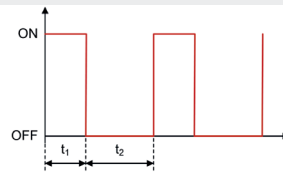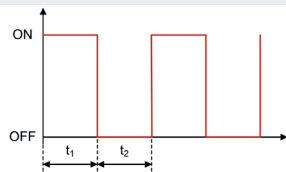




**Q1 FET Voltage**

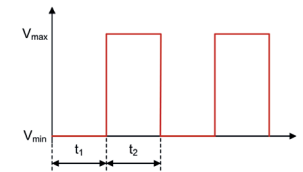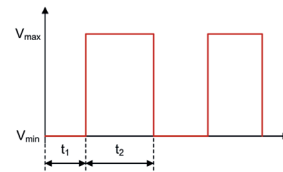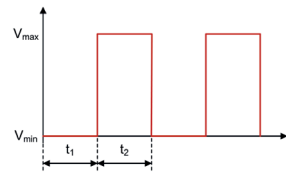




**Q1 FET Current**

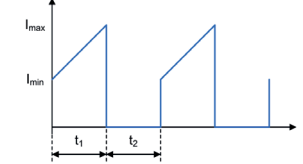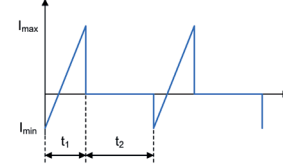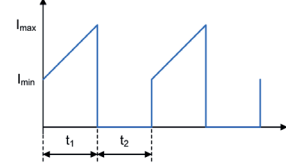




**D1 Diode / Q2 FET Voltage**

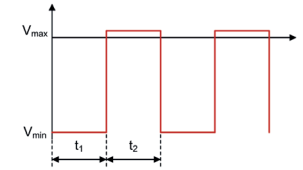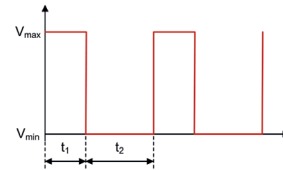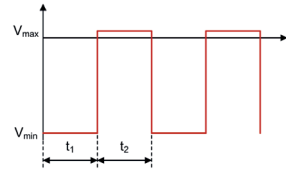


**D1 Diode / Q2 FET Current**

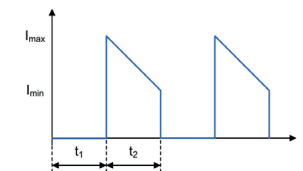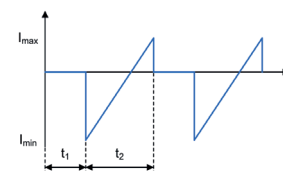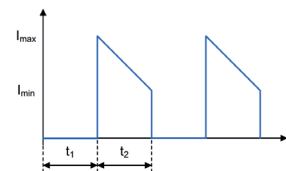

**L1 Inductor Current**

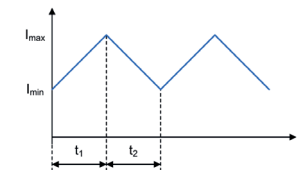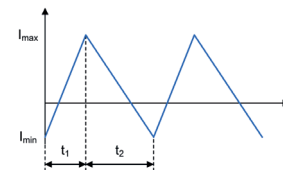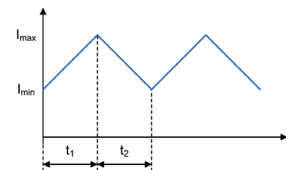

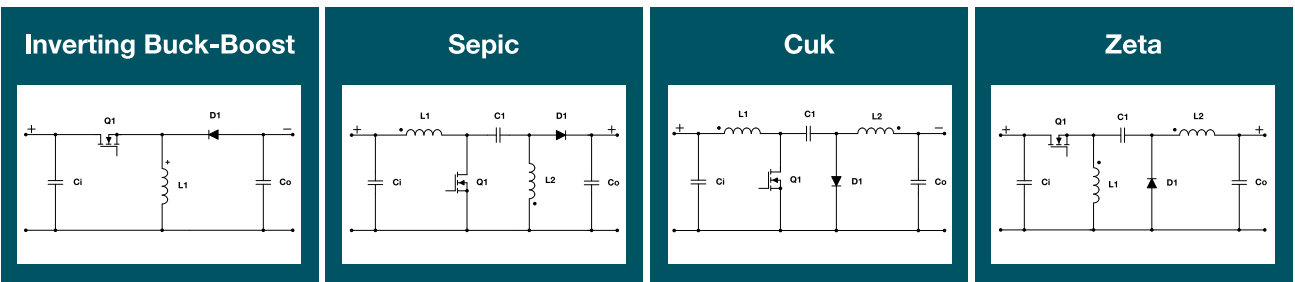

**Duty Cycle**

$$D = \frac{-V_{out} + V_f}{-V_{out} + V_f + V_{in}}$$

$$D = \frac{V_{out} + V_f}{V_{out} + V_f + V_{in}}$$

$$D = \frac{-V_{out} + V_f}{-V_{out} + V_f + V_{in}}$$

$$D = \frac{V_{out} + V_f}{V_{out} + V_f + V_{in}}$$

**Q1 FET Voltage**

$$V_{Q1} = V_{in} + V_f - V_{out}$$

$$V_{Q1} = V_{in} + V_{out} + V_f + \frac{V_{C1,ripple}}{2}$$

$$V_{Q1} = V_{in} - V_{out} + V_f + \frac{V_{C1,ripple}}{2}$$

$$V_{Q1} = V_{in} + V_{out} + V_f + \frac{V_{C1,ripple}}{2}$$

**D1 Diode Voltage**





$$V_{D1} = V_{in} - V_{out}$$

$$V_{D1} = V_{in} + V_{out} + \frac{V_{C1,ripple}}{2}$$





$$V_{D1} = V_{in} - V_{out} + \frac{V_{C1,ripple}}{2}$$

$$V_{D1} = V_{in} + V_{out} + \frac{V_{C1,ripple}}{2}$$





**PWM**

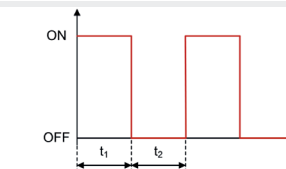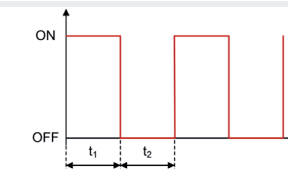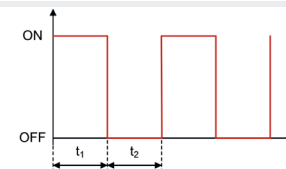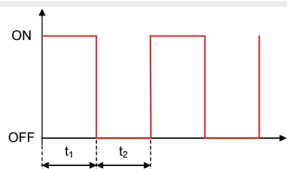





**Q1 FET Voltage**

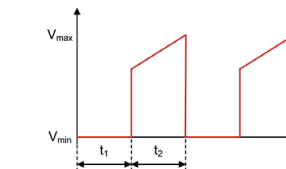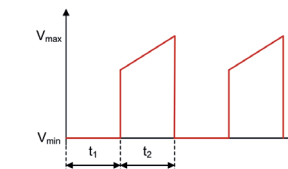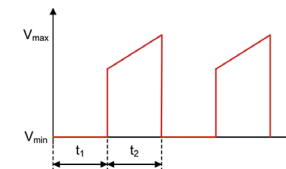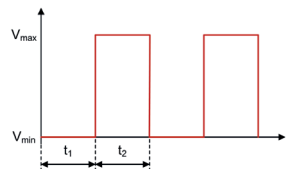





**Q1 FET Current**

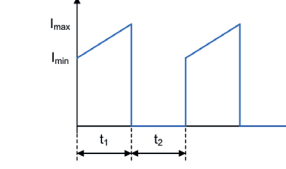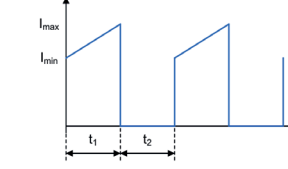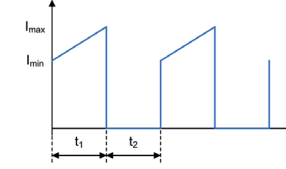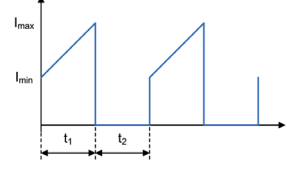





**D1 Diode / Q2 FET Voltage**

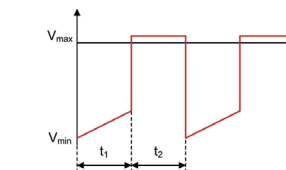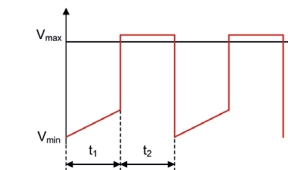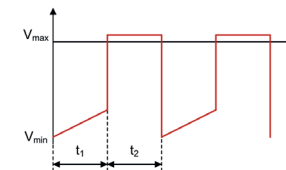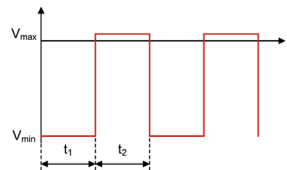




**D1 Diode / Q2 FET Current**

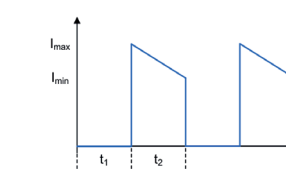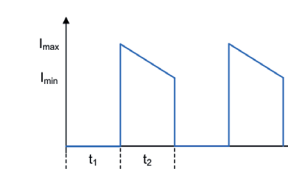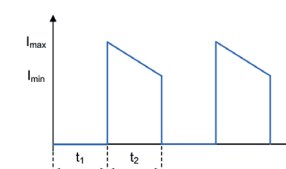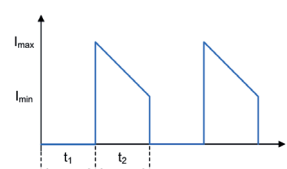


**L1 Inductor Current**

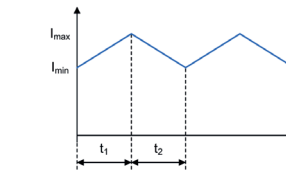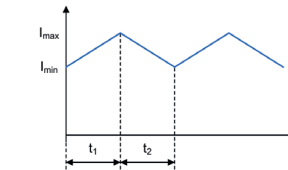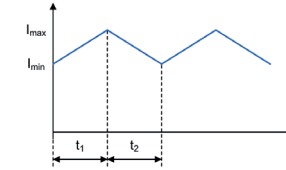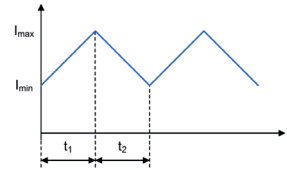


**L2 Inductor Current**

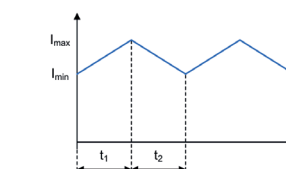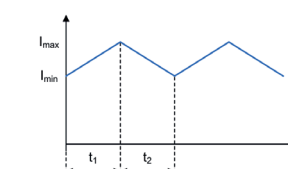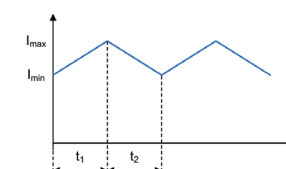


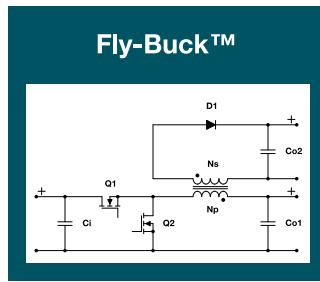

**Fly-Buck™**

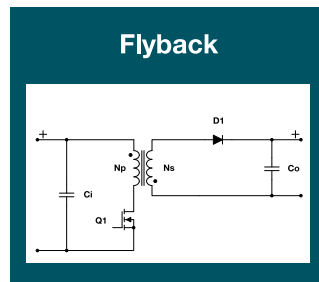

**Flyback**

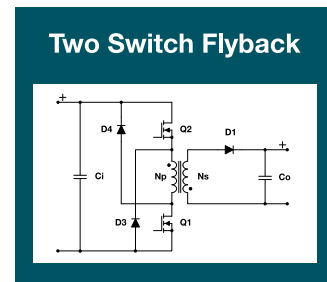

**Two Switch Flyback**

**Duty Cycle**

$$D = \frac{V_{out\_pri}}{V_{in}}$$

$$D = \frac{(V_{out} + V_f) \cdot \frac{N_p}{N_s}}{V_{in} + (V_{out} + V_f) \cdot \frac{N_p}{N_s}}$$

$$D = \frac{(V_{out} + V_f) \cdot \frac{N_p}{N_s}}{V_{in} + (V_{out} + V_f) \cdot \frac{N_p}{N_s}}$$

**Q1 FET Voltage**

$$V_{Q1} = V_{in}$$

$$V_{Q1} = V_{in} + (V_{out} + V_f) \cdot \frac{N_p}{N_s}$$

$$V_{Q1} = \frac{V_{in} + (V_{out} + V_f) \cdot \frac{N_p}{N_s}}{2}$$




**D1 Diode Voltage**

$$V_{D1} = V_{out\_sec} + (V_{in} - V_{out\_pri}) \cdot \frac{N_s}{N_p}$$




$$V_{D1} = V_{out} + V_{in} \cdot \frac{N_s}{N_p}$$

$$V_{D1} = V_{out} + V_{in} \cdot \frac{N_s}{N_p}$$




**PWM**

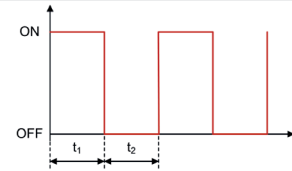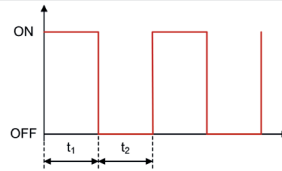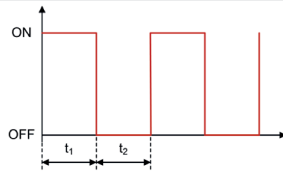




**Q1 FET Voltage**

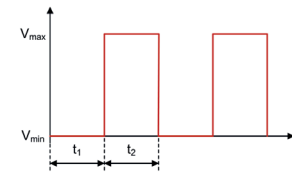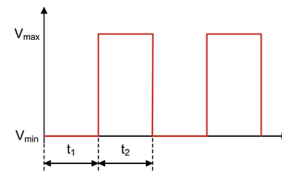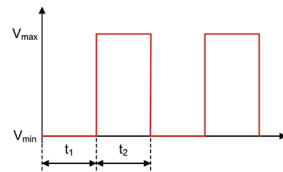




**Q1 FET Current**

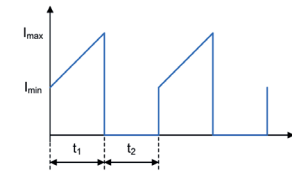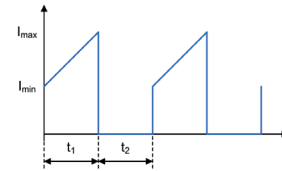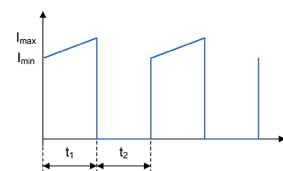




**D1 Diode Voltage**

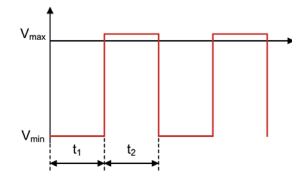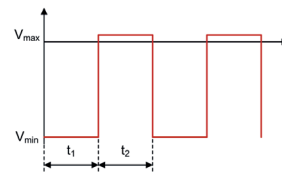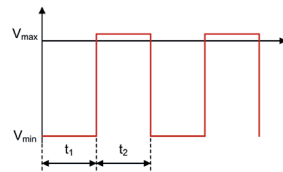




**D1 Diode Current**

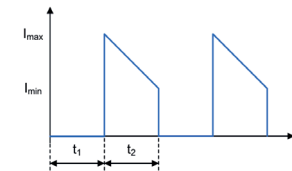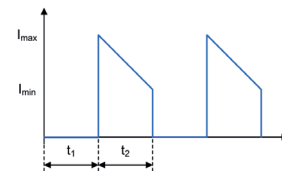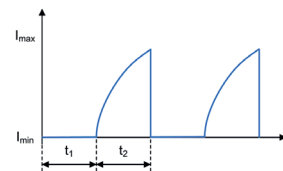


**Np Primary Current**

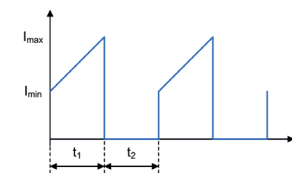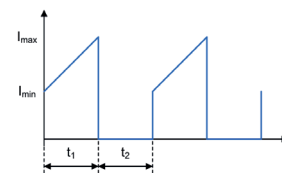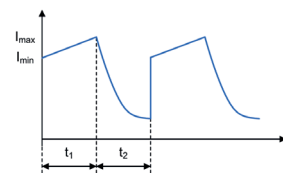


**Ns Secondary Current**

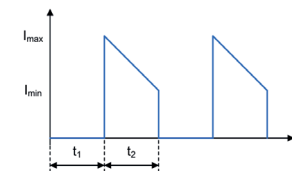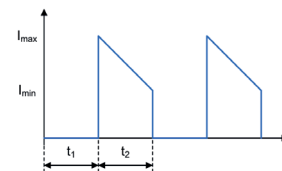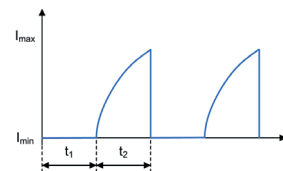


### Active Clamp Forward

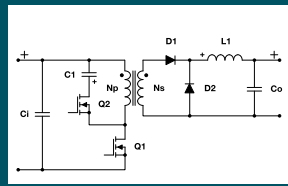

### Single Switch Forward

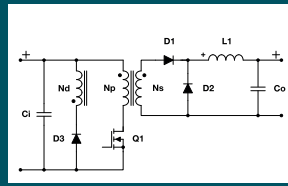

### Two Switch Forward

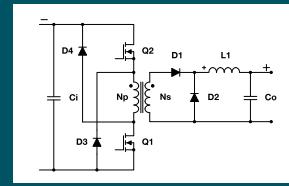

**Duty Cycle**

$$D = \frac{V_{out} + V_f}{V_{in} \cdot \frac{N_s}{N_p}}$$

$$D = \frac{V_{out} + V_f}{V_{in} \cdot \frac{N_s}{N_p}}$$

$$D = \frac{V_{out} + V_f}{V_{in} \cdot \frac{N_s}{N_p}}$$

**Q1 FET Voltage**

$$V_{Q1} = \frac{V_{in}}{(1-D)}$$

$$V_{Q1} = 2 \cdot V_{in} + V_f$$

$$V_{Q1} = V_{in} + V_f$$

**D1 Diode Voltage**

$$V_{D1} = V_{clamp} \cdot \frac{N_s}{N_p} - V_f$$

$$V_{D1} = (V_{in} + V_f) \cdot \frac{N_s}{N_d} - V_f$$

$$V_{D1} = (V_{in} + 2 \cdot V_f) \cdot \frac{N_s}{N_p} - V_f$$




**D2 Diode Voltage**

$$V_{D2} = V_{in} \cdot \frac{N_s}{N_p} - V_f$$




$$V_{D2} = V_{in} \cdot \frac{N_s}{N_p} - V_f$$

$$V_{D2} = V_{in} \cdot \frac{N_s}{N_p} - V_f$$




**PWM**

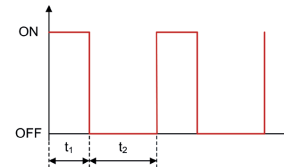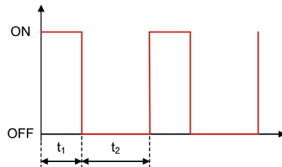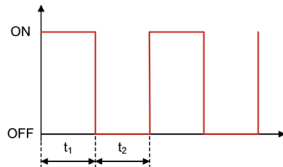




**Q1 FET Voltage**

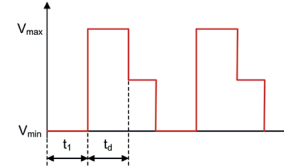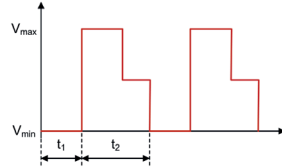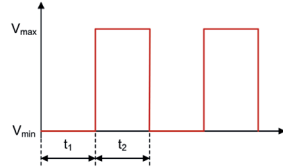




**Q1 FET Current**

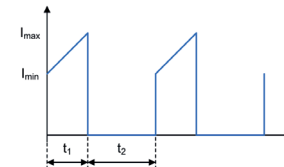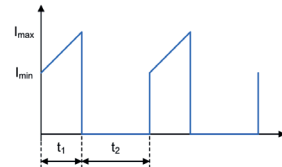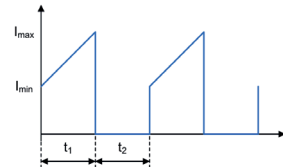




**Np Primary Current**

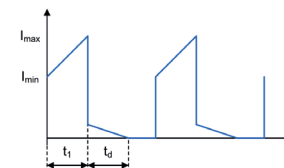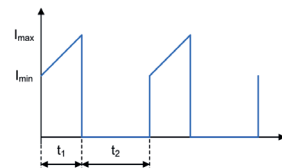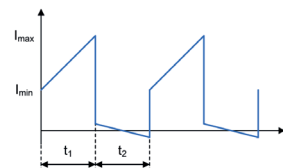


**Ns Secondary Current**

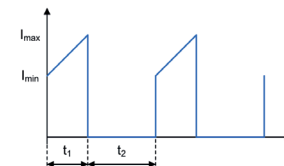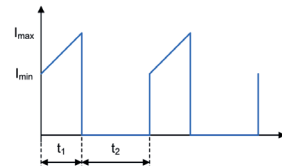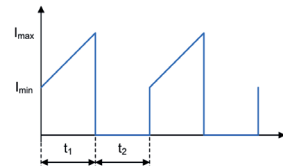

**L1 Inductor Current**

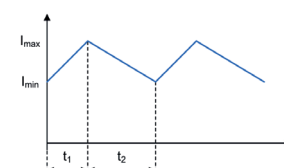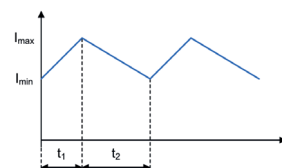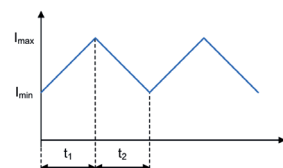

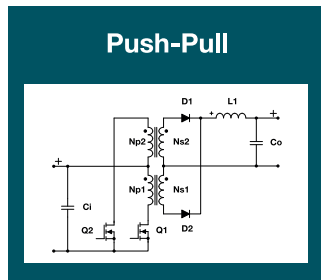

**Duty Cycle**

$$D = \frac{1}{2} \cdot \frac{(V_{out} + V_f)}{V_{in} \cdot \frac{N_s}{N_p}}$$


**Q1 FET Voltage**

$$V_{Q1} = 2 \cdot V_{in}$$


**D1 Diode Voltage**

$$V_{D1} = 2 \cdot V_{in} \cdot \frac{N_s}{N_p} - V_f$$


**PWM**

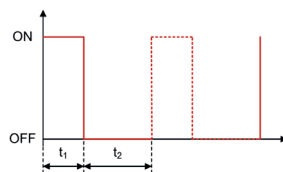


**Q1 FET Voltage**

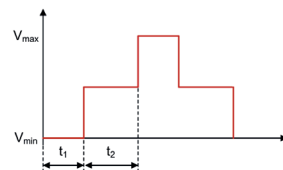


**Q1 FET Current**

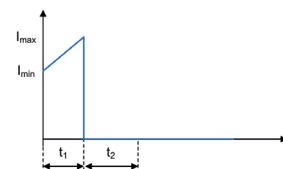



**Np1 Primary Current**

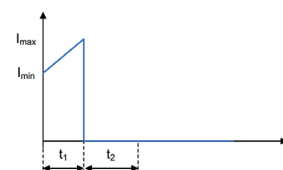

**Ns2 Secondary Current**

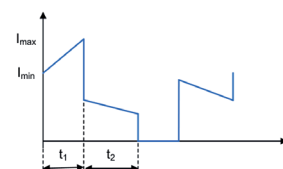

**L1 Inductor Current**

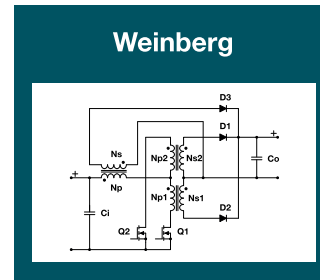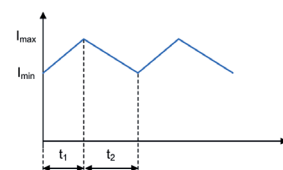

**Duty Cycle**

$$D = \frac{1}{2} \cdot \frac{V_{out} + V_f}{V_{in} \cdot \frac{N_s}{N_p}}$$


**Q1 FET Voltage**

$$V_{Q1} = V_{in} + 2 \cdot \frac{N_p}{N_s} \cdot (V_{out} + V_f)$$


**D1 Diode Voltage**

$$V_{D1} = 2 \cdot (V_{out} + V_f)$$


**PWM**

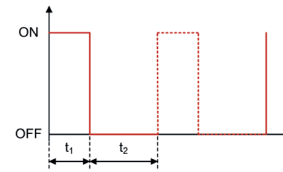


**Q1 FET Voltage**

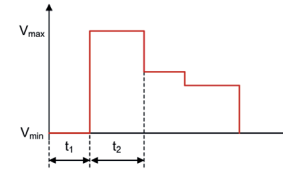


**Q1 FET Current**

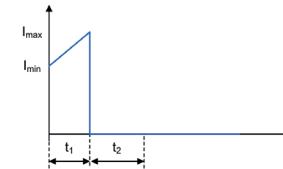


**Np Primary Current**

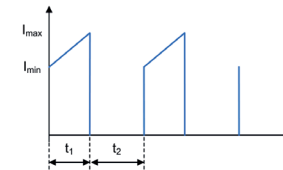


**Ns Secondary Current**



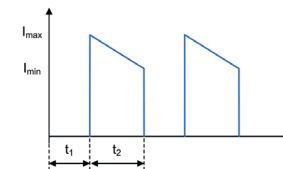


**Np1 Primary Current**

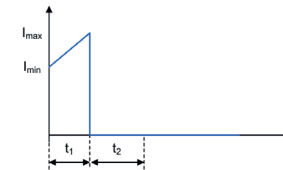

**Ns1 Secondary Current**

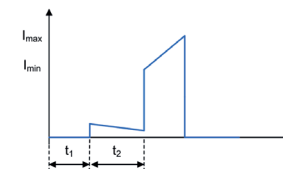

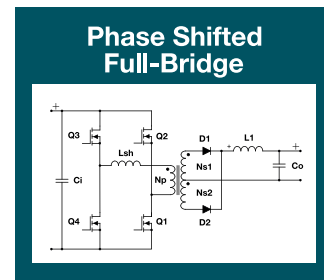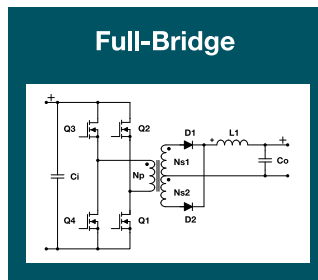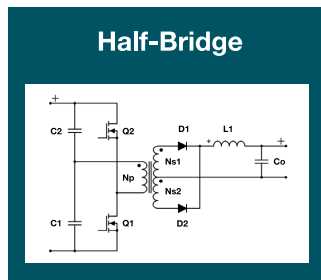

**Duty Cycle**

$$D = \frac{V_{out} + V_f}{V_{in} \cdot \frac{N_s}{N_p}}$$

$$D = \frac{1}{2} \cdot \frac{V_{out} + V_f}{V_{in} \cdot \frac{N_s}{N_p}}$$

$$D = \frac{V_{out} + V_f}{\frac{V_{in} \cdot L_p}{L_p + L_{sh}} \cdot \frac{N_s}{N_p}} \quad (\text{Transformer})$$

**Q1 FET Voltage**

$$V_{Q1} = V_{in}$$

$$V_{Q1} = V_{in}$$

$$V_{Q1} = V_{in}$$




**D1 Diode Voltage**

$$V_{D1} = V_{in} \cdot \frac{N_s}{N_p} - V_f$$




$$V_{D1} = 2 \cdot V_{in} \cdot \frac{N_s}{N_p} - V_f$$

$$V_{D1} = \frac{2 \cdot V_{in} \cdot L_p}{L_p + L_s} \cdot \frac{N_s}{N_p} - V_f$$




**PWM**

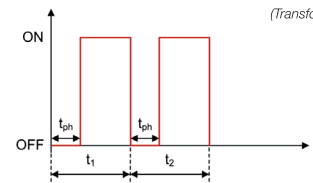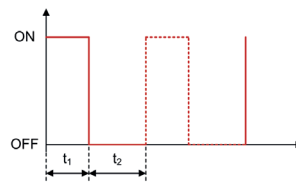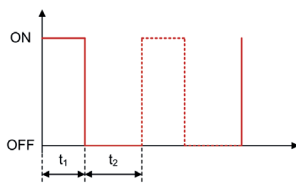




**Q1 FET Voltage**

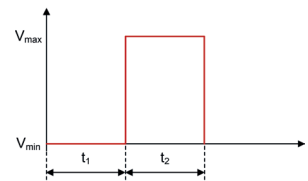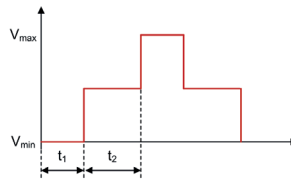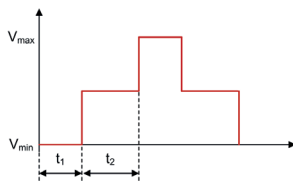




**Q1 FET Current**

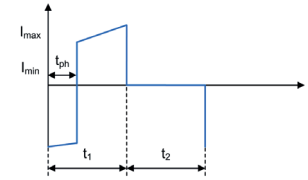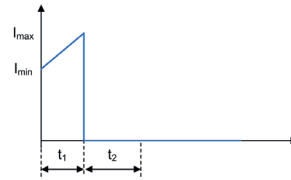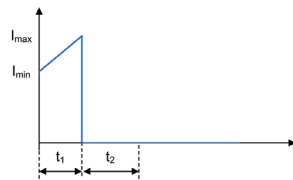




**Np Primary Current**

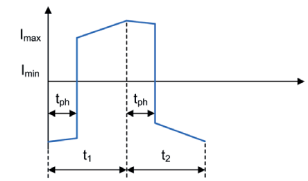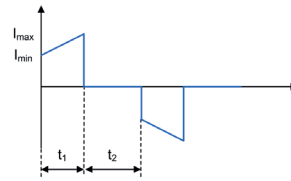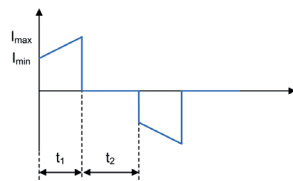

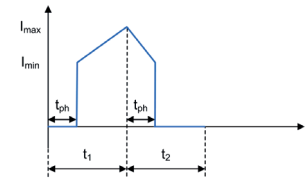
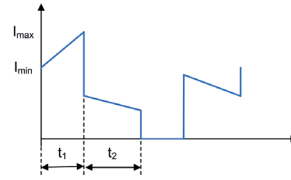
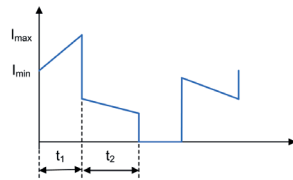
**Ns Secondary Current & D1 Diode Current**





**D1 Diode Voltage**

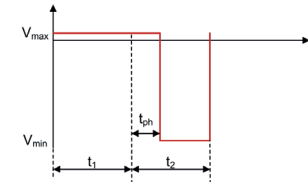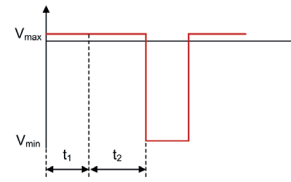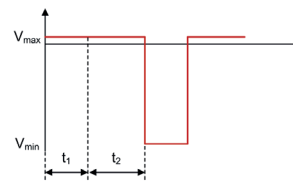

**L1 Inductor Current**

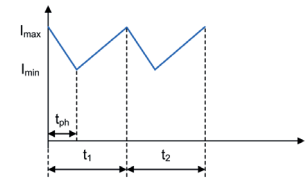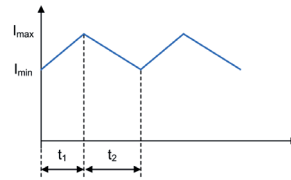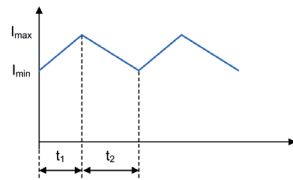

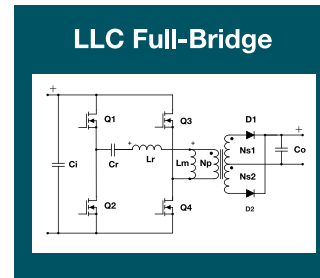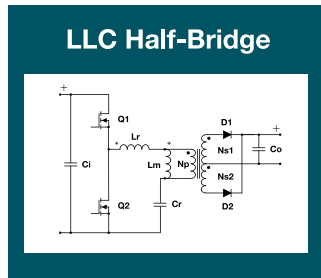

\*Regulation through Frequency Modulation

**Duty Cycle** 50%\*

50%\*



**Q1 FET Voltage**  $V_{Q1} = V_{in}$

$V_{Q1} = V_{in}$



**D1 Diode Voltage**  $V_{D1} = 2 \cdot V_{out} + V_f$

$V_{D1} = 2 \cdot V_{out} + V_f$



**Q1 FET Voltage**

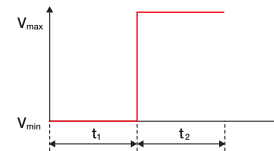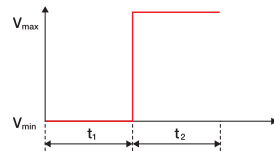



**Q1 FET Current**

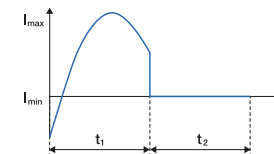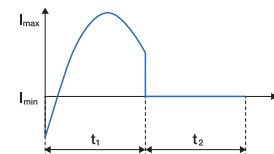



**Lr Resonant Inductor Voltage**

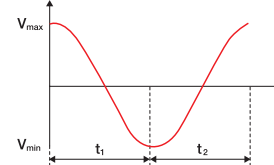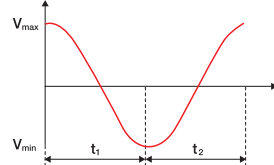



**Lr Resonant Inductor Current**

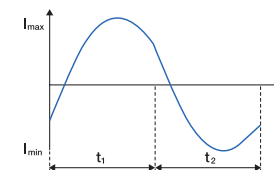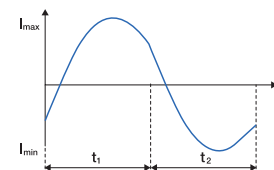



**Np Primary Current**

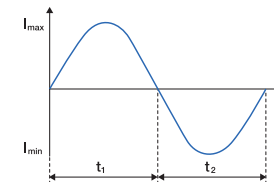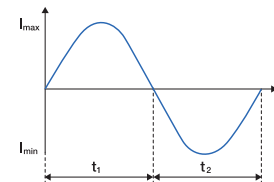

**Ns Secondary & D1 Diode Current**

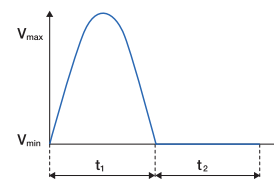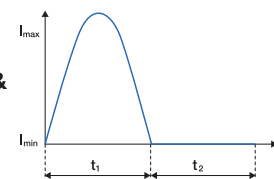

**D1 Diode Voltage**

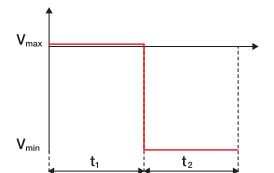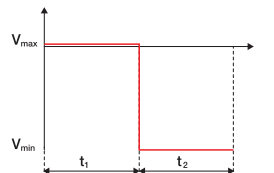



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES “AS IS” AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated