



Joshua Salinas, Jasdeep Mehndiratta

Introduction

This application brief reviews common design questions related to ground-level translators. The goal of this document is to improve overall understanding of how these devices operate in real-world systems.

What are the differences between ground-level translators and digital isolators?

Digital isolators are a galvanic-based solution optimized for high-voltage systems that provide several safety features, such as high CMTI, EMC robustness, and regulatory certifications. While essential for device protection, this level of isolation is generally unnecessary when simply translating digital signals between different ground potentials. Ground-level translators ([TXG product family](#)) were developed to bridge the gap in separating DC and AC ground offsets while providing a reduced solution size and improved switching performance. Ground-level translators and digital isolators serve different purposes depending on system requirements such as isolation, size, speed and leakage performance. [Table 1](#) lists the differences between the two devices.

Table 1. Differences between Ground-Level Translators and Digital Isolators

	Ground-Level Translators	Digital Isolators
GND _A to GND _B Difference	80V	3kV _{rms}
Galvanic Barrier	No	Yes
GND _A to GND _B Leakage (VCC to GND Shorted)	70nA	<1nA
Size (4-Channel)	4mm ²	29.4mm ²
Propagation Delay (3.3V)	5.8ns	18.5ns
Ch-Ch Skew (3.3V)	0.35ns	4.7ns
Data Rate	>250Mbps	100Mbps
Level Shifting Capability	1.71 to 5.5V	1.71 to 1.89V and 2.2 to 5.5V
Operating Temperature	-40C to 125C	-40C to 125C
CMTI	1kV/us	100kV/us
Certification (UL, VDE, Surge)	No	Yes
EMC (EFT, RI, IEC-ESD)	No	Yes

Can a negative PWM signal be generated from a positive PWM signal?

A negative PWM signal can be generated using a ground-level translator if the system includes a negative supply rail. To prevent device damage, the voltage difference between VCC and GND must remain within the recommended operating conditions.

In [Figure 1](#), VCC and GND for both the A-port and B-port fall within allowable limits. As a result, the output toggles between VCC_B and GND_B, which in this case corresponds to 0V and -4V.

 


Figure 1. TXG Outputting Negative PWM Signal

Using the same conditions on TXG8041, the output waveform (pink) toggles between GND and -4V as seen in Figure 2

 


Figure 2. Waveform Capture of Negative PWM Signal

Is DC ground shifting possible when both supplies are connected together?

Ground shifting requires the voltage supplies to be separated and to remain within the recommended operating conditions.

In Figure 3 (a), GNDB shifts by -5V due to parasitic effects while A-side remains within the device limits. However, B-side exceeds its supply-to-ground absolute maximum rating. To avoid this condition, TI recommends that both supplies and their respective grounds remain separated from each other as shown on Figure 3 (b).

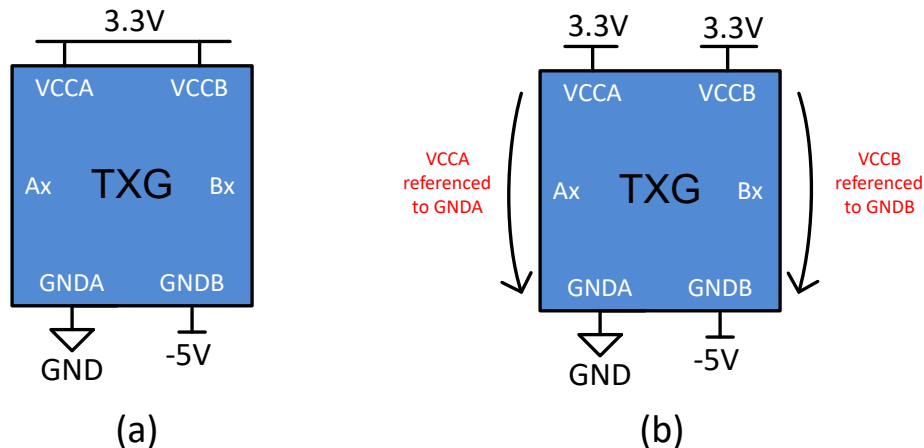


Figure 3. Incorrect Setup (a), Supplies and respective ground remain separated (b)

Can TXG be used as a simple level translator and buffer?

The TXG product family can be used as a standard level translator ($V_{CCA} > V_{CCB}$ or $V_{CCA} < V_{CCB}$) or in a buffer configuration when V_{CCA} equals V_{CCB} .

If ground shifting is not required but high data rate and low output skew are important, GNDA and GNDB can be tied together.

If ground shifting is required, $V_{CCA}/GNDA$ and $V_{CCB}/GNDB$ must remain separated, as shown in [Figure 4](#).

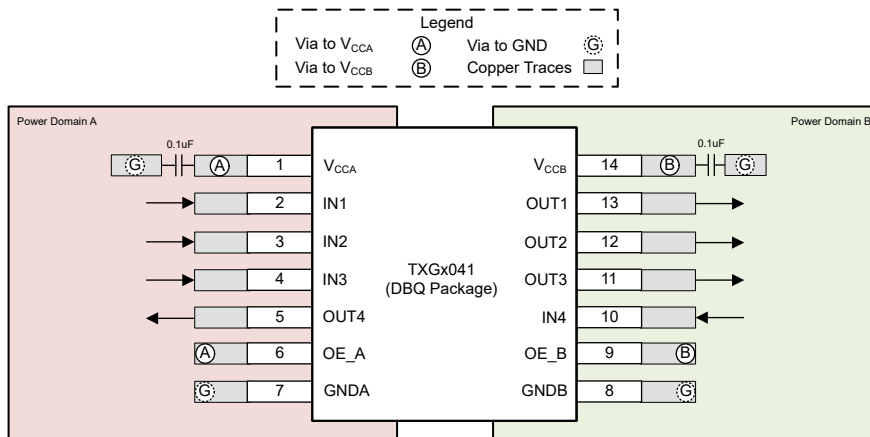


Figure 4. Separated Power Domains on TXG

What is the leakage between two grounds?

The leakage between two grounds is specified in the Electrical Characteristics section in the device datasheet.

[Table 2](#) shows the ground-to-ground leakage values of TXG1041

Table 2. Ground-to-Ground Leakage

Test Condition	VCCA	VCCB	TYP
All channels combined (VCC and GND shorted)	1.71V - 5.5V	1.71V - 5.5V	28nA
All channels combined (VCC both sides are powered on and inputs are all low)	1.71V - 5.5V	1.71V - 5.5V	28nA
All channels combined (VCC both sides are powered on and inputs are all high)	1.71V - 5.5V	1.71V - 5.5V	33nA

How far apart can two systems be when using ground-level translator devices?

Open-Drain Architecture

For I2C applications, the allowable distance between systems is primarily limited by total bus capacitance. The I2C specification limits bus capacitance to 400pF for Standard and Fast Mode, and 500pF for Fast mode Plus. These same limitations apply when using devices such as TXG8122-Q1.

Total bus capacitance is determined by two main factors:

1. **Input Capacitance** - Each SDA and SCL pin contributes ~5pF. While this is minimal for a single device, the total input capacitance increases as additional peripherals are added to the bus.
2. **Cable Capacitance** - A common rule of thumb is approximately 1pF per centimeter of cable length. Under Standard Mode operation, this limits cable lengths to approximately four meters (13 feet).

To support higher capacitive loads, TI recommends TXG8122-Q1 Side 2 (SDA2 and SCL2) with all other I2C peripherals

Push-Pull Architecture

For push-pull architectures such as SPI, the allowable distance depends on the output drive capability of the signal source.

For example, if the microcontroller (signal source) has a high output drive strength, the ground-level translator does not need to be placed next to the source. Instead, the translator may be placed closer to the receiver.

If the microcontroller has limited output capability, TI recommends placing the ground-level translator close to the driver. This allows the translator to use the output drive capability to re-drive the signal over longer distances.

Can unused input pins be left floating on ground-level translators?

For standard logic and level translator devices, it is not recommended to leave input pins floating. Unused inputs should instead be tied to a defined logic level, either VCC or GND, to prevent unintended switching and excess in-rush current.

However, push-pull versions of ground-level translators feature an integrated pull-down resistor on each input pin (typically 5M Ω). As a result, unused input pins do not need to be externally tied to a defined logic level. The internal pull-down resistor forces the input to a logic low-state, which in turn drives a logic low level at the corresponding output.

Conclusion

This document went over the top design questions that have been received to date. If additional clarification is needed or if new questions arise, submit a thread on the [TI E2E™ Community](#) forum. As frequently asked questions are received, this document is updated accordingly.

Trademarks

TI E2E™ is a trademark of Texas Instruments.

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025