

# Application Brief

## Multiphase Operation of LM5171



### Key Concepts of Multiphase Operation

Multiphase operation, often called interleaving, uses multiple parallel converters to share the high load current. Multiphase operation provides benefits like ripple cancellation, reduced component size and easier thermal management.

To achieve multiphase operation, phase interleaving and current sharing must be considered.

See [6.3.18 Multiphase Configurations \(SYNCO, OPT\)](#) in the LM5171-Q1 datasheet to achieve phase interleaving.

Current sharing is achieved by connecting ISET1 and ISET2 (ISETx) pins together as shown in [Figure 1](#). Usually, the ISETx comes from the voltage loop error amplifiers output (ERRHV or ERRLV) of the primary LM5171. As shown in [Figure 1](#), two diodes create an OR connection between ERRHV and ERRLV. The following resistor divider is selected based on the required maximum ISETx voltage. The average inductor current is limited when the maximum ISETx voltage is limited. The resistor divider provides an additional overcurrent limit. The voltage loop error amplifiers (ERRHV or ERRLV) of the secondary LM5171s are not used.

With average current mode control, the average current of each phase tracks the ISETx voltage. The same average current is expected across all phases, regardless of differences in inductance, input voltage or output voltage.

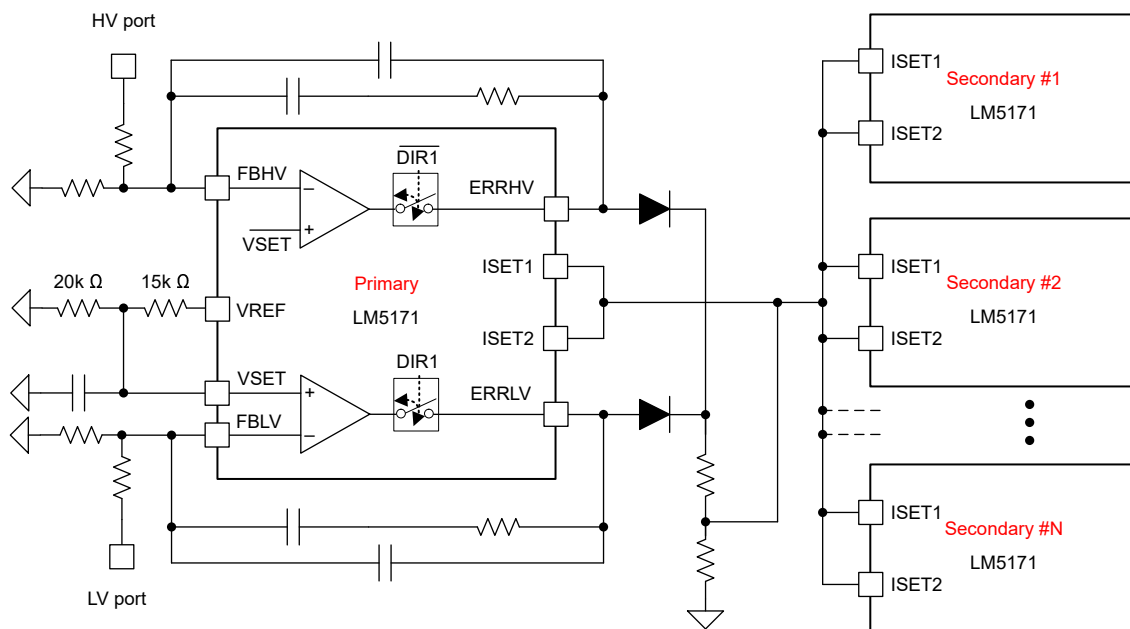


Figure 1. Multiphase Operation of LM5171



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025