

Application Description

Pulse-width modulation (PWM) is a method of providing a square or rectangular wave signal with a varying duty cycle commonly used in applications such as power conversion or controlling LED brightness. Some TI Programmable Logic Devices (TPLD) offer integrated pulse-width modulation generators that allow a designer to easily generate and control a square wave with variable duty cycle. This document provides an overview of the PWM generators included in the [TPLD1202](#), namely what the available settings are and how to configure them in InterConnect Studio (ICS).

PWM Generator Components

When instantiated in ICS, the PWM generator (*pwm0*) appears alongside a counter module (*cnt0*) in Finite-State Machine (FSM) mode, as well as an internal oscillator (*osc0*), as shown in [Figure 1](#).

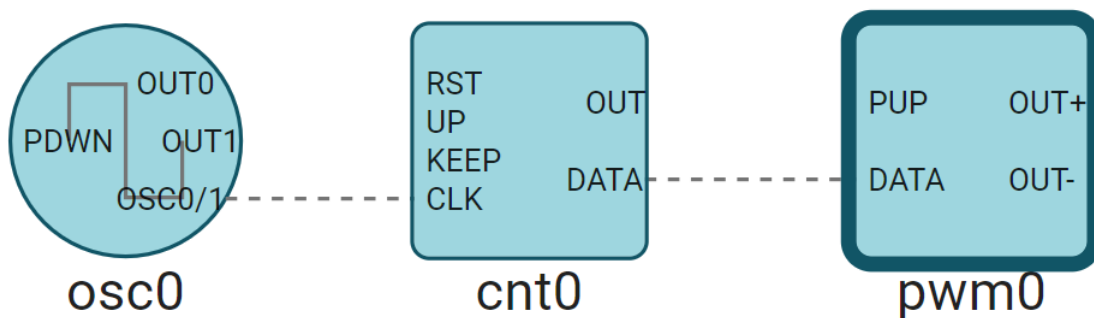


Figure 1. PWM Generator in ICS

The internal oscillator is automatically set to act as the clock to both the counter and PWM generator. The internal oscillator has settings that allow for a change in output frequency. You can divide the frequency by changing the clock source setting on either the counter or PWM generator; the clock source setting also allows for use of an external clock source if desired. Though not explicitly shown, the PWM generator operates off the same clock input as the counter module. Configuration of the oscillator module is described in more detail in [Utilizing Timing Components in TPLD](#).

Counter FSM Functionality

By default, the counter FSM works by counting down one value from the *Control Data* value for every clock pulse received until the internal count value is zero, at which point FSM provides an output pulse for one clock cycle, then resets to the *Control Data* value. [Figure 2](#) shows an example of TPLD1202 counter behavior where the *Control Data* was set to 3 as seen in the counter settings shown in [Figure 3](#); note that the counter (brown) pulses high every three clock cycles (white).

COUNTER ⓘ	
Name	cnt0
Label	
Clock Source	External Clock ▼
Control Data	3
RST Sync Bypass	2-DFF sync ▼
Initial Value	Bypass initial ▼
Output Polarity	Non-inverted ▼
Reset Mode	High Level Reset ▼
Enable FSM Mode	<input checked="" type="checkbox"/>
UP Sync Bypass	2-DFF sync ▼
KEEP Sync Bypass	Bypass 2-DFF ▼
Device MacroCell Allocated	Any(CNT_FSM_0) ▼

Figure 2. Counter Module Settings

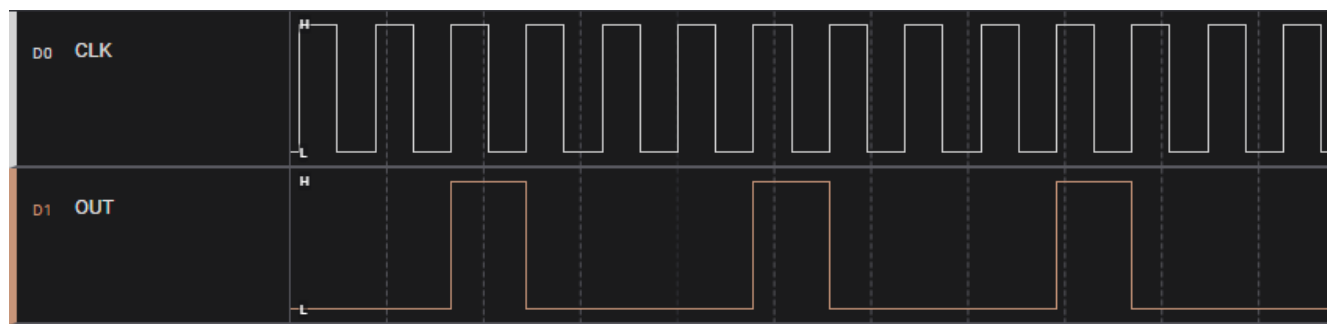


Figure 3. Counter Simulation With Control Data of 3

The *DATA* connection shown in Figure 1 is the counter providing the current internal count value to the PWM generator. This value determines the duty cycle of the PWM generator outputs. The duty cycle of the PWM signal can be calculated by: $\text{Duty cycle (\%)} = (\text{DATA} / 256) \times 100$, with a minimum duty cycle of 0% (0/256) and a maximum of 99.61% (255/256). Each change in count value provides an additive 0.39% increase or decrease in duty cycle.

The counter input signals *UP*, and *KEEP* as seen in Figure 1 exist when the *Enable FSM Mode* setting, visible in Figure 2, is selected for a given counter (counters providing *DATA* to a PWM are locked in FSM mode). These signals can be used to control the internal count value/*DATA* provided by the counter and thus dynamically change the duty cycle of the PWM generator. A logic high on *UP* causes the counter to count up to 255 before emitting a pulse, instead of down to 0. A logic high on *KEEP* maintains the current internal count value, regardless of any incoming clock pulses. A logic high on the *RST* input resets the current internal count value to the initial value set by the *Control Data* setting.

Figure 4 shows a test of the TPLD1202s counter with the various FSM signals employed. From top to bottom, white is the clock, brown is the counter output, red is the *RST* input, orange is the *UP* input, and green is the *KEEP* input.

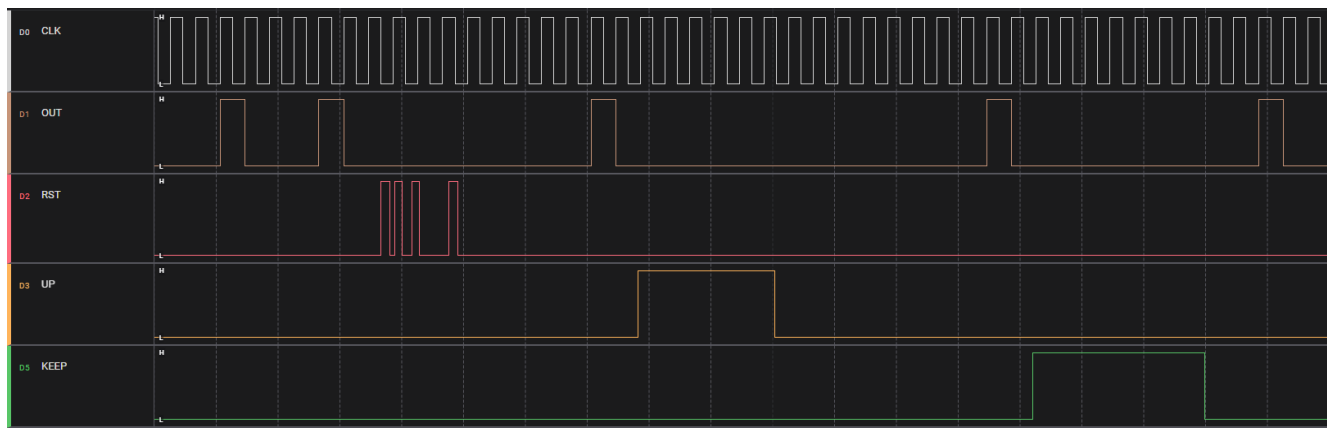


Figure 4. Counter FSM Simulation With Control Data of 3

PWM Generator Configuration

In addition to the *CLK* and *DATA* connections, the PWM generator has a *PUP* (power-up) input that must be a logic high for the generator to provide an output signal, and two outputs *OUT+* and *OUT-* that are in-phase with each other by default, as seen in [Figure 1](#). The PWM configuration options are shown in [Figure 5](#).

PULSE WIDTH MODULATOR ⓘ

Name	<input type="text" value="pwm0"/>
Label	<input type="text"/>
Clock Select	<input type="text" value="OSC0/1"/> ▼
Output - Inversion	<input type="checkbox"/>
Output + Inversion	<input type="checkbox"/>
Deadband Time	<input type="text" value="No Deadband"/> ▼
Source Select	<input type="text" value="CNTFSM0"/> ▼
Device MacroCell Allocated	<input type="text" value="Any(PWM_0)"/> ▼

Figure 5. PWM Configuration Options

Both *OUT+* and *OUT-* can be inverted by checking the appropriate *Output Inversion* box. A deadband of 0, 1, 2, or 5 clocks can be selected for *OUT-*; this setting reduces potential for shoot-through current when the PWM is used on circuits such as an H-bridge. A simulation waveform of the PWM generator with *DATA* of 128 (50% duty cycle), inverted *OUT-* output, and 5-clock deadband is shown in [Figure 6](#). *OUT-* is blue and *OUT+* is yellow. One full output period takes 255 clock cycles and is determined by the PWMs input clock source.

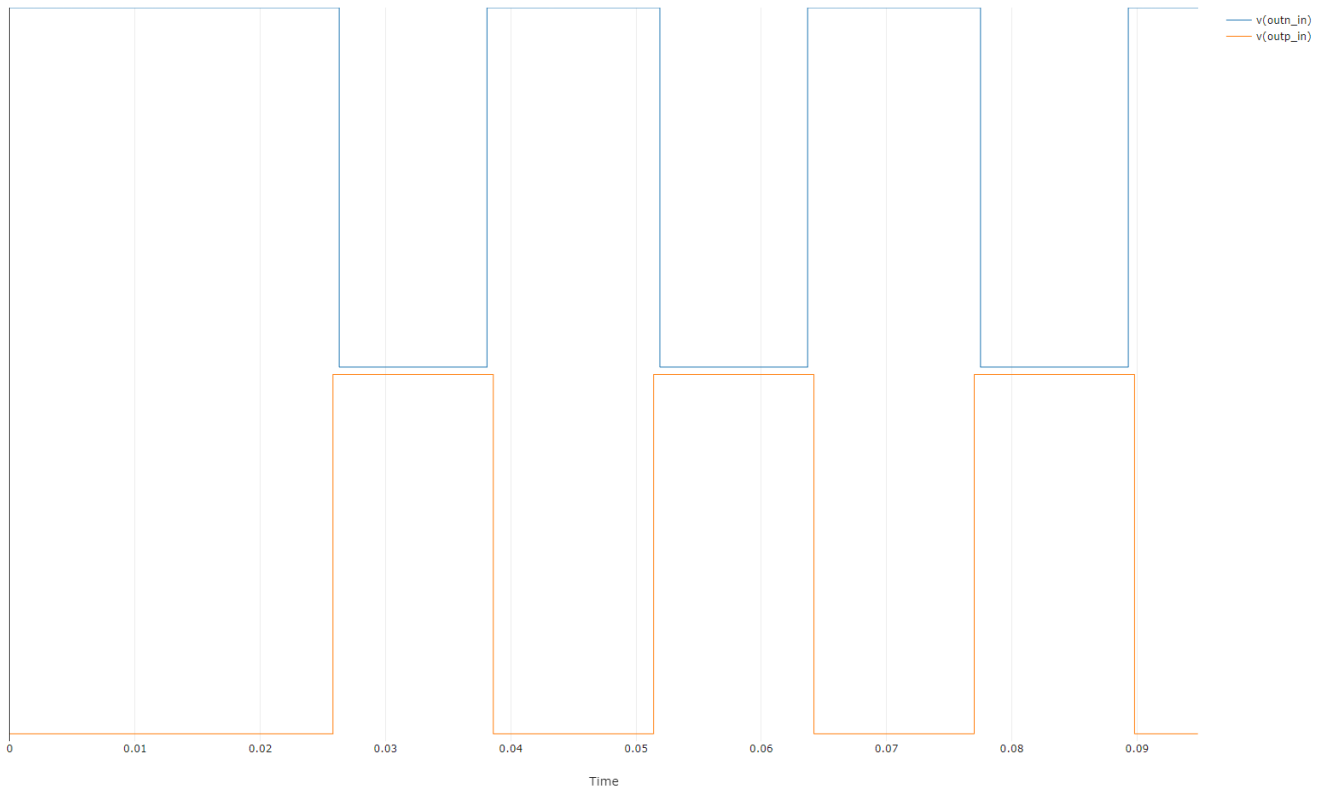


Figure 6. PWM Simulation

Example Circuit

The circuit in Figure 7 is configured to dynamically vary the PWM generator's duty cycle in an example overvoltage and undervoltage detection and control application. The PWM is set to run at 50% duty cycle by default (*cnt0* is given a control data of 128), with *KEEP* set to be a logic high. The multi-channel analog comparator (*mcacmp0*) is used to detect voltages below 800mV and above 1.216V. When a voltage above 1.216V is detected, *KEEP* is set low and the counter is allowed to count down to decrease the duty cycle until the voltage falls below the 1.216V threshold. When a voltage below 800mV is detected, the *KEEP* is set to low and *UP* is set high so that the counter increases the duty cycle. Simulation of this circuit is shown in Figure 8. The PWM output is shown in blue, and the input voltage is shown in yellow.

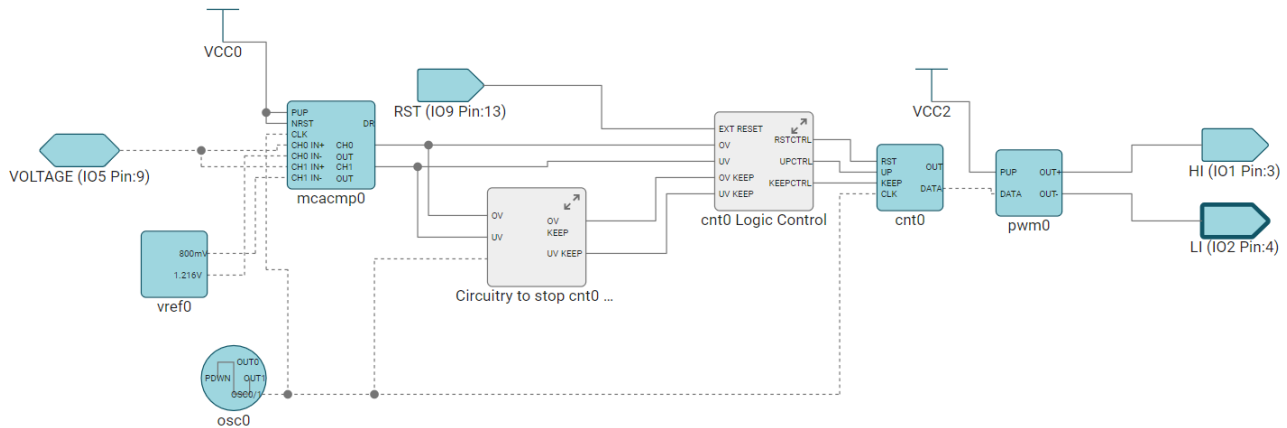


Figure 7. Overvoltage and Undervoltage PWM Circuit

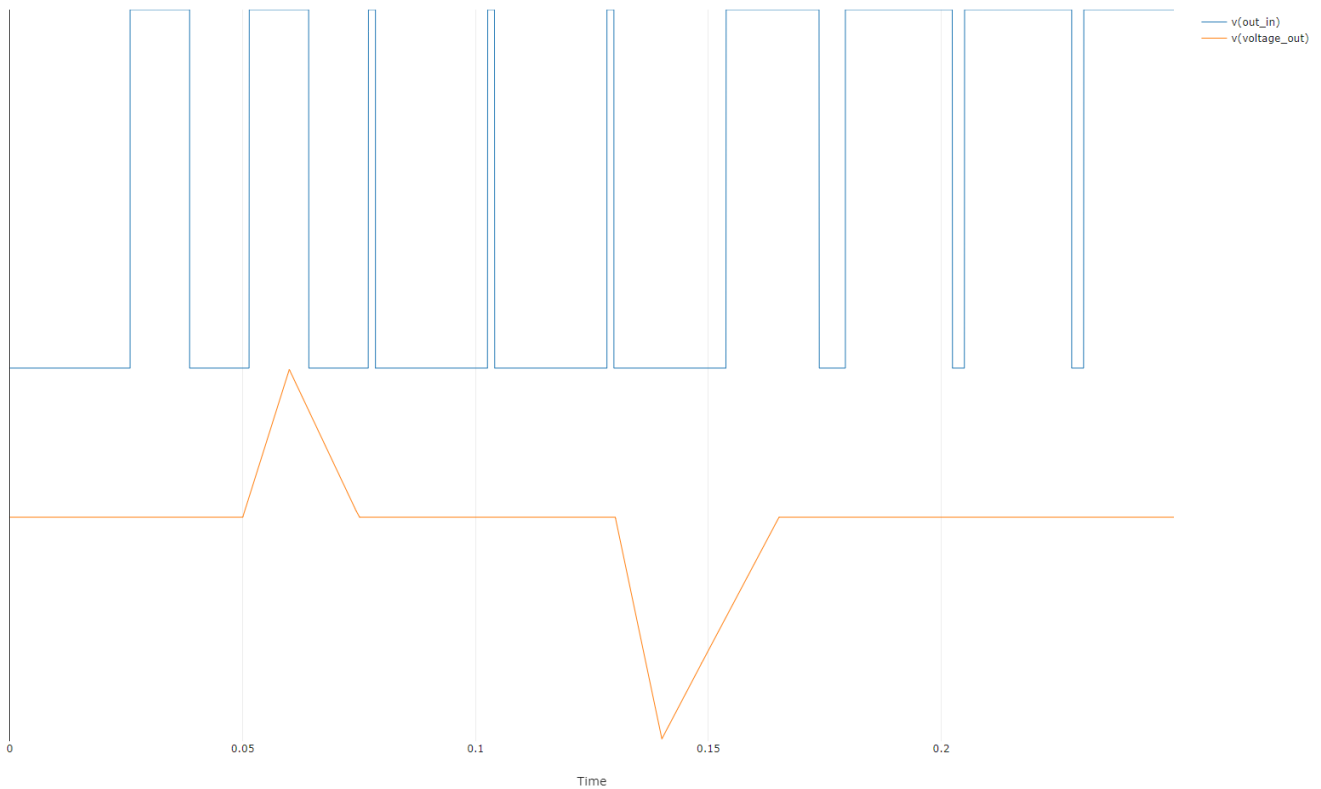


Figure 8. PWM Circuit Simulation

As previously described in [Counter FSM Functionality](#), the counter module counts down to 0 or up to 255 and then resets the count value. Thus, additional circuitry is required to pause *cnt0* near the values of 0 or 255 to maintain the minimum and maximum duty cycle and prevent the counter from looping. This circuitry is shown in [Figure 9](#); *cntOV* is configured with a control data of 125 (three lower than *cnt0*) and *cntUV* is configured with a control data of 131 (three higher than *cnt0*). Upon entering an overvoltage state, both *cnt0* and *cntOV* are reset and begin counting down; *cntOV* counts to 0 before *cnt0* due to having a lower control data, and the corresponding output pulse is latched by *dff0* and used to set *KEEP* high and hold the current count value of *cnt0*. For an undervoltage state, *cntUV* operates the same way, counting up instead of down.

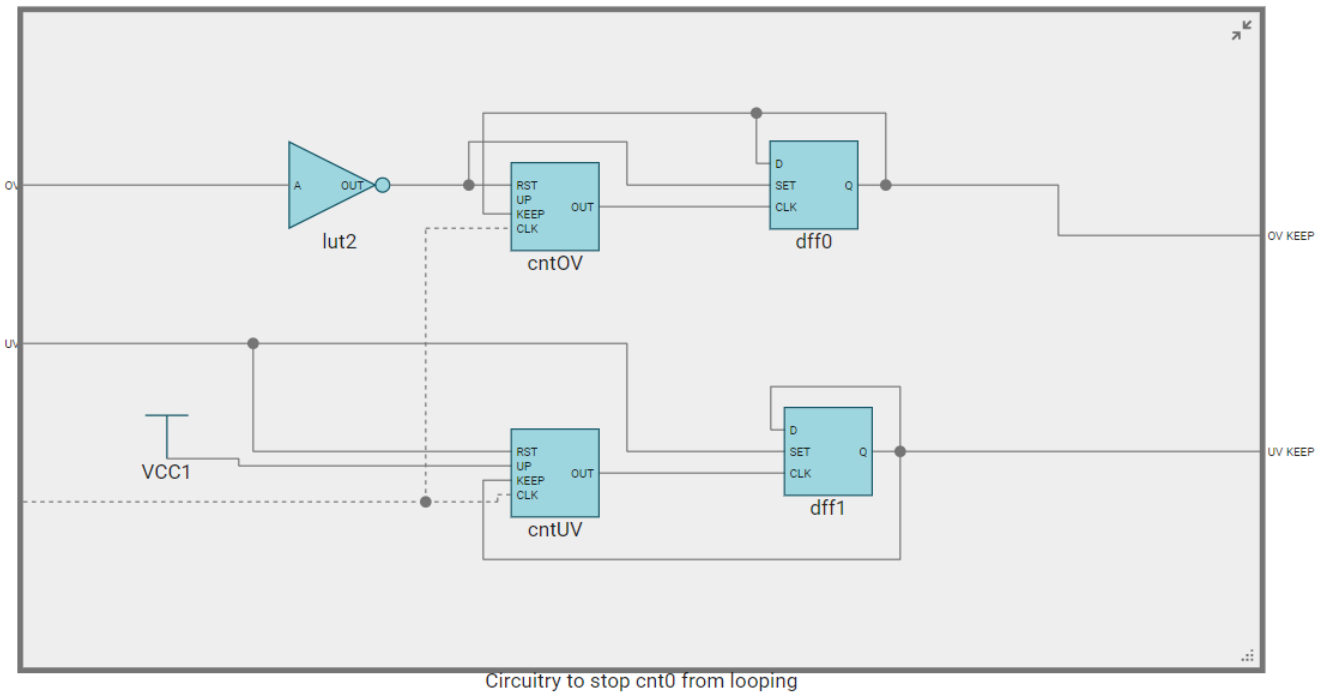


Figure 9. PWM Looping Prevention Circuit

To maintain that *cntOV* and *cntUV* finish counting before *cnt0*, *cnt0* must also be reset upon a transition to an overvoltage or undervoltage state. This means the duty cycle resets to 50% upon a transition to either state. The logic for controlling the reset and FSM signals into *cnt0* is shown in Figure 10.


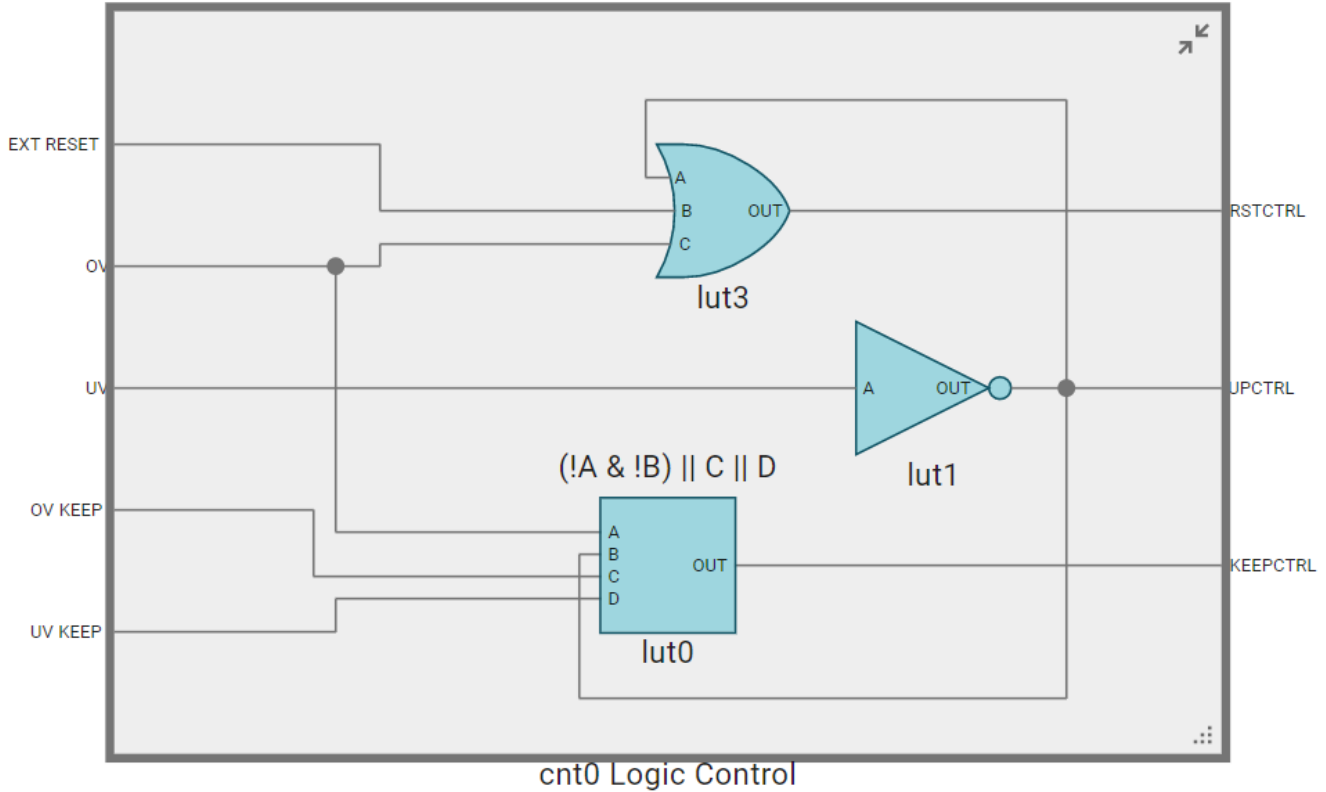


Figure 10. PWM Counter FSM Control Circuit

Additional Considerations

Figure 8 shows that the PWM output reaches the maximum and minimum duty cycle values quickly. More gradual changes in duty cycle can be achieved by circuitry that limits the amount of time the *KEEP* pin of the counter FSM is asserted low. For example, a one-shot module connected and configured as shown in Figure 11 drives the *KEEP* pin and provides a much more gradual transition in duty cycle, as shown in Figure 12.

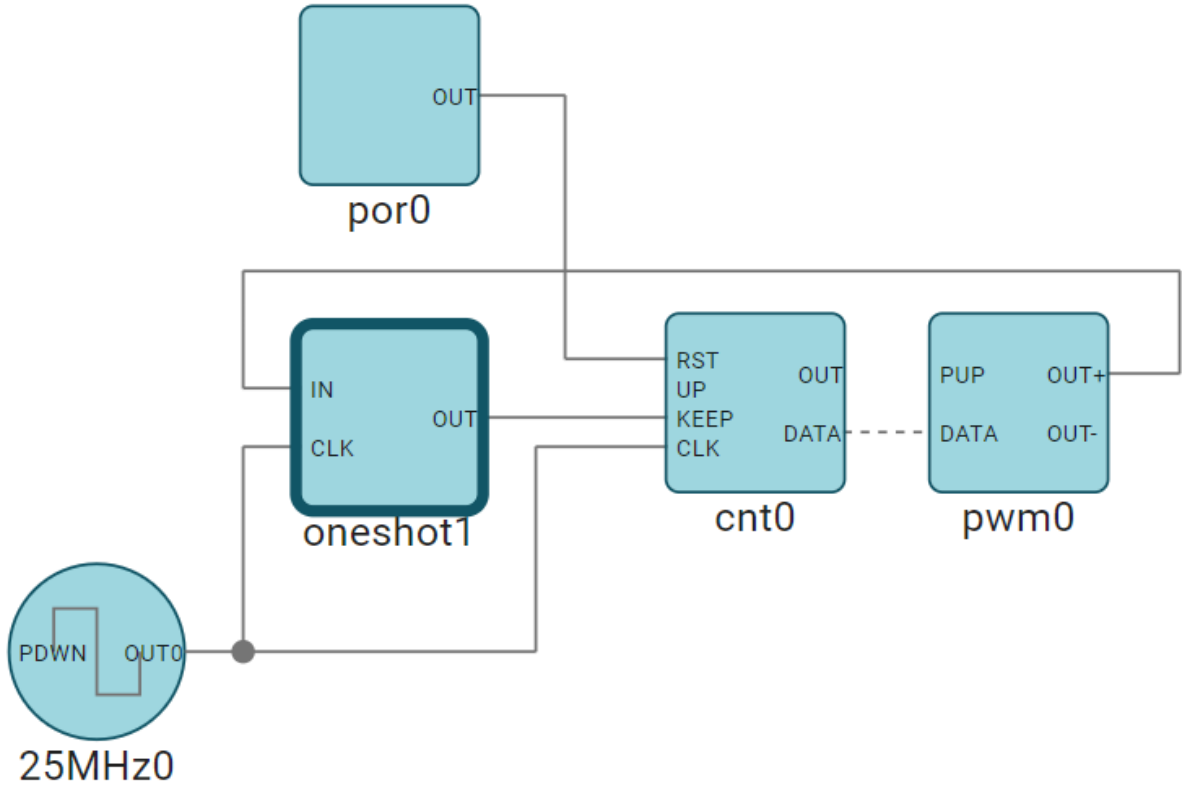

ONE-SHOT ©	
Name	oneshot1
Label	
Clock Source	External Clock
Control Data	255
RST Sync Bypass	Bypass 2-DFF
Initial Value	Bypass initial
Output Polarity	Non-inverted
Edge Trigger	Both falling and rising edges
Device MacroCell Allocated	Any(CNT7_FSM1)

Figure 11. PWM with One Shot

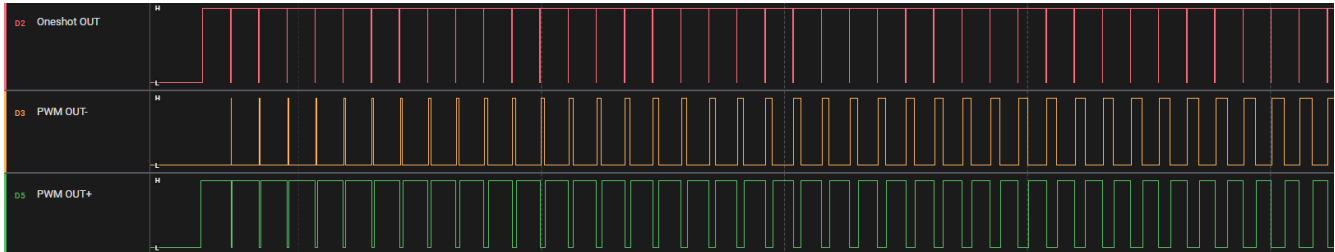


Figure 12. PWM with One Shot Output

The PWM duty cycle can also be controlled using the I2C or SPI Receiver and writing the desired control data to the appropriate counter FSM's data register.

Conclusions

The PWM module allows for TPLD to generate square waves with varying duty cycles. By incorporating several different logic functions and analog sensors, TPLD provides an integrated design for real-time PWM generation and control.

[Learn more about TI's portfolio of programmable logic devices](#)

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025