



-48-V ATCA Hot Swap Reference Design Using the TPS2350

Reference Design

–48-V ATCA Hot Swap Reference Design Using the TPS2350

Jim Bird

Power Supply Control Products

ABSTRACT

This reference design uses the TPS2350 to control dual –48-V power supplies for a 200-W board in compliance with ATCA requirements.

Contents

1. Introduction	2
2. ATCA Specific Circuitry	3

1 Introduction

Fets are used to OR the –48-V feeds instead of the typical diodes. This significantly reduces the diode VI losses, especially as currents increase. Although similar to the standard TPS2350 design, a number of components have been added to satisfy ATCA energy storage requirements and to protect the pass fet. These changes accommodate the large bulk capacitors needed by ATCA and improve board survivability.

Nominal values for UV/OV and over current thresholds, as well as fault and ramp timing, are presented. If the designer needs to change any of these parameters the procedures are thoroughly covered in the TPS2350 datasheet.

2 ATCA Specific Circuitry

R3 and R14 perform a power limiting function to protect FET Q3 from operating outside the specified SOA of Q3. As VIN increase R3 bleeds more current into the SNS pin of the TPS2350 which biases the overcurrent (OC) comparator in the TPS2350. As the bias current increases, less load current is required to trip the OC comparator, effectively lowering the programmed I_{MAX}.

RT1 and Q10 control the current into C5 during charging. This prevents the TPS2350 from declaring an OC fault condition while C5 is charging at startup. If energy stored in C5 is needed to provide power to the load D7 allows current to flow without being limited by RT1. Although RT1 dissipates 0 watts during quiescent operation it could momentarily see 72 V during the charge cycle and temporarily dissipate over 10 W. For this reason a positive temperature coefficient resistor is used for RT1.

Q10 and U2 prevent C5 from charging until the TPS2350 has asserted power good (PG). This allows sequential charging of onboard bulk capacitors. The 100- μ F – 200- μ F capacitors typically required at power converter inputs are allowed to charge first. Once they have completed charging and the TPS2350 declares power good Q4 is turned on by PG and C5 is allowed to charge at a rate determined by RT1.

Insertion detection (ID) pins provided by ATCA are named ENABLE_A and ENABLE_B. These pins are tied to RTN_A and RTN_B, respectively, on the backplane. ID is not required by ATCA but some designs may use it. Since ATCA requires that boards remain operational even if one power feed goes open there can be a conflict with certain ID implementations. If a single return line goes open the associated ENABLE pin could sense a nonexistent module extraction which causes the board to shut down. The design presented is not susceptible to such false failures and will continue to operate despite the loss of a single power feed. As ATCA designs mature the ID function most likely integrates into the intelligent platform management interface (IPMI) controller, thus allowing more flexibility in response to ID events. If ID is not required then Q1, Q2, R6–R9, R12, R13, D5, and D6 may all be removed from the circuit presented.

Table 1 shows alternate component values for lower power boards.

Table 1. Values For 50-W / 80-W / 130-W / 180-W Board

Power Level (W)	R17 m Ω	C5 μ F
50	16	1400
80	10	2240
130	6	3640
180	4.5	5040

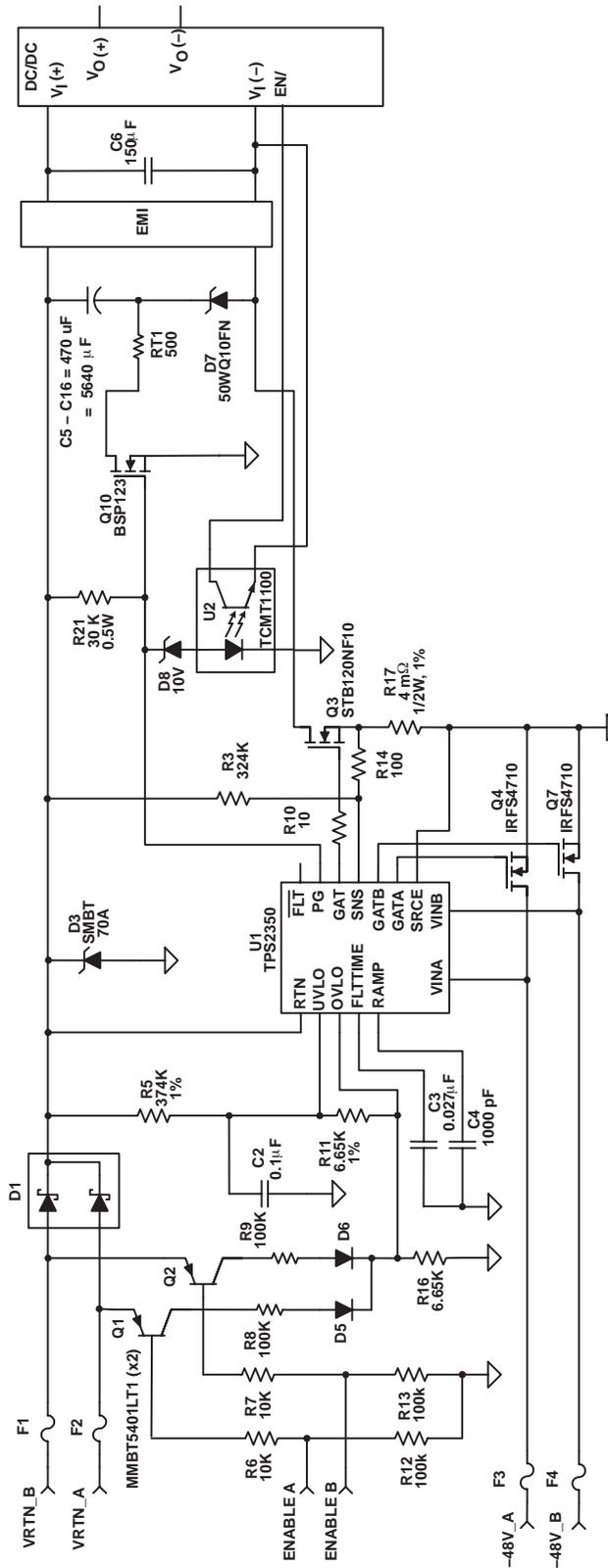


Figure 1. ATCA Hotswap Using the TPS2350

Table 2. TPS2350 Reference Design List of Materials

REF DES	COUNT	DESCRIPTION	MFR	PART NUMBER
C1	1	Capacitor, aluminum, SM, 150 μ F \pm 20%, 100 V, 0.670 X 0.697	Panasonic	EEV-FK2A151M
C2	1	Capacitor, ceramic, 0.1 μ F, 16 V, X7R, 10%, 805	Vishay	Std
C3	1	Capacitor, ceramic, 0.027 μ F, 16 V, X7R, 10%, 805	Vishay	Std
C4	1	Capacitor, ceramic, 1000 pF, 16 V, X7R, 10%, 805	Vishay	Std
C5-C16	12	Capacitor, aluminum, axial lead, 470 μ F \pm 20%, 100 V, 38mm x 18mm	BC Components	2222 138 19471
D1	1	Diode, dual schottky, 20 A, 100 V, D2PAK	Vishay	MBRB20100CT
D3	1	Diode, TVS, 70 V, 600 W, SMB	Diodes	SMBT70A
D5, D6	2	Diode, switching, 200 mA, 200 V, 330 mW, SOT-23	Vishay	BAS21
D7	1	Diode, schottky, 5.5 A, 100 V, DPAK	IR	50WQ10FN
D8	1	Diode, zener, 10 V, 350 mW, SOT-23	Vishay	BZX84C10
F1, F2	2	Fuse, 8 A, 250 V, 0.250 x 1.250	Littelfuse	326 008
F3, F4	2	Fuse, 7 A, 250 V, 0.250 x 1.250	Littelfuse	326 007
Q1, Q2	2	Bipolar, PNP, 150 V, 500 mA, SOT-23	ON Semi	MMBT5401LT1
Q10	1	MOSFET, N-channel, 100 V, 0.380 A, 6 Ω , SOT-23	Infineon	BSP123
Q3	1	MOSFET, N-channel, 100 V, 120 A, 0.009 Ω , D2-PAK	ST Micro	STB120NF10
Q4, Q7	2	MOSFET, N-channel, 100 V, 75 A, 0.014 Ω , D2-PAK	IR	IRFS4710
R10	1	Resistor, chip, 10 Ω , 1/10 W, 1%, 805	Std	Std
R11, R16	2	Resistor, chip, 6.65 k Ω , 1/10 W, 1%, 805	Std	Std
R14	1	Resistor, chip, 100 Ω , 1/10 W, 1%, 805	Std	Std
R15	1	Resistor, chip, 0.004 Ω , 1/2 W, 1%, 2010	Vishay	WSL-2010.004
R21	1	Resistor, chip, 30 k Ω , 1/2 W, 5%, 2010	Vishay	CRCW2010-303J
R3	1	Resistor, chip, 324 k Ω , 1/10 W, 1%, 805	Std	Std
R5	1	Resistor, chip, 374 k Ω , 1/10 W, 1%, 805	Std	Std
R6, R7	2	Resistor, chip, 10 k Ω , 1/10 W, 1%, 805	Std	Std
R8, R9, R12, R13	4	Resistor, chip, 100 k Ω , 1/10 W, 1%, 805	Std	Std
RT1	1	Thermistor, PTC, 500 Ω , 0.197 dia.	Vishay	2322 660 52893
U1	1	IC, Redundant -48-V Hot-Swap Controller, PW14	TI	TPS2350PW
U2	1	IC, opto-coupler, MF4	Vishay	TCMT1100

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265