

Monitoring Five Different Voltage Rails Using the TPS3103 and TPS3306

Dennis Hudgins

Power Management Products/Portable Power DC-DC Apps

ABSTRACT

As portable power designs get more complex, the number of power supply rails are increasing. Finding a simple supervisor circuit to monitor all the voltage rails can be complicated due to the number of different rail voltages and desired SVS trip voltages. To provide a solution for the more complex designs, the TPS3103 and TPS3306 can be used to monitor up to five different voltage rails. This design also features a watchdog timer that can be easily disabled.

The circuit shown in Figure 1 can be used to monitor 1.2-V, 1.5-V, 1.8-V, 2.5-V, and 3.3-V rails. The design is implemented with the TPS3103e12 and the TPS3306-15D. The open drain /PFO and /RESET outputs featured in these supervisors enable these outputs to be connected together in a wired-OR configuration.

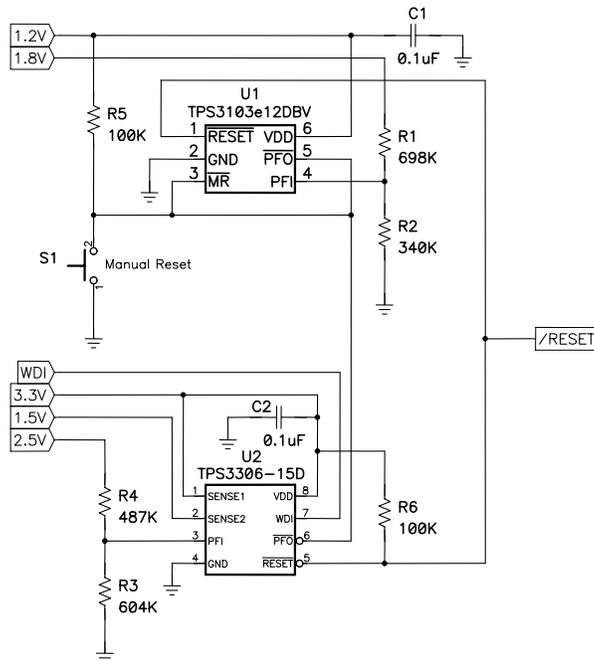


Figure 1. SVS Solution to Monitor Five Different Voltage Rails

By connecting the two /PFO outputs together to the /MR pin of the TPS3103e12, it is possible to monitor two additional voltage rails. The reset delay time for these rails is set by the TPS3103e12 and is typically 130 ms. The delay time for the 3.3-V and 1.5-V rails is set by the TPS3306-15D and is typically 200 ms. If the watchdog function of the TPS3306 is not desired, leaving the WDI pin open disables the watchdog timer. The open-drain /RESET output can be pulled up to 3.3 V without causing problems for the TPS3103, which has a supply voltage of only 1.2 V.

Table 1 shows the rails that can be monitored by changing the voltage version of the TPS3103 and TPS3306. The voltages monitored on rails 2 and 5 are adjustable by an external resistor divider network. The trip voltage at the PFI pin for the adjustable rails is typically 0.551 V for the TPS3103 and 1.25 V for the TPS3306.

Table 1. All Possible Rail Voltages for Different Voltage Devices

TPS3103		TPS3306		
Rail 1	Rail 2	Rail 3	Rail 4	Rail 5
1.2, 1.5, 2.0, 3.3	Adjustable	3.3, 5.0	1.5, 1.8, 2.0, 2.5, 3.3	Adjustable

Because the reset delay time for the TPS3103 is typically 130 ms, no deglitching circuitry is needed for the manual reset switch shown in Figure 1.

Since the supply current for the TPS3103 is less than the TPS3306 supply current, the propagation delay from power fault to reset output is longer for the TPS3103. For most applications, some propagation delay is desired to provide additional noise immunity. See the TPS3103 and TPS3306 data sheets (SLVS363 and SLVS290) for additional information about the propagation delays for /MR, VDD, and SENSE to /RESET output.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2003, Texas Instruments Incorporated