

Analog Dimming With the TPS61500 Using an Analog Input Signal

Jeff Falin

PMP - DC/DC Low-Power Converters

ABSTRACT

Although designed to perform analog white LED dimming from a PWM input signal, the TPS61500 also can perform analog dimming from an analog input signal such as a digital-to-analog converter, for example.

Figure 1 shows how to configure the TPS61500 to perform analog dimming from an analog input signal.

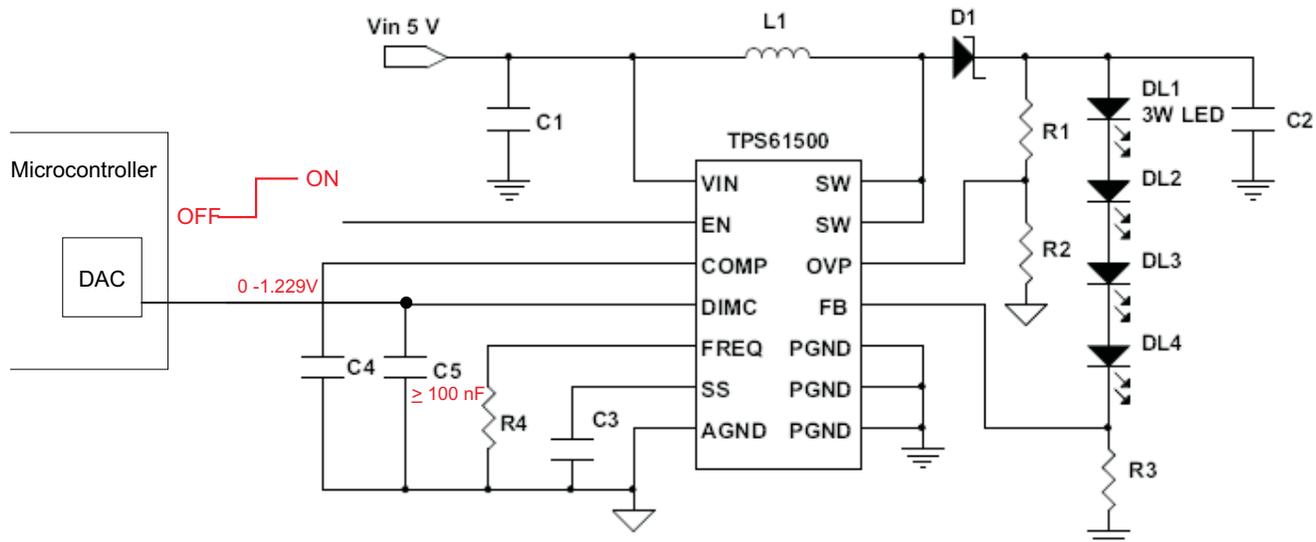


Figure 1. Circuit for the TPS61500 to Perform Analog Dimming Using an Injected Analog Signal

The analog input signal can come from the digital-to-analog converter (DAC) output of a microcontroller or a stand-alone DAC. The input analog signal (V_{DAC}) range must be from 0 to 1.229 V. This externally applied voltage overrides the internal voltage to which the DIMC pin is internally pulled up. Equation 1 gives the regulated WLED current

$$I_{LED} = \frac{V_{FBmax}}{R3} \times \frac{V_{DAC}}{1.229V} \quad (1)$$

In order for the IC to properly configure itself for analog dimming instead of PWM dimming, a capacitor of 100 nF or higher must still be connected to the DIMC pin and no external voltage higher than 0 ± 50 mV can be applied to the DIMC pin until 200 μ s after EN is pulled high. In the event that the DAC cannot be programmed to provide 0 V when the TPS61500 is enabled, a FET with RC turnon delay circuit (shown in Figure 2) can be inserted between the DAC and DIMC pin to isolate the DAC from the DIMC until the IC has configured itself for analog dimming.

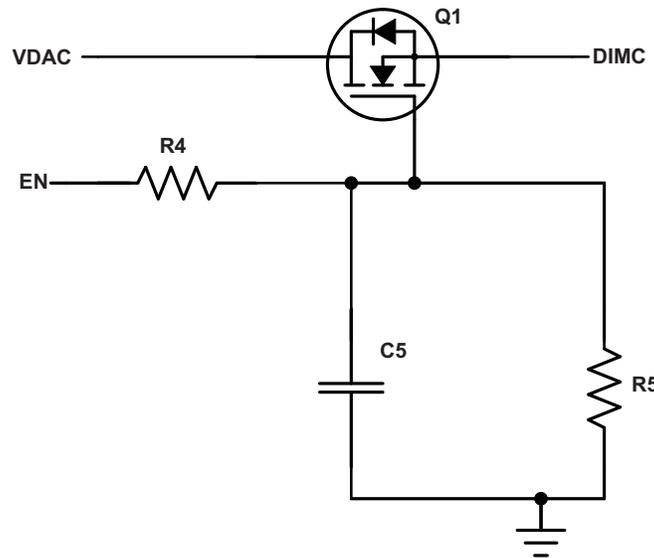


Figure 2. Isolation Circuit With RC Delayed Turnon

Equation 2 and Equation 3 show how to size the delay circuit's resistors and capacitor:

$$3 \times C5 \times \frac{R4 \times R5}{R4 + R5} \geq 200 \mu\text{s} \tag{2}$$

$$1.229 \text{ V} + V_{\text{THmin}} < V_{\text{EN}} \times \frac{R5}{R4 + R5} < V_{\text{GSmax}} \tag{3}$$

where V_{THmin} is Q1's minimum threshold voltage and V_{GSmax} is Q1's maximum gate-to-source voltage. Because low current flows through it, Q1 can be a low-cost NFET, such as the 2N7002.

Figure 3 shows the analog dimming linearity as a function of duty cycle and V_{DAC} .

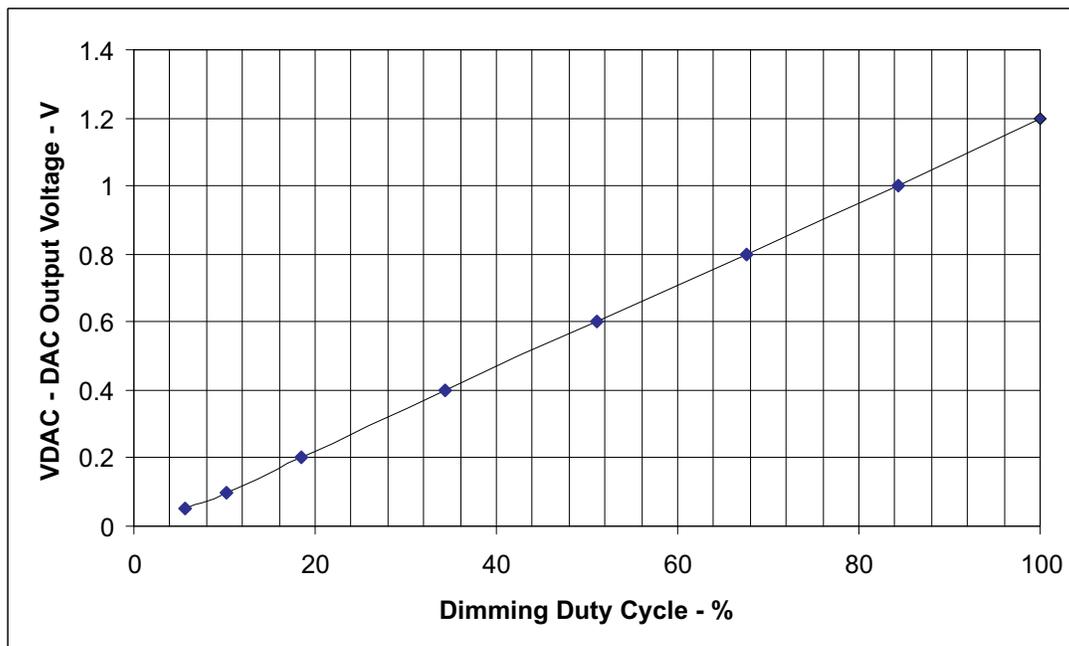


Figure 3. Analog Dimming Linearity

Figure 4 shows the output voltage and LED current from the TPS61500EVM-369 when a 0.61-V signal is applied directly to the DIMC pin and $R3 = 0.39 \Omega$. As expected, the regulated WLED current is

$$\frac{0.2 \text{ V}}{0.39 \Omega} \times \frac{0.61 \text{ V}}{1.229 \text{ V}} = 0.254 \text{ A} \quad (4)$$

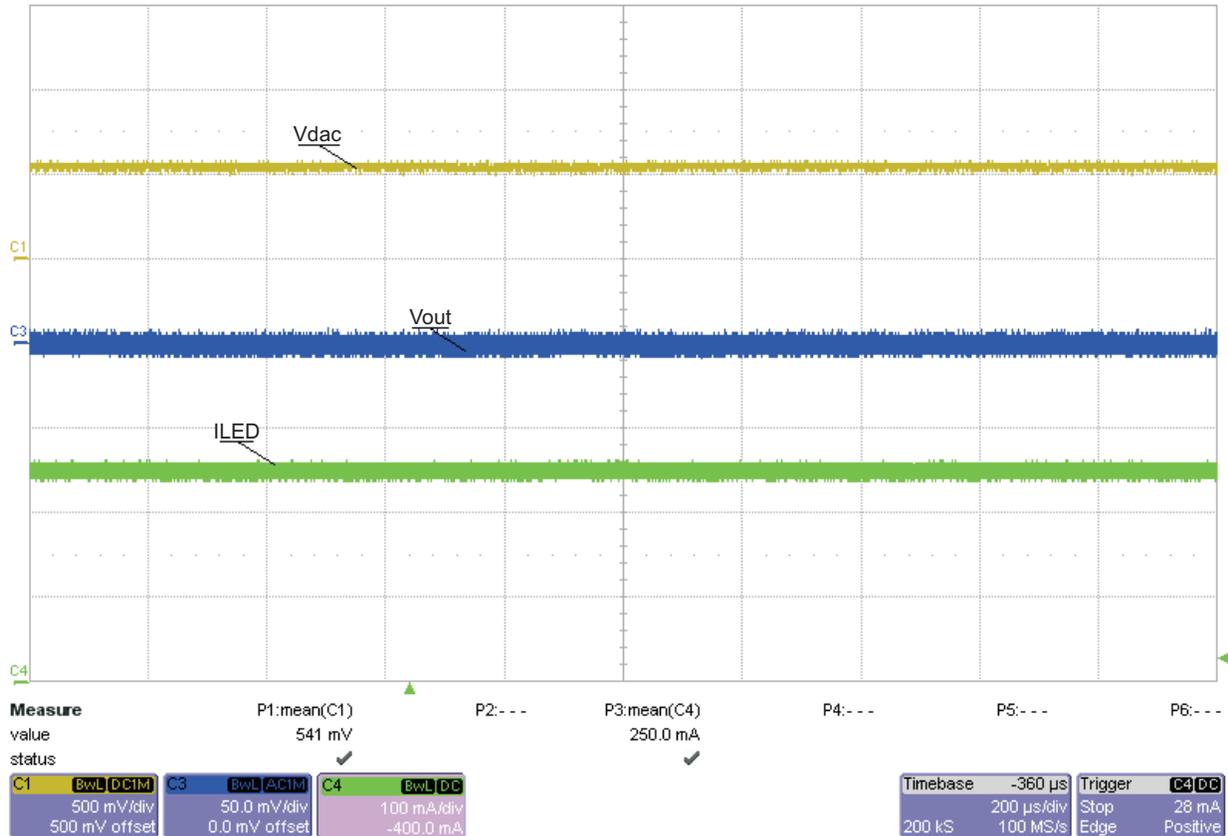


Figure 4. Output Voltage and LED Current With $V_{IN} = 5 \text{ V}$ and $V_{DAC} = 0.61 \text{ V}$

Note that the output voltage shows no output voltage ripple, other than the expected switching noise, on V_{OUT} when an analog signal is injected to perform analog dimming as compared to a PWM signal as shown in Figure 10 of the data sheet ([SLVS893](#)).

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated