

# Introduction to Anti-Audible Noise Function in TPS65235-1

Zhao Ma

## ABSTRACT

The TPS65235-1 implements an anti-audible noise function to eliminate the audible noise in forced continuous conduction mode (FCCM). This application note introduces this anti-audible noise function, which includes the root cause of audible noise, the circuit modifications in design, and the EVM laboratory validation. In addition, the BOOST converter output filter capacitor and inductor selection are also discussed.

## Contents

1	Introduction .....	2
2	Audible Noise.....	2
3	Anti-Audible Noise Principle .....	4
4	TPS65235 and TPS65235-1 Comparison .....	5
5	Application Information.....	6
6	EVM Laboratory Validation .....	8
7	Summary.....	9
8	References .....	10

## List of Figures

1	BOOST Ripple Amplitude and Frequency in TPS65235 .....	2
2	TPS65235-1 EVM Schematic .....	3
3	MLCC and PCB Subtle Vibration .....	3
4	OVP Comparator Block Diagram .....	4
5	TPS65235: $V_{PP}= 1.03\text{ V}$ , $F_{RIPPLE}= 560.5\text{ Hz}$ .....	5
6	TPS65235-1: $V_{PP}=20.8\text{ mV}$ , $F_{RIPPLE}=22.5\text{ kHz}$ .....	5
7	$V_{PP} = 25.6\text{ mV}$ , $C_{BOOST} = 2*22\text{ }\mu\text{F}$ .....	6
8	$V_{PP} = 12.4\text{ mV}$ , $C_{BOOST} = 3*22\text{ }\mu\text{F}$ .....	6
9	BOOST Ripple Under $V_{LNB} = 18.2\text{ V}$ , Load = 1-A Condition .....	7
10	C3216X5R1V226M DC Bias Characteristic .....	7
11	$V_{PP} = 26\text{ mV}$ , $L = 4.7\text{ }\mu\text{H}$ .....	8
12	$V_{PP}= 20.8\text{ mV}$ , $L = 10\text{ }\mu\text{H}$ .....	8
13	$V_{PP} = 20.8\text{ mV}$ , $F_{RIPPLE} = 22.5\text{ kHz}$ , Load = 0 A.....	8
14	$V_{PP} = 38\text{ mV}$ , $F_{RIPPLE} = 42\text{ kHz}$ , Load = 10 mA.....	8
15	$V_{PP} = 43.2\text{ mV}$ , $F_{RIPPLE} = 58.5\text{ kHz}$ , Load = 20 mA .....	8
16	$V_{PP} = 42\text{ mV}$ , $F_{RIPPLE} = 70.4\text{ kHz}$ , Load = 30 mA .....	8
17	$V_{PP} = 46.8\text{ mV}$ , $F_{RIPPLE} = 62.5\text{ kHz}$ , Load = 50 mA .....	8
18	$V_{PP} = 47.2\text{ mV}$ , $F_{RIPPLE} = 47.6\text{ kHz}$ , Load = 60 mA .....	8
19	$V_{PP} = 33.2\text{ mV}$ , $F_{RIPPLE} = 40.3\text{ kHz}$ , Load = 70 mA .....	9
20	$V_{PP} = 7.2\text{ mV}$ , $F_{RIPPLE} = 1.05\text{ MHz}$ , Load = 80 mA.....	9

## List of Tables

1	EVM Test Conditions .....	5
---	---------------------------	---

## Trademarks

All trademarks are the property of their respective owners.

## 1 Introduction

TPS65235 is a low noise block (LNB) voltage regulator for satellite receivers. The device is composed of an internal compensated boost converter and LDO regulator, and it is optimized to provide good performance with minimum external component counts.

However, there is a very common phenomenon in application. When  $V_{IN}$  is closer to  $V_{LNB}$  under light load condition, a continuous buzzing sound will be heard, which is called audible or acoustic noise.

The TPS65235-1 implements an anti-audible noise function in FCCM to eliminate the audible noise.

## 2 Audible Noise

### 2.1 Audible Frequency Range

Audible frequency is characterized as a periodic vibration with a frequency audible to the average human. The generally accepted standard range of audible frequencies is 20 Hz to 20 kHz—though the range of frequencies individuals can hear is greatly influenced by environmental factors.

### 2.2 Audible Noise

When  $V_{IN}$  is closer to  $V_{LNB}$  at light load, the audible noise is very easily perceived in FCCM for the following two reasons:

1. Overvoltage protection (OVP) occurs periodically, which causes the LX skipping frequency is within audio-frequency range (20 Hz to 20 kHz).
2. OVP comparator has 1-V hysteresis, which causes the BOOST ripple amplitude to be about 1 V.

Figure 1 shows the BOOST ripple frequency at 560.5 Hz and the ripple amplitude at 1.03 V under  $V_{IN} = 12$  V,  $V_{LNB} = 12.8$  V, no load condition.

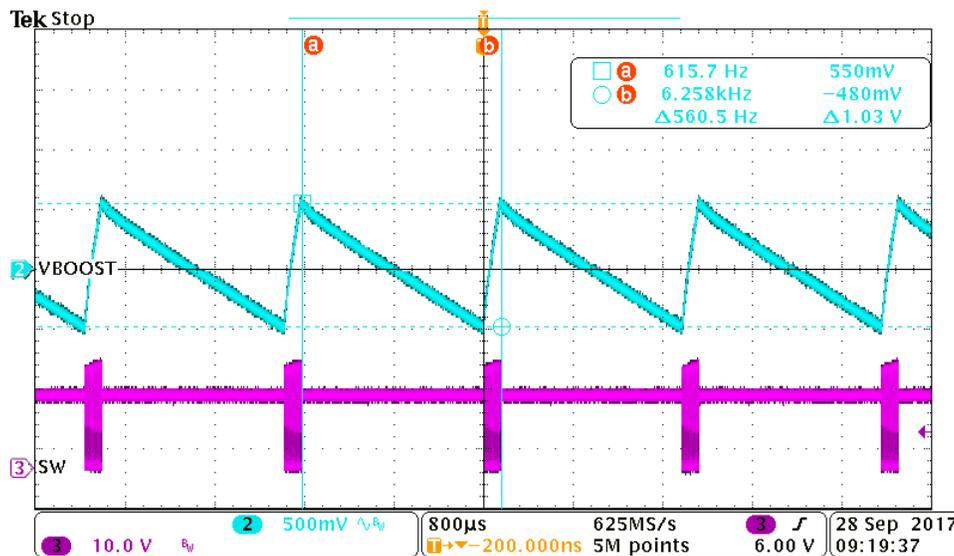


Figure 1. BOOST Ripple Amplitude and Frequency in TPS65235

### 2.3 Audible Noise Root Cause

The audible noise is generated by the BOOST output filter capacitor ( $C_{BOOST} = C8 + C9$ ), which is the multi-layer ceramic capacitor (MLCC) in [Figure 2](#).

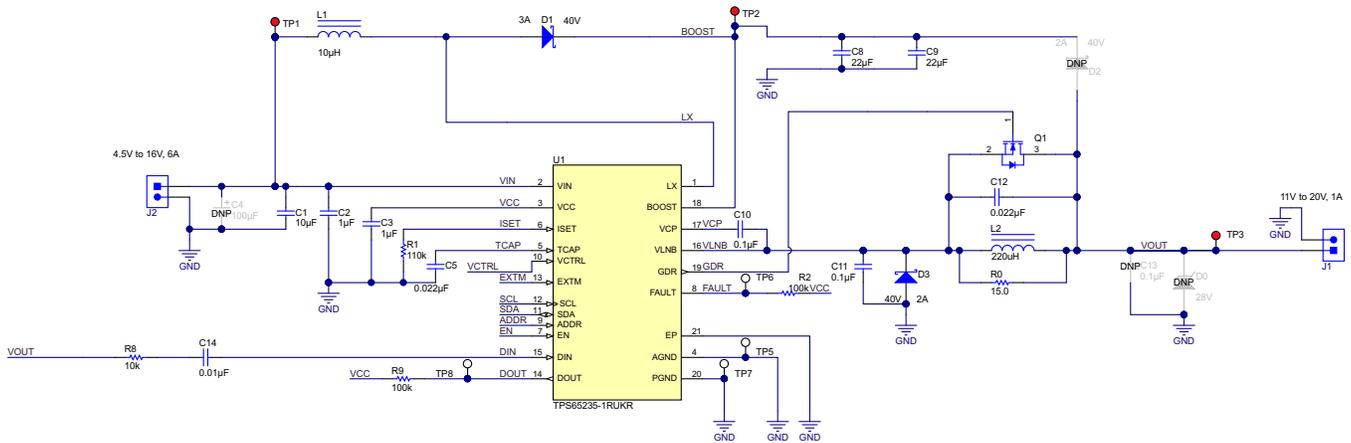


Figure 2. TPS65235-1 EVM Schematic

The MLCC uses dielectrics with piezoelectric characteristic. [Figure 3](#) shows when the AC voltage is applied to MLCC, the dielectrics will cause a subtle vibration by expanding and contracting, and the vibration travels to PCB surface. If the AC frequency is within audio-frequency range, the sound will be perceived by human ear.

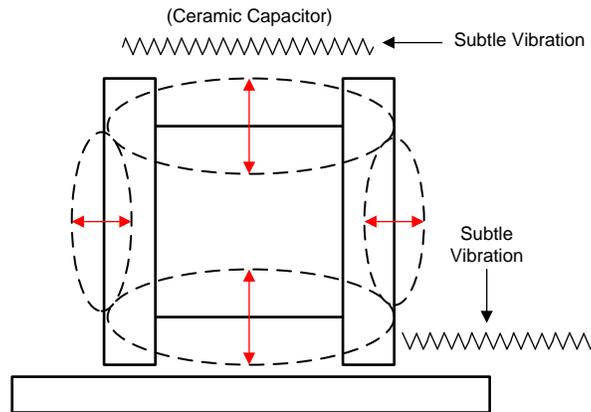


Figure 3. MLCC and PCB Subtle Vibration


### 3 Anti-Audible Noise Principle

Whether the audible noise is heard depends on the following two principles:

1. BOOST ripple frequency is within audio-frequency range (20 Hz to 20 kHz).
2. BOOST ripple amplitude must be large enough.

The BOOST converter in TPS65235-1 adopts non-synchronous topology where out of audio (OOA) function cannot be implemented. Based on the two discussed principles, the TPS65235-1 made the following two modifications for OVP comparator (shown in Figure 4).

1. Remove 1-V hysteresis of OVP comparator, which can reduce the BOOST ripple amplitude.
2. Use a fast OVP comparator, which can increase the LX skipping frequency and further reduce the BOOST ripple amplitude.

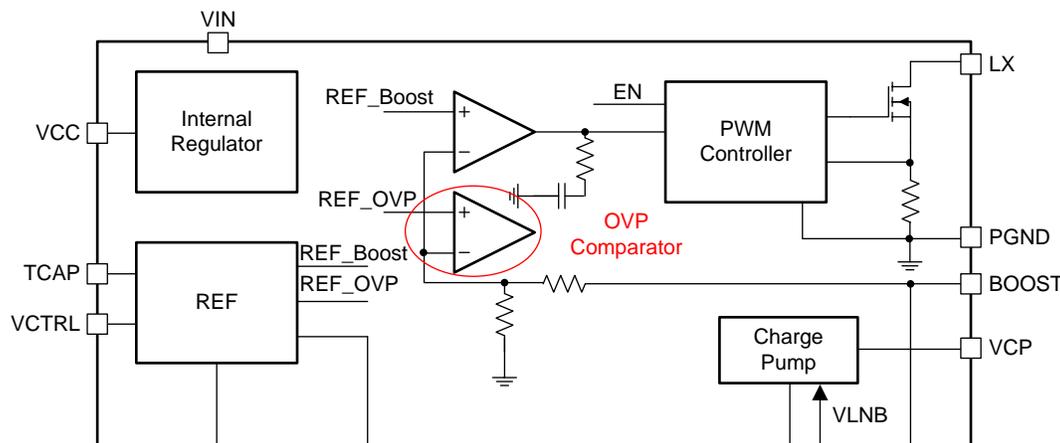

**Figure 4. OVP Comparator Block Diagram**

#### 4 TPS65235 and TPS65235-1 Comparison

Figure 5 and Figure 6 show the BOOST ripple amplitude and frequency comparison between TPS65235 and TPS65235-1 under Table 1 conditions.

Table 1. EVM Test Conditions

PARAMETER	VALUE
$V_{IN}$	12 V
$V_{LNB}$	12.8 V
Inductor	10 $\mu$ H
$C_{BOOST}$	2*22 $\mu$ F
Switching frequency	1 MHz
Working mode	FCCM
Loading	0 A

Compared with TPS65235, the BOOST ripple frequency of TPS65235-1 is increased from 560.5 Hz to 22.5 kHz, the BOOST ripple amplitude is decreased from 1.03 V to 20.8 mV, and the audible noise on disappears.

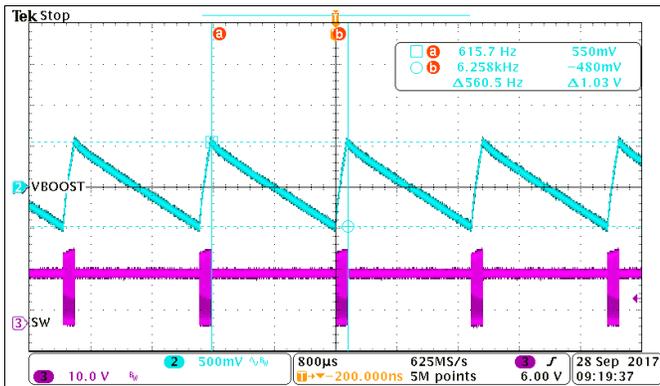


Figure 5. TPS65235:  $V_{PP}=1.03$  V,  $F_{RIPPLE}=560.5$  Hz

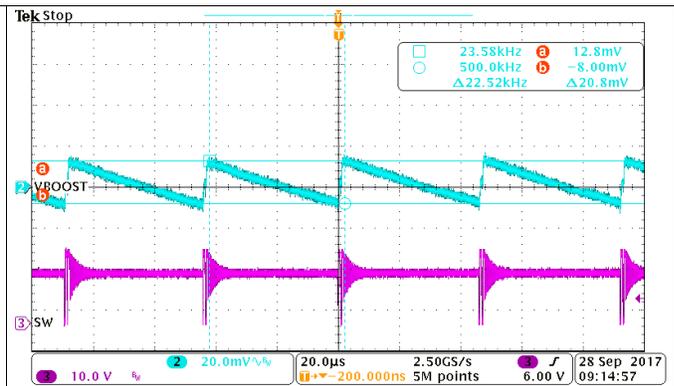


Figure 6. TPS65235-1:  $V_{PP}=20.8$  mV,  $F_{RIPPLE}=22.5$  kHz


## 5 Application Information

This section presents a discussion of proper external component selection for TPS65235-1 in application.

### 5.1 BOOST Output Filter Capacitor Selection

Increasing the BOOST output filter capacitance can reduce the BOOST ripple amplitude.

Figure 7 and Figure 8 show the BOOST ripple comparison between  $C_{BOOST} = 2 \times 22 \mu F$  and  $C_{BOOST} = 3 \times 22 \mu F$ . Under  $V_{IN} = 12 V$ ,  $V_{LNB} = 12.8 V$ , no load condition, the BOOST ripple amplitude in Figure 8 is reduced by 32.7%.

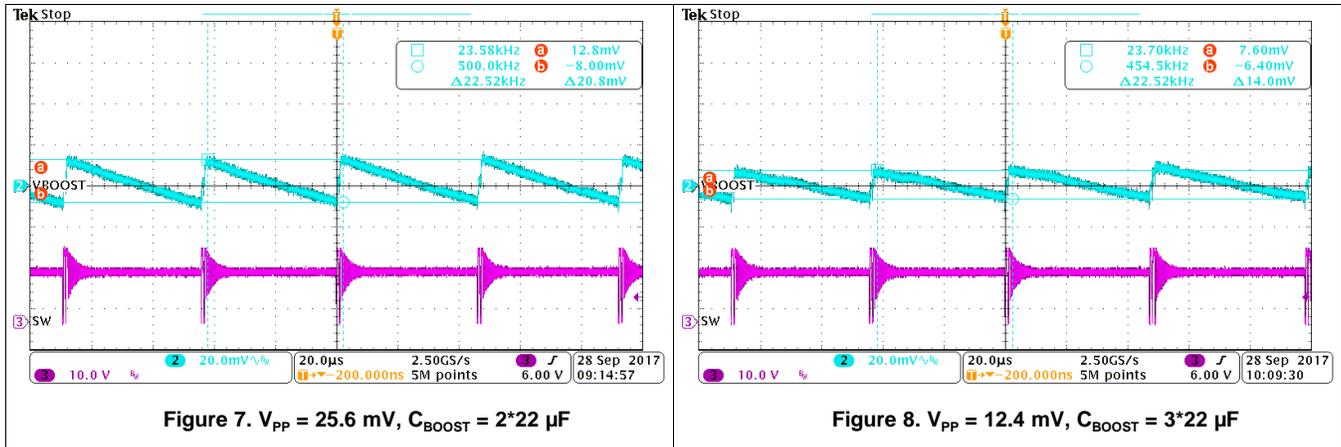

When selecting the MLCC as BOOST output filter capacitor, the capacitance derating should be considered. The following introduces a method to evaluate the MLCC actual capacitance.


Figure 9 shows the waveform that TPS65235-1 works under  $V_{IN} = 12 V$ ,  $V_{LNB} = 18.2 V$ , load = 1-A condition. Ignoring the influence of ESR, the actual capacitance can be calculated by Equation 1.

$$C_{actual} (\mu F) = \left( \frac{I_{load} \times T_{on}}{V_{pp}} \right) = \left( \frac{1A \times 336nS}{50.8 \text{ mV}} \right) = 6.6 \mu F \quad (1)$$

Where:


- $C_{actual}$  = actual capacitance of BOOST output filter capacitor
- $I_{load}$  = output load current
- $T_{ON}$  = ON state time of POWER MOSFET
- $V_{PP}$  = BOOST ripple peak-peak amplitude

Compared with the  $C_{BOOST}$  nominal capacitance, the actual capacitance degrades from  $2 \times 22 \mu F$  to  $6.6 \mu F$  when biased  $V_{BOOST} = 20.2\text{-V}$  DC voltage, which is decreased by 85%.

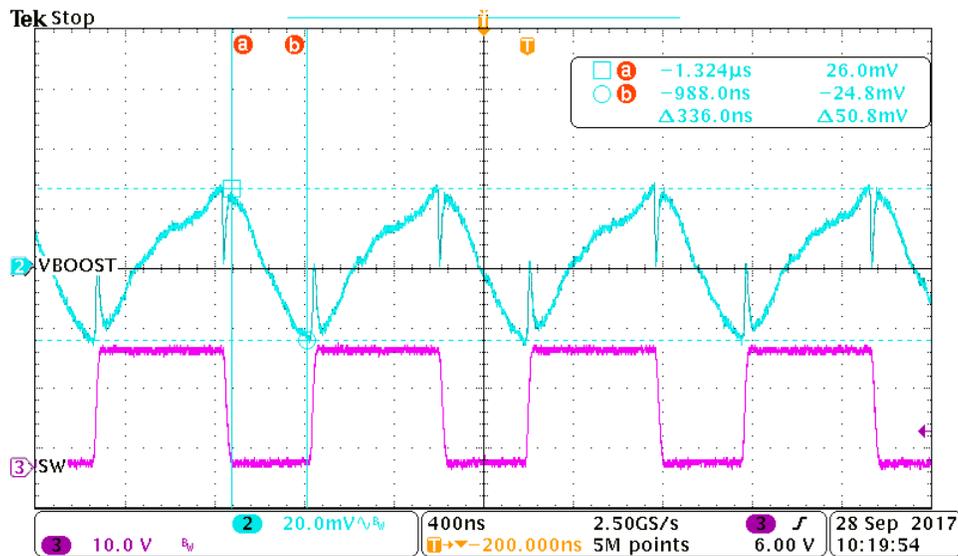

**Figure 9. BOOST Ripple Under  $V_{LNB} = 18.2$  V, Load = 1-A Condition**

The MLCC actual capacitance can also be obtained from DC Bias Characteristic in its characteristic graph. Figure 10 shows a TDK MLCC DC bias characteristic, C3216X5R1V226M (22  $\mu$ F, 35V, X5R, 1206 package). The capacitance degrades 86% at 20-V bias DC voltage, which is approximately equal to the Equation 1 calculation.

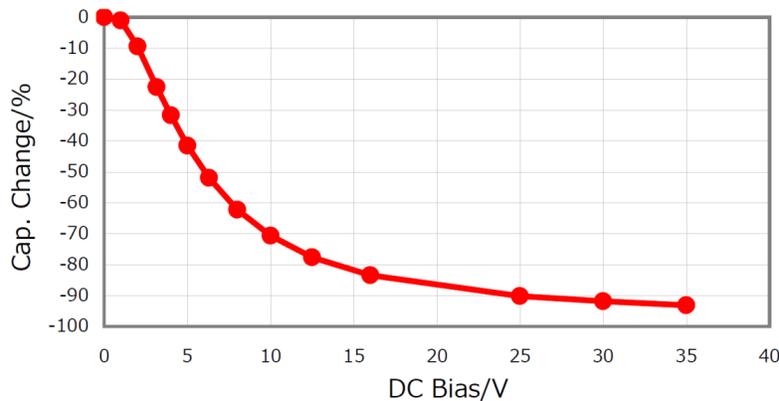



**Figure 10. C3216X5R1V226M DC Bias Characteristic**

In addition, the dielectric layer of electrolytic capacitor (ECAP) and polymer capacitor (POSCAP and SPCAP) do not have piezoelectric characteristic, and the layer will not vibrate with biased AC voltage. When selecting ECAP, POSCAP, or SPCAP as BOOST output filter capacitor, there will be no audible noise.

## 5.2 Boost Inductor Selection

At light load, the BOOST converter outputs the minimum ON time during each cycle. When using bigger inductance, the inductor peak current will be smaller. During OFF time, the inductor will release less energy to BOOST output filter capacitor, so using bigger inductance can reduce the BOOST ripple amplitude.



Figure 11 and Figure 12 show the BOOST ripple amplitude comparison between  $L = 10 \mu\text{H}$  and  $L = 4.7 \mu\text{H}$  under  $V_{\text{IN}} = 12 \text{ V}$ ,  $V_{\text{LNB}} = 11.6 \text{ V}$ , no load condition. The BOOST ripple amplitude of  $L = 10 \mu\text{H}$  is reduced by 20%.





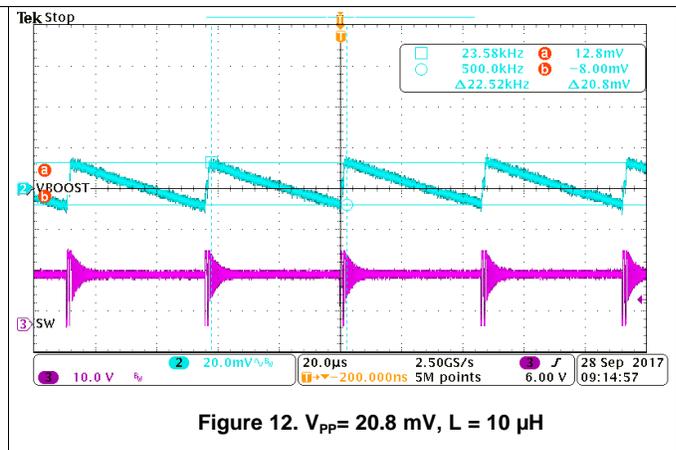
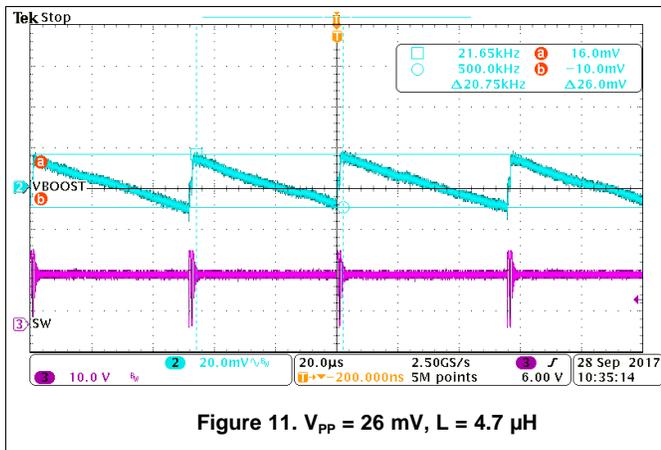

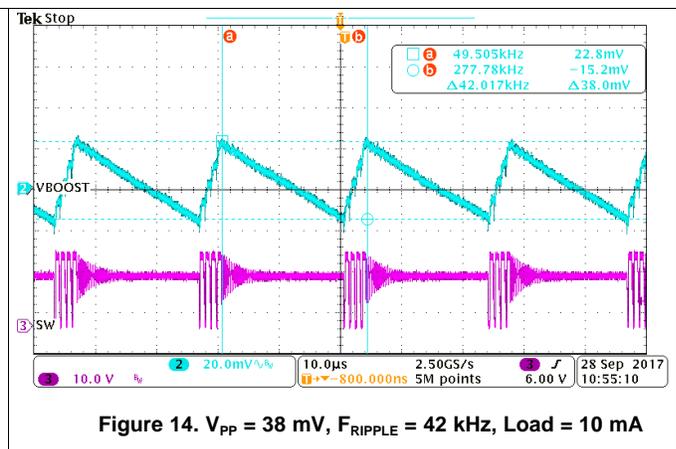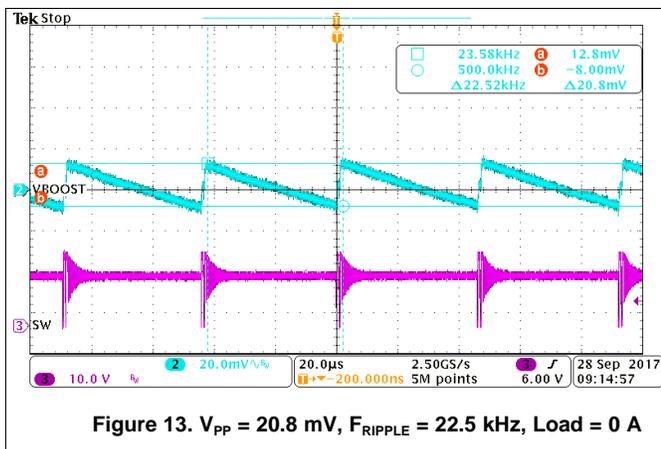
## 6 EVM Laboratory Validation

TPS65235-1EVM is tested under Table 1 condition, the following figures show the BOOST ripple frequency ( $F_{\text{RIPPLE}}$ ) and ripple peak-peak amplitude ( $V_{\text{PP}}$ ) waveforms when changing load from 0 A to 100 mA. All of  $F_{\text{RIPPLE}}$  are out of audio-frequency range, and all of  $V_{\text{PP}}$  are small, so there is no audible noise.

In addition, under different  $V_{\text{IN}}$  and  $V_{\text{LNB}}$  condition, after full laboratory validation, there is no audible noise too



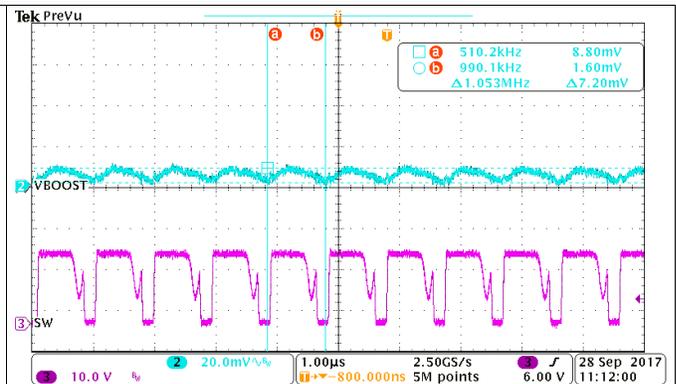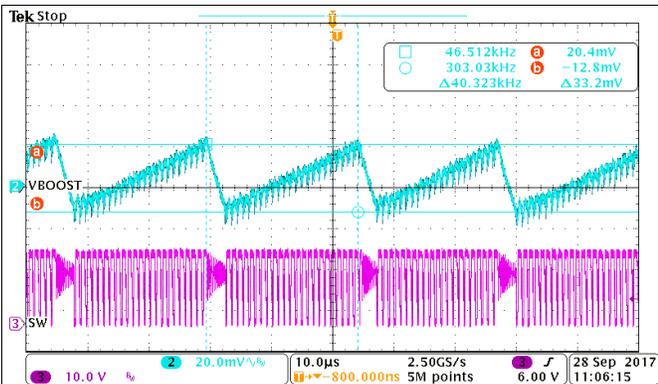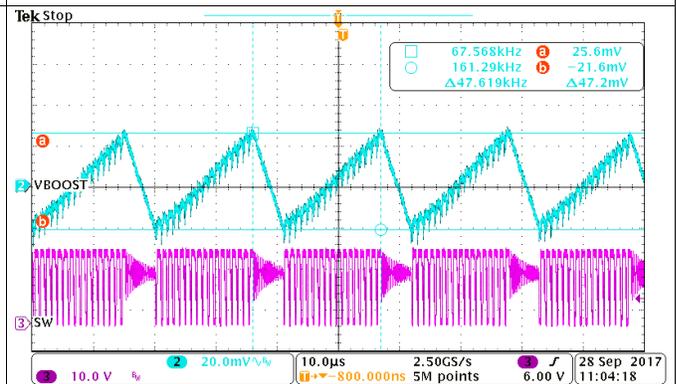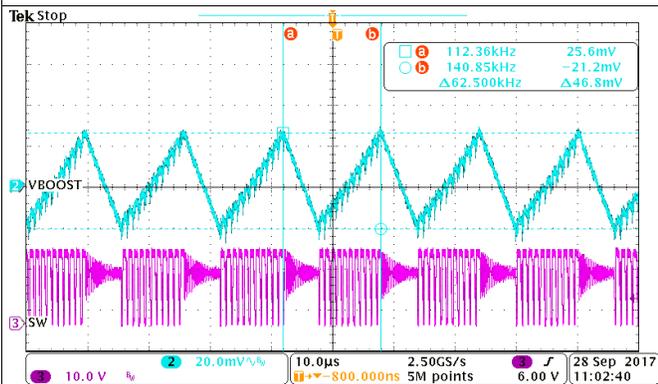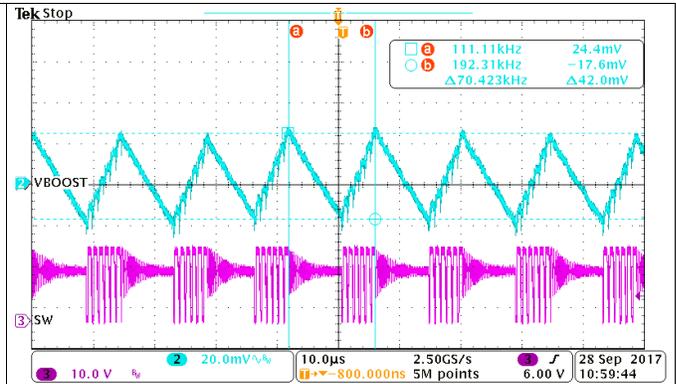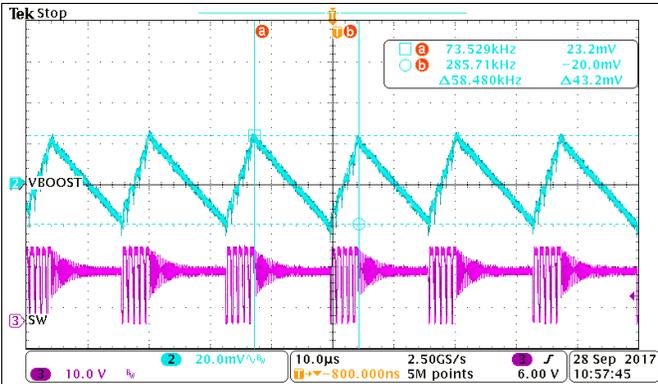

## 7 Summary

Stringent laboratory validation proves that the anti-audible noise function is effective. TPS65235-1 with proper external components can eliminate the audible noise completely in FCCM.

## 8 References

1. Texas Instruments, [TPS65235-1 LNB Voltage Regulator With I<sup>2</sup>C Interface Data Sheet](#)
2. TDK, [MLCC with Dipped Radial Lead](#)
3. Murata, [Examples of Noise Countermeasures \(Video\)](#)
4. Texas Instruments, [Evaluation Module for the TPS65235-1 LNB Voltage Regulator With I<sup>2</sup>C Interface for DiSEqC2.x Application User's Guide](#)
5. Texas Instruments, [DiSEqC™ Protocol and Low-Noise Block Voltage Regulator TPS65235 for Satellite – STB/TV Application Report](#)
6. Texas Instruments, [LNB Design Considerations on TPS65233 and TPS65235 Application Report](#)
7. TDK, [Multilayer Ceramic Chip Capacitors:C3216X5R1V226M160AC Detailed Information](#)

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated