

# **Designing Boost Converter TPS61372 in Low Power Application**

---



---

*Jasper Li*

## **ABSTRACT**

The application report introduces how to design a small power, small solution size boost converter using the TPS61372 device. The external components of the converter are calculated and selected based on the designed target. The stable and transient performances are measured at different conditions to show the behavior of the converter.

---

### **Contents**

1	Introduction .....	2
2	External Component Design .....	2
3	Bench Test Result .....	3
4	Summary .....	5
5	References .....	5

### **List of Figures**

1	Operating Mode at Different Load Conditions .....	2
2	Output Voltage Ripple at No Load Condition .....	3
3	Output Voltage Ripple at 50-mA Load condition .....	3
4	Output Ripple at 5-V Output and no load condition .....	4
5	Output Ripple at 16-V Output and No Load Condition.....	4
6	Start-up at No Load Condition .....	4
7	Start-up at 50-mA load .....	4
8	Load Transient From 5 mA to 45 mA .....	4
9	Efficiency at Different Input Voltages.....	5

### **List of Tables**

## **Trademarks**

All trademarks are the property of their respective owners.

## 1 Introduction

TPS61372 is a 16-V, 3.6-A peak current synchronous boost converter. The integrated synchronous MOSFET improves the solution efficiency and also provides capability for forced PWM operation if fixed switching frequency is required. The isolation MOSFET in series with the synchronous MOSFET disconnects the input from output when TPS61372 shuts down. This feature reduces the shutdown current consumption below 1  $\mu$ A. The isolation MOSFET also protects the TPS61372 and the power source when short circuit happens at the output.


The typical output power of the TPS61372 is 5 Watts. However, the device can also be used in low power applications. This application report provides a small solution targeting following application condition:

- Input voltage  $V_{IN}$ : 3.6 V
- Output voltage  $V_{OUT}$ : 12 V
- Output current  $I_{OUT}$ : 50 mA

## 2 External Component Design

The TPS61372 has a MODE pin to set the operation mode. When the mode is logic high, the device operates at forced pulse width modulation (PWM) mode. At forced PWM mode, the device switches with 1.5 MHz (typical) disregarding the loading. This results in very low efficiency at light load condition. To improve efficiency, the MODE pin is set to low in this application report. The TPS61372 can operate at three types of mode depending on the loading, as shown in [Figure 1](#)

- At light load, the device operates at pulse frequency modulation (PFM). At PFM, the inductor peak current is clamped at  $I_{CLAMP}$ , which is typical 900 mA at 12-V output voltage. The  $I_{CLAMP}$  decrease to 500 mA at 5-V output and increases to 1200 mA at 16-V output. The frequency  $f_{PFM}$  changes with loading to regulate the output voltage.
- At medium load, the device operates discontinued conduction mode (DCM). At this mode, the device has fixed operating frequency  $f_{DCM}$ , which is approximately 1.5 MHz. The inductor peak current is higher than  $I_{CLAMP}$  and increase with the loading. The inductor current decline to zero before next cycle. Both the high side and low side power MOSFET turn off during zero inductor current period.
- At high load, the device operates at continued conduction mode (CCM). The switching frequency  $f_{CCM}$  is the same as  $f_{DCM}$ , and peak inductor current increases with the loading. The minimum inductor current is higher than zero, so there will be one power MOSFET turning on at any time. both the DCM and CCM belong to PWM.

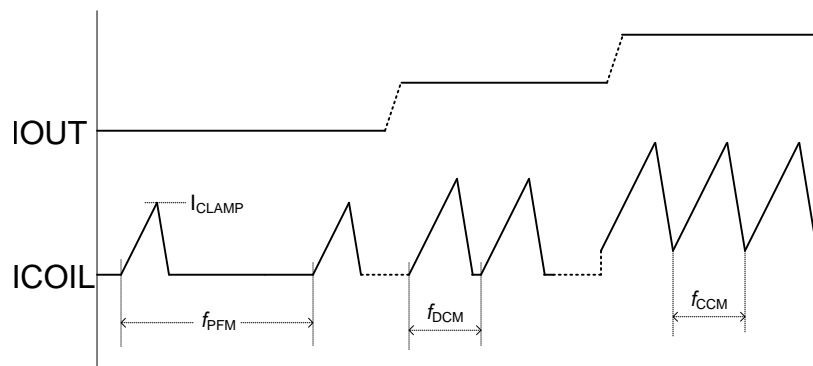

**Figure 1. Operating Mode at Different Load Conditions**

The boundary loading current between PFM and DCM is defined by [Equation 1](#).

$$I_{OUT\_B} = \frac{1}{2} \frac{\eta \cdot L \cdot I_{CLAMP} \cdot f_{DCM}}{V_{OUT} - V_{IN}}$$

where

- $I_{OUT\_B}$  is the boundary output current between PFM and DCM.
- $\eta$  is efficiency of the boost converter. It can be set to 0.8.
- $L$  is the inductor value.
- $I_{CLAMP}$  is approximately 900 mA.
- $f_{DCM}$  is 1.5 MHz,
- $V_{OUT}$  and  $V_{IN}$  is the output voltage and input voltage, respectively.

(1)

According the TI application note [How to Select a Proper Inductor for Low Power Boost Converter](#), a 1- $\mu$ H inductor can be selected to reduce the solution size. At 3.6-V input voltage and 12-V output voltage condition, the  $I_{OUT\_B}$  is approximately 64 mA. As the  $I_{OUT\_B}$  is higher than designed maximum output current, the device always operates at PFM. Based on the inductance and peak current, DFE201208S-1R0M = P2 or other similar components can be selected.

The output capacitor is selected through the ripple requirement. In PFM operation, the maximum output ripple happens at no load condition, thus the maximum output ripple can be calculated by [Equation 2](#).

$$V_{RIP} = \frac{L \cdot I_{CLAMP}^2}{2(V_{OUT} - V_{IN}) \cdot C_{OUT}}$$

(2)

Setting output voltage ripple to 30mV, the output capacitance will be approximately 1.7  $\mu$ F. Note that this is the effective capacitance. For a ceramic capacitor, the effective capacitance could be much lower than the rating capacitance after applying DC bias voltage. For example, a 10- $\mu$ F, 25-V, 0603 package capacitor GRM188R61E106MA73 has only 1.6  $\mu$ F effective capacitance at 12-V bias voltage. So the GRM188R61E106MA73 is selected for this application condition.

In PFM mode, compensation resistor and capacitor connected to COMP pin don't impact the respond of the converter. The converter is controlled by internal parameter. However, the compensation resistor and capacitor can be still designed based on PWM operation to ensure the stability of the converter at any load condition. With  $V_{IN} = 3.6$  V,  $V_{OUT} = 12$  V, 1- $\mu$ H inductor, 1.6- $\mu$ F output capacitance and 50-mA loading, the compensation resistor and capacitor can be set to 40 K and 680 pF to stabilize the device even at PWM mode operation.

### 3 Bench Test Result

The ripple waveforms of the TPS61372 at 0-mA and 50-mA loading condition are shown in [Figure 2](#) and [Figure 3](#). In the waveforms, the blue line is output voltage ripple, and the green line is the inductor. The device operates at PFM and its switching frequency changes with the loading. the output voltage ripple is approximately 30 mV as the calculation.

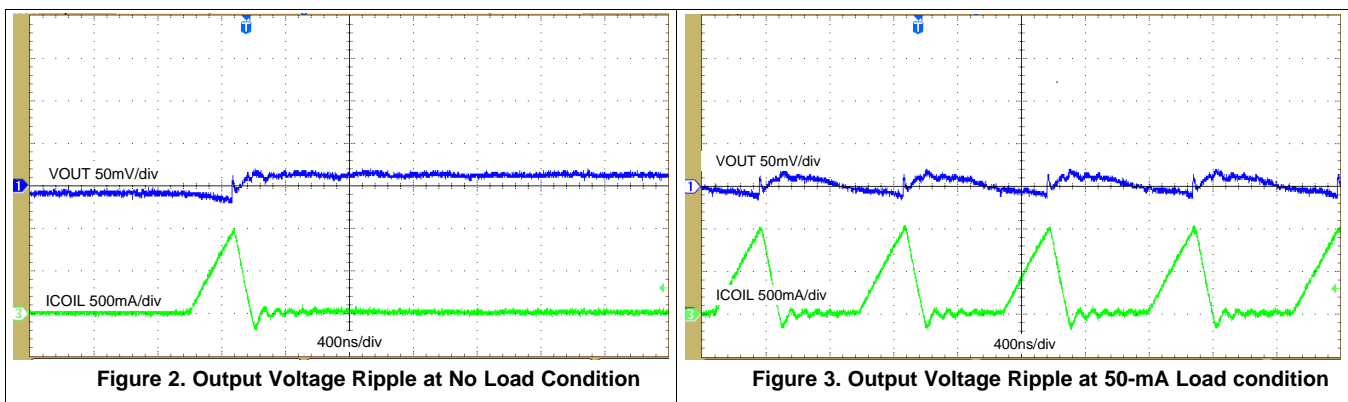


Figure 4 and Figure 5 shows the output ripple at different output voltage and no load condition. The peak current is approximately 500 mA at 5-V output voltage condition and 1200 mA at 16-V output voltage condition. The output capacitance can be increased if want to have smaller ripple.

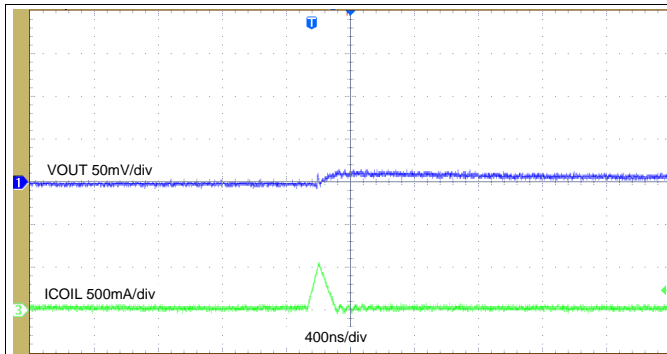


Figure 4. Output Ripple at 5-V Output and no load condition

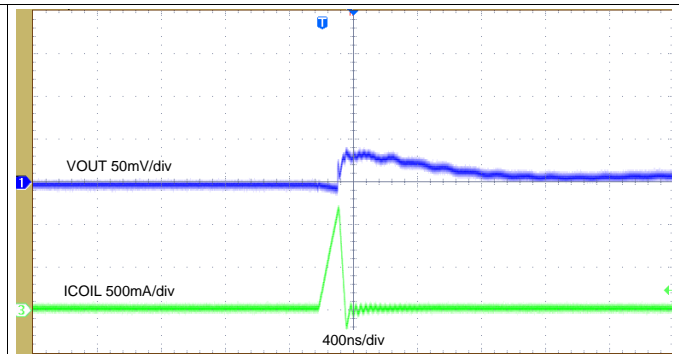


Figure 5. Output Ripple at 16-V Output and No Load Condition

The start-up waveforms by EN pin are shown in Figure 6 and Figure 7. The output voltage starts from zero and increases to 12 V smoothly.

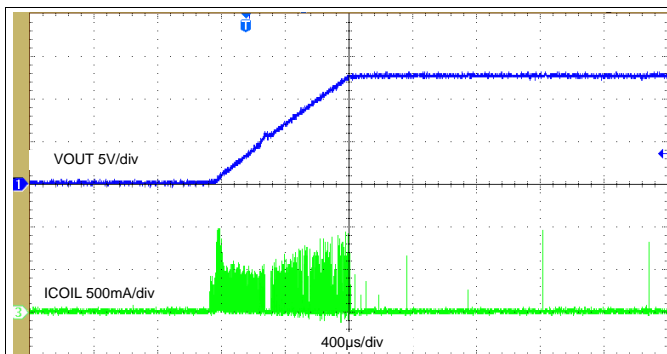


Figure 6. Start-up at No Load Condition

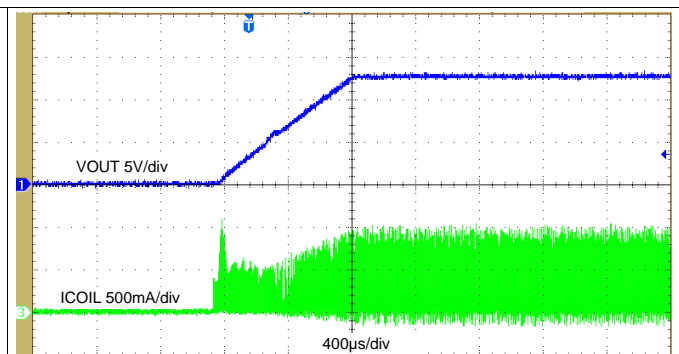


Figure 7. Start-up at 50-mA load

To estimate the stability of the converter, load transient performance can be measured. The load transient performance from 5 mA to 45 mA is shown in Figure 8. The output voltage recovers to the setting output voltage smoothly during the load transient, which means the stability of the device is good.


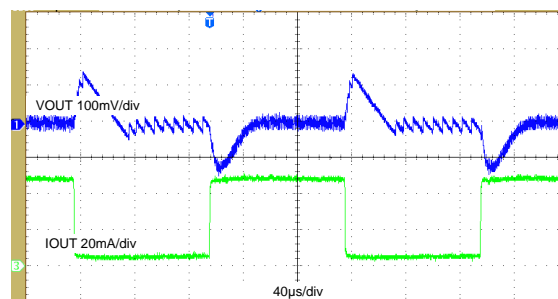


Figure 8. Load Transient From 5 mA to 45 mA

Figure 9 shows the efficiency of the solution at different input from 0.1 mA to 50 mA. The efficiency is approximately 83% at 3.6-V input voltage and 50-mA output current.

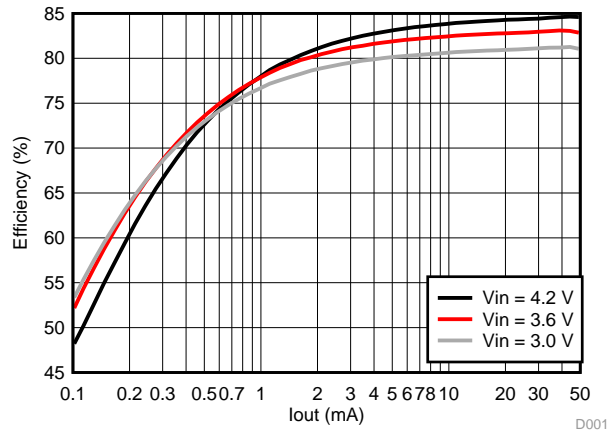

**Figure 9. Efficiency at Different Input Voltages**

#### 4 Summary

This application report introduces the behavior of TPS61372 at different load conditions. With this device, a small power boost converter solution is designed. Output ripple, start-up waveform, stability performance and efficiency are tested to verify the solution.

#### 5 References

- TI data sheet [TPS61372 16 V/3.6 A Sync Boost With Load Disconnect](#)
- TI application note [How to Select a Proper Inductor for Low Power Boost Converter](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2018, Texas Instruments Incorporated