Application Note **Power Delivery in Cordless Power Tools Using DRV8329**



Aaron Barrera

ABSTRACT

Cordless power tools require a small form factor and power stage to deliver up to hundreds of amps to the motor. High-performance tools, such as drills, require robust system performance powered from many types of high-quality and entry-level battery packs used across power tool platforms. To provide high torque, power tools require varying amounts of current which can deplete the battery voltage during stall conditions.

The DRV8329, a 3-phase BLDC gate driver, can help address these challenges through its hybrid bootstrap + trickle charge pump gate drive architecture to make it capable of providing at least 10V of gate-source voltage at low (~6V) supply voltages. In this application note, we will discuss how the DRV8329 meets application requirements for power tool platforms in various operating modes while also enabling system protection, consuming low quiescent current in sleep and standby modes, and maintaining a small form factor.



Figure 1-1. Various Types of Cordless Power Tools Including Drills, Saws, Cutters, Grinders, Rotary Hammers, and Impact Drivers

Table of Contents

1 DRV8329 Key Features	2
2 Power Tool Requirements	
2.1 Performance	
2.2 Robustness	
2.3 Scalability	4
3 Summary	

List of Figures

Figure 1-1. Various Types of Cordless Power Tools Including Drills, Saws, Cutters, Grinders, Rotary Hammers, and	
Impact Drivers	1
Figure 1-1. Simplified Schematic for DRV8329	<mark>2</mark>
Figure 2-1. High-Performance Cordless Power Drill	
Figure 2-2. Protections Implemented on the DRV8329AEVM Applicable for Power Tools	
Figure 2-3. Battery Packs With Varying Voltage and Quality for Power Tool Applications	5
Figure 2-4. DRV8329 GVDD Voltage Över PVDD Voltage	

Trademarks

All trademarks are the property of their respective owners.

1



1 DRV8329 Key Features

The DRV8329 is a bootstrap-based 3-phase Brushless-DC motor gate driver rated for 4.5V to 60V, and it is capable of driving 3 high-side and 3 low-side MOSFETs with up to 1-A peak source gate current and 2-A peak sink gate current. It uses a bootstrap-based architecture, which means 3 external bootstrap capacitors provide the voltage for the high-side gate driver outputs. In order to support up to 100% duty cycle, the DRV8329 includes a trickle charge pump in order to keep in the high-side MOSFETs fully on and deliver maximum motor current supported by the MOSFETs.

Furthermore, it uses a hardware interface for configuration and integrates a variety of features such as adjustable driver dead time and overcurrent threshold, an independent DRVOFF gate driver shutoff pin, current sense amplifier with low input offset and adjustable gain, a 3.3V 80-mA capable LDO, a 65-V tolerant sleep mode pin with <1uA sleep mode current, and multiple other protection features.

Available in a 36-pin, compact, 5x4mm QFN package, the DRV8329 is ideal for 2S to 10S power tool platforms with an absolute maximum rating of 65-V. This app brief showcases how the DRV8329 meets the most critical power tool requirements: performance, robustness, and scalability.

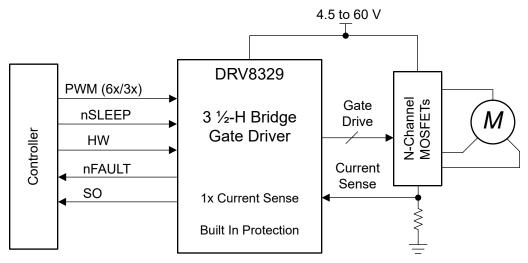


Figure 1-1. Simplified Schematic for DRV8329



2 Power Tool Requirements

2.1 Performance

Power tools should have sufficient performance from no load to maximum load conditions. For instance, an 18-V cordless power drill in a no-load condition may spin at high speeds (up to 2000 RPM) while torque remains minimal. At a maximum load condition, the power drill may spin at very slow speeds or stall while supplying high torque (up to 1200 lb-in). Regardless of the load conditions, the Brushless-DC motor needs to deliver the required power to the mechanical load by commutating the motor with a sufficient Brushless-DC gate driver and power stage.



Figure 2-1. High-Performance Cordless Power Drill

Because the Brushless-DC motor in a power tool can deliver kilowatts of power, the power stage is designed to deliver up to several hundred amps of current. This requires using N-type power MOSFETs that have large gate-to-drain charges (QGD), continuous drain current ratings (ID), and voltage overhead for motor transients (VDS). In order to drive six power MOSFETs or 12 parallel MOSFETs, the DRV8329 reliably supports at least 10-V of gate-to-source voltage across 2S to 10S operating range to fully saturate the MOSFETs with up to 1-A peak source and 2-A peak sink gate currents. Additionally, the DRV8329 provides 100% duty cycle support to efficiently switch motor current and deliver large amounts of power to the BLDC motor.

2.2 Robustness

In addition to delivering large amounts of torque, the system needs to be protected from unforeseen effects due to external load conditions, PCB parasitics, ambient temperatures, or materials such as dust. Problems that can occur during power tool operation include overcurrent conditions, motor undervoltage, supply undervoltage, or overtemperature. A well-designed PCB layout can combat many of the most frequently faced issues during evaluation, but a suitable BLDC gate driver should be prepared to disable the gate driver circuits quickly if a fault occurs. As tools continue to have high standards of quality and performance, it also is important that backup forms of protection exist, such as redundant device protection features and external circuits to shutoff the gate drivers or disconnect the supply.



The DRV8329 includes two forms of overcurrent protection to protect the power stage from short-circuit conditions: VDS (MOSFET drain-to-source voltage) and VSEN (sense resistor voltage) overcurrent protection. VDS overcurrent protection is set by an analog VDSLVL input voltage to control the overcurrent threshold across the high- and low-side MOSFETs, and VSEN overcurrent protection is a fixed 0.5 V threshold across the sense resistor from the low-side MOSFETs to the motor ground.

Additionally, the DRV8329 integrates an adjustable open-loop dead time to prevent against shoot-through conditions and reduce software-related complexities. To protect against undervoltage conditions, the DRV8329 implements supply, bootstrap, gate drive voltage, and LDO undervoltage lockouts so that there is sufficient voltage to power the gate driver and/or external circuits.

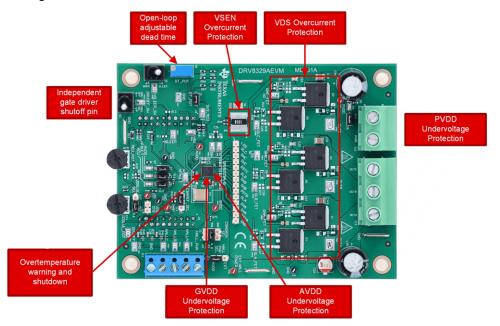


Figure 2-2. Protections Implemented on the DRV8329AEVM Applicable for Power Tools

2.3 Scalability

A high-power motor driver system should be designed for the maximum voltage and current provided from the lithium-ion battery pack. In power tool applications, a lithium ion battery can provide up to hundreds of amps of instantaneous current as a function of the battery pack impedance. It is common for power tool designers to optimize their design so it can scale across multiple different battery pack architectures with varying architectures of cells. Battery packs with cells in series affect the supply voltage, and battery packs with cells in parallel affect the battery pack capacity and effective impedance. A robust motor driver such as the DRV8329 assures suitable MOSFET gate drive voltages across all possible load and battery conditions.

2.3.1 Battery Pack Quality

Power tool batteries have varying series impedance due to the battery cells. High-grade batteries may have 1's of milliohms of series impedance, whereas entry-level battery packs may have up to 100's of milliohms of series impedance. Under heavy loads, the impedance introduced to the power tool system by the battery pack results in a voltage drop decreasing the available supply voltage to drive the motor. To scale across battery pack grades, the motor driver selected should have a low minimum operating range to provide sufficient gate drive voltages to fully saturate the MOSFETs.



2.3.2 Battery Pack Voltage

Power tool batteries can range from 4VDC to 60VDC. During operation, instantaneous changes in motor current can cause transients up to 2x the battery's nominal voltage rating. It is beneficial to select a motor driver than can support these transients while also providing a wide input voltage range so the driver and power stage design can be re-used across multiple platforms for simplicity and lowering BOM cost. For instance, a power tool platform can be scaled up to 24-V in well-designed systems for a motor driver with a 60-V absolute maximum rating.



Figure 2-3. Battery Packs With Varying Voltage and Quality for Power Tool Applications

The DRV8329 is an ideal Brushless-DC gate driver to scale across power tool platforms. With a wide recommended operating range of 4.5-V to 60-V, it can support 2S to 10S power tools with at least 10 volts of gate-to-source voltage to switch power MOSFETs during power tool operation. With low input supply voltages, the integrated charge pump in the DRV8329 automatically scales the supply voltage to a sufficient gate drive voltage to continue driving the FETs. An example application is when power tools apply high amounts of torque, which causes the motor to stall and supply voltages to drop down due to stall current conducting through the battery impedance. This is ideal for low-cost power tool applications that use Tier 2 battery suppliers, operate a low voltage ranges, have smaller supply bulk capacitance, or require smaller form factors.

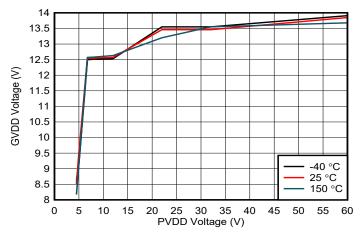


Figure 2-4. DRV8329 GVDD Voltage Over PVDD Voltage

3 Summary

The DRV8329 three-phase Brushless-DC gate driver addresses a wide variety of system requirements for power tool applications while delivering robust performance across a range of supply voltages and providing scalability for a variety of power tool and battery pack platforms. As a low-cost gate driver with small form factor, the DRV8329 is a versatile solution for not just cordless power tools but also many high power Brushless-DC motor driver applications such as ESCs and electric bikes. The power tool market continues to expand and become



more competitive as consumers are scaling battery and driver solutions to lower system cost while providing exceptional Brushless-DC power delivery.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2022, Texas Instruments Incorporated